



Faculty of Engineering and Technology
Department of Electrical and Computer Engineering
DIGITAL INTEGRATED CIRCUITS

Homework - 3

Prepared by:
Nour Naji– 1190270


Supervised by: Dr. Khader Mohammad
Section: 3

Date: 8/6/2022


Layout design of a CMOS Circuits

Part 1:



- NAND gate in PSpise

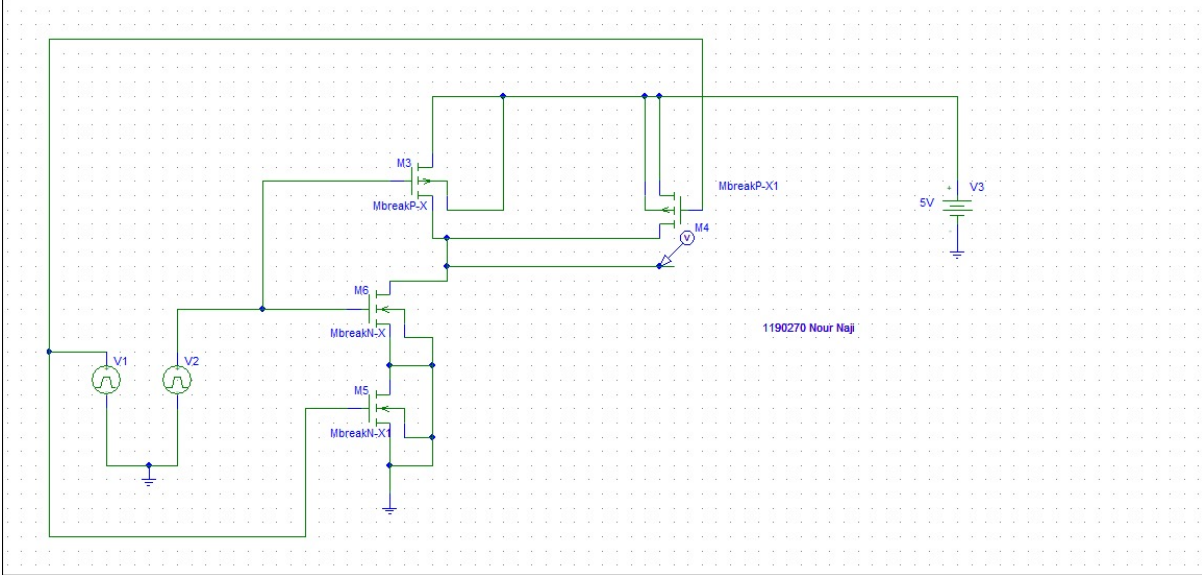


→ Simulation:

 

▪ **NAND gate and Layout:**

  

 



A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

Part 2:


Two Bit Full Adders are the Logical Circuits that have two inputs for the input bits and one for the carry and as a result, Sum of the bits along with the carry are obtained at sum and carry Terminals respectively.

Let us consider first one-bit full-adder adds three one-bit numbers, often written as A, B, and Cin; A and B are the operands, and Cin is a bit carried in from the previous less-significant stage.

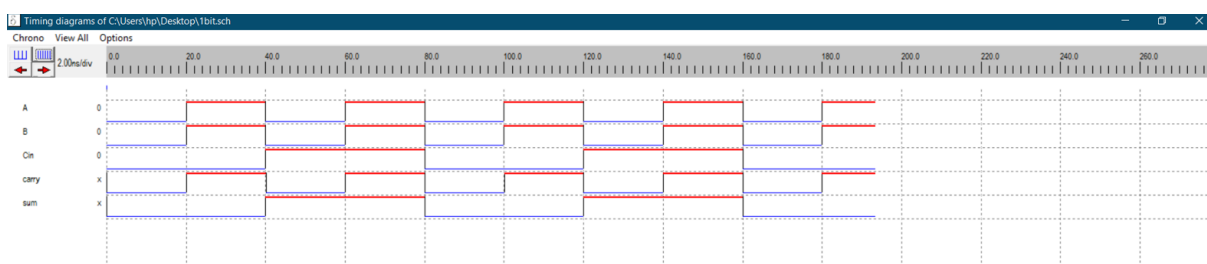 - $0+0+0 = 0$, 0 carry output
- $0+1+0 = 1$, 0 carry output
- $1+0+0 = 1$, 0 carry output
- $1+1+0 = 0$, 1 carry output
- $0+0+1 = 1$, 0 carry output
- $0+1+1 = 0$, 1 carry output
- $1+0+1 = 0$, 1 carry output
- $1+1+1 = 1$, 1 carry output



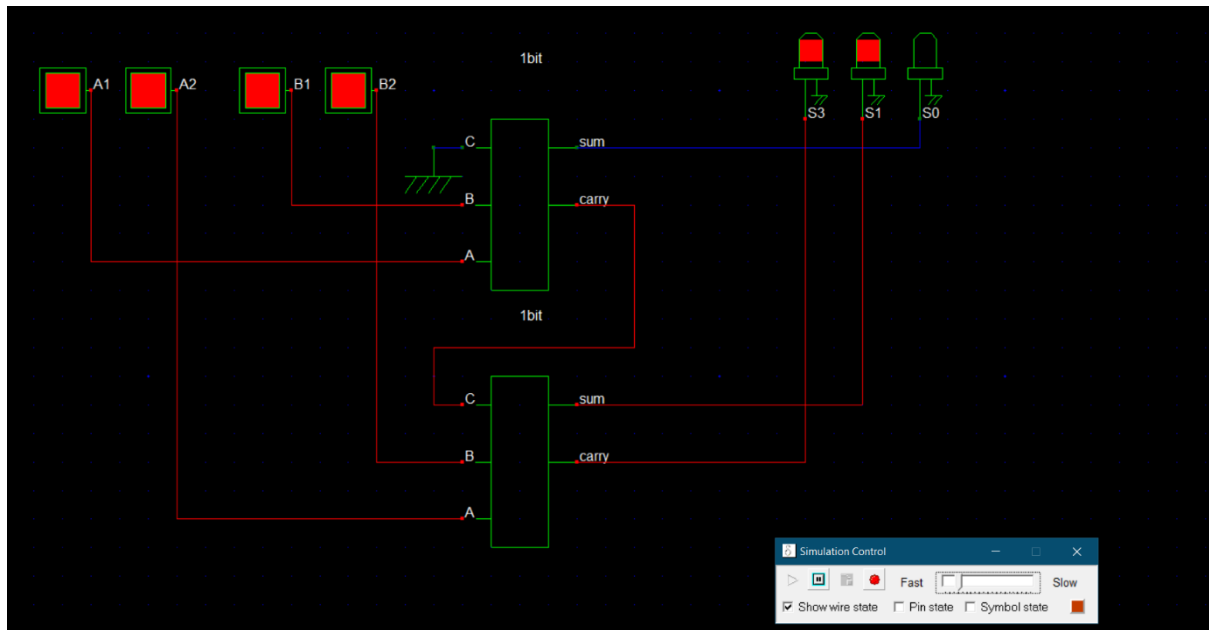If you cascade 2 binary full adder blocks you will get a 2-bit full adder. The general block diagram is as below.



the truth table :

A0	B0	A1	B1	S3	S1	S0
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	0	0	1
0	0	1	1	0	1	1
0	1	0	0	0	1	0
0	1	0	1	1	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	0
1	1	0	0	0	1	1
1	1	0	1	1	0	1
1	1	1	0	1	0	0
1	1	1	1	1	1	0

```
;module example( B2,A2,A1,B1,S0,S1,S3)
;input B2,A2,A1,B1
;output S0,S1,S3
;wire w4,w10,w11,w12,w13,w14,w15
;xor xor2_1_1(w10,A1,B1)
;xor xor2_2_2(S0,w10,vss)
;and and2_3_3(w11,w10,vss)
;and and2_4_4(w12,A1,B1)
;or or2_5_5(w4,w11,w12)
;xor xor2_1_6(w13,A2,B2)
;xor xor2_2_7(S1,w13,w4)
;and and2_3_8(w14,w13,w4)
;and and2_4_9(w15,A2,B2)
;or or2_5_10(S3,w14,w15)
endmodule
```



Simulation parameters in Verilog Format //

```
always
;B2=~B2 #200
;A2=~A2 #400
;A1=~A1 #800
;B1=~B1 #1600
```

Simulation parameters //

```
B2 CLK 1 1 //
A2 CLK 2 2 //
A1 CLK 4 4 //
B1 CLK 8 8 //
: Layout
```

: Layout

 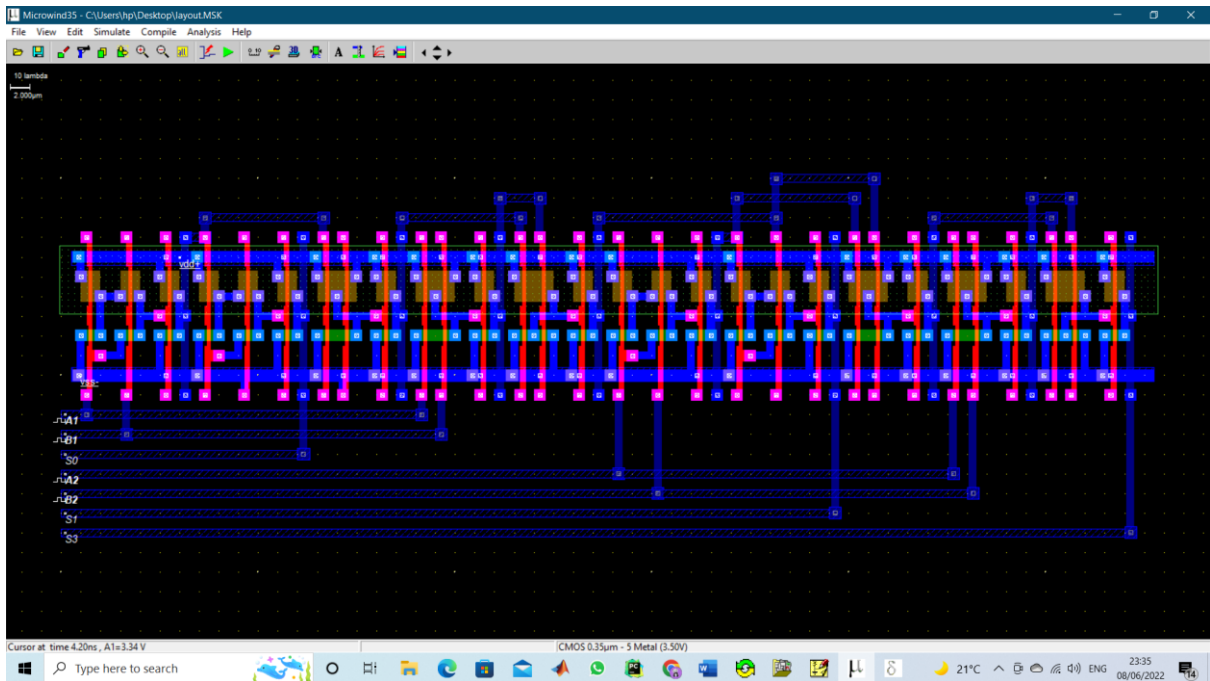

✓ We note that the results are identical to the Truth table