



Faculty of Engineering and Technology

Electrical and Computer Engineering Department

Digital Integrated Circuit

ENCS333

Quiz No. 3

- **Prepared by:** Ayham Hashesh 1161301

- **Instructor:** Dr. Khader Mohammad

- **Section No.:** 1

- **Date:** 28-4-2020

1. List three advantage of domino design (Dynamic Logic)?

- ✓ Full swing outputs ($V_{OL} = GND$ and $V_{OH} = V_{DD}$).
- ✓ Non-ratioed sizing of the devices does not affect the logic levels.
- ✓ Faster switching speed.


2. What are the issues of domino design (Dynamic Logic)?

- ✓ Overall power dissipation usually higher than static CMOS.
- ✓ Pull down network starts to work as soon as the input signals exceeds V_{TN} , so V_M , V_{IH} and V_{IL} equal to V_{TN} . (Low noise margin)
- ✓ Needs a precharge/evaluate clock.

3. List three CMOS Logic advantage?


- ✓ Full rail-to-rail swing: **High Noise Margin**.
- ✓ No direct path steady state between power and ground: **No static power dissipation**.
- ✓ Always a path to V_{DD} or Ground in steady state: **Low output impedance**.

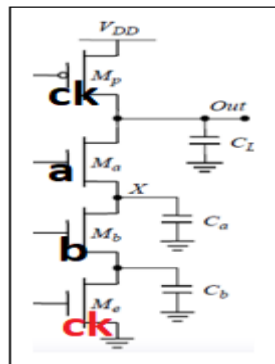4. Define Charge Sharing? Do we have charge sharing problem in the attached figure? if yes how do we solve it



- ✓ Charge sharing: Charge stored originally in C_L is redistributed (shared) over C_L and other capacitors leading to reduce robustness.
- ✓ Yes we have charge sharing problem.
- ✓ To solve: Precharge internal nodes using a clock driven transistor (at the cost of increased area and power).

 5. What is the function of the attached layout? Is this an optimal design? Explain



- ✓ Nand Gate.
- ✓ No, It's not the optimal design as there exists many capacitance which can be reduced if we shred the diffusion