



DEPARTMENT OF COMPUTER SYSTEM ENGINEERING

Digital Integrated Circuits - ENCS333

Dr. Khader Mohammad

Lecture #4

Introduction

The CMOS inverter

Digital Integrated Circuits

Course topics and Schedule	
	Subject
1	Introduction to Digital Integrated Circuits Design
2	Semiconductor material: pn-junction, NMOS, PMOS
3	IC Manufacturing and Design Metrics CMOS
4	Transistor Devices and Logic Design The CMOS inverter
5	Combinational logic structures
6	Sequential logic gates; Latches and Flip-Flops
7	Layout of an Inverter and basic gates
8	Parasitic Capacitance Estimation
9	Device modeling parameterization from I-V curves.
	Short Test
10	Arithmetic building blocks
11	Interconnect: R, L and C - Wire modeling
12	Timing Power dissipation;
13	SPICE Simulation Techniques (Project)
14	Memories and array structures
	Midterm
15	Clock Distribution
16	Supply and Threshold Voltage Scaling
17	Reliability and IC qualification process
18	Advanced Voltage Scaling Techniques
19	Power Reduction Through Switching Activity Reduction
20	CAD tools and algorithms
21	Final & Project discussion


Abstraction Level

Structural Verilog:

```
wire s;  
wire sbar;  
NOT not1(s, sbar);
```

Behavioral Verilog:

```
wire s, sbar;  
sbar = ~s;
```

 

Architecture SPEC

RTL

Schematics

Physical Design (Layout)

Silicon


High



Abstraction Level




Low

 

NMOS

PMOS

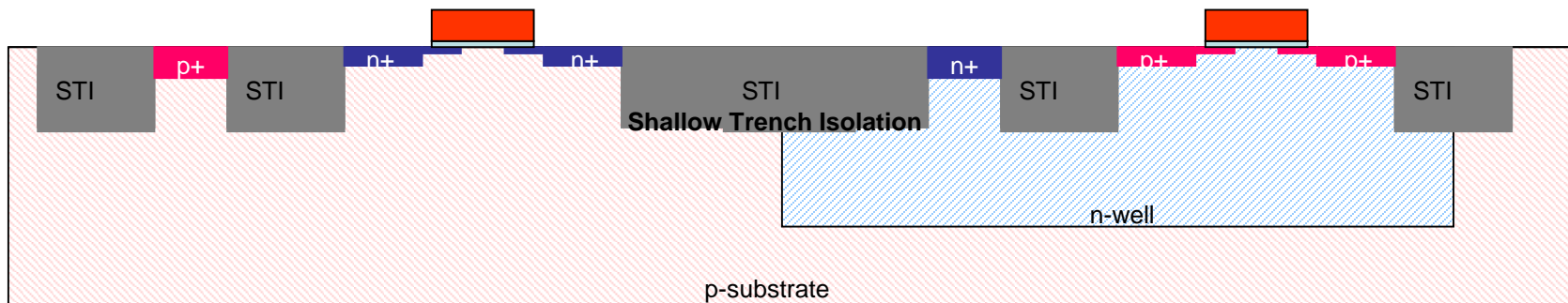


DIGITAL GATES


Fundamental Parameters

- Functionality
- Reliability, Robustness
- Area
- Performance
 - Speed (delay)
 - Power Consumption
 - Energy

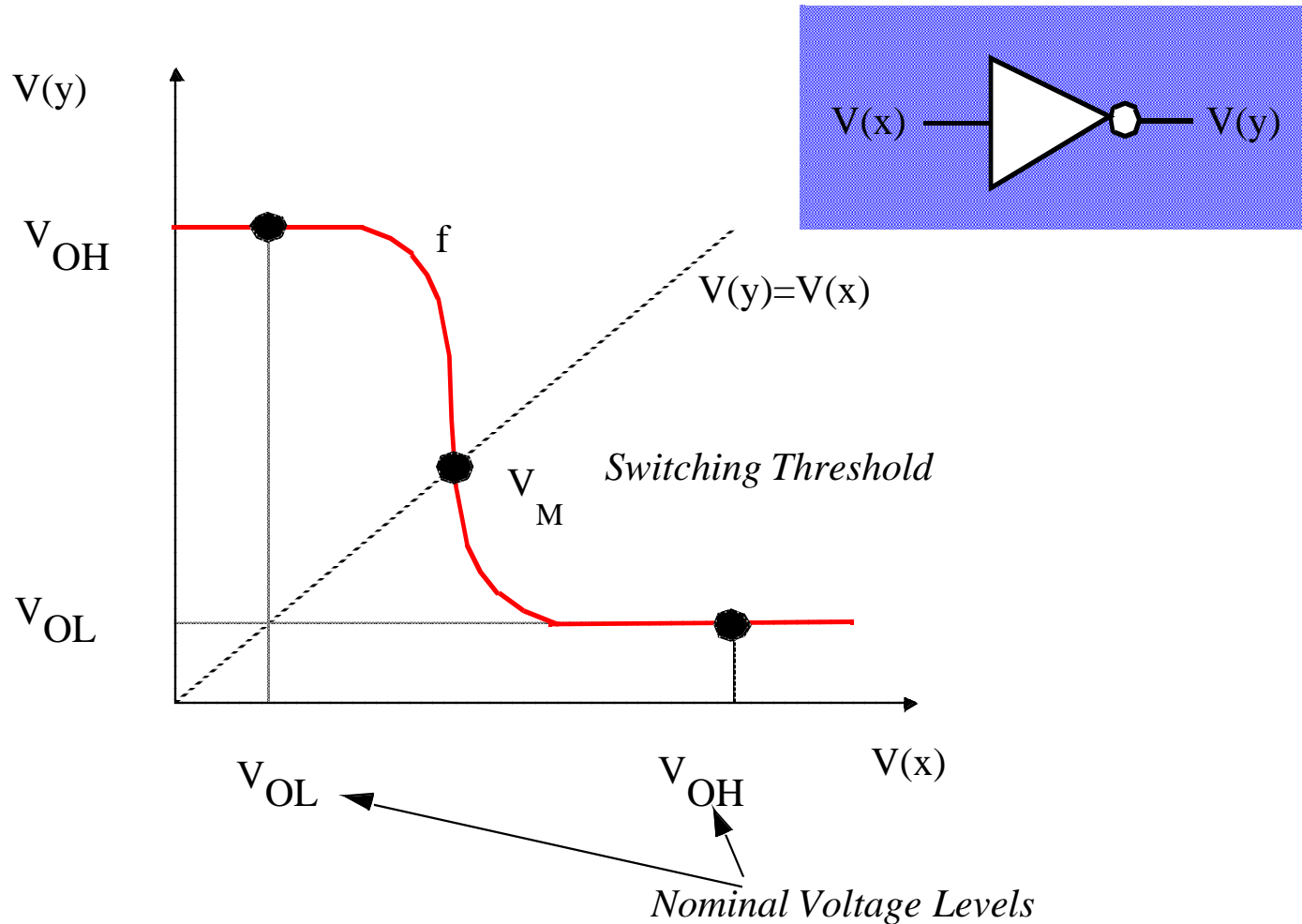
DC Operation: Voltage Transfer Characteristic




The CMOS Inverter: A First Glance

 

The CMOS Inverter

 

CMOS Inverter VTC

 


- **Cut-off** : $I_{ds} = 0$ (for now)
when $V_{gs} < V_T$
- **Linear** : $I_{ds} = \beta([V_{gs} - V_T] V_{ds} - \frac{V_{ds}^2}{2})$
when $0 < V_{ds} < V_{gs} - V_T$
- **Saturation** : $I_{ds} = \frac{\beta}{2}(V_{gs} - V_T)^2$ (for now)
when $0 < V_{gs} - V_T < V_{ds}$
This is obtained by using $V_{ds} = V_{gs} - V_T$ in the equation for linear I_{ds} (see comment two pages prior to this one)


- **Cut-off** : $V_{gs} < V_T$
- **Linear** : $0 < V_{ds} < V_{gs} - V_T$
- **Saturation** : $0 < V_{gs} - V_T < V_{ds}$

- Where $\beta = \frac{\mu\epsilon}{t_{ox}}(\frac{W}{L})$


Switch Model of CMOS Transistor

 


CMOS Inverter: Steady State Response

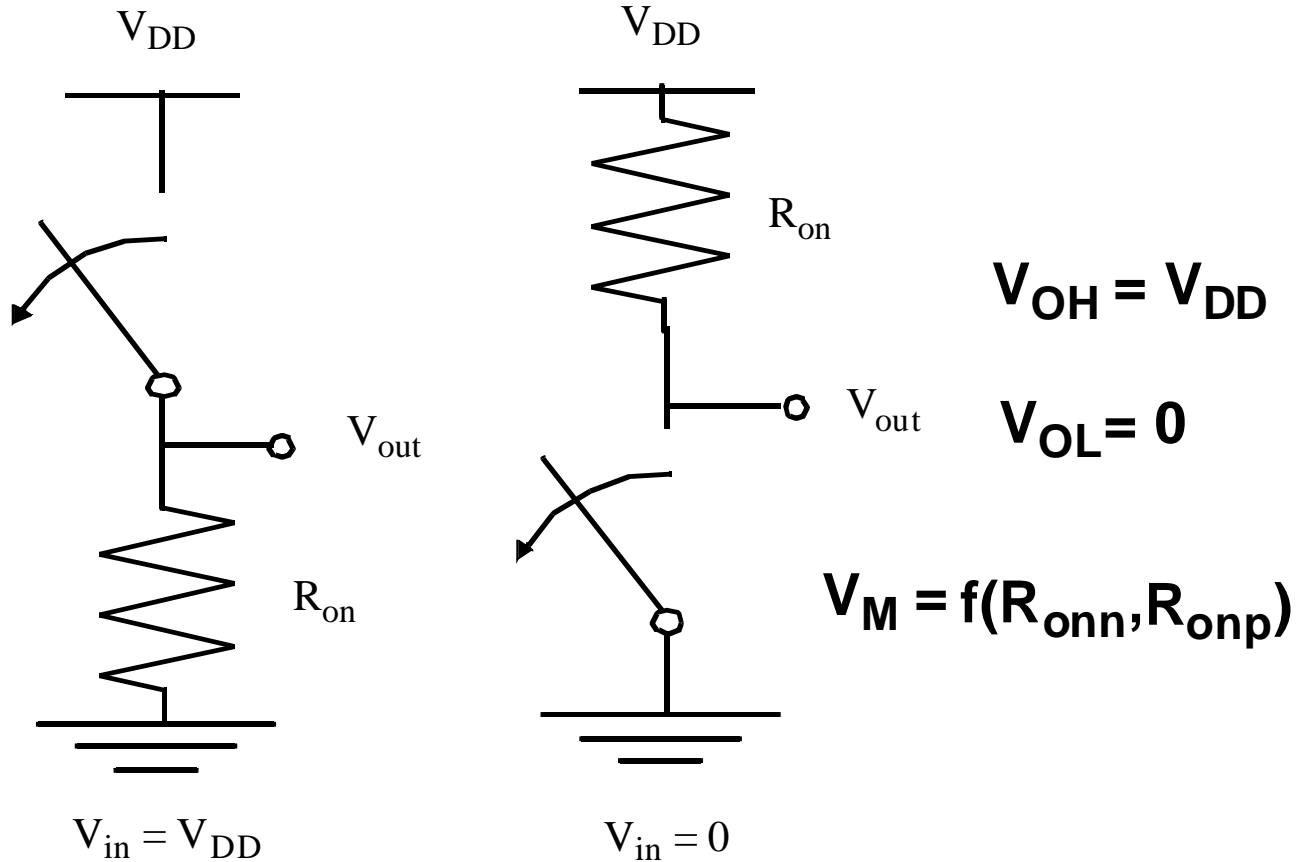


CMOS Inverter: Transient Response

 
 
$$t_{pHL} = f(R_{on} \cdot C_L)$$
$$= 0.69 R_{on} C_L$$




 Switching Threshold as a Function of Transistor Ratio




$$I_{dn}(V_M) = I_{dp}(V_M)$$

Impact of Sizing

 

DC inverter Characteristics

 

Region	Condition	PMOS	NMOS	V_{out}
A	$0 \leq V_{in} \leq V_{T_N}$	linear	cutoff	V_{DD}
B	$V_{T_N} \leq V_{in} \leq V_{DD}/2$	linear	sat	see below
C	$V_{in} = V_{DD}/2$	sat	sat	$V_{out} \neq f(V_{in})$
D	$V_{DD}/2 \leq V_{in} \leq V_{DD} - V_{T_p} $	sat	linear	see below
E	$V_{in} \geq V_{DD} - V_{T_p} $	cutoff	linear	0

- NMOS is easy to see, but how do we determine PMOS device state? For this, assume an inverter with $V_{DD} = 5V$, $V_{T_N} = -V_{T_P} = 1V$.


Regions A, B, C, D and E based on state of P and N devices

V_{in}	$V_{gs_p} - V_{T_p}$	Relation	V_{ds_p}	Device state
0	$-5 + 1$	$<$	0	linear
1	$-4 + 1$	$<$	~ -1	linear
2.5	$-2.5 + 1$	$>$	~ -2.5	saturation
4	$-1 + 1$	$>$	~ -4	saturation
5	$0 + 1 \geq 0$	-	-	cutoff

DC characteristics, so no capacitors involved. We will talk about capacitors when we consider AC characteristics.

MOS Transistor as a Switch


- Discharging a capacitor

 

$$i_D = i_D(v_{DS})$$

$$i_D = C \frac{dV_{DS}}{dt}$$

- We modeled this with:

 



$$t_p = \ln(2) RC$$

MOS Transistor as a Switch

- Real transistors aren't exactly resistors
 - Look more like current sources in saturation
- Two questions:
 - Which region of IV curve determines delay?
 - How can that match up with the RC model?

Transistor Discharging a Capacitor



- With a step input:

  

Transistor is in (velocity) saturation during entire transition from V_{DD} to $V_{DD}/2$

Switching Delay

  
- In saturation, transistor basically acts like a current source



$$V_{OUT} = V_{DD} - (I_{DSAT}/C)t \longrightarrow t_p = C(V_{DD}/2)/I_{DSAT}$$

Switching Delay (with Output Conductance)

- Including output conductance:

 


$$V_{OUT} = (V_{DD} + \lambda^{-1}) e^{-t/(C/\lambda I_{DSAT})} - \lambda^{-1}$$

- For “small” λ :

$$t_p \approx \frac{C(V_{DD}/2)}{(1 + \lambda V_{DD}) I_{DSAT}}$$

The Transistor as a Switch


 


The Transistor as a Switch


Table 3.3 Equivalent resistance R_{eq} ($W/L=1$) of NMOS and PMOS transistors in 0.25 μm CMOS process (with $L=L_{min}$). For larger devices, divide R_{eq} by W/L .

V_{DD} (V)	1	1.5	2	2.5
NMOS ($\text{k}\Omega$)	35	19	15	13
PMOS ($\text{k}\Omega$)	115	55	38	31

  Mapping between analog and digital signals







Definition of Noise Margins

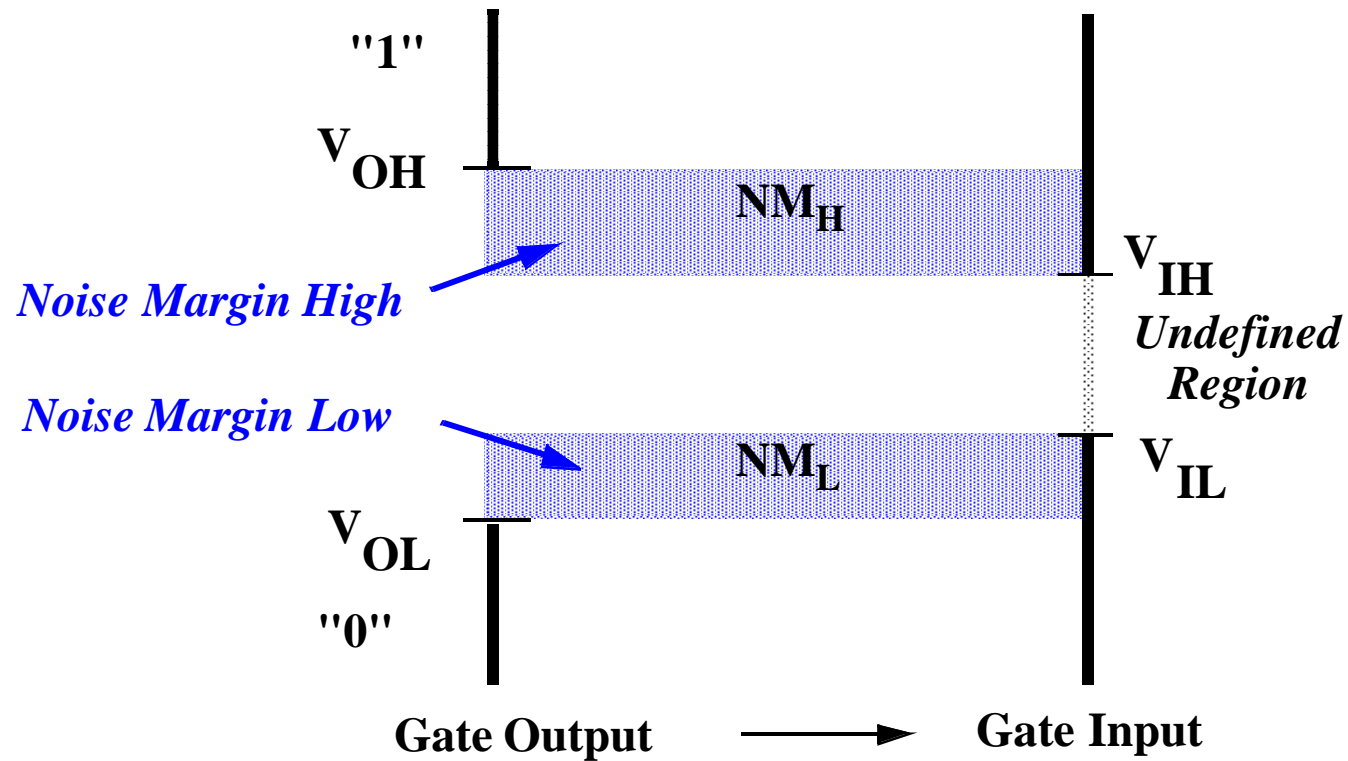


Noise Margin

- NM_H and NM_L are the high-side and low-side noise margins.
- The high output excursion should **not** be larger than the high input excursion. Same for the low excursions. If this is violated, then the corresponding noise margin is negative.
- Why worry about it? Perhaps the V_{DD} or GND of the driver glitches relative to the driven gate. In that situation, I want to know what magnitude of glitch can I tolerate before a wrong value is interpreted.

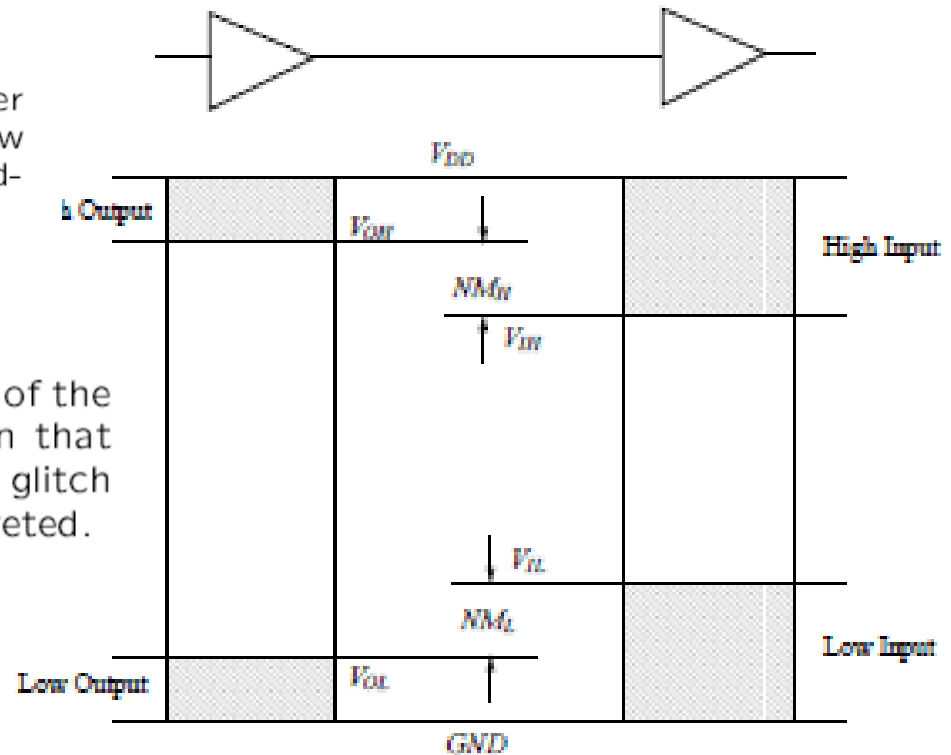


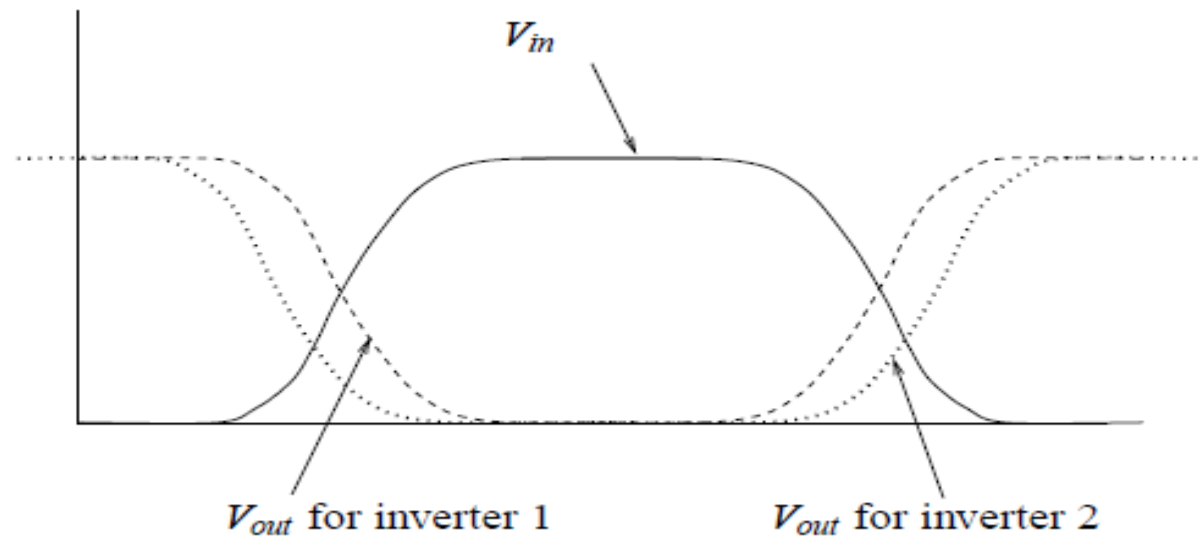
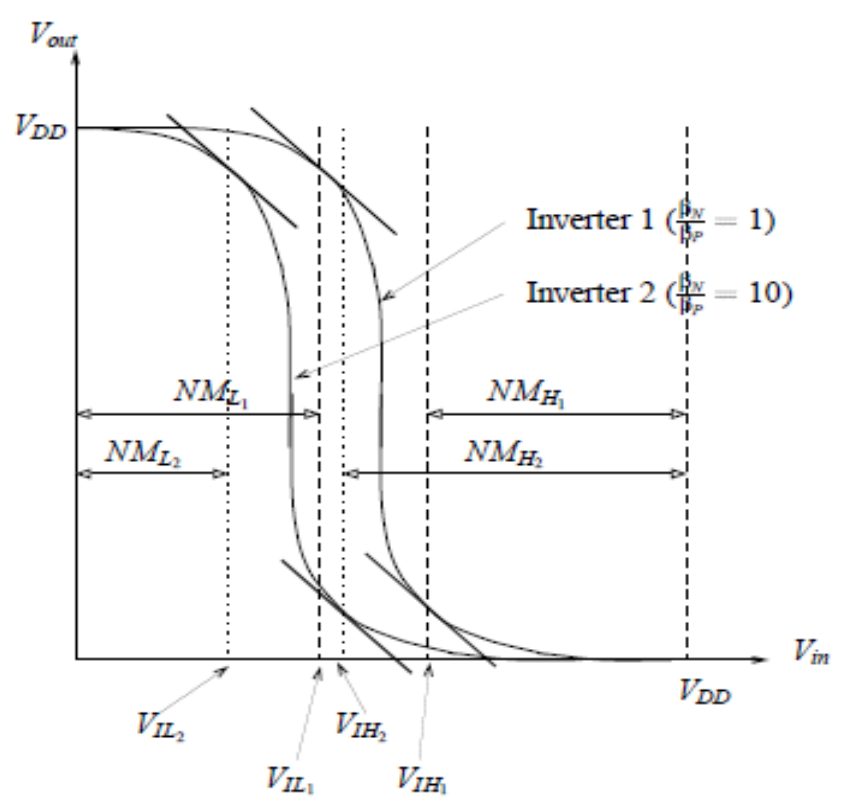
 


The Ideal Gate

 


$$R_i = \infty$$


$$R_o = 0$$

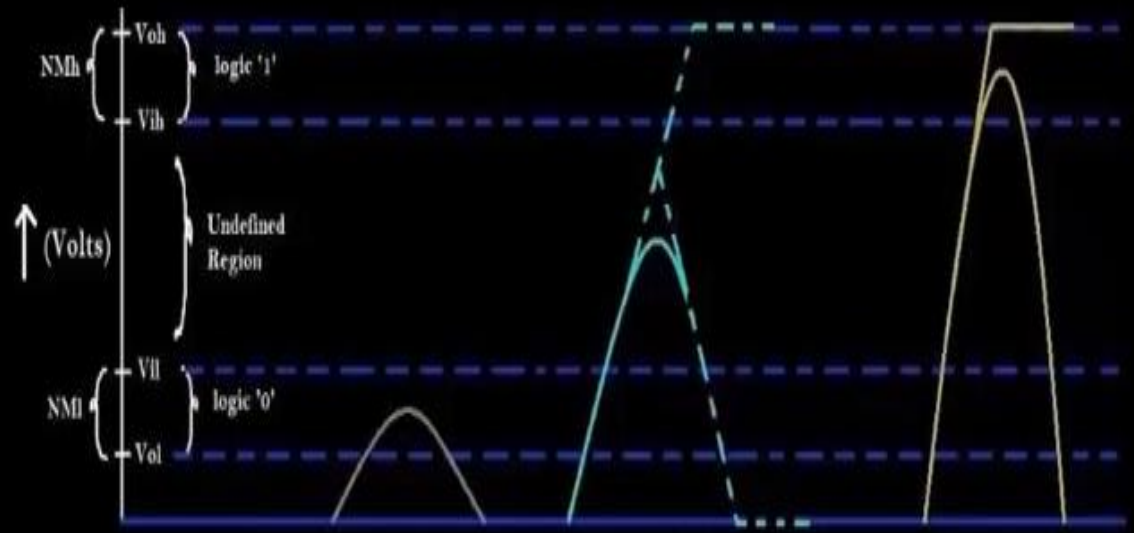   


The Regenerative Property

 

(a) A chain of inverters.


 


(b) Regenerative gate

 


(c) Non-regenerative gate


Fan-in and Fan-out

  



VTC of Real Inverter

 

Delay Definitions

 

Ring Oscillator

  

$$T = 2 \times t_p \times N$$

Power Dissipation

$$P_{peak} = i_{peak} V_{supply} = \max(p(t))$$

$$P_{av} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_{supply}}{T} \int_0^T i_{supply}(t) dt$$

Power-Delay Product

$$PDP = t_p \times P_{av}$$


= Energy dissipated per operation



CMOS Properties

- Full rail-to-rail swing
- Symmetrical VTC
- Propagation delay function of load capacitance and resistance of transistors
- No static power dissipation
- Direct path current during switching


Voltage Transfer Characteristic

CMOS Inverter Load Characteristics

 


  

Simulated VTC

 

Gate Switching Threshold

 

$$V_M = \frac{r(V_{DD} - |V_{Tp}|) + V_{Tn}}{1 + r} \quad \text{with} \quad r = \sqrt{\frac{k_p}{k_n}}$$

CMOS Inverter VTC

- In linear region :

- Channel resistance = $R_{c_{lin}} =$

$$\lim_{V_{ds} \rightarrow 0} \left(\frac{dI_{ds}}{dV_{ds}} \right)^{-1}$$

$$= \frac{1}{\beta(V_{gs} - V_T)}$$


- Depends on V_{gs}

- Transconductance = $g_m = \left(\frac{dI_{ds}}{dV_{gs}} \right) = \beta V_{ds}$


- Higher current gain with higher V_{ds}

- In saturation region :

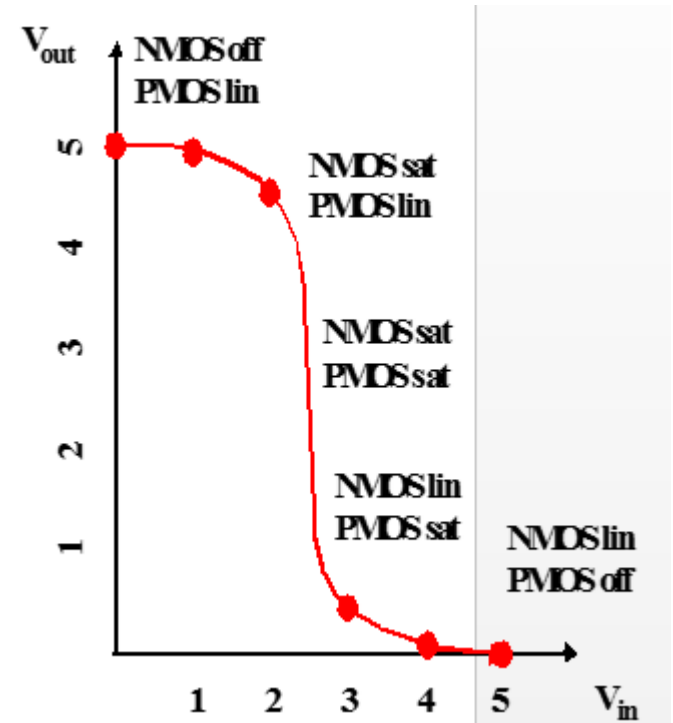- Transconductance = $g_m = \left(\frac{dI_{ds}}{dV_{gs}} \right) = \beta(V_{gs} - V_T)$



MOS Transistor Small Signal Model

 


	g_m	r_o
linear	kV_{DS}	$[k(V_{GS}-V_T-V_{DS})]^{-1}$
saturation	$k(V_{GS}-V_T)$	$1/N_D$

Determining V_{IH} and V_{IL}

At V_{IH} (V_{IL}): $\frac{\partial V_{out}}{\partial V_{in}} = -1$


small-signal model of inverter

 


$$g = \frac{v_{out}}{v_{in}} = -(g_{mn} + g_{mp}) \times (r_{on} \parallel r_{op}) = -1$$

Propagation Delay


CMOS Inverter: Transient Response

 
 
$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$




CMOS Inverter Propagation Delay

 

$$t_{pHL} = \frac{C_L V_{swing}/2}{I_{av}}$$


$$\sim \frac{C_L}{k_n V_{DD}}$$

Computing the Capacitances

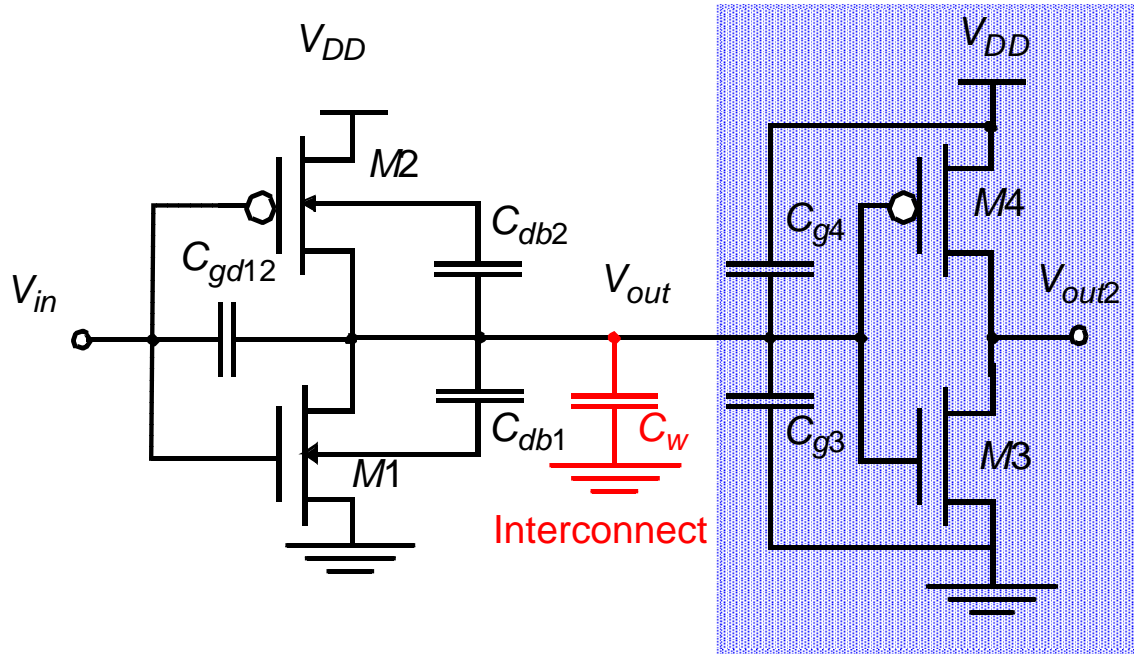


Fanout

Simplified Model

 


Capacitor	Expression
C_{gd1}	$2 \text{ CGD0 } W_n$
C_{gd2}	$2 \text{ CGD0 } W_p$
C_{db1}	$K_{eqn} (AD_n \text{ CJ} + PD_n \text{ CJSW})$
C_{db2}	$K_{eqp} (AD_p \text{ CJ} + PD_p \text{ CJSW})$
C_{g3}	$C_{ox} W_n L_n$
C_{g4}	$C_{ox} W_p L_p$
C_w	From Extraction
C_L	Σ

CMOS Inverters

 


The Miller Effect

 


“A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.”

Impact of Rise Time on Delay

 

$$t_{pHL} = \sqrt{t_{pHL(step)}^2 + (t_r / 2)^2}$$

Delay as a function of V_{DD}

 

Where Does Power Go in CMOS?

- **Dynamic Power Consumption**

Charging and Discharging Capacitors


- **Short Circuit Currents**

Short Circuit Path between Supply Rails during Switching

- **Leakage**

Leaking diodes and transistors

Dynamic Power Dissipation

 

$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

- Not a function of transistor sizes!
- Need to reduce C_L , V_{dd} , and f to reduce power.

Power Dissipation

- Energy from power supply needed to charge up the capacitor:

$$E_{charge} = \int V_{DD} i(t) dt = V_{DD} Q = V_{DD}^2 C_L$$

- Energy stored in capacitor:

$$E_{store} = 1/2 C_L V_{DD}^2$$

- Energy lost in p-channel MOSFET during charging:

$$E_{diss} = E_{charge} - E_{store} = 1/2 C_L V_{DD}^2$$

- During discharge the n-channel MOSFET dissipates an identical amount of energy. • If the charge/discharge cycle is repeated f times/second, where f is the clock frequency, the dynamic power dissipation is:

$$P = 2E_{diss} * f = C_L V_{DD}^2 f$$


In practice many gates do not change state every clock cycle which lowers the power dissipation.

Impact of Technology Scaling

Technology Evolution


Year of Introduction	1994	1997	2000	2003	2006	2009
Channel length (μm)	0.4	0.3	0.25	0.18	0.13	0.1
Gate oxide (nm)	12	7	6	4.5	4	4
V_{DD} (V)	3.3	2.2	2.2	1.5	1.5	1.5
V_T (V)	0.7	0.7	0.7	0.6	0.6	0.6
NMOS I_{Dsat} (mA/ μm) (@ $V_{GS} = V_{DD}$)	0.35	0.27	0.31	0.21	0.29	0.33
PMOS I_{Dsat} (mA/ μm) (@ $V_{GS} = V_{DD}$)	0.16	0.11	0.14	0.09	0.13	0.16

Technology Scaling (1)

 


Minimum Feature Size

Technology Scaling (2)

 

Number of components per chip

Propagation Delay Scaling

 

Technology Scaling Models

- **Full Scaling (Constant Electrical Field)**

ideal model — dimensions and voltage scale together by the same factor S


- **Fixed Voltage Scaling**

most common model until recently —
only dimensions scale, voltages remain constant


- **General Scaling**

most realistic for today's situation —
voltages and dimensions scale with different factors


Delay as a function of VDD

 

Device Sizing

 

NMOS/PMOS ratio

 



$$\beta = W_p/W_n$$

Inverter Chain/Sizing

If C_L is given: - How many stages are needed to minimize the delay?
How to size the inverters?

May need some additional constraints.

  - Minimum length devices, $L=0.25\mu\text{m}$
- Assume that for $W_P = 2W_N = 2W$
- same pull-up and pull-down currents
- approx. equal resistances $R_N = R_P$
- approx. equal rise t_{pLH} and fall t_{pHL} delays
- Analyze as an RC network



$$R_P = R_{unit} \left(\frac{W_P}{W_{unit}} \right)^{-1} \approx R_{unit} \left(\frac{W_N}{W_{unit}} \right)^{-1} = R_N = R_W$$

$$\text{Delay (D): } t_{pHL} = (\ln 2) R_N C_L \quad t_{pLH} = (\ln 2) R_P C_L$$

Load for the next stage:
$$C_{gin} = 3 \frac{W}{W_{unit}} C_{unit}$$



Inverter Chain/Sizing

$$t_p = k R_W C_L$$

k is a constant, equal to 0.69



Assumptions: no load -> zero delay

$$W_{unit} = 1$$

  

$$\begin{aligned} \text{Delay} &= kR_W(C_{int} + C_L) = kR_W C_{int} + kR_W C_L = kR_W C_{int}(1 + C_L / C_{int}) \\ &= \text{Delay (Internal)} + \text{Delay (Load)} \end{aligned}$$
  
$$\text{Delay} \sim R_W (C_{int} + C_L)$$



$$t_p = kR_W C_{int} (1 + C_L / C_{int}) = t_{p0} (1 + f / g)$$

nFET vs. pFET

$$R_n = \frac{1}{\beta_n (V_{DD} - V_{Tn})} \quad \beta_n = \mu_n C_{ox} \left(\frac{W}{L} \right)_n$$

$$R_p = \frac{1}{\beta_p (V_{DD} - |V_{Tp}|)} \quad \beta_p = \mu_p C_{ox} \left(\frac{W}{L} \right)_p$$

$$\frac{\mu_n}{\mu_p} = r \quad \text{Typically} \\ (2 \dots 3)$$


(μ is the carrier mobility through device)

(We will return to this later ...)


See notes for sizing

Layout of an inverter to help identify the layers

Nwell – dashed brown outline

 


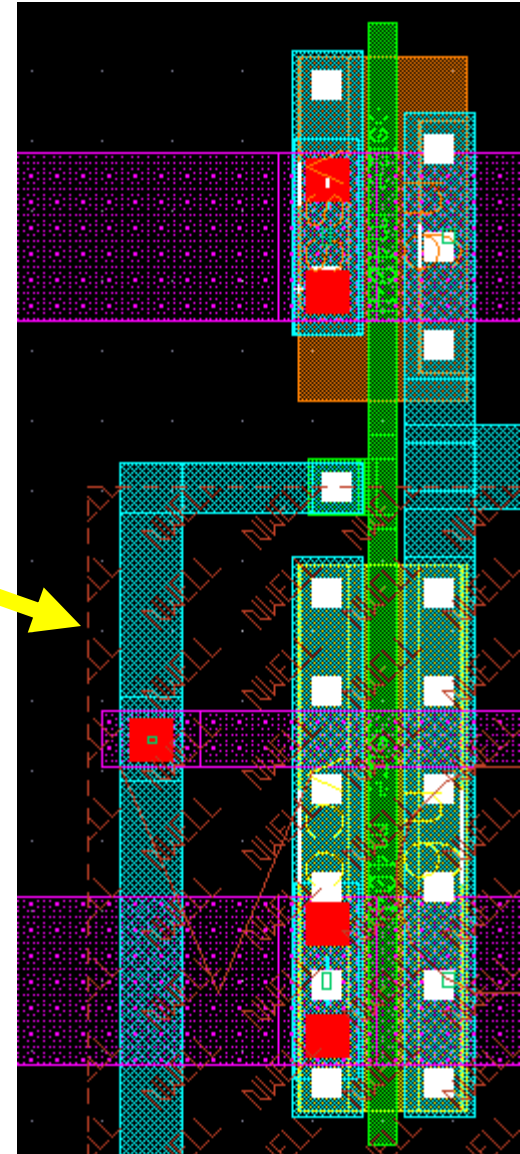Note, nwell not fully shown.
What is also not shown?



Layout of an inverter to help identify the layers

Well tap and substrate taps not shown

 


Layout of an inverter to help identify the layers

N diffusion – brown




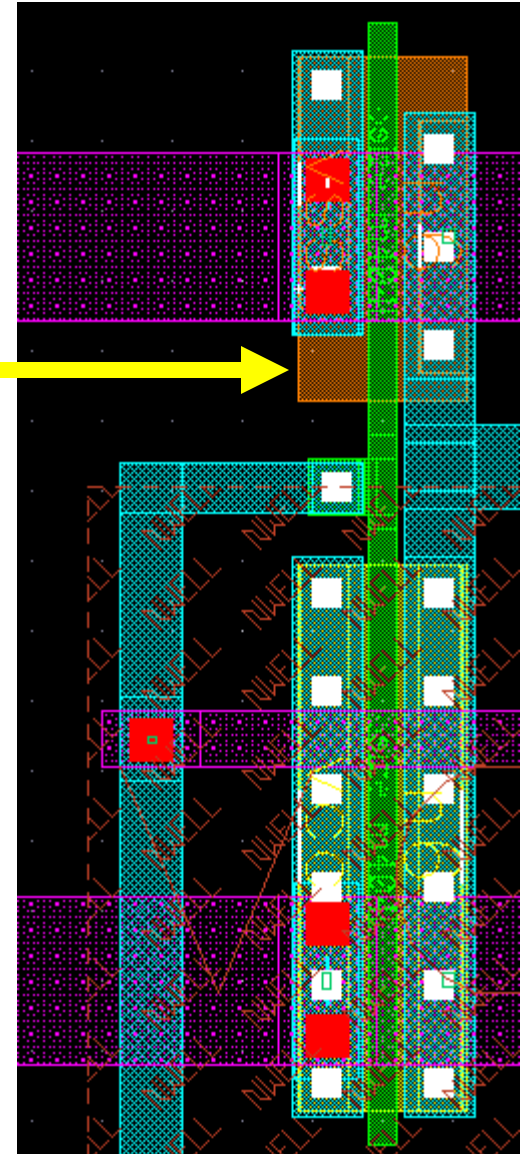
Sits in the p substrate. Not shown is the substrate tap



Layout of an inverter to help identify the layers

P diffusion – yellow

Sits in the nwell

  


Layout of an inverter to help identify the layers

poly – green




 Transistor occurs wherever there is poly over diffusion.
In this case we have 2 transistors:
1 NMOS and 1 PMOS



Layout of an inverter to help identify the layers

 
NMOS in yellow circle
PMOS in white circle



Layout of an inverter to help identify the layers

Contacts

 
Contact are used to connect both diffusion to M1 (yellow lines) and poly to M1 (purple lines)



Layout of an inverter to help identify the layers

M1 – first real routing layer

 
M1 is used here to connect VCC, VSS and the output and to route the input to the poly



Layout of an inverter to help identify the layers


Via 1 connects
M1 to M2

 In this case the output of the
Inverter does not go to M2




Layout of an inverter to help identify the layers



M2 routes
horizontally

 

CMOS Inverters \rightarrow buffer

 

Latchup in CMOS

 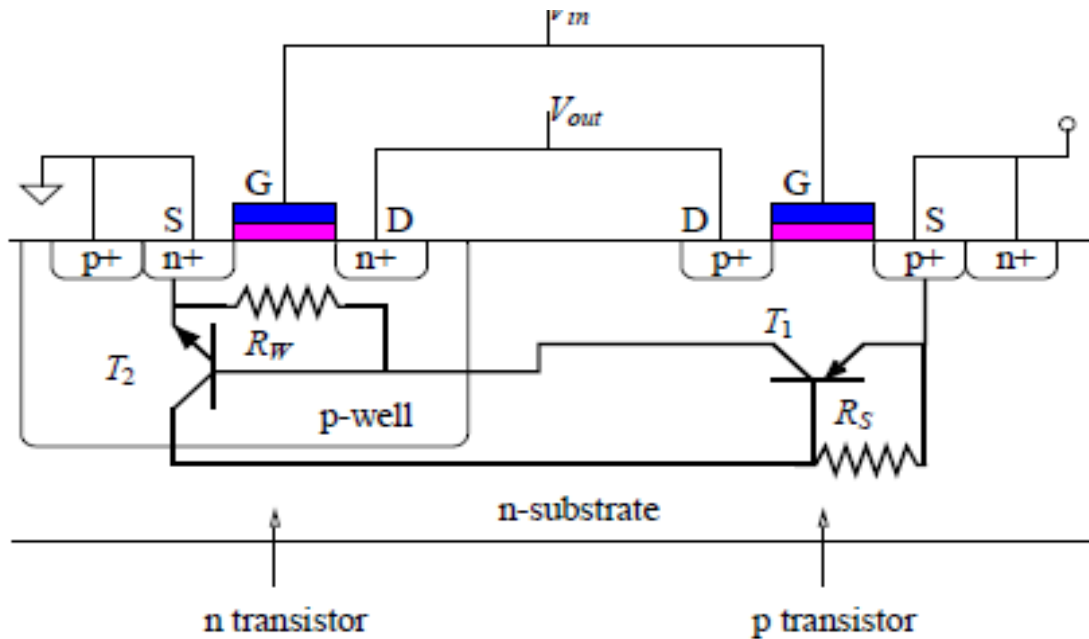

- There exist parasitic bipolar transistors (PNP and NPN) in a CMOS structure.
- Additionally the well and substrate have resistances R_W and R_S respectively.

- Latchup behavior slowed the introduction of CMOS
- Avoiding latchup is done by keeping R_W and R_S low.
 - This is done by **substrate contacts**.
 - When there is a substrate contact, current preferentially flows into the substrate contact, instead of the p-well or n-substrate.
 - Effectively, then, R_S is in parallel with a very small resistance to the PMOS substrate contact, and therefore R_S does not carry enough current to forward bias the base-emitter junction.