



DEPARTMENT OF COMPUTER SYSTEM ENGINEERING

Digital Integrated Circuits - ENCS333

Dr. Khader Mohammad
Lecture #9

Sequential logic gates; Latches and Flip-Flops

Digital Integrated Circuits

Course topics and Schedule	
Subject	
1	Introduction to Digital Integrated Circuits Design
2	Semiconductor material: pn-junction, NMOS, PMOS
3	IC Manufacturing and Design Metrics CMOS
4	Transistor Devices and Logic Design The CMOS inverter
5	Combinational logic structures
6	Layout of an Inverter and basic gates
7	Static CMOS Logic
8	Dynamic Logic
9	Sequential logic gates; Latches and Flip-Flops
	Arithmetic building blocks
	Parasitic Capacitance Estimation
	Device modeling parameterization from I-V curves.
	Interconnect: R, L and C - Wire modeling
	Timing
	Power dissipation;
	SPICE Simulation Techniques (Project)
	Memories and array structures
	Midterm
	Clock Distribution
	Supply and Threshold Voltage Scaling
	Reliability and IC qualification process
	Advanced Voltage Scaling Techniques
	Power Reduction Through Switching Activity Reduction
	CAD tools and algorithms

Agenda



- Basics of sequentials
- Latch and flop details
- Flop based design
- Other types of sequentials
- Understanding the power implications of flops

Sequential Gates


- Several Uses
 - Used to store state of the machine (Like a register)
 - Used in finite state machine to represent different states of the machine
 - Also used in pipelined machine to designate pipestages
- Always accept clock as an input to synchronize pipestages
- Types:
 - Latch (Phase 1/Phase 2)
 - Flip-flop (Rising/Falling edge)
- Flavors
 - Enabled
 - Synchronous Set/Reset
 - Asynchronous Set/Reset

Traditional N-Latch

 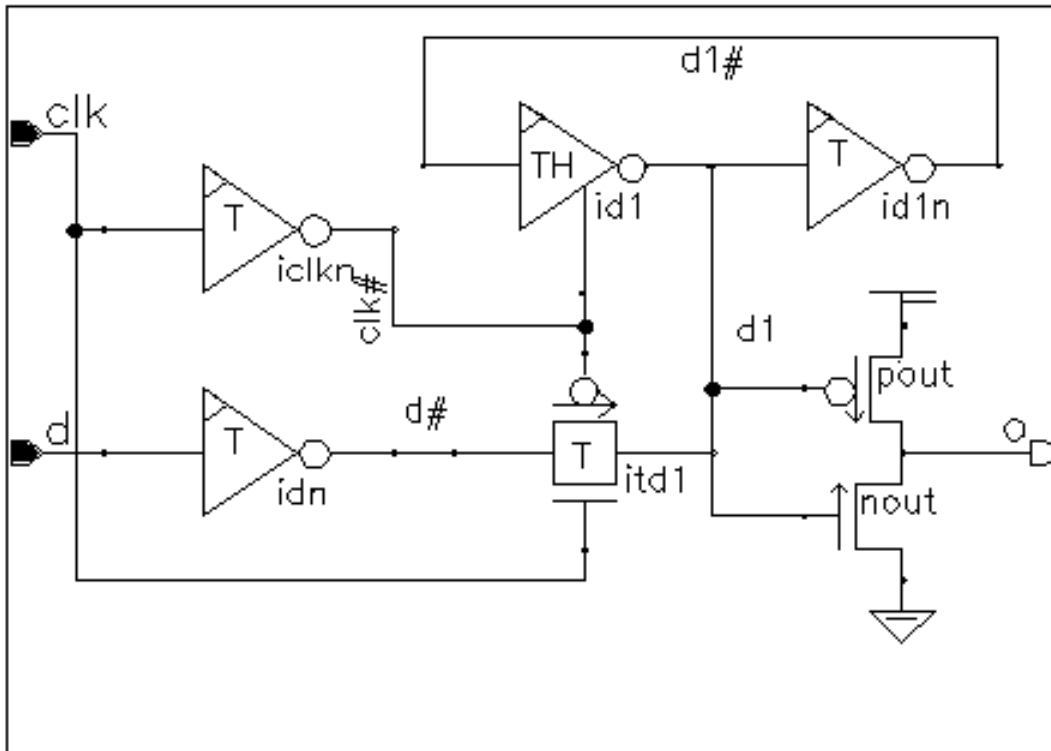- Level sensitive (Phase 1 open when clk is high)
- Also called N first or phase 1 latch





Traditional N-Latch

 


Traditional P-Latch

 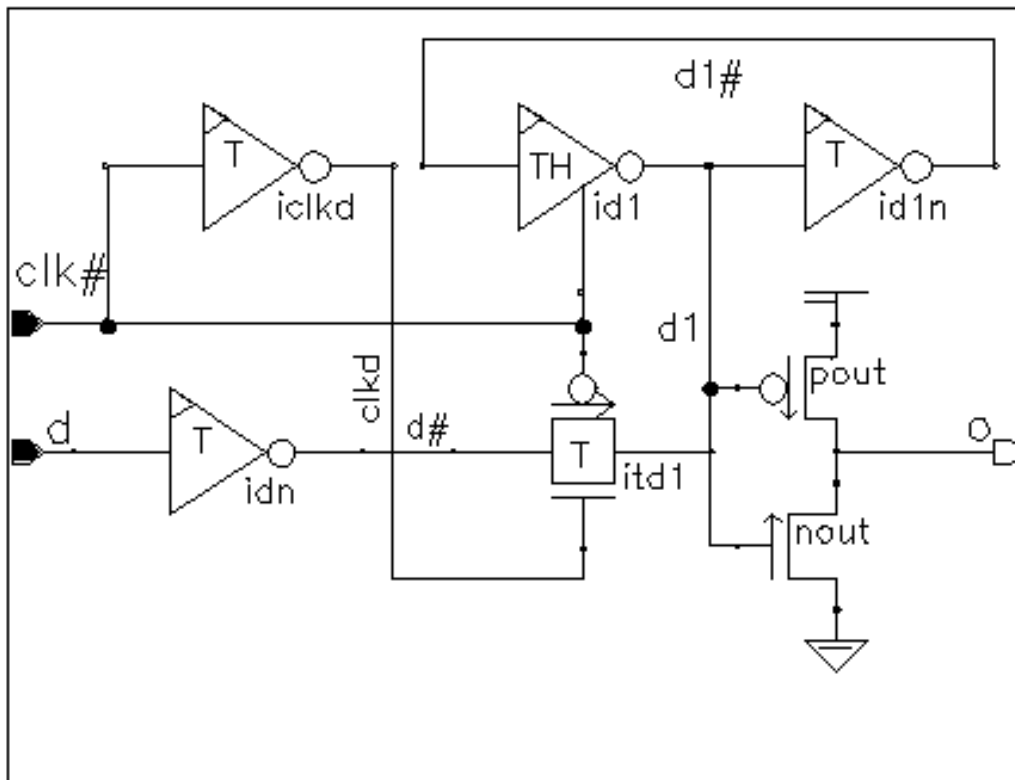- Level sensitive (Phase 2 open when clk is low)
- Also called P first or Phase 2 Latch





Traditional P-Latch

 


Positive Edge Flip-flop

 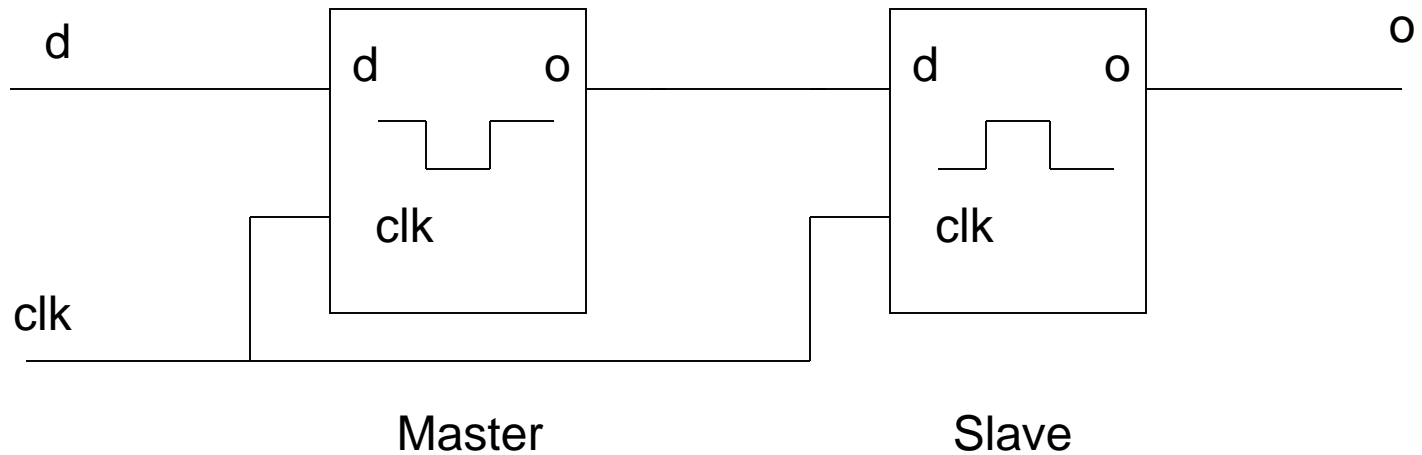- Edge sensitive
 - FF captures and drives data on rising edge of clk.
 - When clk rises, P latch shuts off, N latch turns on





Positive Edge Flip-flop

 


Negative Edge Flip-flop

 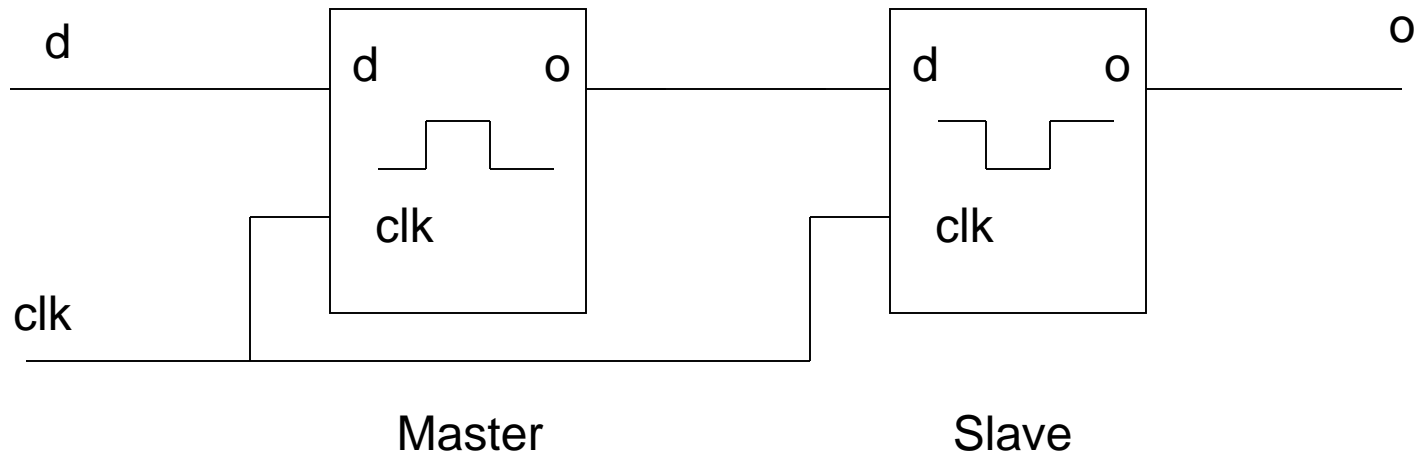- Edge sensitive (FF captures and drives data on falling edge of clk)




Latch parameters

- Setup time
 - Time, before the latch closes, that the data must arrive to guarantee the data is captured correctly after the latch closes
- Hold time
 - Time, after the latch closes, that the data can not switch to guarantee the data is captured correctly when the latch closes
- Clk to out delay
 - Delay from clk to out when the data is setup before the clk
- Data to out delay
 - Delay from data to out when the data arrives after the clk

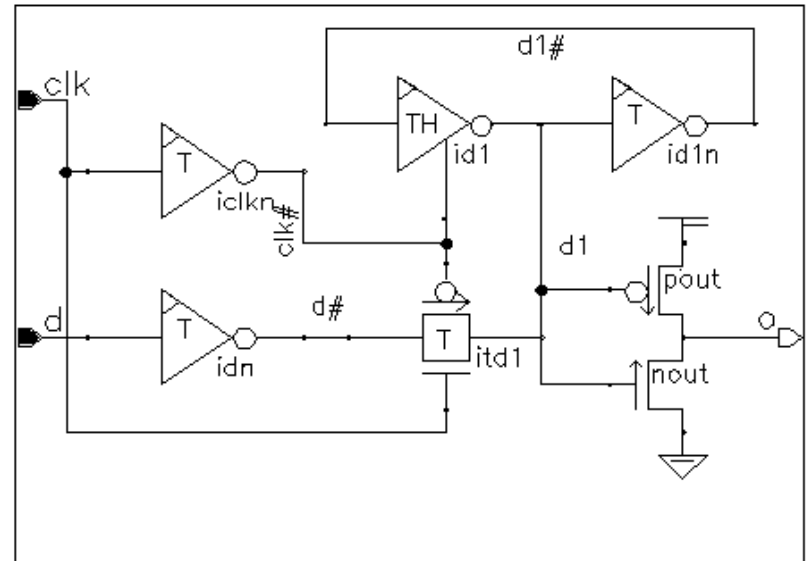

Traditional N-Latch

 


Flip-flop parameters

- Setup time
 - Time, before the opening clk edge, that the data must arrive to guarantee the data is captured correctly
- Hold time
 - Time, after the clk edge, that the data can not switch to guarantee the data is captured correctly
- Clk to out delay
 - Delay from clk to out when the data is setup before the clk.
- Note that there is no data to out delay since flops must have data setup to the edge.



Full keeper

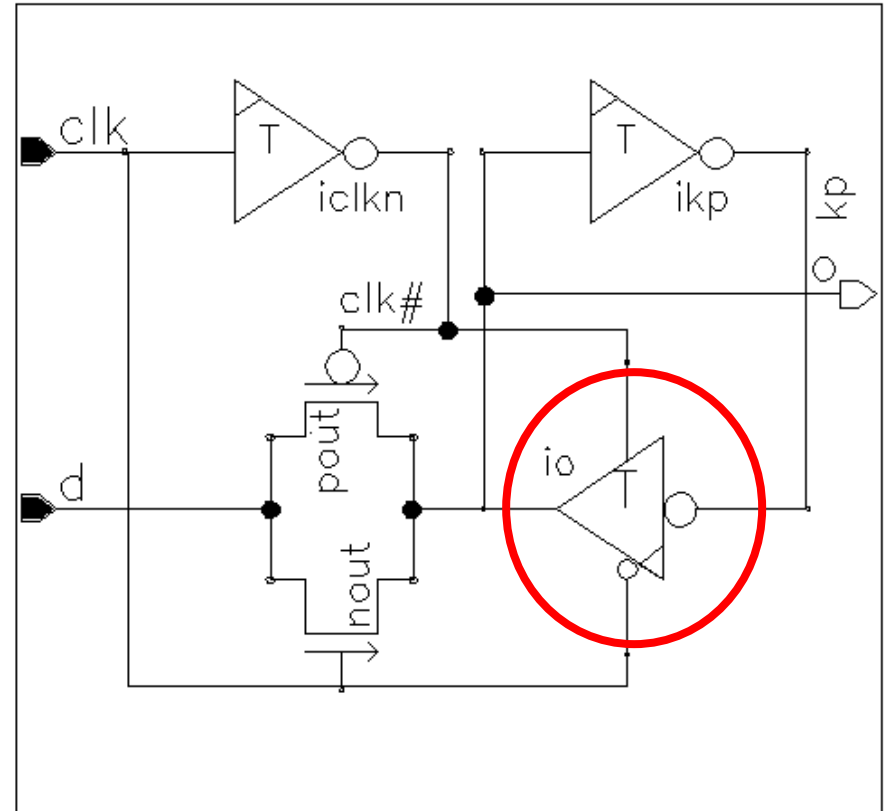- Feedback device has tristated both N and P.
- Writing of output through passgate has no opposition




Pipelining Sequence

  - For proper pipelining, must always alternate N-latch and P-latch.
- Flops must be consecutive rising edge flops




What about Latch/Flop boundary?

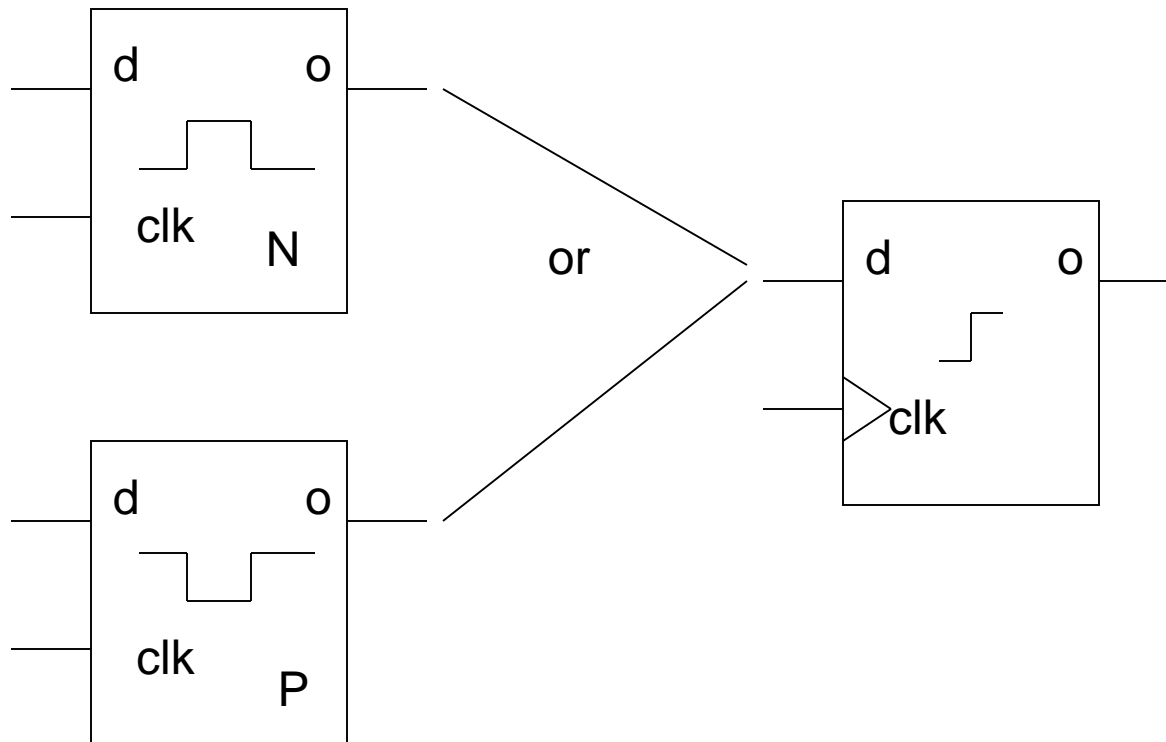- What type of latch should be in front of a rising edge flop?



What about Latch/Flop boundary?

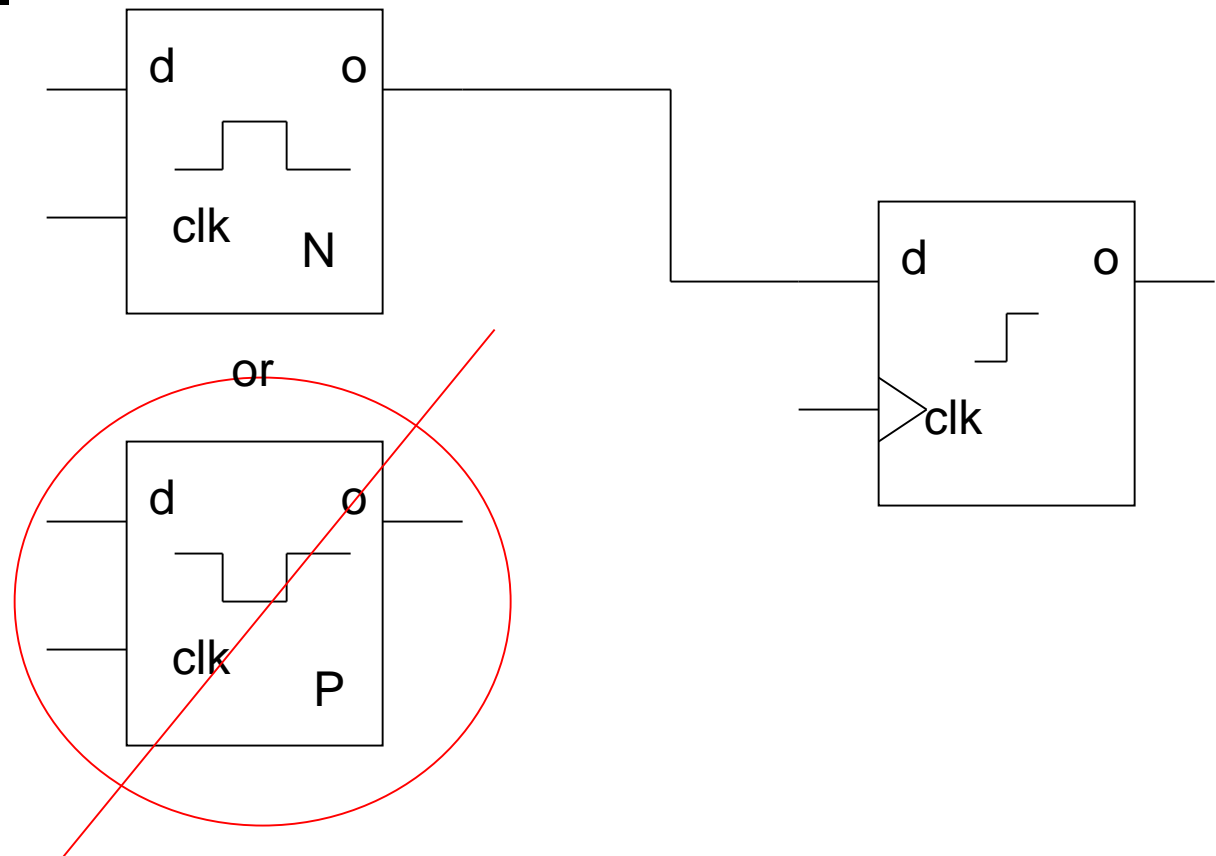- Since in a flop, the master is a P-latch, we **MUST** have a N-latch in front of a rising edge flop.




Likewise, Flop must drive to a P-latch

- On the other hand, since the slave is an n-latch, a rising edge flop must be followed by a p-latch




Flop issues

 - Assuming 100ps setup time, skew and clk-out delay
- How many paths are there and how many cycles?
- What is max frequency this circuit could run?




Flop Answers

 - 2 paths (A->B and B->C) each 1 cycle
- $200\text{ps} + 100\text{ps} = 300\text{ps}$. $1/300\text{ps} = 3.33\text{GHz}$
- $100\text{ps} + 100\text{ps} = 200\text{ps}$. $1/200\text{ps} = 5.0\text{GHz}$
- Max frequency = 3.33GHz




Time borrowing

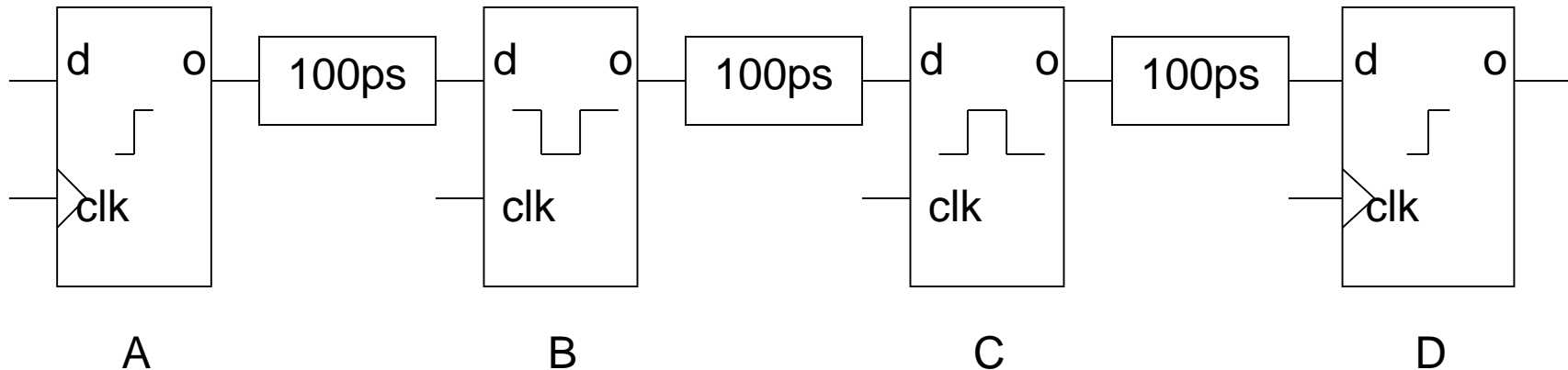- Time borrowing is a technique to increase frequency by converting flops to latches.
 - Allows amortizing skew, jitter, clk to out and data delays across more than 1 cycle
- How many paths are there and how many cycles?
- What is the new frequency assuming data-out delay is 50ps?




6 paths

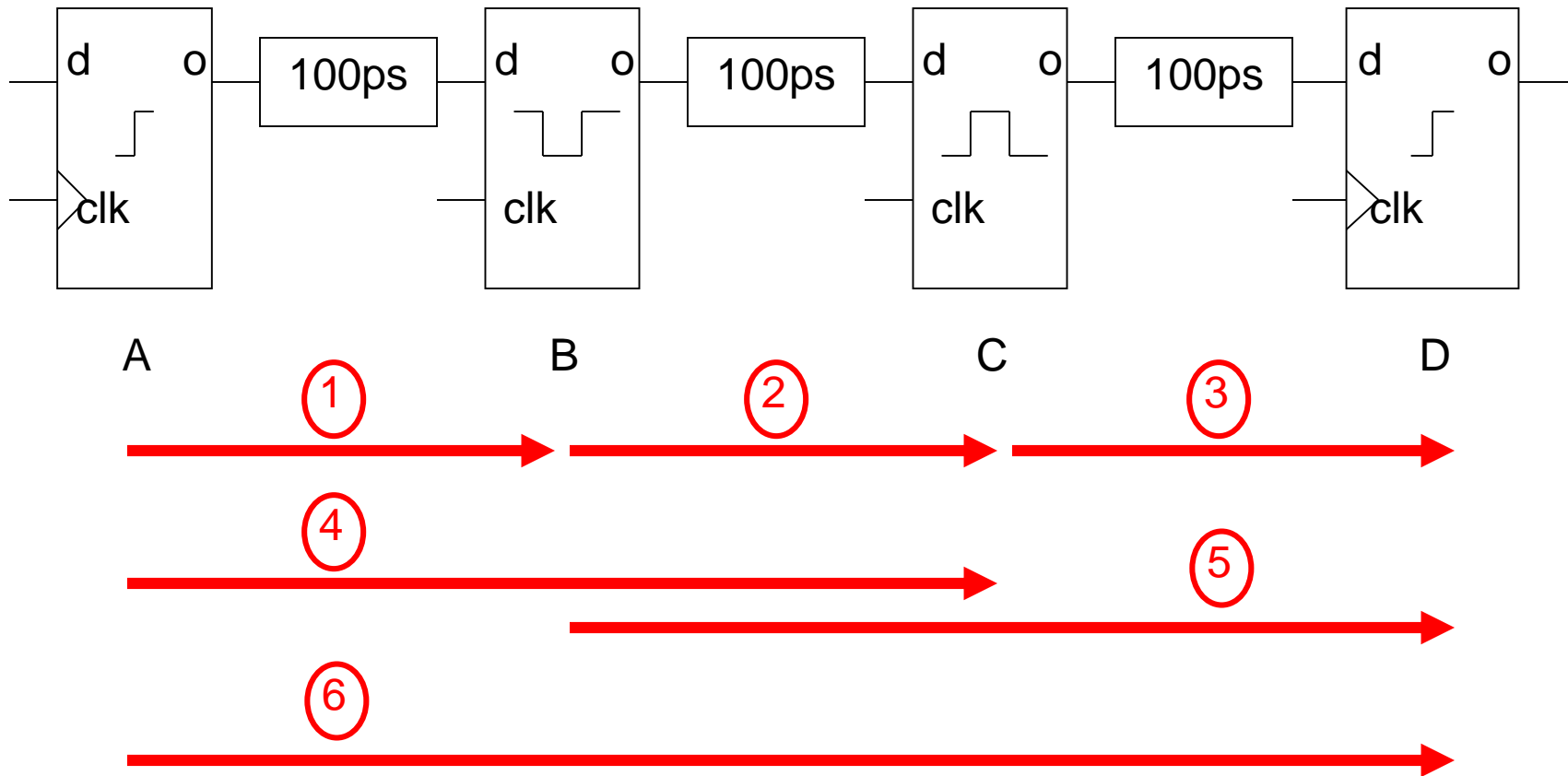- 6 paths (A-B, A-C, A-D, B-C, B-D, C-D).




6 paths

 - 6 paths (A-B, A-C, A-D, B-C, B-D, C-D).




Time borrowing Frequency calculations

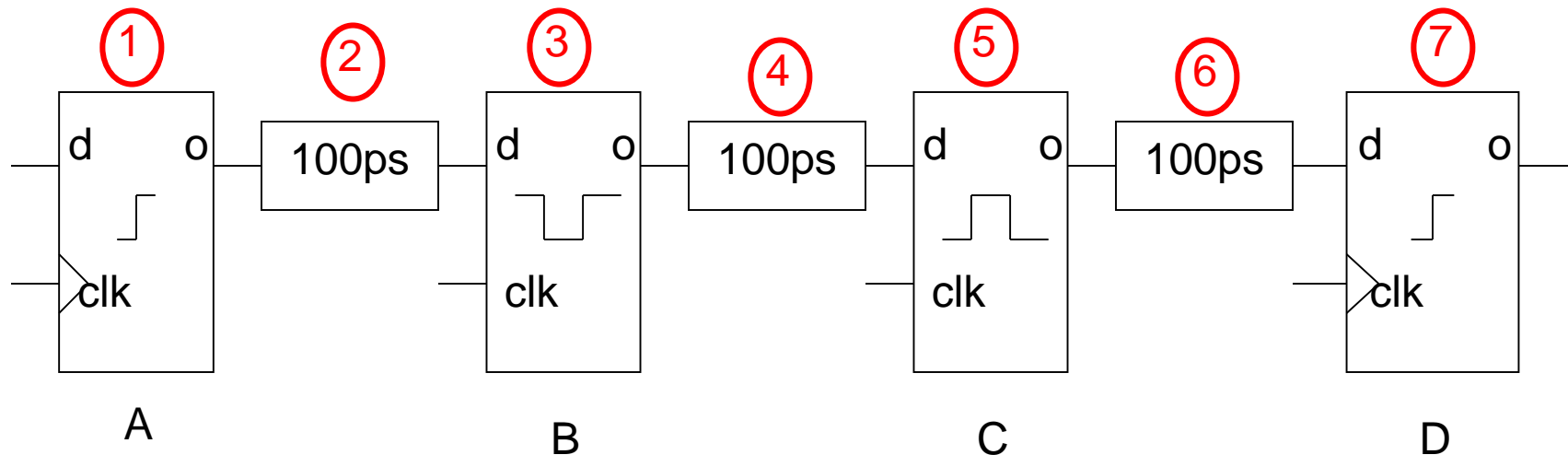- 2 paths -> 6 paths (A-B, A-C, A-D, B-C, B-D, C-D).
- A-B, B-C, C-D: 1 cycle path (100ps + 100ps) = 200ps = 5GHz
- A-C, B-D: 1.5 cycle path (100 + 50 + 100 + 100) = 350ps :
 $1.5/350\text{ps} = 4.28\text{GHz}$
- A-D: 2 cycle path (100 + 50 + 100 + 50 + 100 + 100) = 500ps :
 $2/500\text{ps} = 4\text{GHz}$
- New frequency = 4GHz



A-D path explained

- Assume 50ps clk-out and 50ps setup

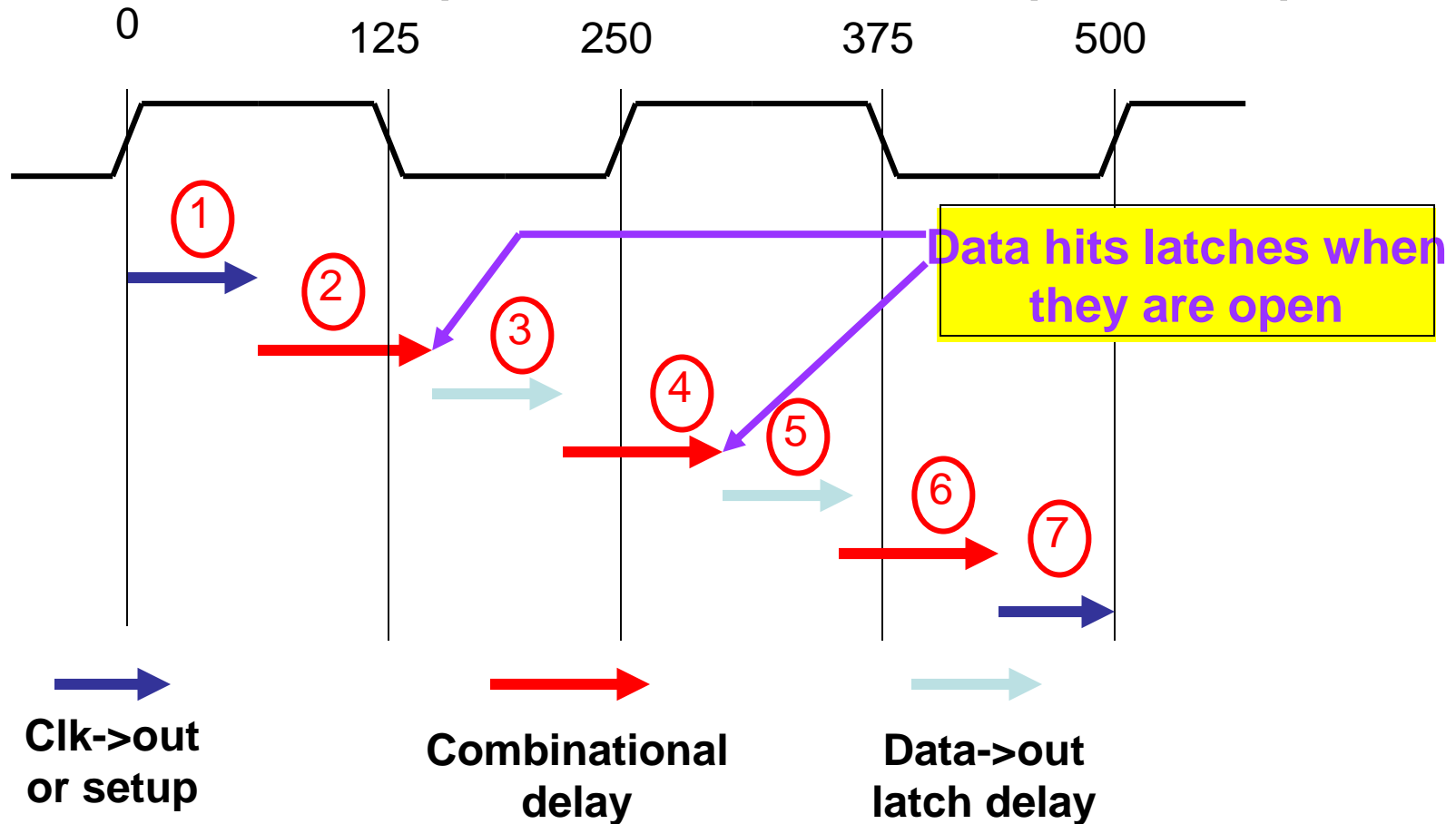

When/Why time borrowing works


- 2 advantages of time borrowing
 - Allows “borrowing” time from a cycle that has extra margin to a cycle that doesn’t
 - In our example, the cycle that ran at 3.33GHz borrows time from the cycle that had 5GHz
 - Allows amortization of setup time and skew over several cycles
 - In our example, the 100ps overhead penalty is now over 2 cycles so the per cycle penalty is 50ps

Time borrowing

- Positives:
 - Allows some amount of time borrowing without some of the negative of time borrowing
 - Very little extra clock load
 - No latch explosion
 - No RTL change
- Negatives:
 - Only allows only a buffer delay of borrowing
 - Min delay of the first path has been worsened by 1 buffer delay.
 - Skew has increased


Enabled latches

 - When enable is a 0, latch does keeps passgate closed




Synchronous Set latches

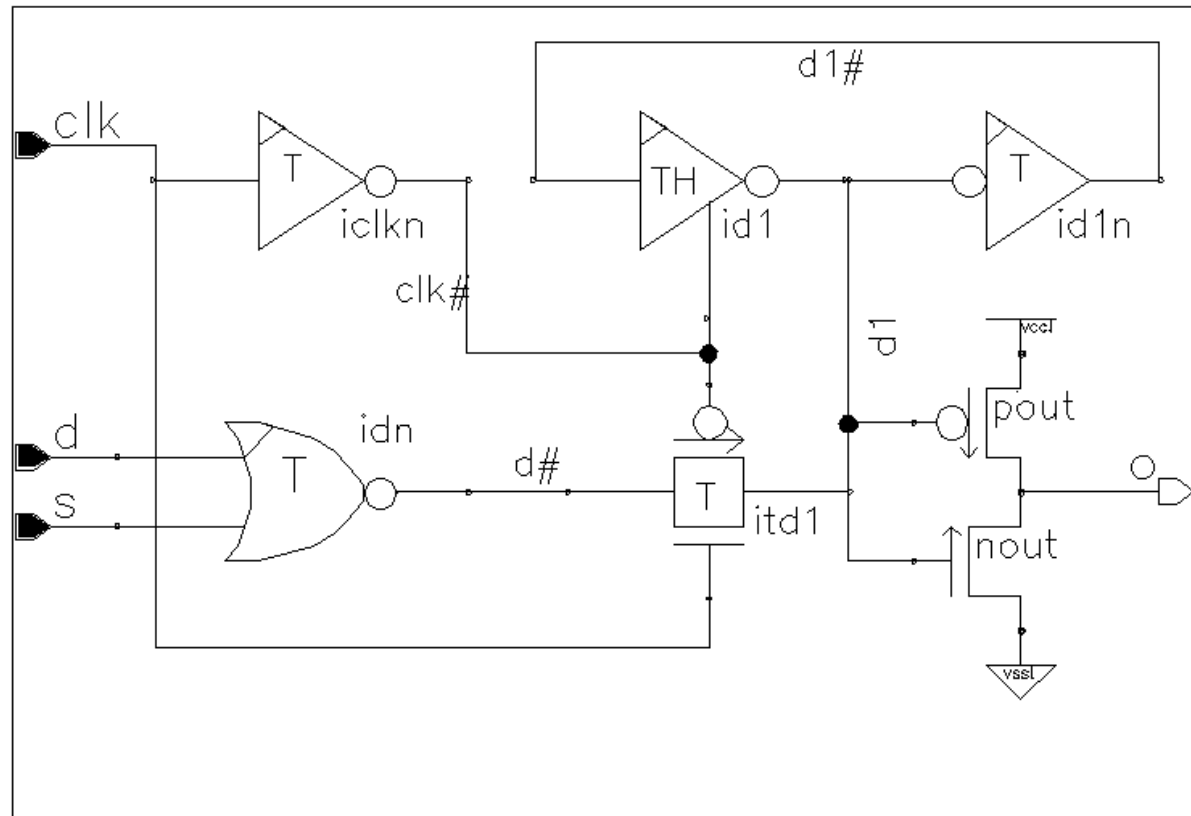- When set is a 1, when clk is open, latch stores a 1




Synchronous Reset latches

 - When $r\#$ is a 0, when clk is open, latch stores a 0




Asynchronous Set Flops

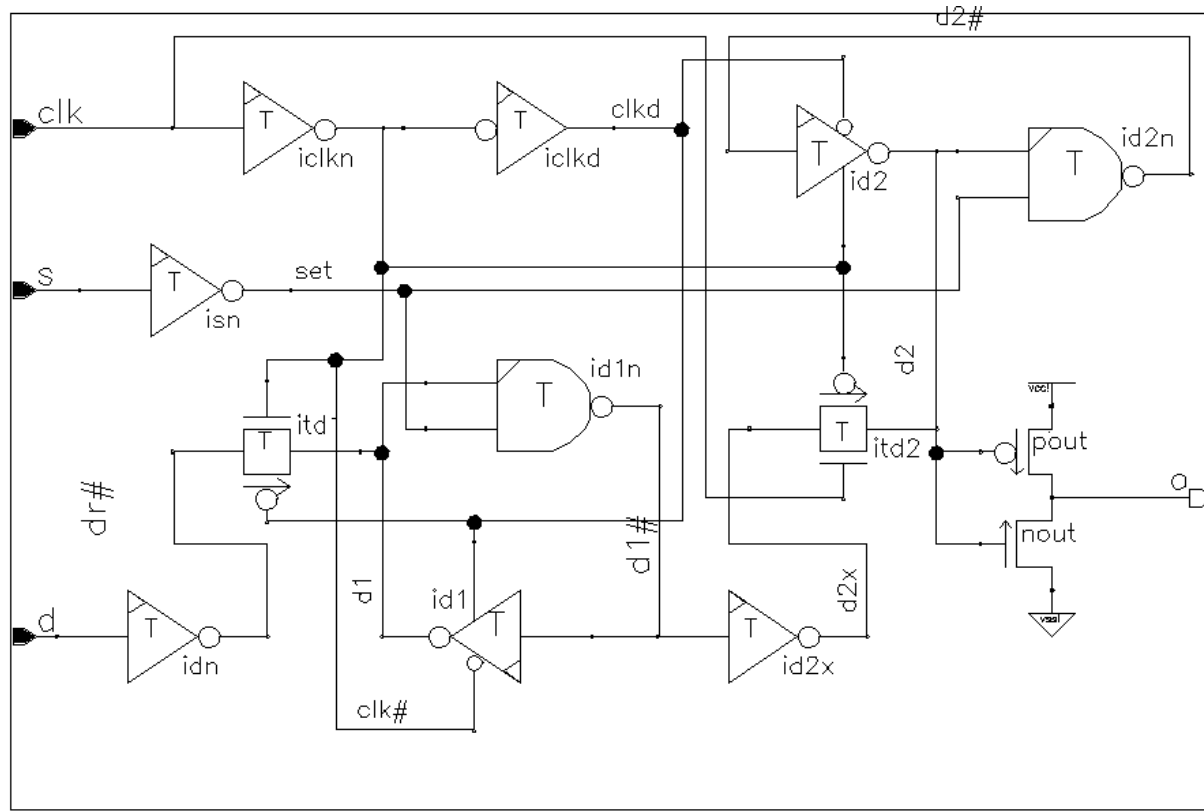- When set is a 1, output immediately changes to a 1
- Does not wait for rising edge of a clock




Mux latches

 - Note selects are muxed qualified clocks




Unprotected latches

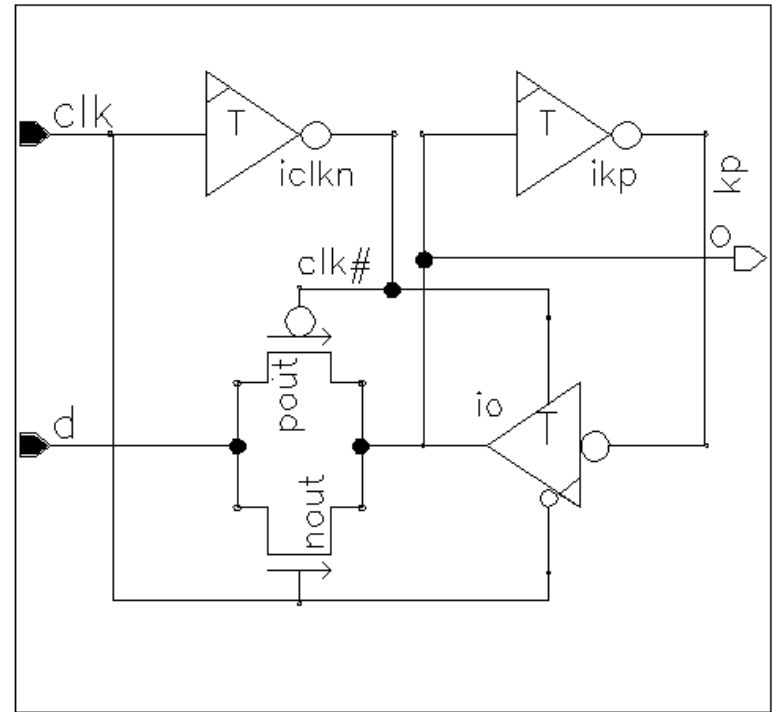- Either no input protection, output protection or both
- Allows converting the inverter to logic gates or customize the inverters normally in a latch
- Loss of output protection require extra caution not to disturb latch node
- To guarantee latch writability, should use a full keeper




Using the Enabled/Set/Reset sequentials

- Problem: How can we improve this?

 


Use a Reset Latch to reduce logic

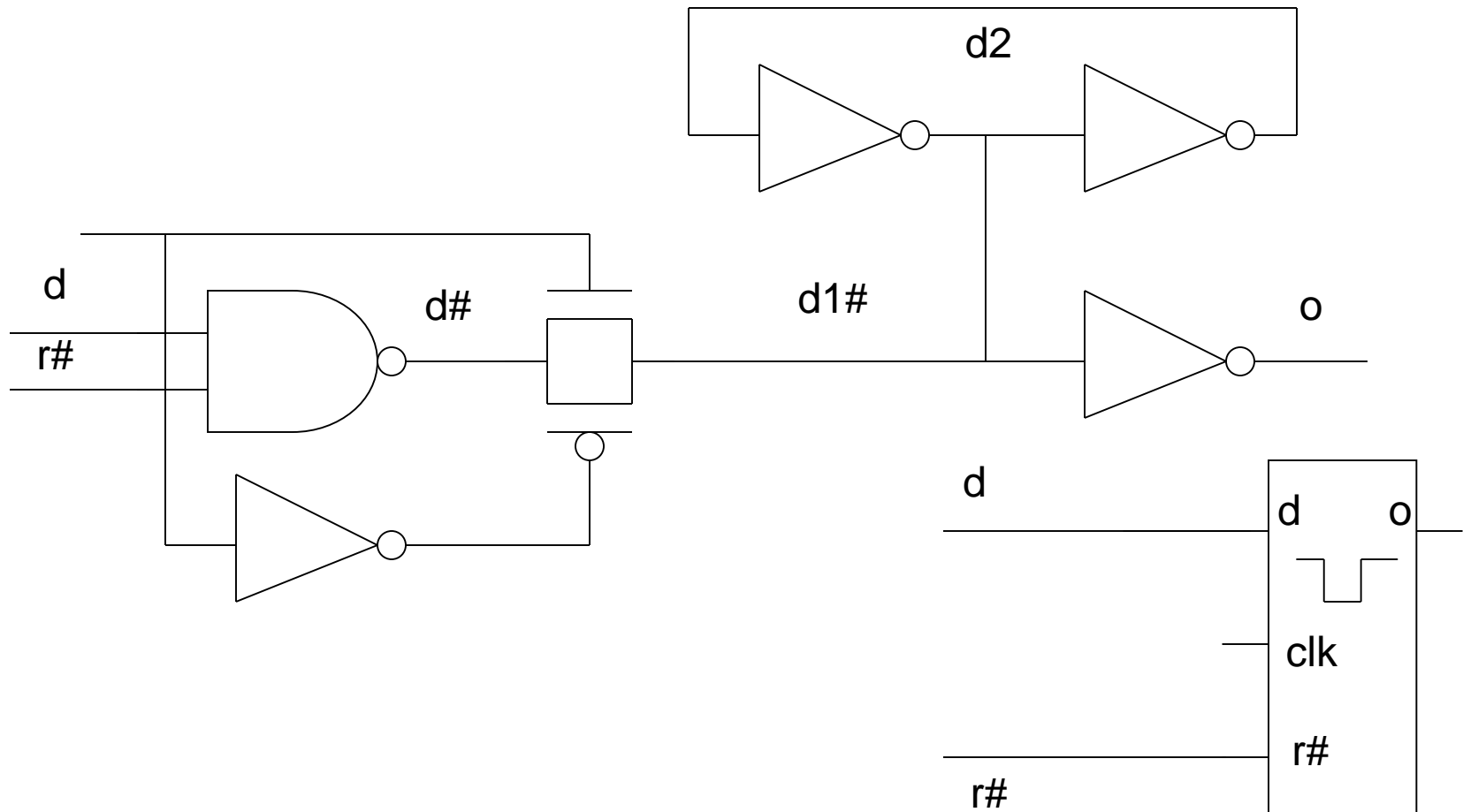- Converts the first inverter in a latch to a nand gate to eliminate 2 gates



Power issues

 
- Sequentials mean clock power!
 - Keep sequentials as small as possible by buffering outputs when timing allows to keep the sizing of the flip-flop small.



- Avoid duplicating/unnecessary flops (Look for opportunities for flop reduction)

Power issues




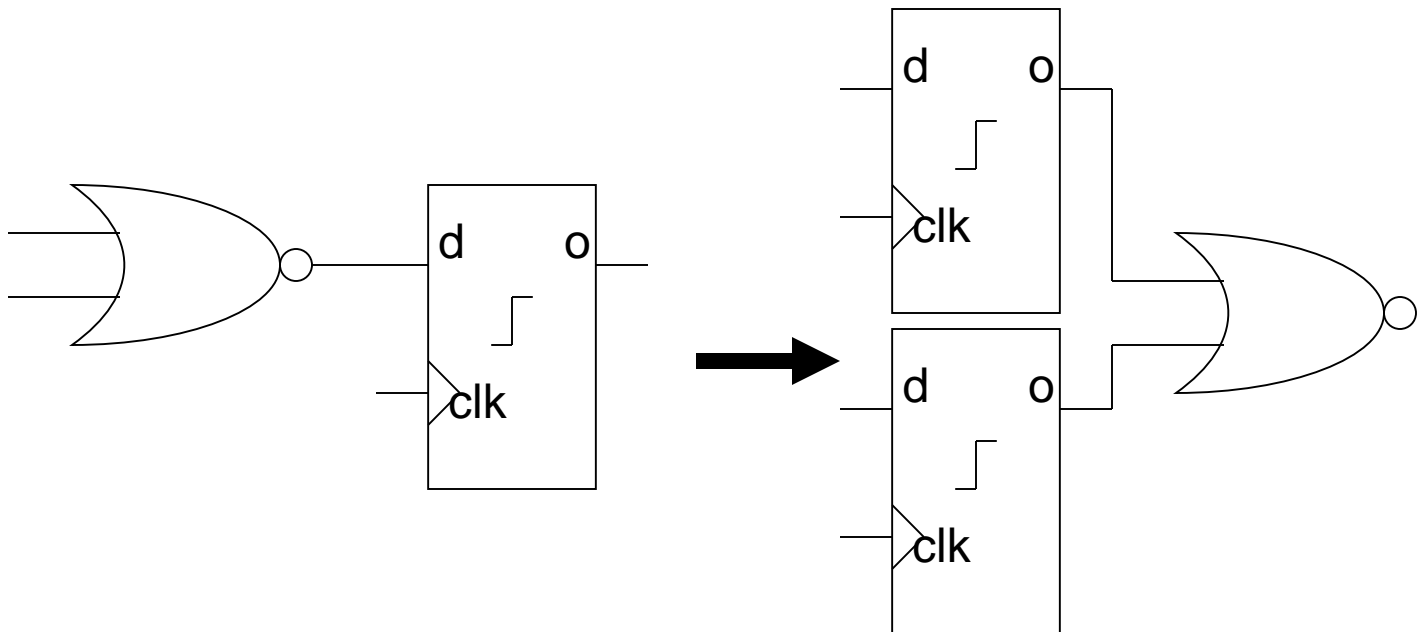
- Be careful where to select flops
 - When fixing speed paths by moving logic from 1 stage to another, watch for flop explosion
 - Same issue with flop->latch conversion



Summary


- Know the different types of sequential and the order they need to be used.
- Understanding time borrowing can help solve speed paths in a path at the expense of complexity, clock power
 - Select flop to latch conversion or time borrowing flop where appropriate
- **ALWAYS** think about power. Keep sequential count as low as possible and keep sequential sizes small by buffering outputs.

Basic LATCH Operation

  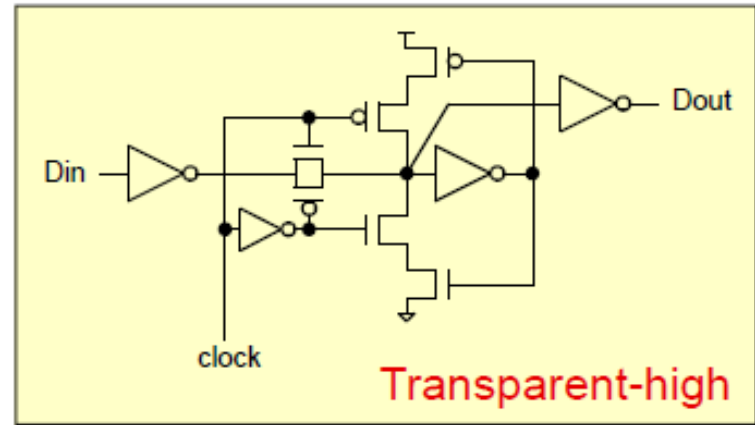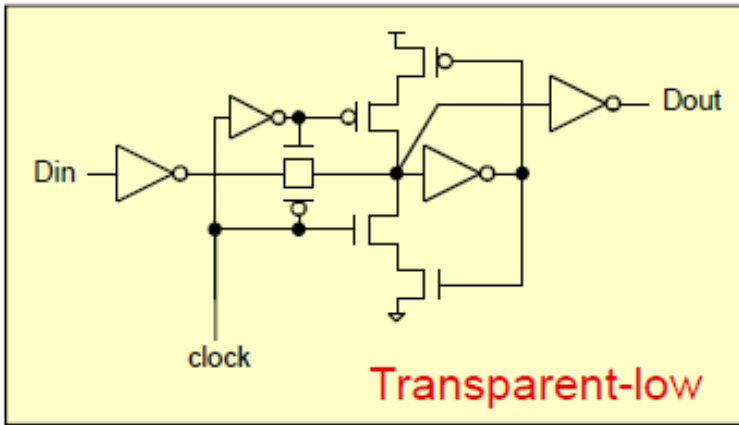


FLOP Delay

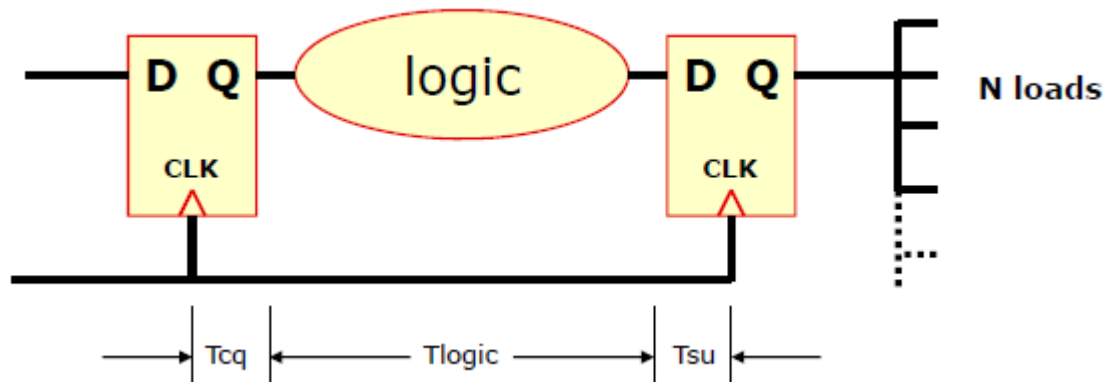
- Sum of setup time and Clk-output delay is the only true measure of the performance with respect to the system speed (MAXDELAY)
- $T_{cycle} = T_{cq} + T_{logic} + T_{su} + T_{skew}$
- T_{logic} contains interconnect delay



Building a FLOP with Two Latches


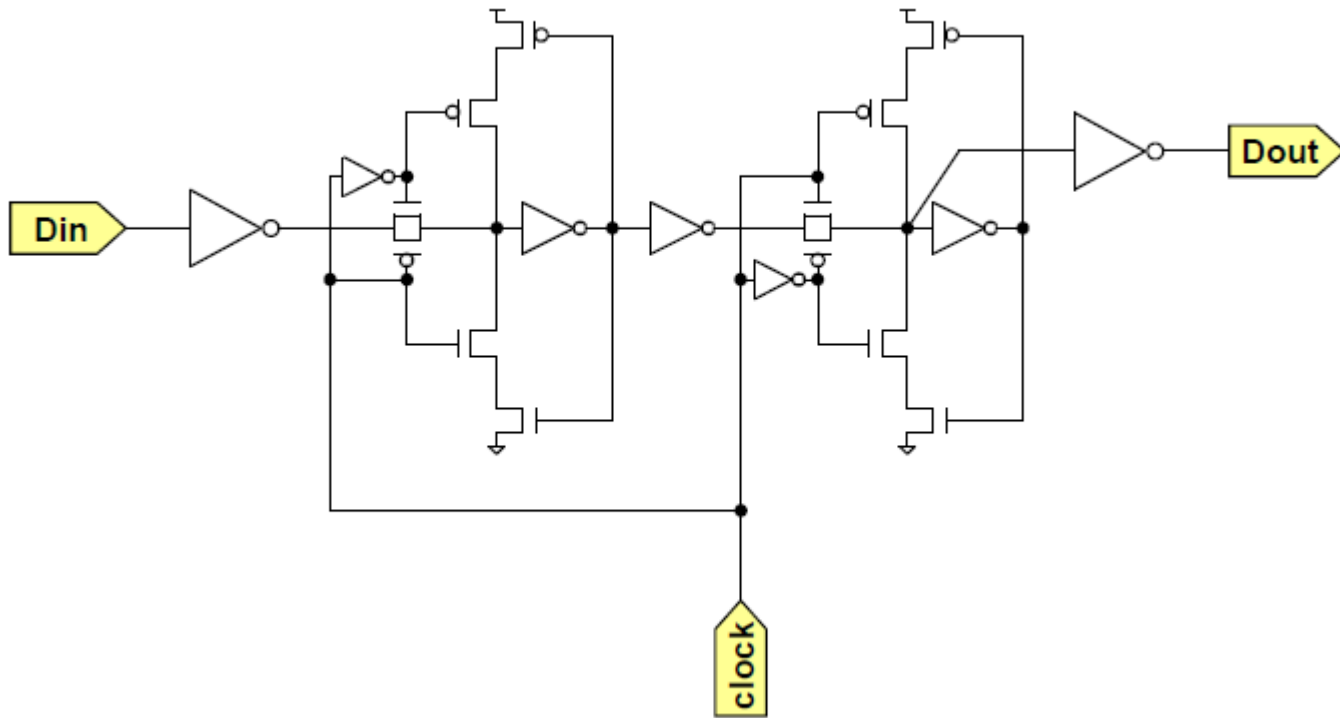


FLOP Timing Diagrams

 



- Tsu** : input setup time
- Thold** : input hold time
- Tcq** : clock to out
- Tdata to out = Tsu + Tcq**

MAXDELAY

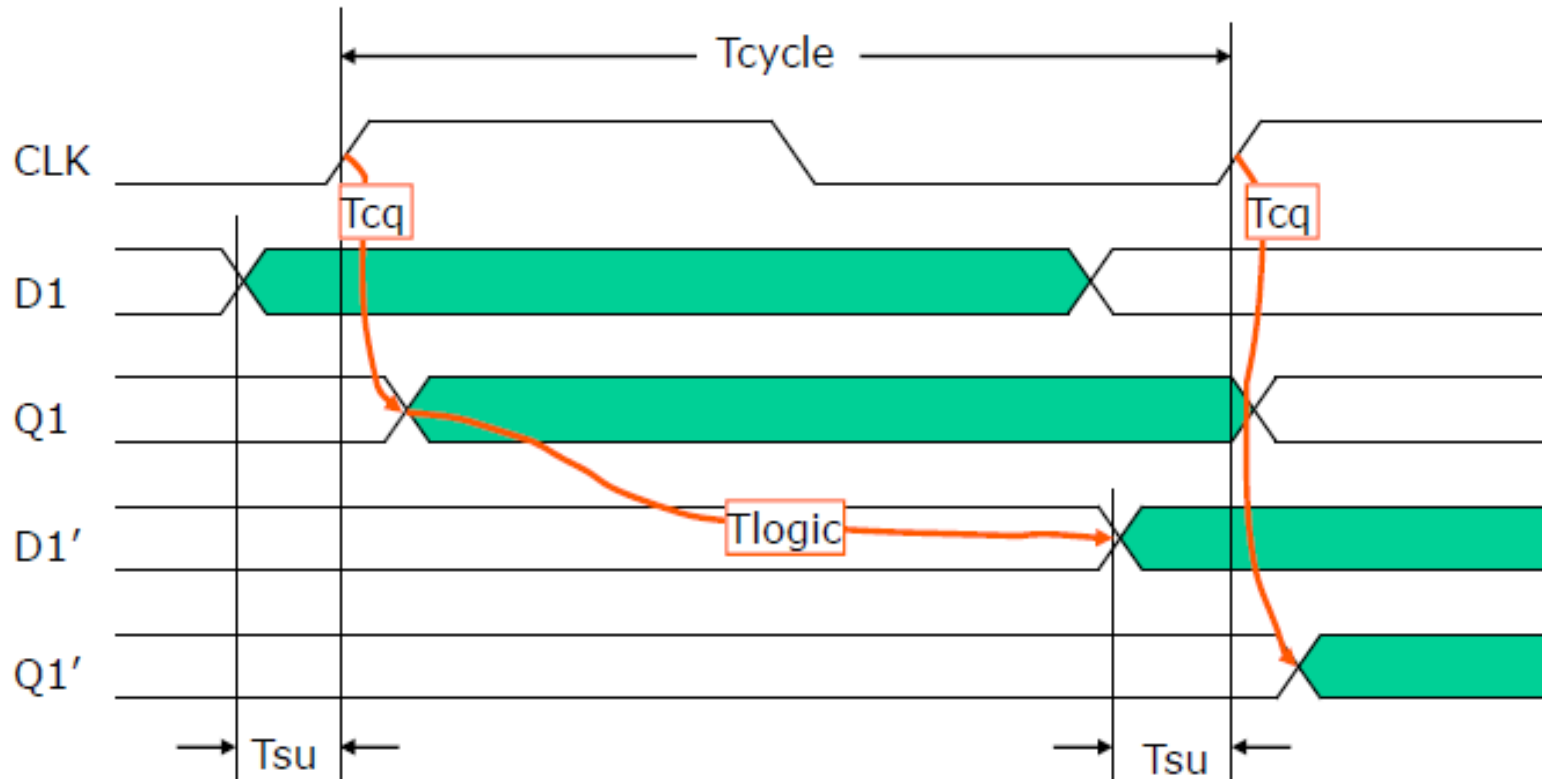 

$T_{logic} < T_{cycle} - (T_{cq} + T_{su})$ or **$T_{cycle} \leq T_{logic} + T_{cq} + T_{su}$**



MINDELAY

  


$$T_{logic} > T_{hold} - T_{cq} + T_{skew}$$

FLOP with SCAN

SCAN GADGET

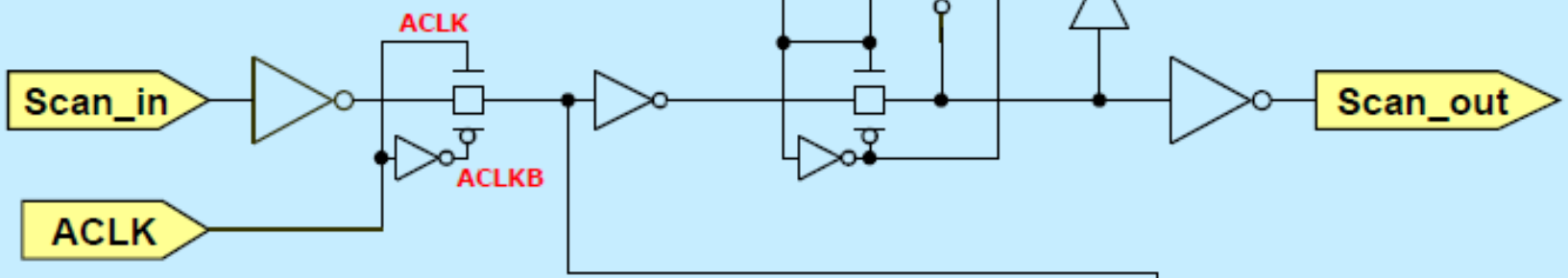 


FUNCTIONAL

 

QZ

- What is this circuit ?

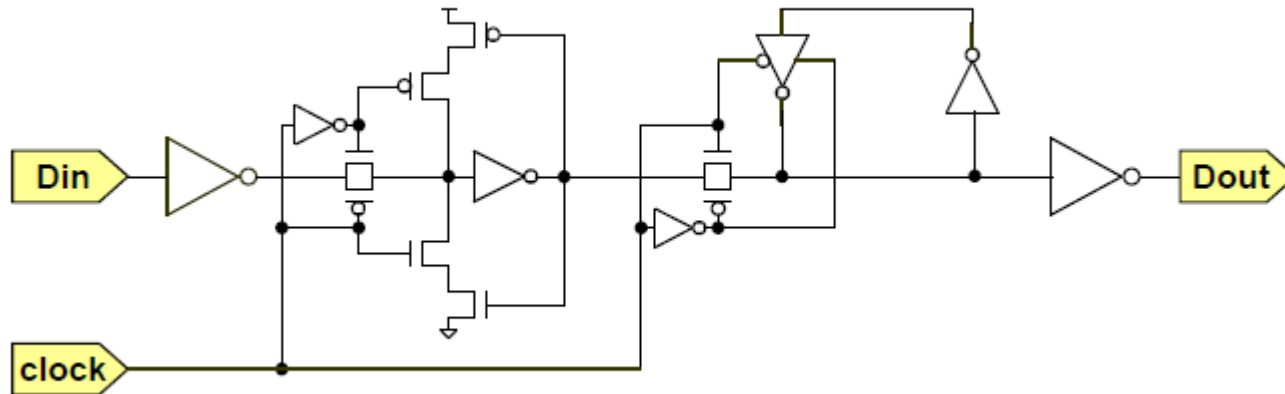

INVERTING MSFF