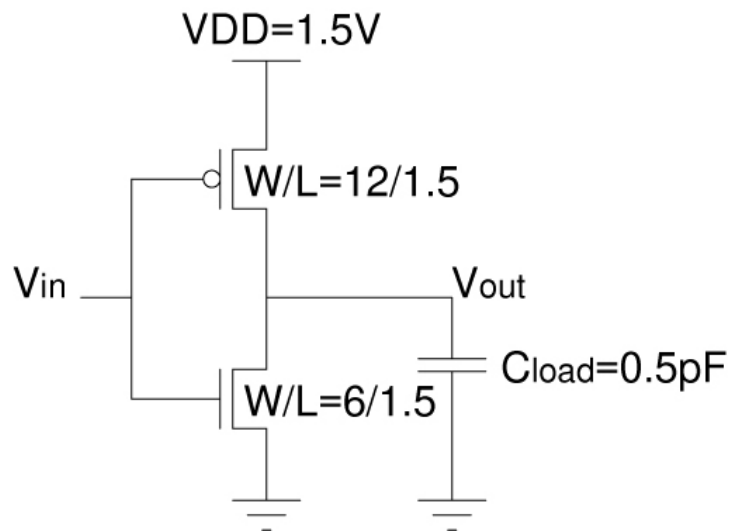


Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science
6.012
Microelectronic Devices and Circuits
Spring 2007
March 16, 2007 - Homework #4
Due - March 23, 2007

Problem 1

Consider the CMOS inverter pictured below. Take channel length modulation into account.



Parameter	NMOS	PMOS
V_{TO}	0.5 V	-0.5 V
μ	220 cm^2/Vs	110 cm^2/Vs
λ	0.1 V^{-1}	0.1 V^{-1}
T_{ox}	15 nm	15 nm

• **Dimensions of W and L are in μm**

- Calculate V_M , the voltage midpoint.
- Calculate A_V , the voltage gain at $V_{in}=V_M$.
- Calculate N_{ML} and N_{MH} , the noise margin low and noise margin high.
- Calculate t_{PHL} and t_{PLH} , the propagation delay from high-to-low and propagation delay from low-to-high.

a) We set the drain current of the PMOS equal to the drain current of the NMOS, and plug in $V_{in}=V_{out}=V_M$.

$$V_M = 0.75V$$

b) Voltage gain, $A_V = -(g_{mn} + g_{mp}) * (r_{on} || r_{op})$

$$g_{mn} = g_{mp} = 50 \mu S$$

$$r_{on} = r_{op} = 1.47 M\Omega$$

$$A_V = -74$$

c) $NM_L = V_M + (V_{DD} - V_M) / A_V = 0.74V$

$$NM_H = V_{DD} - V_M + V_M / A_V = 0.74V$$

d) propagation delay = $\Delta V * C / I$

$$\Delta V = 0.75V = 50\% \text{ of the total value}$$

$$C = 500fF$$

$$I_{D,pmos} = I_{D,nmos} = 202 \mu A$$


$$T_{PH} = T_{PL} = 1.856ns$$


Problem 2


We will now use the following SPICE model and compare our hand calculations from Problem 1 with simulated results.

```
.MODEL N15 NMOS LEVEL=1 VT0=0.5 TOX=1.5e-8 U0=220 LAMBDA=1.0e-1
+GAMMA=0.6 CJ=1e-4 CJSW=5e-10 PB=0.95
.MODEL P15 PMOS LEVEL=1 VT0=-0.5 TOX=1.5e-8 U0=110 LAMBDA=1.0e-1
+GAMMA=0.6 CJ=3e-4 CJSW=3.5e-10 PB=0.9
```

 - Use the DC sweep on the input voltage to simulate transfer characteristics using SPICE. Compare V_M , A_V , N_{ML} , N_{MH} , with the calculated results.
- Use the Pulse input to simulate an input waveform shown below using SPICE. Compare t_{PHL} and t_{PLH} with your hand calculations.



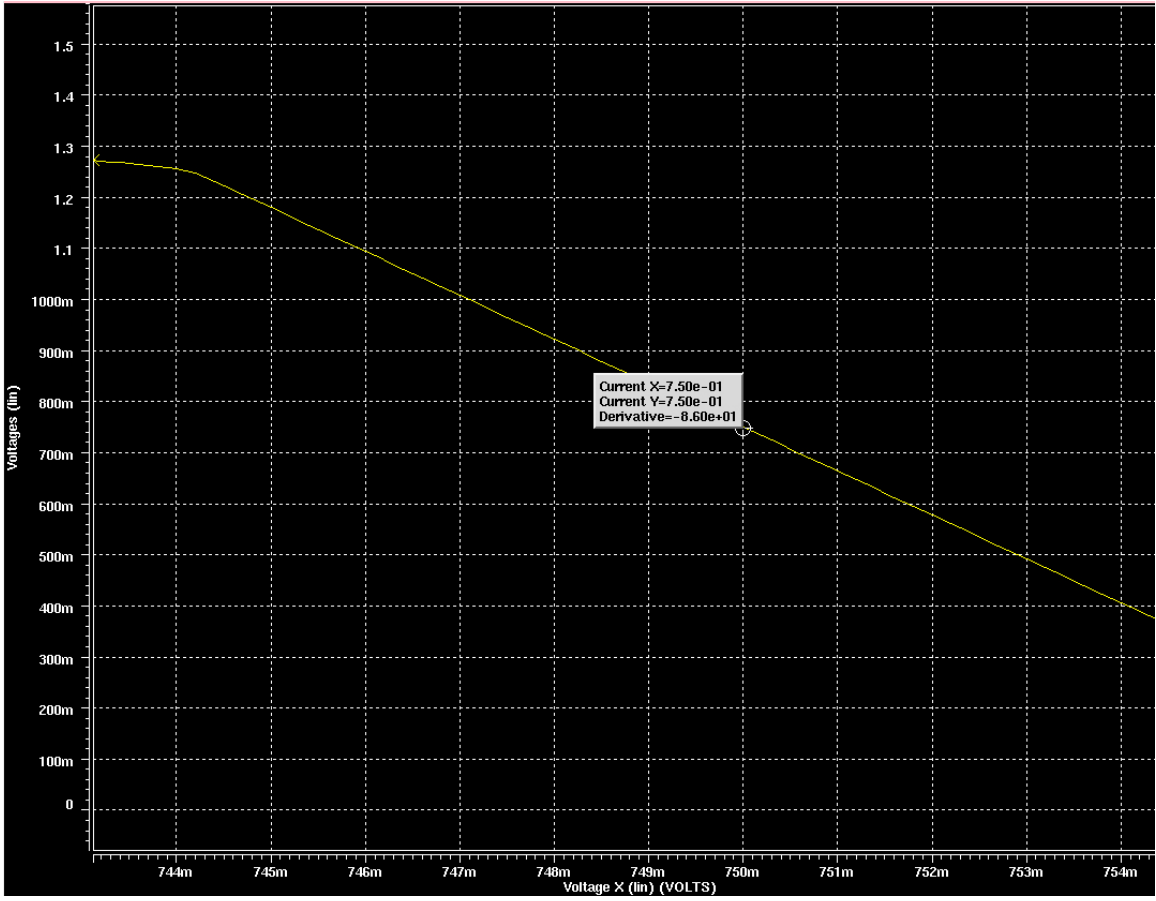


 


We see $V_M=0.75V$.

$$N_{ML} = V_{IL}-V_{OL} \sim 0.677V-0.0625V=0.615V$$
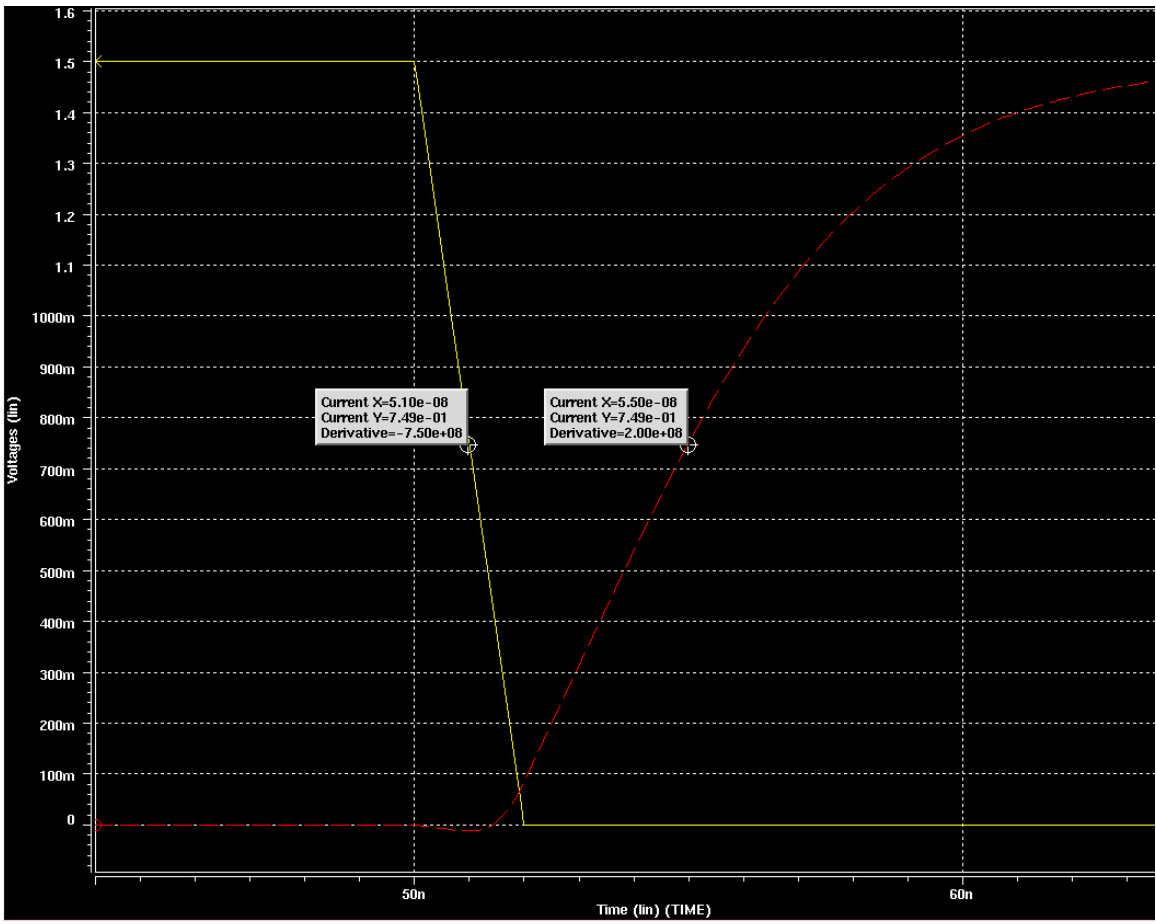
$$N_{MH} = V_{OH}-V_{IH} \sim 1.44V-0.821V=0.619V$$



 


$$t_{PLH} \sim 4 \text{ ns}$$

$$t_{PHL} \sim 4.1 \text{ ns}$$

 Problem 3

Consider the circuit below, which consists of an NMOS device and resistor load. Disregard channel length modulation for this problem.

- Calculate V_M , V_{OH} , V_{OL} . Remember, for hand calculations we assume $V_{OH} = V_{MAX}$, and $V_{OL} = V_{MIN}$.
- Calculate the voltage gain of this circuit, when $V_{in} = V_M$.



- a) Set the current through the resistor equal to the current through the NMOS, with $V_{in} = V_{out} = V_M$.

$$\frac{V_{DD} - V_M}{R} = \frac{1}{2} \frac{W}{L} \mu C_{ox} (V_M - V_{Tn})^2$$

$$V_M = 1.16V$$

When the input is 0V (low), the NMOS is in cutoff, so no current flows. Therefore, $V_{OH} = V_{MAX} = 1.5V$

When the input is 1.5V (high), the NMOS is in triode. We must solve as we did earlier, setting the current through the resistor equal to the NMOS in triode. V_{in} is set to 1.5V.

$$\frac{V_{DD} - V_{min}}{R} = \frac{W}{L} \mu C_{ox} \left(V_{DD} - \frac{V_{min}}{2} - V_{Tn} \right) V_{min}$$

$$V_{OL} = V_{MIN} = 0.63V$$

- b) The small signal gain of this circuit is $-g_m * R$.


$$g_m = \sqrt{2 \frac{W}{L} \mu C_{ox} I_{DSat}} = 1.34mA/V$$

$$A_V = -1.34$$

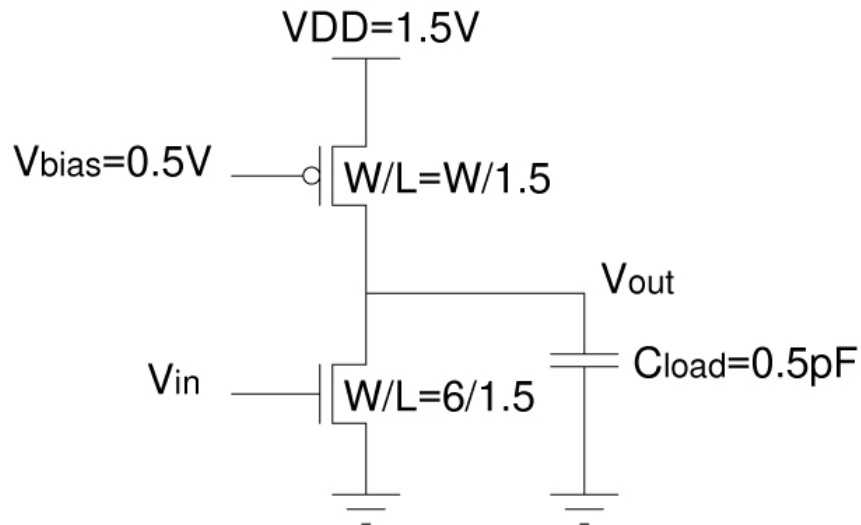Problem 4

Consider the circuit below, which consists of an NMOS device and PMOS current source load. *Do not* neglect channel length modulation.

- Calculate the width of the PMOS device so its saturation current is $50\mu\text{A}$.
- Calculate V_M , V_{OH} , V_{OL} . Remember, for hand calculations we assume $V_{OH}=V_{MAX}$, and $V_{OL}=V_{MIN}$.
- Calculate the voltage gain of this circuit, when $V_{in}=V_M$.



$$a) 50\mu\text{A} = \frac{1}{2} \frac{W}{1.5} \mu_p C_{ox} (1 - 0.5)^2$$

Width of device, $W = 23.7$ microns

b) Setting the saturation drain current of the NMOS equal to that of the PMOS, we find

$$V_M = 1.175\text{V}$$

When the input is low, the NMOS is in cutoff, therefore

$$V_{OH} = V_{DD}$$

When the input is high, the NMOS is in triode. Setting the current through the NMOS equal to the PMOS,

$$\frac{1}{2} \frac{23.7}{1.5} \mu_p C_{ox} (1 - 0.5)^2 (1 + .1(V_{DD} - V_{min})) = \frac{6}{1.5} \mu C_{ox} \left(V_{DD} - \frac{V_{min}}{2} - 0.5 \right) V_{min}$$

$$V_{MIN} = V_{OL} = 0.33V$$

c) For this circuit, the voltage gain is $-g_{mn} * (r_{on} || r_{op})$

$$g_m = \sqrt{2 \frac{W}{L} \mu C_{ox} I_{DSat}} = 0.144 \text{ mA/V}$$

$$r_{on} = r_{op} = \frac{1}{\lambda I_D} \rightarrow I_D = 50 \mu A, r_o = 200 k\Omega$$

$$A_v = -14$$