




Electrical and Computer Systems Engineering Department
ENCS333
Homework 4

Due November 5th

1. Using the rules given in lecture notes, find V_{g2} and V_o required for both transistors to be ON in the two-transistor circuit shown below for each of the listed input voltage combinations. Assume $V_{DD} = 2.5V$, $V_{tn} = 0.5V$, and $|V_{tp}| = 0.5V$.

 - (a) $V_{i1} = 0V$, $V_{i2} = 0V$
- (b) $V_{i1} = 2V$, $V_{i2} = 2V$
- (c) $V_{i1} = 2.5V$, $V_{i2} = 2.5V$
- (d) $V_{i1} = 0V$, $V_{i2} = 1V$



2. Design a transistor-level CMOS logic circuit to implement the function

$$F = \overline{(x + yz) \cdot (w + x)}$$

using the least number of transistors.

HINT: Consider that you may need to expand the equation in order to reduce it using the logic properties shown in the Chapter 2 lecture notes.

3. Construct the CMOS logic circuit that implements $Y = a + \overline{a + b + c\bar{b}}$ using the fewest possible transistors. You are allowed to use inverted inputs (e.g., a') rather than adding inverters to create these signals.

4. Mux design

a) Construct a schematic for a 2:1 MUX using two CMOS transmission gates and an inverter.

- b) Using the 2:1 MUX symbol below, construct a gate-level schematic for a 4:1 multiplexer using only 2:1 multiplexers. The inputs should be s_0 , s_1 , and $P_3:0$ ($P_0 - P_3$) and the output is F .
- c) How many transistors are needed to form the transmission gate based 4:1 MUX in (b)?
- d) Are there any redundant transistors that could be eliminated if you constructed the 4:1 MUX at the transistor level? If so, how many and which ones?

5. A CMOS metal layer with resistivity, ρ , $3 \times 10^{-6} \Omega\text{-cm}$ is $0.6 \mu\text{m}$ thick. It is used to draw a signal trace that is $100 \mu\text{m}$ long and $0.75 \mu\text{m}$ wide.

- a) Calculate the sheet resistance, R_s , of this metal layer.
- b) How many “squares”, n , are in the signal trace?
- c) Use the results in (a) and (b) to determine the resistance of the trace.

6. Draw the schematic for the CMOS circuit that implements the function F described by the truth table below. Use the least possible number of transistors. Explain your procedure and show the reduced function equation used to design the schematic.

<i>Inputs</i>			<i>Output</i>
X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

7. Sketch a color-coded stick diagram for the circuit that implements the function $f = a + \overline{(b \cdot c)} + d$. Organize the layout so that the transistors can be implemented on a continuous strip of active (i.e., do not break the active).