

1. Need to understand and solve all HW questions

Area will be covered in Midterm:

- Semiconductor material: pn-junction, NMOS, PMOS
- IC Manufacturing Process
- Design Metrics CMOS
- Transistor Devices
- The CMOS inverter
- Combinational logic structures
- Layout design rules
- basic gates
- Static & Dynamic CMOS Logic

2. What are the main design matrices ?

3. Determine the region of operation (Cut off, Linear, Saturation, ..) in the following configurations.


See slides for detail answer

Ans: The three modes are: : The three modes are: (a) Accumulation mode when Accumulation mode when V_{gs} is much less than is much less than V_t (b) Depletion Depletion mode when mode when V_{gs} is equal to is equal to V_t (c) Inversion Inversion mode when mode when V_{gs} is greater than is greater than V_t





4. What are the three regions of operation of a MOS transistor?

Ans: The three regions are: : The three regions are: Cut-off region: This is essentially the accumulation mode, where there is no effective flow of current between the source and drain. Non-saturated region saturated region: This is the active, active, linear or weak inversion region, where the drain current is dependent on both the gate and drain voltages. Saturated region: This is the strong inversion region, where the drain current is independent of the drain drain current is independent of the drain-to-source voltage but urce voltage but depends on the gate voltage.

 5. Determine the region of operation (Cut off, Linear, Saturation, Vel. saturation) in the following configurations. You may assume that all transistors have identical sizes. $V_{DD} = 2.5V$. Explain your reasoning, and show your derivations if needed .



•

    

6. How does Increasing W of devices affect its resistance, Gate capacitance and transconductance ?

decreases the resistance; allows more current to flow

A resistor: $R_n = \frac{1}{\mu_n C_{ox} (V_{GS} - V_{Tn})} \left(\frac{L}{W} \right)$

- (among other things ...) Increasing W decreases the resistance; allows more current to flow

Oxide capacitance $C_{ox} = \epsilon_{ox} / t_{ox}$ [F/cm²]


Transconductance $\beta_n = \mu_n C_{ox} \left(\frac{W}{L} \right) = K'_n \left(\frac{W}{L} \right)$

Gate capacitance $C_G = C_{ox} WL$ [F]


7. What is transconductance of a MOS transistor? Explain its role in the operation of the transistor.

Ans: Trans-conductance is represented by the change in drain current for change in gate voltage for constant value of drain voltage. This parameter is somewhat similar to β , the current gain of bipolar junction transistors. The Answer to the Questions of Lec Answer to the Questions of Lec-4 Ajit Pal, IIT Kharagpur the current gain of bipolar junction transistors. The following equation shows the dependence of on various parameters. As MOS transistors are voltage controlled devices, this parameter plays an important role in identifying the efficiency of the MOS transistor.

 
8. Explain the behaviour of a nMOS transistor as a switch.
9. Explain the behaviour of a pMOS transistor as a switch.
10. How one nMOS and one pMOS transistor are combined to behave like an ideal switch.
11. The input of a lightly loaded transmission gate is slowly changes from HIGH level to LOW level. How the currents through the two transistors vary?
12. . How its ON-resistance of a transmission gate changes as the input varies from 0 V to Vdd, when the output has a light capacitive load.
13. Draw stick digial/layout for 2-INPUT AND?



 14. Mark or point to the active, via/contact , M1, poly , NWELL IN THE FIGURE BELOW



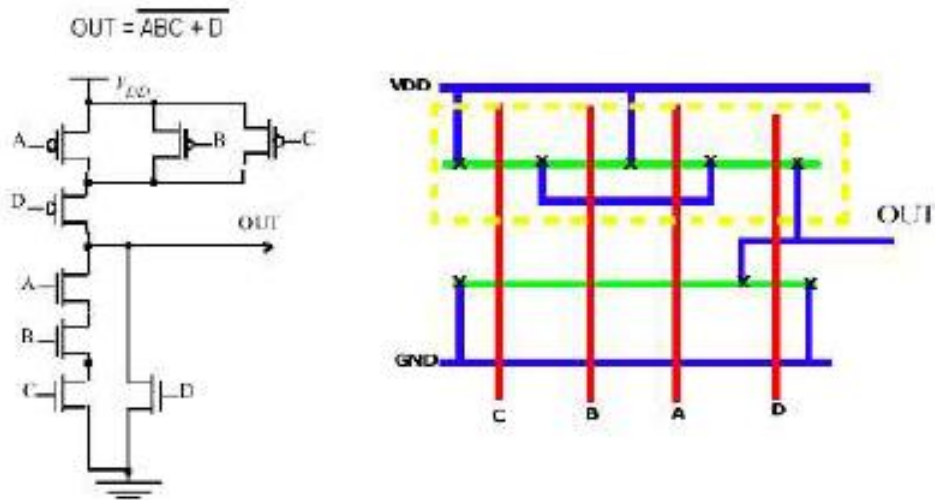15. Draw schematic and stick diagram for $Out = (ABC + D)'$



16. What is the difference between Average, maximum and instantaneous power?

See slide notes for answer

17. Q4. Why leakage power dissipation has become an important issue in deep submicron technology? What are the main factors that affects leakage ?


See slide notes for answer

Ans: In deep submicron technology deep submicron technology the leakage component the leakage component becomes a significant percentage of the total power and the leakage current increases at a

faster rate than dynamic power amic power in new technology generations. That is why the leakage pow generations. That is why the leakage power has become an important issue.

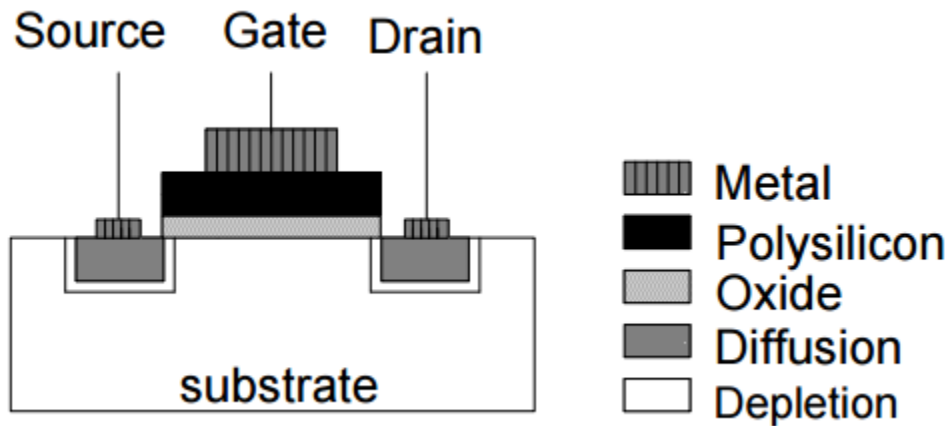18. Show the basic structure of a MOS transistor.

Ans: The basic structure of a MOS transistor is given below. On a lightly doped substrate of silicon two islands of diffusion regions called as source and drain, of opposite polarity of that of the substrate, are created. Between these two regions, a thin insulating layer of silicon dioxide is formed and on top of this a conducting material made of poly-silicon or metal called gate is deposited.





19. What are the commonly used conducting layers used in IC fabrication?

Ans: Fabrication involves fabrication of Fabrication involves fabrication of patterned laye attened layers of the rs of the three conducting materials: metal, poly-silicon silicon and diffusion by using a series of photolithographic techniques and chemical processes involving oxidation of silicon, diffusion of impurities into the silicon and deposition and etching of aluminum or Ajit Pal, IIT Kharagpur polysilicon polysilicon on the silicon to provide interconnectio on the silicon to provide interconnection

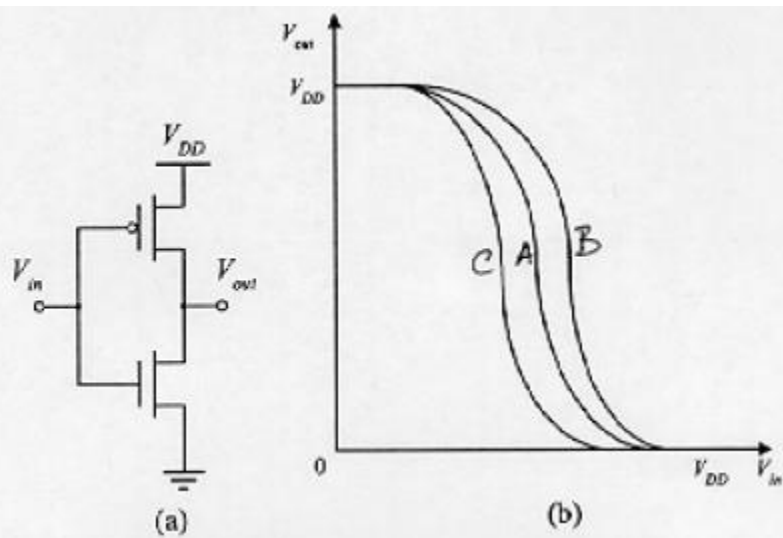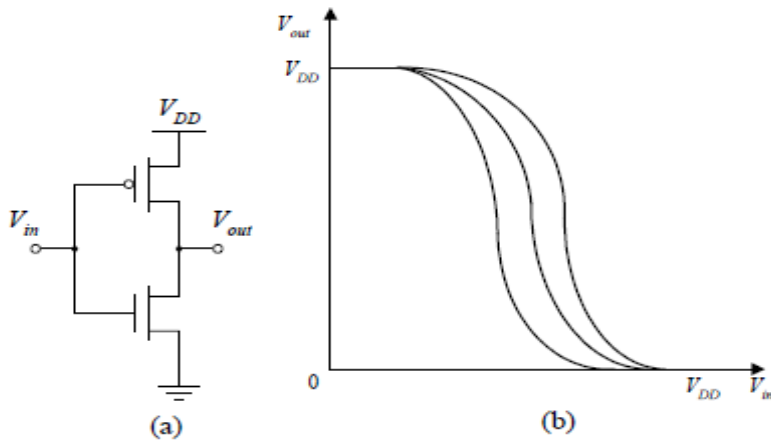20. Consider the CMOS inverter from below. If the NMOS transistor has channel width W_n and the PMOS transistor has channel width, W_p , label the voltage transfer characteristics from FIG. 2.b that correspond to following device sizes:

- A: $W_n = 5\mu\text{m}$, $W_p = 5\mu\text{m}$
- B: $W_n = 1\mu\text{m}$, $W_p = 5\mu\text{m}$
- C: $W_n = 5\mu\text{m}$, $W_p = 1\mu\text{m}$



Maximum, symmetrical margins $\Rightarrow V_M = \frac{V_{DD1} + V_{DD2}}{2}$

$$V_M = 1V$$

$$\frac{W_{p2}}{W_{n2}} = \frac{K_n' V_{DSATn} (V_M - V_{TN} - V_{DSATn}/2)}{K_p' V_{DSATp} (V_{DD} - V_M + V_{TP} + V_{DSATp}/2)} = \left(\begin{array}{l} \text{Both} \\ \text{transistors} \\ \text{in vel.} \\ \text{saturation} \end{array} \right)$$


$$= \frac{115\mu}{30\mu} \frac{0.6}{1} \frac{0.3}{0.6} = 1.15$$

$$W_{p2} = W_{n2} \times 1.15 = 5.75\mu m$$

$$W_{p2} = 5.75\mu m$$

 21. A CMOS inverter with supply voltage $V_{DD1} = 2V$, has to interface to a second CMOS inverter with $V_{DD2} = 2.5V$ supply, as shown below

The transistor widths of the second inverter W_{n2} , W_{p2} , should be determined to assure reliable interfacing, since the high output voltage level of the first inverter is $V_{OH1} = 2V$. If $W_{n2} = 5\mu m$, determine the value of W_{p2} , such that these inverters are interfaced with maximum and symmetrical noise margins.



Maximum, symmetrical margins $\Rightarrow V_{M} = \frac{V_{OH1} + V_{OL1}}{2}$

$V_{M} = 1V$

$$\frac{W_{p2}}{W_{n2}} = \frac{K_n' V_{DSATn} (V_{M} - V_{Tn} - V_{DSATn}/2)}{K_p' V_{DSATp} (V_{DD} - V_{M} + V_{Tp} + V_{DSATp}/2)} = \left(\text{Both transistors in vel. saturation} \right)$$

$$= \frac{115\mu}{30\mu} \frac{0.6}{1} \frac{0.3}{0.6} = 1.15$$

$$W_{p2} = W_{n2} \times 1.15 = 5.75\mu m$$


$W_{p2} = 5.75\mu m$

22. The inverter from FIG. below . has $W_n = 1\mu m$ and $W_p = 2.5\mu m$. $V_{DD} = 2.5V$.

Determine the value of V_{OH} . Assume that the PMOS transistor operates in triode region and

$$\left| \frac{V_{DS}}{2} \right| \ll |V_{GS} - V_T|$$

 , Determine V_{OH} also the value of V_{OL} .



$$I_D = k' \frac{W_P}{L_P} \left[(V_{GS} - V_{TP}) V_{DS} - \frac{V_{DS}^2}{2} \right] \approx$$

$$\approx k' \frac{W_P}{L_P} (V_{GS} - V_{TP}) V_{DS} ; V_{DS} = V_{OH} - V_{DD}$$

$$V_{OH} = R \cdot I_D = R \cdot k' \frac{W}{L} \cdot (V_{GS} - V_{TP}) \cdot (-V_{DD} + V_{OH})$$

$$V_{OH} = \frac{R k' \frac{W}{L} (V_{GS} - V_{TP}) V_{DD}}{1 - R k' \frac{W}{L} (V_{GS} - V_{TP})} = 2.16 \text{ V}$$

$$V_{OL} = 0 \text{ V} ; \text{ PMOS is OFF}$$

$$V_{OH} = 2.16 \text{ V}$$

$$V_{OL} = 0 \text{ V}$$

FIG. 4 CMOS inverter with resistive load

FORMULAS AND EQUATIONS

Diode

$$I_D = I_S(e^{V_D/\phi_T} - 1) = Q_D/\tau_T$$

$$C_j = \frac{C_{j0}}{(1 - V_D/\phi_0)^m}$$

$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1 - m)} \times [(\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m}]$$

MOS Transistor

$$V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$

$$I_D = \frac{k'_n W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \text{ (sat)}$$

$$I_D = v_{sat} C_{ox} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right) (1 + \lambda V_{DS}) \text{ (velocity sat)}$$

$$I_D = k'_n \frac{W}{L} \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right) \text{ (triode)}$$

$$I_D = I_S e^{\frac{V_{GS}}{n k T/q}} \left(1 - e^{-\frac{V_{DS}}{k T/q}} \right) \text{ (subthreshold)}$$

Deep Submicron MOS Unified Model

$$I_D = 0 \text{ for } V_{GT} \leq 0$$

$$I_D = k' \frac{W}{L} \left(V_{GT} V_{min} - \frac{V_{min}^2}{2} \right) (1 + \lambda V_{DS}) \text{ for } V_{GT} \geq 0$$

$$\text{with } V_{min} = \min(V_{GT}, V_{DS}, V_{DSAT})$$

$$\text{and } V_{GT} = V_{GS} - V_T$$

MOS Switch Model

$$R_{eq} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$

Inverter

$$V_{OH} = f(V_{OL})$$

$$V_{OL} = f(V_{OH})$$

$$V_M = f(V_M)$$

$$t_p = 0.69 R_{eq} C_L = \frac{C_L (V_{swing}/2)}{I_{avg}}$$

$$P_{dyn} = C_L V_{DD} V_{swing} f$$

$$P_{stat} = V_{DD} I_{DD}$$

Static CMOS Inverter

$$V_{OH} = V_{DD}$$

$$V_{OL} = GND$$

$$V_M \approx \frac{r V_{DD}}{1 + r} \text{ with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$\text{with } g \approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69 C_L \left(\frac{R_{eqn} + R_{eqp}}{2} \right)$$

$$P_{av} = C_L V_{DD}^2 f$$

Interconnect

$$\text{Lumped RC: } t_p = 0.69 RC$$

$$\text{Distributed RC: } t_p = 0.38 RC$$

RC-chain:

$$\tau_N = \sum_{i=1}^N R_i \sum_{j=i}^N C_j = \sum_{i=1}^N C_i \sum_{j=1}^i R_j$$

Transmission line reflection:

$$\rho = \frac{V_{refl}}{V_{inc}} = \frac{I_{refl}}{I_{inc}} = \frac{R - Z_0}{R + Z_0}$$

Explain bottom-up design methodology.

What is design flow?

What process is called clock tree synthesis?

What is the essence of cell-based design?

What process is called global routing?

What is the essence of full-custom design?

What is characterization?

What are the basic steps of digital design?

What is logic simulation?

What is symbol creation?

What changes do new design challenges require?

What steps are required after completing physical synthesis?

Give an example of intra-layer design rule.

What are the basic design matrixes?

How are the parameters of physical structures of standard I/O cells selected?

What are the advantages of Flip-Chip technology?

What are the trends of clock frequency related to IC evolution?

In each IC Component there are three Types of cells , what are they ?

- **Input/Output (I/O) Cells**
- **Digital Standard Cells**
- **Intellectual Property (IP) Blocks**

Which device passes good 1 and which device passes a good 0 ? Why ?

Derive the current equation for the NMOS transistor in linear region giving that :

- $Q=CV$
- $V=V_{gs}-V_t$
- $I=Dq/dt$

S

$i = \frac{dq}{dt} = \frac{dQ}{dt}$

$Q = C \cdot V = \epsilon_{ox} \cdot \frac{W \cdot L}{t_{ox}} \cdot (V_{GS} - V_t)$

$Q = \frac{\epsilon_{ox}}{t_{ox}} \cdot W \cdot L \cdot (V_{GS} - V_t)$

$t = \frac{L}{v} = \frac{L}{\mu_n \cdot E} = \frac{L}{\mu_n \cdot \frac{V_{DS}}{L}} = \frac{L^2}{\mu_n \cdot V_{DS}}$

$i_D = \mu_n \cdot \frac{\epsilon_{ox}}{t_{ox}} \cdot \frac{W}{L} \cdot (V_{GS} - V_t) \cdot V_{DS}$ small V_{DS} , $V_{GS} > V_t$

$i_D = g \cdot V_{DS}$

$Q = C \cdot V = \epsilon_{ox} \cdot \frac{W \cdot L}{t_{ox}} \cdot (V_{GS} - V_t - \frac{1}{2} V_{DS})$

$t = \frac{L^2}{\mu_n \cdot V_{DS}}$

$i_{DS} = \mu_n \frac{\epsilon_{ox}}{t_{ox}} \cdot \frac{W}{L} \left[V_{GS} - V_t - \frac{1}{2} (V_{GS} - V_t) \right] (V_{GS} - V_t)$


$i_{DS} = \frac{1}{2} \mu_n \cdot \frac{\epsilon_{ox}}{t_{ox}} \cdot \frac{W}{L} (V_{GS} - V_t)^2$

Design Matrics used to How to evaluate performance of a digital circuit (gate, block, ...)?





- Area/Cost

- Reliability
- Scalability
- Speed (delay, operating frequency)
- Power dissipation
- Energy to perform a function

 
Identify where the NMPS/PMOS REGION (Linear, Sat)



What is the output?

    

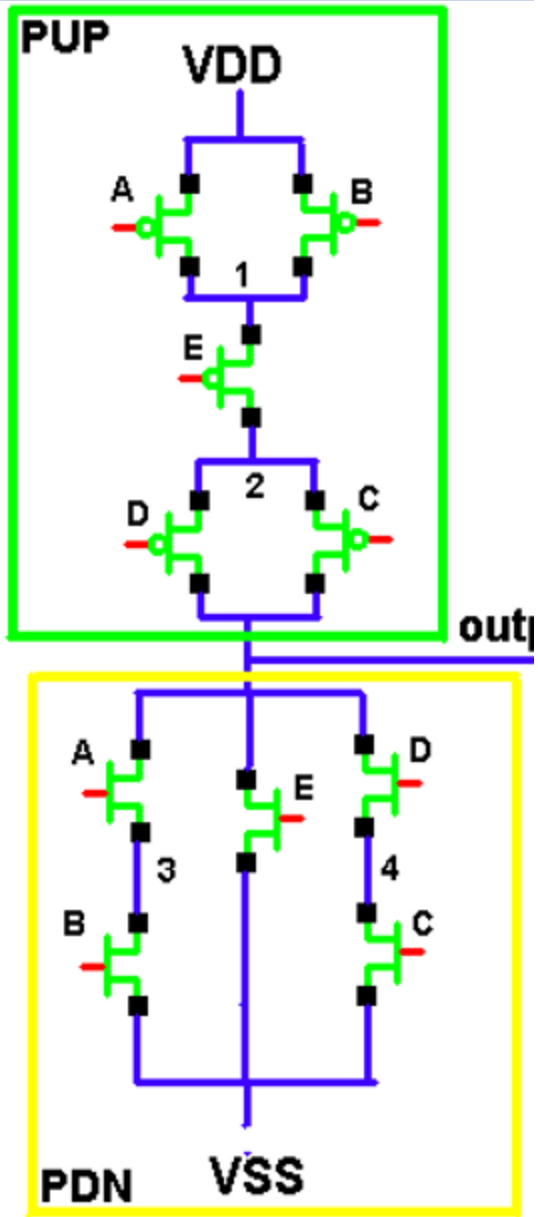What is the logic function for this below circuit? Draw stick diagram :




What are the input files of transistor level simulation?


What are the Levels of Design ?

- What is technology Scaling, how does it affect functions per chip; chip cost and area ?


- Cmos transistor structure

 


Physical structure

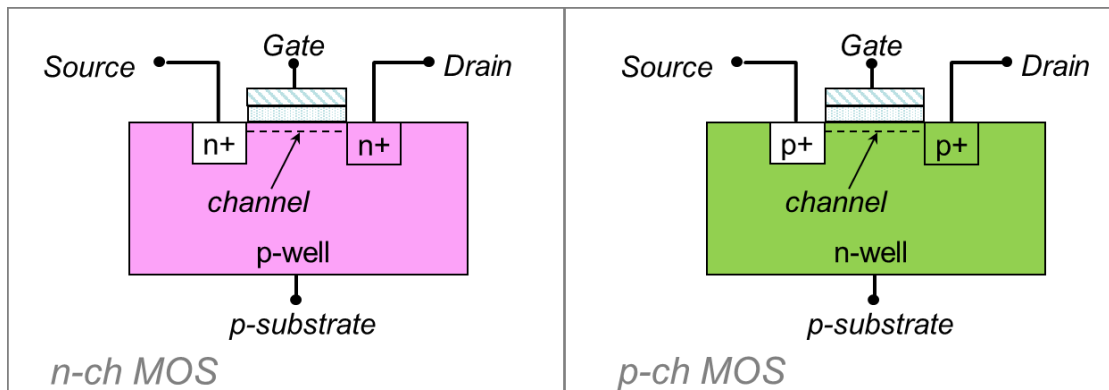


Capacitance of the MOS Transistor

 


Difference between Die and Package ?

 

IC Component Types

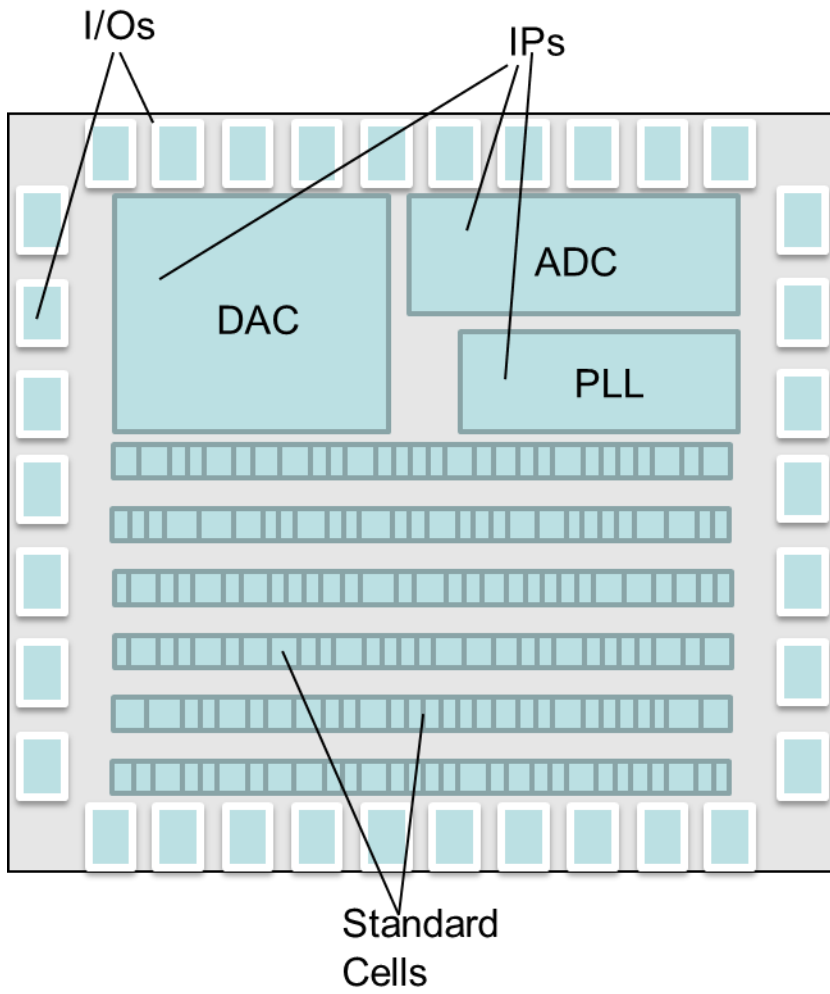

The MOS I-V characteristics

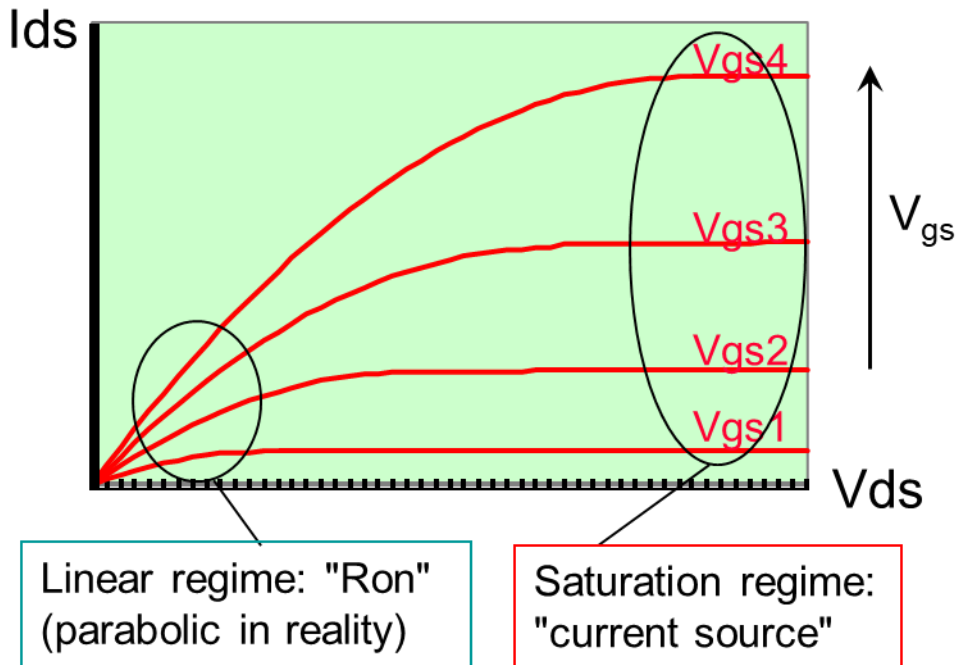


The MOS transistor models

- The simplest model:
 - Cut-off: $I_{ds} = 0$ for $|V_{gs}| < |V_t|$
 - Linear: $I_{ds} = K/2 * [2*(V_{gs}-V_t)*V_{ds} - V_{ds}^2]$ for $|V_{gs}-V_t| > |V_{ds}|$
 - Saturation: $I_{ds} = K/2 *(V_{gs}-V_t)^2$ for $|V_{ds}| > |V_{gs}-V_t|$
 - * where $K = \mu C_{ox} (W/L)$
- These equations can only model giant devices (long channel).
- Note that K is larger if C_{ox} is larger, fast transistors need large C_{ox}
- μ is the electron / hole mobility
 - e: 1300 ; h: 500 $cm^2/V \text{ sec}$, respectively, in bulk Silicon


What is the issue with pass gate ?

- Pass-gates and bi-directional n-ch MOS.
 - Transistors in pass-gates can operate in both directions. Therefore, the degradation occurs at both ends of the transistor.
 - When operating in bi-directional mode, %DIDL is usually greater than in forward operation only (~1.4x in P854 & P856).
- Special design guidelines for pass-gates:
 - Turn-on the p-ch one inversion before the n-ch (usually not practical)
 - Increase the NMOS channel length (some area and power penalty)

 


- **How to evaluate performance of a digital circuit (gate, block, ...)?**
 - **Area/Cost**
 - **Reliability**
 - **Scalability**
 - **Speed (delay, operating frequency)**
 - **Power dissipation**
 - **Energy to perform a function**
- **Lithography : is a basic method of IC fabrication process. Process is used to transfer patterns from masks to each layer of the IC on the surface of a wafer by employing a photosensitive, chemically resistant layer (photoresist).**

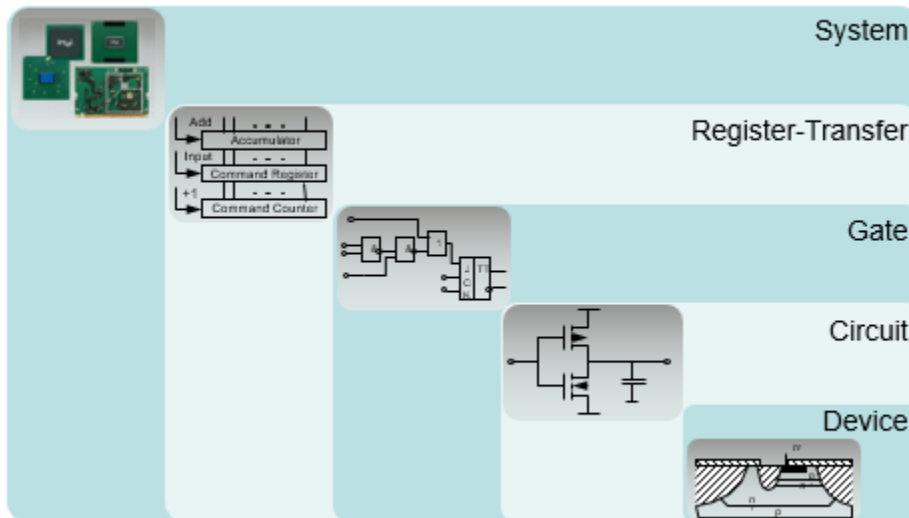There are 5 design levels, what are they ?



- **What is design Verification and what are the methods used for verification :**
 - is used to check if the design object produced by the design step is the same as the needed one
- **Methods:**
 - **Formal Verification**
 - This method mathematically proves that same design at different design levels has fully equivalent function
 - **Static Timing Analysis**
 - Path delay is calculated by summing delays of elements without simulation
 - **Simulation**
 - The behavior of object in time and space is reproduced
 - **Emulation**
 - Using device, which works as the system to be verified, submits test vectors, output signal checks
 - **Prototyping**
 - Building of hardware implementation of design and its testing

Definitions of Noise Margins

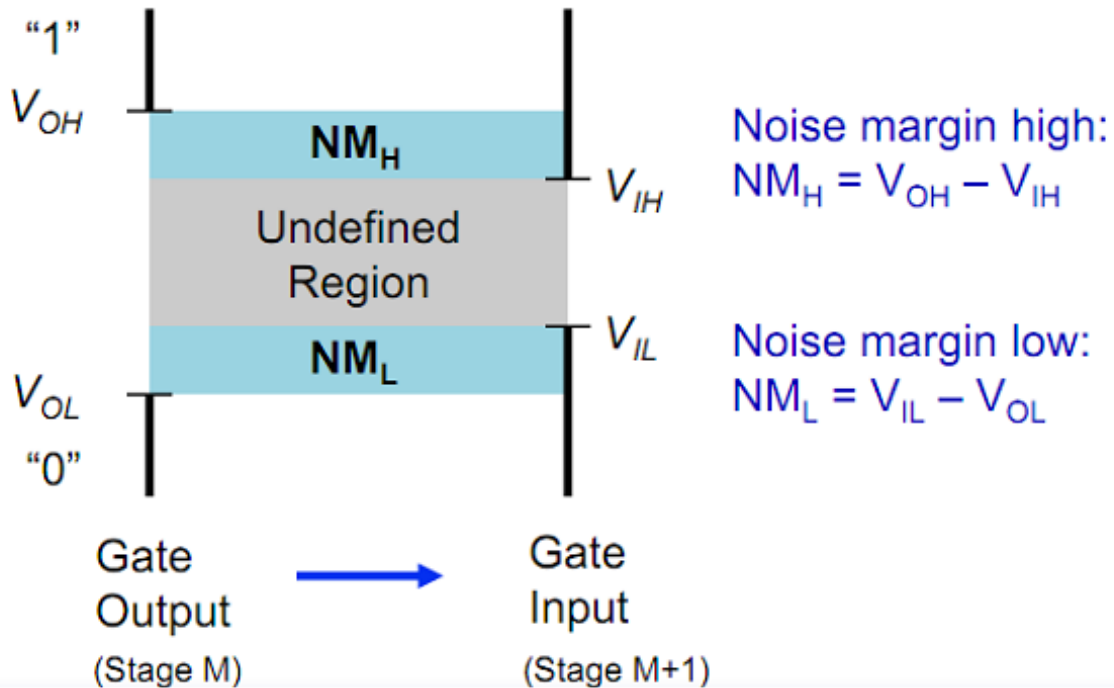

Design 2 bit full adder by :

- 1- Create truth table
- 2- Generate logic function
- 3- Draw transistor level
- 4- Simulate and verify functionality/timing diagram
- 5- Layout
- 6- Determine area

How does cell area affect power ?

Exam

- Allowed: One cheat sheet