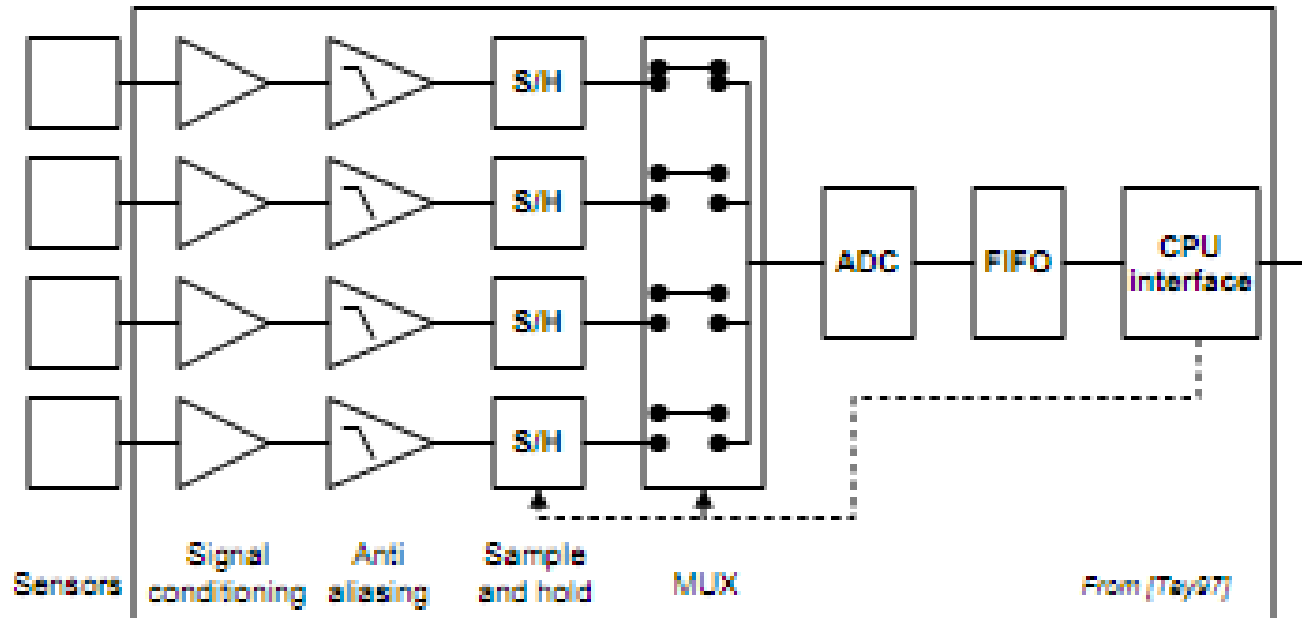



Data Acquisition I

- ▶ Architecture of DAQ systems
 - ▶ Signal conditioning
 - ▶ Aliasing
- 

Architecture of data acquisition systems





Signal conditioning

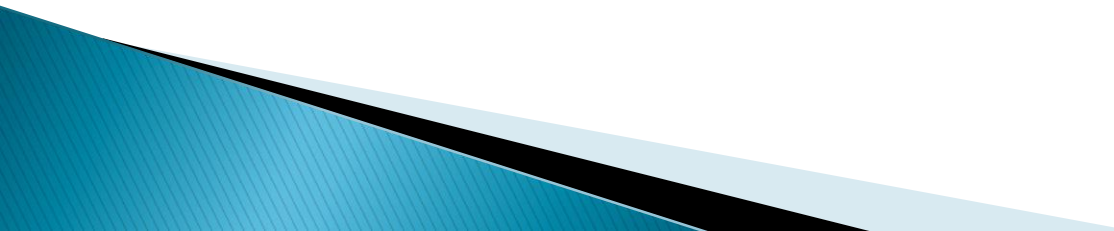- ▶ Instrumentation amplifiers
 - ▶ Filters
 - ▶ Integrators / differentiators
- 

Instrumentation amplifiers

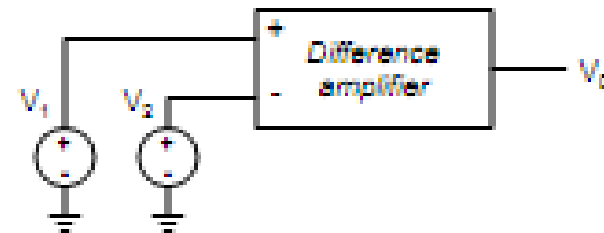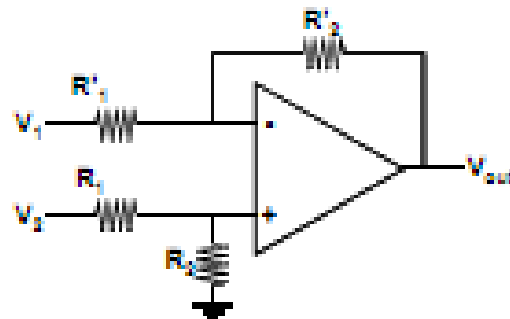
- Consider the difference amplifier we saw in the previous lecture



- We define **COMMON-MODE** and **DIFFERENCE-MODE** voltage as

$$V_{CM} = \frac{V_2 + V_1}{2}$$

$$V_D = V_2 - V_1$$

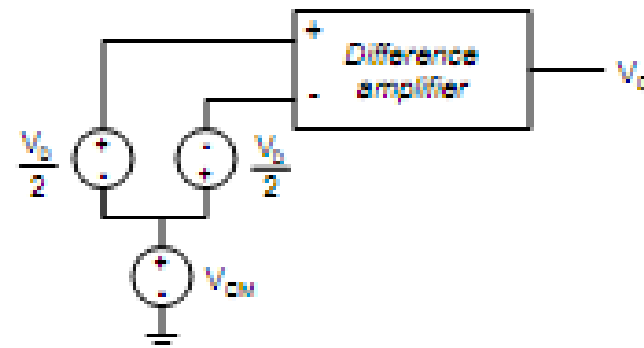

Instrumentation amplifiers

- As a result of a mismatch in the resistors ($R'_k \neq R_k$), the differential inputs may not have the same gain

$$\begin{aligned} V_o &= G(V_2 - V_1) \stackrel{R'_k \neq R_k}{=} G_2 V_2 - G_1 V_1 = G_2 \left(-\frac{V_D}{2} + V_{CM} \right) - G_1 \left(\frac{V_D}{2} + V_{CM} \right) = \\ &= -V_D \left(\frac{G_2 + G_1}{2} \right) + V_{CM} (G_2 - G_1) = -V_D G_D + V_{CM} G_{CM} \end{aligned}$$


- We define **COMMON-MODE REJECTION RATIO** as

$$CMRR = 20 \log_{10} \left(\frac{G_D}{G_{CM}} \right) = 20 \log_{10} \left(\frac{G_2 + G_1}{2(G_2 - G_1)} \right)$$

- CMRR is, in practice, a function of frequency, and its magnitude decreases with increasing frequency
- An additional shortcoming of the difference amplifier is its **LOW INPUT IMPEDANCE**


Instrumentation amplifiers

- ▶ The term INSTRUMENTATION AMPLIFIER is used to denote a difference amplifier with
 - High gain (INA2126)
 - Single-ended output
 - High input impedance
 - High CMRR
- ▶ High input impedance may be achieved by buffering the differential inputs
 - This solution, however, requires high CMRR both in the followers and in the final op-amp
 - Otherwise, since the input buffers have unity gain, all the CM rejection must come in the output op-amp, requiring precise resistor matching

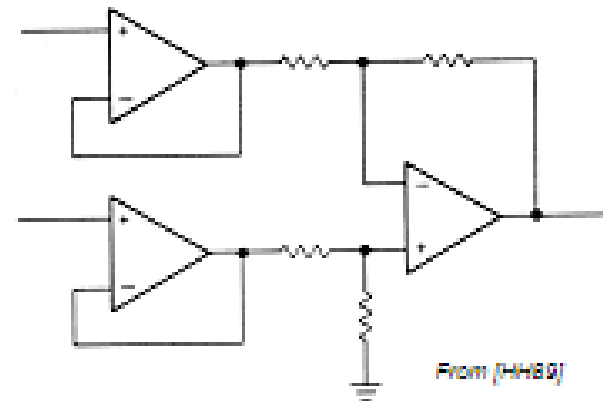


Common mode rejection ratio

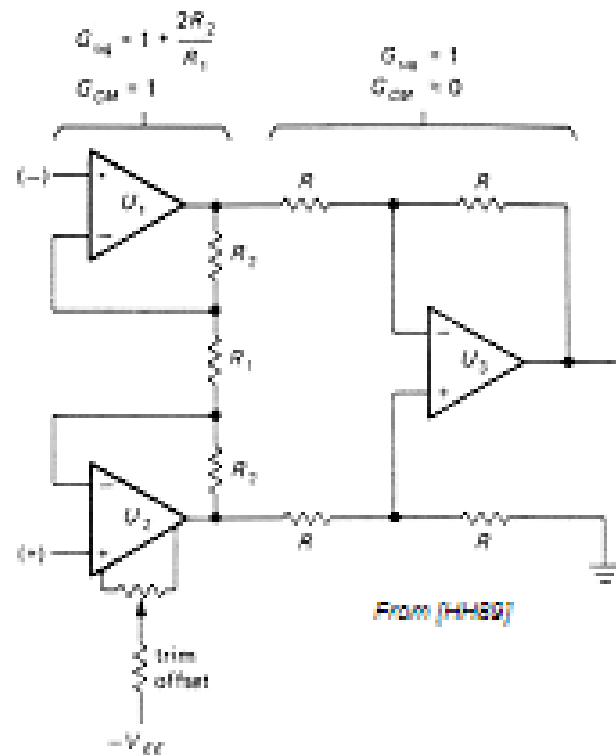
- ▶ A better solution is the “standard” instrumentation amplifier shown below
 - Input stage provides high GD and unity GCM
 - Close resistor (R_2) matching is NOT critical
 - As a result, the output op-amp (U_3) does not require exceptional CMRR and resistor matching in U_3 is not critical
 - Offset trimming can be done at one of the input op-amps



INA...

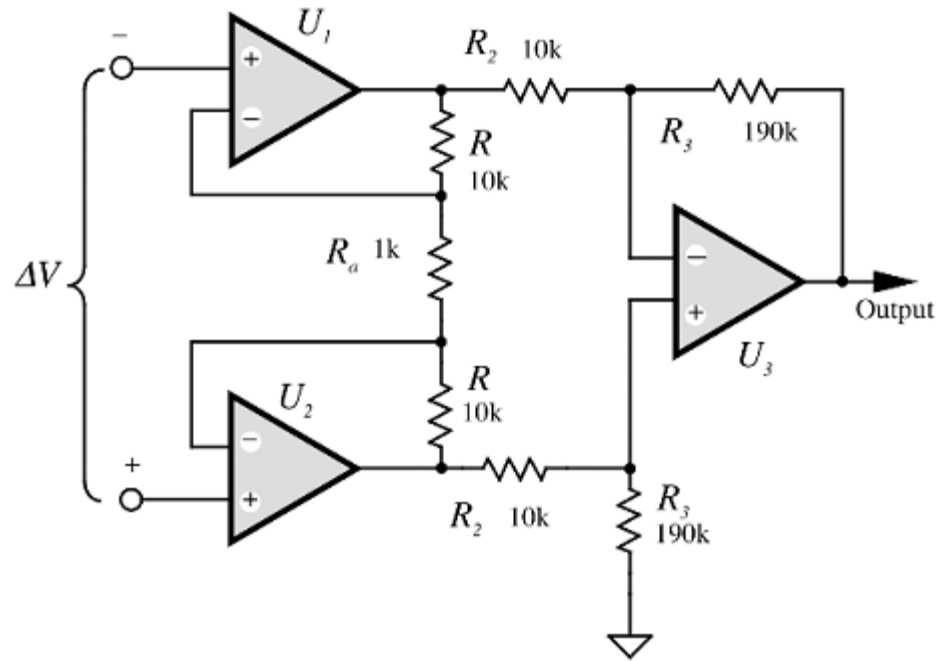

$$A = \left(1 + \frac{2R}{R_a}\right) \frac{R_3}{R_2}$$

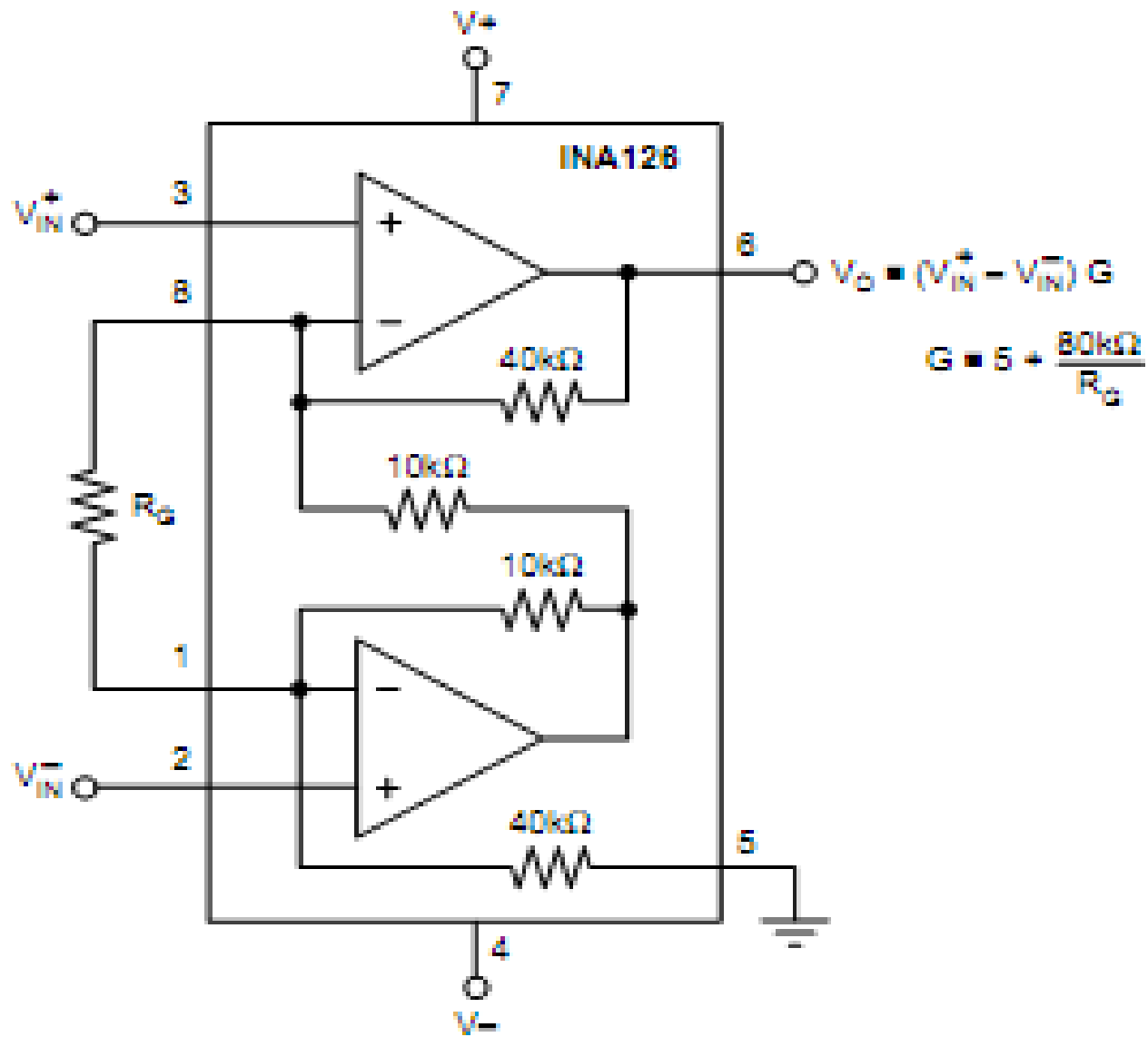

INA126.....




DESIRED GAIN (V/V)	R _G (Ω)	NEAREST 1% R _G VALUE
5	NC	NC
10	16k	15.8k
20	5333	5360
50	1779	1780
100	842	845
200	410	412
500	162	162
1000	80.4	80.6
2000	40.1	40.2
5000	16.0	15.8
10000	8.0	7.87


NC: No Connection.

APPLICATIONS

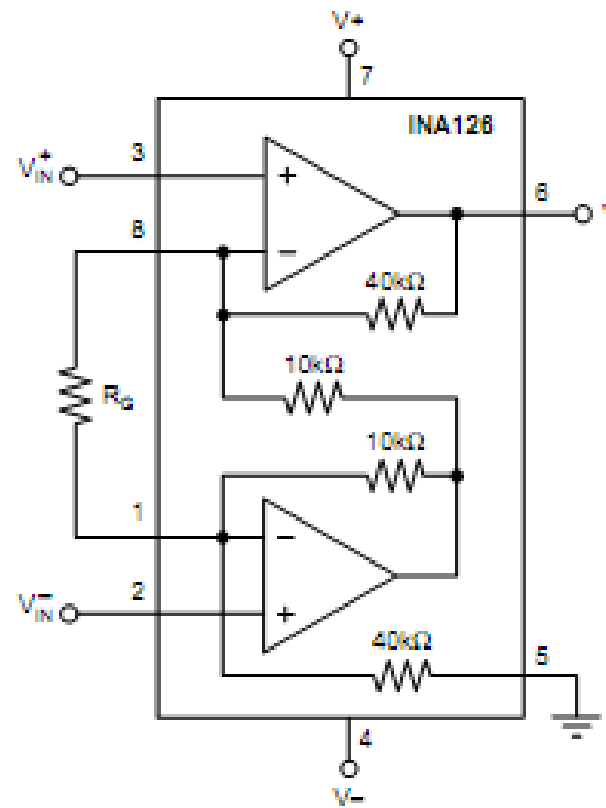- INDUSTRIAL SENSOR AMPLIFIER: Bridge, RTD, Thermocouple
- PHYSIOLOGICAL AMPLIFIER: ECG, EEG, EMG
- MULTI-CHANNEL DATA ACQUISITION
- PORTABLE, BATTERY OPERATED SYSTEMS



PIN CONFIGURATION (Single)

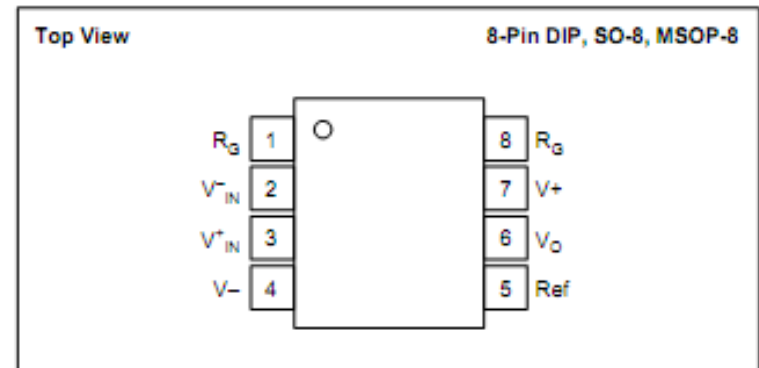


Filters

- ▶ Filters are used to remove unwanted bandwidths from a signal
- ▶ Filter classification according to implementation
 - Active filters include RC networks and op-amps
 - Suitable for low frequency, small signal
 - Active filters are preferred since avoid the bulk and non-linearity of inductors and can have gains greater than 0dB
 - However, active filters require a power supply
 - Passive filters consist of RCL networks
 - Simple, more suitable for frequencies above audio range, where active filters are limited by the op-map bandwidth
- ▶ Digital filters
 - DSP is beyond the scope of this course

Filters





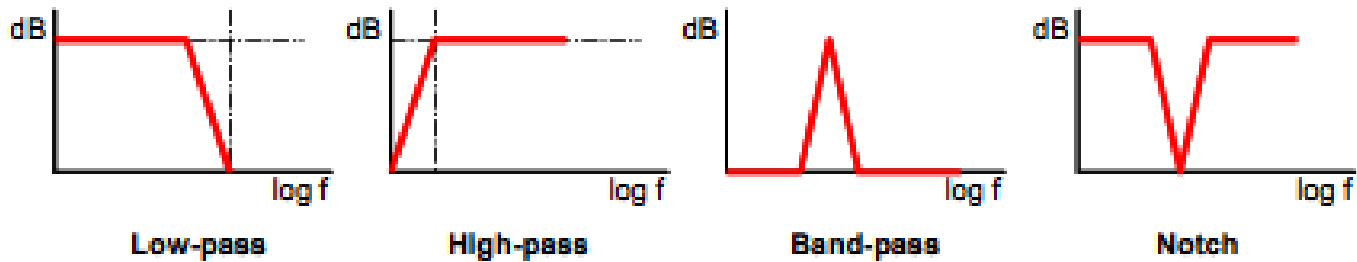
- ▶ Filter classification according to frequency response
 - Low-pass filter
 - High-pass filter
 - Band-pass filter
 - Band-stop (Notch)




Low- and high-pass filters

- Low pass filters

- High pass filters

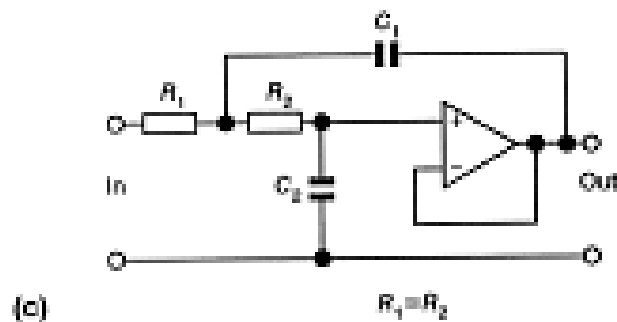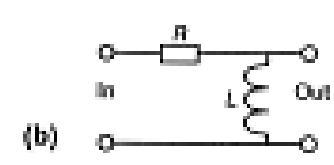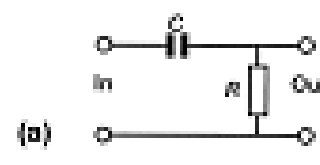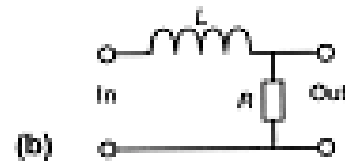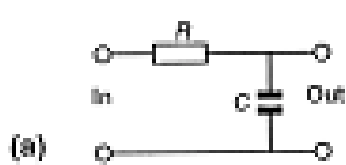

From [Ram96]

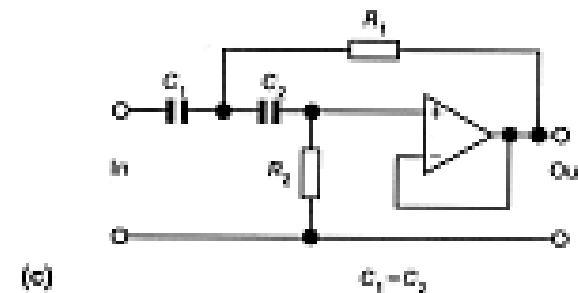


From [Ram96]

Band-pass and band-stop filters


■ Band-pass

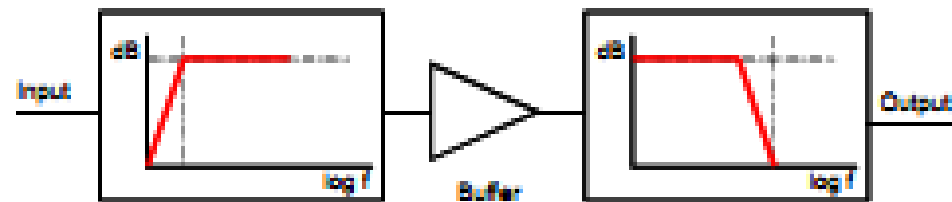- High-pass and low pass in series
 - High-pass should usually precede
 - Corner frequency of low-pass must then be higher
 - If these are passive filters they should be buffered in between




■ Band-stop

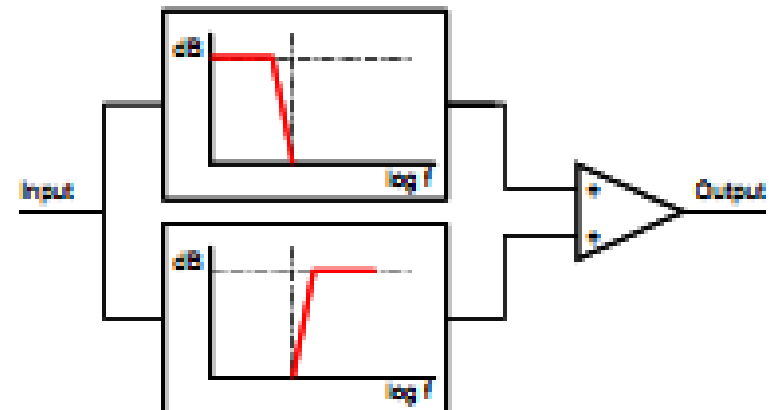- High-pass and low-pass in parallel followed by a summer
 - Corner frequency of high-pass must be higher




Types of Filters

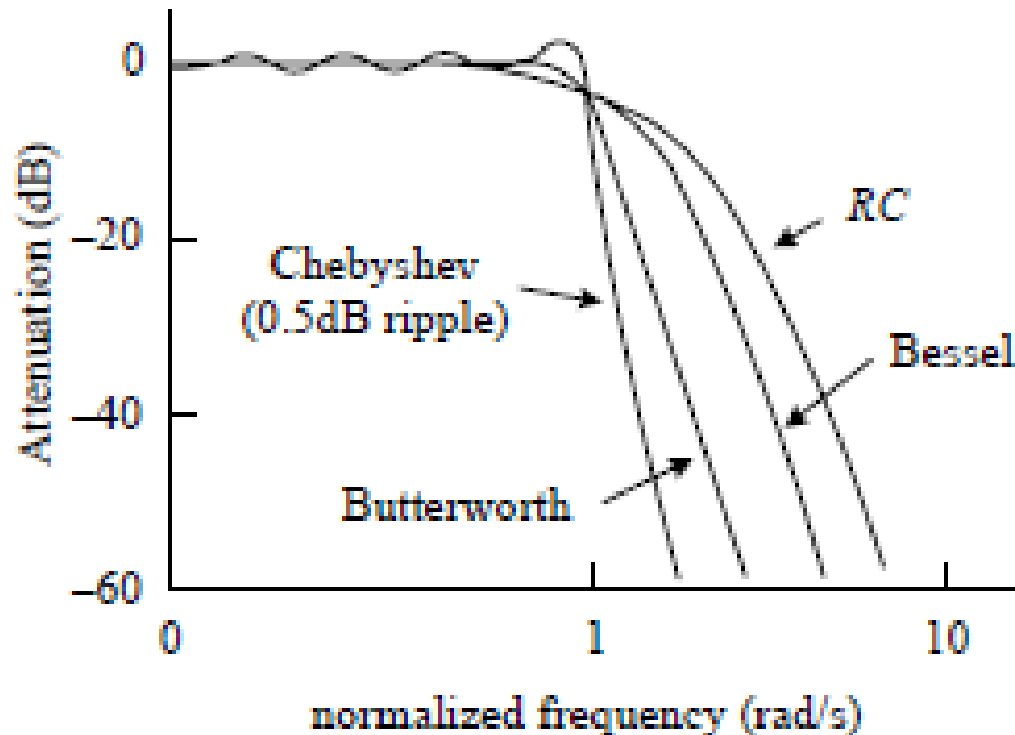
$$T(S) = \frac{V_{out}}{V_{in}} = \frac{N_m S^m + N_{m-1} S^{m-1} + \dots + N_1 S + N_0}{D_n S^n + D_{n-1} S^{n-1} + \dots + D_1 S + D_0}$$



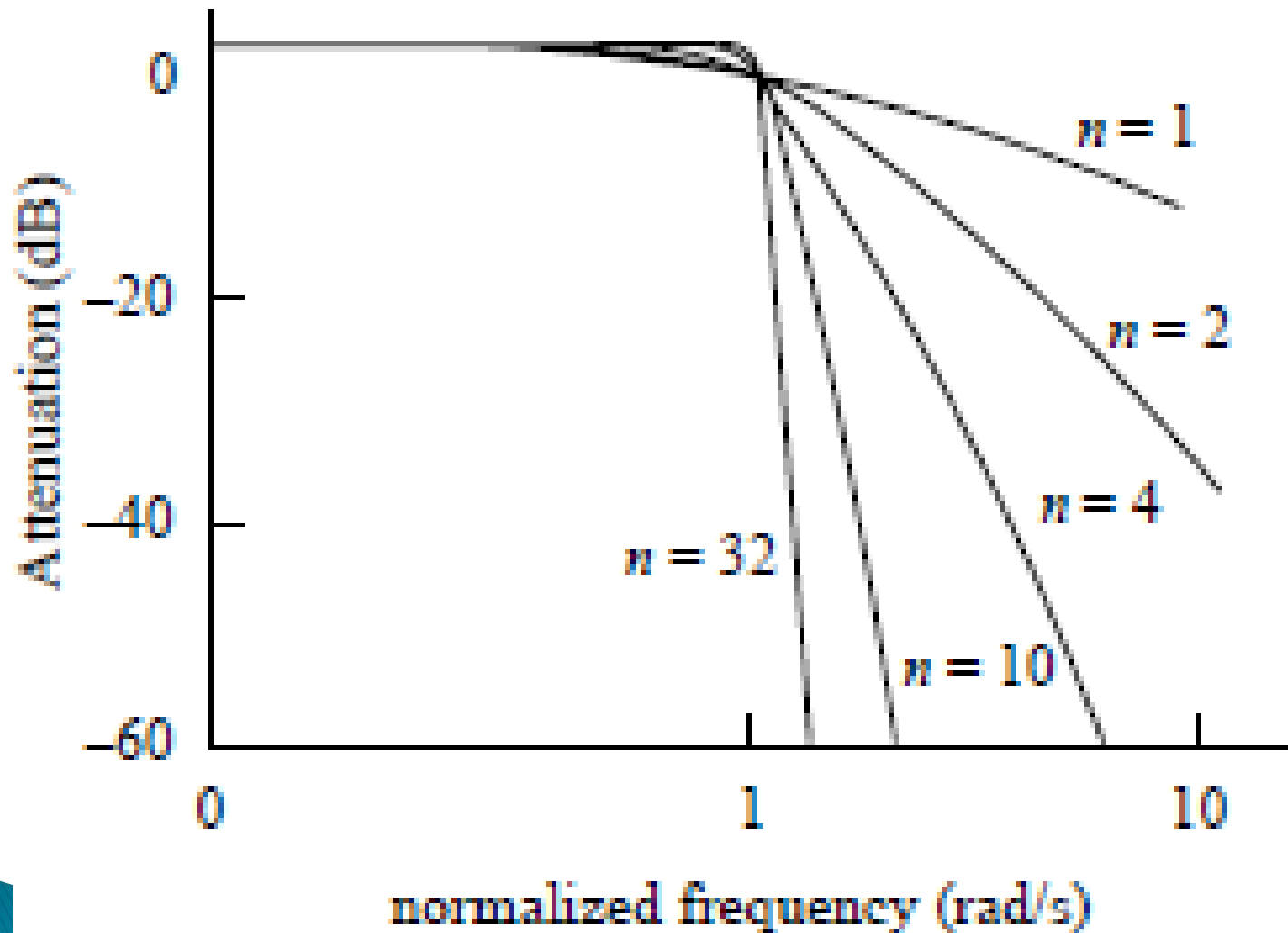
Normalized low-pass Butterworth filter reponse curves



Attenuation curves for Butterworth LPF

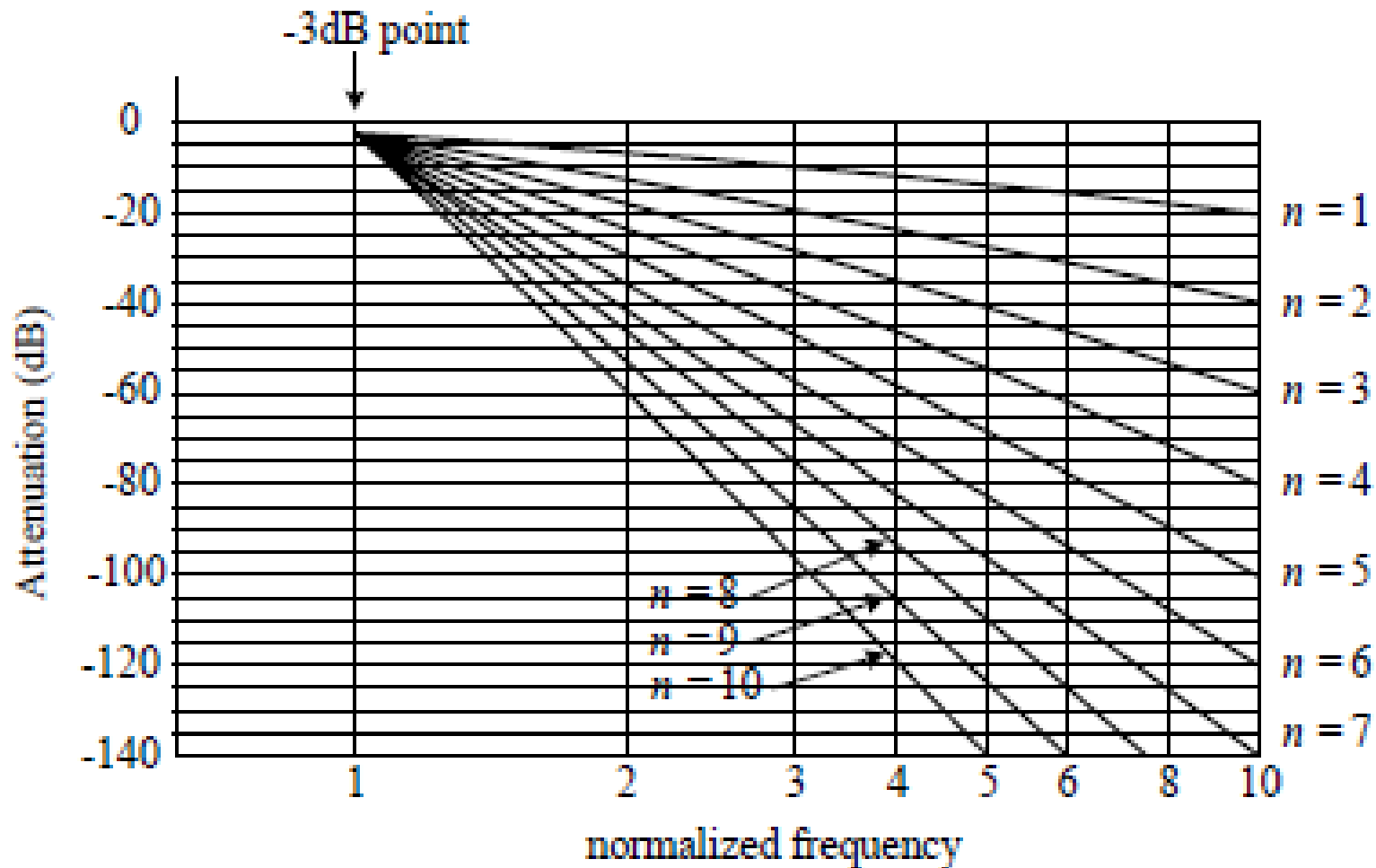

LC Low Pass Filter network

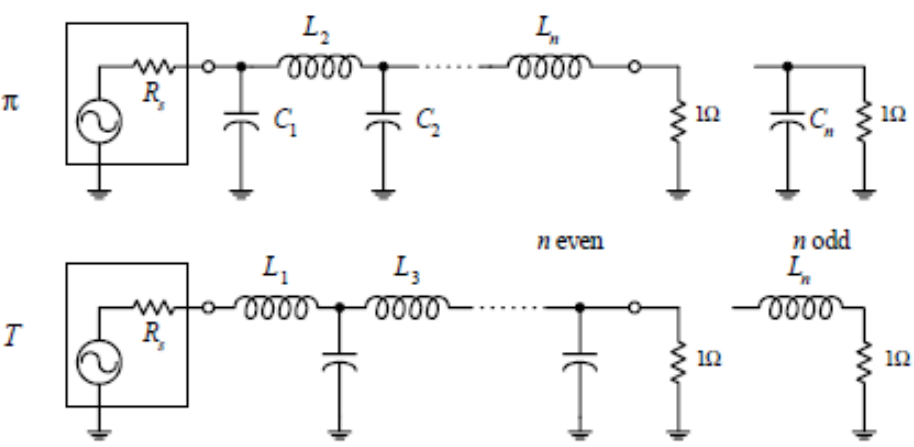



$\frac{\pi}{T}$	R_s ($1/R_s$)	C_1 (L_1)	L_2 (C_2)	C_3 (L_3)	L_4 (C_4)	C_5 (L_5)	L_6 (C_6)	C_7 (L_7)
2	1.000	1.4142	1.4142					
3	1.000	1.0000	2.0000	1.0000				
4	1.000	0.7654	1.8478	1.8478	0.7654			
5	1.000	0.6180	1.6180	2.0000	1.6180	0.6180		
6	1.000	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176	
7	1.000	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450

Note: Values of L_n and C_n are for a 1- Ω load and -3-dB frequency of 1 rad/s and have units of H and F. These values must be scaled down. See text.

Example

Suppose that you want to design a low-pass filter that has a $f_{3\text{dB}} = 3000$ Hz (attenuation is -3 dB at 3000 Hz) and an attenuation of -25 dB at a frequency of 9000 Hz—which will be called the *stop frequency* f_s . Also, let's assume that both the signal-source impedance R_s and the load impedance R_L are equal to 50Ω . How do you design the filter?


Step 1: Normalization

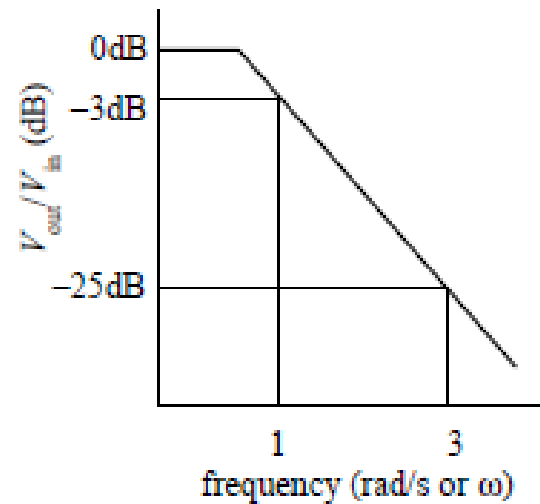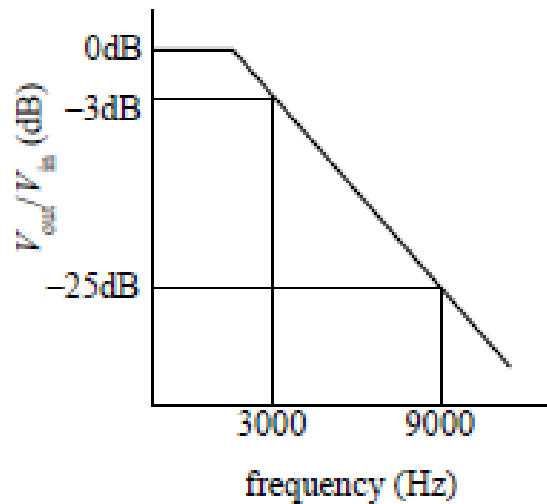

Step 2&3: Pick Response Curve and determine number of Poles

$n=3$ from the curve for Butterworth

Step 4: Create Normalized Filter

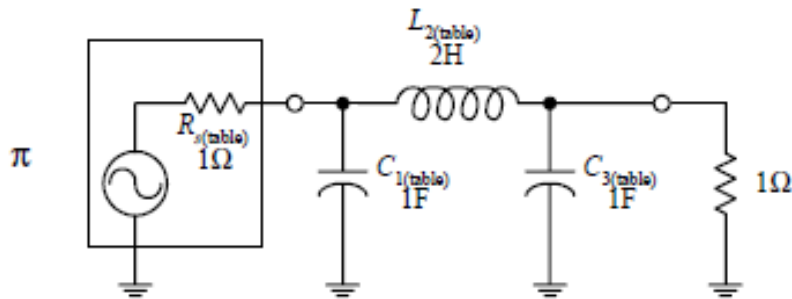


Step 5: Frequency and Impedance Scaling

$$L_{2(\text{actual})} = \frac{R_L L_{2(\text{table})}}{2\pi f_{3\text{dB}}} = \frac{(50\Omega)(2\text{H})}{2\pi(3000\text{Hz})} = 5.3\text{mH}$$


$$C_{1(\text{actual})} = \frac{C_{1(\text{table})}}{2\pi f_{3\text{dB}} R_L} = \frac{1\text{F}}{2\pi(3000\text{Hz})(50\Omega)} = 1.06\mu\text{F}$$
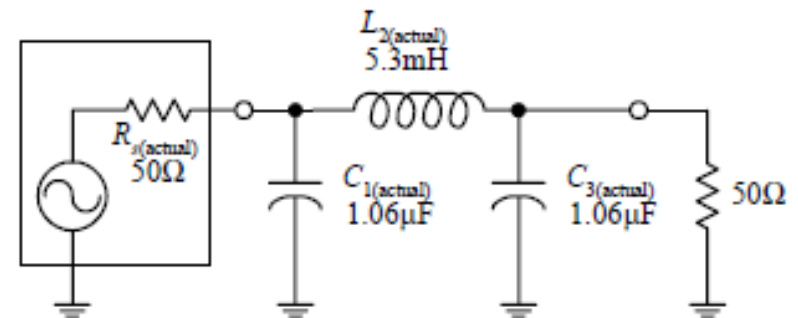
$$C_{3(\text{actual})} = \frac{C_{3(\text{table})}}{2\pi f_{3\text{dB}} R_L} = \frac{1\text{F}}{2\pi(3000\text{Hz})(50\Omega)} = 1.06\mu\text{F}$$




Active Filter Design

Basic two-pole section

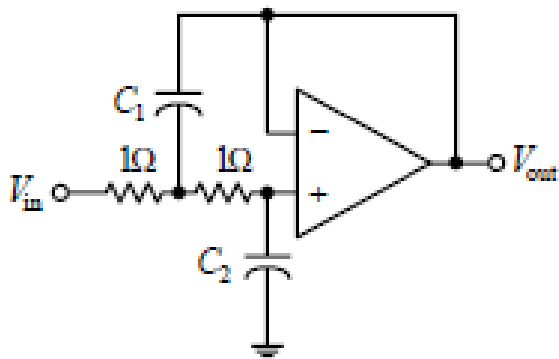

Basic three-pole section

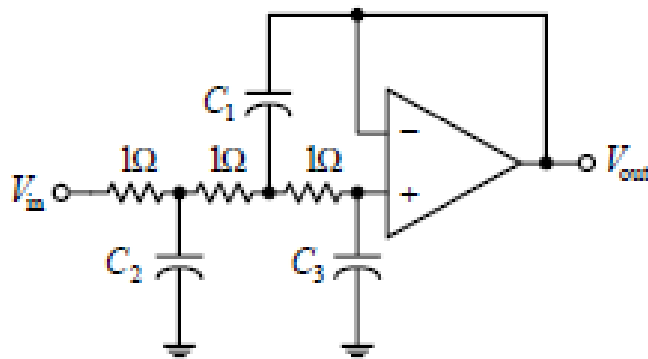

Normalized Curves



TABLE 8.2 Butterworth Normalized Active Low-Pass Filter Values

ORDER n	NUMBER OF SECTIONS	SECTIONS	C_1	C_2	C_3
2	1	2-pole	1.414	0.7071	
3	1	3-pole	3.546	1.392	0.2024
4	2	2-pole 2-pole	1.082 2.613	0.9241 0.3825	
5	2	3-pole 2-pole	1.753 3.235	1.354 0.3090	0.4214
6	3	2-pole 2-pole 2-pole	1.035 1.414 3.863	0.9660 0.7071 0.2588	
7	3	3-pole 2-pole 2-pole	1.531 1.604 4.493	1.336 0.6235 0.2225	0.4885
8	4	2-pole 2-pole 2-pole 2-pole	1.020 1.202 2.000 5.758	0.9809 0.8313 0.5557 0.1950	

Example



Suppose that you wish to design an active low-pass filter that has a 3-dB point at 100 Hz and at least 60 dB worth of attenuation at 400 Hz—which we'll call the *stop frequency* f_s .

Solution

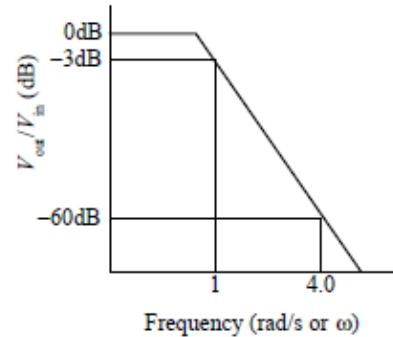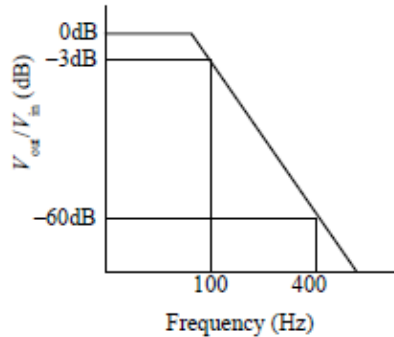

$$A_s = \frac{f_s}{f_{3dB}} = \frac{400 \text{ Hz}}{100 \text{ Hz}} = 4$$

$n=5$ from the curves

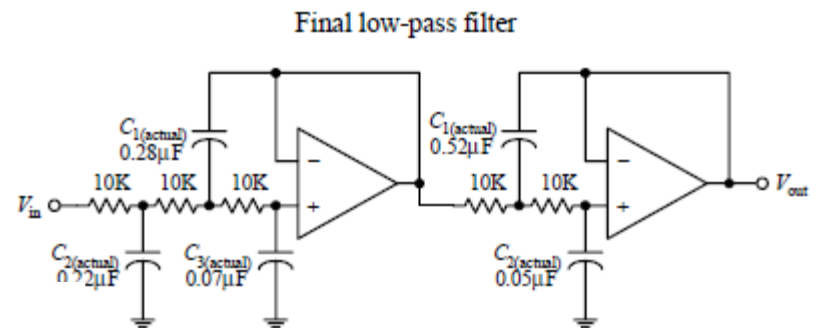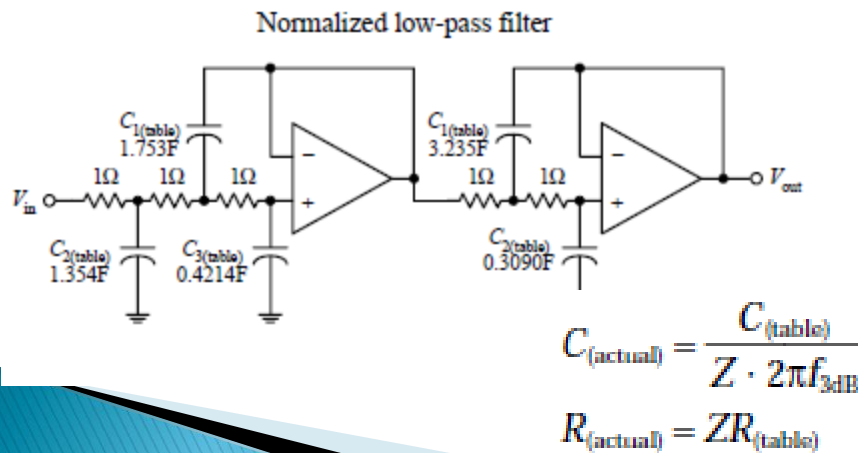


High Pass Filter –Passive–

Suppose that you want to design a high-pass filter that has an $f_{3dB} = 1000 \text{ Hz}$ and an attenuation of at least -45 dB at 300 Hz —which we call the *stop frequency* f_s . Assume that the filter is hooked up to a source and load that both have impedances of 50Ω and that a Butterworth response is desired


How do you design the filter?

Solution

Frequency Response Curve

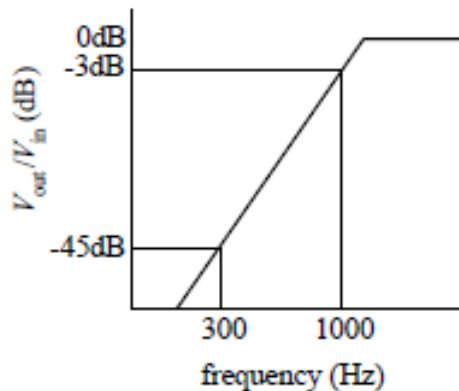

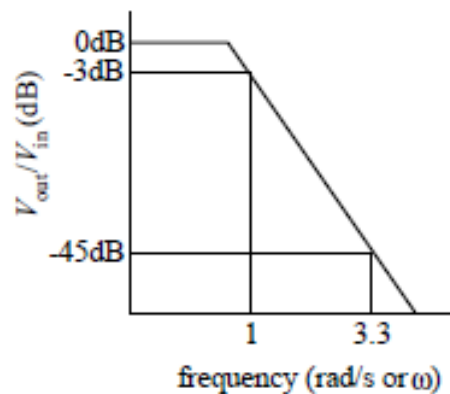Normalized translation to low-pass filter



$$A_s = \frac{f_{3dB}}{f_s} = \frac{1000 \text{ Hz}}{300 \text{ Hz}} = 3.3$$


To convert the low-pass into a high-pass filter, replace the inductors with capacitors that have value of $1/L$, and replace the capacitors with inductors that have values of $1/C$. In other words, do the following:

$$L_{2(transf)} = 1/C_{2(table)} = 1/1.6180 = 0.6180 \text{ H}$$


$$L_{4(transf)} = 1/C_{4(table)} = 1/1.6180 = 0.6180 \text{ H}$$

$n=5$ from the curves

Start with a "T" low-pass filter...

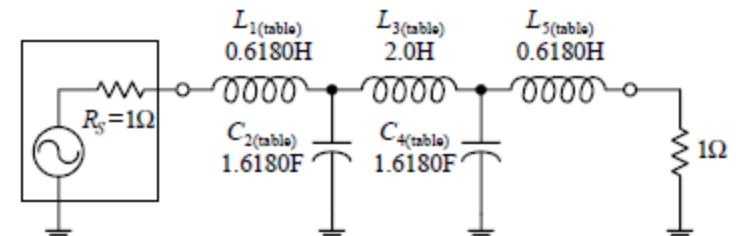

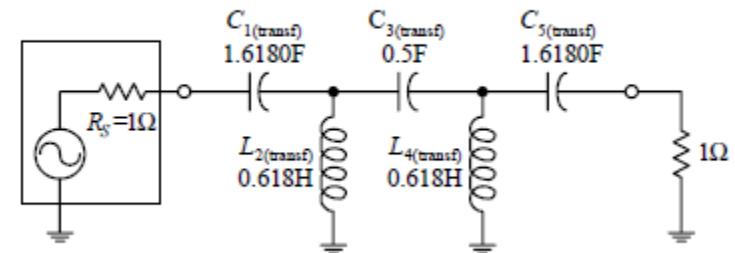Transform low-pass filter into a high-pass filter...



$$C_{1(transf)} = 1/L_{1(table)} = 1/0.6180 = 1.6180 \text{ F}$$

$$C_{3(transf)} = 1/L_{3(table)} = 1/2.0 = 0.5 \text{ F}$$

$$C_{5(transf)} = 1/L_{5(table)} = 1/0.6180 = 1.6180 \text{ F}$$

Now Scaling


Next, frequency and impedance scale to get the actual component values:

$$C_{1(\text{actual})} = \frac{C_{1(\text{trans})}}{2\pi f_{3\text{dB}} R_L} = \frac{1.618 \text{ H}}{2\pi(1000 \text{ Hz})(50 \Omega)} = 5.1 \mu\text{F} \quad L_{2(\text{actual})} = \frac{L_{2(\text{trans})} R_L}{2\pi f_{3\text{dB}}} = \frac{(0.6180 \text{ F})(50 \Omega)}{2\pi(1000 \text{ Hz})} = 4.9 \text{ mH}$$

$$C_{3(\text{actual})} = \frac{C_{3(\text{trans})}}{2\pi f_{3\text{dB}} R_L} = \frac{0.5 \text{ H}}{2\pi(1000 \text{ Hz})(50 \Omega)} = 1.6 \mu\text{F} \quad L_{4(\text{actual})} = \frac{L_{4(\text{trans})} R_L}{2\pi f_{3\text{dB}}} = \frac{(0.6180 \text{ F})(50 \Omega)}{2\pi(1000 \text{ Hz})} = 4.9 \text{ mH}$$

$$C_{5(\text{actual})} = \frac{C_{5(\text{trans})}}{2\pi f_{3\text{dB}} R_L} = \frac{1.618 \text{ H}}{2\pi(1000 \text{ Hz})(50 \Omega)} = 5.1 \mu\text{F}$$

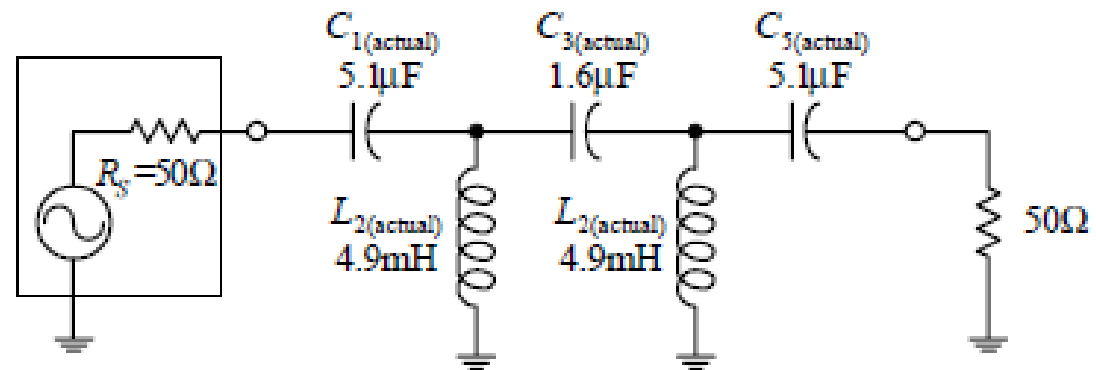Impedance and frequency scale high-pass filter to get final circuit




High Pass Filter–Active–

suppose


that you want to design a high-pass filter with a -3-dB frequency of 1000 Hz and 50 dB worth of attenuation at 300 Hz . What do you do?

$n=5$ from the curves


High-pass frequency response

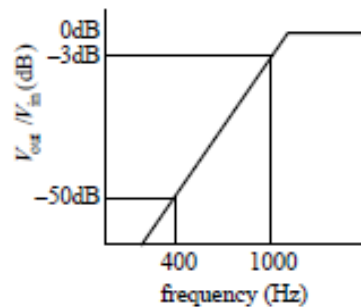

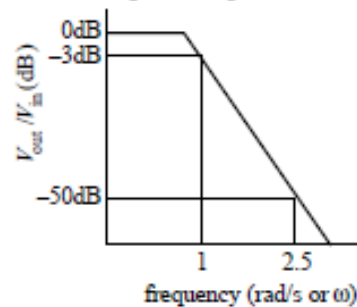Translation to normalized low-pass response




Normalized low-pass filter

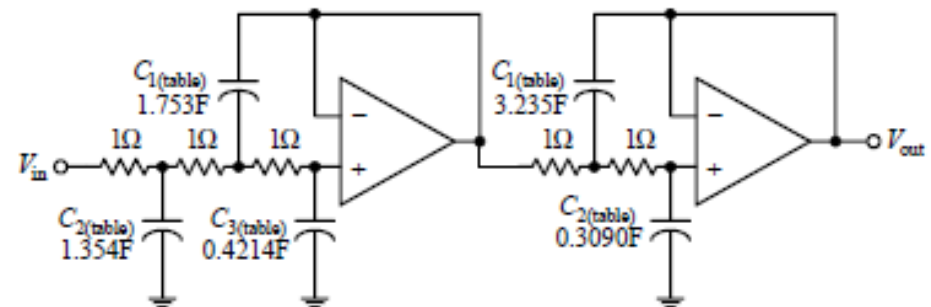

Next, the normalized low-pass filter must be converted into a normalized high-pass filter. To make the conversion, exchange resistors for capacitors that have values of $1/R\text{ F}$, and exchange capacitors with resistors that have values of $1/C\text{ }\Omega$.

Follow.....

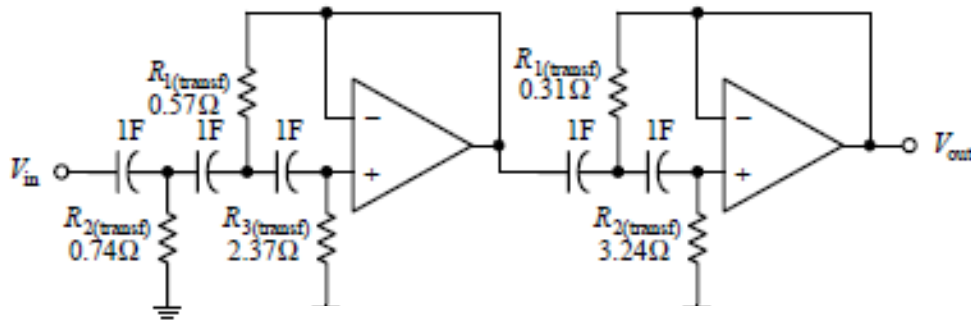Normalized high-pass filter (transformed low-pass filter)




$$C_{(\text{actual})} = \frac{C_{(\text{transf})}}{Z \cdot 2\pi f_{\text{dB}}}$$

$$R_{(\text{actual})} = Z R_{(\text{transf})}$$

let $Z = 10,000 \Omega$.

Final high-pass filter

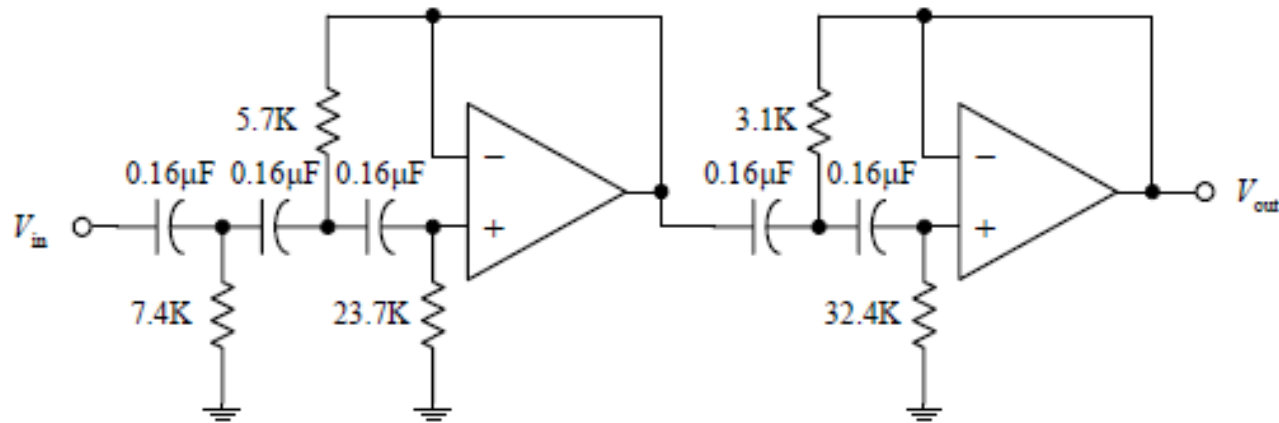

Bandpass Filter Design–Wide Band–Passive–



When is the filter wide band??

If f_2/f_1 is greater than 1.5,

Suppose that you want to design a bandpass filter that has -3 -dB points at $f_1 = 1000$ Hz and $f_2 = 3000$ Hz and at least -45 dB at 300 Hz and more than -25 dB at 9000 Hz. Also, again assume that the source and load impedances are both 50Ω and a Butterworth design is desired.

- Low-pass -3 dB at 3000 Hz
- -25 dB at 9000 Hz
- High-pass -3 dB at 1000 Hz
- -45 dB at 300 Hz

Bandpass Response Curve

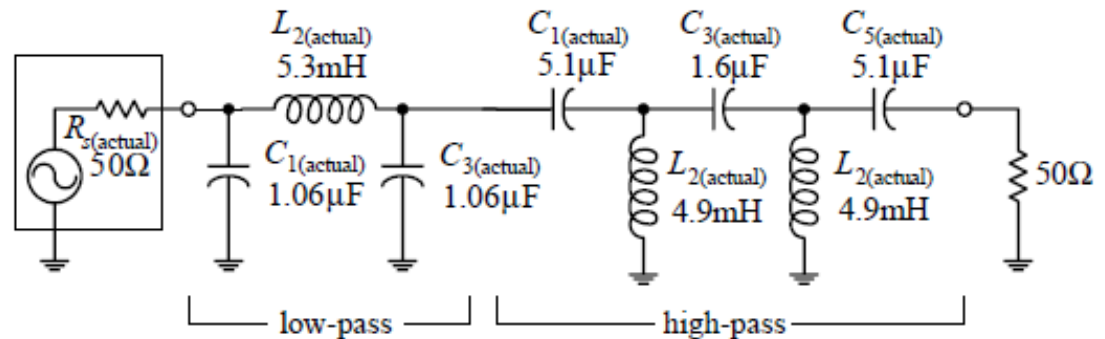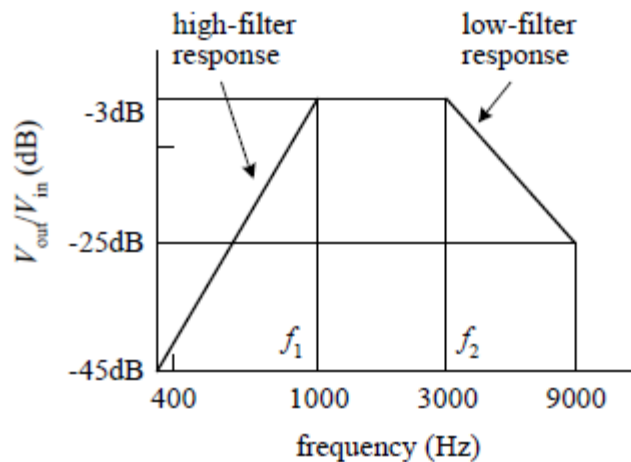

Just Cascade

Bandpass Filter Design–Wide Band–Active–

Suppose that you want to design a bandpass filter that has -3 -dB points at $f_1 = 1000$ Hz and $f_2 = 3000$ Hz and at least -30 dB at 300 and 10,000 Hz. What do you do?

$$\frac{f_2}{f_1} = \frac{3000 \text{ Hz}}{1000 \text{ Hz}} = 3$$

Low-pass: -3 dB at 3000 Hz
 -30 dB at 10,000 Hz

High-pass: -3 dB at 1000 Hz
 -30 dB at 300 Hz


The steepness factor for the low-pass filter is

$$A_s = \frac{f_s}{f_{3\text{dB}}} = \frac{10,000 \text{ Hz}}{3000 \text{ Hz}} = 3.3$$

while the steepness factor for the high-pass filter is


$$A_s = \frac{f_{3\text{dB}}}{f_s} = \frac{1000 \text{ Hz}}{300 \text{ Hz}} = 3.3$$

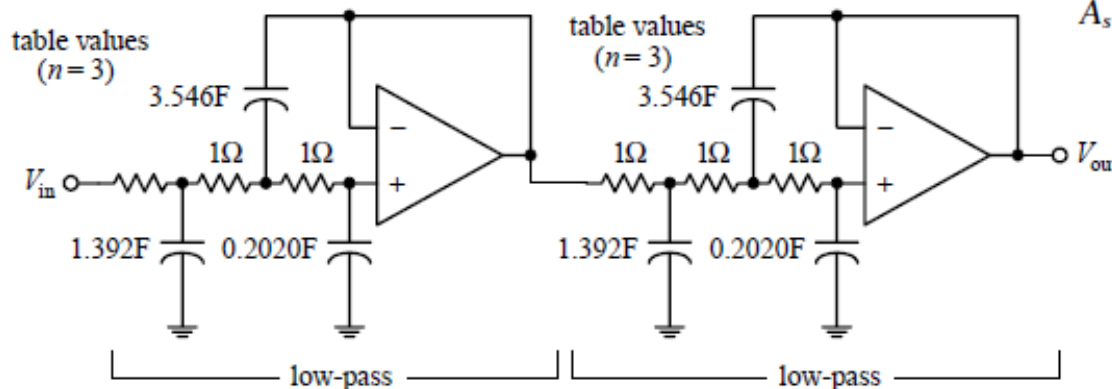Normalized low-pass/low-pass initial setup




Follow...

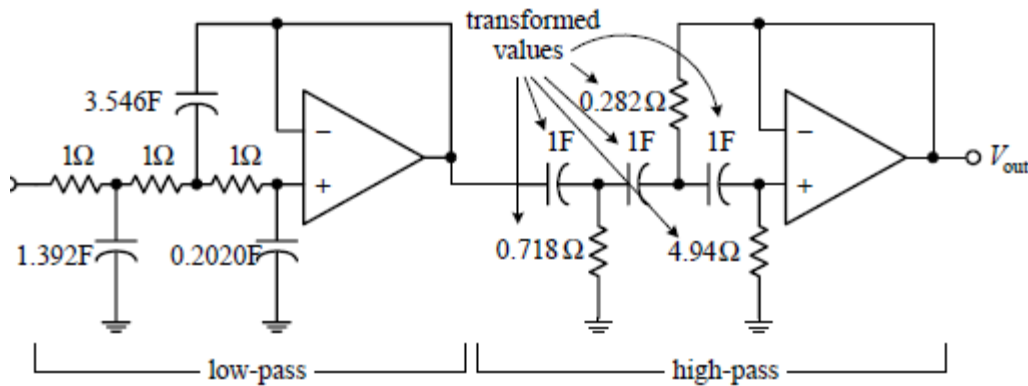Normalized and transformed bandpass filter



Final bandpass filter

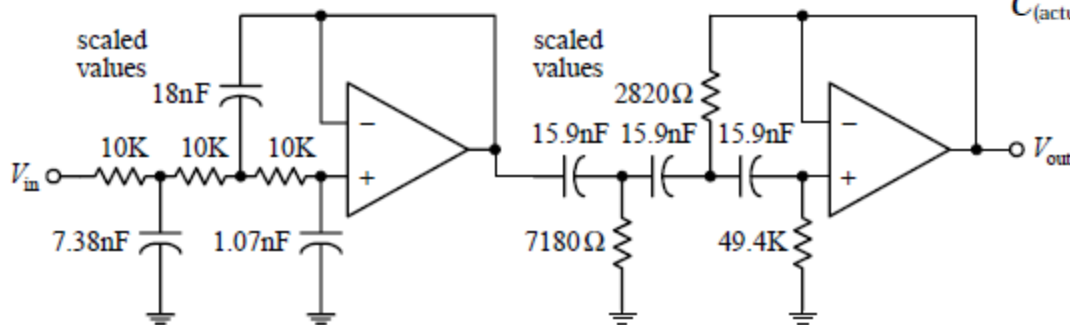

Low-pass section:

$$C_{(\text{actual})} = \frac{C_{\text{table}}}{Z \cdot 2\pi f_{3\text{dB}}} = \frac{C_{\text{table}}}{Z \cdot 2\pi(3000 \text{ Hz})}$$

High-pass section:

$$C_{(\text{actual})} = \frac{C_{\text{table}}}{Z \cdot 2\pi f_{2\text{dB}}} = \frac{C_{\text{table}}}{Z \cdot 2\pi(1000 \text{ Hz})}$$

Narrow Bandwidth BPF–Passive (optional)

Suppose that you want to design a bandpass filter with -3 -dB points at $f_1 = 900$ Hz and $f_2 = 1100$ Hz and at least -20 dB worth of attenuation at 800 and 1200 Hz. Assume that both the source and load impedances are 50Ω and that a Butterworth design is desired.

Since $f_2/f_1 = 1.2$, which is less than 1.5, a narrow-band filter is needed.

geometric center frequency $f_0 = \sqrt{f_1 f_2} = \sqrt{(900 \text{ Hz})(1100)} = 995 \text{ Hz}$

Next, compute the two pair of geometrically related stop-band frequencies by using

$$f_a f_b = f_0^2$$


$$f_a = 800 \text{ Hz} \quad f_b = \frac{f_0^2}{f_a} = \frac{(995 \text{ Hz})^2}{800 \text{ Hz}} = 1237 \text{ Hz} \quad f_b - f_a = 437 \text{ Hz}$$

$$f_b = 1200 \text{ Hz} \quad f_a = \frac{f_0^2}{f_b} = \frac{(995 \text{ Hz})^2}{1200 \text{ Hz}} = 825 \text{ Hz} \quad f_b - f_a = 375 \text{ Hz}$$

Choose the pair having the least separation, which represents more severe requirements—375 Hz

Follow.....


Low-pass bandpass relationship

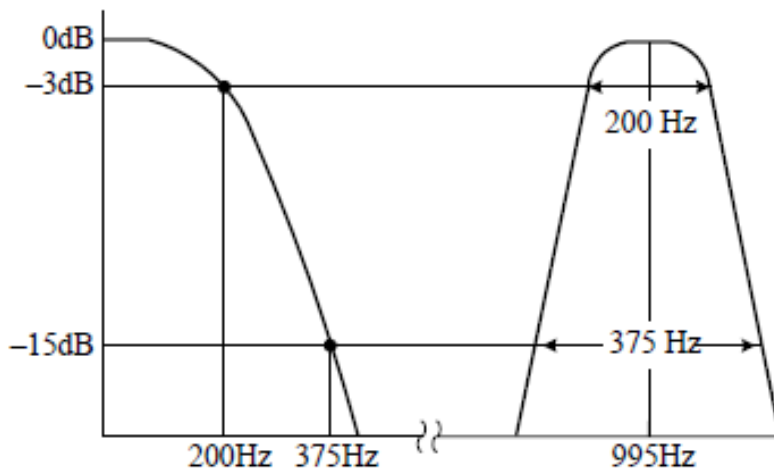


$$A_s = \frac{\text{stop-band bandwidth}}{\text{3-dB bandwidth}} = \frac{375 \text{ Hz}}{200 \text{ Hz}} = 1.88$$

From the curve $n=3$

Normalized low-pass response

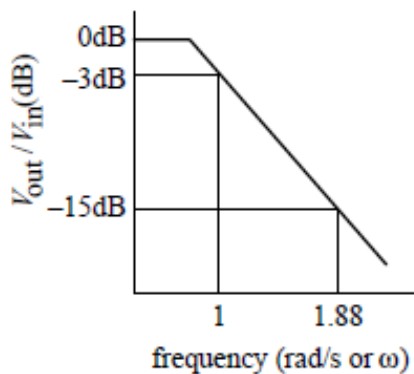

Normalized low-pass filter

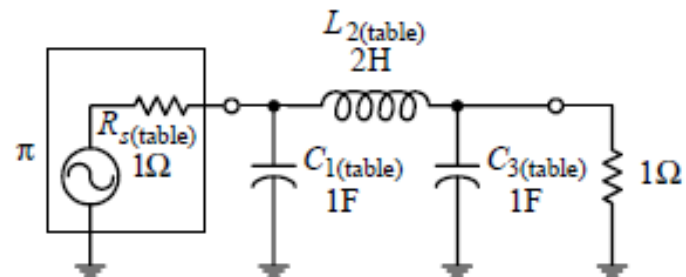


Follow.....

Impedance and frequency scaled low-pass filter

$$C_{1(\text{actual})} = \frac{C_{1(\text{table})}}{2\pi(\Delta f_{BW})R_L} = \frac{1 \text{ F}}{2\pi(200 \text{ Hz})(50 \Omega)} = 15.92 \mu\text{F}$$

$$C_{3(\text{actual})} = \frac{C_{3(\text{table})}}{2\pi(\Delta f_{BW})R_L} = \frac{1 \text{ F}}{2\pi(200 \text{ Hz})(50 \Omega)} = 15.92 \mu\text{F}$$
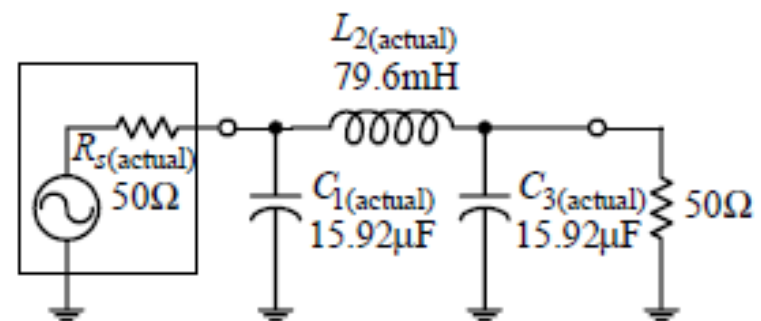
$$L_{2(\text{actual})} = \frac{L_{2(\text{table})}R_L}{2\pi(\Delta f_{BW})} = \frac{(2 \text{ H})(50 \Omega)}{2\pi(200 \text{ Hz})} = 79.6 \text{ mH}$$




The important part comes now. Each circuit branch of the low-pass filter must be resonated to f_0 by adding a series capacitor to each inductor and a parallel inductor to each capacitor. The LC resonant equation is used to determine the additional component values:

$$L_{(\text{parallel with } C_1)} = \frac{1}{(2\pi f_0)^2 C_{1(\text{actual})}} = \frac{1}{(2\pi \cdot 995 \text{ Hz})^2 (15.92 \mu\text{F})} = 1.61 \text{ mH}$$

$$L_{(\text{parallel with } C_3)} = \frac{1}{(2\pi f_0)^2 C_{3(\text{actual})}} = \frac{1}{(2\pi \cdot 995 \text{ Hz})^2 (15.92 \mu\text{F})} = 1.61 \text{ mH}$$

$$C_{(\text{series with } L_2)} = \frac{1}{(2\pi f_0)^2 L_{2(\text{actual})}} = \frac{1}{(2\pi \cdot 995 \text{ Hz})^2 (79.6 \text{ mH})} = 0.32 \mu\text{F}$$

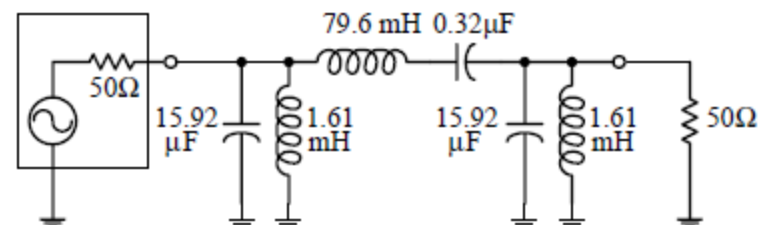Final bandpass filter $f_0 = \frac{1}{2\pi\sqrt{LC}}$




BPF–Narrow Band–Active Design

Suppose that you want to design a bandpass filter that has a center frequency $f_0 = 2000$ Hz and a -3 -dB bandwidth $\Delta f_{BW} = f_2 - f_1 = 40$ Hz. How do you design the filter?

Since $f_2/f_1 = 2040 \text{ Hz}/1960 \text{ Hz} = 1.04$,

No Cascading

Narrow-band filter circuit

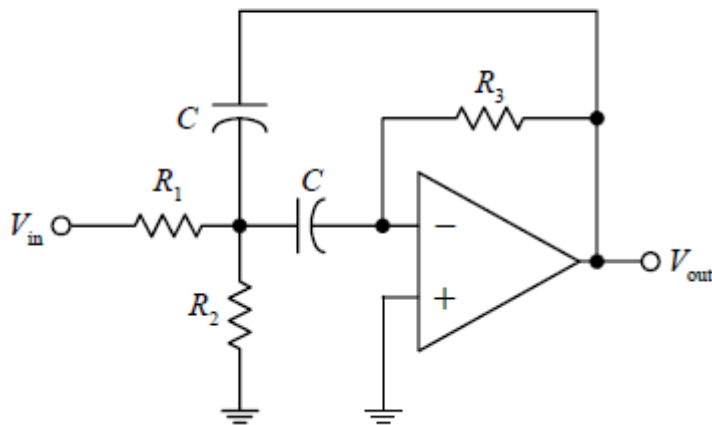

$$Q = \frac{f_0}{f_2 - f_1} = \frac{2000 \text{ Hz}}{40 \text{ Hz}} = 50$$

$$R_1 = \frac{Q}{2\pi f_0 C} \quad R_2 = \frac{R_1}{2Q^2 - 1} \quad R_3 = 2R_1$$

$$R_1 = \frac{50}{2\pi(2000 \text{ Hz})(0.01 \mu\text{F})} = 79.6 \text{ k}\Omega$$


$$R_2 = \frac{79.6 \text{ k}\Omega}{2(50)^2 - 1} = 400 \Omega$$

$$R_3 = 2(79.6 \text{ k}\Omega) = 159 \text{ k}\Omega$$

Choose convenient value of C, let it
0.01 μF

Final Design ...

Final filter circuit

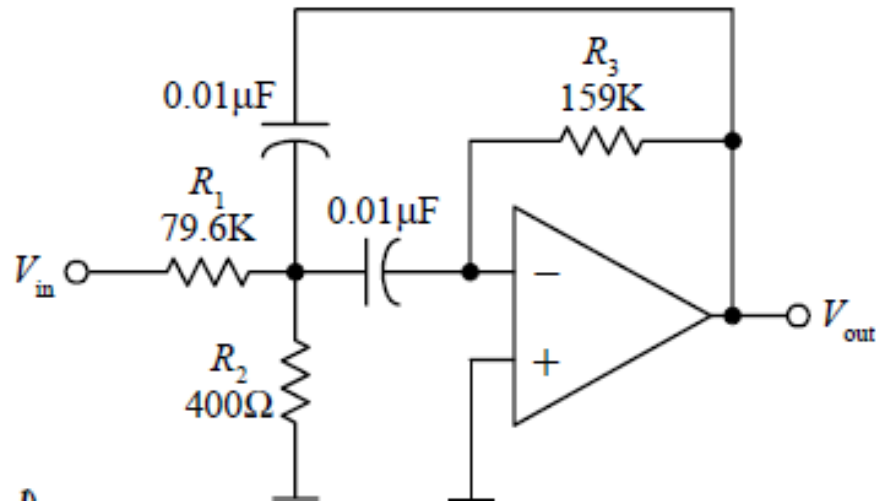

Passive Notch Filter (optional)

EXAMPLE

Suppose that you want to design a notch filter with -3 -dB points at $f_1 = 800$ Hz and $f_2 = 1200$ Hz and at least -20 dB at 900 and 1100 Hz. Let's assume that both the source and load impedances are 600Ω and that a Butterworth design is desired.

First, you find the geometric center frequency:

$$f_0 = \sqrt{f_1 f_2} = \sqrt{(800 \text{ Hz})(1200 \text{ Hz})} = 980 \text{ Hz}$$

Next, compute the two pairs of geometrically related stop-band frequencies:

$$f_a = 900 \text{ Hz} \quad f_b = \frac{f_0^2}{f_a} = \frac{(980 \text{ Hz})^2}{900 \text{ Hz}} = 1067 \text{ Hz}$$

$$f_b - f_a = 1067 \text{ Hz} - 900 \text{ Hz} = 167 \text{ Hz}$$


$$f_b = 1100 \text{ Hz} \quad f_a = \frac{f_0^2}{f_b} = \frac{(980 \text{ Hz})^2}{1100 \text{ Hz}} = 873 \text{ Hz}$$

$$f_b - f_a = 1100 \text{ Hz} - 873 \text{ Hz} = 227 \text{ Hz}$$

Choose the pair of frequencies that gives the more severe requirement—227 Hz.

Follow....

High-pass bandpass relationship

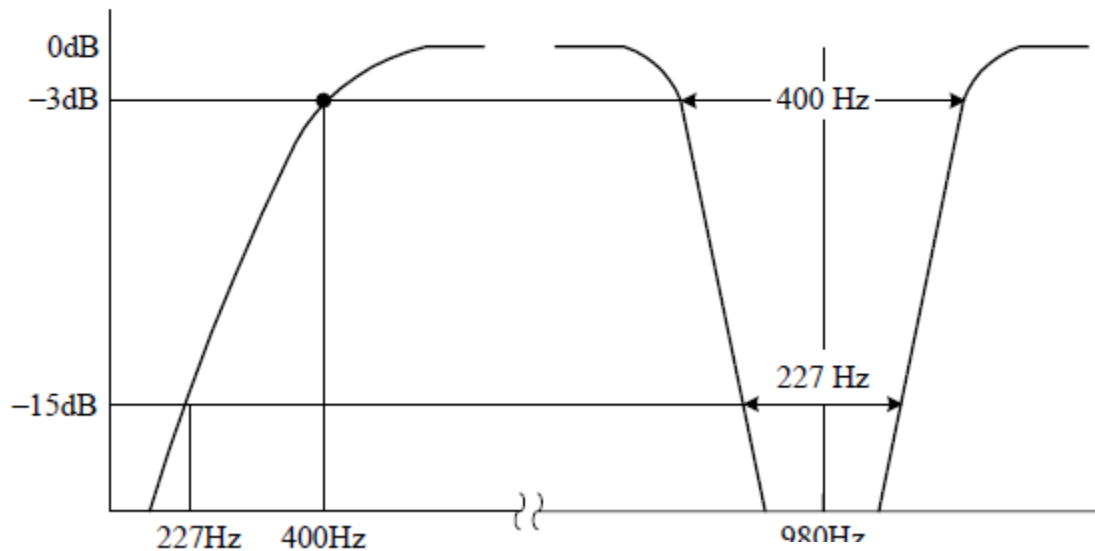

$$A_s = \frac{\text{3-dB bandwidth}}{\text{stop-band bandwidth}} = \frac{400 \text{ Hz}}{227 \text{ Hz}} = 1.7$$


$$L_{1(\text{transf})} = 1/C_{1(\text{table})} = 1/1 = 1 \text{ H}$$

$$L_{3(\text{transf})} = 1/C_{3(\text{table})} = 1/1 = 1 \text{ H}$$


$$C_{2(\text{transf})} = 1/L_{2(\text{table})} = 1/2 = 0.5 \text{ F}$$

Normalized low-pass filter

$n=3$

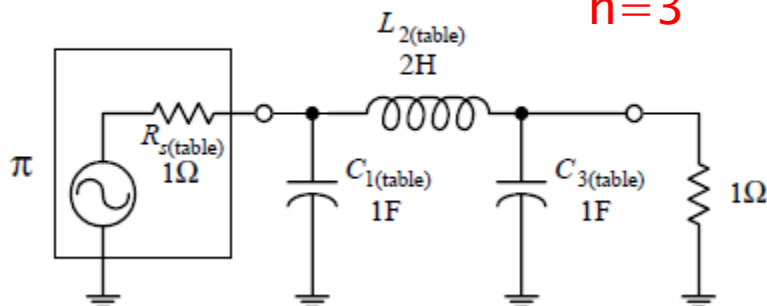


Normalized high-pass filter

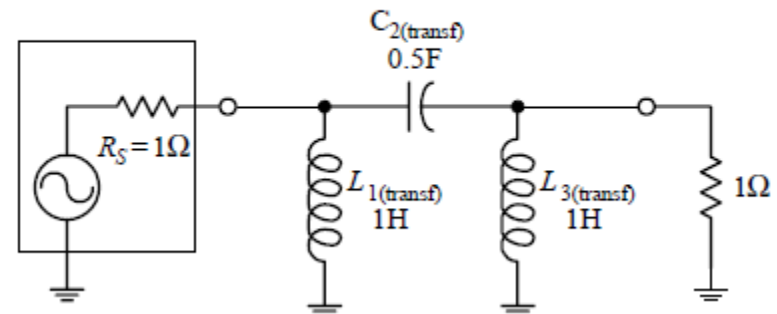

Follow...

Actual high-pass filter

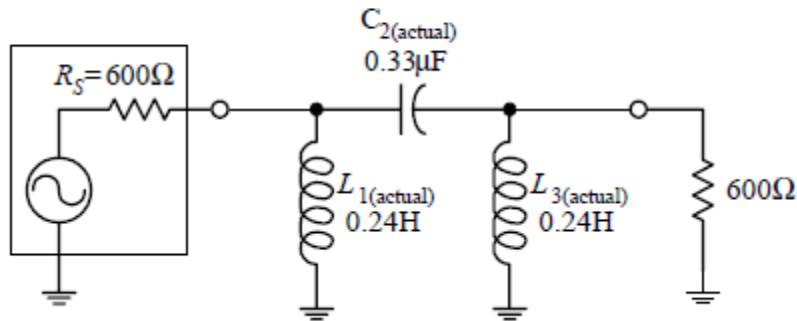


$$L_{1(actual)} = \frac{R_L L_{1(transf)}}{2\pi(\Delta f_{BW})} = \frac{(600\ \Omega)(1\ \text{H})}{2\pi(400\ \text{Hz})} = 0.24\ \text{H}$$

$$L_{3(actual)} = \frac{R_L L_{3(transf)}}{2\pi(\Delta f_{BW})} = \frac{(600\ \Omega)(1\ \text{H})}{2\pi(400\ \text{Hz})} = 0.24\ \text{H}$$

$$C_{2(actual)} = \frac{C_{1(transf)}}{2\pi(\Delta f_{BW})R_L} = \frac{(0.5\ \text{F})}{2\pi(400\ \text{Hz})(600\ \Omega)} = 0.33\ \mu\text{F}$$

Final bandpass filter

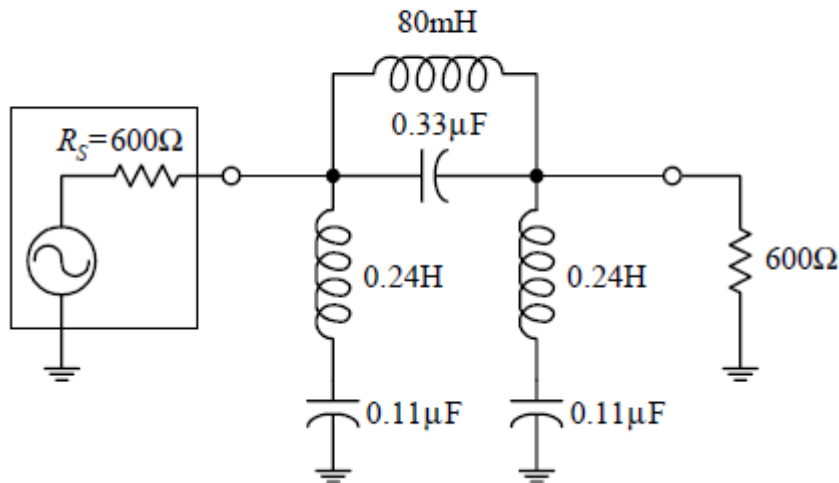


$$C_{(\text{series with } L1)} = \frac{1}{(2\pi f_0)^2 L_{1(actual)}} = \frac{1}{(2\pi \cdot 400\ \text{Hz})^2 (0.24\ \text{H})} = 0.11\ \mu\text{F}$$

$$C_{(\text{series with } L3)} = \frac{1}{(2\pi f_0)^2 L_{3(actual)}} = \frac{1}{(2\pi \cdot 400\ \text{Hz})^2 (0.24\ \text{H})} = 0.11\ \mu\text{F}$$

$$L_{(\text{parallel with } L1)} = \frac{1}{(2\pi f_0)^2 C_{2(actual)}} = \frac{1}{(2\pi \cdot 400\ \text{Hz})^2 (0.33\ \mu\text{F})} = 80\ \text{mH}$$

Active Notch Filter –Wide–Band


Basic wide-band notch filter

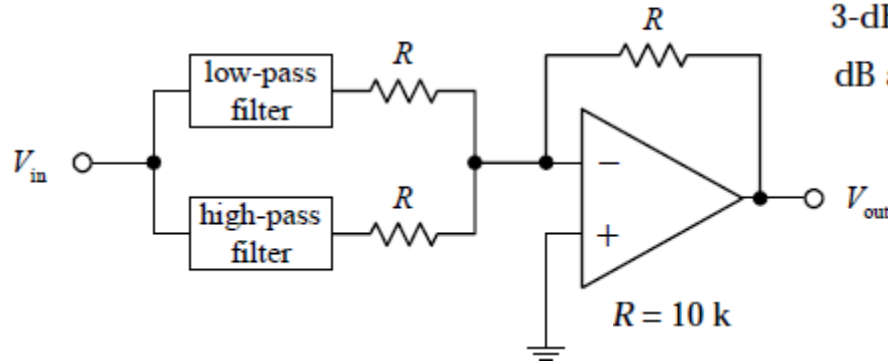

For example, if you need a notch filter to have –3-dB points at 500 and 5000 Hz and at least –15 dB at 1000 and 2500 Hz,

Narrow-Band Notch Filter

Improved notch filter

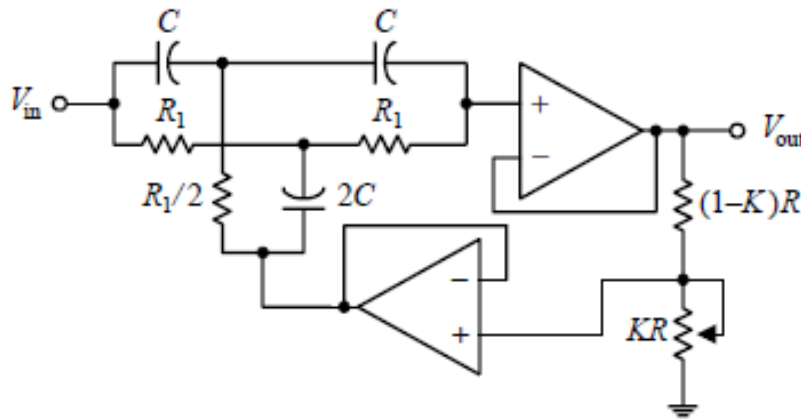

Suppose that you want to make a “notch” at $f_0 = 2000$ Hz and desire a -3 -dB bandwidth of $\Delta f_{BW} = 100$ Hz. To get this desired response, do the following: First determine the Q :

$$Q = \frac{\text{“notch” frequency}}{-3\text{-dB bandwidth}} = \frac{f_0}{\Delta f_{BW}} = \frac{2000 \text{ Hz}}{100 \text{ Hz}} = 20$$

$$R_1 = \frac{1}{2\pi f_0 C} \quad \text{and} \quad K = \frac{4Q - 1}{4Q}$$

Now arbitrarily choose R and C ; say, let $R = 10$ k and $C = 0.01$ μ F. Next, solve for R_1 and K :


$$R_1 = \frac{1}{2\pi f_0 C} = \frac{1}{2\pi(2000 \text{ Hz})(0.01 \mu\text{F})} = 7961 \Omega$$

$$K = \frac{4Q - 1}{4Q} = \frac{4(20) - 1}{4(20)} = 0.9875$$

Anti-aliasing

▶ The sampling theorem

- A continuous signal can be represented completely by, and reconstructed from, a set of instantaneous measurements or samples of its voltage which are made at equally-spaced times. The interval $T(=1/f_s)$ between such samples must be less than one-half the period of the highest-frequency component f_{MAX} in the signal
- In other words: you must sample at least twice the rate of the maximum frequency in your signal to prevent aliasing ($F_s \geq 2F_{MAX}$)
- The sampling rate $F_s = 2F_{MAX}$ is called the Nyquist rate

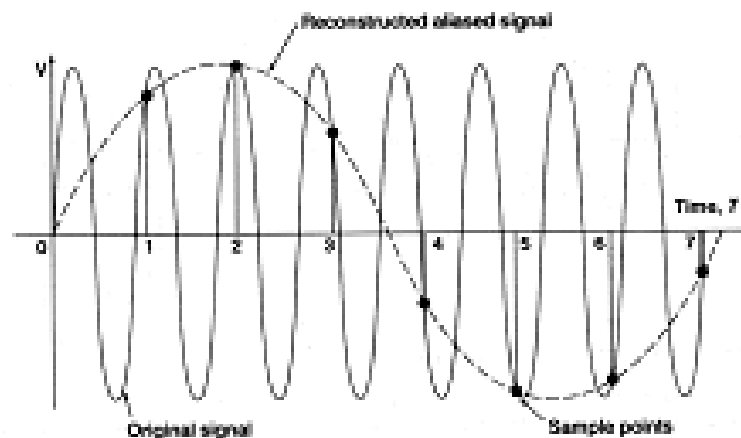

Anti-aliasing

- The effects of aliasing can also be observed on the frequency spectrum of the signal
- In the figures below
 - F_1 appears correctly since $F_1 \leq F_s/2$
 - F_2 , F_3 and F_4 have aliases at 30, 40 and 10Hz, respectively
 - You can compute these aliased frequencies by folding the spectrum around $F_s/2$ or with the expression

$$\text{Alias frequency } \hat{F} = \min |kF_s - F|_{k \text{ Integer}}$$

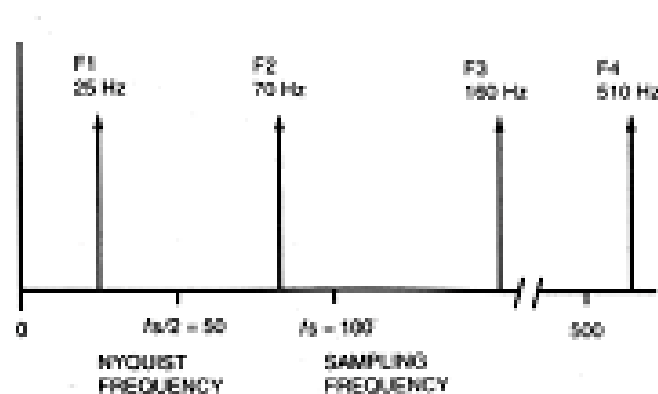


FIGURE 117.5 Spectral of signal with multiple frequencies.

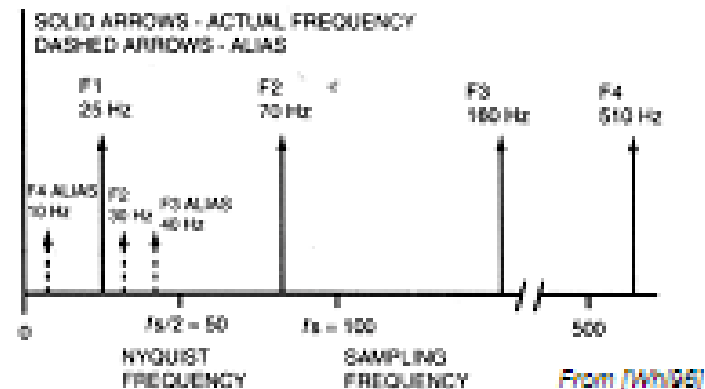


FIGURE 117.6 Spectral of signal with multiple frequencies after sampled at $f_s = 100$ Hz.

Anti-aliasing filters

- ▶ An anti-aliasing filter is a low-pass filter designed to filter out frequencies higher than the sampling frequency
 - An anti-aliasing filter should have
 - Steep cut-off and
 - Flat response in the frequency band
- ▶ Typical filters are:
 - Butterworth: flattest response in the frequency band but phase shifts well below the break frequency
 - Bessel: phase shift proportional to frequency, so the signal is not distorted by the filter
 - Recommended for anti-aliasing if it is important to preserve the waveform
 - Chebyshev: steepest cut-off but it has ripples in the band-pass

