
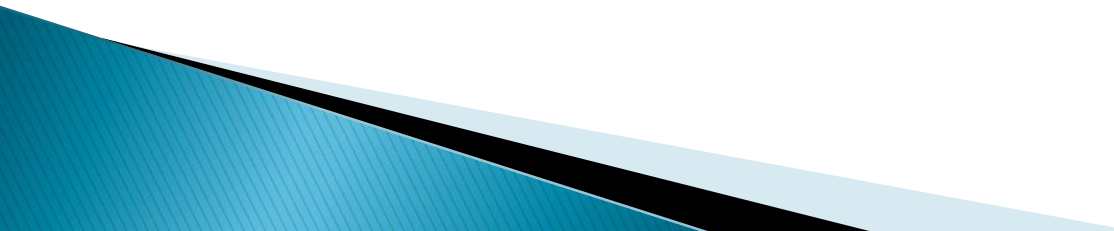


Data Acquisition II

- ▶ Sample and hold
 - ▶ Multiplexing
 - ▶ Analog to digital conversion
 - ▶ Digital to analog conversion
- 

Architecture of data acquisition systems

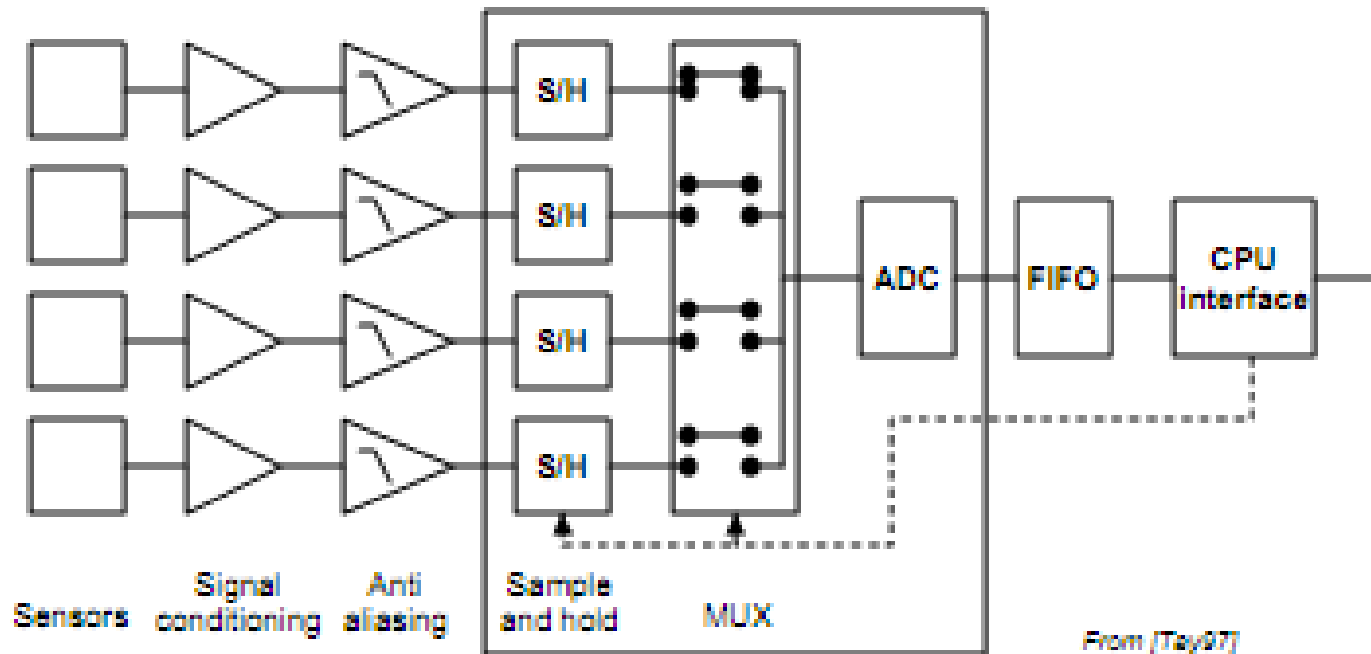

ANALOG \Leftrightarrow DIGITAL CONVERSION

Physical world is analog (mostly)


Analog is infinitely variable, while digital is discrete in both time and value

Analog/digital conversion can be part of the instrument or part of the actuator, e.g.

- Incremental encoder – analog position gets encoded into digital pulse
- Stepper motor – digital step pulse gets transformed to analog position

ANALOG \Leftrightarrow DIGITAL CONVERSION

 To be processed by computers, all information must be converted to a binary representation possessing a finite number of distinct values that combine logical low (0) and logical high (1):



Digital coding is arbitrary, but natural binary order is most often used

ANALOG \Leftrightarrow DIGITAL CONVERSION

For notational compactness and ease of reading, binary (base 2) representations are often expressed in octal (base 8) or hexadecimal (base 16):

$$10100110_2 = 0246_8 = 166_{10} = A6_{16}$$

Arduino code:

Binary:	<code>B10100110</code>	(leading 'B', only 8-bit values)
Octal:	<code>0246</code>	(leading '0')
Decimal:	<code>166</code>	(no formatting needed)
Hexadecimal:	<code>0xA6</code>	(leading "0x", chars 0-9, A-F, a-f)

DIGITAL REPRESENTATION

When using natural binary order, the digital code consists of an N -bit binary word:

$$b_{N-1} b_{N-2} b_{N-3} \dots b_1 b_0$$

where b_{N-1} is the most-significant bit (MSB) and b_0 is the least-significant bit (LSB)

8-bit digital word: **byte** (or octet).

4-bit digital word: **nibble** (or quartet).

DIGITAL REPRESENTATION

The fractional value of the digital word is:

$$2^{-1} b_{N-1} + 2^{-2} b_{N-2} + 2^{-3} b_{N-3} + \dots + 2^{-N} b_0$$

with a range of $0 \rightarrow (1 - 2^{-N})$ and a precision of 2^{-N}


Digital fractions sometimes notated with leading point notation:

$$.1011_2 = .6875_{10}$$

Example:


- 4-bits
- Range = $0 \rightarrow (1 - 2^{-4}) = 0 \rightarrow \frac{15}{16}$ (nearly 1)
- Precision (absolute and relative) = $2^{-4} = \frac{1}{16}$
- Code of 1011 = $\frac{1}{2} + \frac{1}{8} + \frac{1}{16} = \frac{11}{16} = .6875$

DIGITAL REPRESENTATION

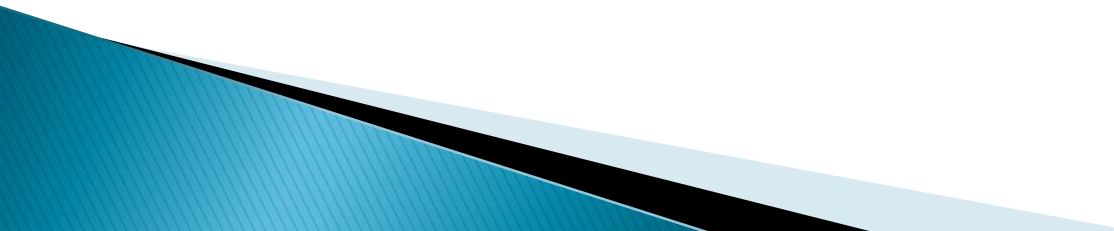- Digital codes have no inherent units, so scaling must be defined for code to have real-world meaning.
 - How to assign relationship between binary code and analog values? It depends on the application...
- 


DIGITAL REPRESENTATION

 For a unipolar signal, it seems obvious to associate V_{\min} with binary zero. Do we associate V_{\max} with binary 2^N (fractional value of 1), or with binary 2^N-1 (and its fraction value of $1-2^{-N}$)?




DIGITAL REPRESENTATION

 To maximize the conversion range for N-bit coding of a *unipolar* value, we often associate V_{\min} with binary zero and V_{\max} with binary 2^N-1 . For example, for a 0-10V signal, we may assign values such that:



DIGITAL REPRESENTATION

 
However, it is common to associate a reference value of V_{ref} with the digital code used to denote a fraction of 1



DIGITAL REPRESENTATION


In such an arrangement, with $V_{\min} = 0$,
 
$$V_{fs} = V_{\max} = V_{\text{ref}} \left(\frac{2^N - 1}{2^N} \right)$$



DIGITAL REPRESENTATION

 
If V_{\min} is less than binary zero, or V_{\max} is more than binary 2^N-1 , then *amplitude clipping* may result.



DIGITAL REPRESENTATION

Quantization Level: change in analog output associated with each discrete step

 - We assume this step size to be fixed, although in sophisticated applications, it may vary across the signal range, or adapt to signal characteristics.



DIGITAL REPRESENTATION

Quantization Level (Q)

- Signal change associated with LSB
- For an N-bit converter:

- $$Q = \frac{V_{\text{fullscale}}}{2^N - 1} = \frac{V_{\text{ref}}}{2^N}$$

- Quantization *error* ranges from $-\frac{Q}{2}$ to $+\frac{Q}{2}$

Example:

- 4-bits, 12 volts full-scale, binary code of 1001
- $Q = 12V / (2^4 - 1) = .8V$
- $|Q_{\text{error}}| \leq .4V$
- $V_{\text{analog}} = Q \times (8 \cdot 1 + 4 \cdot 0 + 2 \cdot 0 + 1) = .8V \times 9 = 7.2V$

DIGITAL REPRESENTATION

Quantization

- An irreversible process
- A source of information loss
- Increasing the number of bits lowers information loss, but usually raises the cost and processing time

Example:

- 10 volts full-scale, with 1% precision required
- $Q = 1\% \cdot 10 = 0.1V$
- $N \geq \log_2 [V_{FS}/Q + 1] = 6.7 \text{ bits} \Rightarrow \text{at least 7 bits}$

INTEGER CODES

Unipolar Voltages

- Can be coded to unsigned integers
- Example – 0-5 volts coded to 3 bit unsigned integer

Voltage	Digital Value	Decimal Equivalent
0	000	0
0.71	001	1
1.43	010	2
2.14	011	3
2.86	100	4
3.57	101	5
4.29	110	6
5	111	7

INTEGER CODES

Bipolar Coding

- Two's Complement

Voltage(1)	Voltage(2)	Digital Value	Decimal Equivalent
+3.75	+5	011	3
+2.50	+3.33	010	2
+1.25	+1.67	001	1
0	0	000	0
-1.25	-1.67	111	-1
-2.50	-3.33	110	-2
-3.75	-5	101	-3
-5	--	100	-4

- MSB is treated with a weighting of -2^{N-1}

$$-3 = -2^{(3-1)} + 1 = -2^2 + 1 = -4 + 1 \rightarrow 101$$







DIGITAL-TO-ANALOG CONVERTER (DAC)

Converts digital values to analog outputs of either voltage or current



DIGITAL-TO-ANALOG (D/A) CONVERSION

Ideal DA Conversion:

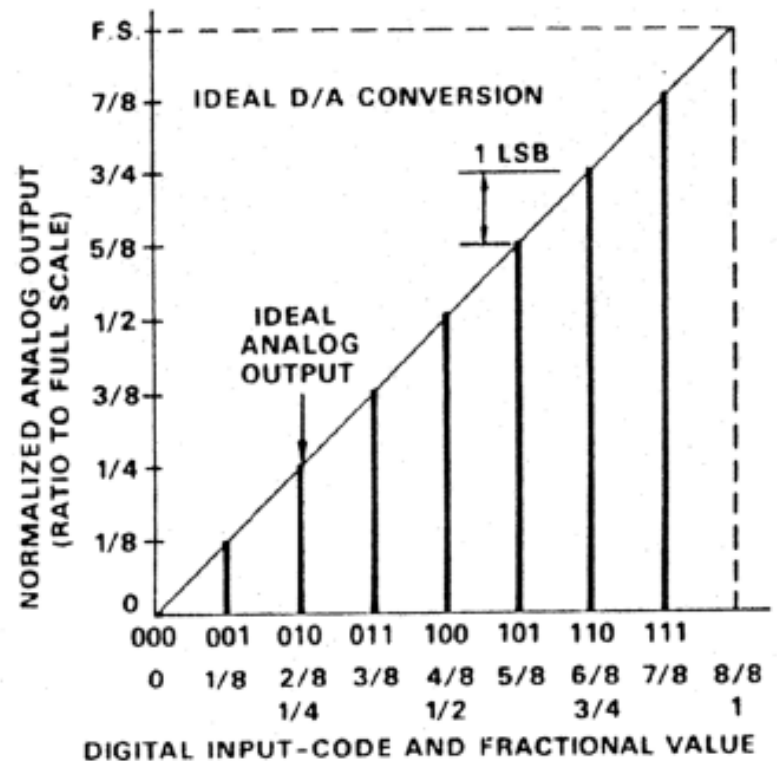     


DIGITAL-TO-ANALOG (D/A) CONVERSION

Digital value is stored in a register (latch), then converted.
Duration of conversion is called *settling time*.

Output of the DAC remains the same until the next value is sent to the register (latch) – a zero-order hold.

Basic concept:
 
$$V_{OUT} = \underbrace{(b_{N-1} \cdot 2^{N-1} + b_{N-2} \cdot 2^{N-2} + \dots + b_1 \cdot 2^1 + b_0 \cdot 2^0)}_{\text{Integer equivalent of binary code}} \cdot Q$$




DIGITAL-TO-ANALOG (D/A) CONVERSION

Weighted (Scaled) Resistor DAC

- Fast, but not practical for high bit count due to expense of high precision resistors across a wide magnitude range
- Virtual ground at inverting op-amp input
- Requires
 - Accurate reference voltage.
 - Higher precision resistor.

$$V_{OUT} = -\sum I_i \frac{R}{2} = -V_{REF} \left(\frac{b_{N-1}}{2} + \frac{b_{N-2}}{4} + \dots + \frac{b_0}{2^N} \right)$$


Can $|V_{OUT}| = |V_{REF}|$?

 

DIGITAL-TO-ANALOG (D/A) CONVERSION

R/2R Ladder DAC

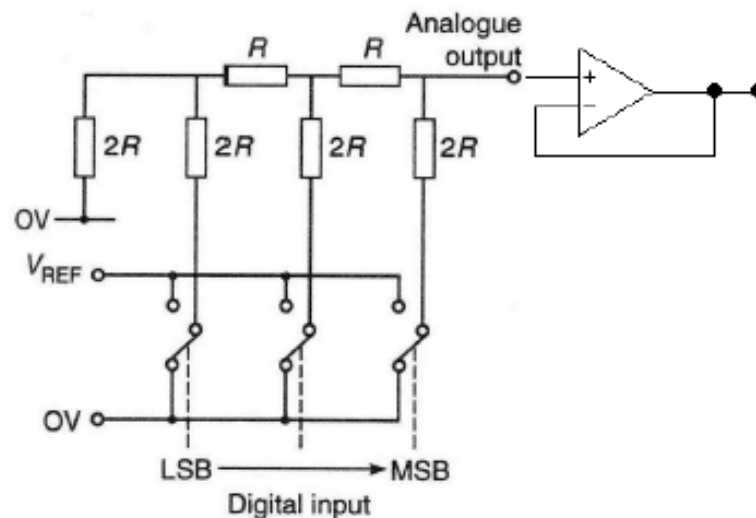- Uses just two resistance values ($2R$ and R , closely matched)
- Input switches define a specific resistor divider network



If only MSB (100) is asserted:

$$V_{OUT} = \frac{4}{8} \cdot V_{REF} = \frac{1}{2} \cdot V_{REF}$$

If all bits are asserted (111):

$$V_{OUT} = \frac{7}{8} \cdot V_{REF}$$

$$V_{OUT} = (b_{N-1} \cdot 2^{N-1} + b_{N-2} \cdot 2^{N-2} + \dots + b_1 \cdot 2^1 + b_0 \cdot 2^0) \cdot \frac{V_{REF}}{2^N}$$

- Bipolar output can be achieved by substituting the ground with a negative voltage source.


DIGITAL-TO-ANALOG (D/A) CONVERSION

Multiplying DAC


- Conventional DAC has internal reference voltage V_{REF} that is derived from the fixed power supply.
- Multiplying DAC has an externally supplied reference voltage.

$$V_{OUT} = (b_{N-1} \cdot 2^{N-1} + b_{N-2} \cdot 2^{N-2} + \dots + b_1 \cdot 2^1 + b_0 \cdot 2^0) \cdot \frac{V_{REF}}{2^N}$$

 - Advantages:
 - Use a constant frequency sinusoidal reference signal to achieve amplitude modulation, i.e. let $V_{REF} = V_R \sin(\omega t)$.
 - External V_{REF} can be precisely controlled to compensate for drift.



Internally Referenced

 

Multiplying DAC
(Externally Referenced)

INTERFACING WITH A DAC

- Non-multiplying DAC – use AD558 (8 bit DAC) as example

 




Table I. AD558 Control Logic Truth Table

Input Data	$\overline{\text{CE}}$	$\overline{\text{CS}}$	DAC Data	Latch Condition
0	0	0	0	"Transparent"
1	0	0	1	"Transparent"
0	g	0	0	Latching
1	g	0	1	Latching
0	0	g	0	Latching
1	0	g	1	Latching
X	1	X	Previous Data	Latched
X	X	1	Previous Data	Latched


NOTES

X = Does not matter.

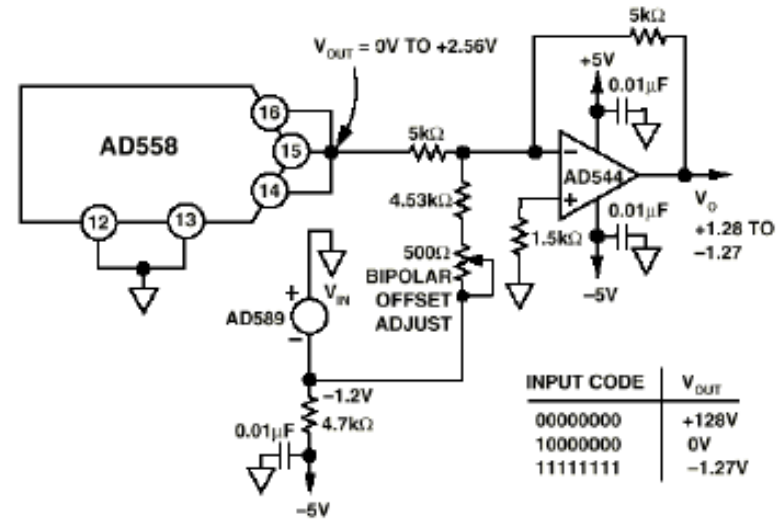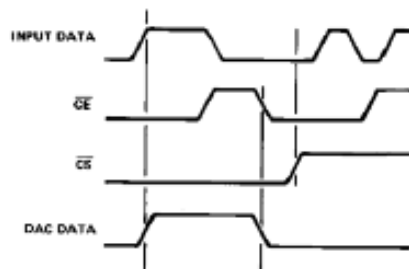g = Logic Threshold at Positive-Going Transition.



INPUT CODE	V_{OUT}
00000000	+128V
10000000	0V
11111111	-1.27V

 

t_W = STORAGE PULSE WIDTH = 200ns MIN

t_{DH} = DATA HOLD TIME = 10ns MIN

t_{DS} = DATA SETUP TIME = 200ns MIN


DIGITAL-TO-ANALOG (D/A) CONVERSION

Resistor methods rely on voltage dividers

- Many precision resistors necessary
- Wasted energy dissipated as heat

Pulse Width Modulation (PWM)

 - Rectangular pulse wave
- Duty cycle controls average voltage
- Very high frequency
- Need a low-pass filter to remove the sharp transitions at edges of the pulses!
- About 90% efficiency



DIGITAL-TO-ANALOG (D/A) CONVERSION


Pulse Width Modulation (PWM)

- Poor man's DAC
- Low pass filtering the PWM signal can produce an analog signal whose magnitude is proportional to the pulse width of the PWM signal
- For motor/motion control, the motor/motion system will act as the low pass filter
- Unipolar output
- Best suited when an analog output is needed but does not require a high resolution DAC

PULSE WIDTH MODULATION (PWM)

$$\text{Duty Cycle} = \frac{t_{ON}}{T} \Rightarrow 0 - 100\%$$
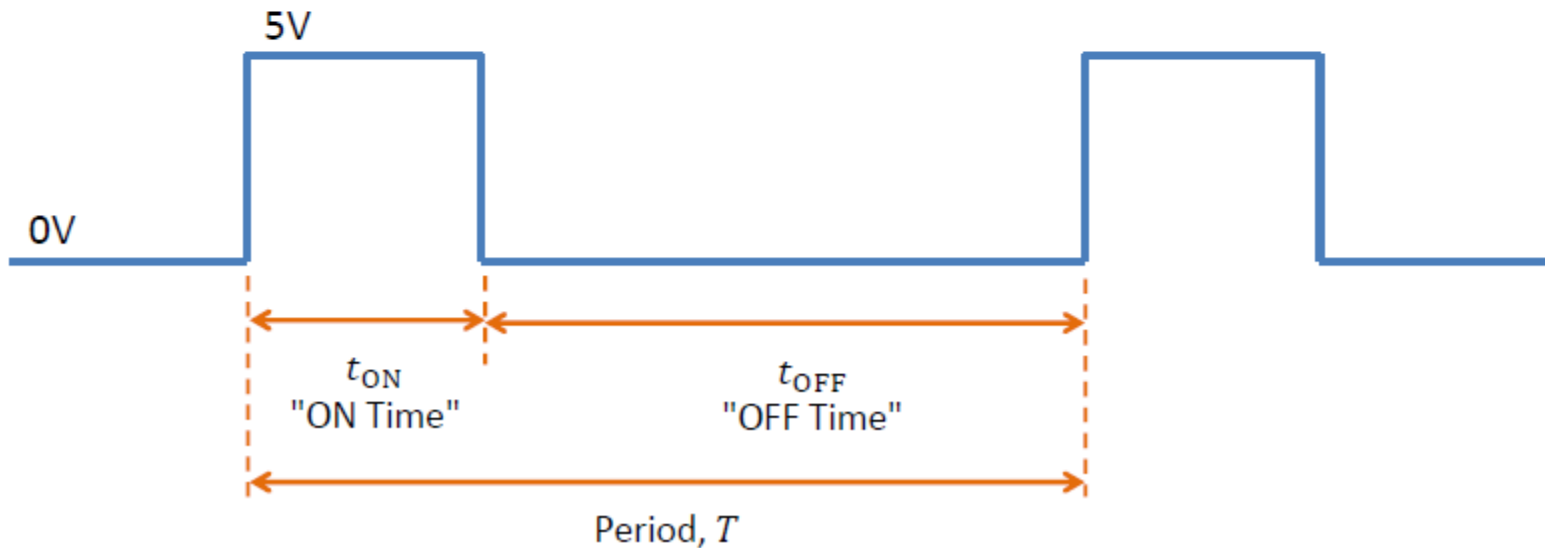
$$\text{Frequency (rad/sec)} = \frac{1}{T}$$




PULSE WIDTH MODULATION (PWM)

8-bit resolution:



- $100\%/255 \Rightarrow 0.39\%$ per step
- $5V/255 \Rightarrow 19.6$ mV per step

Arduino default PWM frequency:


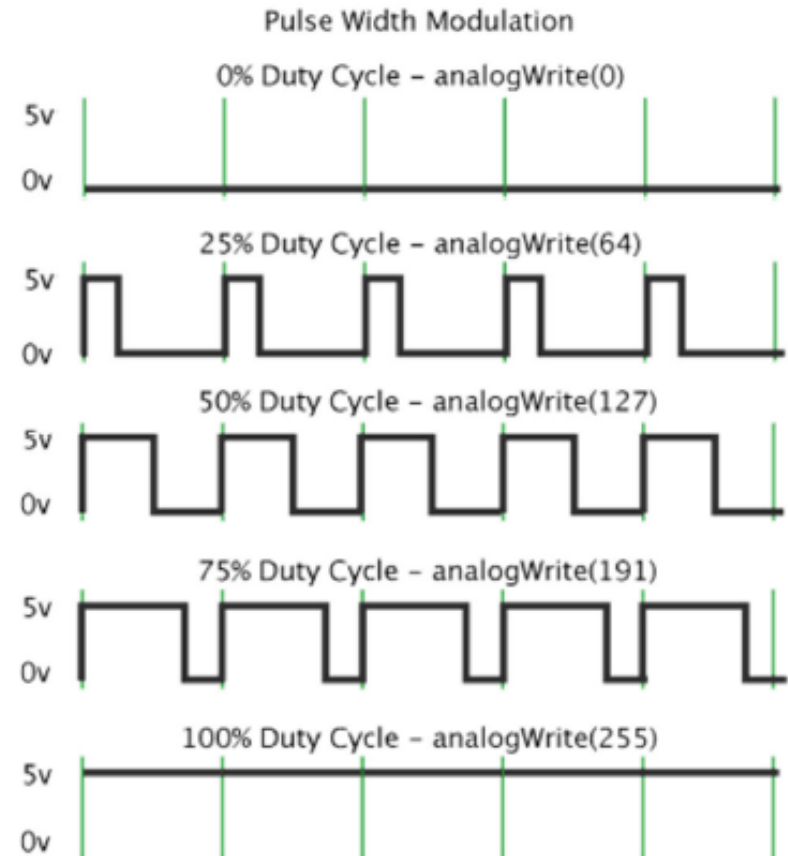
- Pins 5/6: ~ 976 Hz
- Pins 3/9/10/11: ~ 488 Hz
- Frequency can be increased to as much as 62.5 kHz by altering timer control registers
 - Pins 5/6: TCCR0B
 - Pins 9/10: TCCR1B
 - Pins 3/11: TCCR2B




DIGITAL-TO-ANALOG (D/A) CONVERSION

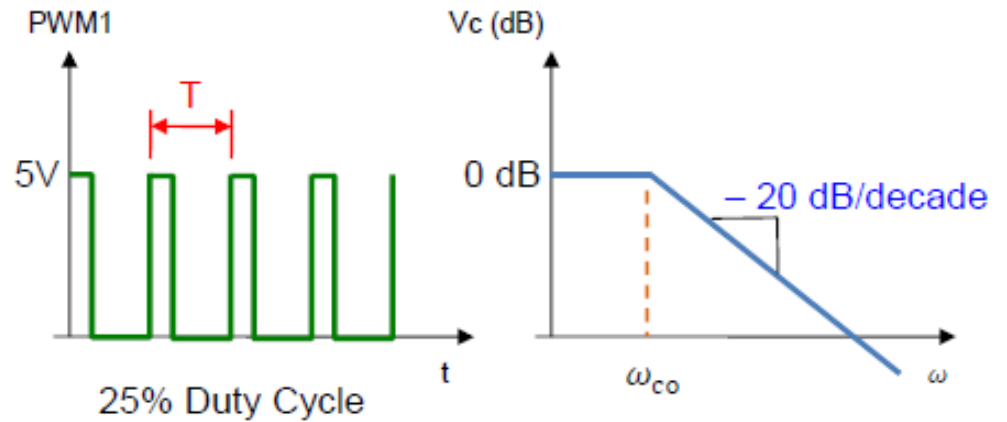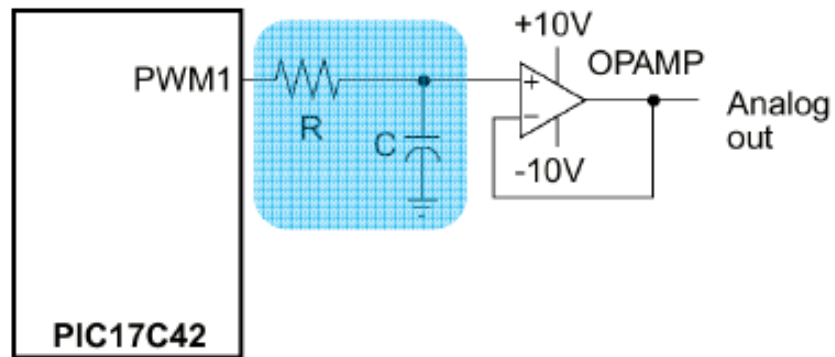


DIGITAL-TO-ANALOG (D/A) CONVERSION

 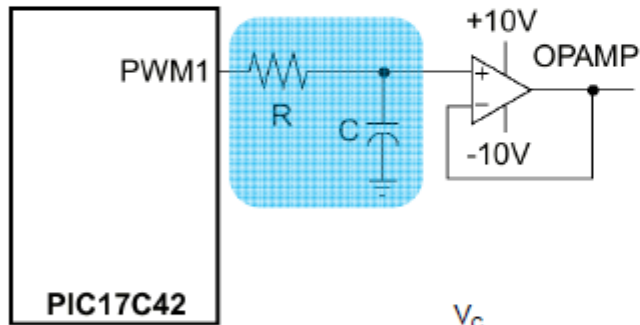

 
At low PWM frequency ($\omega_{pwm} \ll \omega_{co}$), capacitor can fully charge and discharge





DIGITAL-TO-ANALOG (D/A) CONVERSION

 

 
As PWM frequency increases, capacitor can barely charge and discharge fully





DIGITAL-TO-ANALOG (D/A) CONVERSION

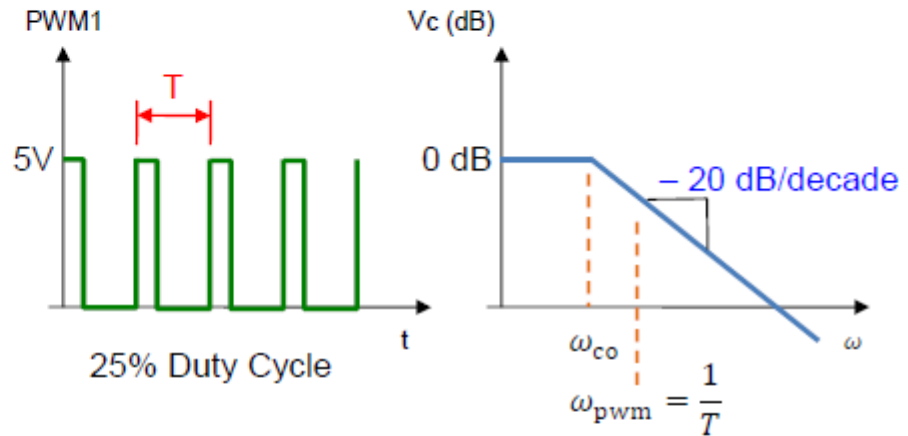 

 
As PWM frequency increases further, capacitor voltage slowly increases, since capacitor cannot fully discharge before next cycle begins





DIGITAL-TO-ANALOG (D/A) CONVERSION

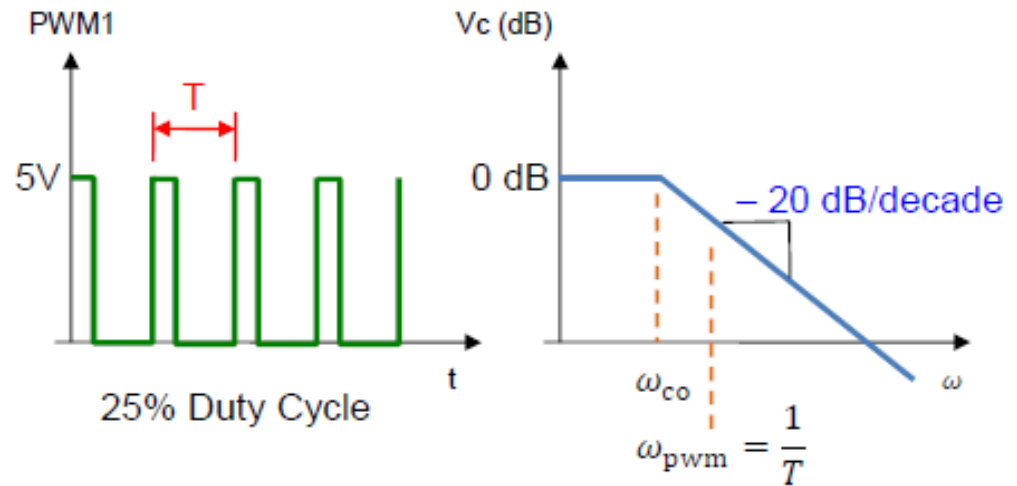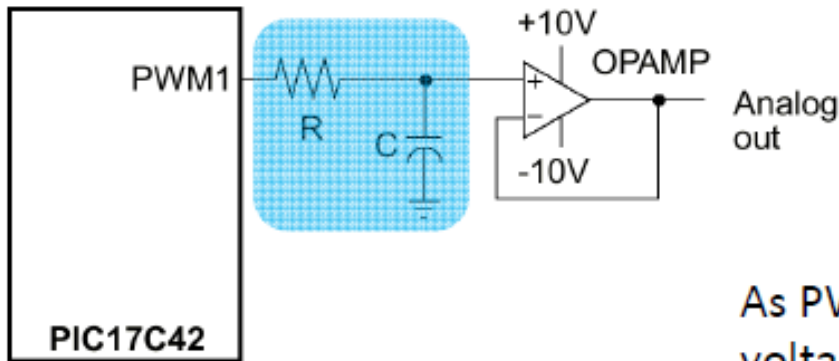

 
As PWM frequency increases further, capacitor voltage slowly increases, since capacitor cannot fully discharge before next cycle begins



DIGITAL-TO-ANALOG (D/A) CONVERSION

 
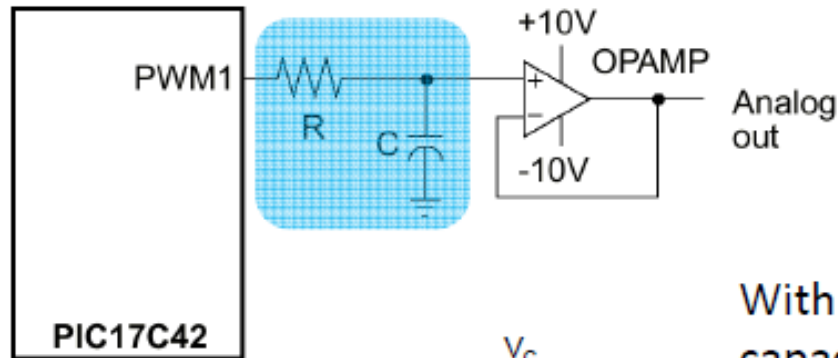


 With PWM frequency well above cutoff frequency, capacitor voltage loses saw-tooth appearance




$$V_{C, \text{ steady state}} = V_{pwm} \times \text{Duty Cycle \%}$$

DIGITAL-TO-ANALOG (D/A) CONVERSION

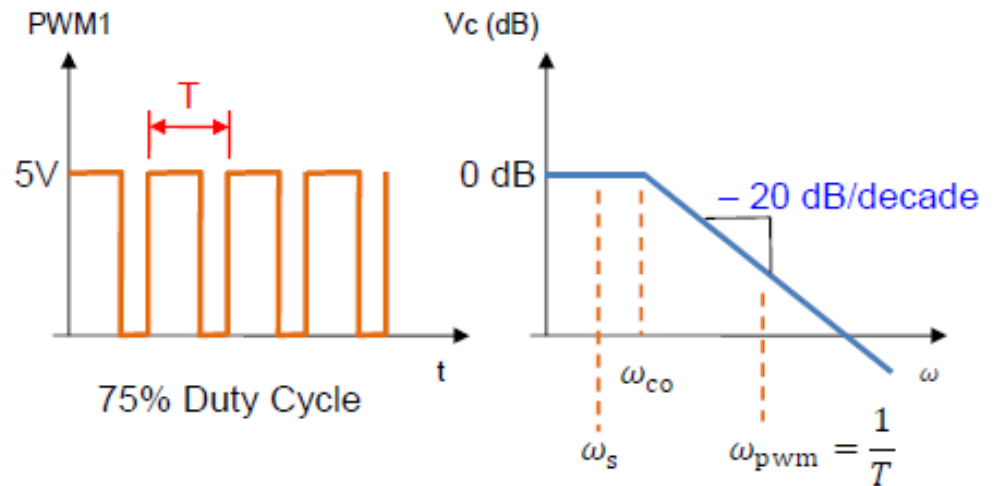 

 
Want signal frequency ω_s less than ω_{co} . Can't always adjust ω_{pwm} , so often have to play with ω_s and ω_{co}




$$V_{C, \text{ steady state}} = V_{pwm} \times \text{Duty Cycle \%}$$

DIGITAL-TO-ANALOG (D/A) CONVERSION

Digital Input

 

PWM Waveform

 



ANALOG TO DIGITAL CONVERTER (ADC)

Converts analog inputs to digital values




ANALOG-TO-DIGITAL (A/D) CONVERSION


Ideal AD Conversion:

  


(a) OFFSET ERROR

 

(b) SCALE FACTOR ERROR

 

(c) LINEARITY ERROR

 

(d) MISSED CODES

SAMPLING AND ALIASING

The process of converting from analog to digital cannot be instantaneous. Thus, inputs need to be stabilized while conversion is performed.


When signal (data) is sampled, temporal information is lost.

Sampling theorem (Shannon, Nyquist) gives limits

- Sampling rate must be faster than twice the highest frequency present (even if the highest frequency is noise) to preserve knowledge of the original signal's frequency content.


Slower sampling preserves amplitude information, but suggests incorrect frequency content; this is called *aliasing*.

SAMPLING AND ALIASING

 

ANTI-ALIASING

 Located upstream of the sampling device, anti-aliasing (low-pass) filters attempt to limit signal bandwidths to no more than half the sampling frequency, thus limiting the extent to which aliasing occurs.




Maxim's 8th-order, low-pass, elliptic, switched-capacitor filters operate from a single +3V or +5V supply

Sample and hold

- **A Sample and hold (S/H) circuit has two basic operating modes**
 - **Sample mode:** The output follows the input
 - **Hold mode:** The output is held constant until sample mode is resumed

 
- **The main application of S/H circuits is to hold the input signal to an ADC constant during conversion**
 - **Why?** Imagine trying to photograph a moving object!



From [FB00]

Basic S/H circuit

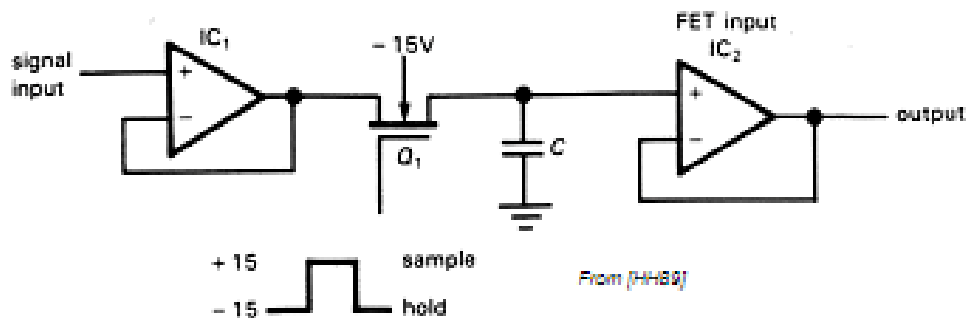
- ▶ Basic elements
 - Voltage followers
 - FET switch



- Operation
 - IC1 provides low Z_{out} version of input signal
 - Q1 passes the signal during 'sample' and disconnects during 'hold'
 - C preserves the value during 'hold'
 - IC2 is a high Z_{in} op-amp to minimize capacitor discharge during 'hold'


S/H response characteristics

- ▶ Response parameters
 - Aperture time: time required for the switch to open ($\sim 50\text{ns}$)
 - Droop: capacitor discharge ($\sim 1\text{mV/ms}$)
 - Acquisition time: switch operation plus capacitor charging time
- ▶ Considerations for choosing C
 - C should be large enough to minimize 'droop' caused by leakage currents in Q1 and IC2
 - C should be small enough to track fast signals since it forms a low-pass filter with Q1's ON resistance!
 - In practice, the slew rate of the entire circuit is determined by IC1's output current and Q1's ON resistance

 


Multiplexers

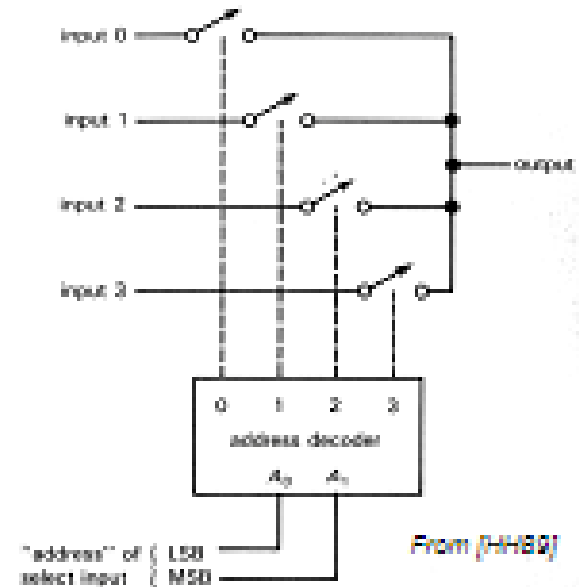- A multiplexer is a circuit that allows you to select any of several inputs, as specified by digital control signals
 - Since analog switches are bi-directional, this circuit could also be used as a de-multiplexer!
 - It could also be used as a digital MUX since logic levels are just voltages




- FET analog switches

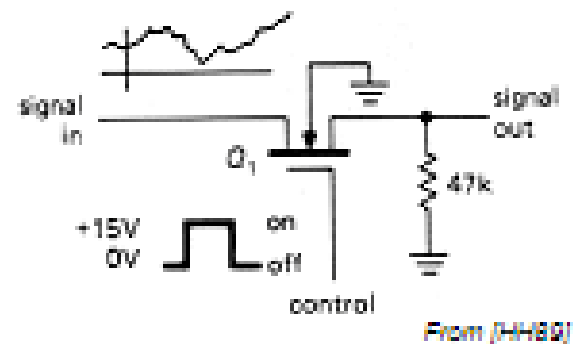- N-channel enhancement-mode MOS-FET
 - When Gate is grounded or negative, the FET is non-conducting
 - Drain-source resistance in the order of $10,000\text{M}\Omega$
 - Bringing the Gate to +15V puts the drain-source channel into conduction
 - Drain-source resistance in the order of 100Ω



Analog-to-digital converters

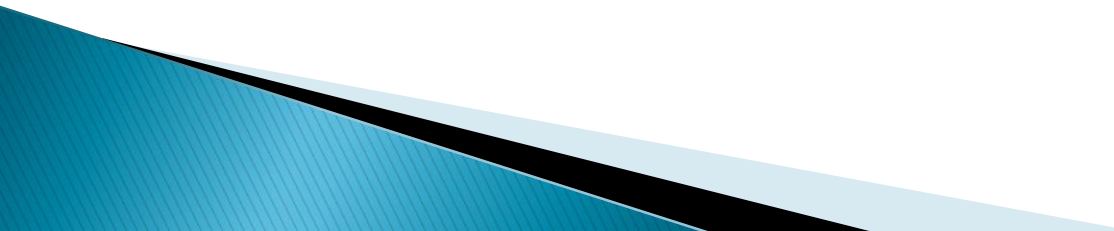- ▶ Single slope or ramp
 - ▶ Successive approximation
 - ▶ Dual slope
 - ▶ Parallel or 'flash'
- 

ADC

$$V_{in} \cong V_{REF} (B_1 * 2^{-1} + B_2 * 2^{-2} + \dots B_N * 2^{-n}) \cong \frac{N_{10}}{2^n} V_{REF}$$

$$N_{10} = INT\left(\frac{V_{in}}{V_{REF}} 2^n\right)$$

Note: In Bipolar ADC $V_{ref}/2$ should be subtracted

Example:

Temperature is to be measured by a sensor with an output of 0.02V/C. Determine required ADC (Reference, word size) to measure 0–100C with 0.1C resolution.

Solution

At max. temperature of 100C

$$.02 * 100 = 2V$$

So 2V reference is taken

A 0.1 C resolution results in $.1 * 0.02 = 2mV$


We need a word $2mV = 2(2 * \exp(-y))$

$$y \approx 9.996$$

Take $n = 10$.

Single slope or ramp ADC

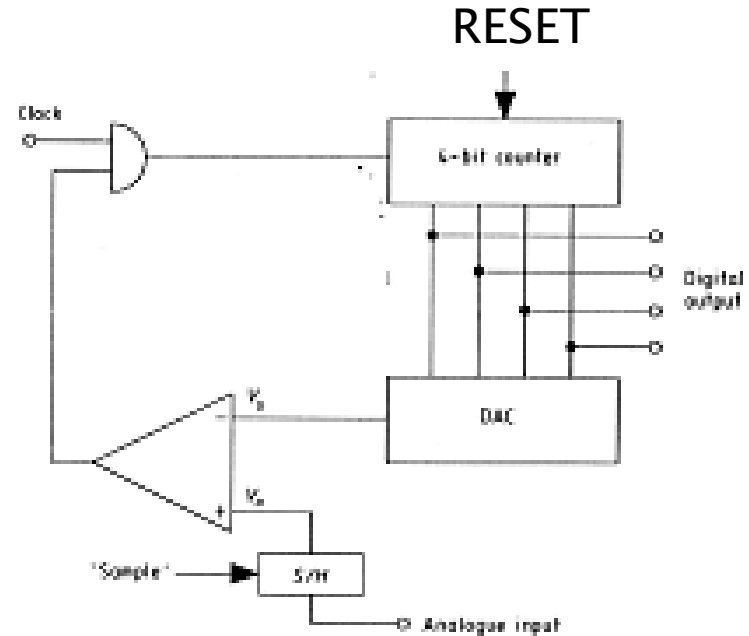- ▶ Composed of three basic elements
 - A binary counter
 - A digital-to-analog converter
 - An analog comparator



From [BWD61]


Operation

- Counter is reset
- Analog input is sampled
- While $V_A > V_B$ counter increments
- When $V_A = V_B$ counter stops and binary code is available at the output
- Characteristics
- Relatively slow since conversion time could be up to $2N$, where N is the resolution of the ADC

Successive approximation ADC

■ Basic elements

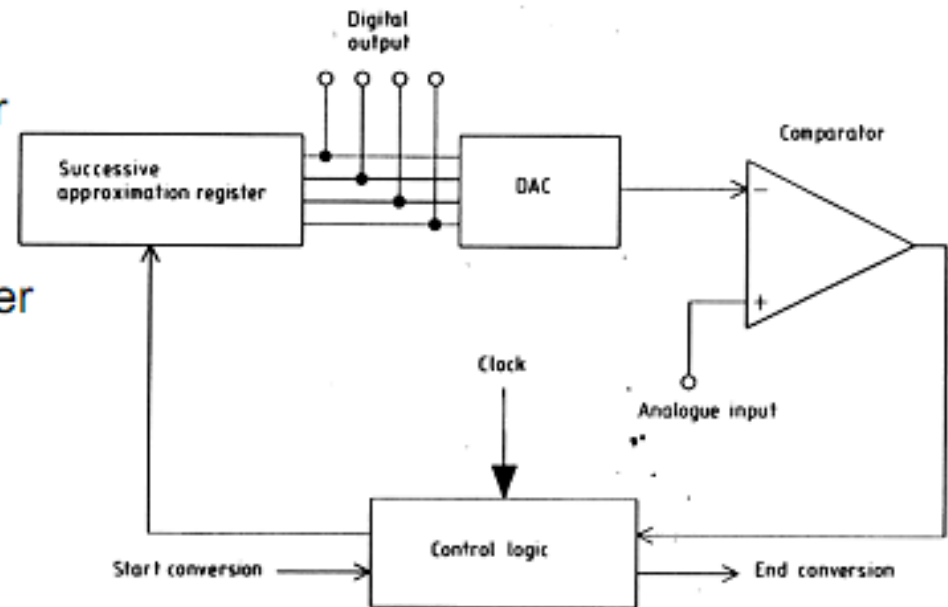- A digital-to-analog converter
- An analog comparator
- A control logic module
- A successive approx. register



From [BW96]


■ Operation is based on a binary search

- Initially, the register provides an output corresponding to half the range (1000...0)
 - If the analog input is greater, then MSB=1, else MSB=0
- The register performs the same operation from MSB to LSB


■ Characteristics

- Conversion requires only N steps, where N is the resolution of the ADC
 - Conversion times of μs are typical

Dual slope ADC

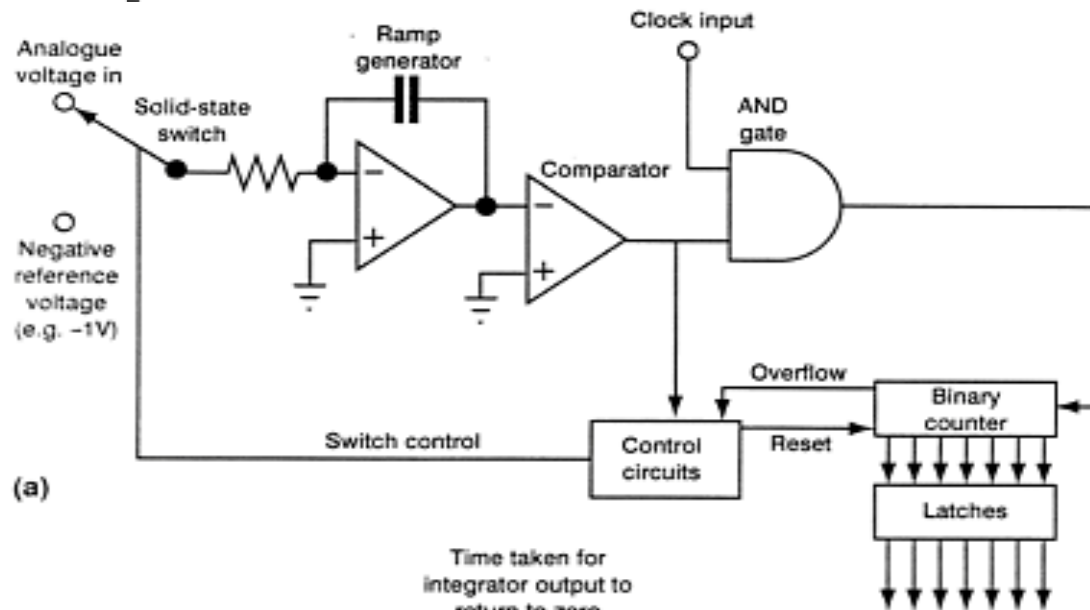

(a)

 

(b)

Dual slope ADC

■ Basic elements

- An integrator
- A zero-crossing detector
- A binary counter
- Logic gates and switches

■ Operation

- Counter is reset and switch is connected to the analog input
 - The integrator generates a negative ramp whose slope is proportional to the analog input
 - The comparator goes HIGH, enabling clock pulses into the counter
- When counter overflows, it resets to zero and the control circuit switches the switch to a reference negative voltage
 - This causes the integrator to generate a positive slope ramp
 - When this ramp reaches zero, the comparator goes low and stops the counter, whose value represents the analog input

■ Characteristics

- Very high resolution, but also slower (30 conversions/sec)
 - Widely used in digital multi-meters
- Insensitive to clock drift, RC drifts and high-frequency noise

Parallel or flash ADC

■ Basic elements

- A multiple voltage divider
- A set of comparators
- A priority encoder

■ Operation


- Analog input applied to all comparators
- Priority encoder converts comparator pattern into binary

■ E.g.: A 3-bit ADC:



- For comparator outputs of 0001111, priority encoder generates 100
- For comparator outputs of 0111111, priority encoder generates 110

■ Characteristics

 - Very fast (e.g., 8-bit ADCs capable of 20 million conversions/sec)
- Very expensive for large N since the number of comparators is $2^N - 1$




Flash ADC

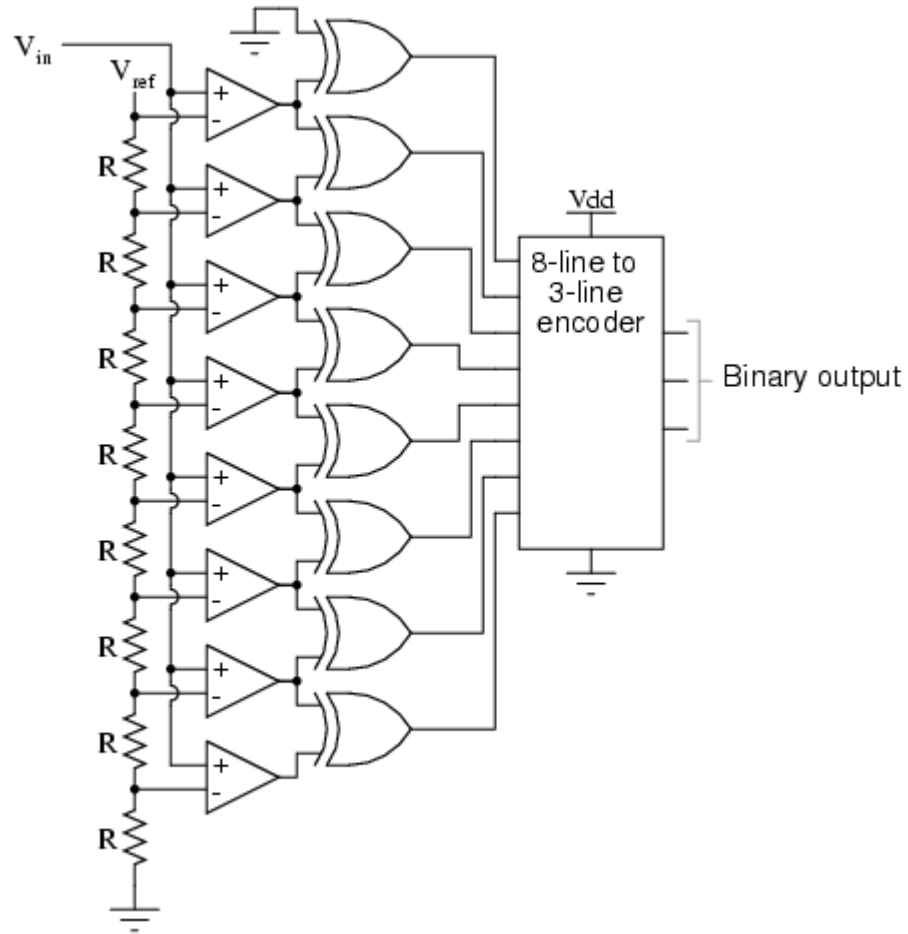 

ANALOG-TO-DIGITAL (A/D) CONVERSION

Flash ADC


- Example: 2 bit Flash ADC

 

- Needs: 3 comparators Use truth table to get output values:

- C1: $V > 1.25$
- C2: $V > 2.5$
- C3: $V > 3.75$

C3	C2	C1	MSB	LSB
0	0	0	0	0
0	0	1	0	1
0	1	0	X	X
0	1	1	1	0
1	0	0	X	X
1	0	1	X	X
1	1	0	X	X
1	1	1	1	1

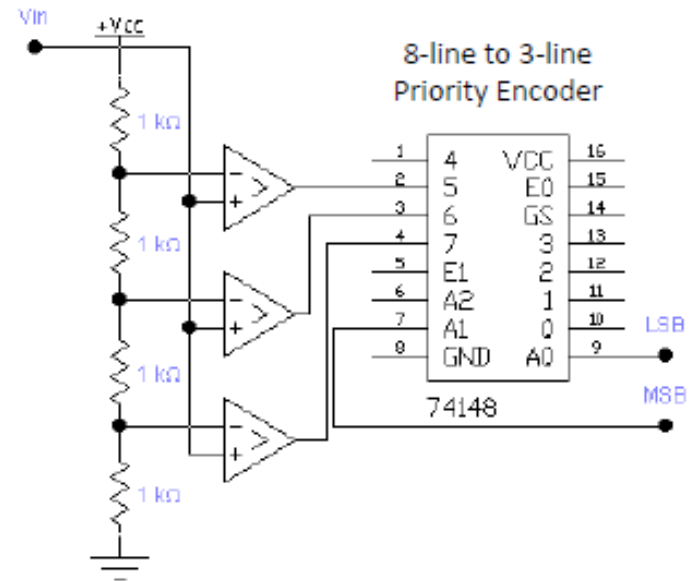


ANALOG-TO-DIGITAL (A/D) CONVERSION

Flash ADC

- Need to provide sample-and-hold at the input -- if input is changing during conversion, erroneous values will be produced.
- Output valid for only a short time after input is held.
- Requires $2^N - 1$ comparators.
- Adjacent comparators must have monotonic range change.

ANALOG-TO-DIGITAL (A/D) CONVERSION

Successive Approximation ADC:

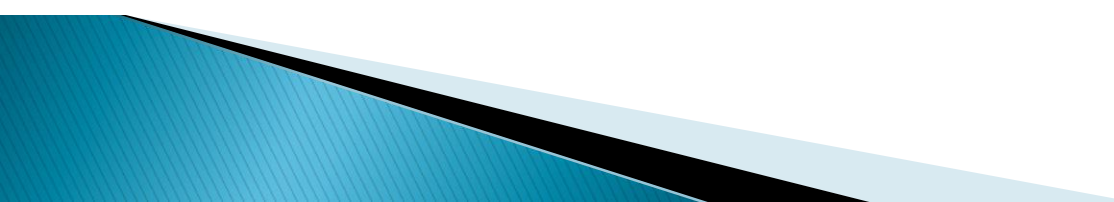- Workhorse method.
 - Used for wide variety of applications
 - Typical conversion time: 1 – 100 μ sec. Slower than flash ADC.
 - Easily extensible to higher precision.
 - Precision is limited by the quality of the components.
- 

SUCCESSIVE APPROXIMATION ADC

Basic idea: Check bits starting from the high order bit (MSB).

- Algorithm:


```
START CONVERSION
  SET Result to 0
  FOR i = N-1 TO 0
    SET i-th bit of Result to 1
    IF INPUT VOLTAGE < DtoA(Result)
      SET i-th bit of Result to 0
  END FOR-loop
  OUTPUT Result
END CONVERSION
```

This is a form of *interval halving*.

SUCCESSIVE APPROXIMATION ADC

General structure:

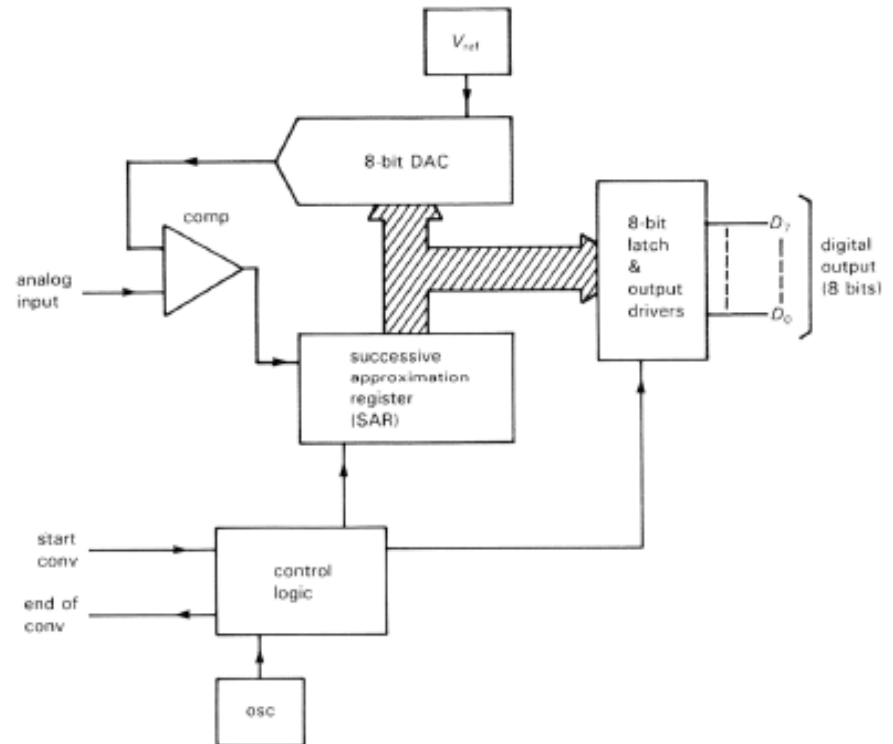
- Successive-approximation converters are quite expensive.
- Usually used with a multiplexer -- many channels feed to a single converter.
- Effective conversion speed for multiplexed ADC depends on number of channels used.
- Sample-and-hold normally precedes the converter.




SUCCESSIVE APPROXIMATION ADC

Arduino ADC

6-channel 10-bit ADC

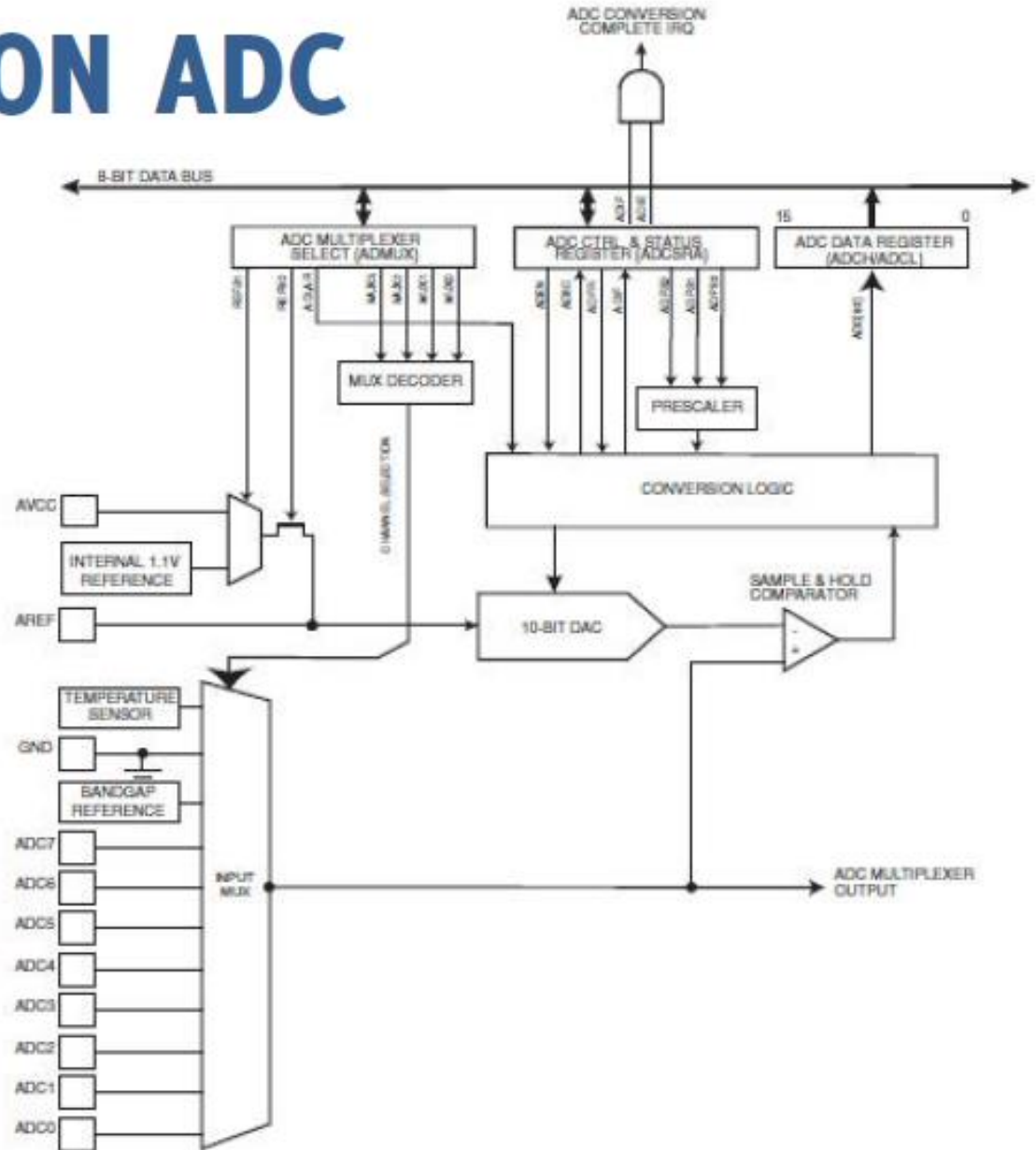

INTEGRATING CONVERTERS

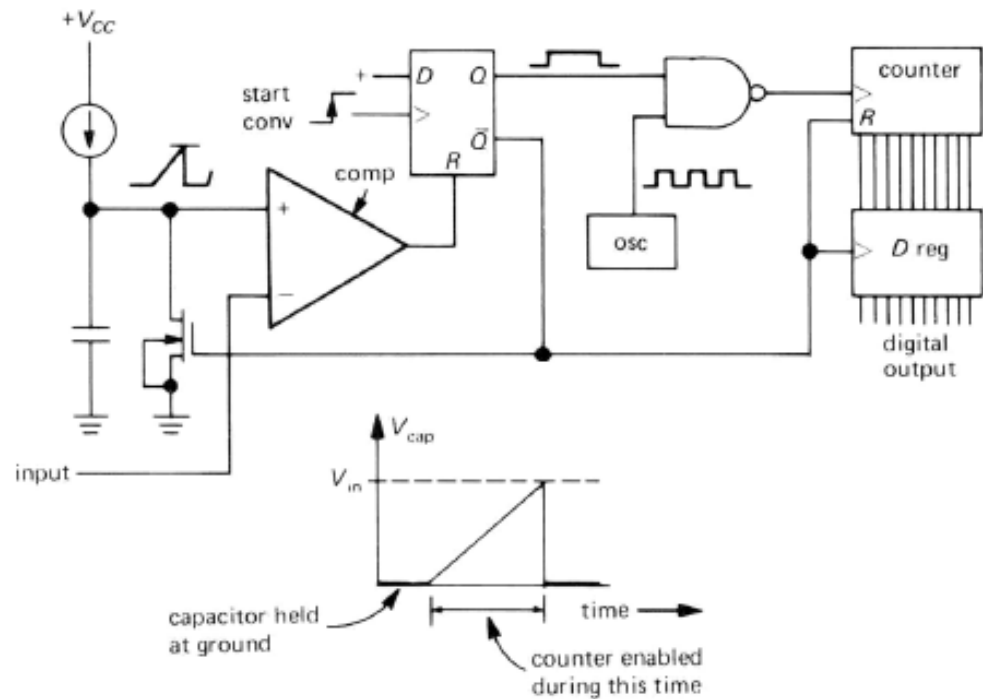



Slowest of the commonly used converters. Typical conversion time is many milliseconds.

Can be made very accurate and precise – used in DVMs (several conversion per second).


Uses timing to determine digital value of unknown (input) voltage.

INTERFACING WITH AN ADC

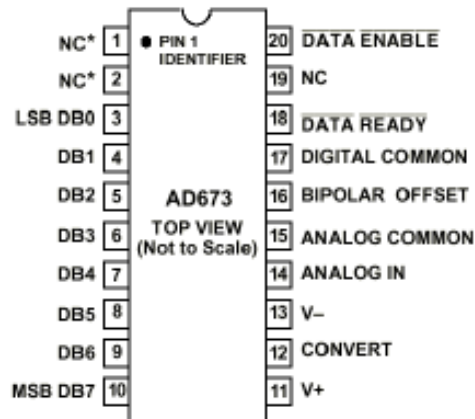
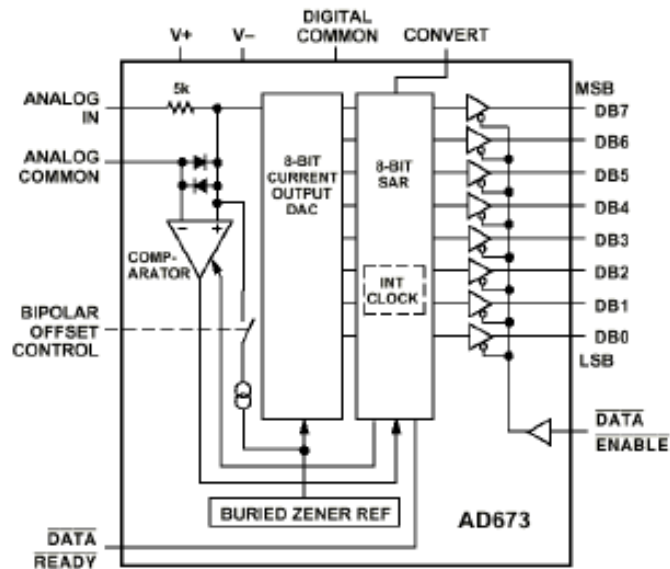
- Successive approximation ADC – use AD673 as example



Convert timing

 

Reading timing

  

ANALOG-TO-DIGITAL (A/D) CONVERSION

ADC with Serial Output

- Reduce pinouts and package size
- Can be easily interfaced with a microcontroller or a microprocessor with built in serial interface (SCLK, SDATA, T/R)
- Sample rate limited by the maximum SCLK rate.
- Use AD7476 as example – 1 MSPS 6 pin ADC

