

Interfacing Circuits

- ▶ Measurement of resistance
 - Voltage dividers
 - Wheatstone Bridge
 - Temperature compensation for strain gauges
- ▶ AC bridges
 - Measurement of capacitance
 - Measurement of impedance

Capacitors and inductors

- ▶ A capacitor is an element capable of storing charge
 - The amount of charge is proportional to the voltage across the capacitor

$$Q = CV$$

- C is known as the capacitance (measured in Farads)
- Taking derivatives

$$\frac{dQ}{dt} = \frac{d(CV)}{dt} \Rightarrow I = C \frac{dV}{dt}$$

- Therefore, a capacitor is an element whose rate of voltage change is proportional to the current through it
- ▶ Similarly, an inductor is an element whose rate of current change is proportional to the voltage applied across it

$$V = L \frac{dI}{dt}$$


- L is called the inductance and is measured in Henrys

High Pass Filter

- High pass filter

- The current through cap and resistor is
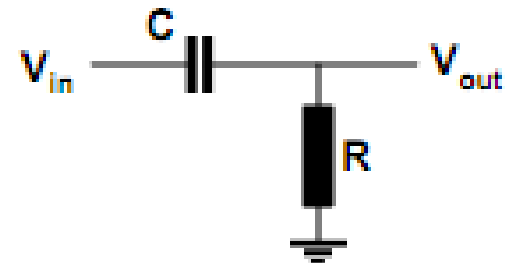
$$I = \frac{V_{in}}{Z} = \frac{V_{in}}{R + \frac{1}{j\omega C}}$$



- The output voltage is equal to the voltage differential across the resistor

$$V_{out} = RI = R \frac{V_{in}}{R + \frac{1}{j\omega C}}$$

- If we focus on amplitude and ignore phase

$$|V_{out}| = R \frac{|V_{in}|}{\left| R + \frac{1}{j\omega C} \right|} = R \frac{|V_{in}|}{\sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}} = |V_{in}| \frac{\omega RC}{\sqrt{(\omega RC)^2 + 1}}$$

- Asymptotic behavior...

- Corner frequency $\omega_{CORNER} = \frac{1}{RC} \Rightarrow 20 \log_{10} \frac{|V_{out}|}{|V_{in}|} = 20 \log_{10} \frac{1}{\sqrt{1+1}} = -3.010 \text{ dB}$

Voltage divider

► Assumptions

- Interested in measuring the fractional change in resistance x of the sensor:
 $R_s = R_0(1+x)$
 - R_0 is the sensor resistance in the absence of a stimuli
- Load resistor expressed as $R_L = R_0 k$ for convenience



► The output voltage of the circuit is

$$\begin{aligned} V_{out} &= V_{CC} \frac{R_L}{R_s + R_L} = \\ &= V_{CC} \frac{R_0(1+x)}{R_0(1+x) + R_0 k} = V_{CC} \frac{1+x}{1+x+k} \end{aligned}$$

Questions

What if we reverse R_s and R_L ?

How can we recover R_s from V_{out} ?

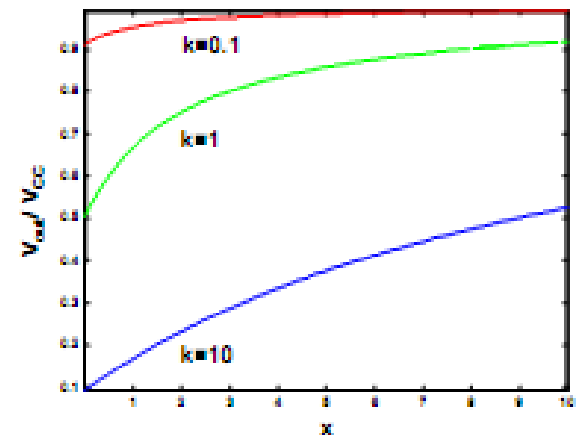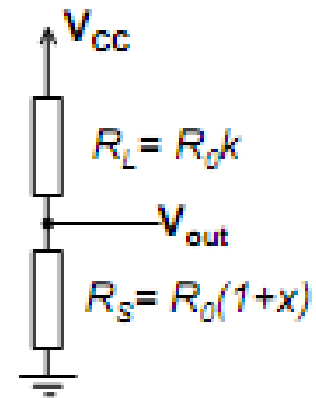

Voltage Divider


- What is the sensitivity of this circuit?

$$\begin{aligned} S &= \frac{dV_{out}}{dx} = \frac{d}{dx} \left(V_{CC} \frac{1+x}{1+x+k} \right) = \\ &= V_{CC} \frac{(1+x+k) - (1+x)}{(1+x+k)^2} = \\ &= V_{CC} \frac{k}{(1+x+k)^2} \end{aligned}$$

- For which R_L do we achieve maximum sensitivity?

$$\frac{dS}{dk} = 0 \Rightarrow \frac{d}{dk} \left(V_{CC} \frac{k}{(1+x+k)^2} \right) = 0 \Rightarrow \frac{(1+x+k)^2 - k2(1+x+k)}{(1+x+k)^2} = 0 \Rightarrow k = 1+x$$

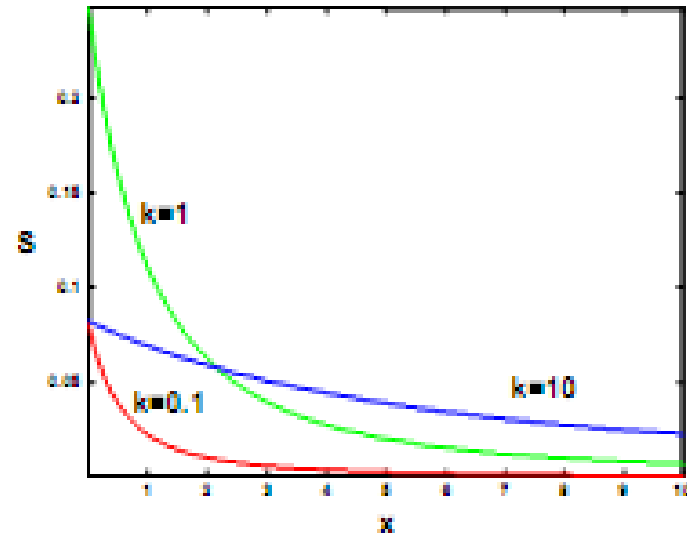- This is, the sensitivity is maximum when $R_L = R_S$



Wheatstone bridge

- A circuit that consists of two dividers

- A reference voltage divider (left)
- A sensor voltage divider

- Wheatstone bridge operating modes

- Null mode
 - R_4 adjusted until the balance condition is met:

$$V_{out} = 0 \Leftrightarrow R_3 = R_4 \frac{R_2}{R_1}$$


- Advantage: measurement is independent of fluctuations in V_{CC}

- Deflection mode

- The unbalanced voltage V_{out} is used as the output of the circuit

$$V_{out} = V_{CC} \left(\frac{R_3}{R_2 + R_3} - \frac{R_4}{R_3 + R_4} \right)$$

- Advantage: speed

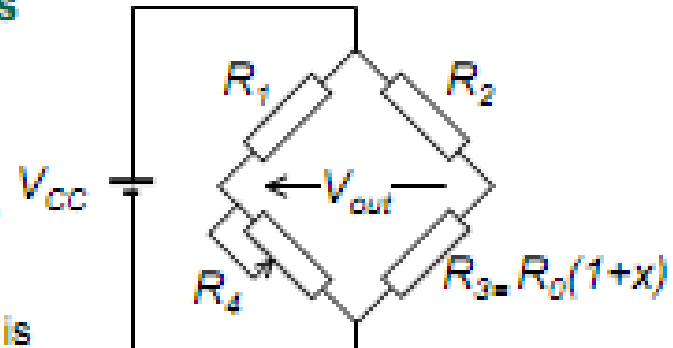


Wheatstone bridge

■ Assumptions

- Want to measure sensor fractional resistance changes $R_S = R_0(1+x)$
- Bridge is operating near the balance condition:
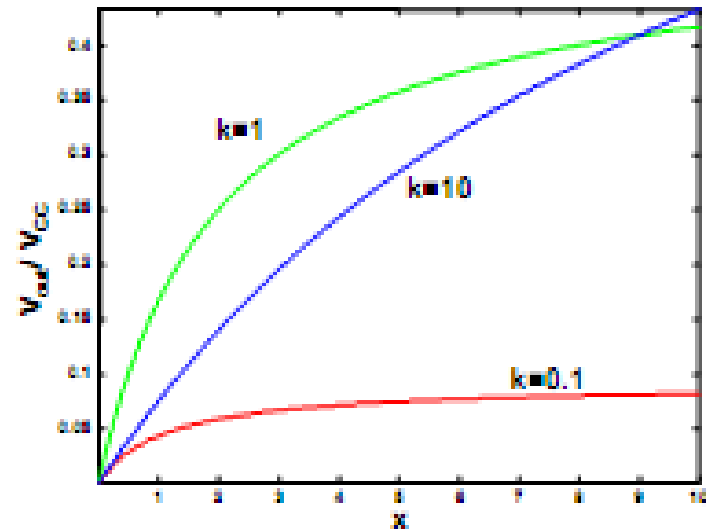
$$k = \frac{R_1}{R_4} = \frac{R_2}{R_0}$$



■ The output voltage becomes

$$\begin{aligned} V_{out} &= V_{CC} \left(\frac{R_0(1+x)}{R_0k + R_0(1+x)} - \frac{R_4}{R_4k + R_4} \right) = \\ &= V_{CC} \left(\frac{(1+x)}{k + (1+x)} - \frac{1}{k+1} \right) = V_{CC} \frac{kx}{(1+k)(1+k+x)} \end{aligned}$$


- ▶ What is the sensitivity of the Wheatstone bridge?

$$\begin{aligned} S &= \frac{dV_{out}}{dx} = V_{cc} \frac{d}{dx} \left(\frac{kx}{(1+k)(1+k+x)} \right) = \\ &= V_{cc} \frac{k(1+k)(1+k+x) - kx(1+k)}{(1+k)^2(1+k+x)^2} = \\ &= V_{cc} \frac{k}{(1+k+x)^2} \end{aligned}$$

- ❑ The sensitivity of the Wheatstone bridge is the same as that of a voltage divider
 - You can think of the Wheatstone bridge as a DC offset removal circuit
- ❑ So what are the advantages, if any, of the Wheatstone bridge?



Voltage divider vs. Wheatstone for small x

- ▶ The figures below show the output of both circuits for small fractional resistance changes
 - The voltage divider has a large DC offset compared to the voltage swing, which makes the curves look “flat” (zero sensitivity)
 - Imagine measuring the height of a person standing on top of a tall building by running a large tape measure from the street
- ▶ The sensitivity of both circuits is the same!
 - However, the Wheatstone bridge sensitivity can be boosted with a gain stage
 - Assuming that our DAQ hardware dynamic range is 0–5VDC, $0 < x < 0.01$ and $k=1$, estimate the maximum gain that could be applied to each circuit

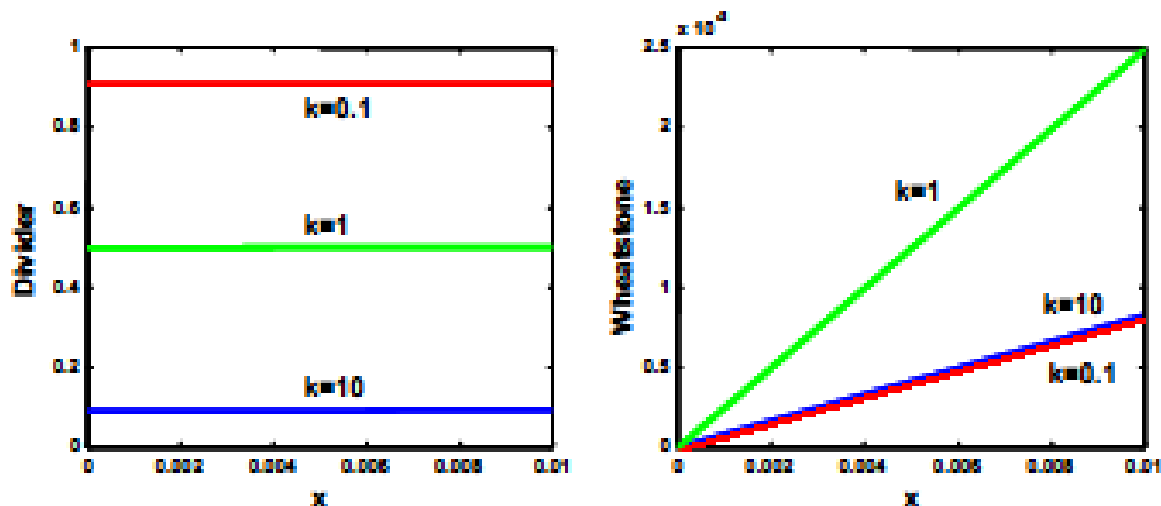

Compensation in a Wheatstone bridge

- ▶ Strain gauges are quite sensitive to temperature
 - A Wheatstone bridge and a dummy strain gauge may be used to compensate for this effect
 - The “active” gauge R_A is subject to temperature (x) and strain (y) stimuli
 - The dummy gauge R_D , placed near the “active” gauge, is only subject to temperature
 - The gauges are arranged according to the figures below
 - The effect of $(1 + y)$ on the right divider cancels out

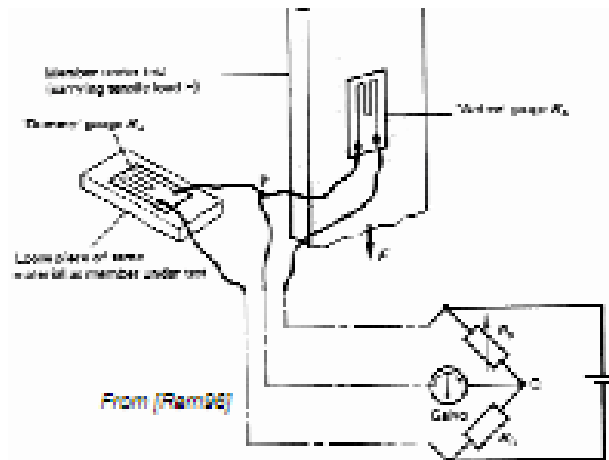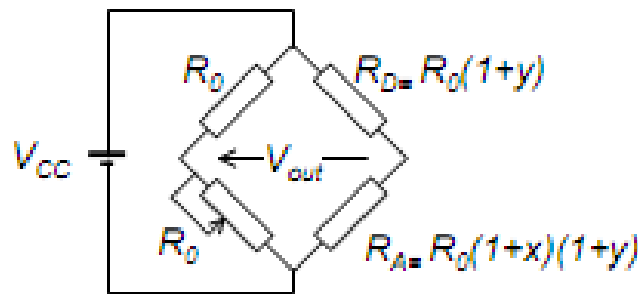

AC bridges

- **The structure of the Wheatstone bridge can be used to measure capacitive and inductive sensors**

- Resistance replaced by generalized impedance
- DC bridge excitation replaced by an AC source


- **The balance condition becomes**

$$\frac{Z_1}{Z_4} = \frac{Z_2}{Z_3}$$

- which yields two equalities, for real and imaginary components

$$R_1 R_3 - X_1 X_3 = R_2 R_4 - X_2 X_4$$
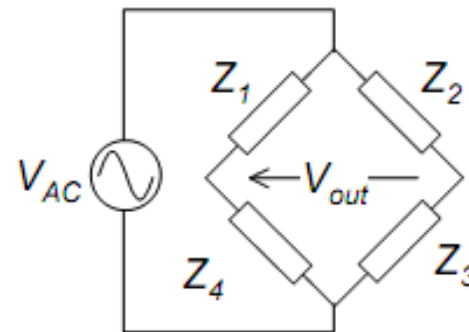
$$R_1 X_3 + X_1 R_3 = R_2 X_4 + X_2 R_4$$





- **There is a large number of AC bridge arrangements**

- These are named after their respective developer

AC Bridges



■ Capacitance measurement

- Schering bridge
- Wien bridge

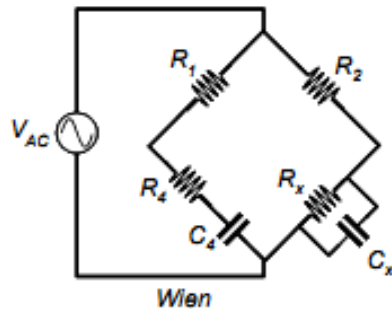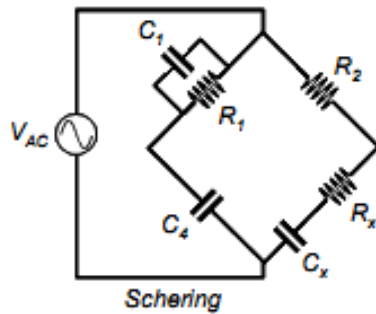


■ Inductance measurement

- Hay bridge
- Owen bridge

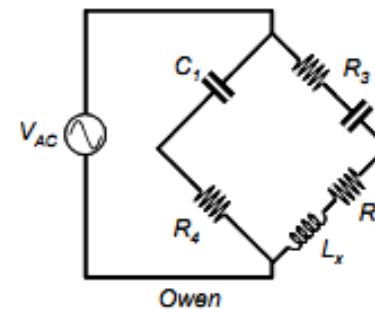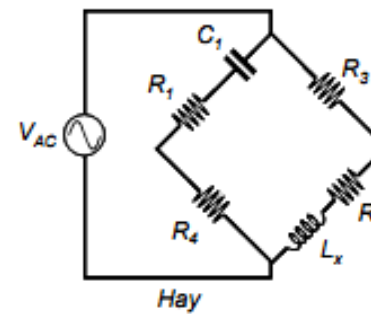

The ideal operational amplifier

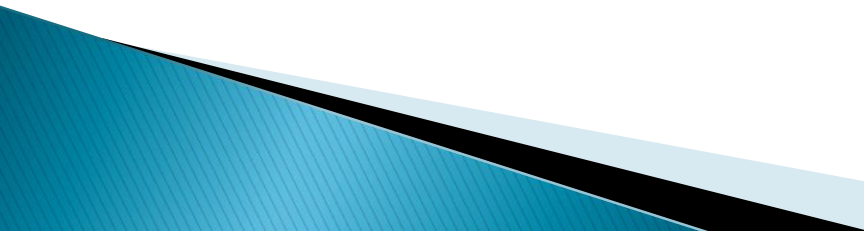- ▶ The ideal operational amplifier
 - Terminals
 - Basic ideal op-amp properties
 - ▶ Op-amp families
 - ▶ Operational amplifier circuits
 - Comparator and buffer
 - Inverting and non-inverting amplifier
 - Summing and differential amplifier
 - Integrating and differentiating amplifier
 - Current-voltage conversion
- 

The ideal op-amp

- ▶ Primary op-amp terminals
 - Inverting input
 - Non-inverting input
 - Output
 - Power supply

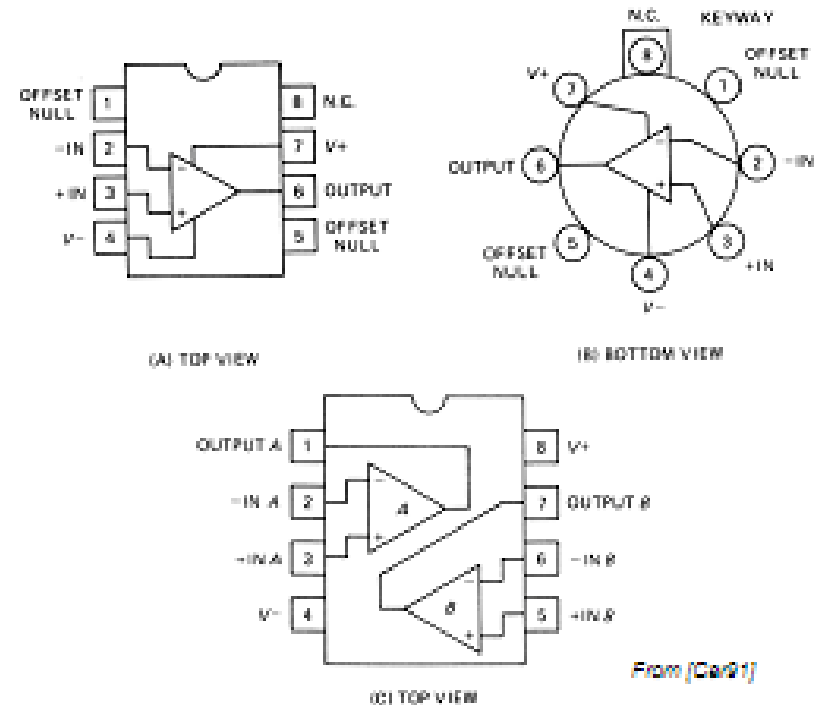


Fig. 12-6 Packaging for industry standard op-amp (741) in (A) DIP and (B) metal can packages, (C) dual op-amp such as 1458 device.

Ideal op-amp characteristics

- ▶ The ideal op-amp is characterized by seven properties
 - Knowledge of these properties is sufficient to design and analyze a large number of useful circuits
- ▶ Basic op-amp properties
 - Infinite open-loop voltage gain
 - Infinite input impedance
 - Zero output impedance
 - Zero noise contribution
 - Zero DC output offset
 - Infinite bandwidth
 - Differential inputs that stick together

Ideal Op-Amp Properties

- ▶ Property No.1: Infinite Open-Loop Gain
 - Open-Loop Gain A_{vol} is the gain of the op-amp without positive or negative feedback
 - In the ideal op-amp A_{vol} is infinite
 - Typical values range from 20,000 to 200,000 in real devices
- ▶ Property No.2: Infinite Input Impedance

- Input impedance is the ratio of input voltage to input current


$$Z_{in} = \frac{V_{in}}{I_{in}}$$

- When Z_{in} is infinite, the input current $I_{in}=0$
 - High-grade op-amps can have input impedance in the T Ω range
 - Some low-grade op-amps, on the other hand, can have mA input currents

Ideal Op-Amp Properties

▶ Property No. 3: Zero Output Impedance

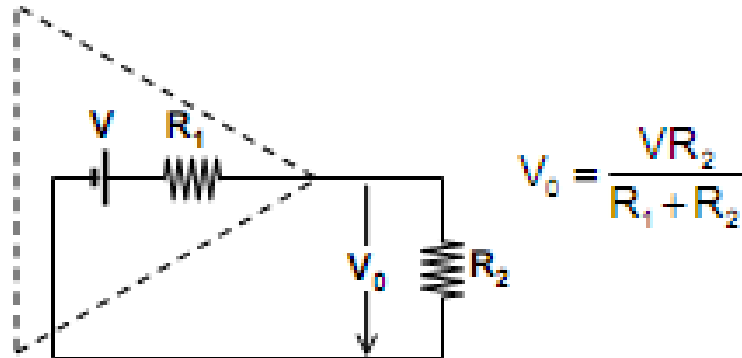
- The ideal op-amp acts as a perfect internal voltage source with no internal resistance
 - This internal resistance is in series with the load, reducing the output voltage available to the load
 - Real op-amps have output-impedance in the 100–20Ω range
- Example



$$V_0 = \frac{VR_2}{R_1 + R_2}$$

Ideal Op-Amp Properties

- ▶ Property No.4: Zero Noise Contribution
 - In the ideal op-amp, zero noise voltage is produced internally
 - This is, any noise at the output must have been at the input as well
 - Practical op-amp are affected by several noise sources, such as resistive and semiconductor noise
 - These effects can have considerable effects in low signal-level applications
- ▶ Property No. 5: Zero output Offset
 - The output offset is the output voltage of an amplifier when both inputs are grounded
 - The ideal op-amp has zero output offset, but real op-amps have some amount of output offset voltage

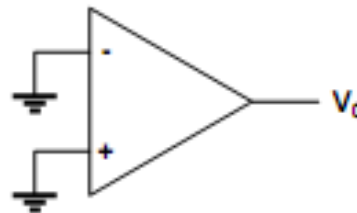

Ideal Op–Amp Properties

- ▶ **Property No. 6: Infinite Bandwidth**
 - The ideal op–amp will amplify all signals from DC to the highest AC frequencies
 - In real opamps, the bandwidth is rather limited
 - This limitation is specified by the Gain–Bandwidth product (GB), which is equal to the frequency where the amplifier gain becomes unity
 - Some op–amps, such as the 741 family, have very limited bandwidth of up to a few KHz
- ▶ **Property No. 7: Differential Inputs Stick Together**
 - In the ideal op–amp, a voltage applied to one input also appears at the other input

Operational amplifier types

▶ General-Purpose Op-Amps

- These devices are designed for a very wide range of applications
 - These op-amps have limited bandwidth but in return have very good stability (they are called frequency compensated)
 - Non-compensated op-amps have wider frequency response but have a tendency to oscillate

▶ Voltage Comparators

- These are devices that have no negative feedback networks and therefore saturate with very low (μV) input signal voltages
 - Used to compare signal levels of the inputs

▶ Low Input Current Op-Amps

- Op-amps with very low (pico-amp) input currents, as opposed to μA or mA input currents found in other devices

▶ Low Noise Op-Amps

- Optimized to reduce internal noise
 - Typically employed in the first stages of amplification circuits

▶ Low Power Op-Amps

- Optimized for low power consumption
 - These devices can operate at low power-supply voltages (i.e., $\pm 1.5\text{VDC}$)

▶ Low Drift Op-Amps


- Internally compensated to minimize drift caused by temperature
 - Typically employed in instrumentation circuits with low-level input signals

Operational amplifier types

- ▶ **Wide Bandwidth Op–Amps**
 - These devices have a very high GB product (i.e., 100MHz) compared to 741–type op–amps (0.3–1.2MHz)
 - These devices are sometimes called video op–amps
- ▶ **Single DC Supply Op–Amps**
 - Devices that operate from a monopolar DC power supply voltage
- ▶ **High–Voltage Op–Amps**
 - Devices that operate at high DC power supply voltages (i.e. $\pm 44\text{VDC}$) compared to most other op–amps ($\pm 6\text{V}$ to $\pm 22\text{V}$)
- ▶ **Multiple Devices**
 - Those that have more than one op–amp in the same package (i.e., dual or quad op–amps)
- ▶ **Instrumentation Op–Amps**
 - These are DC differential amplifiers made with 2–3 internal op–amps
 - Voltage gain is commonly set with external resistors

Families of operational amplifiers



Table 12-1
Families of Operational Amplifiers

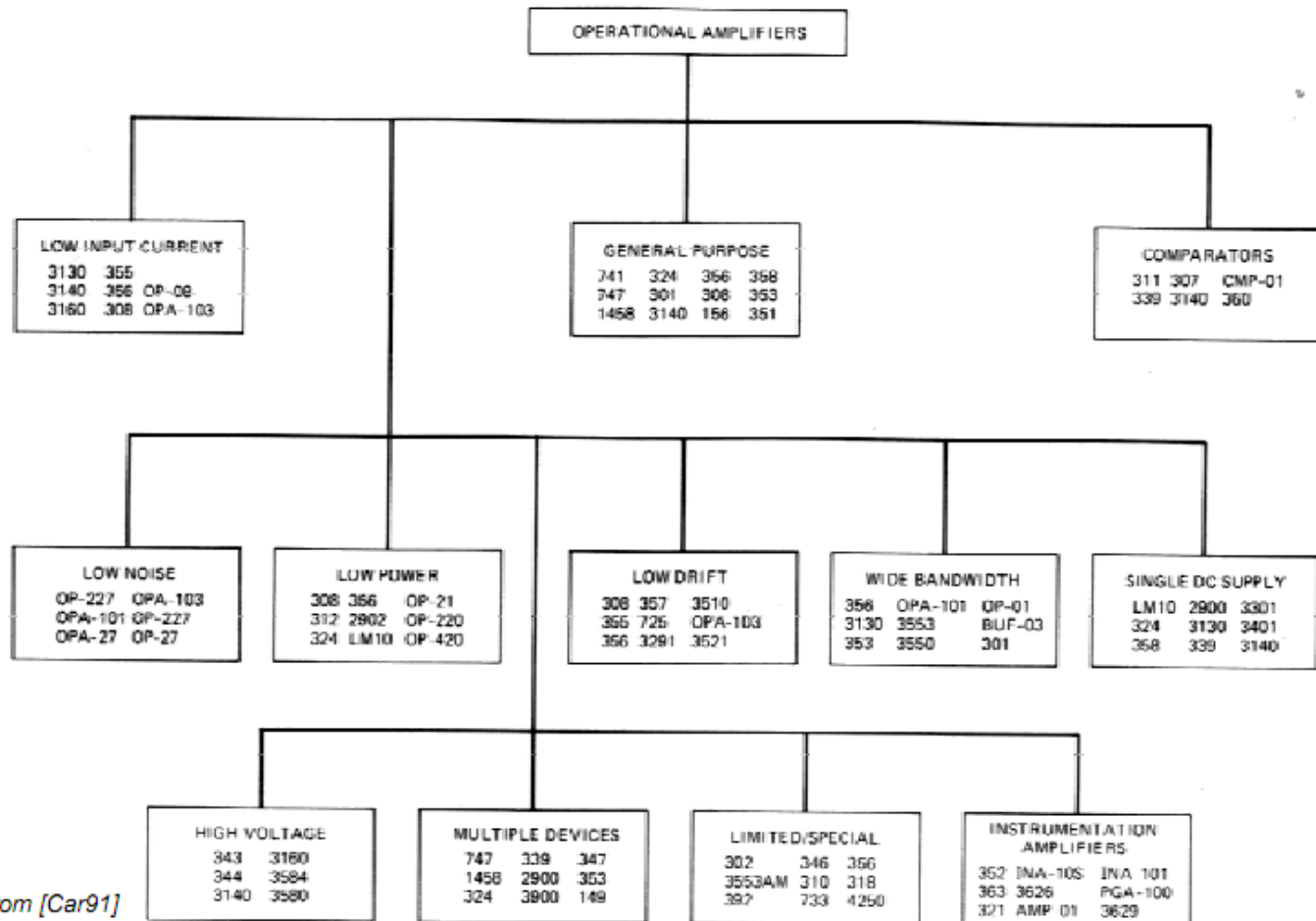

From [Car91]


Op-amp practical circuits

■ Voltage comparator

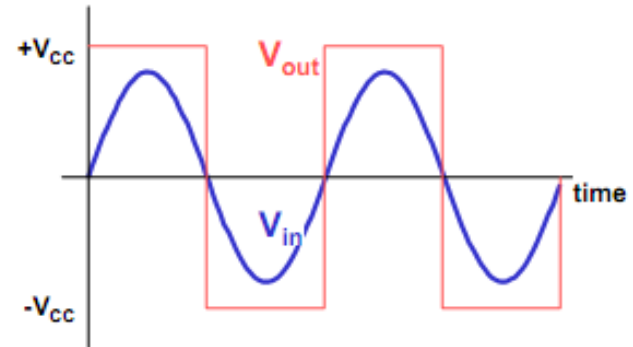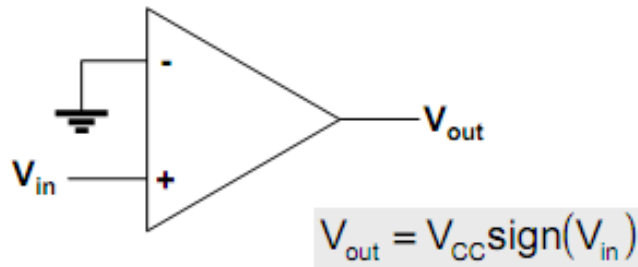


■ Voltage follower

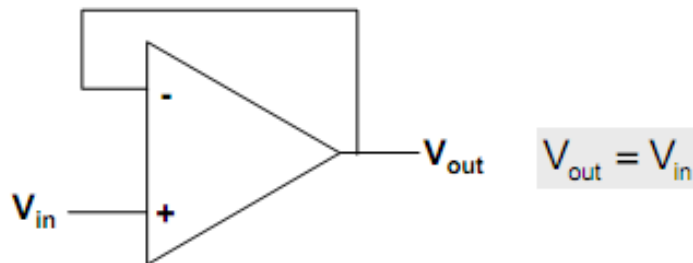- What is the main use of this circuit?
 - Buffering




Inverting and non-inverting amplifiers

■ Non-inverting amplifier

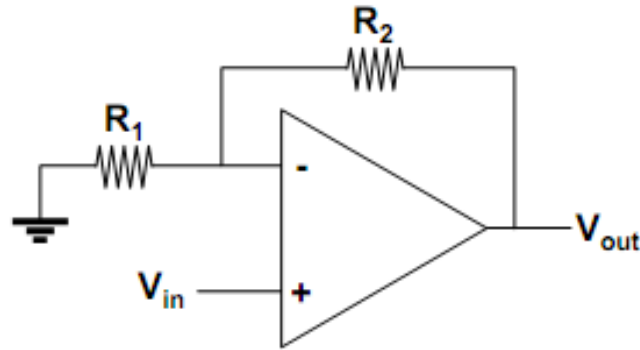

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$


■ Inverting amplifier

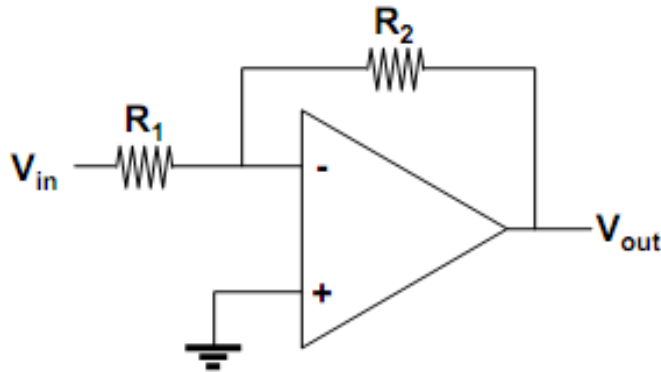

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$


Summing and differential amplifier

■ Summing amplifier

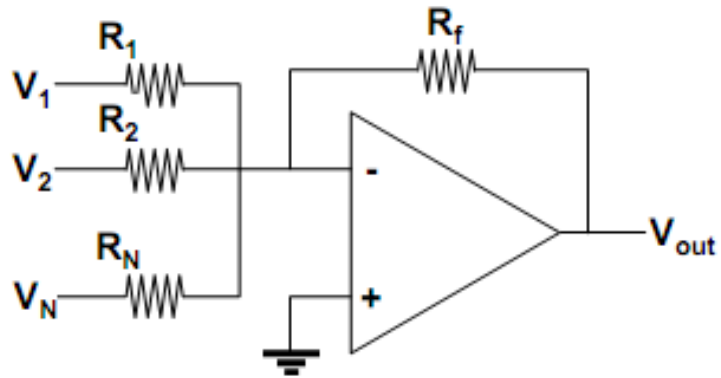

$$V_{out} = - \left(V_1 \frac{R_f}{R_1} + V_2 \frac{R_f}{R_2} + \dots + V_N \frac{R_f}{R_N} \right)$$


■ Differential amplifier

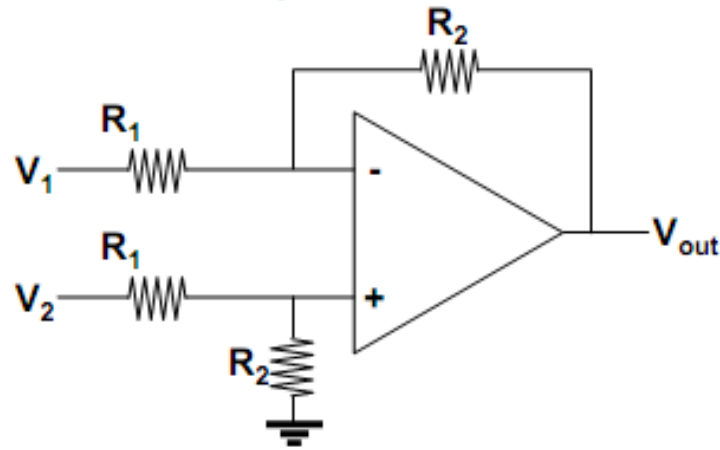

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$


Integrating and differentiating amplifier

■ Integrating amplifier

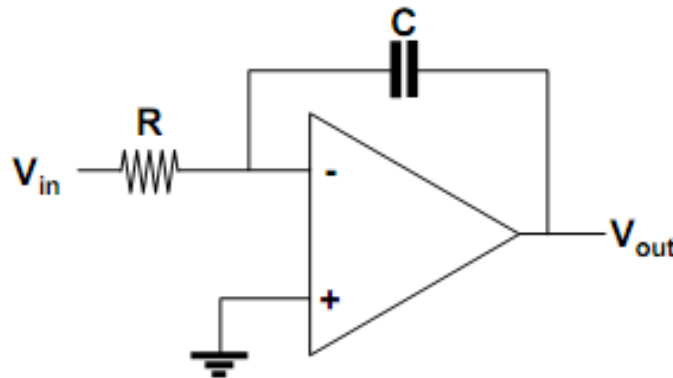

$$V_{out} = -\frac{1}{j\omega CR} V_{in} = -\frac{1}{RC} \int V_{in} dt$$


■ Differentiating amplifier

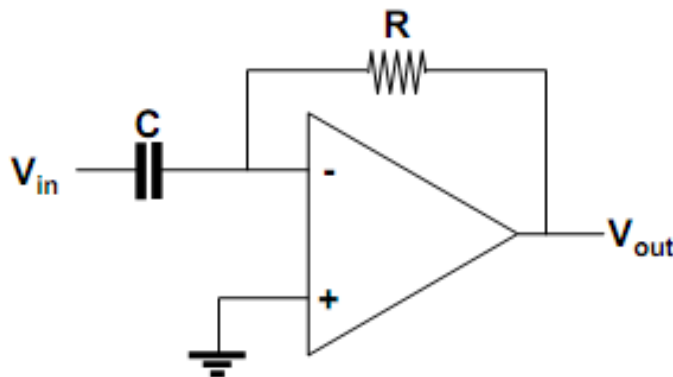


$$V_{out} = -\frac{R}{\frac{1}{j\omega C}} V_{in} = -RC \frac{dV_{in}}{dt}$$

Current to voltage conversion

■ Current-to-voltage

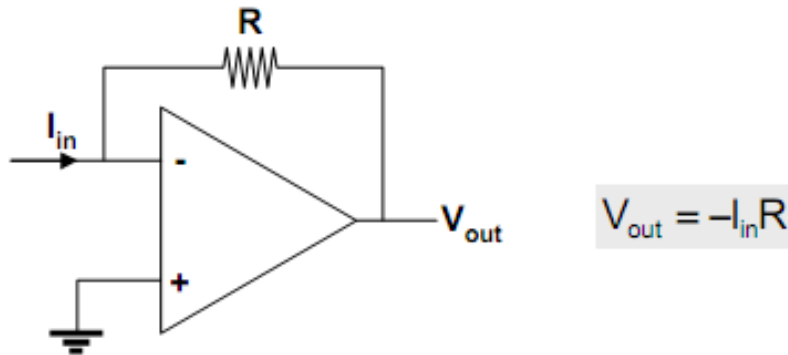

■ Voltage to current

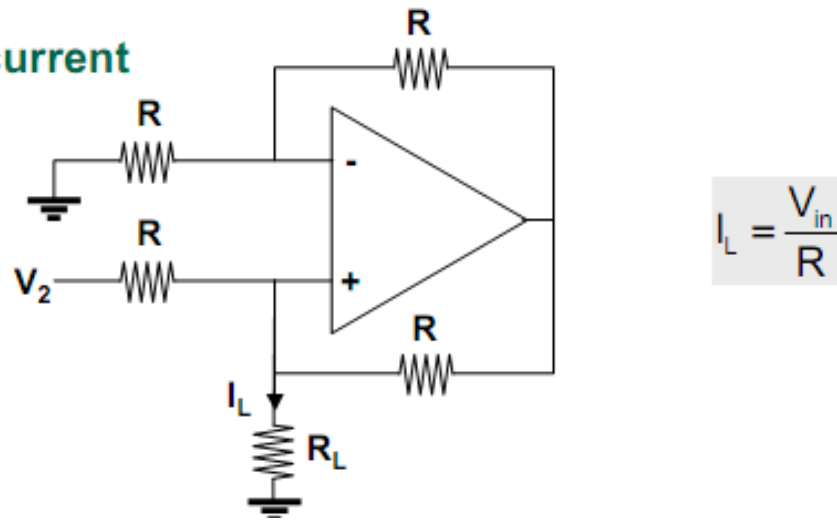

References

- ▶ [1] J. C. Whitaker, 1996, The Electronics Handbook, CRC Press
 - ▶ [2] P. Elgar, 1998, Sensors for Measurement and Control, Addison Wesley Longman, Essex, UK.
 - ▶ [3] R. Pallas–Areny and J. G. Webster, 1991, Sensors and Signal Conditioning, Wiley, New York
- 