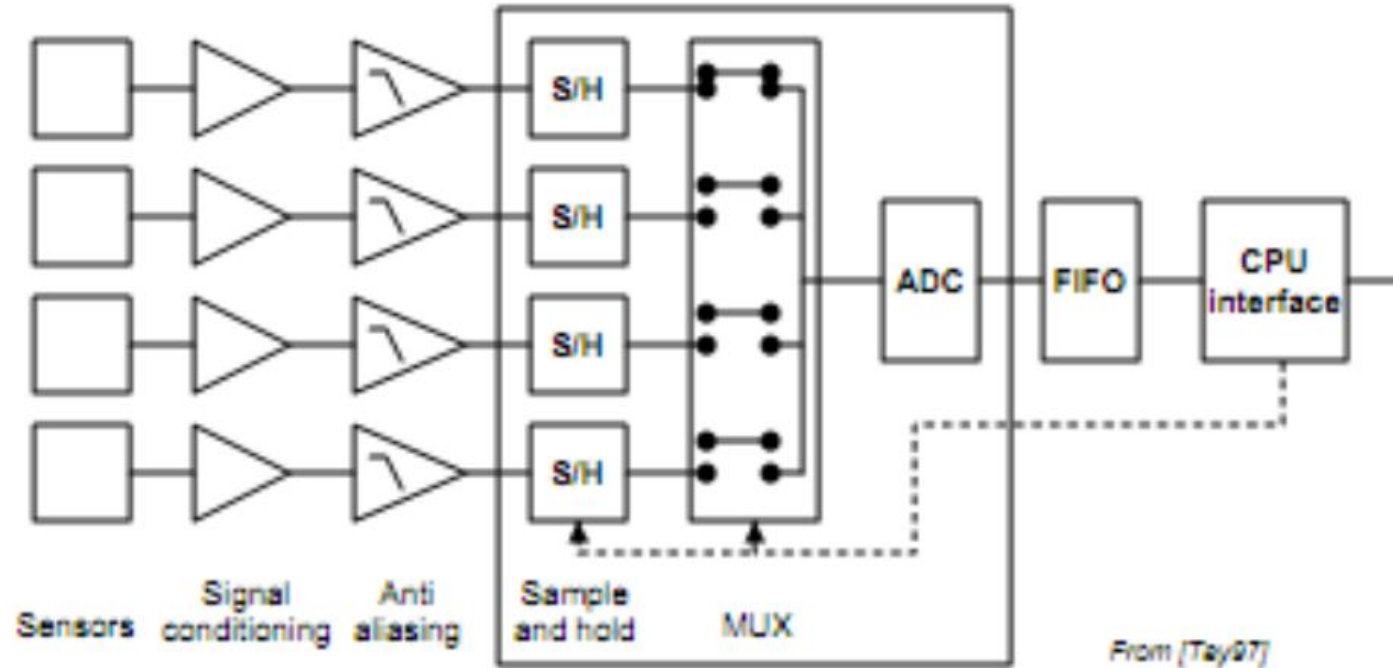


Data Acquisition II

- ▶ Sample and hold
- ▶ Multiplexing
- ▶ Analog to digital conversion
- ▶ Digital to analog conversion

Architecture of data acquisition systems



ANALOG \Leftrightarrow DIGITAL CONVERSION

Physical world is analog (mostly)


Analog is infinitely variable, while digital is discrete in both time and value

Analog/digital conversion can be part of the instrument or part of the actuator, e.g.

- Incremental encoder – analog position gets encoded into digital pulse
- Stepper motor – digital step pulse gets transformed to analog position

ANALOG \Leftrightarrow DIGITAL CONVERSION

 To be processed by computers, all information must be converted to a binary representation possessing a finite number of distinct values that combine logical low (0) and logical high (1):



Digital coding is arbitrary, but natural binary order is most often used

ANALOG ↔ DIGITAL CONVERSION

For notational compactness and ease of reading, binary (base 2) representations are often expressed in octal (base 8) or hexadecimal (base 16):

$$10100110_2 = 0246_8 = 166_{10} = A6_{16}$$

Arduino code:

Binary:	<code>B10100110</code>	(leading 'B', only 8-bit values)
Octal:	<code>0246</code>	(leading '0')
Decimal:	<code>166</code>	(no formatting needed)
Hexadecimal:	<code>0xA6</code>	(leading "0x", chars 0-9, A-F, a-f)

DIGITAL REPRESENTATION

When using natural binary order, the digital code consists of an N -bit binary word:

$$b_{N-1} b_{N-2} b_{N-3} \dots b_1 b_0$$

where b_{N-1} is the most-significant bit (MSB) and b_0 is the least-significant bit (LSB)

8-bit digital word: **byte** (or octet).

4-bit digital word: **nibble** (or quartet).

DIGITAL REPRESENTATION

The fractional value of the digital word is:

$$2^{-1} b_{N-1} + 2^{-2} b_{N-2} + 2^{-3} b_{N-3} + \dots + 2^{-N} b_0$$

with a range of $0 \rightarrow (1 - 2^{-N})$ and a precision of 2^{-N}

Digital fractions sometimes notated with leading point notation:

$$.1011_2 = .6875_{10}$$

Example:


- 4-bits
- Range = $0 \rightarrow (1 - 2^{-4}) = 0 \rightarrow \frac{15}{16}$ (nearly 1)
- Precision (absolute and relative) = $2^{-4} = \frac{1}{16}$
- Code of 1011 = $\frac{1}{2} + \frac{1}{8} + \frac{1}{16} = \frac{11}{16} = .6875$

DIGITAL REPRESENTATION

- Digital codes have no inherent units, so scaling must be defined for code to have real-world meaning.
- How to assign relationship between binary code and analog values? It depends on the application...


DIGITAL REPRESENTATION

 For a unipolar signal, it seems obvious to associate V_{\min} with binary zero. Do we associate V_{\max} with binary 2^N (fractional value of 1), or with binary 2^N-1 (and its fraction value of $1-2^{-N}$)?




DIGITAL REPRESENTATION

 To maximize the conversion range for N-bit coding of a *unipolar* value, we often associate V_{\min} with binary zero and V_{\max} with binary 2^N-1 . For example, for a 0-10V signal, we may assign values such that:



DIGITAL REPRESENTATION

 
However, it is common to associate a reference value of V_{ref} with the digital code used to denote a fraction of 1



DIGITAL REPRESENTATION


In such an arrangement, with $V_{\min} = 0$,
 
$$V_{fs} = V_{\max} = V_{\text{ref}} \left(\frac{2^N - 1}{2^N} \right)$$



DIGITAL REPRESENTATION

 
If V_{\min} is less than binary zero, or V_{\max} is more than binary 2^N-1 , then *amplitude clipping* may result.



DIGITAL REPRESENTATION

Quantization Level: change in analog output associated with each discrete step

 - We assume this step size to be fixed, although in sophisticated applications, it may vary across the signal range, or adapt to signal characteristics.



DIGITAL REPRESENTATION

Quantization Level (Q)

- Signal change associated with LSB
- For an N-bit converter:

- $$Q = \frac{V_{\text{fullscale}}}{2^N - 1} = \frac{V_{\text{ref}}}{2^N}$$

- Quantization *error* ranges from $-\frac{Q}{2}$ to $+\frac{Q}{2}$

Example:

- 4-bits, 12 volts full-scale, binary code of 1001
- $Q = 12V / (2^4 - 1) = .8V$
- $|Q_{\text{error}}| \leq .4V$
- $V_{\text{analog}} = Q \times (8 \cdot 1 + 4 \cdot 0 + 2 \cdot 0 + 1) = .8V \times 9 = 7.2V$

DIGITAL REPRESENTATION

Quantization

- An irreversible process
- A source of information loss
- Increasing the number of bits lowers information loss, but usually raises the cost and processing time

Example:

- 10 volts full-scale, with 1% precision required
- $Q = 1\% \cdot 10 = 0.1V$
- $N \geq \log_2 [V_{FS}/Q + 1] = 6.7 \text{ bits} \Rightarrow \text{at least 7 bits}$

INTEGER CODES

Unipolar Voltages

- Can be coded to unsigned integers
- Example – 0-5 volts coded to 3 bit unsigned integer

Voltage	Digital Value	Decimal Equivalent
0	000	0
0.71	001	1
1.43	010	2
2.14	011	3
2.86	100	4
3.57	101	5
4.29	110	6
5	111	7

INTEGER CODES

Bipolar Coding

- Two's Complement

Voltage(1)	Voltage(2)	Digital Value	Decimal Equivalent
+3.75	+5	011	3
+2.50	+3.33	010	2
+1.25	+1.67	001	1
0	0	000	0
-1.25	-1.67	111	-1
-2.50	-3.33	110	-2
-3.75	-5	101	-3
-5	--	100	-4

- MSB is treated with a weighting of -2^{N-1}

$$-3 = -2^{(3-1)} + 1 = -2^2 + 1 = -4 + 1 \rightarrow 101$$



DIGITAL-TO-ANALOG CONVERTER (DAC)

Converts digital values to analog outputs of either voltage or current




DIGITAL-TO-ANALOG (D/A) CONVERSION


Ideal DA Conversion:

  


(a) OFFSET ERROR

 


(b) SCALE FACTOR ERROR

 

(c) LINEARITY ERROR

 

 (d) NON-MONOTONICITY (DUE TO EXCESSIVE DIFFERENTIAL NONLINEARITY)




DIGITAL-TO-ANALOG (D/A) CONVERSION

Digital value is stored in a register (latch), then converted.
Duration of conversion is called *settling time*.

Output of the DAC remains the same until the next value is sent to the register (latch) – a zero-order hold.

Basic concept:
 
$$V_{OUT} = \underbrace{(b_{N-1} \cdot 2^{N-1} + b_{N-2} \cdot 2^{N-2} + \dots + b_1 \cdot 2^1 + b_0 \cdot 2^0)}_{\text{Integer equivalent of binary code}} \cdot Q$$




DIGITAL-TO-ANALOG (D/A) CONVERSION

Weighted (Scaled) Resistor DAC

- Fast, but not practical for high bit count due to expense of high precision resistors across a wide magnitude range
- Virtual ground at inverting op-amp input
- Requires
 - Accurate reference voltage.
 - Higher precision resistor.

$$V_{OUT} = -\sum I_i \frac{R}{2} = -V_{REF} \left(\frac{b_{N-1}}{2} + \frac{b_{N-2}}{4} + \dots + \frac{b_0}{2^N} \right)$$

Can $|V_{OUT}| = |V_{REF}|$?

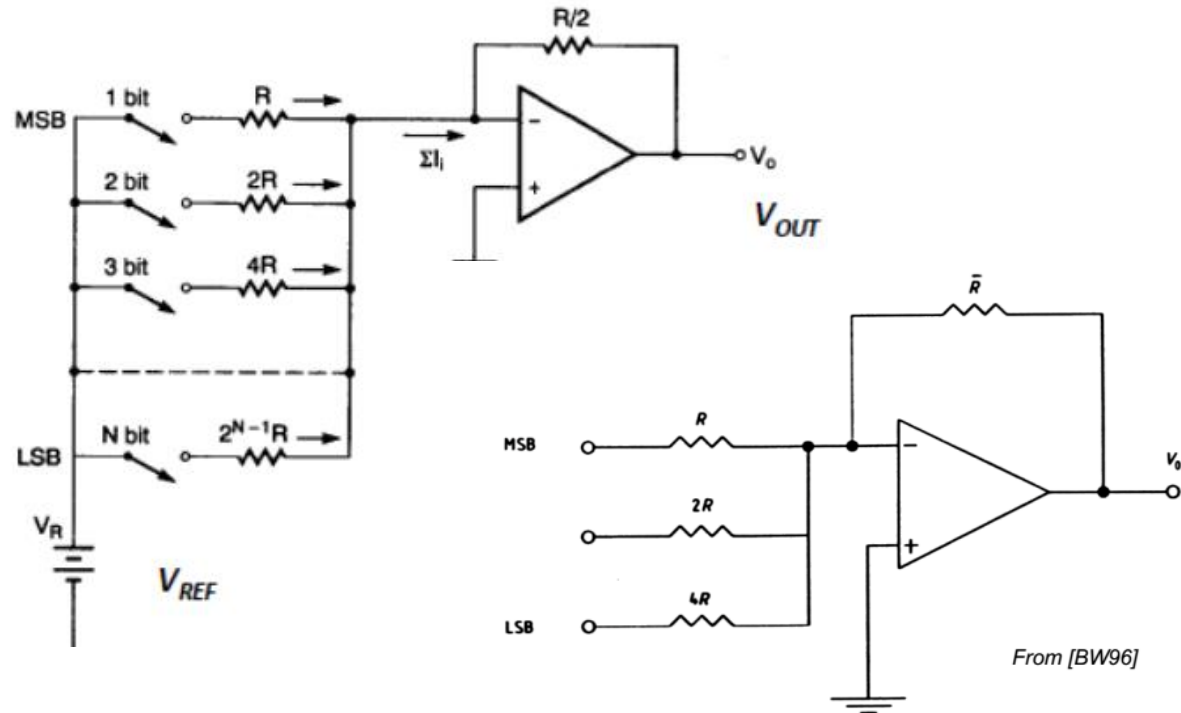


From [BW96]

DIGITAL-TO-ANALOG (D/A) CONVERSION

R/2R Ladder DAC

 - Uses just two resistance values ($2R$ and R , closely matched)
- Input switches define a specific resistor divider network



If only MSB (100) is asserted:

$$V_{OUT} = \frac{4}{8} \cdot V_{REF} = \frac{1}{2} \cdot V_{REF}$$

If all bits are asserted (111):

$$V_{OUT} = \frac{7}{8} \cdot V_{REF}$$


$$V_{OUT} = (b_{N-1} \cdot 2^{N-1} + b_{N-2} \cdot 2^{N-2} + \dots + b_1 \cdot 2^1 + b_0 \cdot 2^0) \cdot \frac{V_{REF}}{2^N}$$

- Bipolar output can be achieved by substituting the ground with a negative voltage source.

R-2R ladder

■ Basic elements

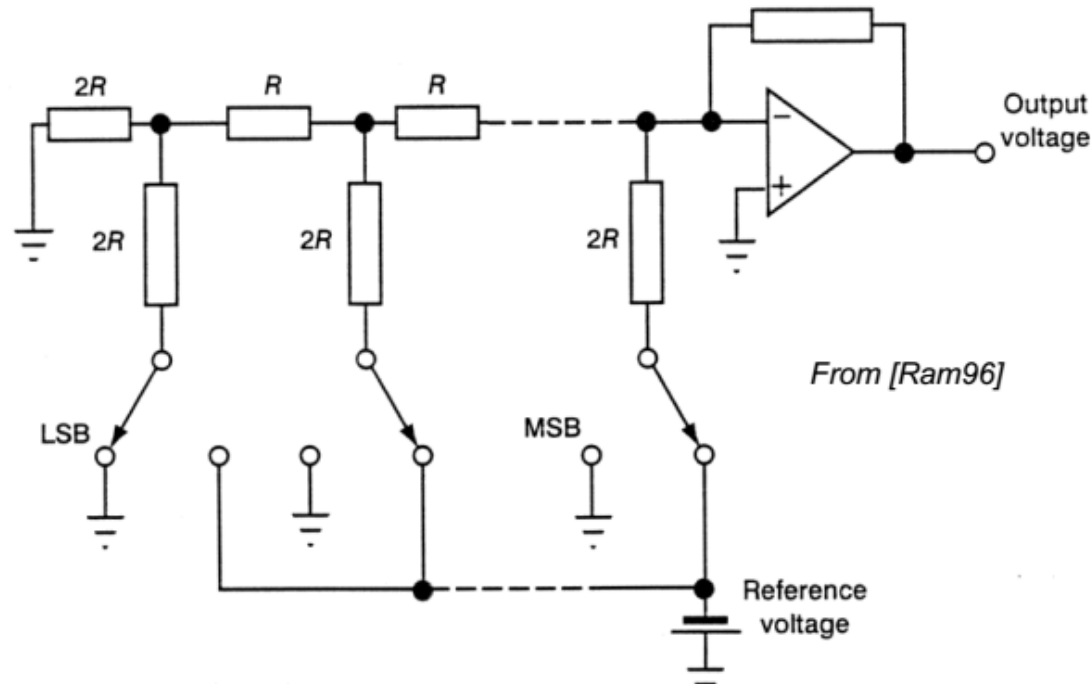- $2N$ resistors
- An op-amp
- N switches





■ Operation

- Switches
 - When bit $I_k=1$, the corresponding switch is connected to V_{REF}
 - When bit $I_k=0$, the corresponding switch is connected to GND
- Assume all the legs but one are grounded
 - The one connected to V_{REF} will generate a current that flows towards the inverting input of the op-amp
 - This current is halved by the resistor network at each node
 - Therefore, the current contribution of each input is weighted by its position in the binary number

R-2R ladder

■ The R-2R operation is better understood by redrawing the resistor network

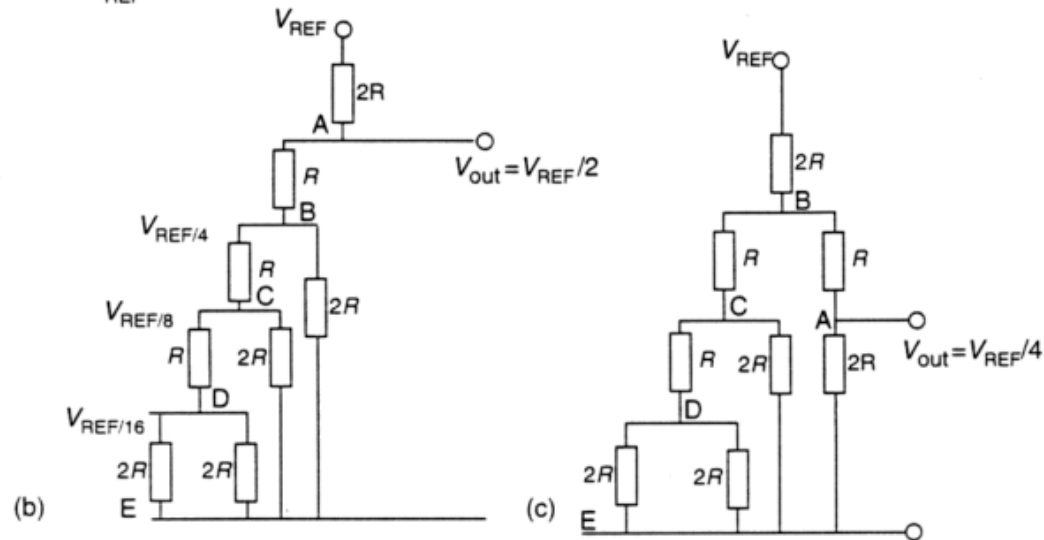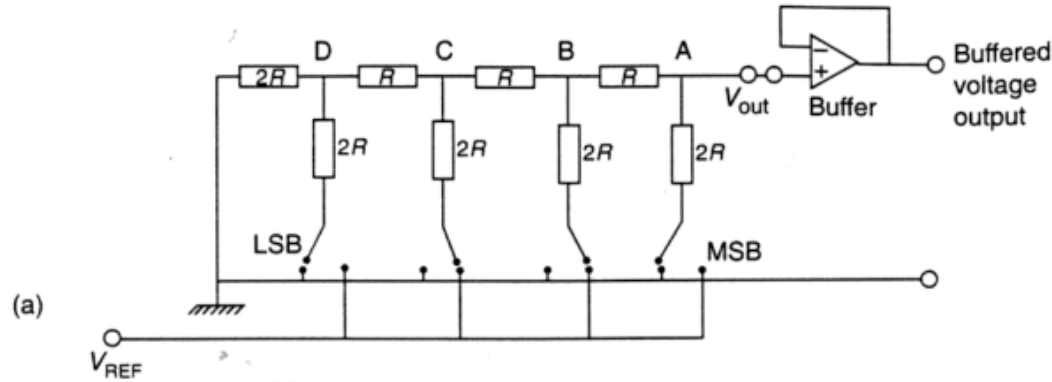
- In (b) only the MSB is ON
- In (c) only the next bit to the MSB is ON



From [Tay97]

Multiplying DAC

MDAC current to voltage conversion

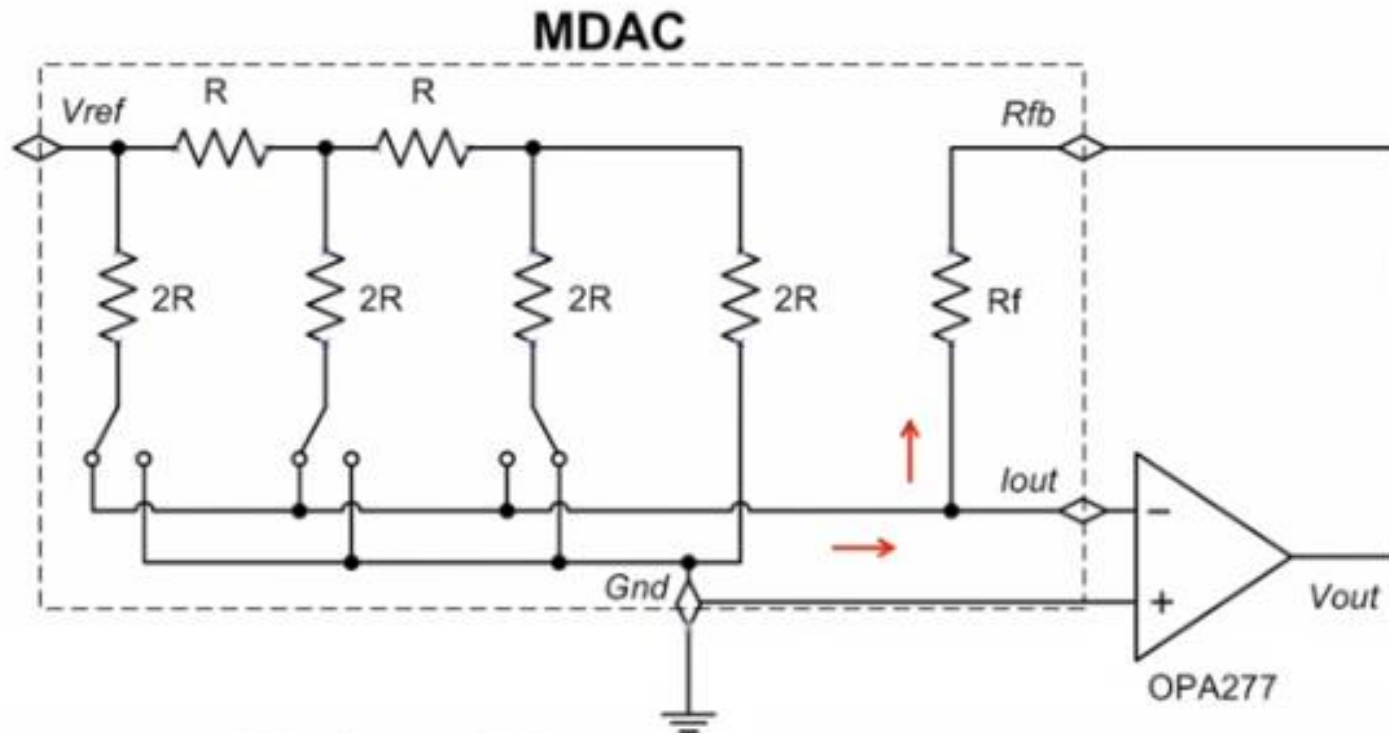

$$V_{out} = -\left(\frac{V_{ref}}{R}\right) \times \left(\frac{Code}{2^N}\right) \times R_f$$


DIGITAL-TO-ANALOG (D/A) CONVERSION

Multiplying DAC


- Conventional DAC has internal reference voltage V_{REF} that is derived from the fixed power supply.
- Multiplying DAC has an externally supplied reference voltage.

$$V_{OUT} = (b_{N-1} \cdot 2^{N-1} + b_{N-2} \cdot 2^{N-2} + \dots + b_1 \cdot 2^1 + b_0 \cdot 2^0) \cdot \frac{V_{REF}}{2^N}$$

 - Advantages:
 - Use a constant frequency sinusoidal reference signal to achieve amplitude modulation, i.e. let $V_{REF} = V_R \sin(\omega t)$.
 - External V_{REF} can be precisely controlled to compensate for drift.



Internally Referenced

 

Multiplying DAC
(Externally Referenced)


DIGITAL-TO-ANALOG (D/A) CONVERSION

Resistor methods rely on voltage dividers

- Many precision resistors necessary
- Wasted energy dissipated as heat

Pulse Width Modulation (PWM)

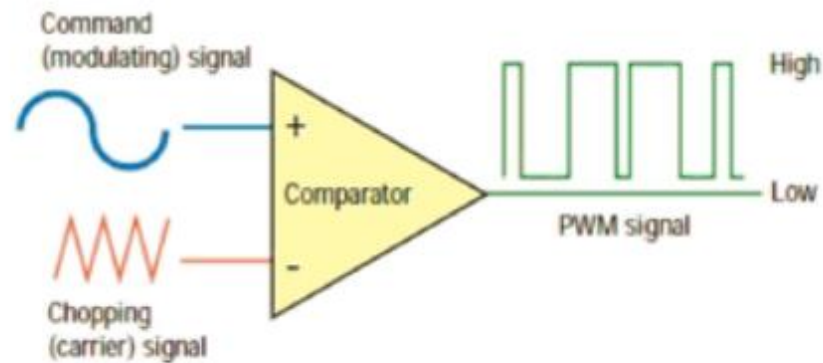- Rectangular pulse wave
- Duty cycle controls average voltage
- Very high frequency
- Need a low-pass filter to remove the sharp transitions at edges of the pulses!
- About 90% efficiency



DIGITAL-TO-ANALOG (D/A) CONVERSION


Pulse Width Modulation (PWM)

- Poor man's DAC
- Low pass filtering the PWM signal can produce an analog signal whose magnitude is proportional to the pulse width of the PWM signal
- For motor/motion control, the motor/motion system will act as the low pass filter
- Unipolar output
- Best suited when an analog output is needed but does not require a high resolution DAC

PULSE WIDTH MODULATION (PWM)

$$\text{Duty Cycle} = \frac{t_{ON}}{T} \Rightarrow 0 - 100\%$$
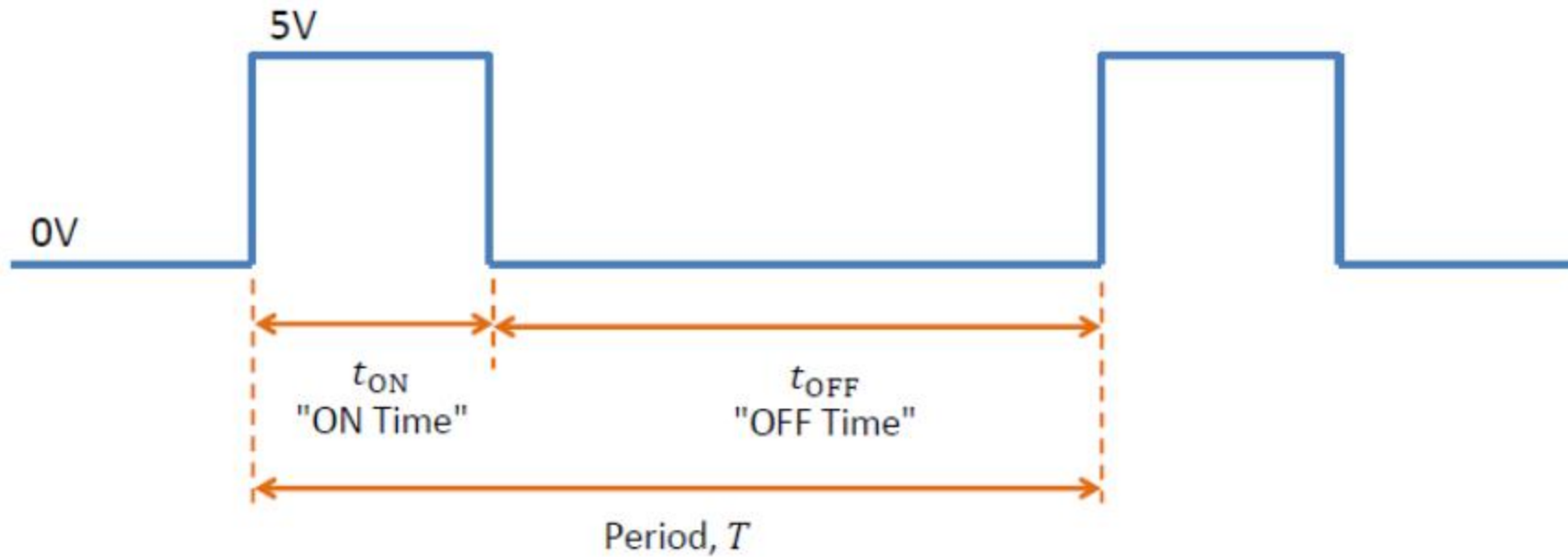
$$\text{Frequency (rad/sec)} = \frac{1}{T}$$




PULSE WIDTH MODULATION (PWM)

8-bit resolution:




- $100\%/255 \Rightarrow 0.39\%$ per step
- $5V/255 \Rightarrow 19.6$ mV per step

Arduino default PWM frequency:


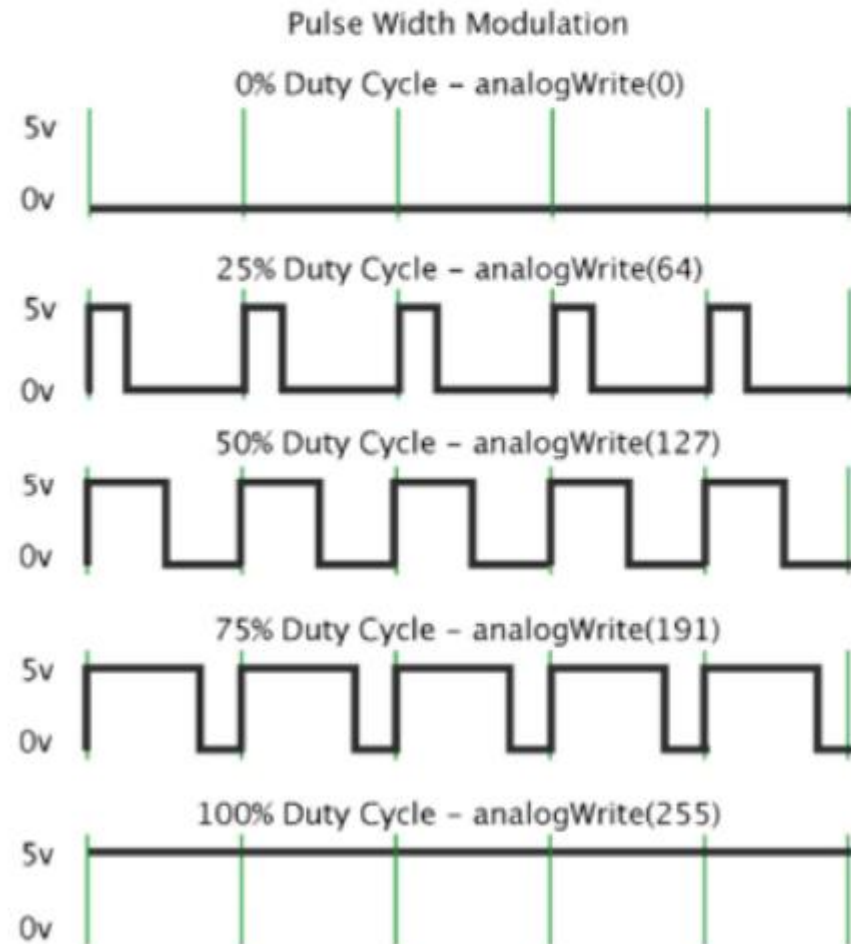
- Pins 5/6: ~976 Hz
- Pins 3/9/10/11: ~488 Hz
- Frequency can be increased to as much as 62.5 kHz by altering timer control registers
 - Pins 5/6: TCCR0B
 - Pins 9/10: TCCR1B
 - Pins 3/11: TCCR2B




DIGITAL-TO-ANALOG (D/A) CONVERSION

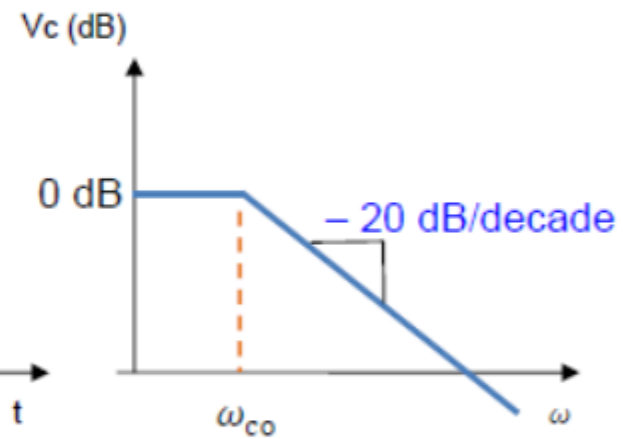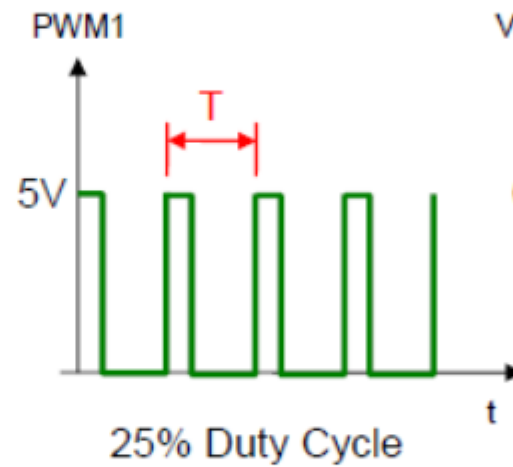 



DIGITAL-TO-ANALOG (D/A) CONVERSION

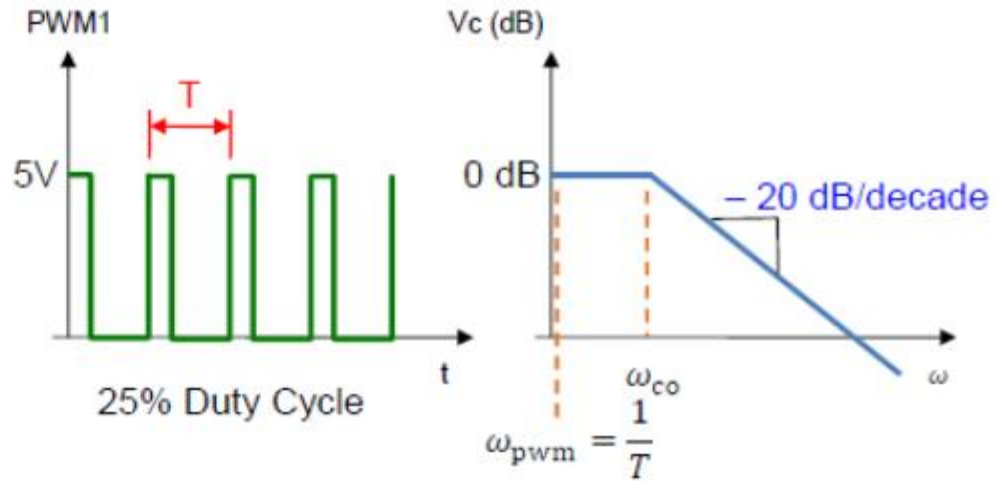 

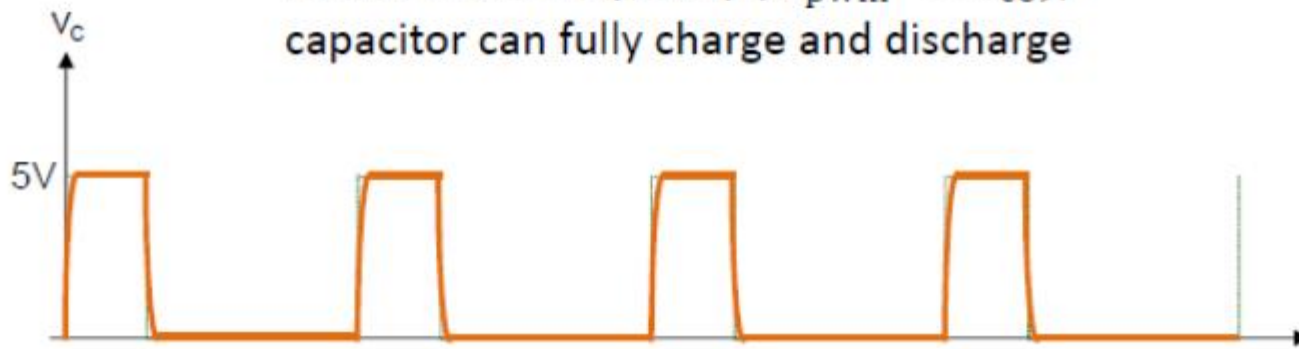
At low PWM frequency ($\omega_{pwm} \ll \omega_{co}$),
capacitor can fully charge and discharge




DIGITAL-TO-ANALOG (D/A) CONVERSION

  

 
As PWM frequency increases, capacitor can barely charge and discharge fully






DIGITAL-TO-ANALOG (D/A) CONVERSION

 

 
As PWM frequency increases further, capacitor voltage slowly increases, since capacitor cannot fully discharge before next cycle begins




DIGITAL-TO-ANALOG (D/A) CONVERSION

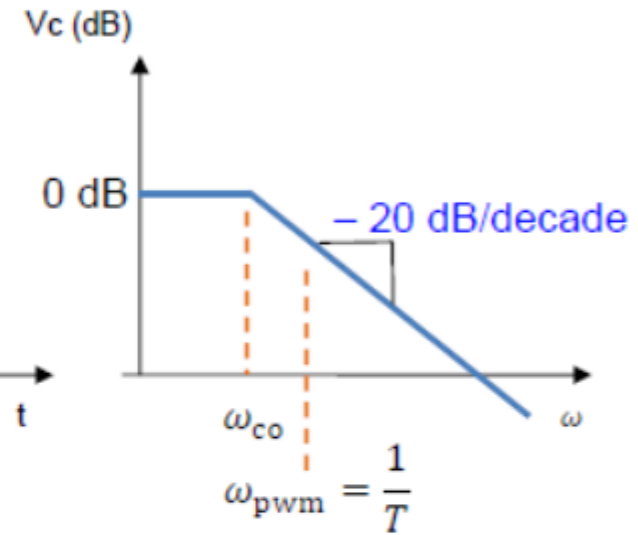  

 
As PWM frequency increases further, capacitor voltage slowly increases, since capacitor cannot fully discharge before next cycle begins



DIGITAL-TO-ANALOG (D/A) CONVERSION

 


 With PWM frequency well above cutoff frequency, capacitor voltage loses saw-tooth appearance




$$V_{C, \text{ steady state}} = V_{\text{pwm}} \times \text{Duty Cycle \%}$$

DIGITAL-TO-ANALOG (D/A) CONVERSION

 

 Want signal frequency ω_s less than ω_{co} . Can't always adjust ω_{pwm} , so often have to play with ω_s and ω_{co}



$$V_{C, \text{ steady state}} = V_{pwm} \times \text{Duty Cycle \%}$$

RC Low-pass Filter Design for PWM

Calculated peak-to-peak ripple voltage and settling time at a given PWM frequency and cut-off frequency or values of R and C.

<http://sim.okawa-denshi.jp/en/PWMtool.php>

How to adjust Arduino PWM frequencies

Pins 5 and 6: controlled by Timer 0 in fast PWM mode
(cycle length = 256)

Setting	Divisor	Frequency
0x01	1	62500
0x02	8	7812.5
0x03	64	976.5625 <--DEFAULT
0x04	256	244.140625
0x05	1024	61.03515625

```
TCCR0B = (TCCR0B & 0b11111000) | <setting>;
```