

ENCS238: Computer Organization

Mano - Chapter 4

Register Transfer and Microoperations

Contents

- **Register Transfer Language (RTL)**
- **Register Transfer**
- **Bus and Memory Transfers**
- **Arithmetic Microoperations**
- **Logic Microoperations**
- **Shift Microoperations**
- **Arithmetic Logic Shift Unit**

What is Register?

- **A special, high-speed storage area within the CPU.**
- **Registers are normally measured by the number of bits they can hold,**
 - for example, an "8-bit register" or a "32-bit register".
- **All data must be represented in a register before it can be processed.**
 - For example, if two numbers are to be multiplied, both numbers must be in registers, and the result is also placed in a register.
- **The register can contain the address of a memory location where data is stored rather than the actual data itself**


R1

4-1 Register Transfer Language (RTL)

- **Digital System:** An interconnection of hardware modules that do a certain task on the information
- **Registers + Operations** performed on the data stored in them = **Digital Module**
- Modules are interconnected with **common data** and **control paths** to form a **digital computer system**

 4-1 Register Transfer Language ^{cont.}

- **Microoperations:** operations executed on data stored in one or more registers.
- For any function of the computer, a sequence of microoperations is used to describe it
- The result of the operation may be:
 - Replace the previous binary information of a register **or**
 - Transferred to another register



4-1 Register Transfer Language ^{cont.}

- The internal hardware organization of a digital computer is defined by specifying:
 - The **set of registers** it contains and their **function**
 - The sequence of **microoperations** performed on the binary information stored in the registers
 - The **control** that initiates the sequence of microoperations
- Registers + Microoperations Hardware + Control Functions
= **Digital Computer**

4-1 Register Transfer Language ^{cont.}

- **RTL: a symbolic notation to describe the microoperation transfers among registers**

Next steps:

- **Define symbols (**Codes**) for various types of microoperations**
- **Describe the **hardware** that implements these microoperations**

4-2 Register Transfer

- Computer registers are designated by **Capital Letters** (sometimes followed by **Numerals**) to denote the function of the register

R1: processor register


MAR: Memory Address Register (holds an address for a memory unit)

PC: Program Counter

IR: Instruction Register


SR: Status Register

Digital Review: Register

 


 4-2 Register Transfer ^{cont.}

- The individual flip-flops in an n-bit register are numbered in sequence from **0** to **n-1** (from the right position toward the left position)



Register R1

 


Showing individual bits


A block diagram of a register

 4-2 Register Transfer cont.

Other ways of drawing the block diagram of a register:



Numbering of bits

 

Partitioned into two parts

4-2 Register Transfer cont.

- Information transfer from one register to another is described by a *replacement operator*: $R2 \leftarrow R1$

This statement denotes a transfer of the content of register **R1** into register **R2**

- The transfer happens in one **clock cycle**
- The content of the R1 (source) does not change
- The content of the R2 (destination) will be lost and replaced by the new data transferred from R1
- We are assuming that the circuits are available from the outputs of the source register to the inputs of the destination register, and that the destination register has a **parallel load** capability

4-2 Register Transfer cont.

- **Conditional Transfer** occurs only under a control condition
- Representation of a (conditional) transfer

$$\mathbf{P}: \quad R2 \leftarrow R1$$


- A binary condition (P equals to 0 or 1) determines when the transfer occurs
- The content of R1 is transferred into R2 only **if P is 1**

4-2 Register Transfer cont.

Hardware implementation of a controlled transfer:

P: R2 ← R1

Block diagram:

 

4-2 Register Transfer cont.

Basic Symbols for Register Transfers		
Symbol	Description	Examples
Letters & numerals	Denotes a register	MAR R2
Parenthesis ()	Denotes a part of a register	R2(0-7) R2(L)
Arrow ←	Denotes transfer of information	R2 ← R1
Comma ,	Separates two microoperations	R2 ← R1 , R1 ← R2



4-3 Bus and Memory Transfers

- **Paths** must be provided to transfer information from one register to another
- A **Common Bus System** is a scheme for transferring information between registers in a multiple-register configuration
- **A bus**: set of common lines, one for each bit of a register, through which binary information is transferred one at a time
- **Control signals** determine which register is selected by the bus during each particular register transfer


Digital Review: MULTIPLEXER

4-to-1 Multiplexer

Select		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

  

4-3 Bus and Memory Transfers

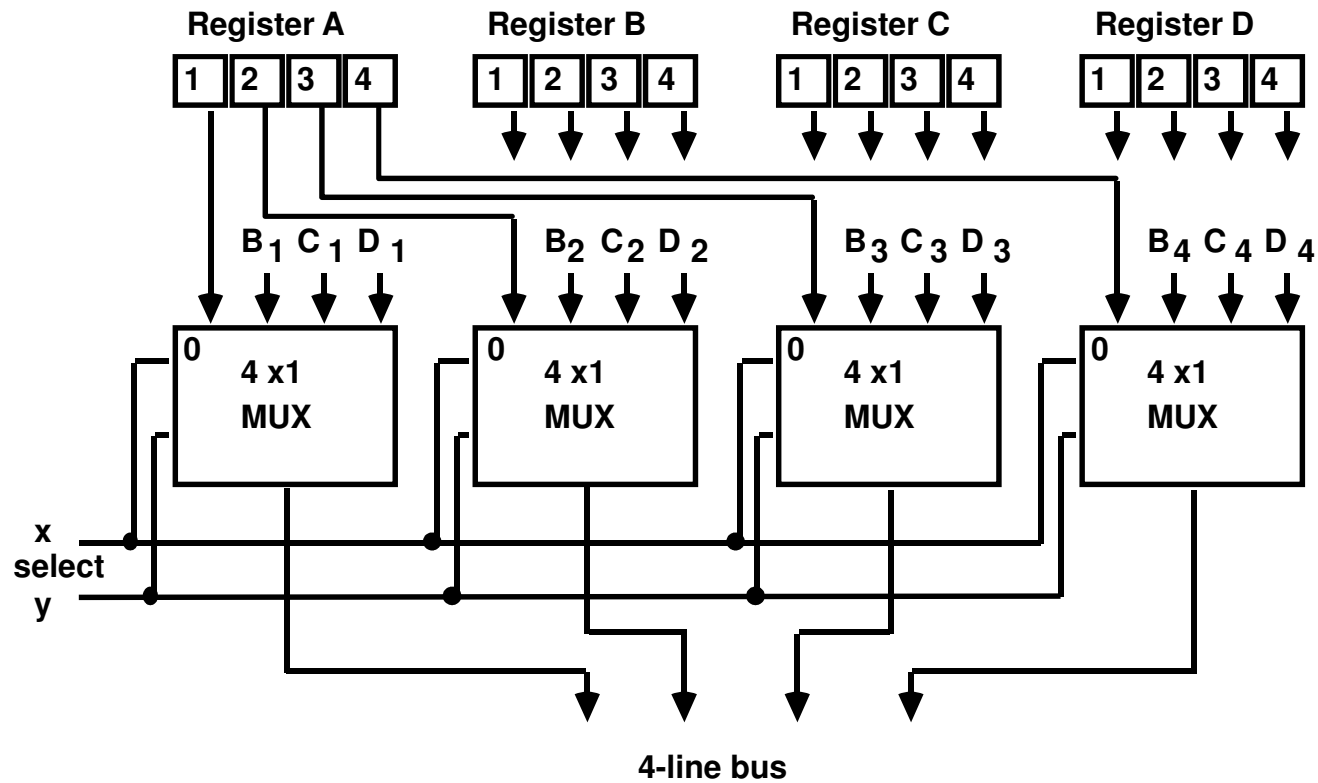


4-3 Bus and Memory Transfers

- The transfer of information from a bus into one of many destination registers is done:
 - By connecting the bus lines to the inputs of all destination registers and then:
 - Activating the **load** control of the particular destination register selected
- We write: $R2 \leftarrow C$ to symbolize that the content of register **C** is *loaded into* the register **R2** using the common system bus
- It is equivalent to:
 $BUS \leftarrow C, (\text{select } C)$
 $R2 \leftarrow BUS (\text{Load } R2)$


Three-State Bus Buffers

 - A bus system can be constructed with **three-state buffer** gates instead of **multiplexers**
- A **three-state buffer** is a digital circuit that exhibits three states:
 - logic-0,
 - logic-1, and
 - high-impedance (Hi-Z)



Three-State Buffer


Three-State Bus Buffers cont.

 


Digital Review **DECODER**

2-to-4 Decoder

E	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

 


Three-State Bus Buffers cont.

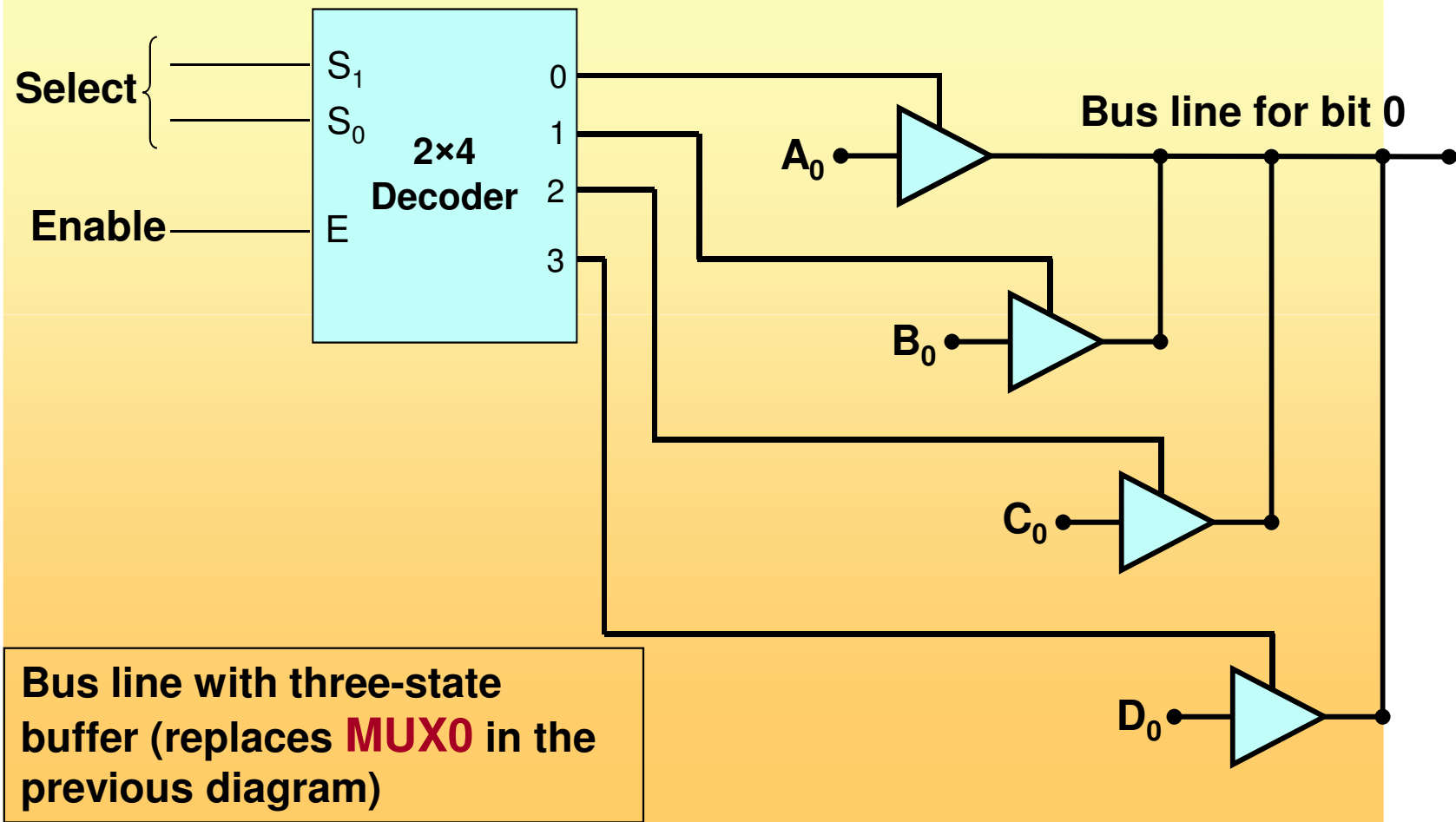


Digital Review: MEMORY COMPONENTS

Logical Organization

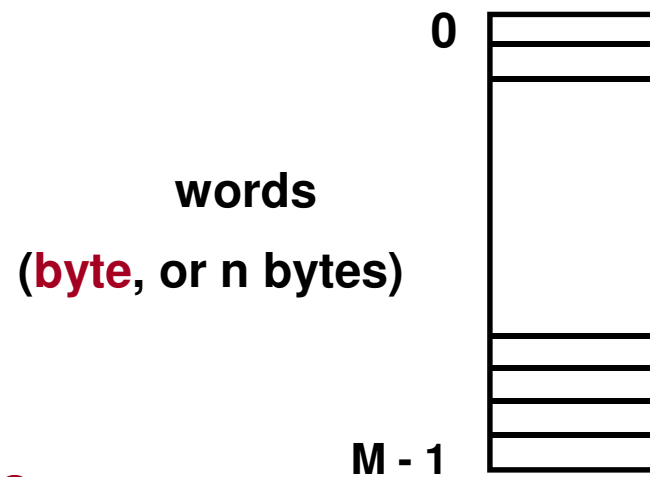

Random Access Memory

 - Each word has a **unique address**
- Access to a word requires the same time independent of the location of the word




Memory Transfer

- **Memory read** : Transfer **from** memory
- **Memory write** : Transfer **to** memory
- Data being read or wrote is called a **Memory Word** (called **M**)
- It is necessary to specify the address of **M** when writing / reading memory
- This is done by enclosing the address in **square brackets** following the letter **M**
- Example: **M[0016]** : the memory contents at address **0X0016**

Memory Transfer cont.

- Assume that the address of a memory unit is stored in a register called the Address Register **AR**
- Lets represent a Data Register with **DR**, then:
 - Read: **DR** \leftarrow **M[AR]**
 - Write: **M[AR]** \leftarrow **DR**

Memory Transfer cont.

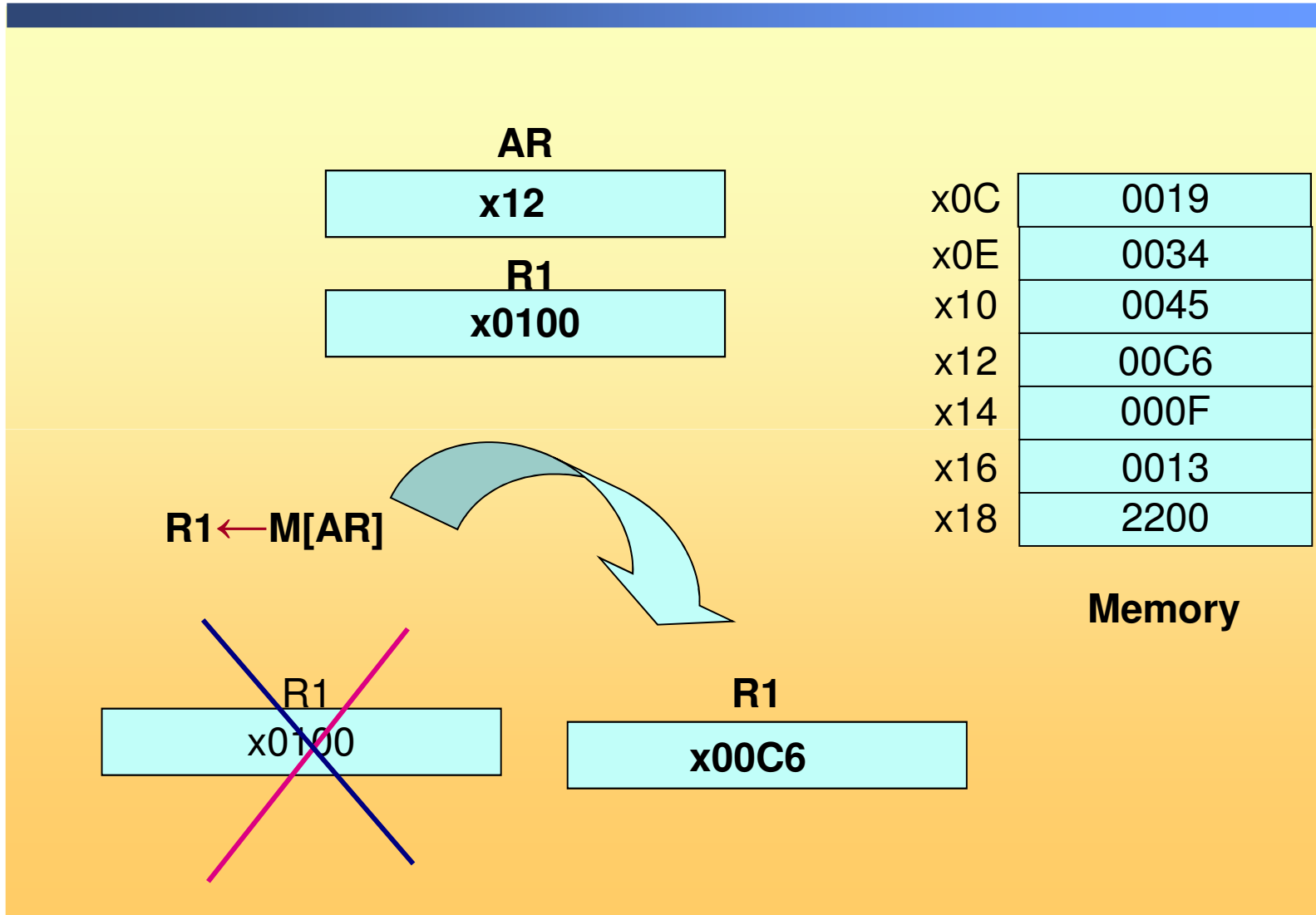

4-4 Arithmetic Microoperations

- The microoperations most often encountered in digital computers are classified into four categories:
 - **Register transfer microoperations**
 - **Arithmetic microoperations** (on numeric data stored in the registers)
 - **Logic microoperations** (bit manipulations on non-numeric data)
 - **Shift microoperations**

4-4 Arithmetic Microoperations ^{cont.}

- The basic arithmetic microoperations are: **addition**, **subtraction**, **increment**, **decrement**, and **shift**

- **Addition Microoperation:**

$$R3 \leftarrow R1 + R2$$

- **Subtraction Microoperation:**

$$R3 \leftarrow R1 - R2$$

or :

$$R3 \leftarrow R1 + \underline{\quad} + 1$$

1's Complement



4-4 Arithmetic Microoperations ^{cont.}

- **One's Complement Microoperation:**

$$R2 \leftarrow \overline{R2}$$

- **Two's Complement Microoperation:**

$$R2 \leftarrow \overline{R2+1}$$

- **Increment Microoperation:**

$$R2 \leftarrow R2+1$$

- **Decrement Microoperation:**

$$R2 \leftarrow R2-1$$

Digital Review Half Adder/Full Adder


Half Adder

x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$c = xy$$


$$s = xy' + x'y$$

$$= x \oplus y$$

 

Full Adder

x	y	C_{n-1}	C_n	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


$$C_n = xy + xC_{n-1} + yC_{n-1}$$


$$= xy + (x \oplus y)C_{n-1}$$

$$s = x'y'C_{n-1} + x'yc'_{n-1} + xy'c'_{n-1} + xyc_{n-1}$$
 
$$= x \oplus y \oplus C_{n-1} = (x \oplus y) \oplus C_{n-1}$$




Binary Adder

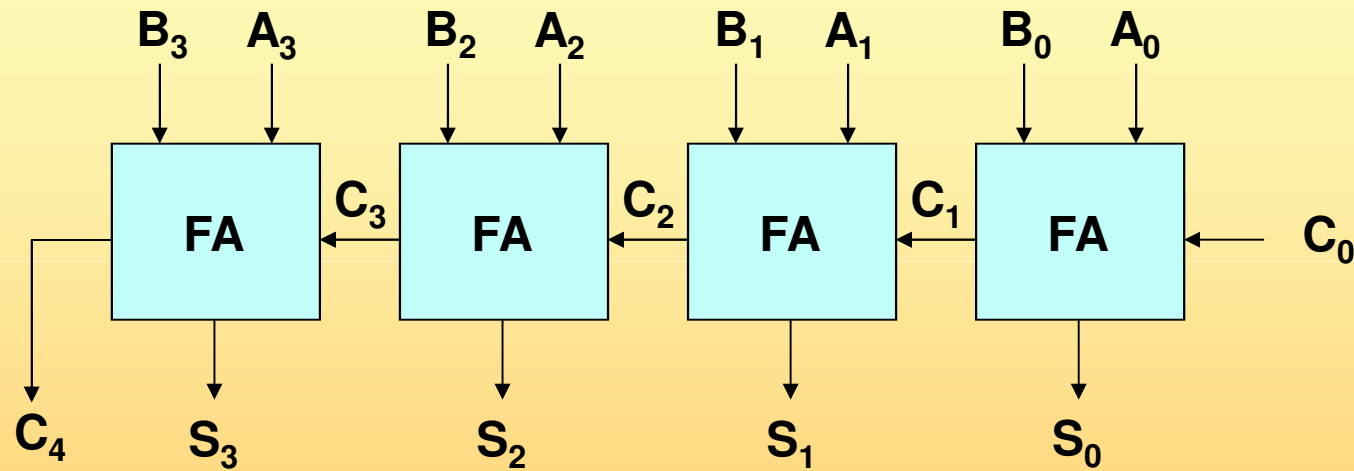


4-bit binary adder
(connection of FAs)

Binary Adder-Subtractor

 

4-bit adder-subtractor

Binary Incrementer

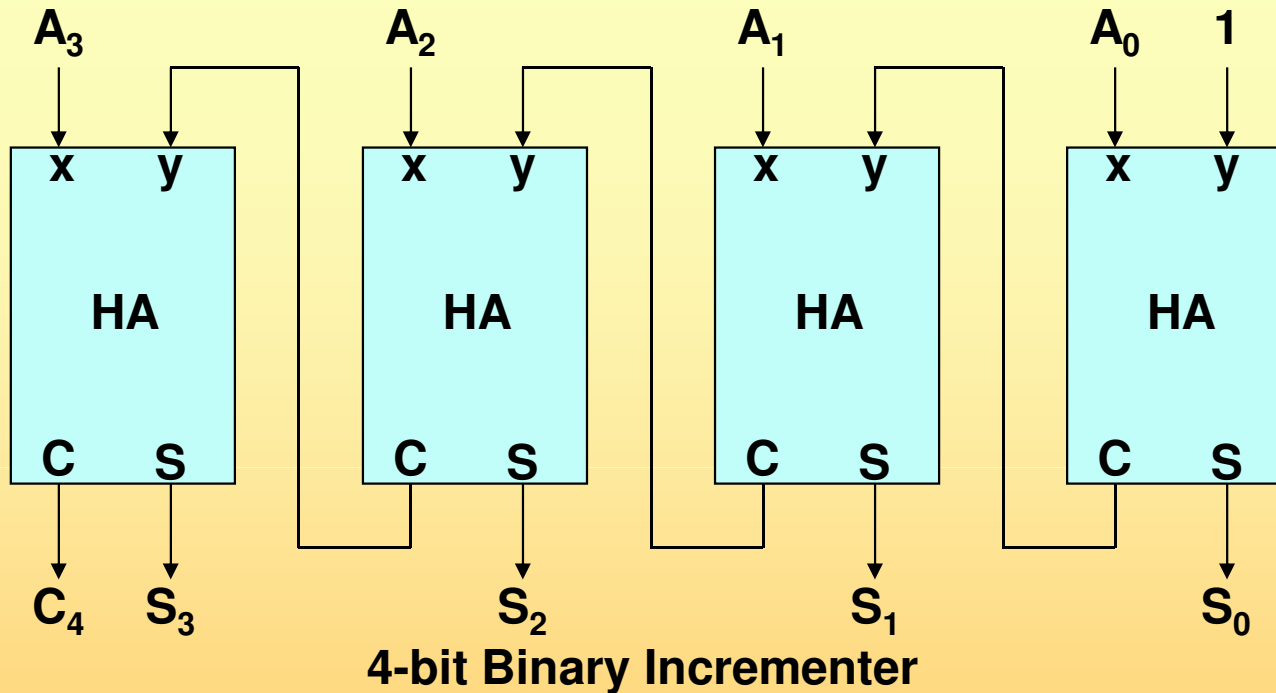

- Binary Incrementer can also be implemented using a **Counter**
- A binary decrementer can be implemented by adding **1's** to the desired register each time!


Arithmetic Circuit

- This circuit performs seven distinct arithmetic operations and the basic component of it is the **parallel adder**
- The output of the binary adder is calculated from the following arithmetic sum:

$$D = A + Y + C_{in}$$

Arithmetic Circuit cont.

Figure A

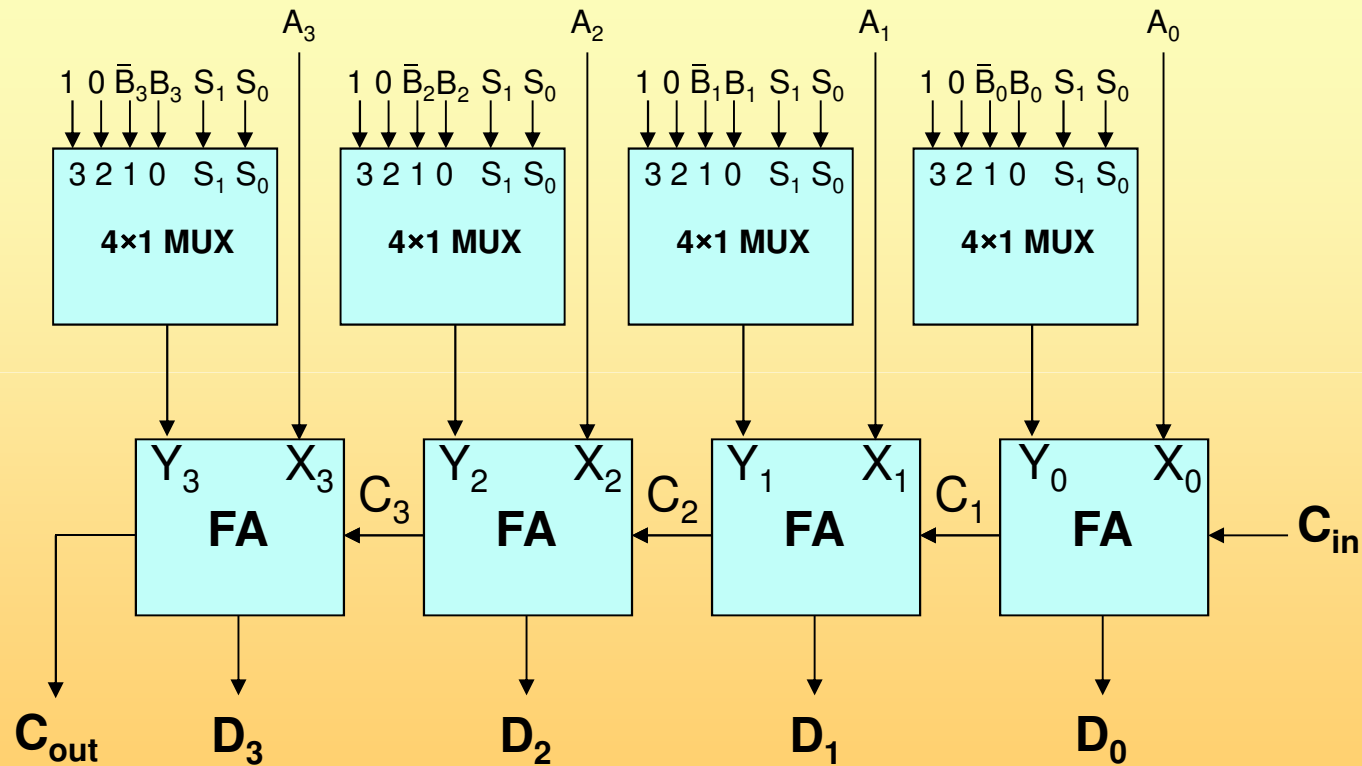

4-bit Arithmetic Circuit

Arithmetic Circuit cont.


	Select			Input Y	Output $D = A + Y + C_{in}$	Microoperations
	S 1	S 0	C _i n			
1	0	0	0	B	$D = A + B$	Add
2	0	0	1	B	$D = A + B + 1$	Add with carry
3	0	1	0	B^-	$D = A + B^-$	Sub. With borrow
4	0	1	1	B^-	$D = A + B^- + 1$	Sub
5	1	0	0	0	$D = A$	Transfer A
6	1	0	1	0	$D = A + 1$	Increment
7	1	1	0	1	$D = A - 1$	Decrement
8	1	1	1	1	$D = A$	Transfer A

The 4 basic Logic microoperations


OR Microoperation

■ Symbol: **U** , **+**

■ Gate:

 

 
■ Example: $0100110_2 \mathbf{U} 1010110_2 = 1110110_2$



The 4 basic logic microoperations ^{cont.}

AND Microoperation

- Symbol: \cap , \cdot

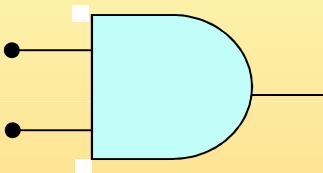
- Gate: A light blue AND gate symbol with two input lines on the left and one output line on the right.

- Example: $100110_2 \cap 1010110_2 = 0000110_2$

The 4 basic logic microoperations ^{cont.}

Complement (NOT) Microoperation

■ Symbol: $\bar{\quad}$

 


■ Example: $\overline{1010110_2} = 0101001_2$

The 4 basic logic microoperations ^{cont.}

XOR (Exclusive-OR) Microoperation

- Symbol: \oplus

- Gate:

 

- Example: $100110_2 \oplus 1010110_2 = 1110000_2$

Other Logic Microoperations

Selective-set Operation

- Used to force selected bits of a register into logic-1 by using the **OR** operation

Example: $0100_2 \mathbf{U} 1000_2 = 1100_2$

Selective-complement (toggling) Operation

- Used to force selected bits of a register to be complemented by using the **XOR** operation

Example: $0001_2 \oplus 1000_2 = 1001_2$

Other Logic Microoperations ^{cont.}

Insert Operation

- Step1: mask the desired bits (**AND**)
 - Step2: **OR** them with the desired value
 - Example: suppose **R1 = 0110 1010**, and we desire to replace the leftmost **4** bits (**0110**) with **1001** then:
 - Step1: **0110** 1010 \cap **0000** 1111
 - Step2: **0000** 1010 \cup **1001** 0000
- R1 = 1001 1010**


4-5 Logic Microoperations

Other Logic Microoperations ^{cont.}

NAND Microoperation

- Symbols: \cap and $\bar{}$

- Gate:

 

- Example: $100110_2 \cap 1010110_2 = 1111001_2$


4-5 Logic Microoperations

Other Logic Microoperations ^{cont.}

NOR Microoperation

- Symbols: **U** and $\overline{}$

- Gate:

 

- Example: $100110_2 \mathbf{U} 1010110_2 = 0001001_2$

4-5 Logic Microoperations

Other Logic Microoperations ^{cont.}

Set (Preset) Microoperation

- Force all bits into 1's by ORing them with a value in which all its bits are being assigned to logic-1
- Example: $100110_2 \cup 111111_2 = 111111_2$

Clear (Reset) Microoperation


- Force all bits into 0's by ANDing them with a value in which all its bits are being assigned to logic-0
- Example: $100110_2 \cap 000000_2 = 000000_2$

4-5 Logic Microoperations Hardware Implementation

- The hardware implementation of logic microoperations requires that logic gates be inserted for each bit or pair of bits in the registers to perform the required logic function
- Most computers use only four (**AND**, **OR**, **XOR**, and **NOT**) from which all others can be derived.

4-5 Logic Microoperations Hardware Implementation ^{cont.}

Figure B

 


S_1	S_0	Output	Operation
0	0	$E = A \oplus B$	XOR
0	1	$E = A \cup B$	OR
1	0	$E = A \cap B$	AND
1	1	$E = \overline{A}$	Complement

This is for one bit **i**


4-6 Shift Microoperations

- Used for **serial** transfer of data
- Also used in conjunction with arithmetic, logic, and other data-processing operations
- The contents of the register can be shifted to the **left** or to the **right**
- As being shifted, the first flip-flop receives its binary information from the serial input
- Three types of shift: **Logical**, **Circular**, and **Arithmetic**

4-6 Shift Microoperations cont.

 


Shift Right

 

Shift Left


Logical Shifts

 - Transfers **0** through the serial input
- Logical Shift Right: $R1 \leftarrow \text{shr } R1$
- Logical Shift Left: $R2 \leftarrow \text{shl } R2$



Circular Shifts (Rotate Operation)

 - Circulates the bits of the register around the two ends without **loss** of information
- Circular Shift Right: $R1 \leftarrow \mathbf{cir} R1$
- Circular Shift Left: $R2 \leftarrow \mathbf{cil} R2$



Circular Shift Left

Arithmetic Shifts

- Shifts a **signed** binary number to the left or right
- An arithmetic shift-left **Multiplies** a signed binary number by **2**



ashl (00100): 01000

- An arithmetic shift-right **Divides** the number by **2**

ashr (00100) : 00010

- An **Overflow** may occur in arithmetic shift-left, and occurs when the sign bit is changed (sign reversal)


Arithmetic Shifts cont.

 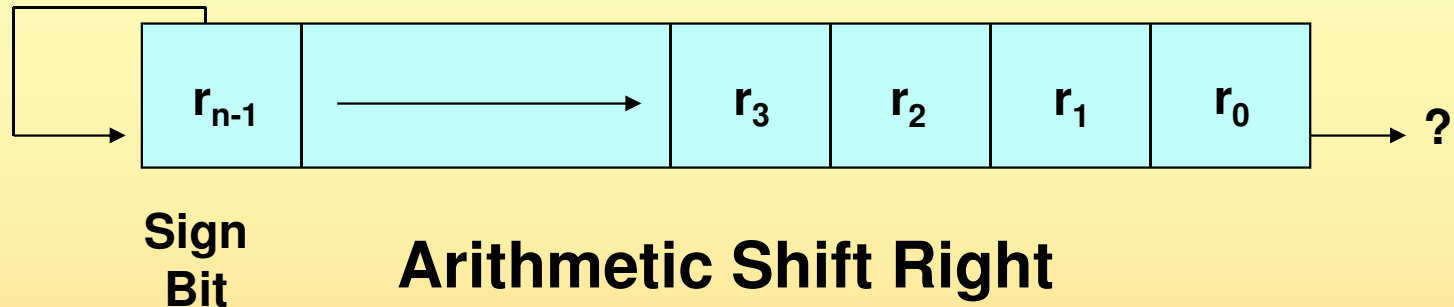

Arithmetic Shifts cont.

- An **overflow** flip-flop V_s can be used to detect an arithmetic shift-left overflow


$$V_s = R_{n-1} \oplus R_{n-2}$$

 

Hardware Implementation ^{cont.}

- A possible choice for a shift unit would be a **bidirectional** shift register with parallel load
- Needs two pulses (the **clock** and the **shift signal** pulse)
 - Not efficient in a processor unit where multiple number of registers share a common bus
- It is more efficient to implement the shift operation with a **combinational circuit**

Hardware Implementation cont.

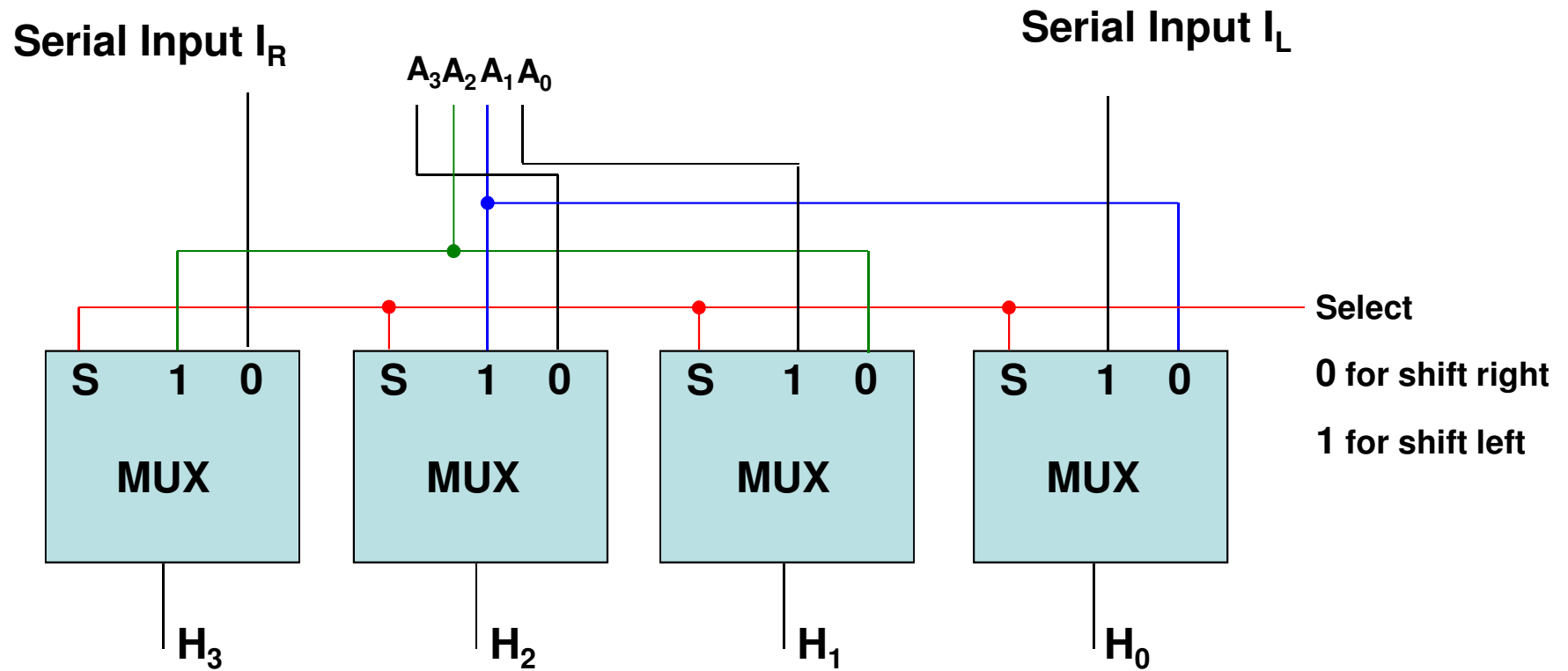


4-bit Combinational Circuit Shifter

4-7 Arithmetic Logic Shift Unit

- Instead of having individual registers performing the microoperations directly, computer systems employ a number of storage registers connected to a common operational unit called an Arithmetic Logic Unit (**ALU**)

4-7 Arithmetic Logic Shift Unit cont.

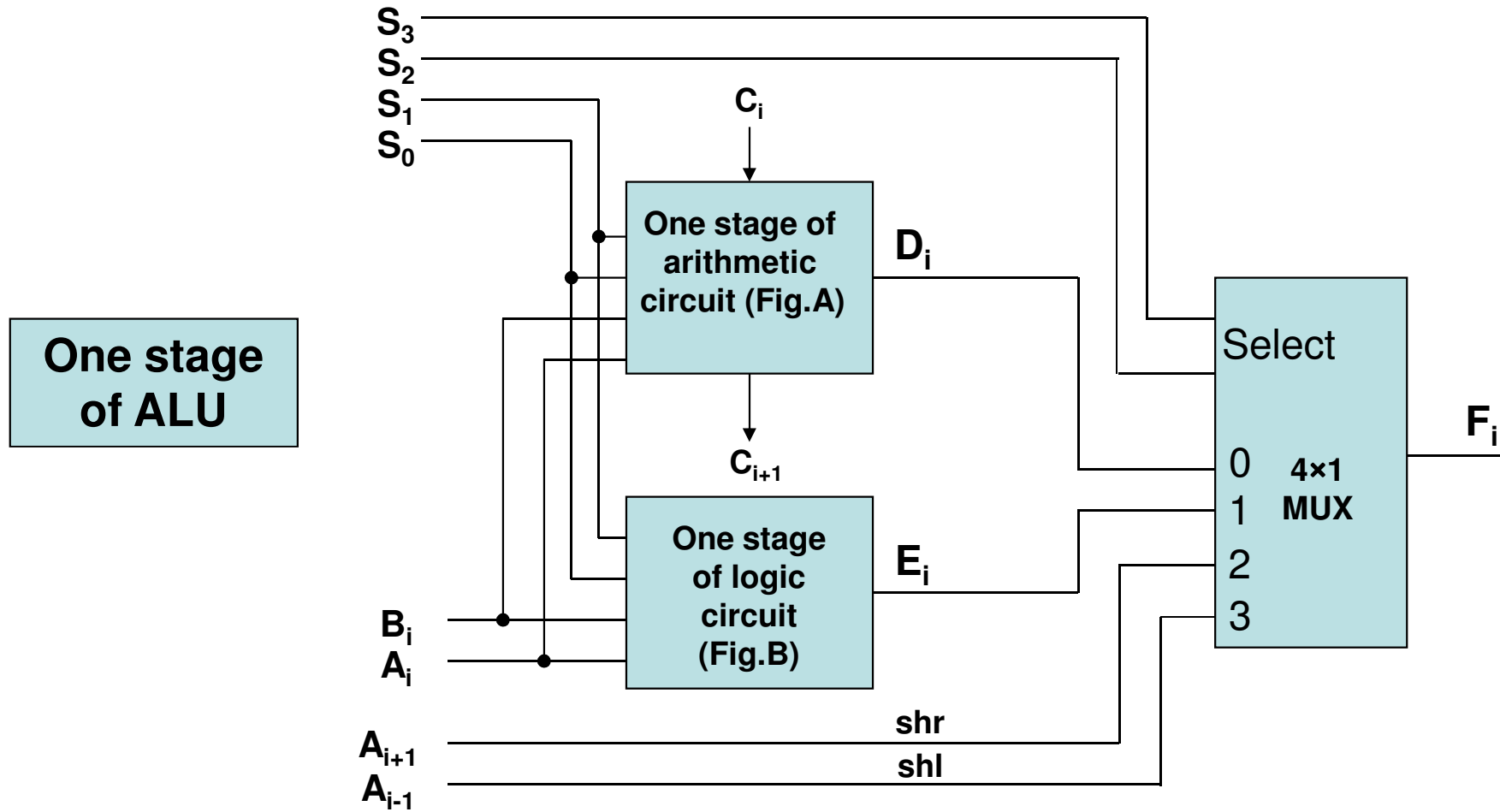

4-7 Arithmetic Logic Shift Unit ^{cont.}

Operation Selection					Operation	Function
S ₃	S ₂	S ₁	S ₀	C _{in}		
0	0	0	0	0	$F = A + B$	Addition
0	0	0	0	1	$F = A + B + 1$	Addition with carry
0	0	0	1	0	$F = A + B^-$	Sub. With borrow
0	0	0	1	1	$F = A + B^- + 1$	Sub
0	0	1	0	0	$F = A$	Transfer A
0	0	1	0	1	$F = A + 1$	Increment
0	0	1	1	0	$F = A - 1$	Decrement
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	X	$F = A \oplus B$	XOR
0	1	0	1	X	$F = A \cup B$	OR
0	1	1	0	X	$F = A \cap B$	AND
0	1	1	1	X	$F = A^-$	Complement
1	0	X	X	X	$F = \text{shr } A$	Shift right A into F
1	1	X	X	X	$F = \text{shl } A$	Shift left into F