
RTL & Micro-Operations

Mano Ch. 4

Register Transfer Language (RTL)

- Digital System: An interconnection of hardware modules that do a certain task on the information.
- Registers + Operations performed on the data stored in them = Digital Module
- Modules are interconnected with common data and control paths to form a digital computer system
- Microoperations: operations executed on data stored in one or more registers.
- For any function of the computer, a sequence of microoperations is used to describe it


Register Transfer Language cont.

- The internal hardware organization of a digital computer is defined by specifying:
 - The set of registers it contains and their function
 - The sequence of microoperations performed on the binary information stored in the registers
 - The control that initiates the sequence of microoperations
- **Register Transfer Language (RTL):** a symbolic notation to describe the microoperation transfers among registers
 - Define symbols for various types of microoperations,
 - Describe the hardware that implements these microoperations

Register Transfer (our first microoperation)


- Computer registers are designated by capital letters (sometimes followed by numerals) to denote the function of the register
 - R1: processor register
 - MAR: Memory Address Register (holds an address for a memory unit)
 - PC: Program Counter
 - IR: Instruction Register
 - SR: Status Register

Computer Components: Top Level View

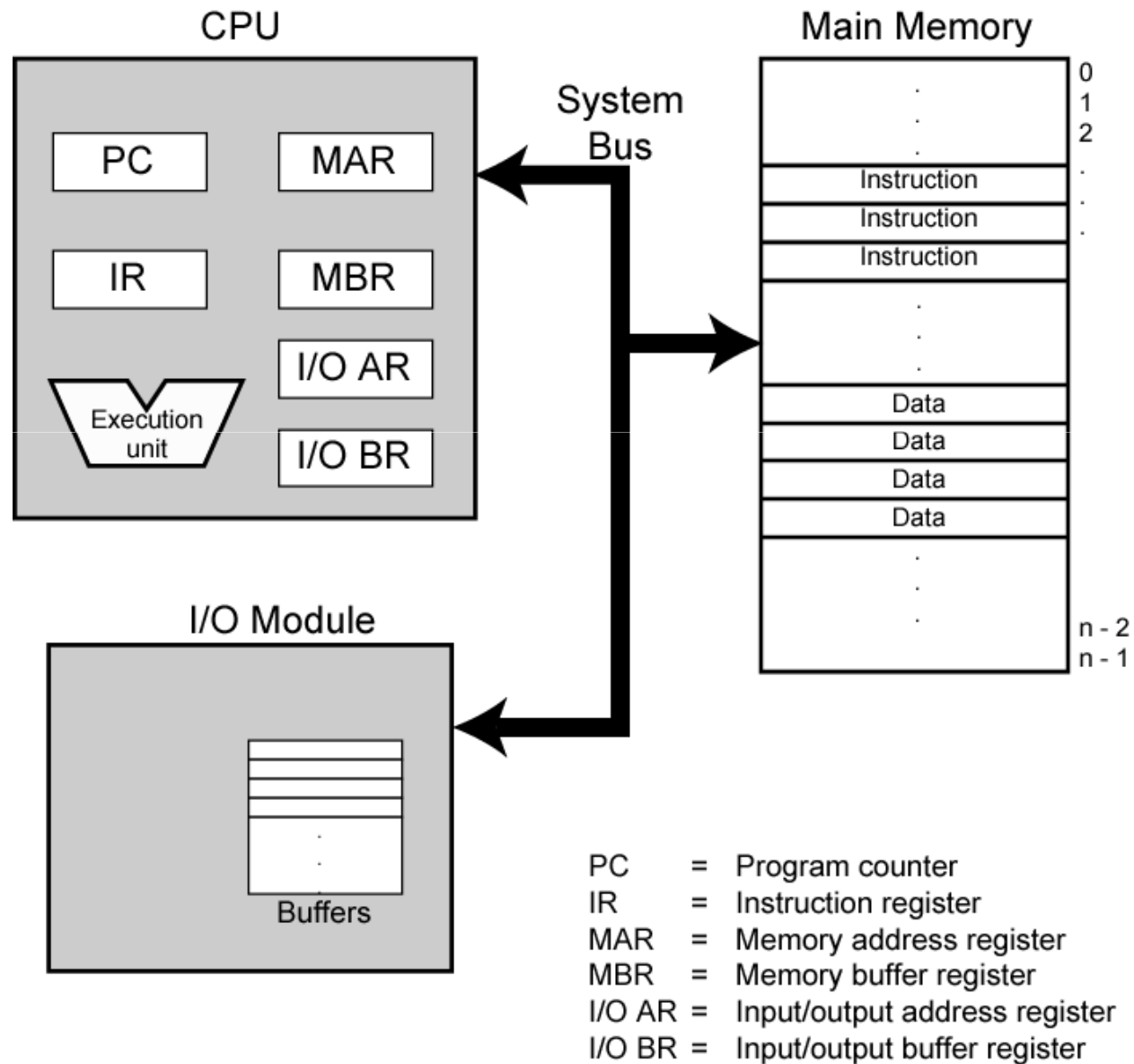

CPU local Bus Organization

- One-Bus Organization

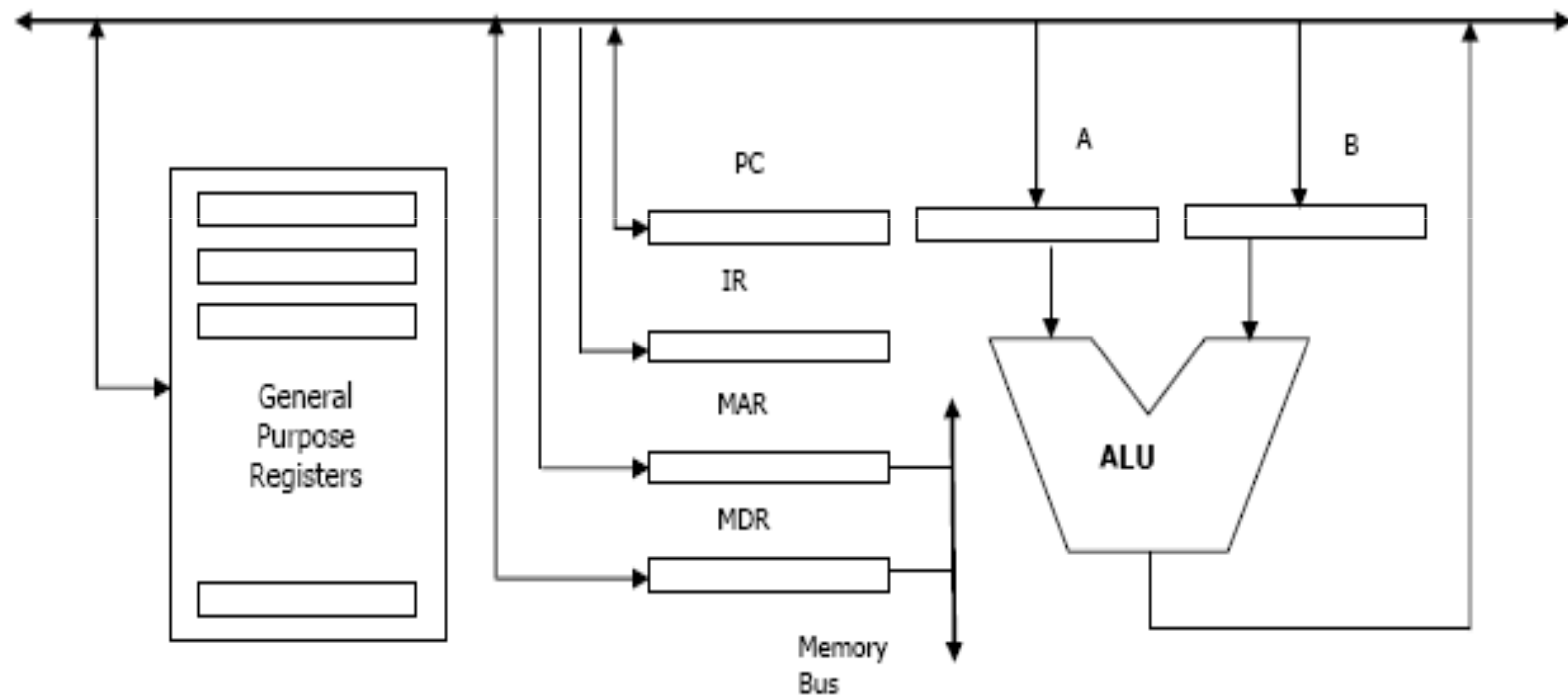

Register Transfer ^{cont.}

- The individual flip-flops in an n-bit register are numbered in sequence from 0 to n-1 (from the right position toward the left position)



Register R1



Showing individual bits


A block diagram of a register

Register Transfer cont.

Other ways of drawing the block diagram of a register:



Numbering of bits

 

Partitioned into two parts

Register Transfer **cont.**

- Information transfer from one register to another is described by a *replacement operator*:

$$\mathbf{R2} \leftarrow \mathbf{R1}$$

- This statement denotes a transfer of the content of register R1 into register R2
- The transfer happens in one clock cycle
- The content of the R1 (source) does not change
- The content of the R2 (destination) will be lost and replaced by the new data transferred from R1
- We are assuming that the circuits are available from the outputs of the source register to the inputs of the destination register, and that the destination register has a parallel load capability

Register Transfer ^{cont.}

- Conditional transfer occurs only under a control condition
- Representation of a (conditional) transfer

$$P: \quad R2 \leftarrow R1$$


- A binary condition (P equals to 0 or 1) determines when the transfer occurs
- The content of R1 is transferred into R2 only if P is 1

Register Transfer cont.


Hardware implementation of a controlled transfer:

$$P: \quad R2 \leftarrow R1$$

Block diagram:

 

Timing diagram

 

Synchronized with the clock


Register Transfer ^{cont.}

Basic Symbols for Register Transfers		
Symbol	Description	Examples
Letters & numerals	Denotes a register	MAR, R2
Parenthesis ()	Denotes a part of a register	R2(0-7), R2(L)
Arrow ←	Denotes transfer of information	R2 ← R1
Comma ,	Separates two microoperations	R2 ← R1, R1 ← R2

Bus and Memory Transfers

- Paths must be provided to transfer information from one register to another
- A Common Bus System is a scheme for transferring information between registers in a multiple-register configuration
- A bus: set of common lines, one for each bit of a register, through which binary information is transferred one at a time
- Control signals determine which register is selected by the bus during each particular register transfer

Bus and Memory Transfers

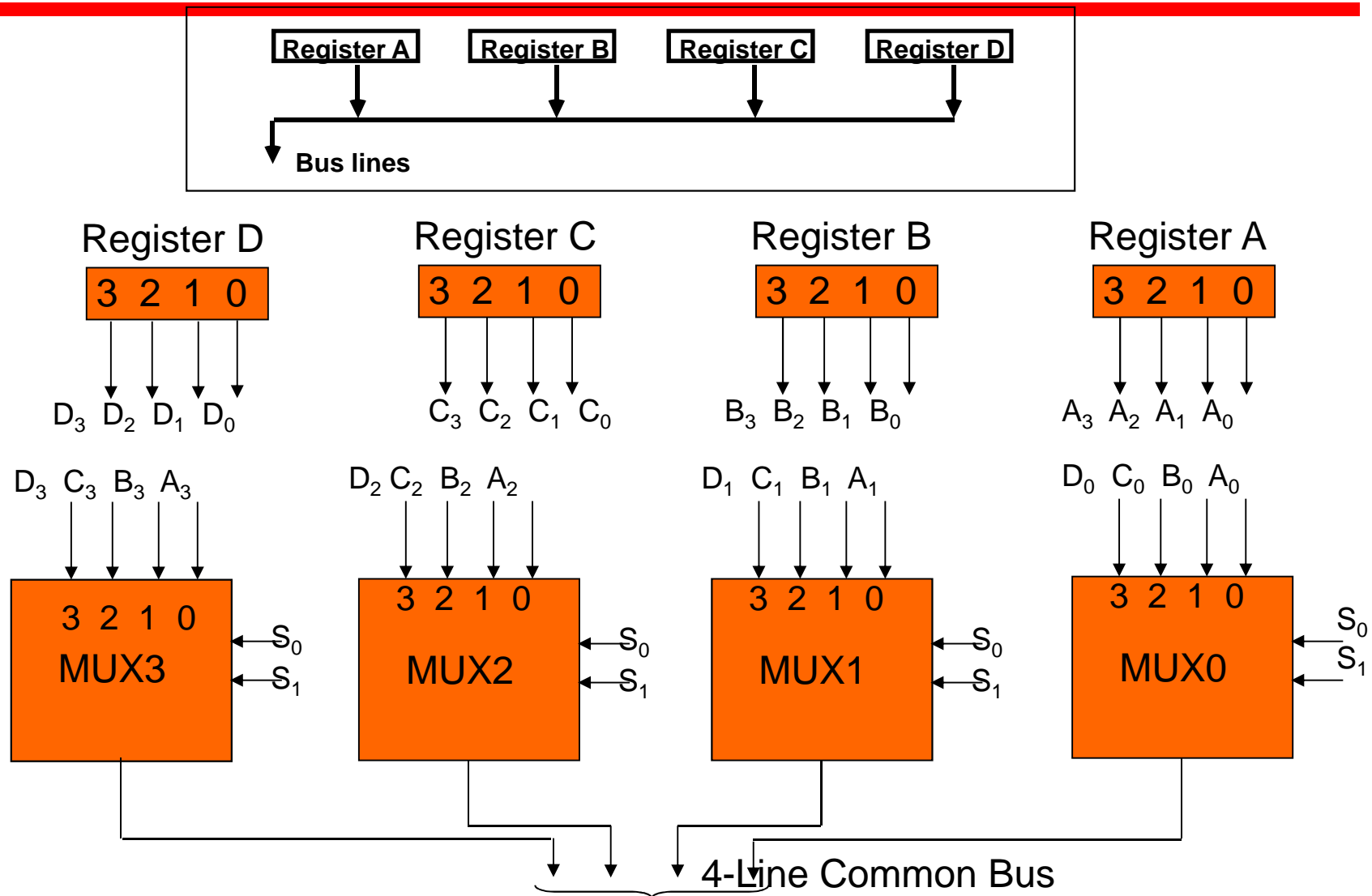


Bus and Memory Transfers

- The transfer of information from a bus into one of many destination registers is done:
 - By connecting the bus lines to the inputs of all destination registers and then:
 - activating the load control of the particular destination register selected
- We write: $R2 \leftarrow C$ to symbolize that the content of register C is *loaded into* the register $R2$ using the common system bus
 - It is equivalent to: $BUS \leftarrow C$, (select C)


$R2 \leftarrow BUS$ (Load $R2$)

Bus and Memory Transfers: Three-State Buffers

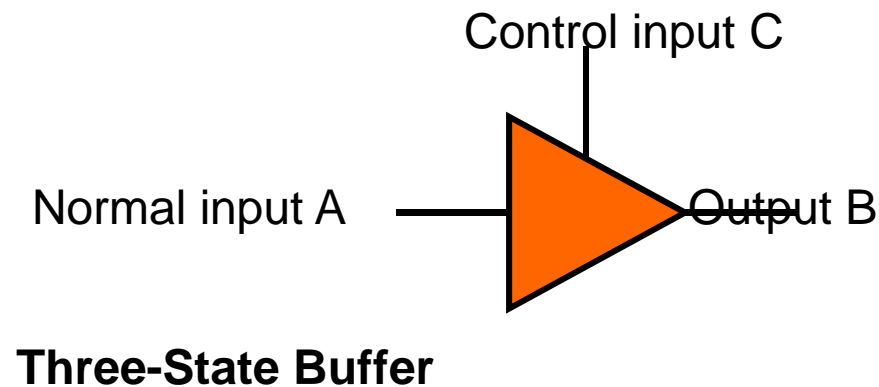
- A bus system can be constructed with three-state buffer gates instead of multiplexers
- A three-state buffer is a digital circuit that exhibits three states: logic-0, logic-1, and high-impedance (Hi-Z)



 Bus and Memory Transfers: Three-State Bus Buffers cont.



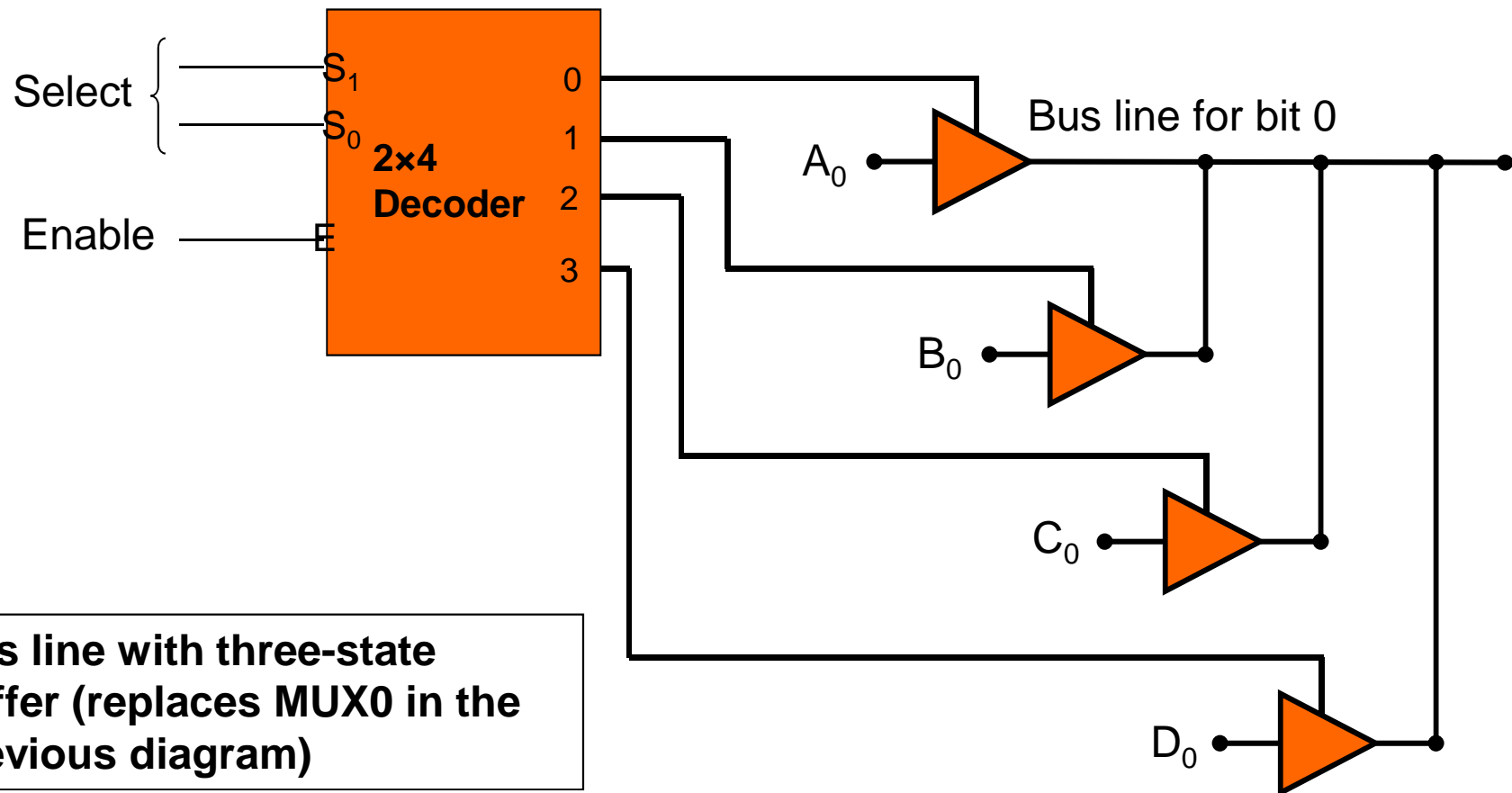Bus and Memory Transfers: Three-State Bus Buffers cont.




Bus and Memory Transfers: **Memory Transfer**

- Memory read : Transfer from memory
- Memory write : Transfer to memory
- Data being read or wrote is called a memory word (called M)- (refer to section 2-7)
- It is necessary to specify the address of M when writing /reading memory
- This is done by enclosing the address in square brackets following the letter M
- Example: M[0016] : the memory contents at address 0x0016

Bus and Memory Transfers: Memory Transfer cont.


- Assume that the address of a memory unit is stored in a register called the Address Register AR
- Lets represent a Data Register with DR, then:
 - Read: $DR \leftarrow M[AR]$
 - Write: $M[AR] \leftarrow DR$

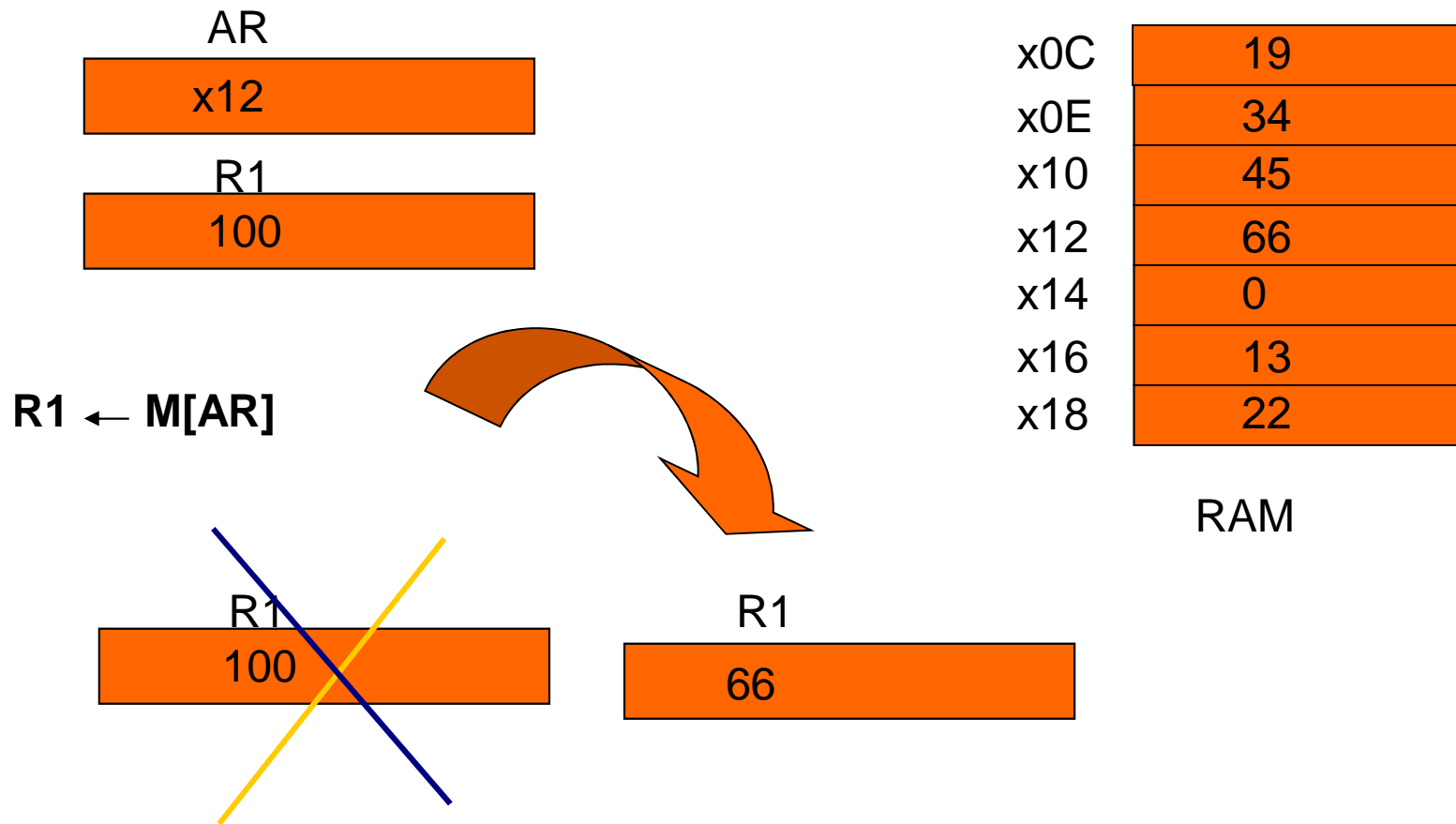Bus and Memory Transfers: Memory Transfer cont.




Arithmetic Micro-operations

- Binary Adder

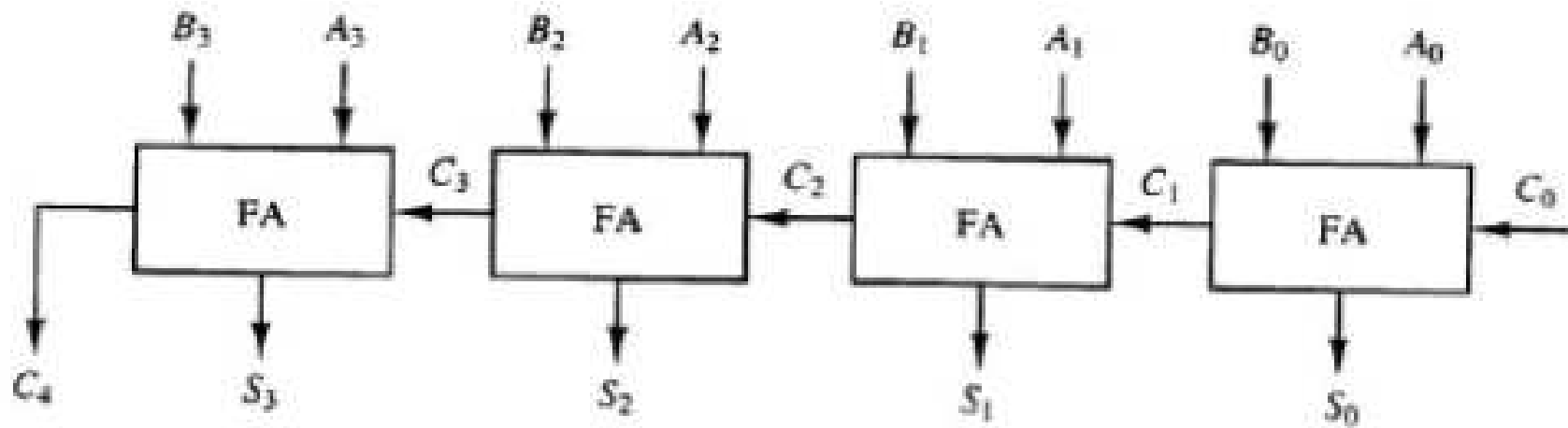


Arithmetic Micro-operations

- Binary Adder/Subtractor

 


Arithmetic Circuit

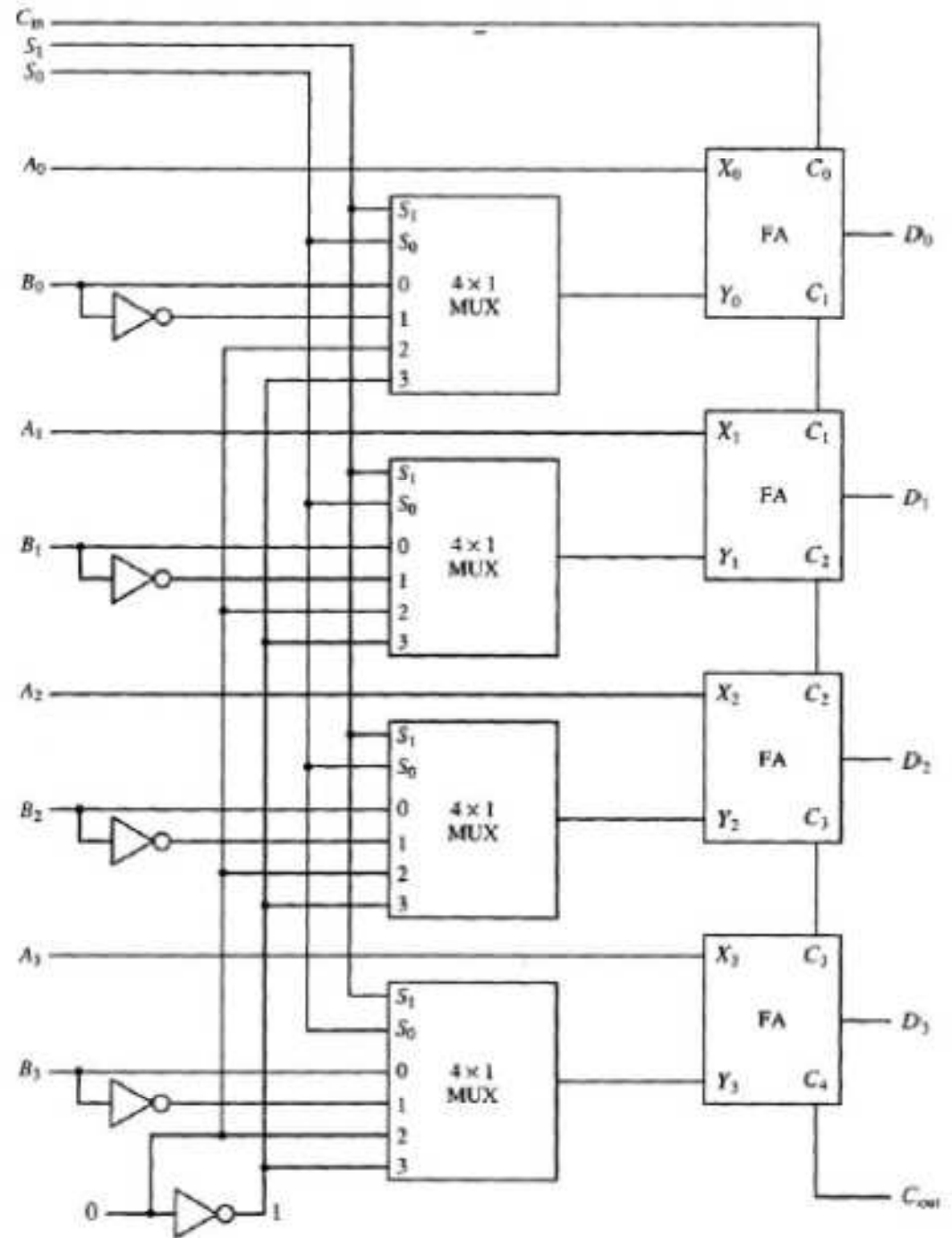

Arithmetic Circuit

Select			Input Y	Output $D = A + Y + C_{in}$	Microoperation
S_1	S_0	C_{in}			
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	\overline{B}	$D = A + \overline{B}$	Subtract with borrow
0	1	1	\overline{B}	$D = A + \overline{B} + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

Logical Circuit

 

(a) Logic diagram

S_1	S_0	Output	Operation
0	0	$E = A \wedge B$	AND
0	1	$E = A \vee B$	OR
1	0	$E = A \oplus B$	XOR
1	1	$E = \bar{A}$	Complement

(b) Function table