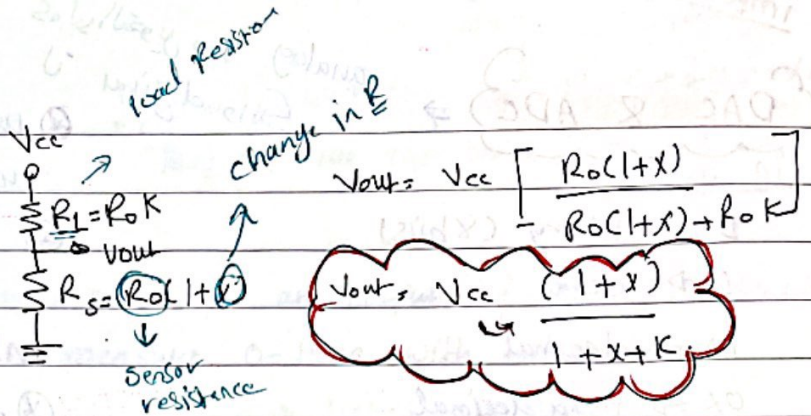


Ac & DC Bridges

Voltage divider



what is the sensitivity?

↳ derivative

$$\frac{d}{dx} \left[\frac{V_{cc}(1+x)}{1+x+K} \right]$$

$$\Rightarrow \frac{V_{cc} K}{(1+x+K)^2} \rightarrow \text{The sensitivity.}$$


What is the value of R_L to achieve max sensitivity?

$$\frac{ds}{dK} = 0 \Rightarrow K = 1+x, \text{ so when } R_s = R_L$$

Wheatstone bridge (DC)

Deflection mode
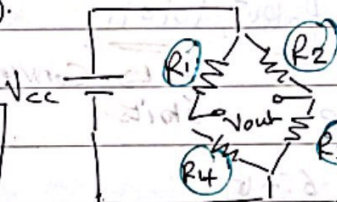
$$V_{out} = V_{cc} \left[\frac{R_3}{R_3+R_2} - \frac{R_4}{R_1+R_3} \right]$$



Null mode

$$V_{out} = 0 \Rightarrow R_3 = R_4 \frac{R_2}{R_1}$$

$$K = \frac{R_1}{R_4} = \frac{R_2}{R_0}$$

$$V_{out} = V_{cc} \frac{Kx}{(1+K)(1+K+x)}$$

Wheatstone bridge is used when change of x is small.

The sensitivity of wheatstone bridge?

$$\frac{dV_{out}}{dx} \rightarrow \text{the same as voltage divider}$$

Null mode → used with measurements is independent of V_{cc}

AC Bridges

Wheatstone bridges can be used to calculate inductance & capacitance

Balance → $\frac{Z_1}{Z_4} = \frac{Z_2}{Z_3}$ → real & imaginary parts $[R + jX]$ each one of them

$$R_1 R_3 - X_1 X_3 = R_4 R_2 - X_4 X_2$$

important


DAC & ADC
in arduino

analogي القوي من
الرقم digital

- B \Rightarrow Binary (8 bits)
- O \Rightarrow Octal
- no \Rightarrow decimal
- 0x \Rightarrow hexa decimal

usually natural binary coding is used

Digital code consist of n bits.

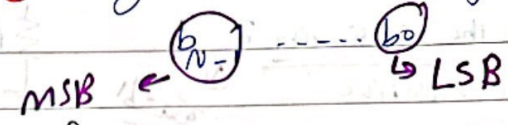

Fractions.

Range: $0 \rightarrow (1 - 2^{-N})$ when N is the # of bits.
Precision: 2^{-N}

ADC

ADC \leftrightarrow DAC

$$\left[\frac{V_{analog}}{V_{ref}} \right] = \frac{N_{10}}{2^N} \times U_{ref}$$

This formula can be used for both DAC & ADC

V_{ref} for DAC $\leftarrow V_{ref} = 10V, 101011$: 101011 لو كان على رقم ديجتال 6 bits
 $= 10V$ \downarrow \rightarrow Convert this to decimal.

what is the analog value?

$$V_{analog} = \frac{43}{2^6} \times 10 = 6.7V$$

لو كان الرقم الالكتري من انا لينا فيه analogي

ADC digital representation

$6.7V = V_{analog}$ متة لغرفة
bits are 6 bits.
 $V_{ref} = 10$

$$N_{10} = 2^N \cdot \frac{V_{analog}}{V_{ref}}$$

$$INT(N_{10}) = 2^6 \cdot \frac{6.7}{10} \approx 43$$

101010 \leftarrow 42

\Rightarrow so we have an error

دقة التحويل الحالية
Resolution of one bit.

$$\Delta V = \frac{V_{ref}}{2^n}$$

Resolution \Rightarrow دقة التحويل
الايتر

clearly, the resolution of ADC or DAC كلما كان الرقم اعظم كان دقة

او دقة الالكتري او ال DAC (دقة الالكتري) كلما كان الرقم اعظم كان دقة

\rightarrow كلما كان عدد ال bits او دقة ال voltage (V_{ref})

about Arduino: Its clear that the arduino have both ADC and DAC
 ↓ at input ↓ at output

لا لارن تكون علمية عدال Bits لكد واحد منهم!
 They are not the same (the # of bits differ).

Example

Temperature is to be measured by a sensor with an output of 0.02 V/C . Determine required ADC (Reference, word size) to measure $0-100\text{C}$ with 0.1 Resolution.
 ↳ # of bits Temp is in Sensor

ادرس ان ADC اللى بيقيد نختار Resolution
 ↳ Resolution 0.1C Resolution لرد 0.1C degree

→ Range $0-100$ with increment 0.1
 So we need $\frac{100}{0.1}$ change → 1000 change ⇒ 10 bits → # of bits.

$0.02 \text{ V/C} \times 100 \text{ C} \Rightarrow 2 \text{ V}$ (V_{ref})
 ↳ must be 2 V + increment of resolution for ADC

Resolution = $\frac{V_{ref}}{2^N}$ Bits. V_{ref} بقدر لعرفه عدال

A 0.1C resolution results in $0.1 \times 0.02 = 2 \text{ mV}$

$2 \text{ mV} = \frac{2}{2^N} \Rightarrow 2^N = 1000$
 $N = 10 \text{ bits}$

او عند مثال العزيمه اللى فزيده

What is the maximum input that we can put at ADC?

V_{ref} هو الحد، لا لارن اقص! منطقياً لارن تكون اقل ب step من V_{ref}

So V_{max}

So the answer is V_{ref} - resolution of 1 bit

V_{ref} لارن تكون اقل ب step من V_{ref}

$V_{min} = 0$, $V_{max} = V_{ref} \left(\frac{2^N - 1}{2^N} \right)$

Step Size = $\frac{V_{max} - V_{min}}{\# \text{ of levels}}$

Q (Step) size = $\frac{V_{fullscale}}{2^N - 1}$
 or $\frac{V_{ref}}{2^N}$

$V_{fullscale} = V_{max} - V_{min}$
 ↳ V_{ref}

Res = $\frac{V_{fullscale}}{2^N}$
 ↳ $\frac{V_{ref}}{2^N}$

Quantization error range
 ↳ $\left[-\frac{\Delta}{2}, \frac{\Delta}{2} \right]$

Res 0.1C
 ↳ $\frac{V_{ref}}{2^N}$

Uni Polar & Bipolar

① Uni Polar

$$V_{analog} = \frac{N_{10}}{2^n} \cdot V_{ref} \leftarrow DAC$$

$$INT[N_{10}] = \frac{V_{analog} \cdot 2^n}{V_{ref}} \leftarrow ADC$$

② Bipolar

$$V_{analog} = \frac{N_{10}}{2^n} \cdot V_{ref} - \frac{V_{ref}}{2} \rightarrow DAC$$

$$INT(N_{10}) = \left[V_{analog} + \frac{V_{ref}}{2} \right] \times 2^n \rightarrow ADC$$

step next V_{ref} in V_{max} or $V_{ref} \times 2$


ADC

\Rightarrow is exactly the same process of DAC

Now, How to realize operation of DAC & ADC?

DAC & ADC

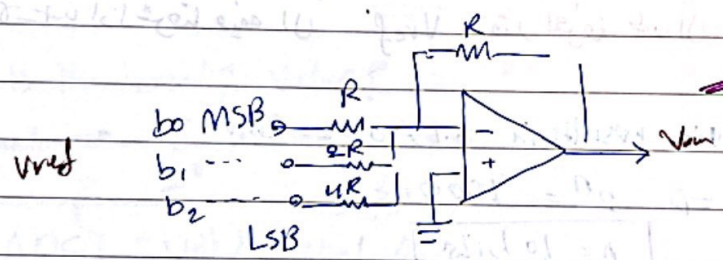كيف يمكن ان يكون الواجهة لتحويل التماثل الى رقمي




Have a problem with resistances.

$$V_{out} = \left[b_0 + \frac{b_1}{2} + \frac{b_2}{2^2} \right] \cdot V_{ref}$$

$$V_{out} = \frac{N_{10}}{2^n} \cdot V_{ref} \Leftrightarrow \underline{DAC} \text{ (Digital to analog)}$$

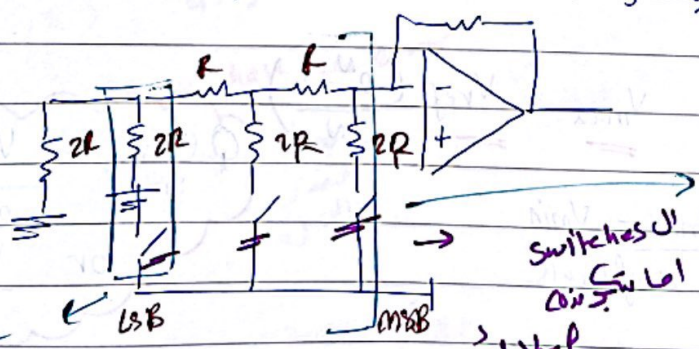كيف يمكن ان يكون الواجهة لتحويل التماثل الى رقمي





Thevenin

Switches ال
او التماثل

each one of these branches is bit

(ground) = 0 or 1, V_{ref}

The circuit become as follow:

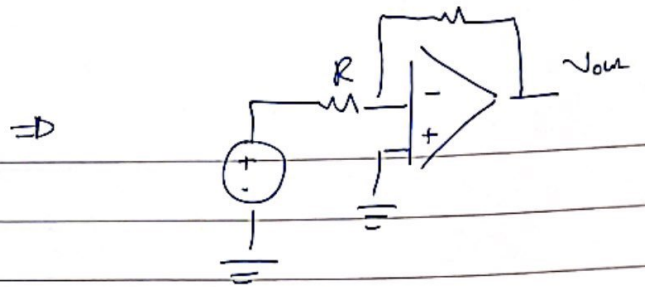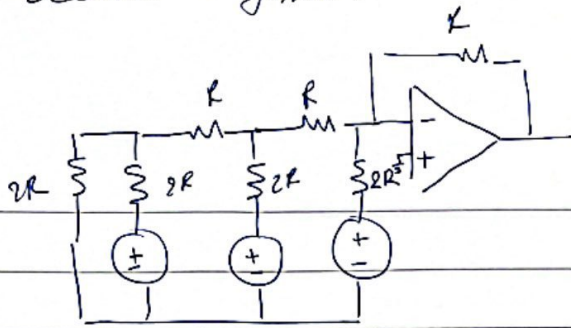

So that $V_{out} = \frac{N}{2^N} \cdot V_{ref}$

PWM

العرضة التي تتغير مع عرضة إشارة الـ signal width

Generating a pulse signal, width of this pulse proportional to amplitude

عرضة النبضة، يتغير مع عرضة إشارة الـ signal width

So, the signal is represented rather than its amplitude and its width.

PWM it is a technique that we could use in order to generate analog value proportional to its input

How to convert PWM to analog?

↳ using Low pass filter

Duty cycle = $\frac{T_{on}}{T}$, 0 → 100%

Frequency = $\frac{1}{T}$ rad/sec

How PWM signal is DC?

DAC → output ليس analog

? PWM ليس output ليس غير الـ signal