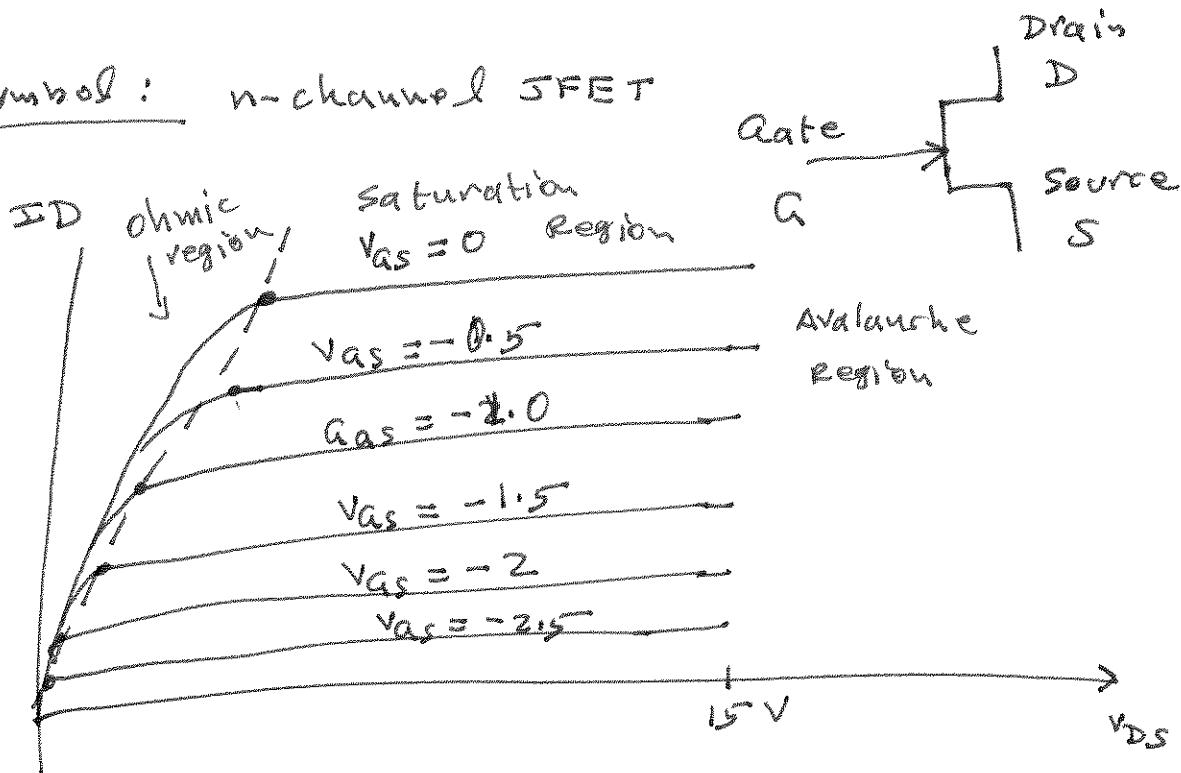


Experiment 8

The Field Effect Transistor

(1)

Symbol: n-channel JFET




Transfer characteristic curve

when V_{DS} is held constant

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$



I_{DSS} : saturation current for D-S

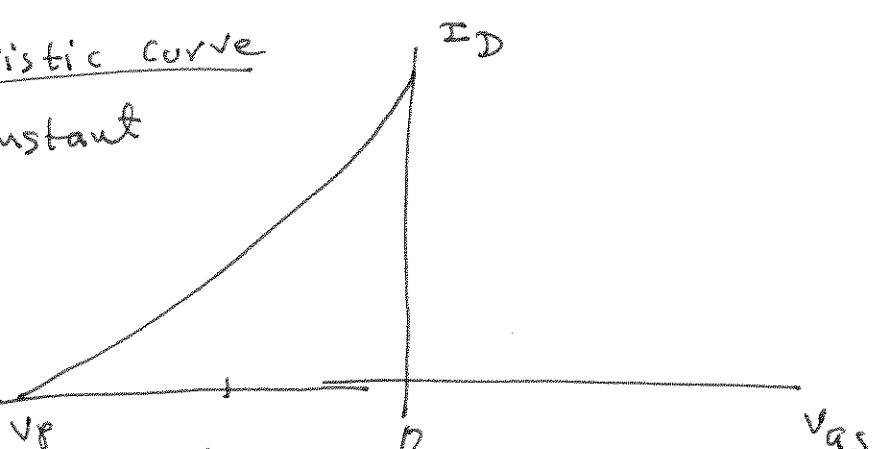

V_p : pinchoff voltage, at voltage below which the transistor turns off.

(2)

JFET Amplifier

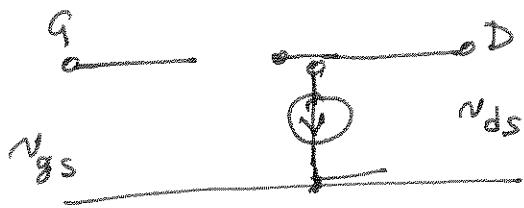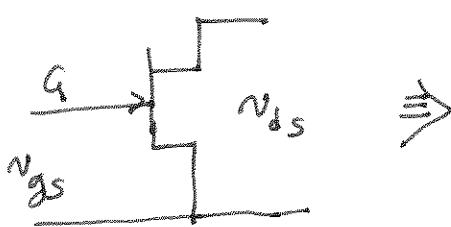

- JFET: $i_d = g_m v_{gs}$: voltage-controlled current amplifier
- JFET: $i_d = k_f e^{i_b}$: current-controlled current amplifier


$$\text{set } v_{DS} = 10 \text{ V}$$

$$R_s = 0$$

$$v_i = 2 \text{ V p-p}$$

$$\text{gain} = \frac{v_o}{v_i}$$

$$R_i = \frac{v_i}{i_i}$$

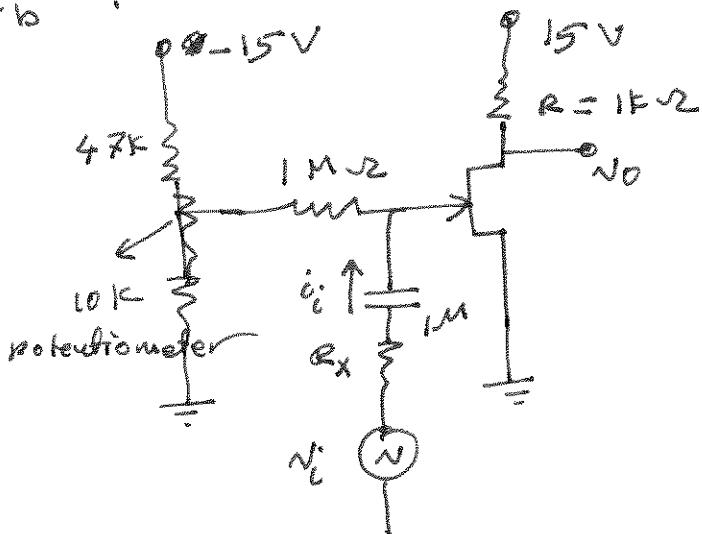


Constant Current Source

$$\text{Here, } v_{AS} = 0$$

$$v_{DD} = I_D R_L + v_{GS}$$

$$R_L = v_{DD} - v_{AS}$$

$$I_D = \frac{v_{DD} - v_{AS}}{R_L}$$

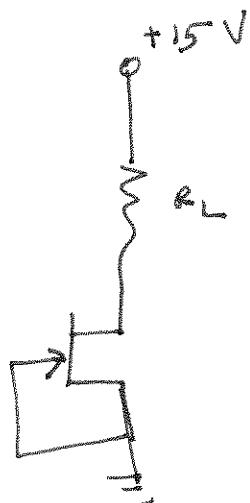

I_D will remain almost constant over a wide range of load resistance.