



Department

Of electrical and computer

Engineering

ENEE2103

CIRCUITS AND ELECTRONICS LABORATORY

Experiment No.10 Report

Report#2

Instructor: Dr. Alhareeth Zyoud

Made By: Yousef Hammad

ID: 1170625

Partners: 1) Islam Jihad

2) Wejdan Aljamal

TA: Eng. Ismail Abualia

Date: 08/11/2021

Abstract

The aim of the experiment is to show how some of the Operational Amplifier Applications works and how to implement the circuits to use them, it shows the adding, voltage follower, comparator, integrator, differentiator, the effect of adding hysteresis and active clipping.

Components used for the experiment:

- DC and AC Voltage sources
- Circuit board
- Op Amp
- Resistors: 100k, 10k, 220, 220k, 50k, 500k.
- Potentiometer 10k
- Capacitors 1uF
- Diode and zener diode

Contents

Abstract	I
List of figures and tables	III
Theory	1
Without feedback	1
Negative feedback	1
Positive feedback	4
Procedure and data analysis	5
I. Adding Application	5
II. Voltage Follower Application	5
III. Comparator Application	7
IV. Integrator and Differentiator	9
V. To investigate the effect of adding hysteresis	12
VI. Active Clipping Circuit	13
Conclusion	15
References	16

List of figures and tables

Figures:

Figure 1. 1 Comparator Circuit	1
Figure 1. 2 Adding circuit.....	2
Figure 1. 3 Voltage follower Circuit.....	2
Figure 1. 4 Integrator circuit	3
Figure 1. 5 Differentiator circuit.....	3
Figure 1. 6 Active Clipping cercuit.....	4

Figure 2. 1 Adding application Circuit	5
Figure 2. 2 Voltage Follower Application Circuit	6
Figure 2. 3 Voltage Follower $V_o(t)$	6
Figure 2. 4 Comparator Application circuit.....	7
Figure 2. 5 Comparator Application square wave output	8
Figure 2. 6 Comparator Application square wave output	8
Figure 2. 7 Integrator Application Circuit	9
Figure 2. 8 Integrator Application sin wave	9
Figure 2. 9 Integrator Application triangular wave	10
Figure 2. 10 Integrator Application square wave.....	10
Figure 2. 11 Differentiator Application Circuit	10
Figure 2. 12 Differentiator Application sin wave	11
Figure 2. 13 Differentiator Application triangular wave	11
Figure 2. 14 Differentiator Application square wave	12
Figure 2. 15 Adding Hysteresis Circuit	12
Figure 2. 16 Adding hysteresis V_o	12
Figure 2. 17 Active Clipping Circuit	13
Figure 2. 18 Active Clipping with V_o positive clipped	13
Figure 2. 19 Active Clipping with V_o negative clipped	14

Tables:

Table 1. 1 Adding Application V_o VS V_1, V_2	5
Table 1. 2 Voltage follower V_i vs V_o for 220Ω	6
Table 1. 3 Voltage follower V_i vs V_o for 220Ω	7

Theory

The theoretical part of the circuits built in this experiment is going to be explained in this part of the report.

There are three main configurations of the op amp connections depending on the feedback on the op amp, the main configurations are:

Without feedback

The only circuit in the experiment connected without feedback is the **comparator Application** circuit.

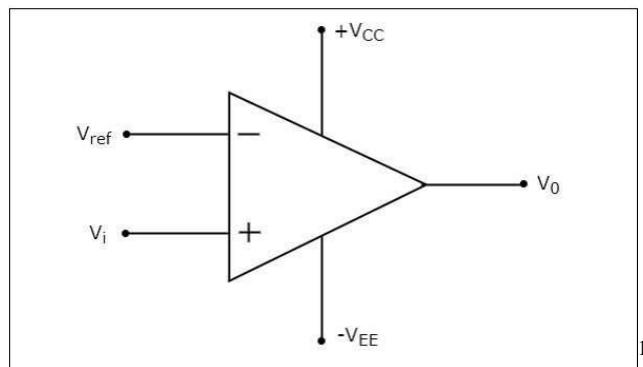


Figure 1. 1 Comparator Circuit

In the circuits shown above, the V_o could be one of three values:

- $V_o = +V_{sat}$; $V_i < V_{ref}$
- $V_o = 0$; $V_i = V_{ref}$
- $V_o = -V_{sat}$; $V_i > V_{ref}$

In the experiment an AC voltage is applied on the positive input of the op amp, in that case V_o is a signal.


Negative feedback

In this configuration, five applications are shown in the experiment.

The five applications are:

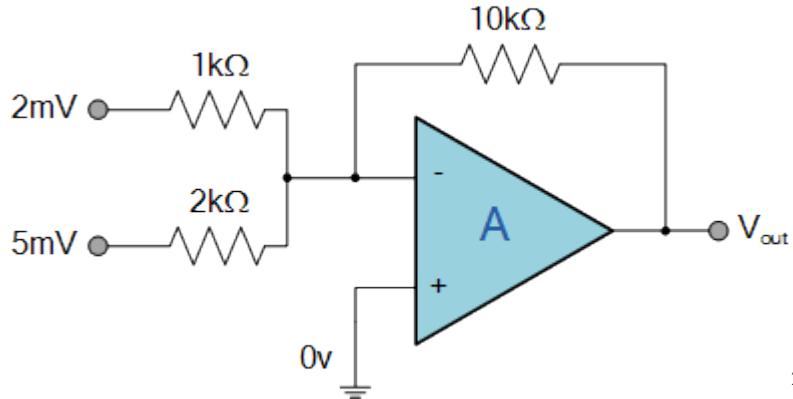1. Adding Application

In this application, two voltages are applied to the negative input of the op amp, each connected with a resistor that controls the weight of the voltage and a resistor called Rref is connected between the output and the negative input of the op amp.



2


Figure 1. 2 Adding circuit

In this circuit:

$$V_{out} = -R_{ref} \cdot \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

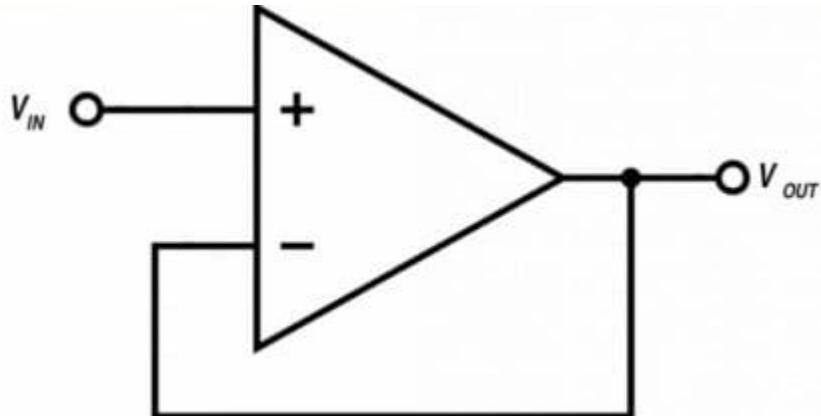2. Voltage follower

In this application, a voltage is applied to the positive terminal of the op amp and the output is connected to the negative input of the op amp.



3

Figure 1. 3 Voltage follower Circuit


² https://www.electronics-tutorials.ws/opamp/opamp_4.html

³ <https://www.allaboutcircuits.com/video-tutorials/op-amp-applications-voltage-follower/>

This circuit is essentially a buffer so $V_o = V_{in}$ but it isolates the input from the output

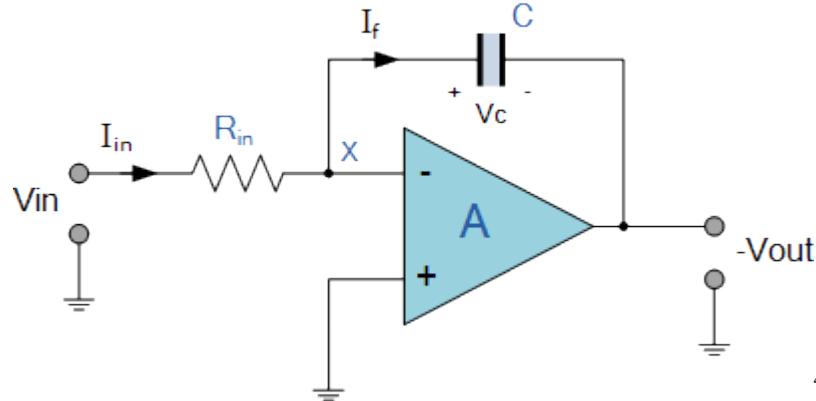3. Integrator

In this application, a voltage source is applied to the negative input of the op amp and the output is connected to the negative input via a capacitor.




4

Figure 1. 4 Integrator circuit

$$V_o = (1/RC) * (V_{in} dt)$$

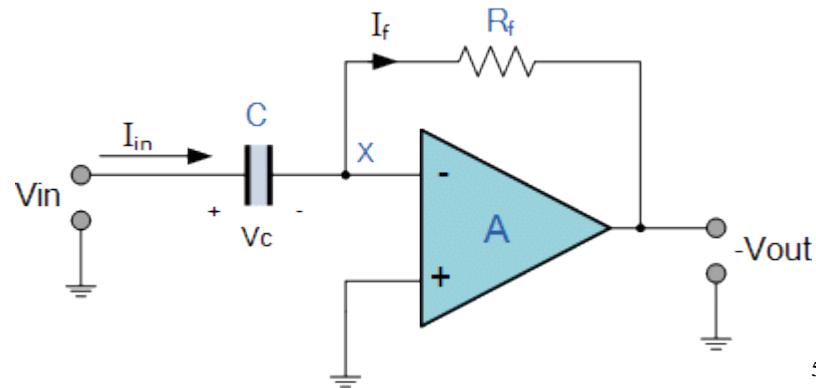4. Differentiator

In this application, a voltage source is connected to the negative input of the op amp via a capacitor and the output is connected to the negative input via a resistor called Rref



5

Figure 1. 5 Differentiator circuit

$$V_{out} = -R_{ref} \cdot C \cdot (dV_{in}/dt)$$

5. Active Clipping

⁴ https://www.electronics-tutorials.ws/opamp/opamp_6.html

⁵ https://www.electronics-tutorials.ws/opamp/opamp_7.html

In this application, a voltage source is applied to the positive input of the op amp and the output is connected to the negative input of the op amp via a diode.

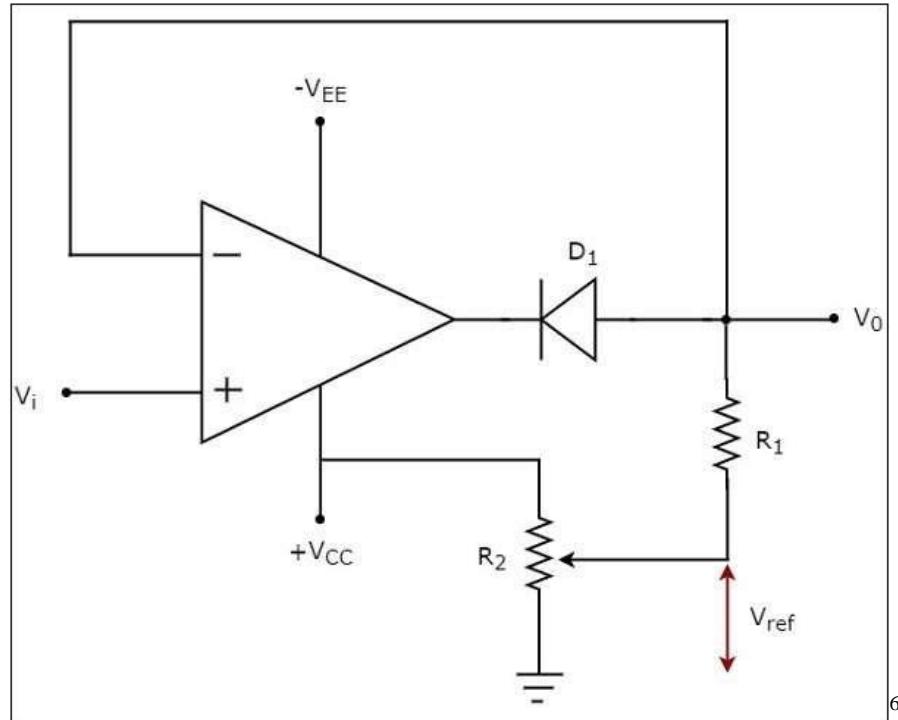


Figure 1. 6 Active Clipping circuit

V_{out} is clipped at certain outputs.

Positive feedback

In this configuration, only one application is shown in the experiment and it's the effect of adding hysteresis.

In this application, a voltage source is applied to the negative input of the op amp and a voltage source is applied to the positive one with a feedback to the positive input.

$V_o = V_{sat}$ in a certain range of V_{in}

$V_o = -V_{sat}$ in the remaining range of V_{in}

Procedure and data analysis

In the following experiment, seven circuits are going to be connected each shows how the op amp works.

I. Adding Application

1. The circuit in figure 2.1 should be connected. The potentiometer will control V1 and V2 will be controlled by the variable DC power supply.

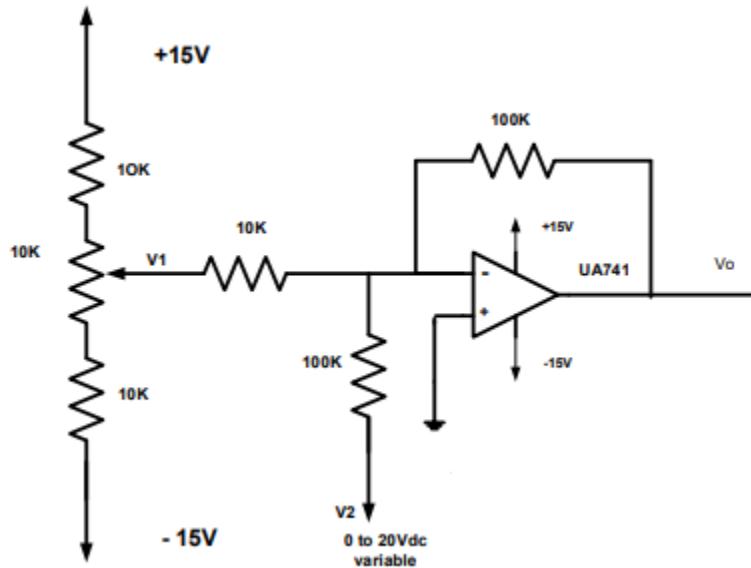


Figure 2. 1 Adding application Circuit

2. The output voltage V_o will be measured by the DC voltmeter for V_1 and V_2 shown in the table 1.1

Input voltage		Output voltage	
V1	V2	V0	Calculated voltage
0.5	2	-7.1	-7
0.1	6	-7.25	-7
0.3	4	-6.95	-7
-0.9	2	6.8	7
-1.1	4	7.03	7
-1.5	6	8.88	9

Table 1. 1 Adding Application V_o VS V_1, V_2

3. The output voltage should be calculated for each entry of the table using the formula: $V_{out} = -R_{ref} * ((V_1/R_1) + (V_2/R_2))$

II. Voltage Follower Application

1. The circuit should be connected as shown in figure 2.2

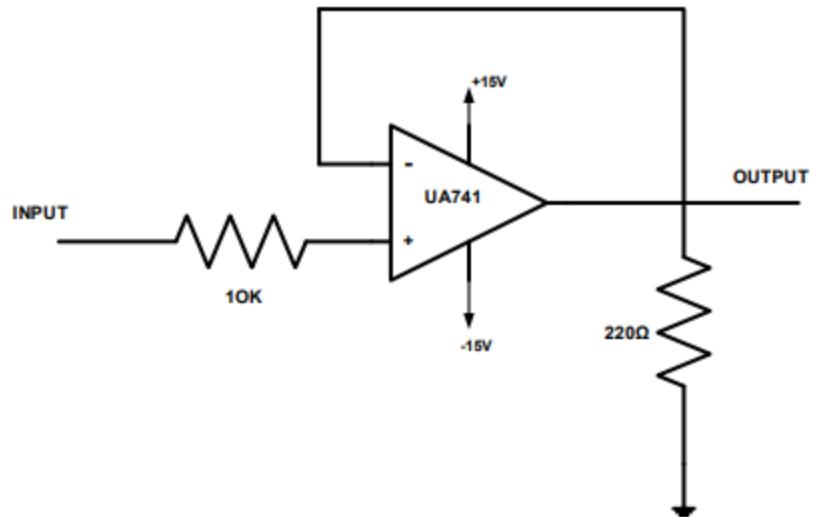


Figure 2. 2 Voltage Follower Application Circuit

2. $V_o(t)$ should be measured on the oscilloscope for $V_i(t) = 2V$ p-p sinusoidal with 100Hz which can be obtained from the AC Voltage supply

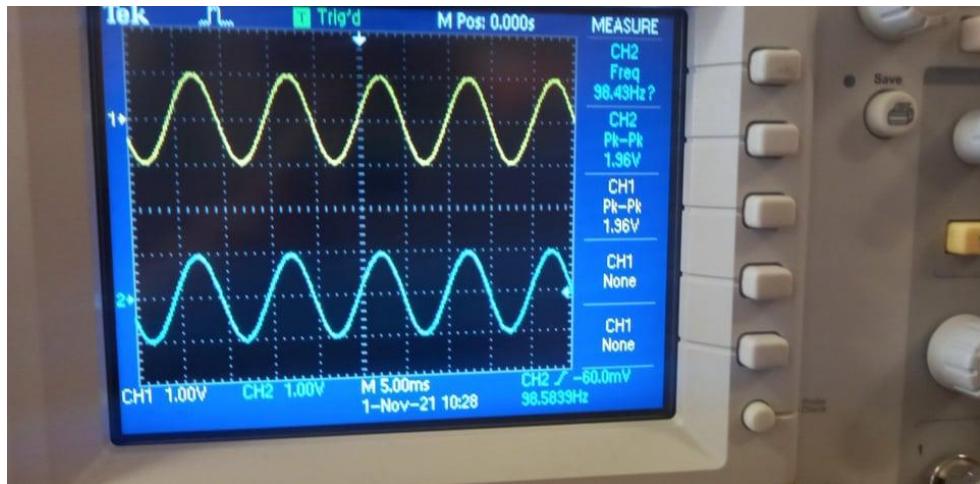


Figure 2. 3 Voltage Follower $V_o(t)$

3. V_o should be measured and recorded for DC V_i in table 1.2

Vi	Vo
2	2
4	4.05
6	6.01
7	6.27

Table 1. 2 Voltage follower Vi vs Vo for 220Ω

4. V_o should be measured and recorded for DC V_i in table 1.3 after R_L is changed from 220Ω to $1k\Omega$

V_i	V_o
6	6.08
8	7.9
10	10.04
12	12.01
15	12.96

Table 1. 3 Voltage follower V_i vs V_o for 220Ω

Question:

- Is this circuit has similar properties as the emitter follower. Explain ?
No its not, the Voltage follower doesn't provide any amplification to the voltage while the emitter follower does
- For what applications is this circuit used?
As a buffer to isolate circuit A from circuit B
- What is the relation between your V_i , V_o ?
 $V_o = V_i$; $V_i < V_{sat}$
 $V_o = V_{sat}$; $V_i \geq V_{sat}$
- What the approximate value of maximum output current of the op-amp?
 $I_{max} = 6.27/220 = 28.5mA$

III. Comparator Application

1. The circuit should be connected as shown in figure 2.4

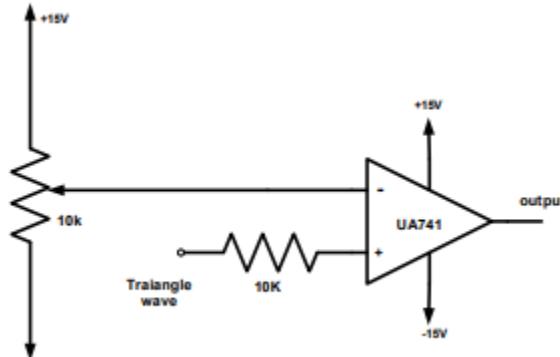


Figure 2. 4 Comparator Application circuit

2. Connect a $V_{in}(t)$ of 1kHz triangular signal from the function generator
3. The input signal should be set to 2 Vp-p and the DC reference voltage should be changed so that the $V_o(t)$ be positive V_{sat} then negative V_{sat} and a square wave
4. the output voltage should be on the oscilloscope

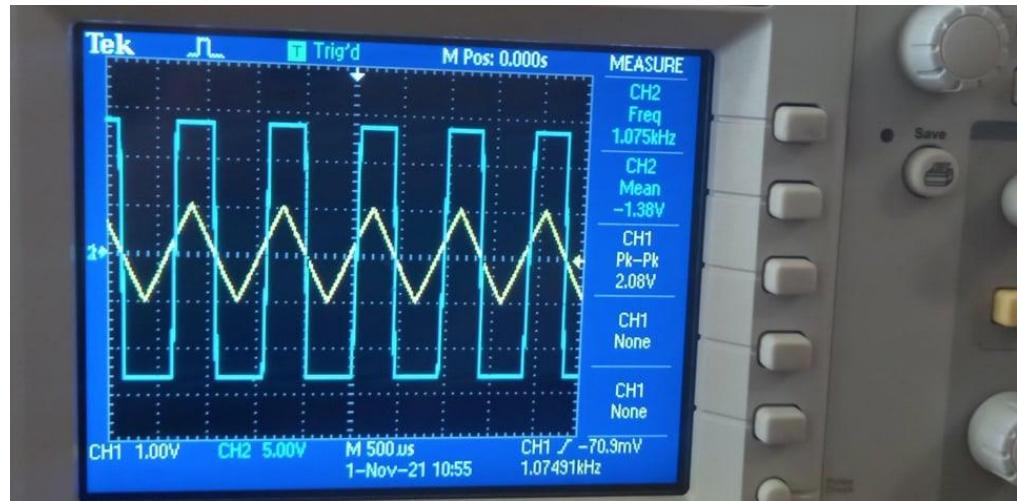


Figure 2.5 Comparator Application square wave output

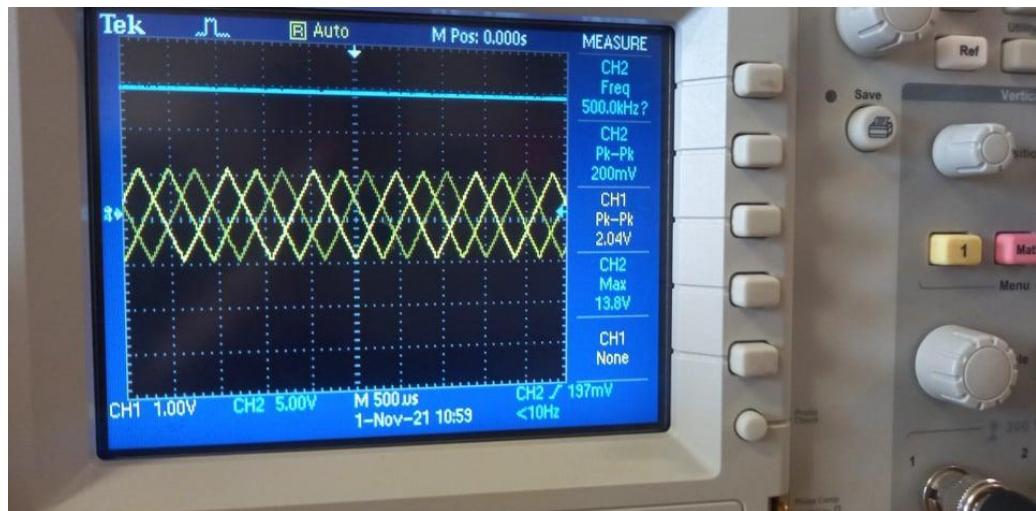


Figure 2.6 Comparator Application square wave output

Question:

5. What happens to the amplifier output?. For what application is this circuit used?
The output of the amplifier is:
 $V_o = V_{+sat}$; if $V_{i1} > V_{i2}$
 $V_o = 0$; if $V_{i1} = V_{i2}$
 $V_o = V_{-sat}$; if $V_{i1} < V_{i2}$
This Application can be used for 1-bit digital comparator and in analog to digital converters
6. Is there any similarity between this circuit and the diff amplifier, what is the shape of the output?

The diff amplifier can give the difference of two voltages but the comparator can only give +Vsat or -Vsat

IV. Integrator and Differentiator

A. Integrator

- the circuit should be connected as shown in figure 2.7

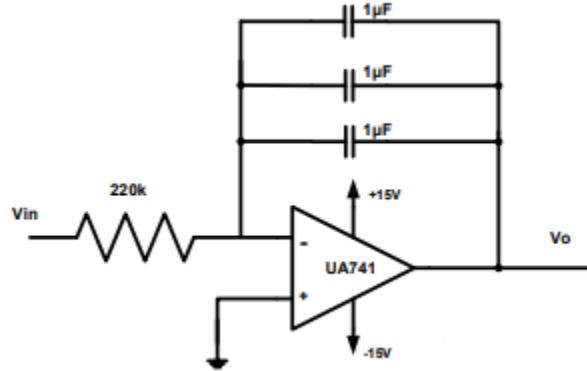


Figure 2. 7 Integrator Application Circuit

- an input signal with 2p-p and frequency of 30Hz from the function generator and dawn from the oscilloscope
- the output should be drawn for input of:
 - sin wave

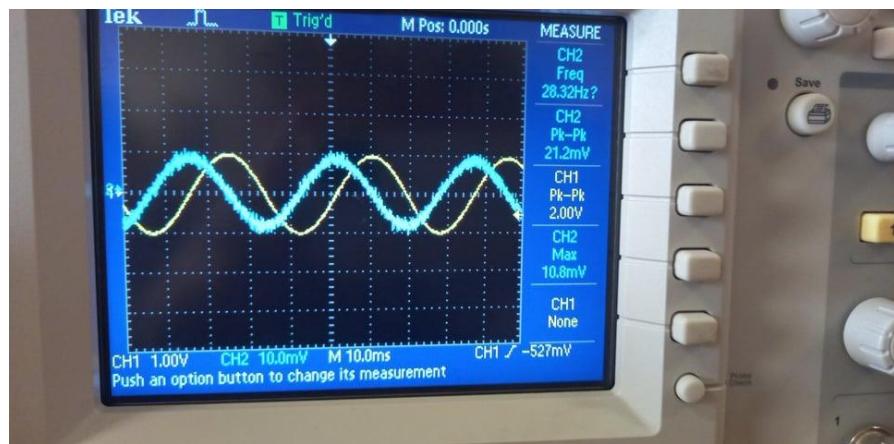


Figure 2. 8 Integrator Application sin wave

- triangular wave

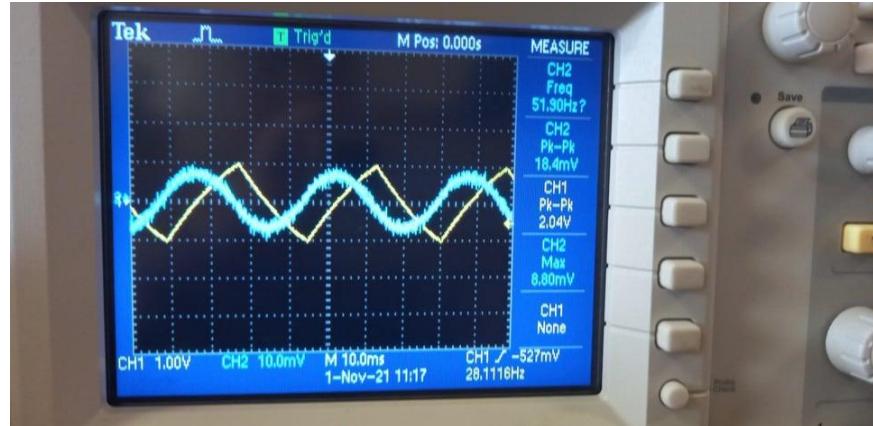


Figure 2. 9 Integrator Application triangular wave

- square wave

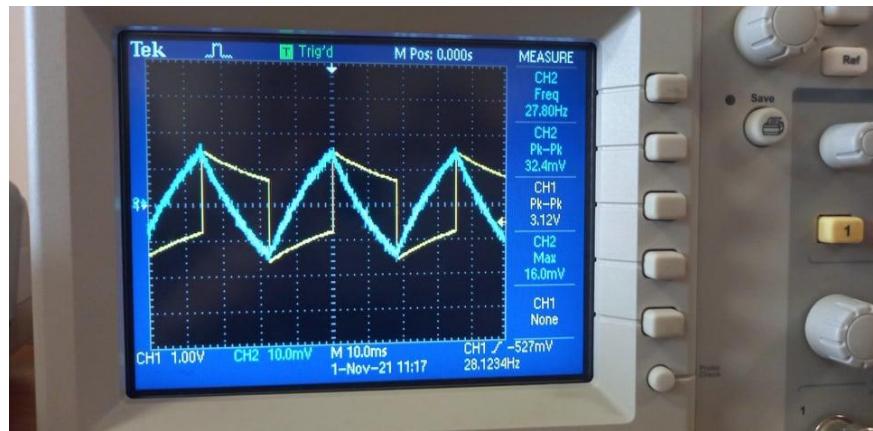


Figure 2. 10 Integrator Application square wave

B. Differentialtor:

1. the circuit should be connected as shown in figure 2.11

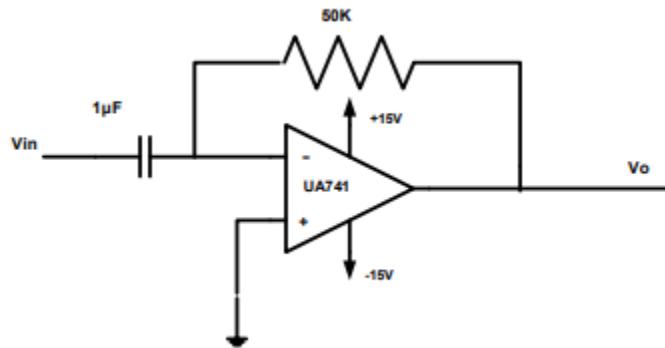


Figure 2. 11 Differentiator Application Circuit

2. an input signal with 2p-p and frequency of 30Hz from the function generator and dawn from the oscilloscope

3. the output should be drawn for input of:

- sin wave

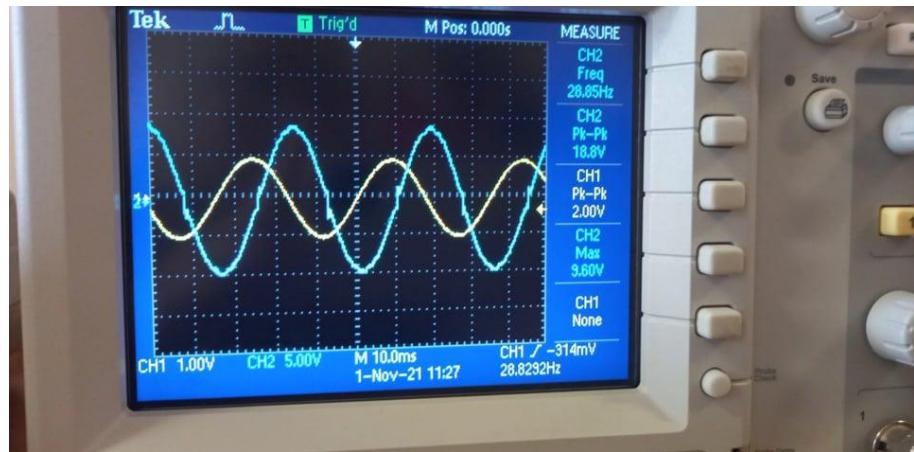


Figure 2. 12 Differentiator Application sin wave

- triangular wave

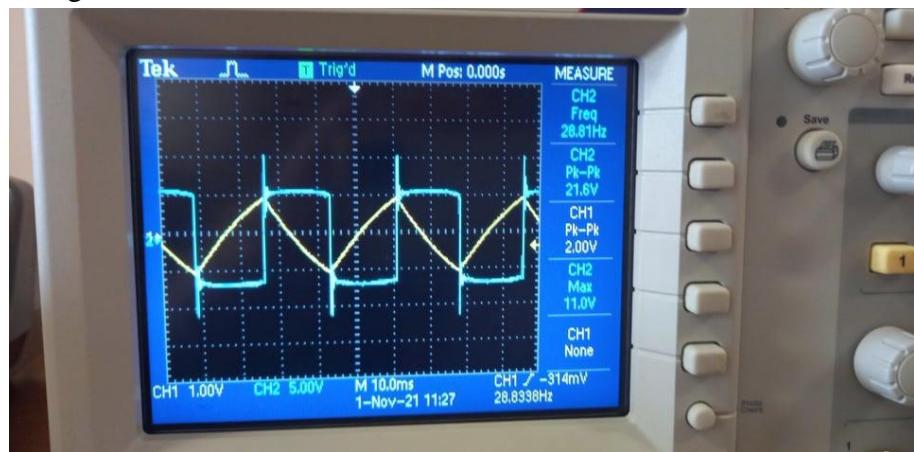


Figure 2. 13 Differentiator Application triangular wave

- square wave

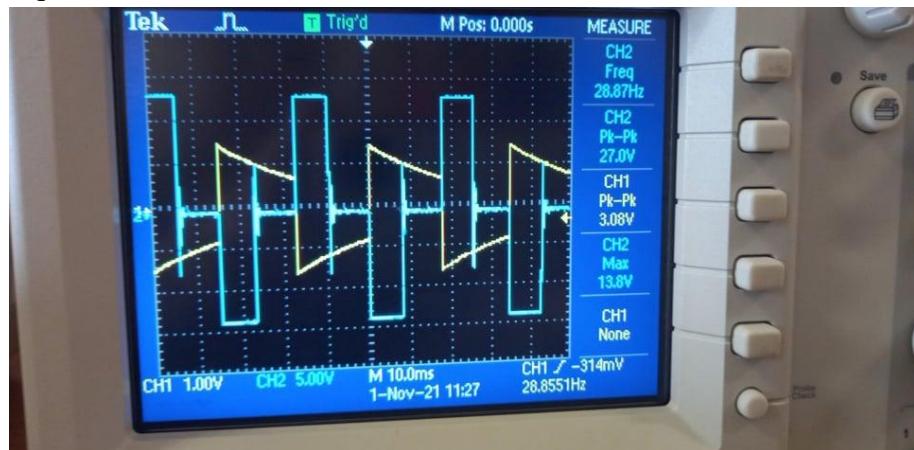


Figure 2. 14 Differentiator Application square wave

Question:

- Is the output realize the differentiation and integration theory?
Yes it does,

V. To investigate the effect of adding hysteresis

1. The circuit should be connected as shown in figure 2.15

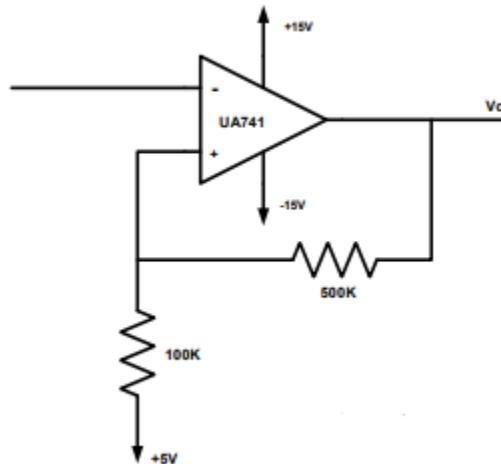


Figure 2. 15 Adding Hysteresis Circuit

2. $V_i(t)$ should be generated from the function generator with a 15Vp-p and frequency of 1kHz
3. $V_o(t)$ should be shown on the oscilloscope
4. The change of $V_o(t)$ level should be indicated on the oscilloscope for $V_i(t)$

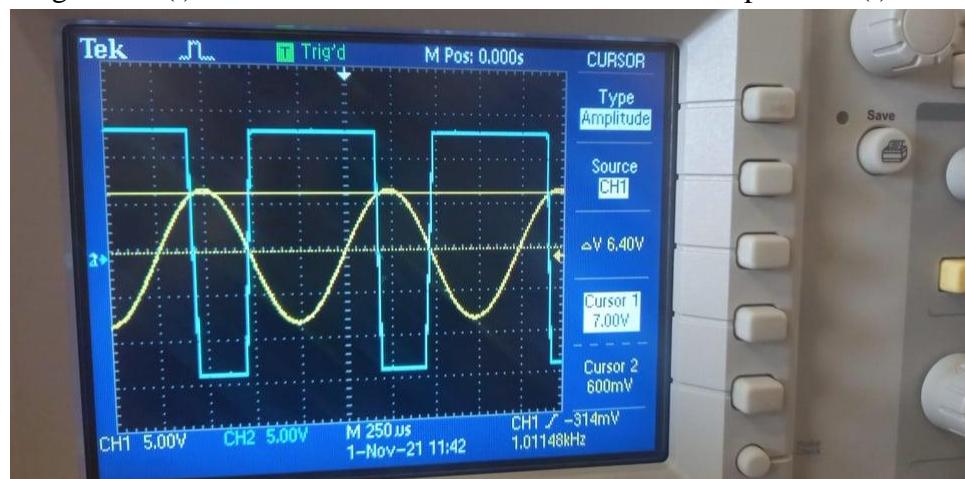


Figure 2. 16 Adding hysteresis V_o

VI. Active Clipping Circuit

1. The circuit should be connected as shown in figure 2.17

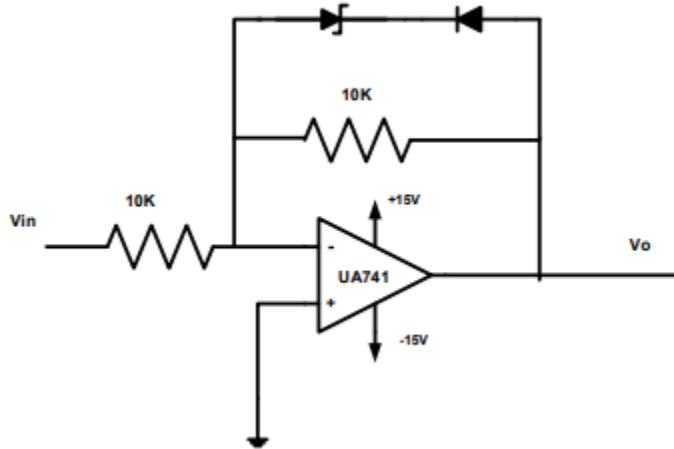


Figure 2. 17 Active Clipping Circuit

2. $V_i(t)$ should be taken from the function generator with frequency of 1kHz
3. The $V_i(t)$ amplitude should be changed until $V_o(t)$ is clipped and record it

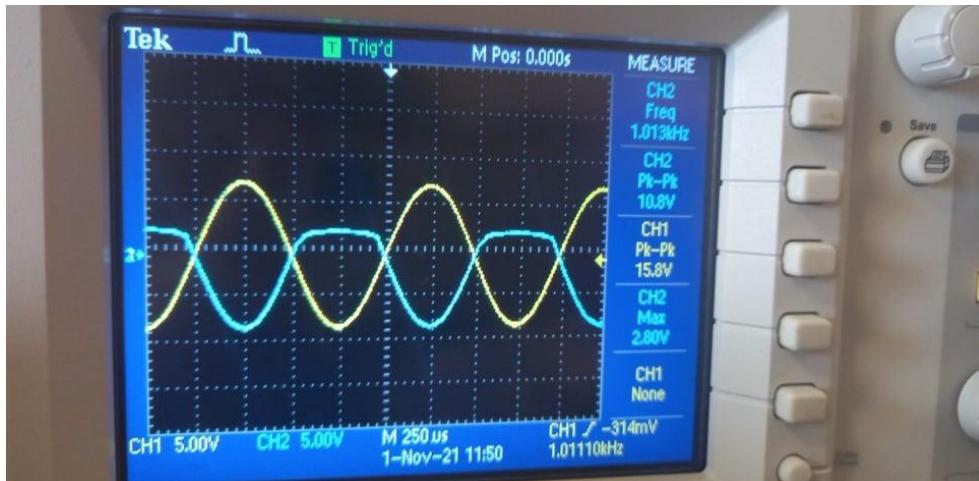


Figure 2. 18 Active Clipping with V_o positive clipped

4. The diodes should be reversed
5. The $V(t)$ amplitude should be changed until $V_o(t)$ is clipped and record it

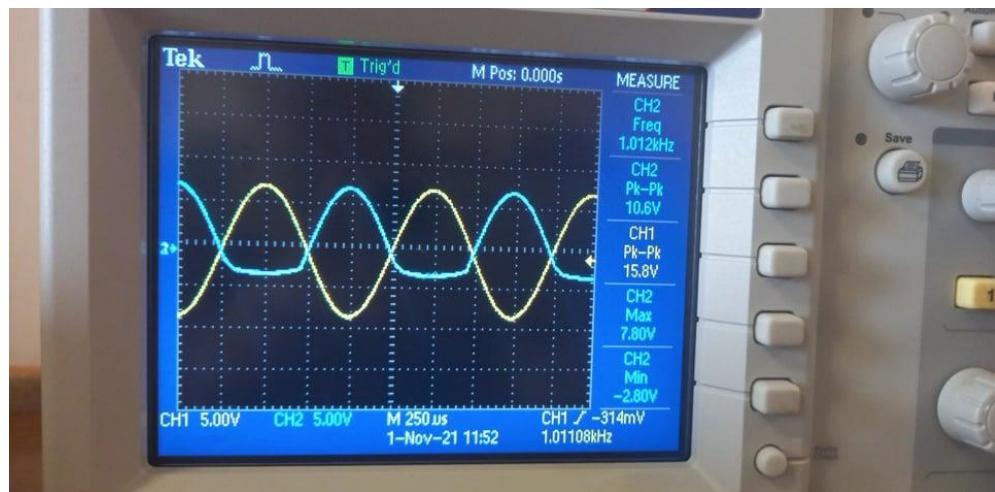


Figure 2. 19 Active Clipping with Vo negative clipped

Conclusion

The experiment showed how much the Operational amplifiers are powerfull, an how it can be used to perform certain mathematical and electrical functions, like adding, comparing, integral and differentiate Voltages, and also how to isolate circuits from others.

This also showed why the op amps where used in creating the early computers.

References

Theory:

<https://www.tutorialspoint.com/>

<https://www.electronics-tutorials.ws/>

<https://www.allaboutcircuits.com/>

Procedure:

Only the manual of the circuits and electronics lab from birzeit university was used