



Department Of electrical and computer Engineering
ENEE2103 CIRCUITS AND ELECTRONICS LABORATORY

Experiment No.9 Prelab

Insructer: Dr. Alhareth Zyoud

Made By: Islam Jihad



ID: 1191375

TA: MR. Ismail Abualia



Date: 7/Nov/2021

I.ZENER DIODE.


Part1:

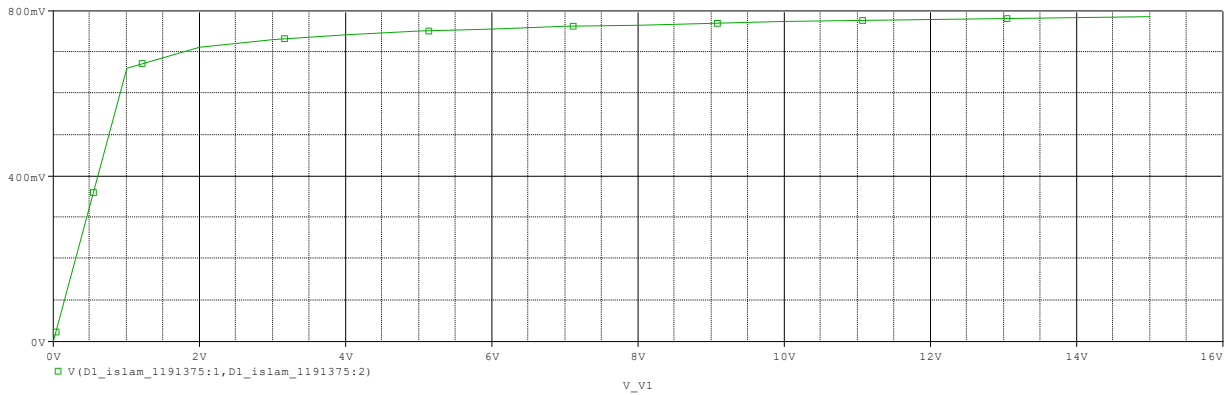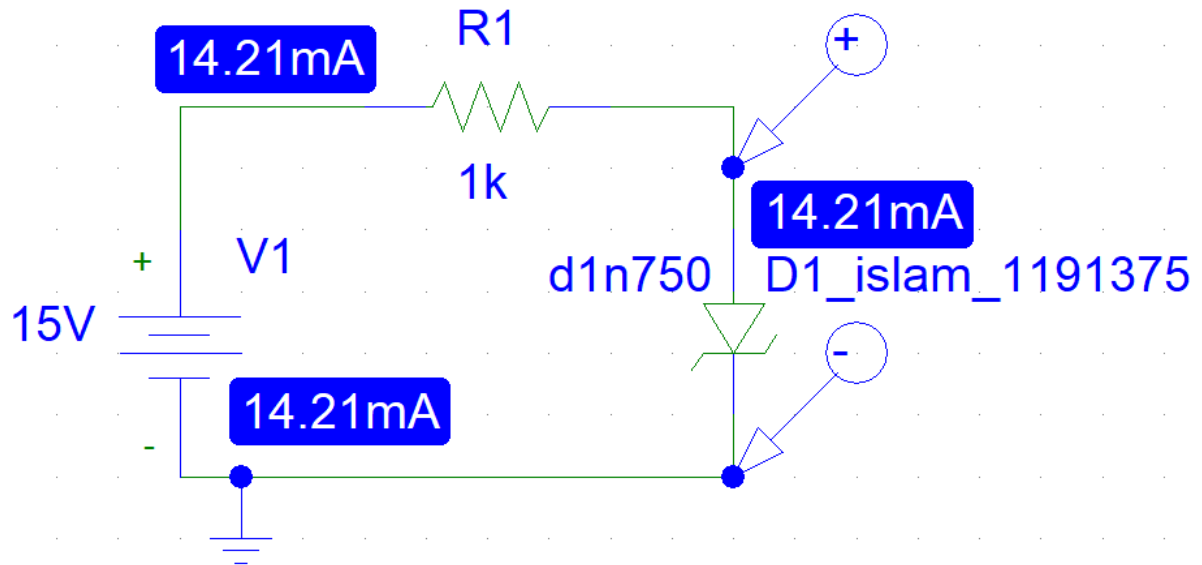


Part2:

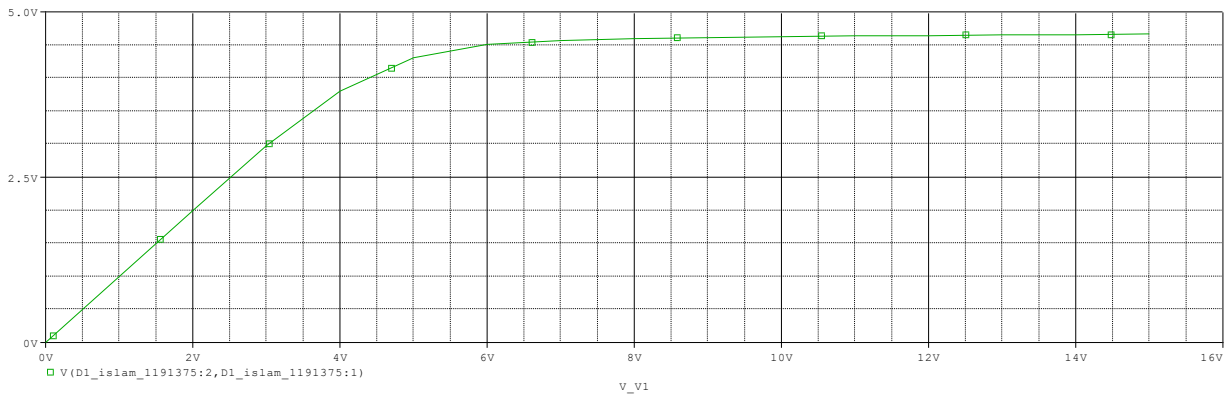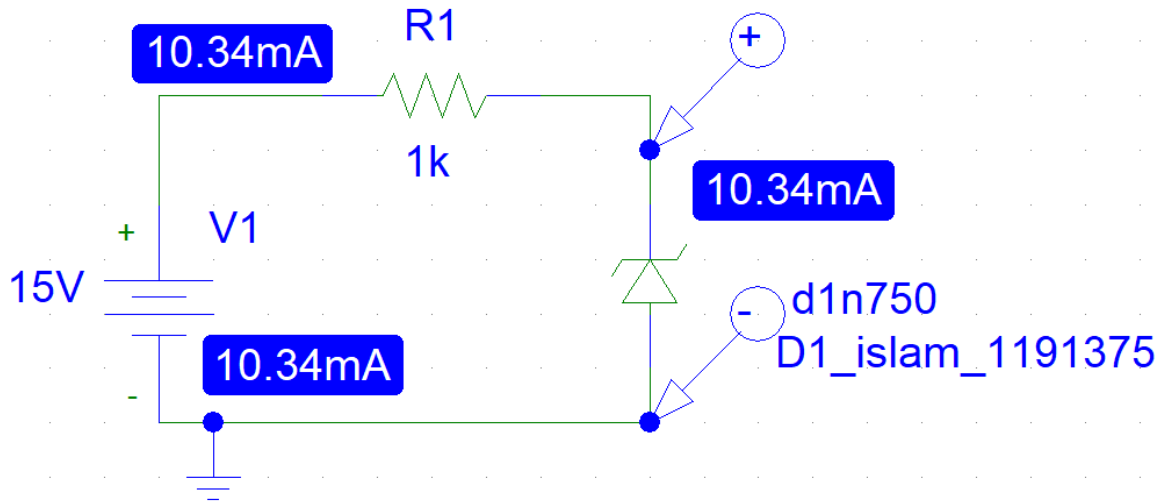



Part3:

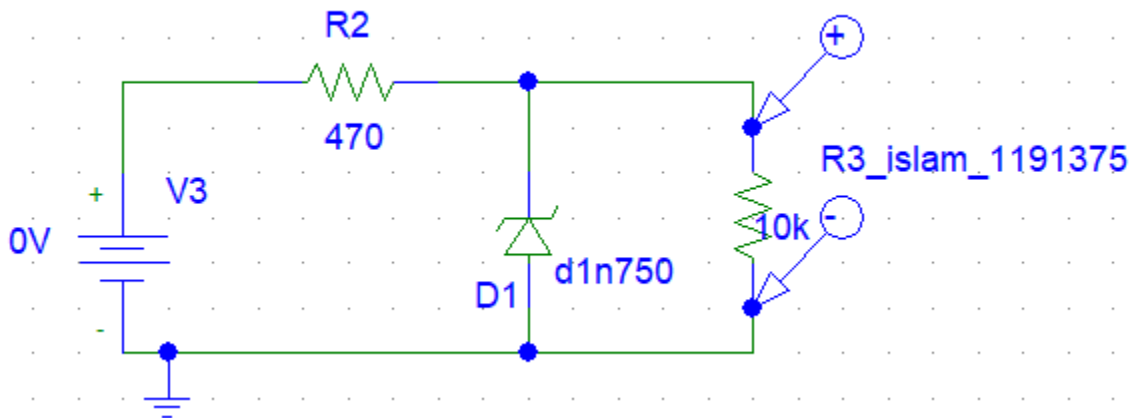


With dc sweep and $V_{in}=0$

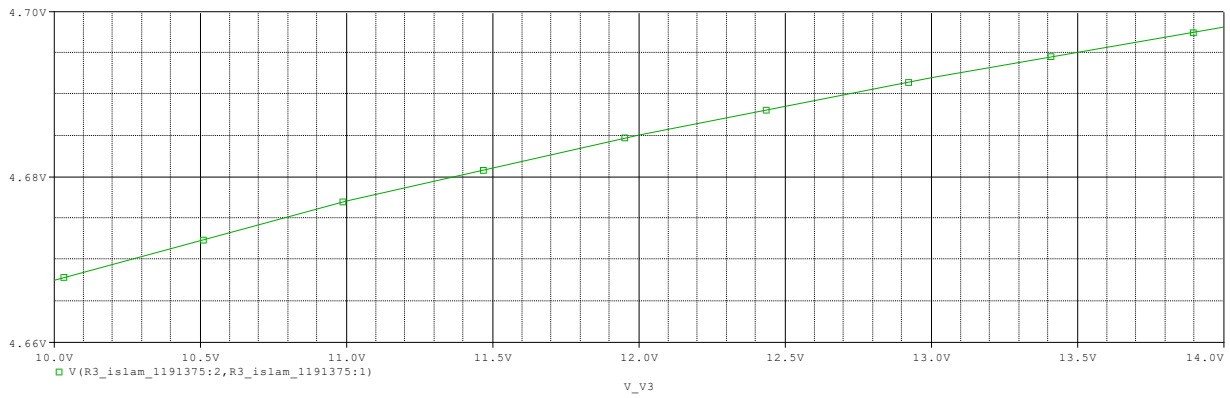

$V_{dc}=10V$ and sweep the resistance

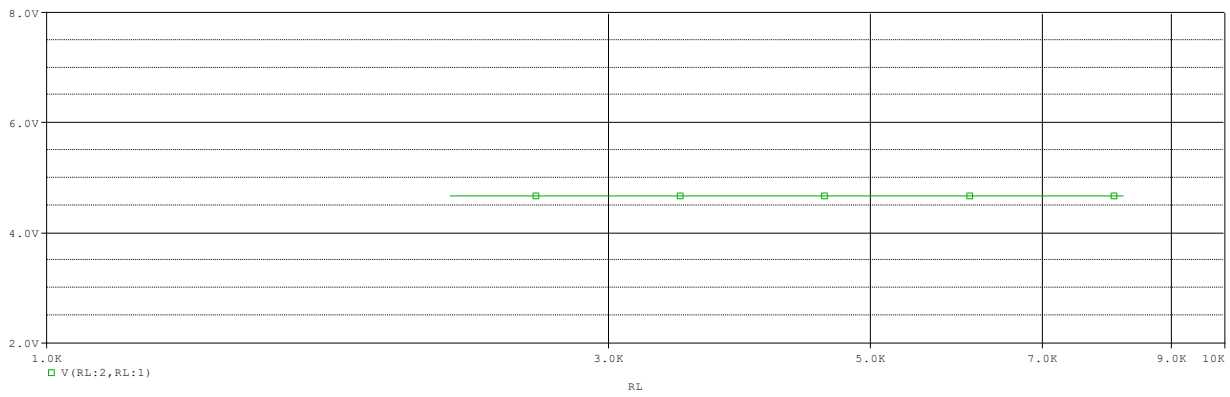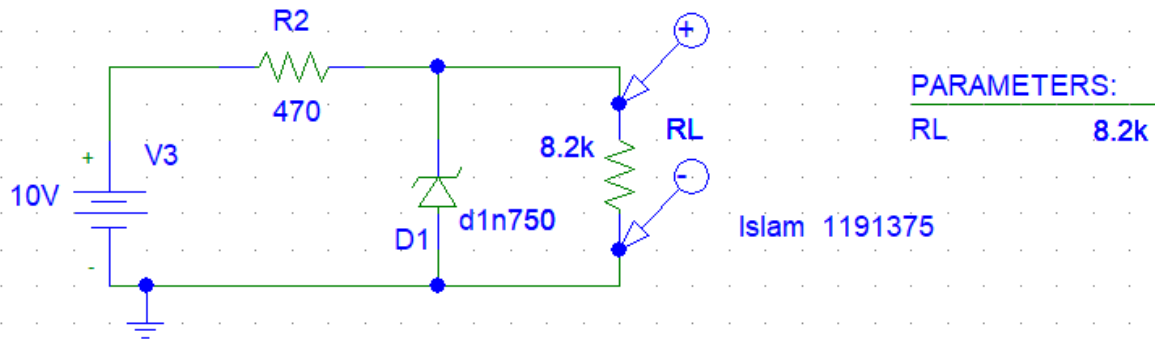

II. THE VOLTAGE REGULATED POWER SUPPLY.

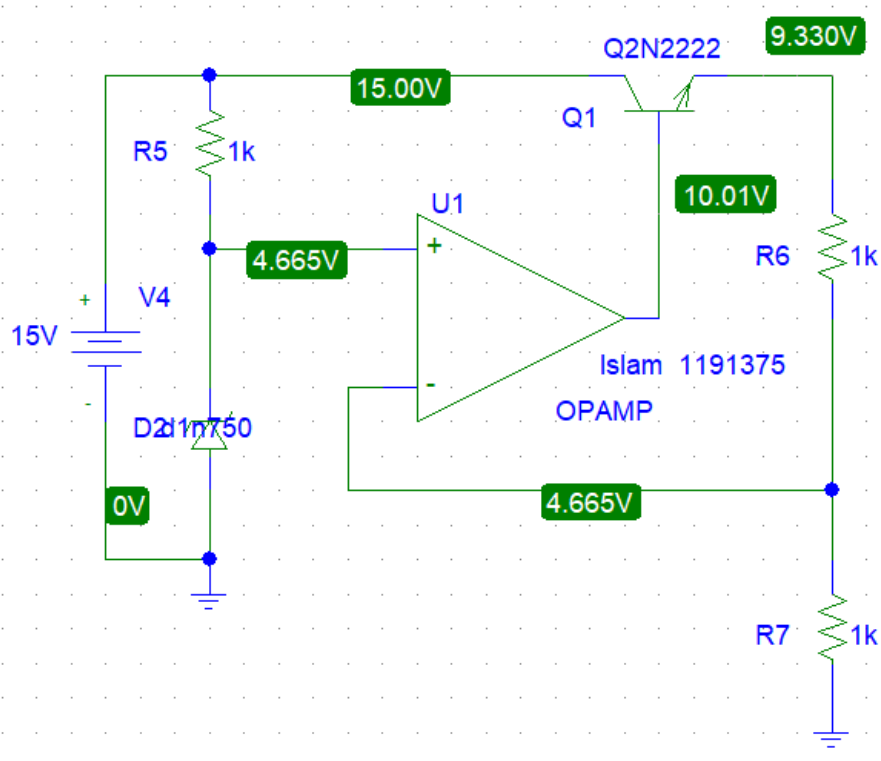

$V_{OUT}=9.33V$

$V_{IN}=15V$

$V_Z=4.665V$

$V_{OUT}= 2*V_Z$

When I added the load resistor to the output the output was=9.3295V

And the current output was=9.33mA

3.



A. for $R=680$ I got the same voltage for $r=1k$ but the current was =13.72mA

B. for $R=470$ I got the same voltage for $r=1k$ but the current was =19.85mA

C. for $R=220$ I got the same voltage for $r=1k$ but the current was =42.41mA


D. for $R=100$ the PSpice can't solve it due to low resistance

4. I got the same error for small values

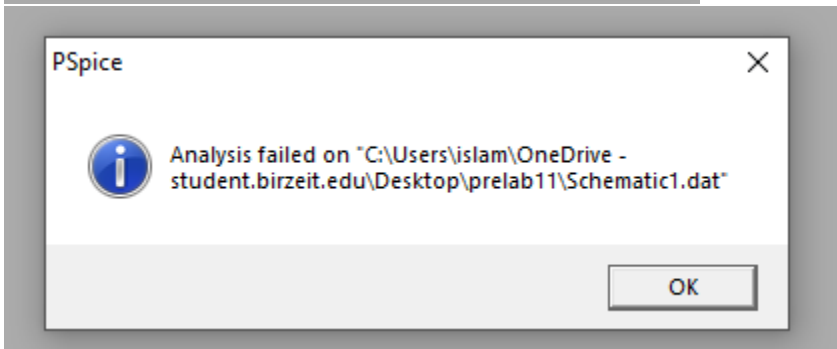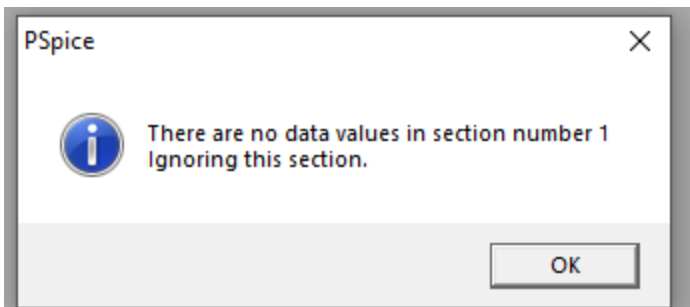

But I think it will be bigger, $V_{out} > V_z$

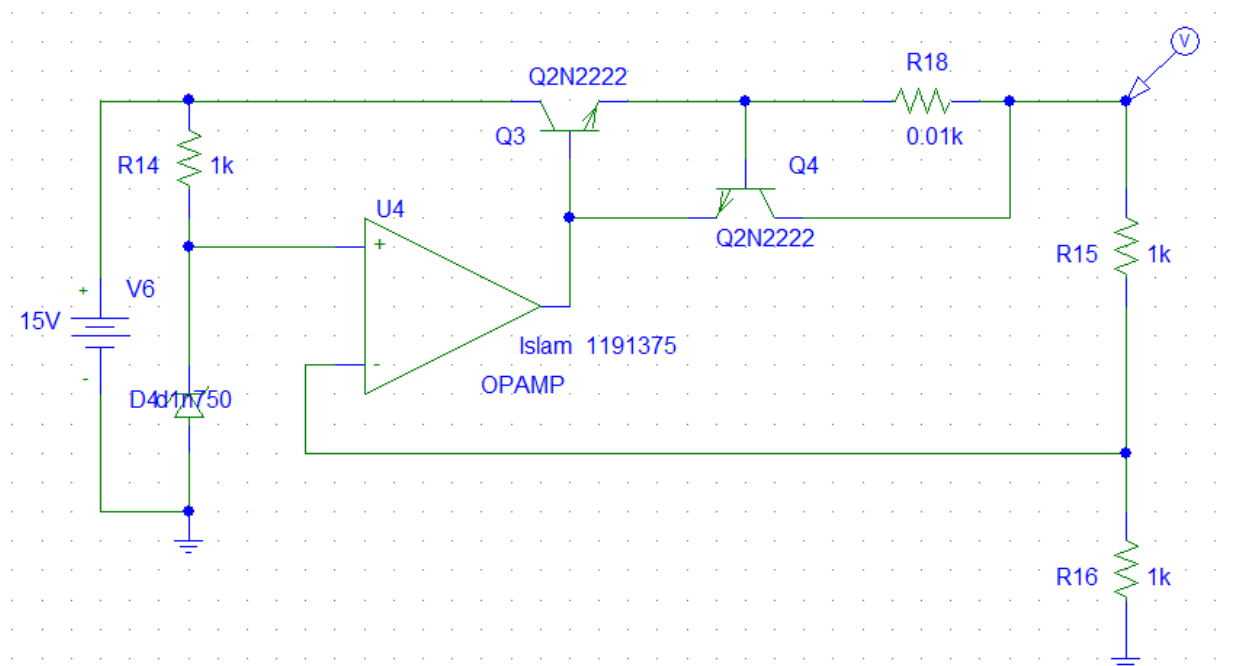5. when $R_2 = 2.2k$ the output voltage were = 6.7851V



- 7. I got the same error because of the 10ohm resistor and I can't calculate anything
- 8. the 10 ohm resistor prevent me from calculating or adding any other component

