



Department Of electrical and computer Engineering
ENEE2103 CIRCUITS AND ELECTRONICS LABORATORY

Experiment No.3 Prelab

Instructor: Dr. Alhareth Zyoud

Made By: Islam Jihad



ID: 1191375

TA: MR. Ismail Abualia

Date: 28/Nov/2021

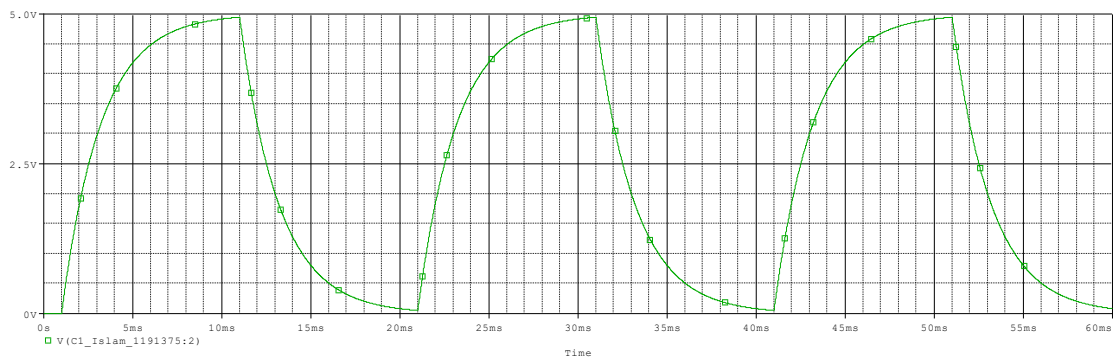
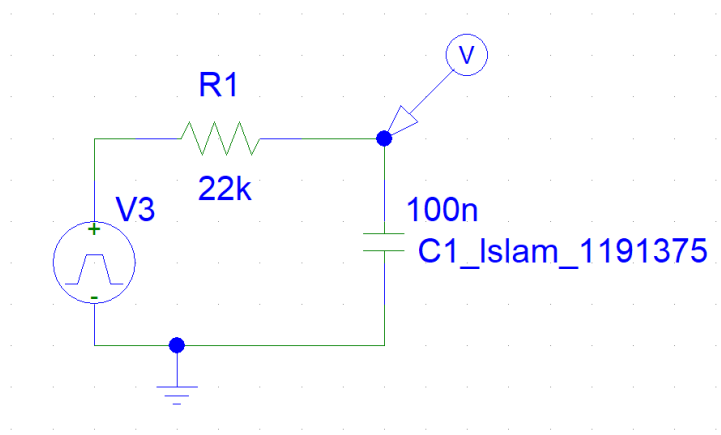
A. RC Circuit:

Constructing the following circuit and received the next simulation results:



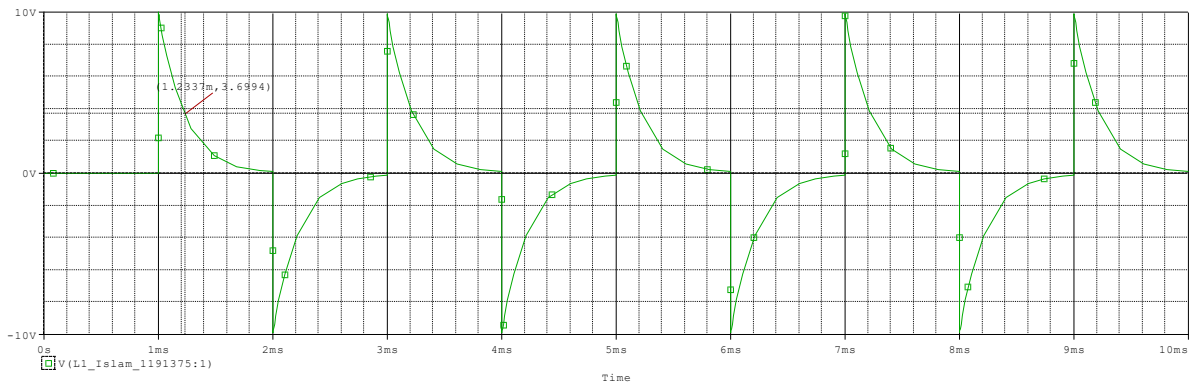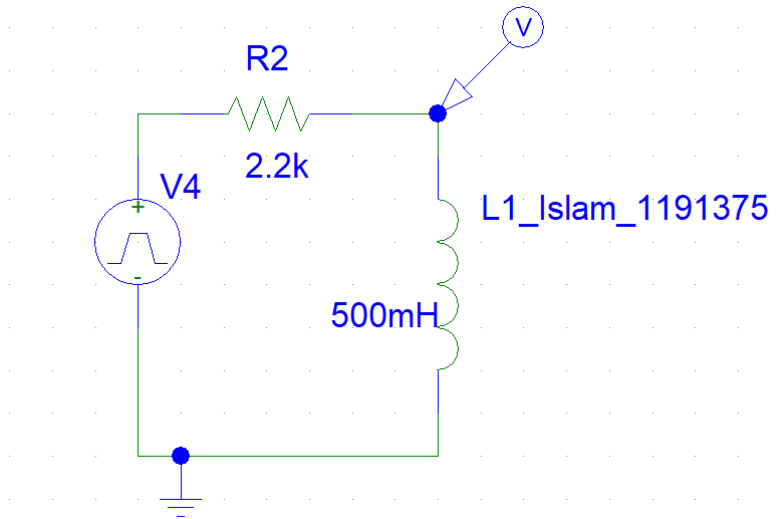
A. RL Circuit:

Constructing the following circuit and received the next simulation results:



Time constant (at $v = 3.6994V$) $\approx 1.2337mSec$ (at 0.37 of V_p for discharging)

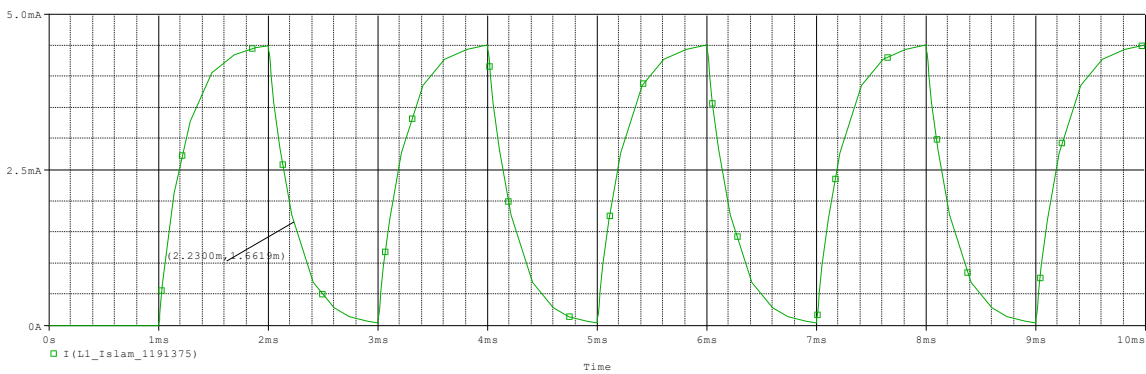the steady state values of the voltage are: 0 & $\pm 10 V$




Time constant (at $I = 1.666mA$) $\approx 2.23mSec$ (at 0.37 of I_p for discharging)


the steady state values of the current are: 0 & 4.5 mA

A. RLC Circuit:

I. Response type:

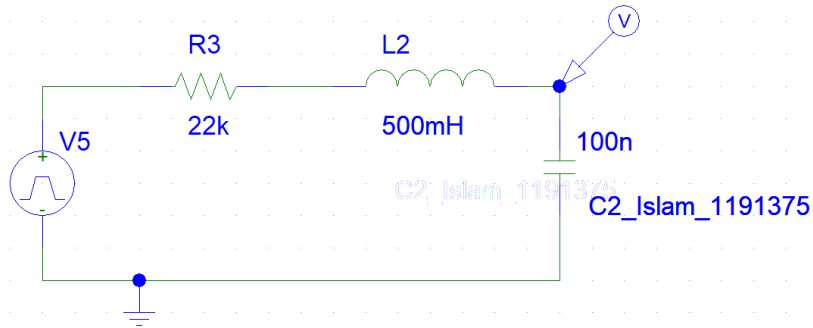

the voltage across the capacitor:

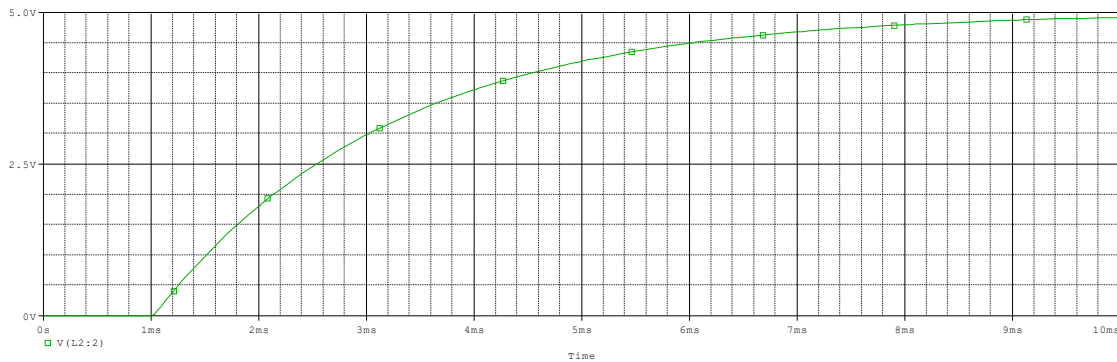


$$R = 2 \cdot \sqrt{L/C}$$


$$= 2 \cdot \sqrt{0.500/100 \times 10^{-9}}$$

$$= 4472 \text{ ohm}$$


Under damping:

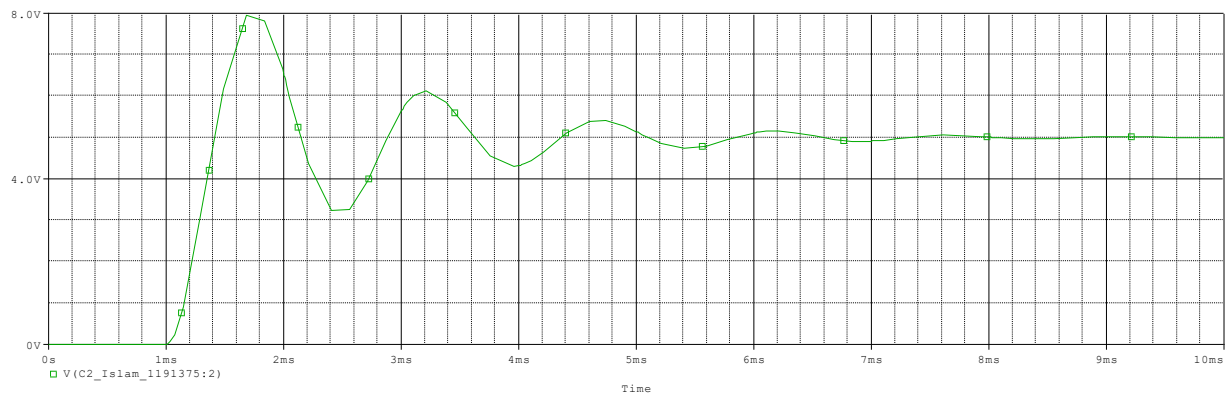


Critical damping:

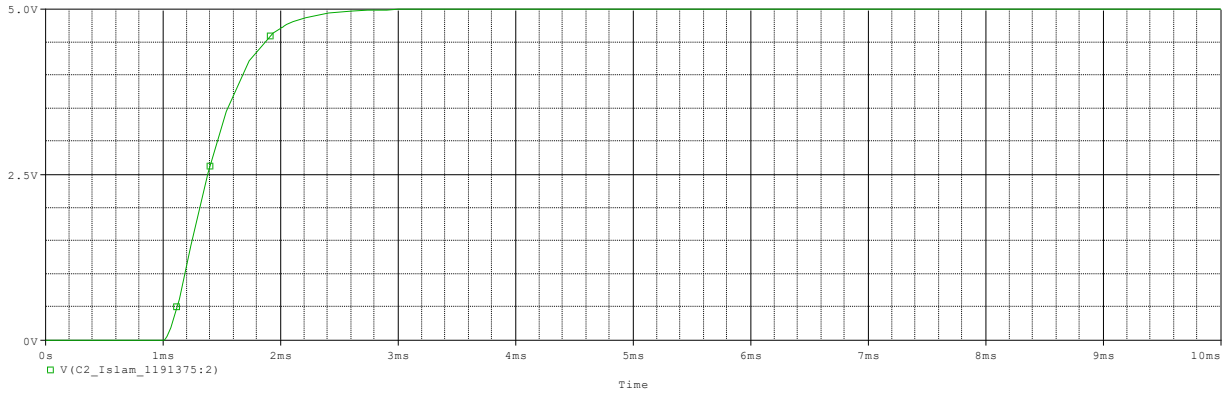

Over damping:

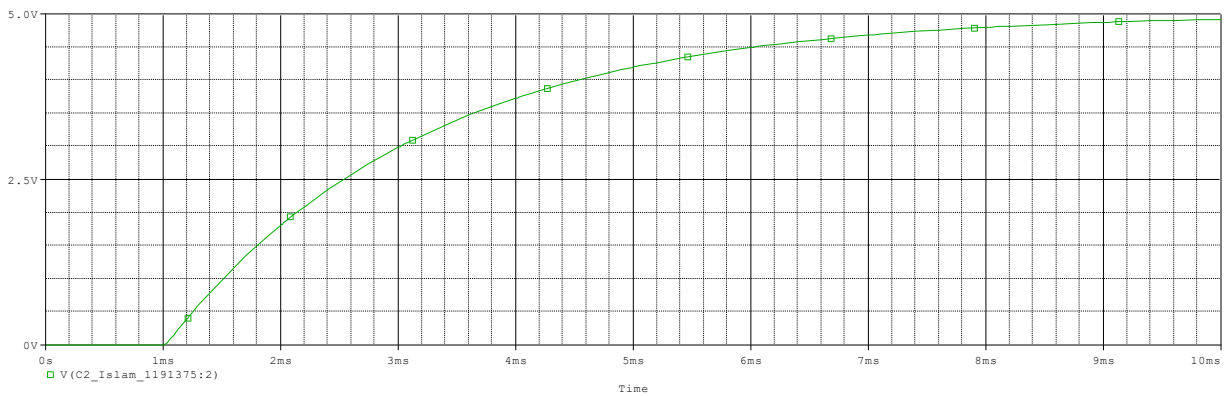

I. Response parameters:

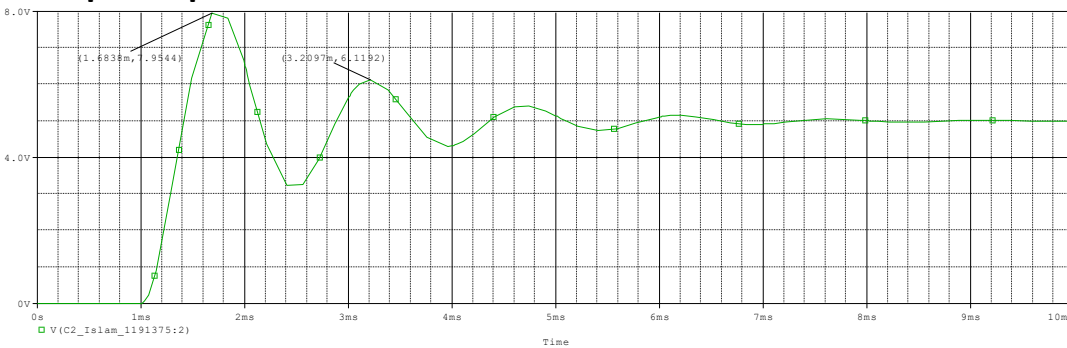

Decay time constant

$$\tau = \frac{t_b - t_a}{\ln\left(\frac{V_a - V_{o(\infty)}}{V_b - V_{o(\infty)}}\right)}$$

$$\tau = \frac{3.2097 - 1.6838}{\ln\left(\frac{7.9544 - 4.93}{6.1192 - 4.93}\right)} = \frac{1.5259}{\ln(2.5432)} = 1.635$$

