



Department Of electrical and computer Engineering
ENEE2103 CIRCUITS AND ELECTRONICS LABORATORY

Experiment No.6 Prelab

Insructer: Dr. Alhareth Zyoud

Made By: Islam Jihad

ID: 1191375




TA: MR. Ismail Abualia

Date: 28/Nov/2021



1. Part A (Impedance):

1.1 Resistive circuit



Frequency = 1 kHz

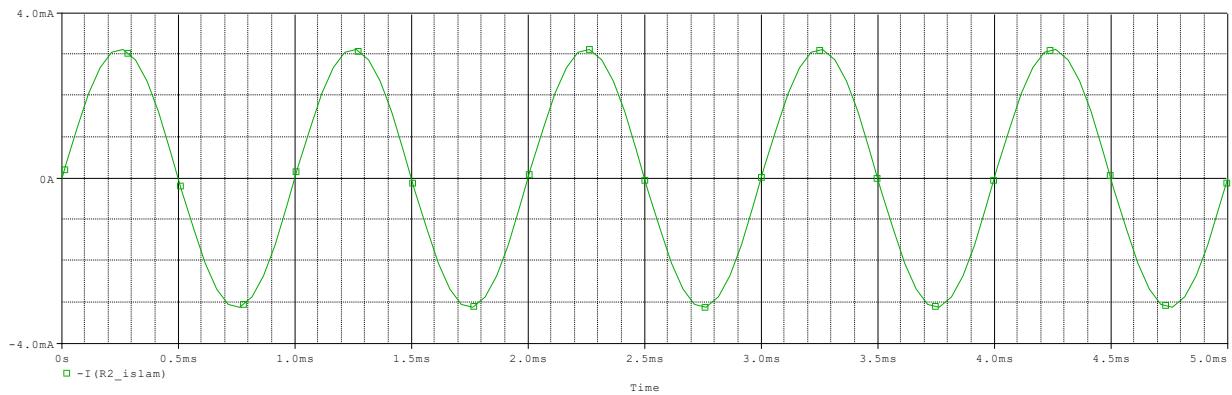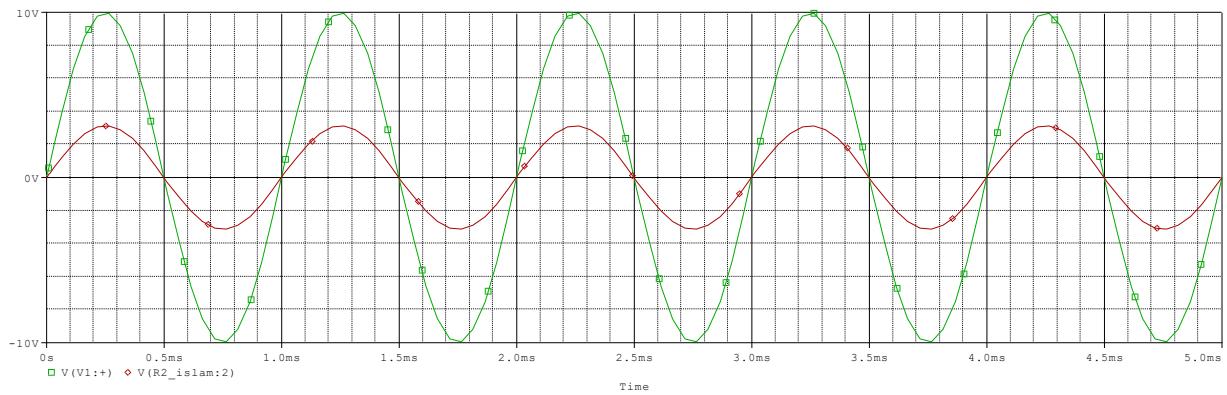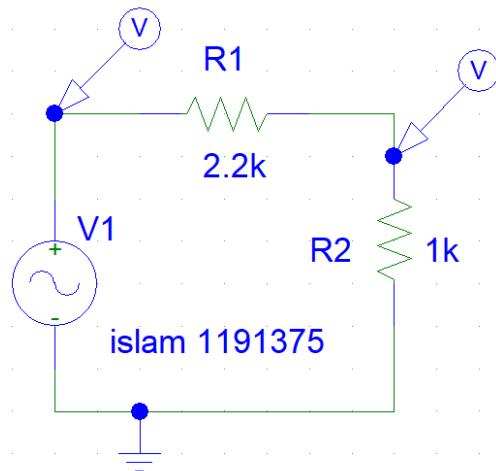


1.1.2 Frequency = 500 Hz

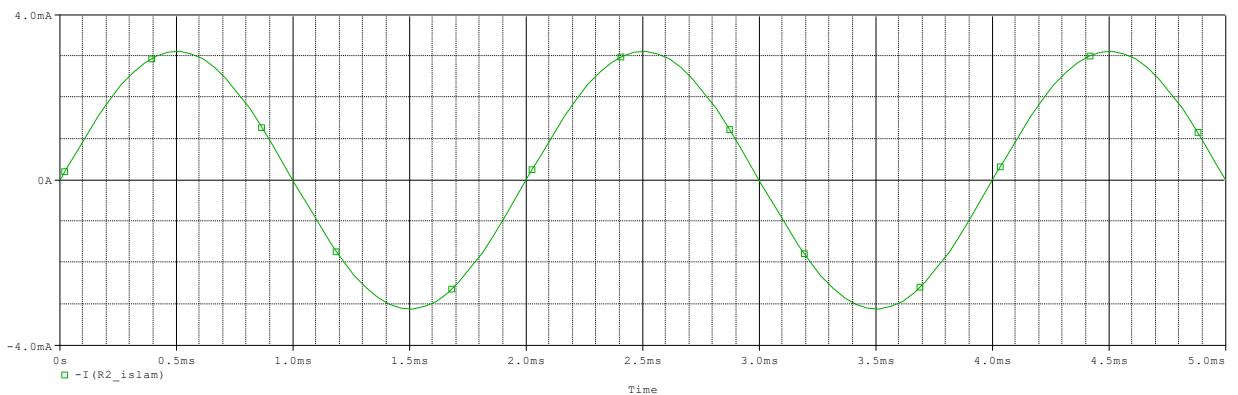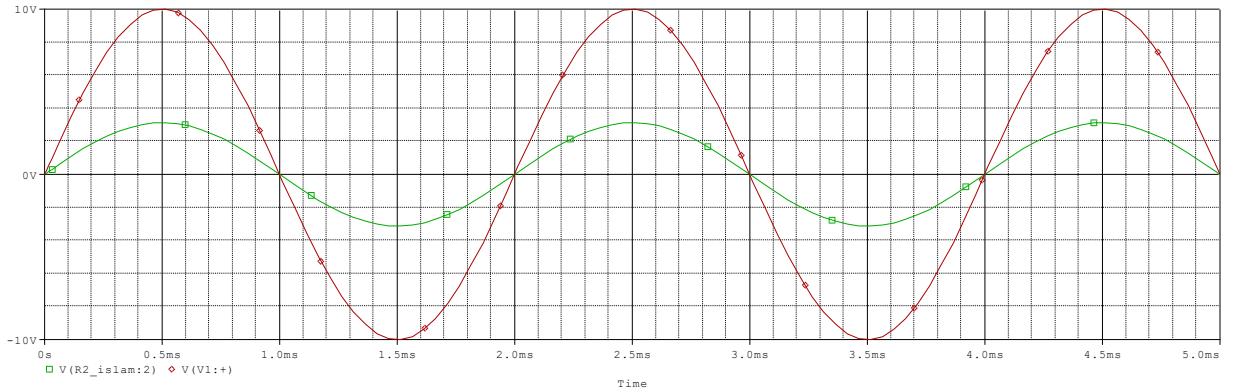



1.1.3 Frequency = 1500 Hz

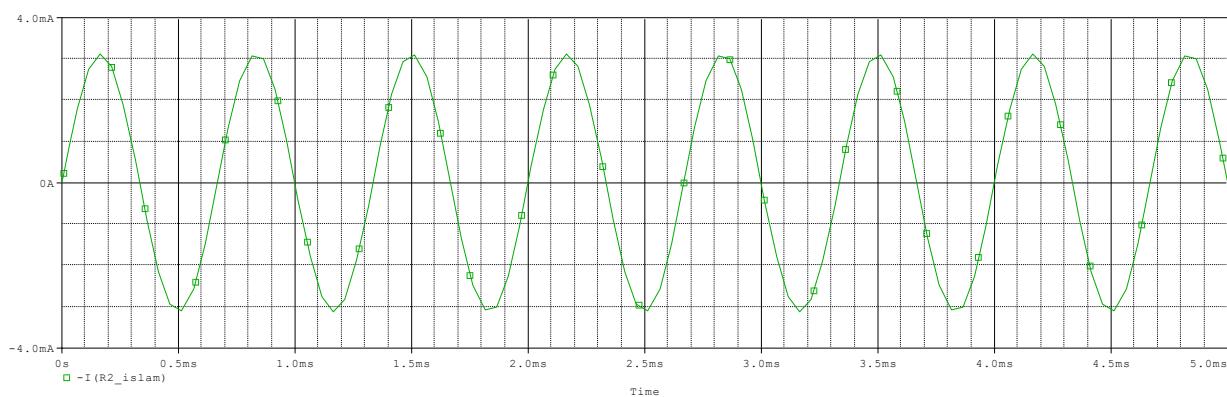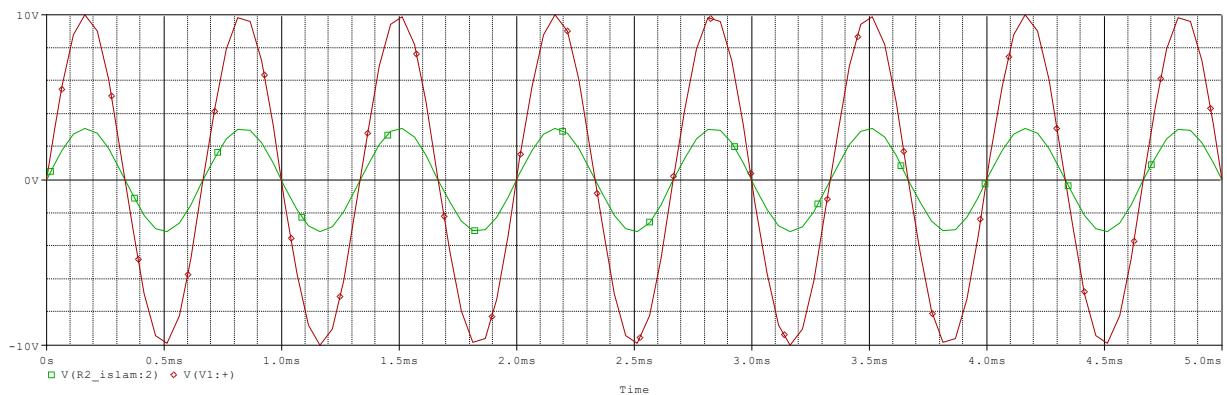


1.2 RC circuit

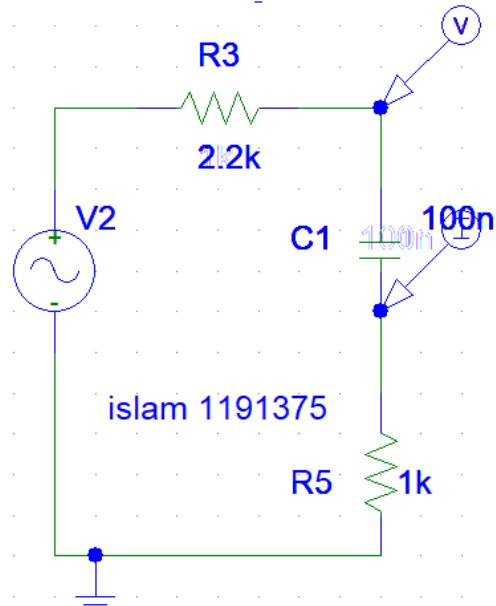


1.2.1 Frequency = 1000 Hz

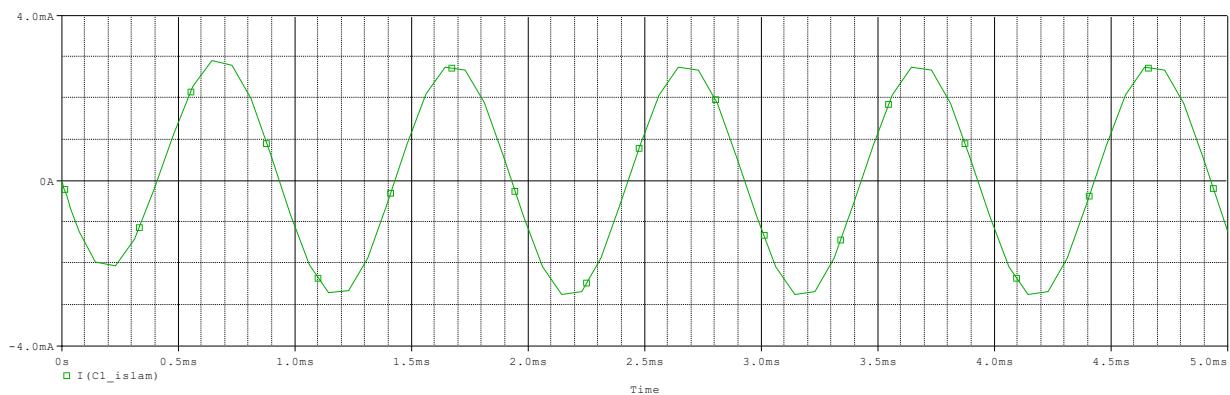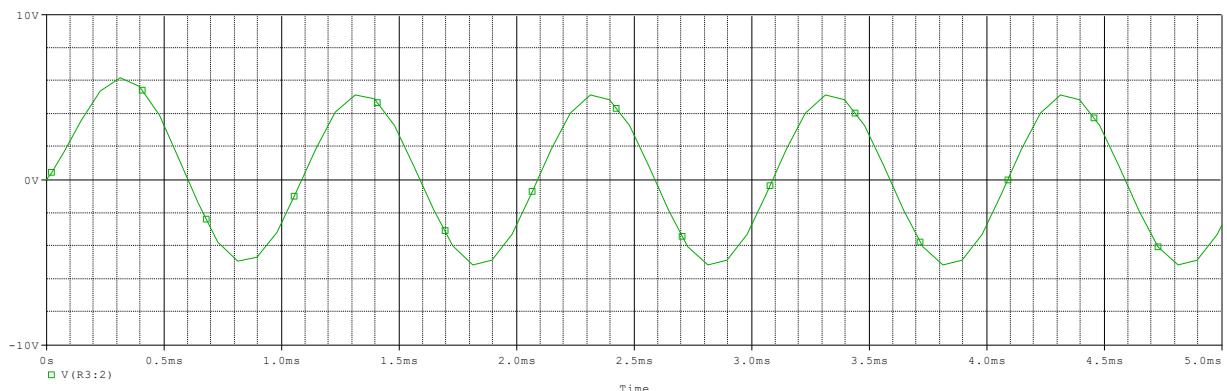


1.2.2 Frequency = 500 Hz

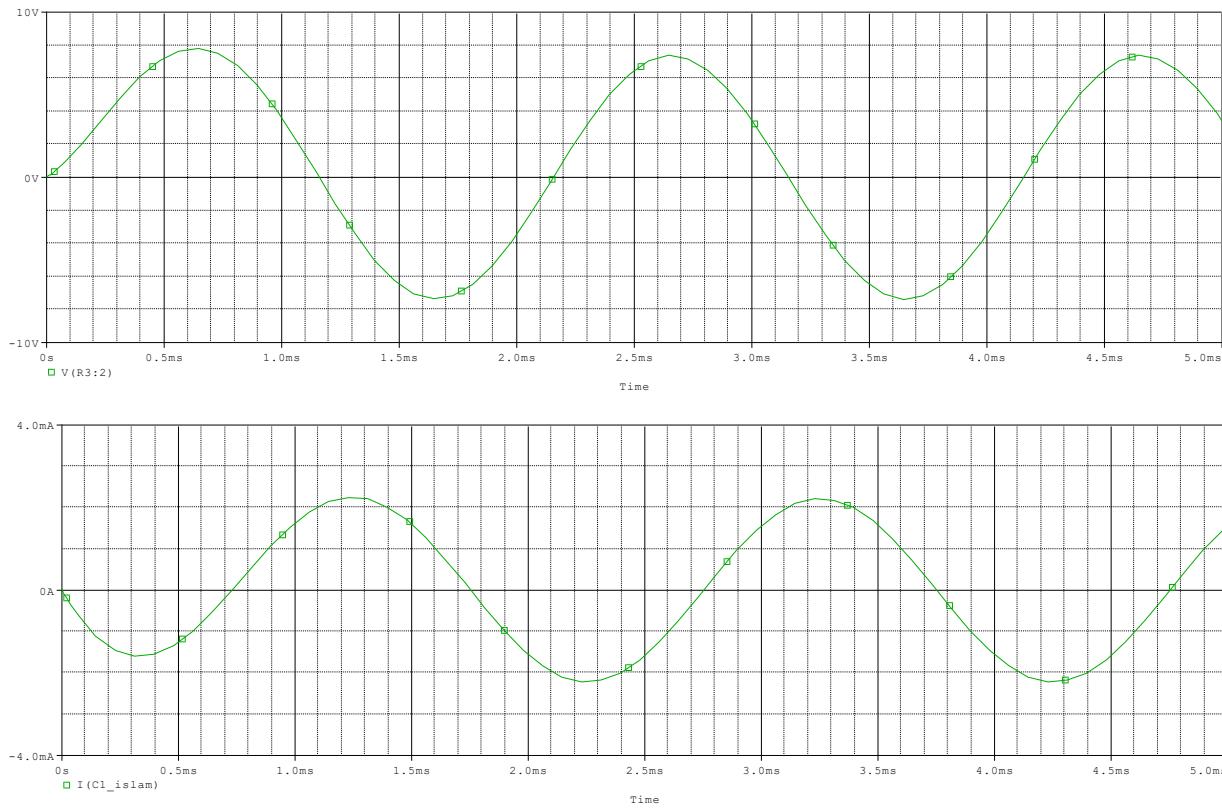



1.2.3 Frequency = 1500 Hz

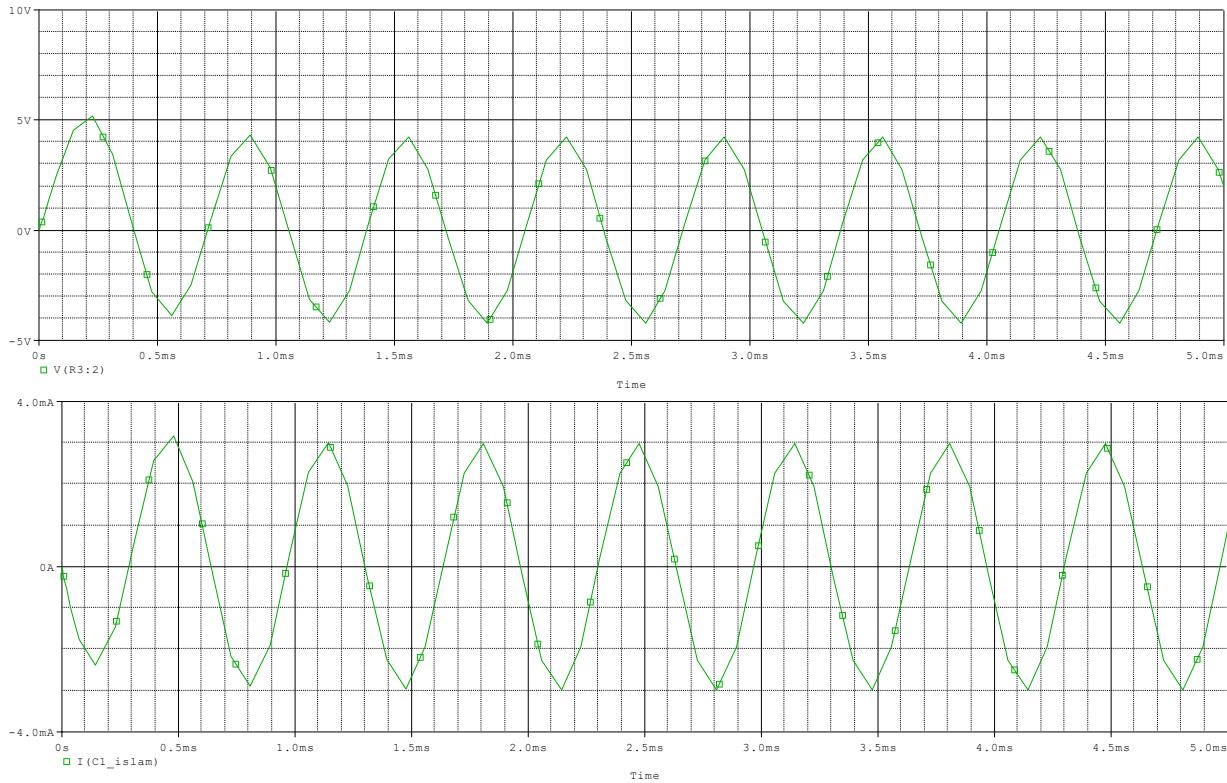


1.3 RL circuit

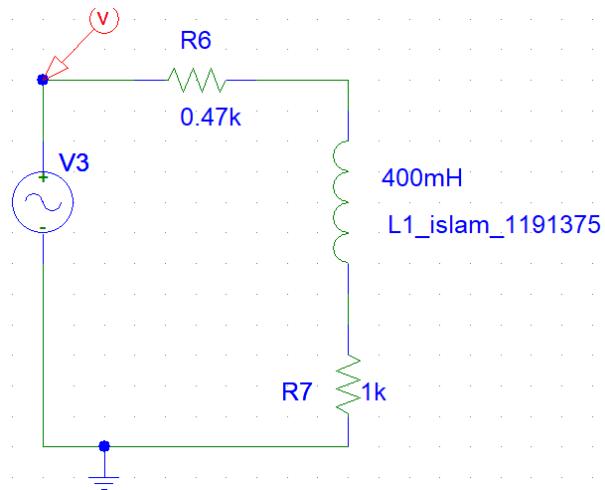


1.3.1 Frequency = 1000 Hz

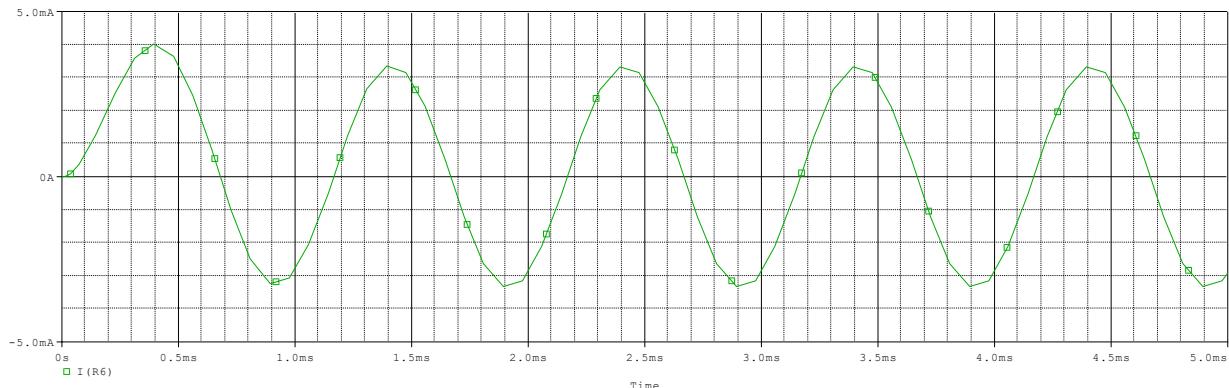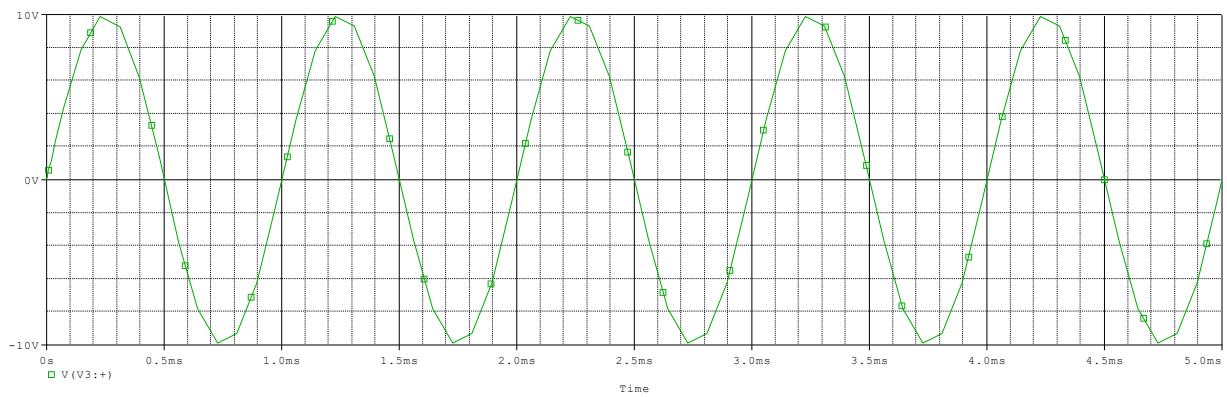


1.3.2 Frequency = 500 Hz

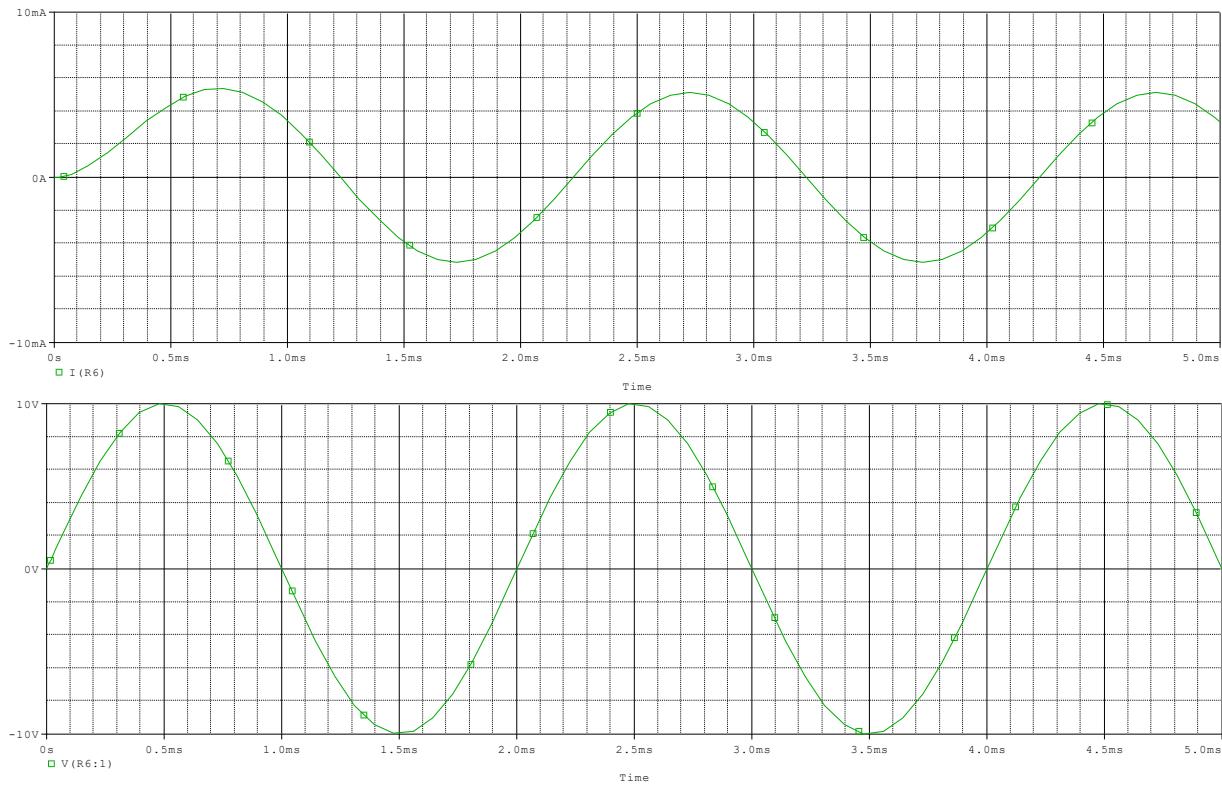



1.3.3 Frequency = 1500 Hz

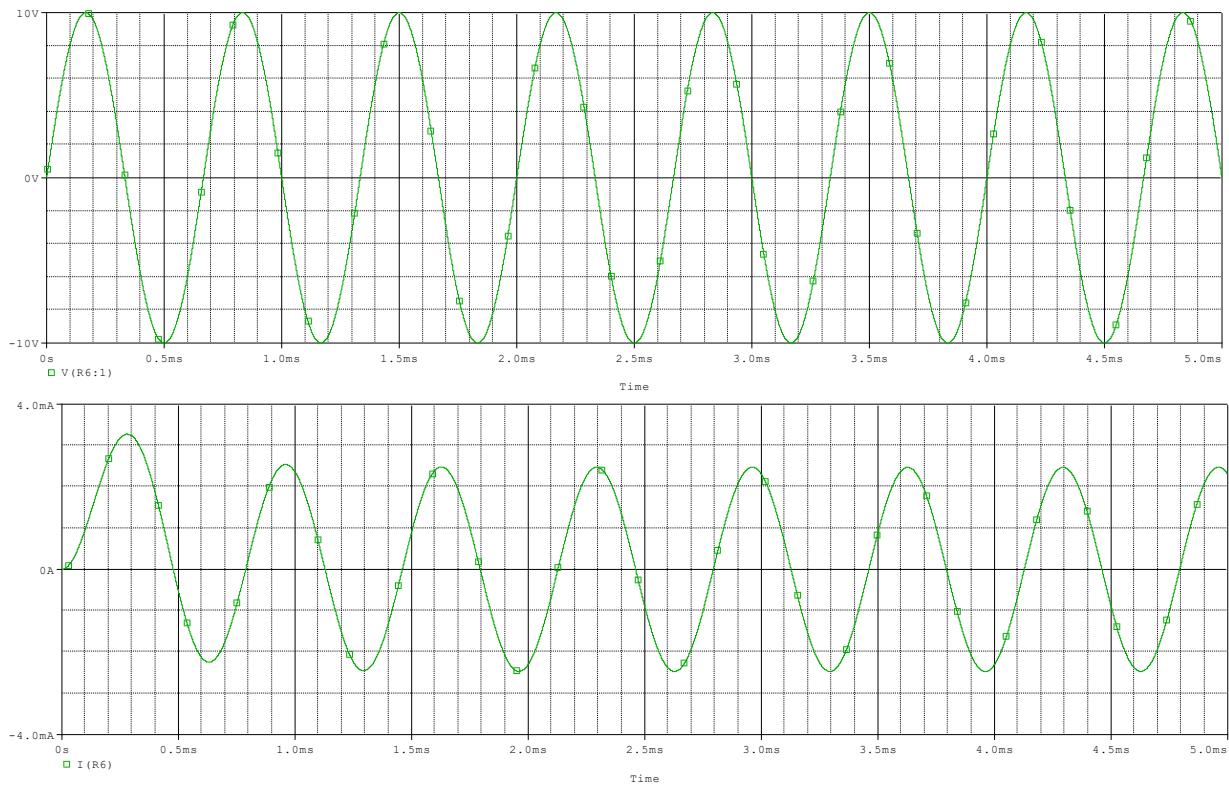

1.4 Capacitive and inductive behavior

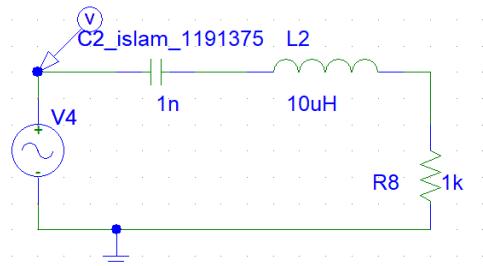



$F=1KHZ$

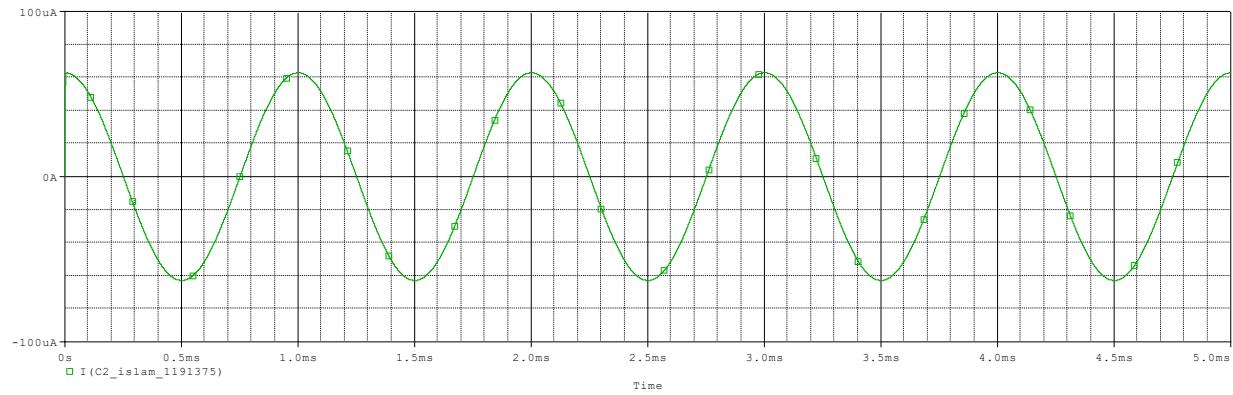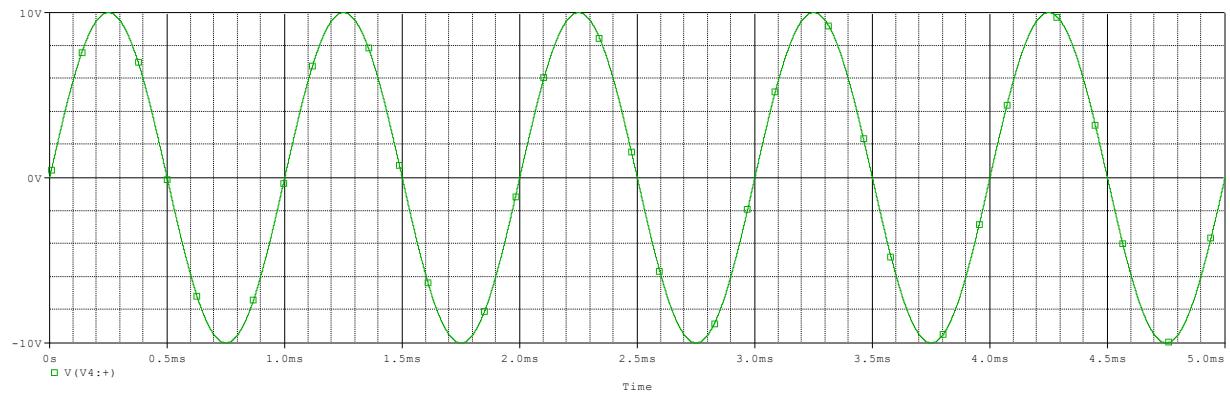



$F = F_o$ (Resonance Frequency):

5033

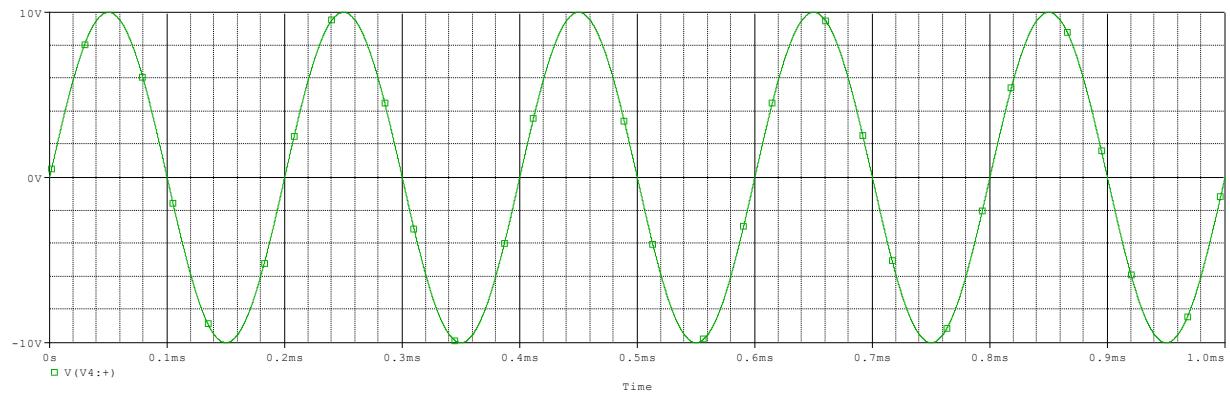


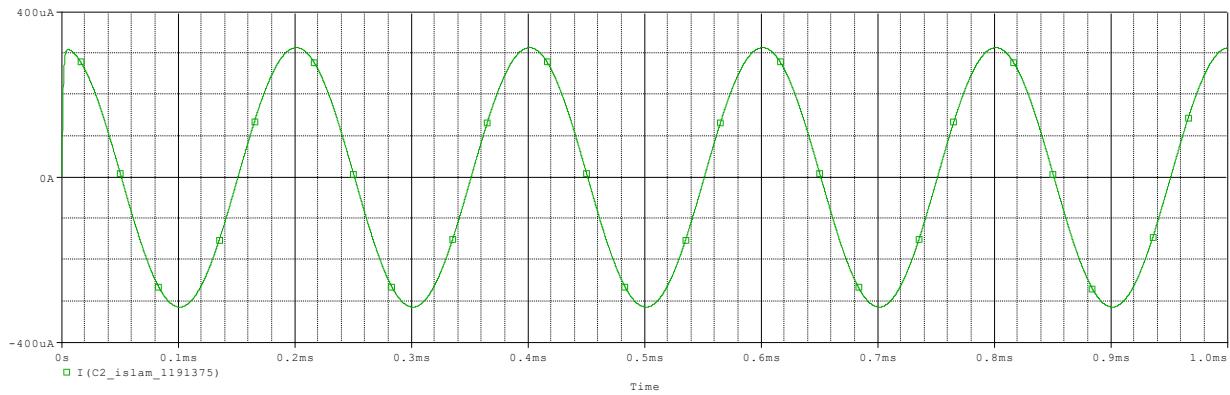


$$F = 2Fo$$

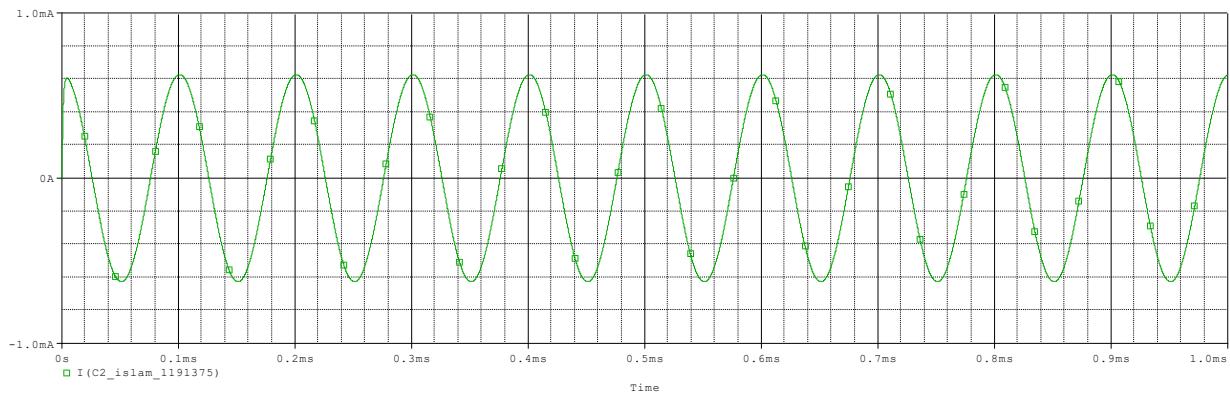
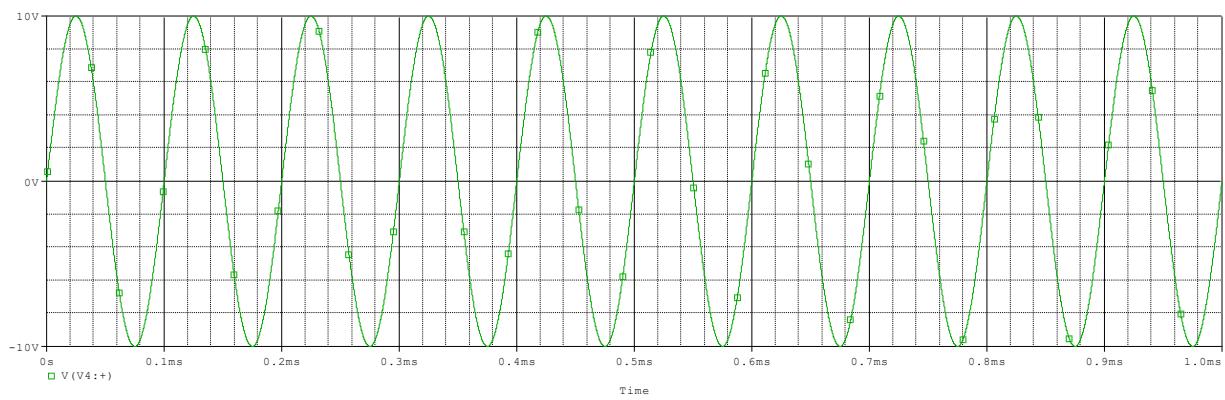


1.4.1 Double the value of the capacitor:

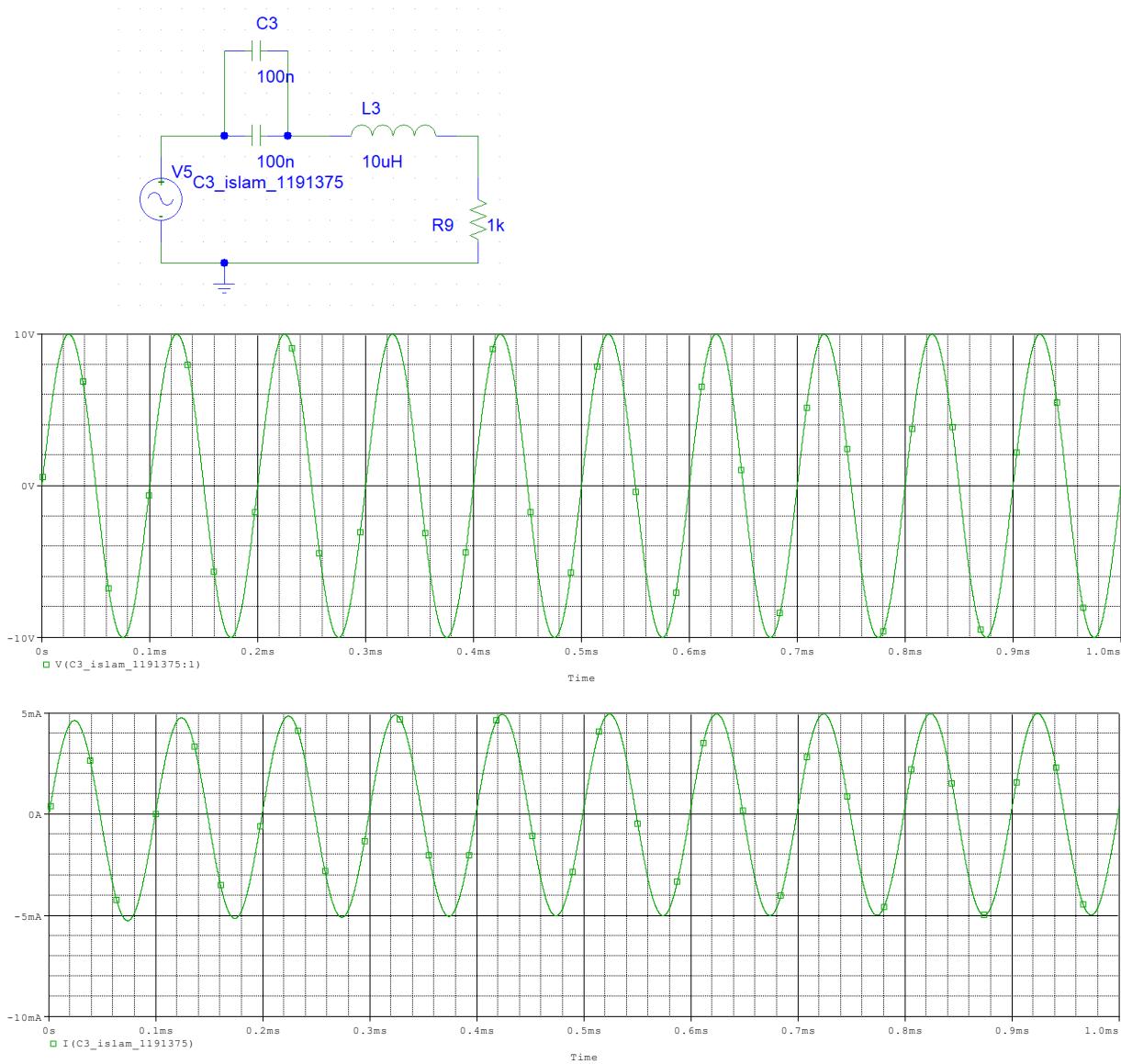


1.4.2 Double the value of the inductor

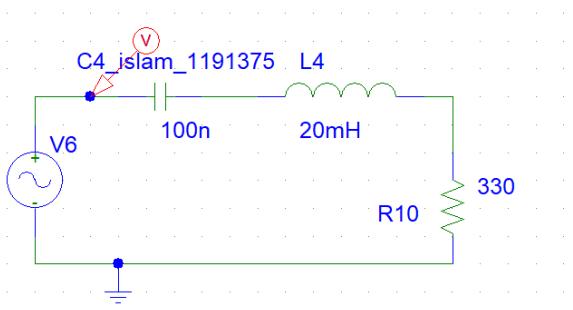


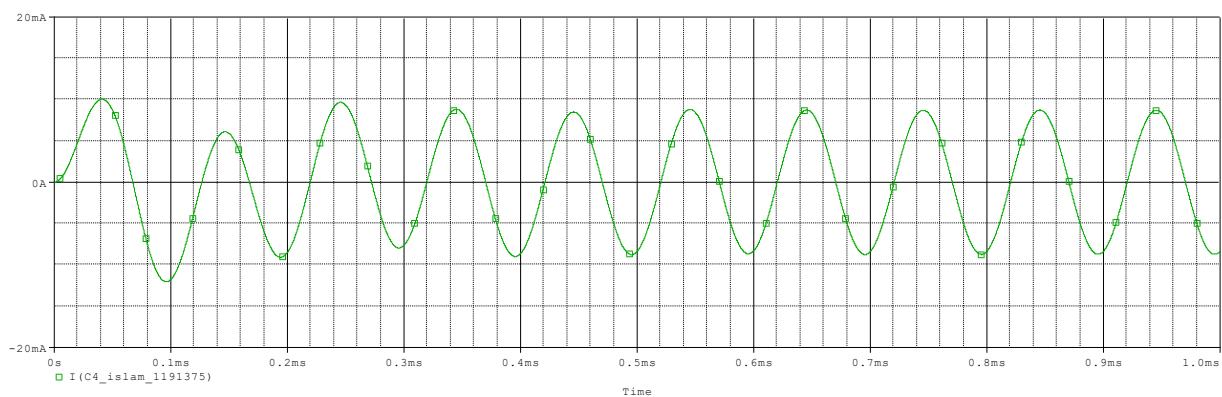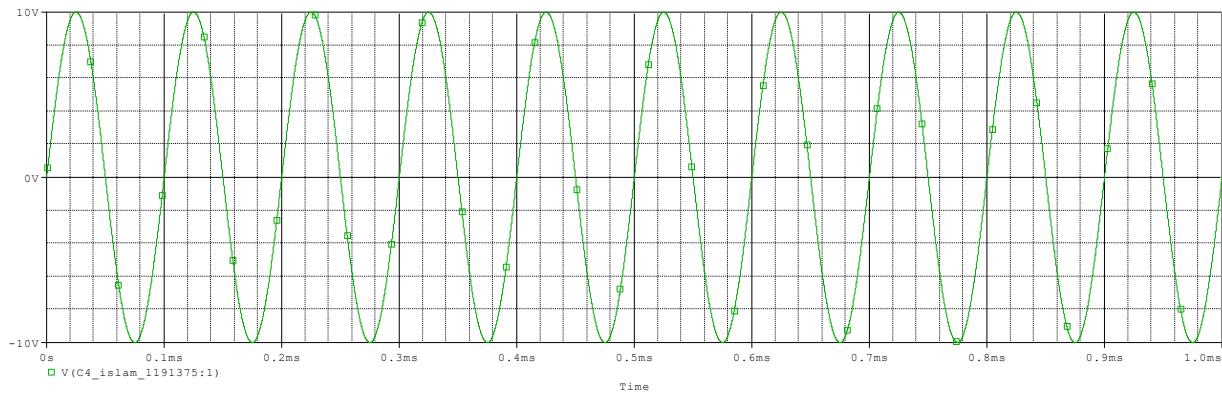



1.5 Sinusoidal steady state power

Plot the voltage and current across R2

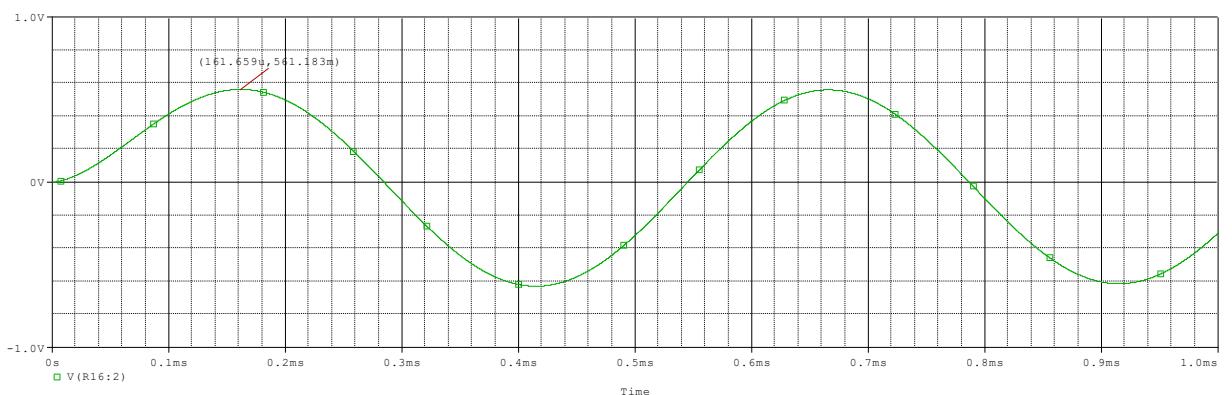


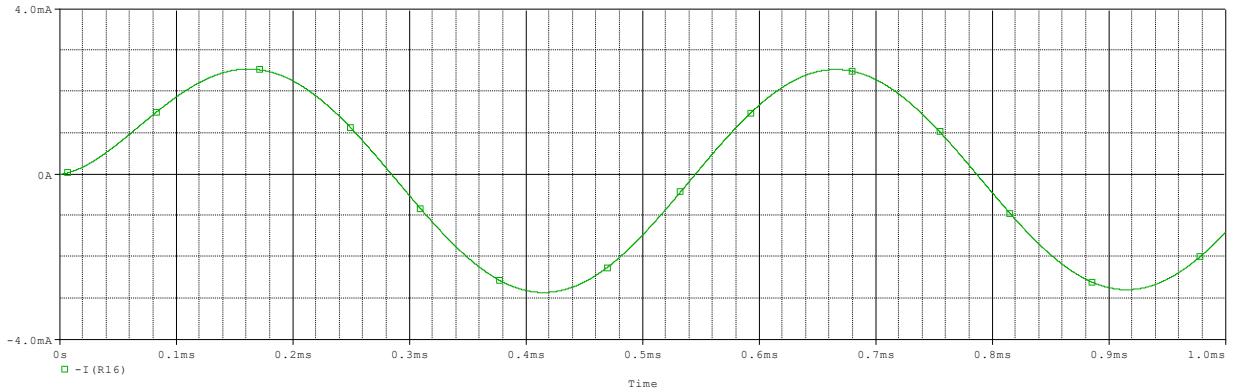


Plot Vs and Is and measure phase shift

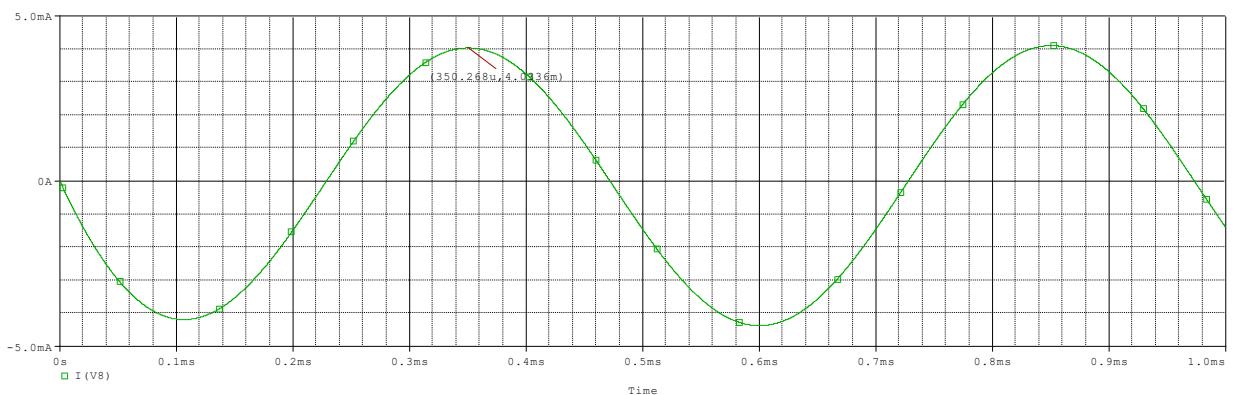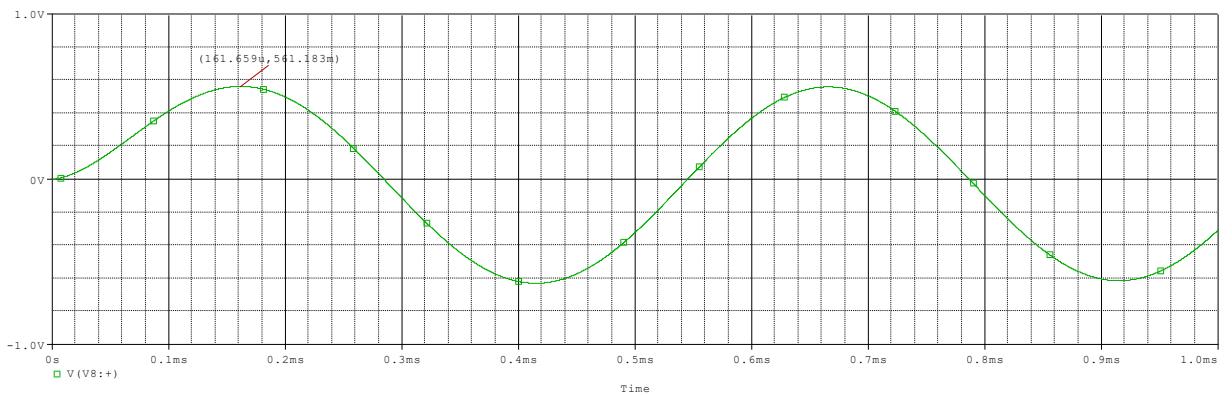


$$\text{Phase shift} = 350.2\mu - 161.6\mu = 188.6\mu \times 360 / 0.5 = 33948$$


Plot V_c and I_c and measure phase shift

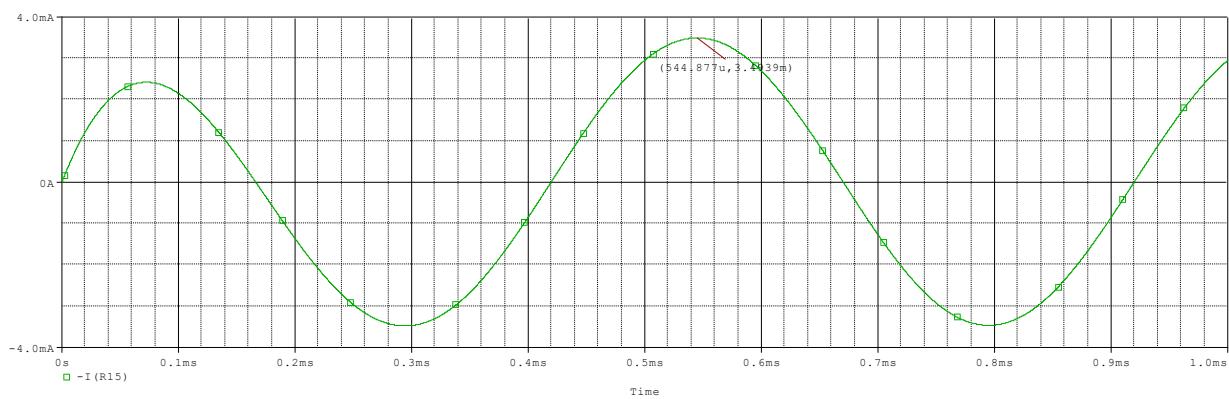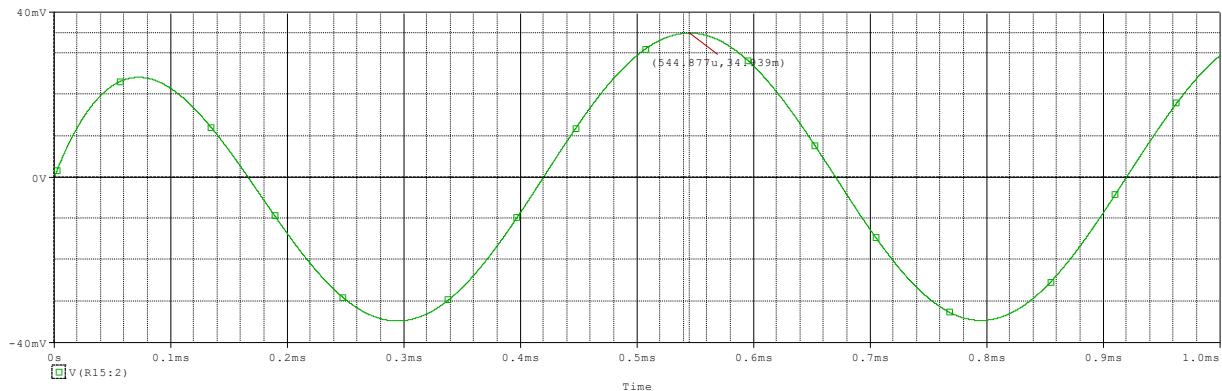

Phase shift= zero as the change in time is zero

Plot VL and IL and measure phase shift

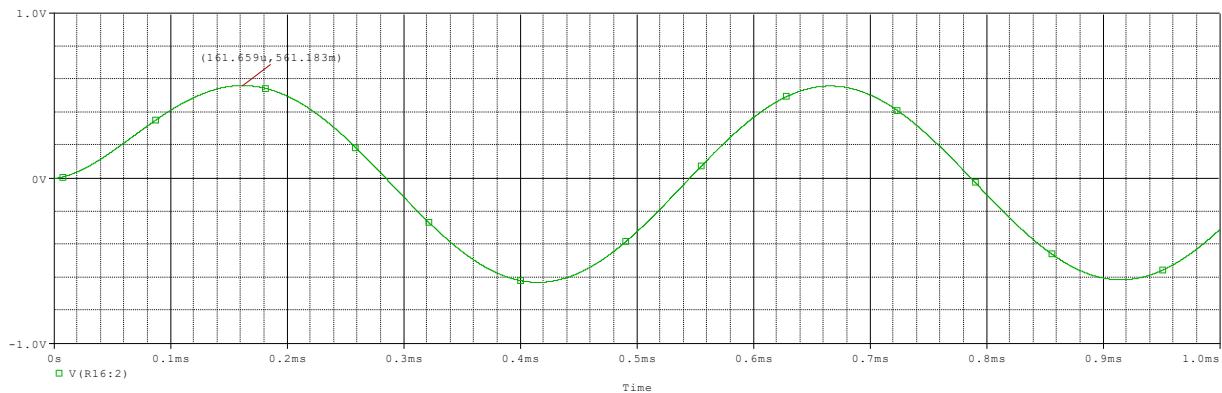

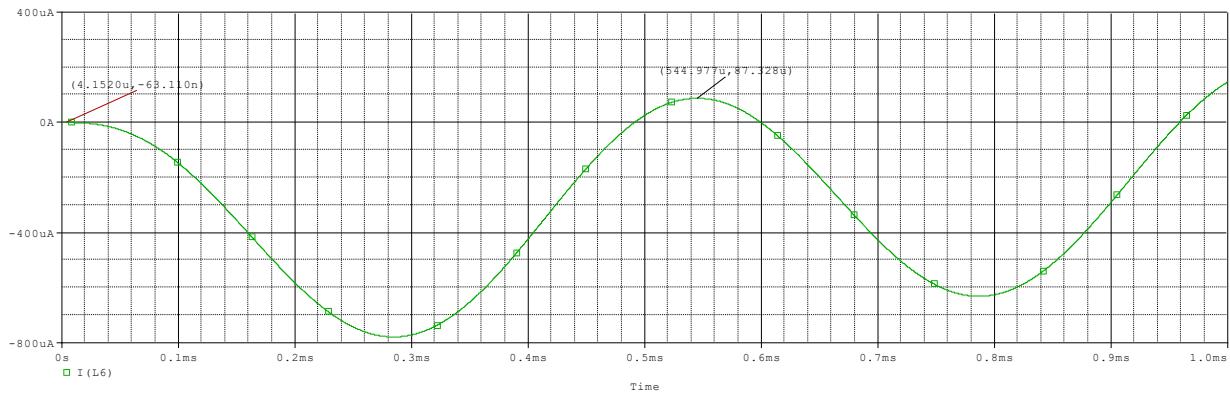


$$\text{Phase shift} = (161.65 - 4.152) * 360 / 0.5$$

$$= 157.498 * 360 / 0.5 = 113,398.56$$

Must be = 87

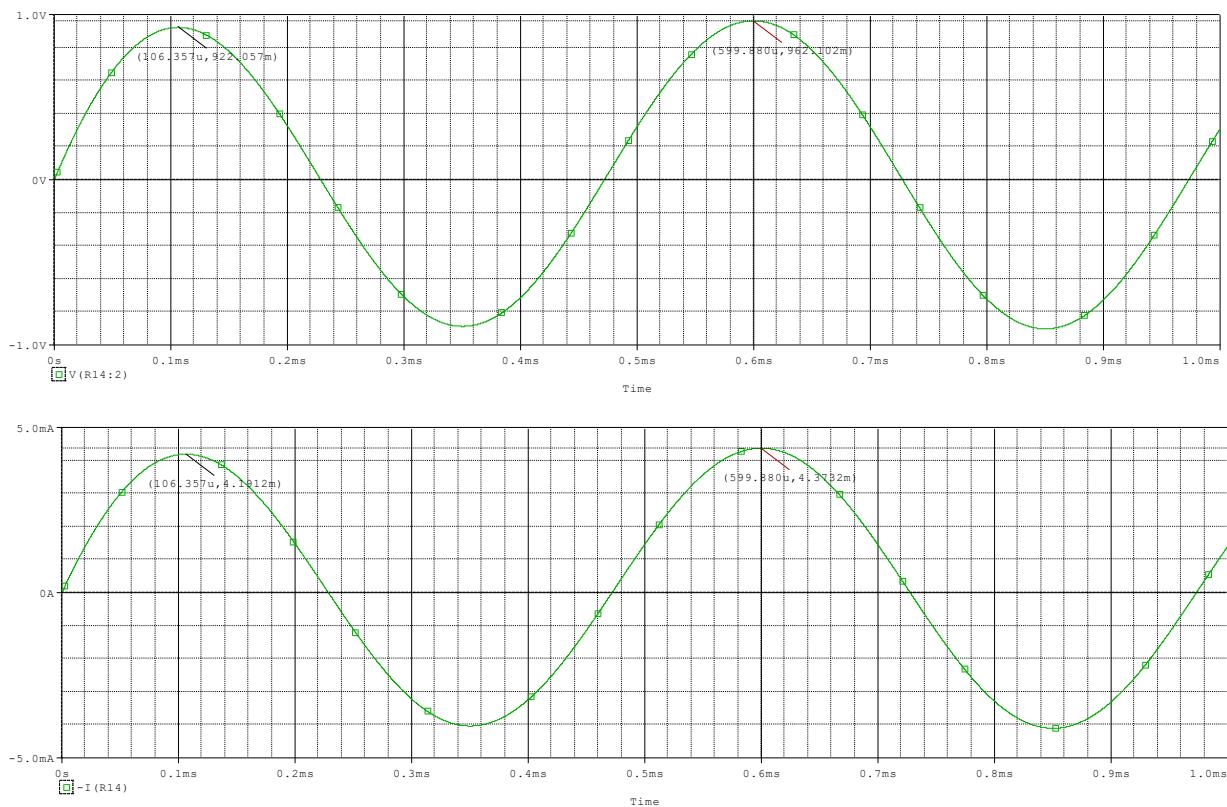Plot voltage across R1 and Is and measure phase shift



Phase shift is almost zero