



Department Of electrical and computer Engineering  
ENEE2103 CIRCUITS AND ELECTRONICS LABORATORY

Experiment No.5 Prelab

Insructer: Dr. Alhareth Zyoud

Made By: Islam Jihad


ID: 1191375

TA: MR. Ismail Abualia


Date: 4/12/2021

**A. Passive filters:**


**I. First order circuits:**

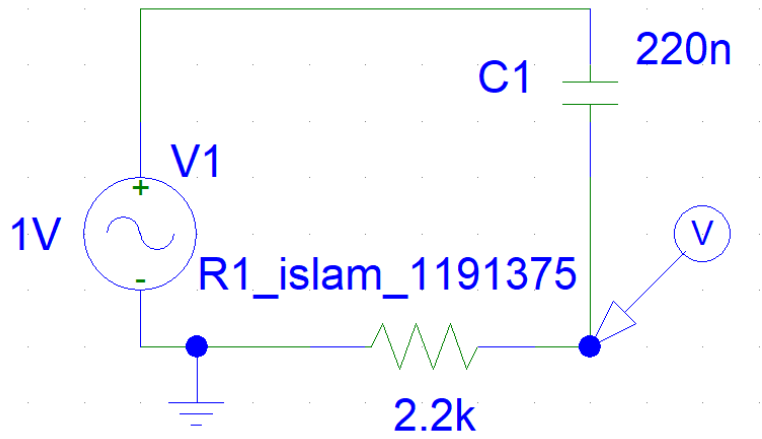


3.

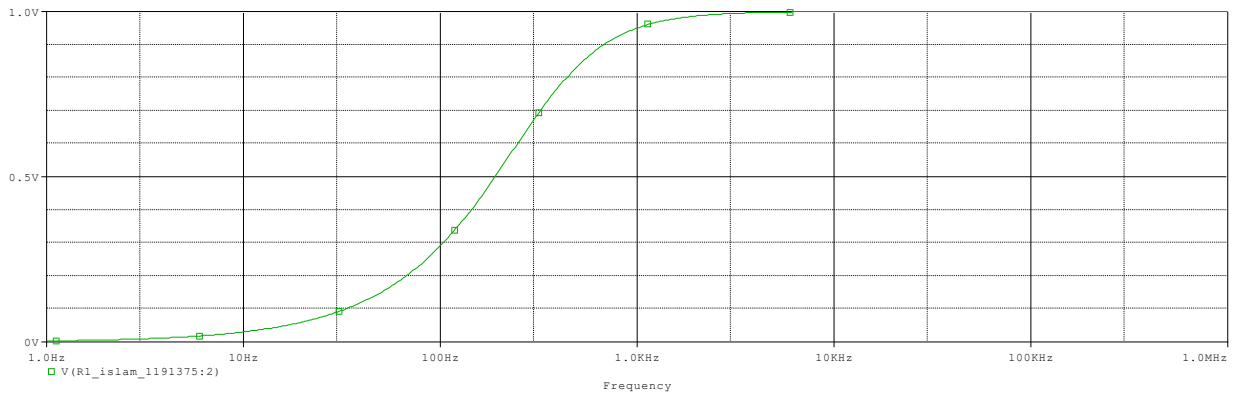


4.

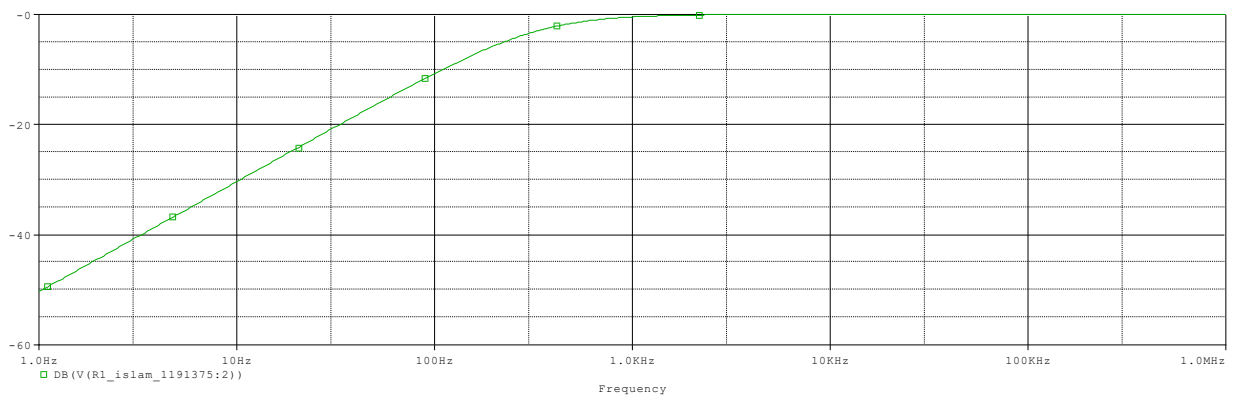

5.

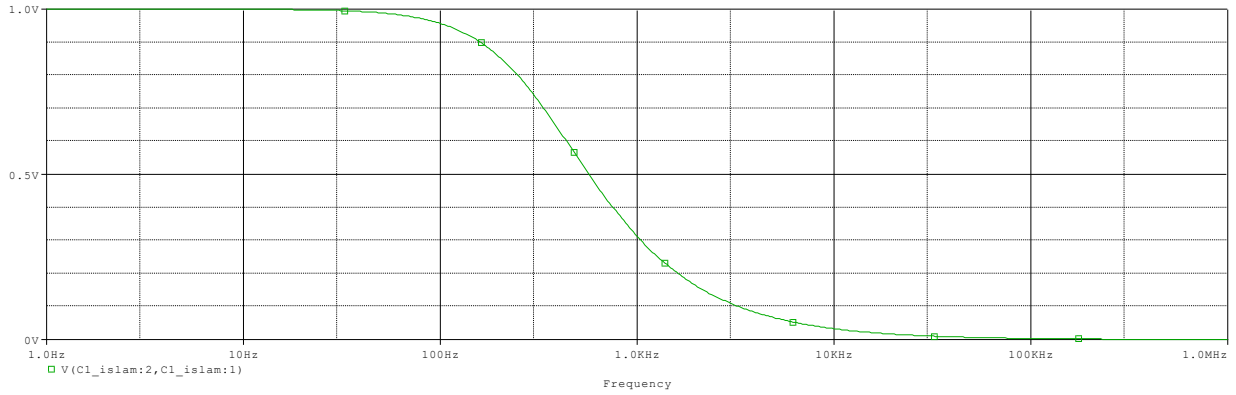

In decibels

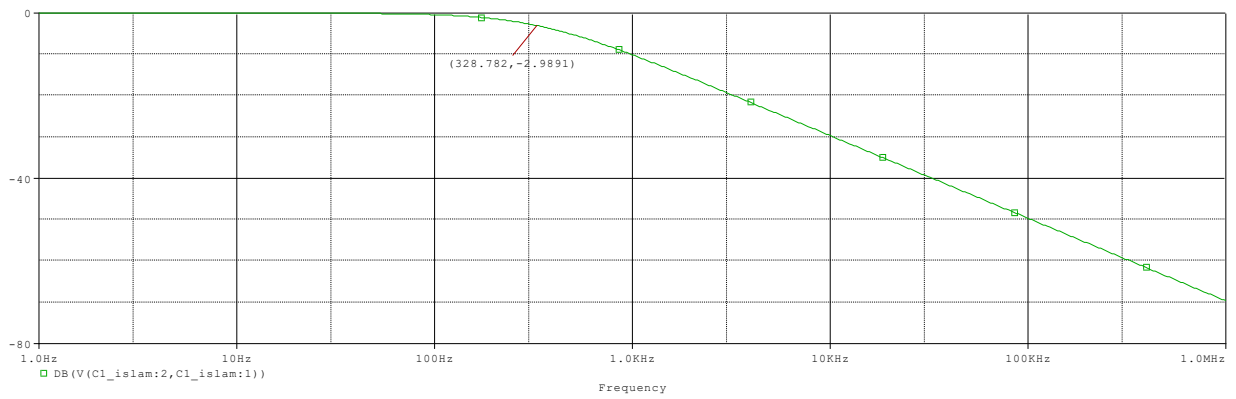


$$F_c = 1/2\pi RC$$

$$= 1/2 * \pi * 2.2k * 220n$$


$$= 328.8$$

6.

P(Vc):

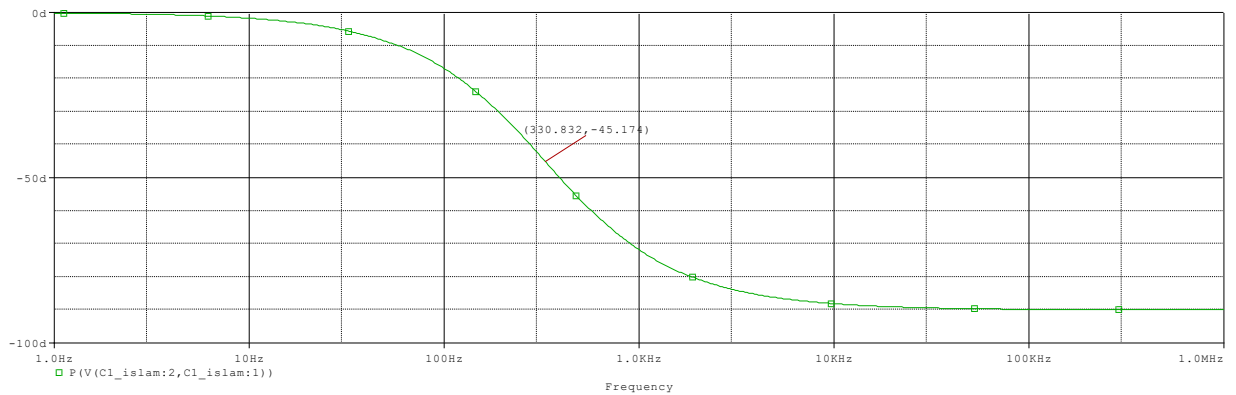


P(Vr):

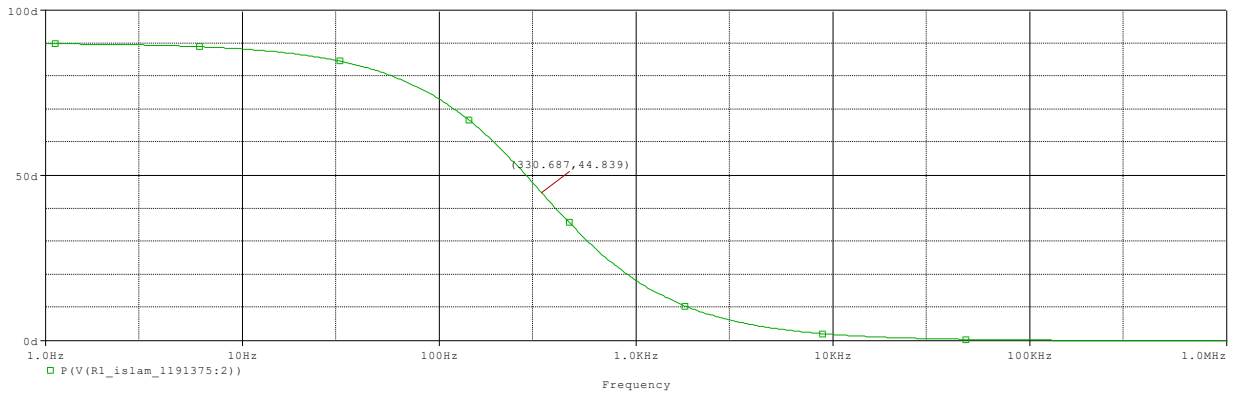


## II. Second Order Fitters:

Vr db amp

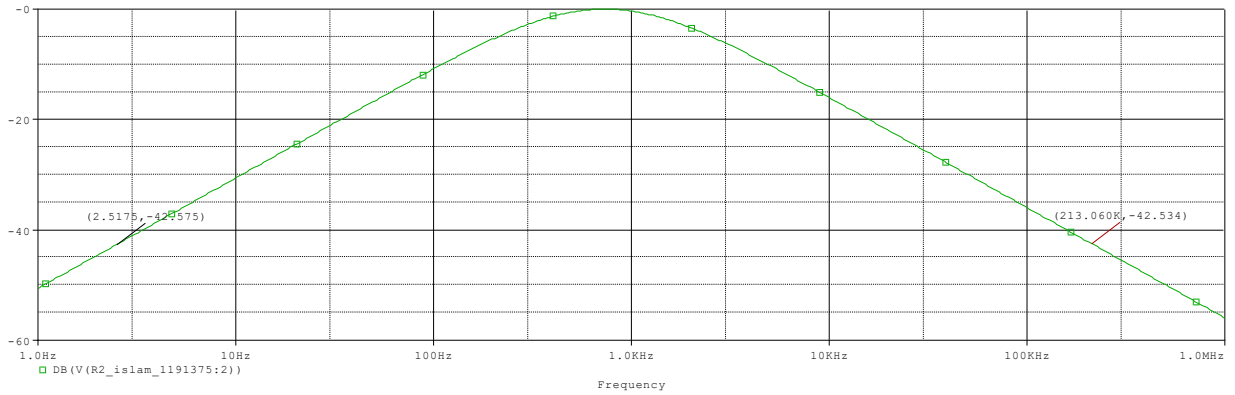


Vr db Phase

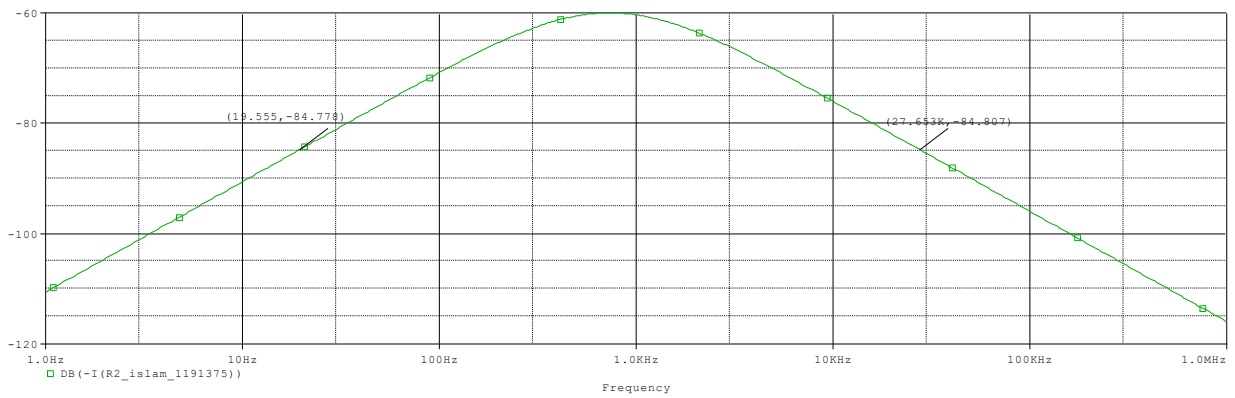


Band Pass Filter

magnitude of  $(V_C+V_L)$  in decibels

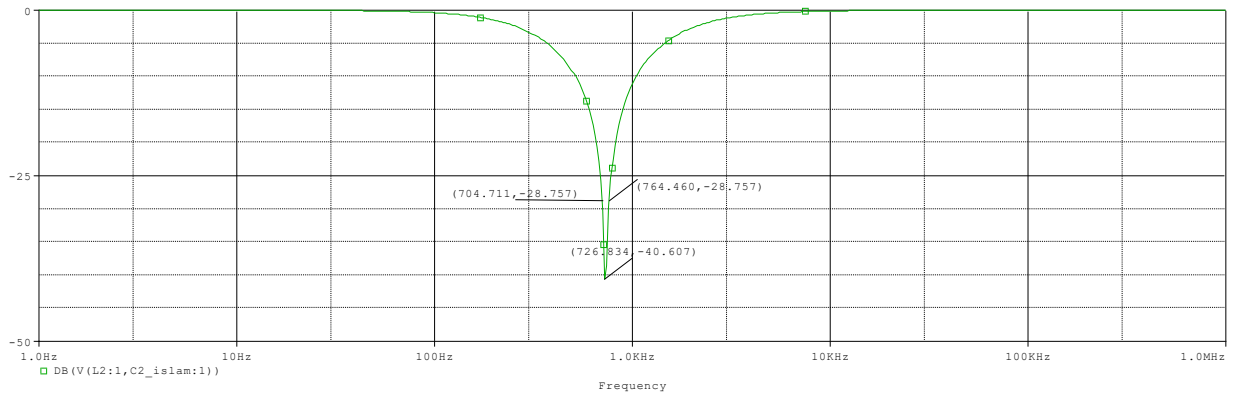


phase of  $(V_C+V_L)$  in decibels

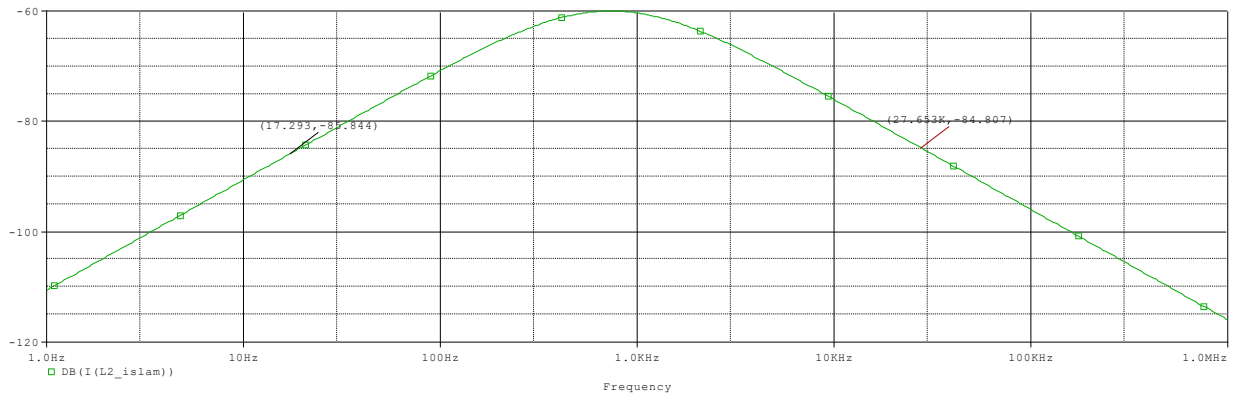


Band Reject Filter


***B. Active filters:***

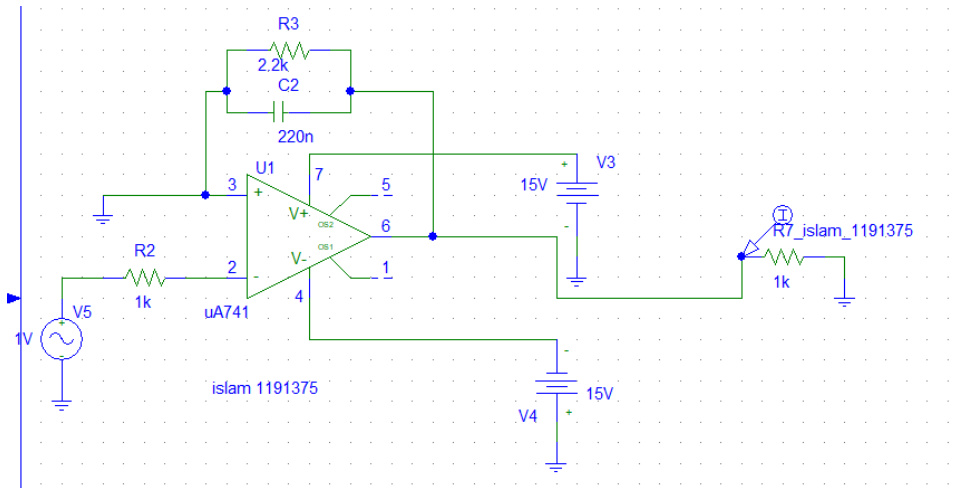

Vout amp

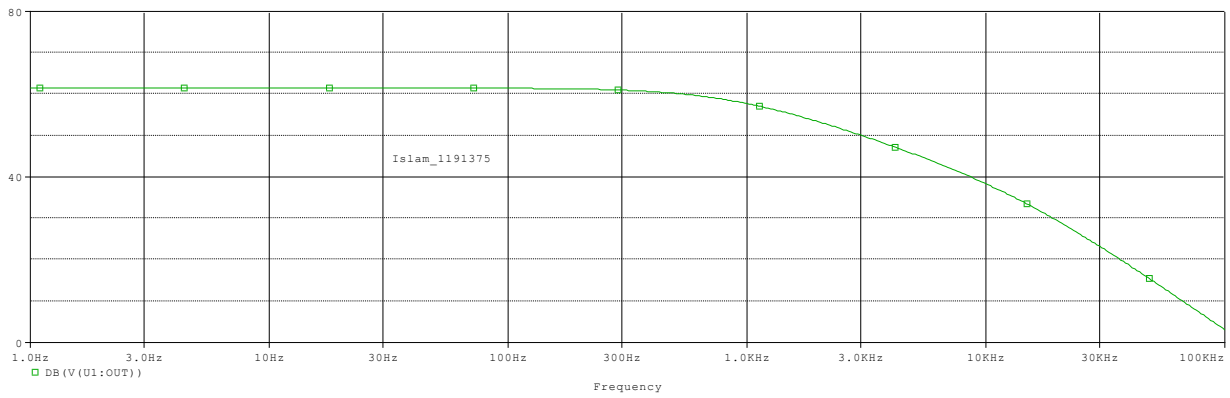

Vo phase

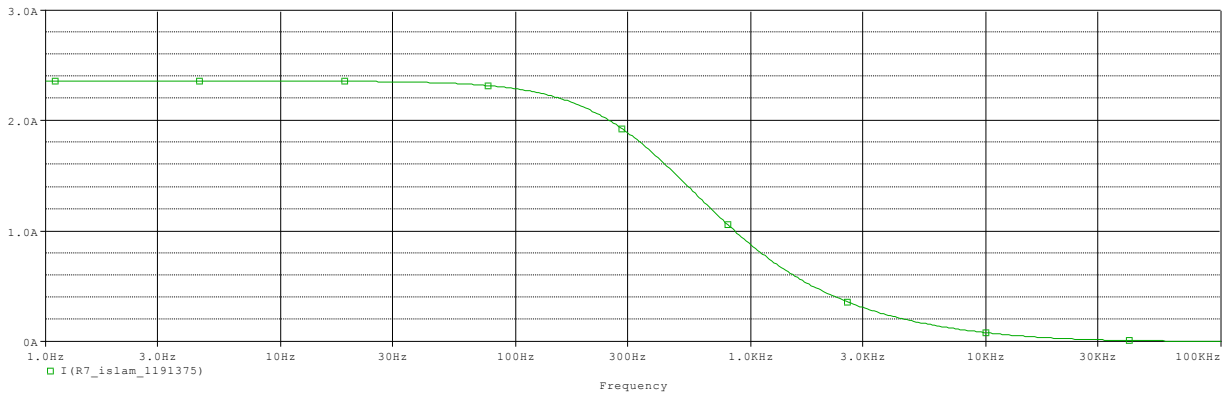

6. The filter type is: low pass filter


7. theoretically →

$$F_c = 1/2\pi RC$$

$$= 1/2 * \pi * 2.2k * 220n$$

$$= 328.8$$

Form the graph:

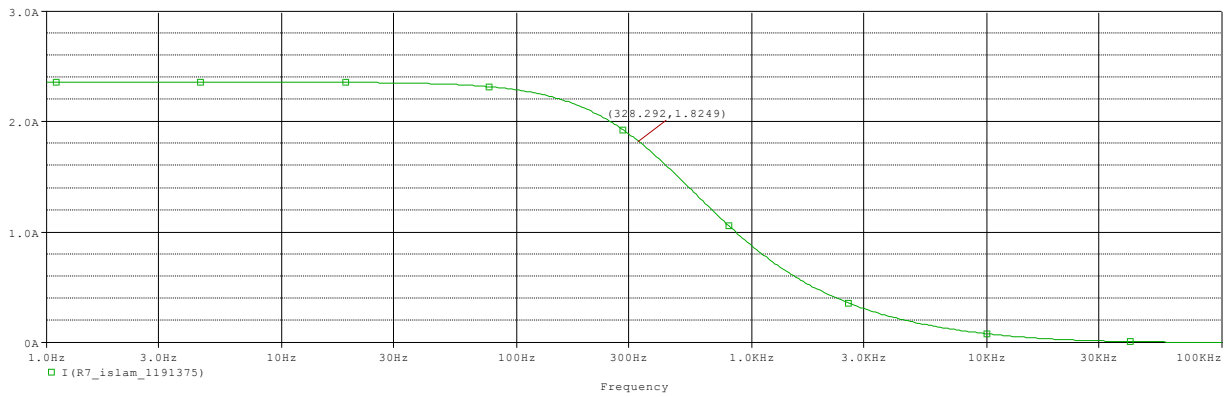

Almost the same