

L 22
17 - 8 - 2021

ENEE2360 Analog Electronics

T11: Operational Amplifiers


Instructor : Nasser Ismail

1

Operational Amplifiers

- Early Operational Amplifiers were constructed with vacuum tubes and were used in analog computers to perform mathematical operations.
- Even as late as 1965, vacuum tube operational amplifiers were still in use and cost in the range of \$75.
- These days, they are linear Integrated circuits (IC) that use low voltage dc supplies , they are reliable and inexpensive
- The operational amplifier has become so cheap in price (often less than \$1.00 per unit) and it can be used in so many applications

Early Vacuum Tube Operational Amplifiers

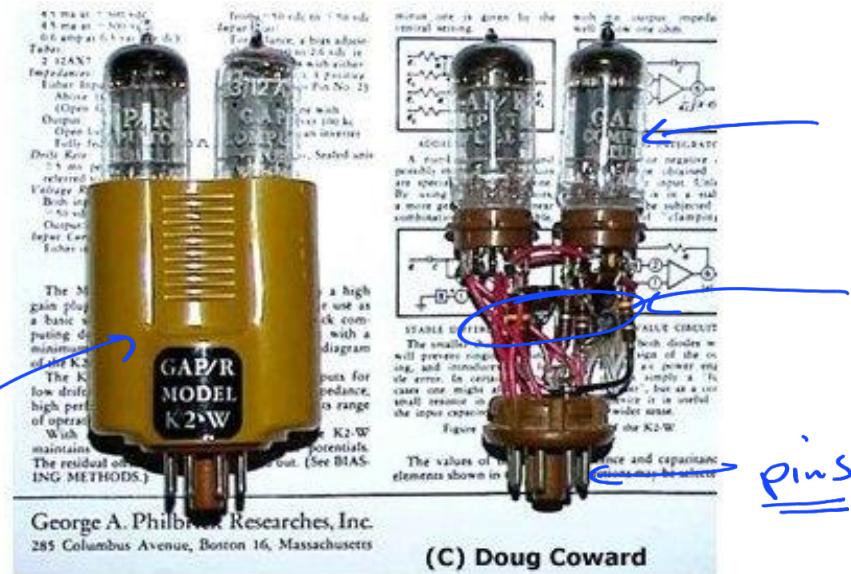

The Philbrick Operational Amplifier (1952)

From “Operational Amplifier”, by Tony van Roon: <http://www.uoguelph.ca/~antoon/gadgets/741/741.html>

Operational Amplifiers

Operational was used as a descriptor early-on because this form of amplifier can perform operations of :

- Adding signals
- Subtracting signals
- Integrating signals, $\int x(t)dt$
- Differentiation of signals,

The applications of operational amplifiers (shortened to op amp) have grown beyond those listed above.


What can you do with Op amps?


- You can make music louder when they are used in stereo equipment.
- You can amplify the heartbeat by using them in medical cardiographs.
- You can use them as comparators in heating systems.

- You can use them for Math operations
- And many other applications in all fields of engineering

Operational Amplifiers → ?

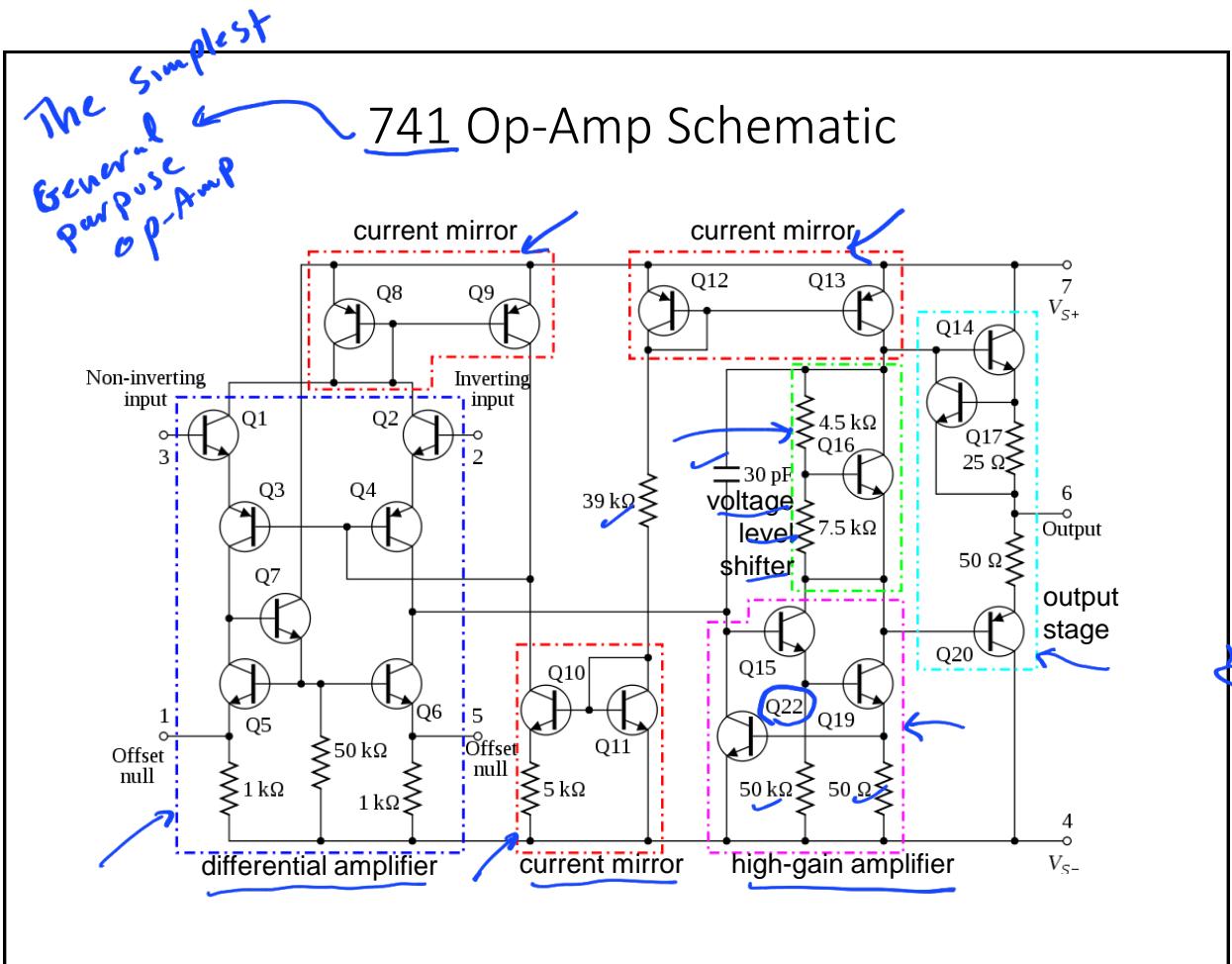- In this course we will be concerned with how to use the op amp as a device.
- The internal configuration (design) is beyond the scope of our study and can be covered in an advanced electronics course.
- The complexity is illustrated in the following block diagram and detailed circuit.



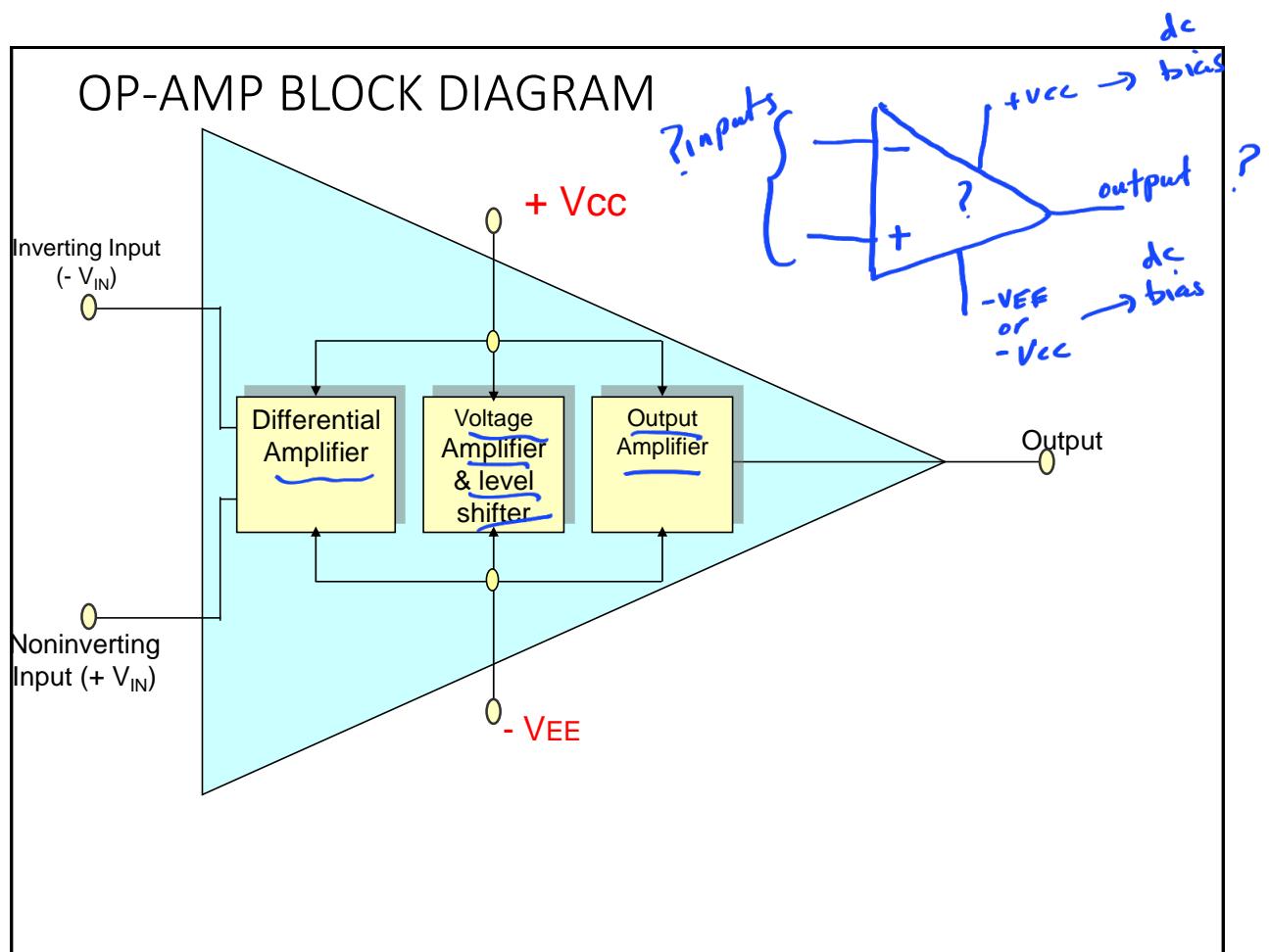

OP-AMP CHARACTERISTICS


1. Very high input impedance (in mega ohms)
 2. Very high gain (> 100,000)
 3. Very low output impedance (in ohms)
- * OP-AMP is a differential, voltage amplifier with high gain.

Operational Amplifiers


Fortunately, we do not have to assemble a circuit with so many transistors and resistors in order to get and use the op amp

The circuit in the previous slide is usually encapsulated into a dual in-line pack (DIP).

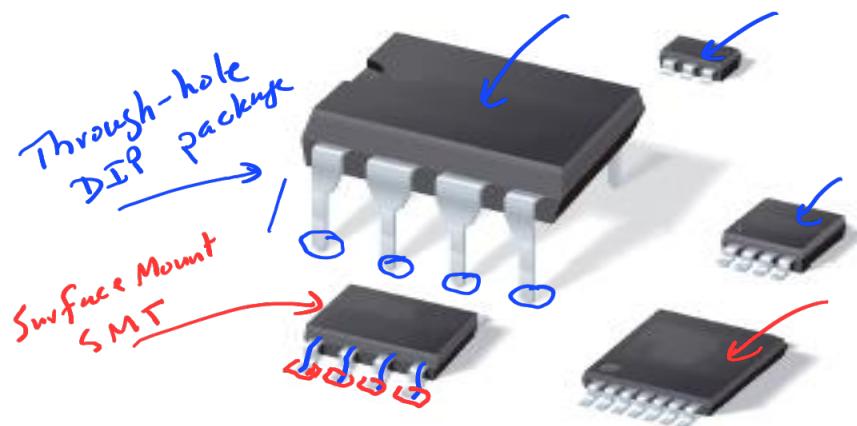
For a single LM741, the pin connections for the chip are shown below.



Packaging Types

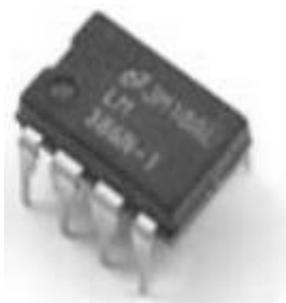

(a) Op Amp 741
8-pins DIP package

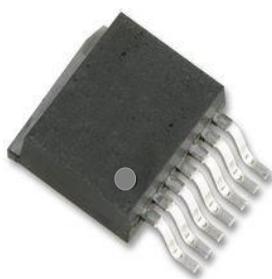

(b) OPA547FKTWT



DIP SMT package

Op Amp packages




(c) TO-5 metal can
8-Leads package

OP-AMP pins identification

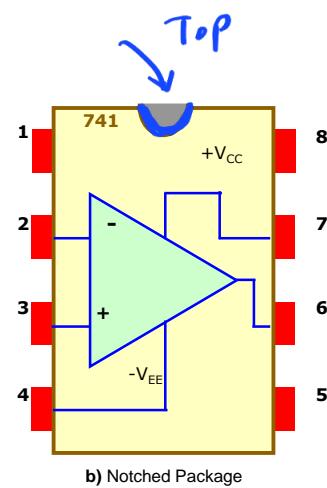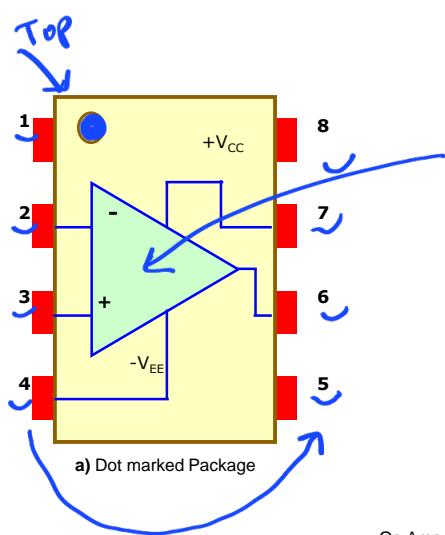


Op Amp pins Identification

What are these pins?

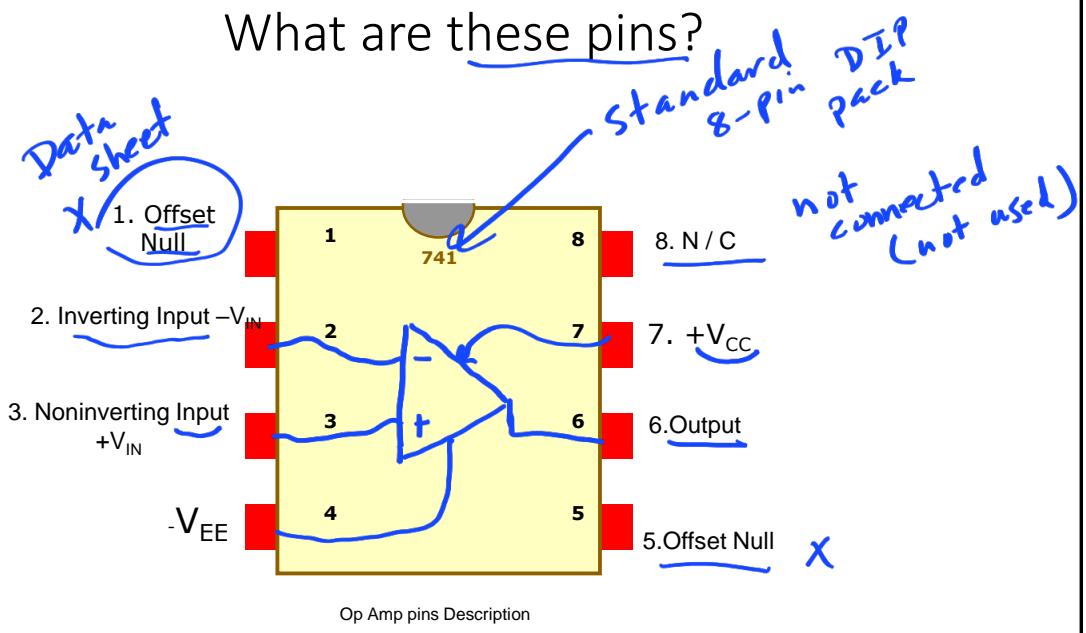

Symbol of OP-AMP

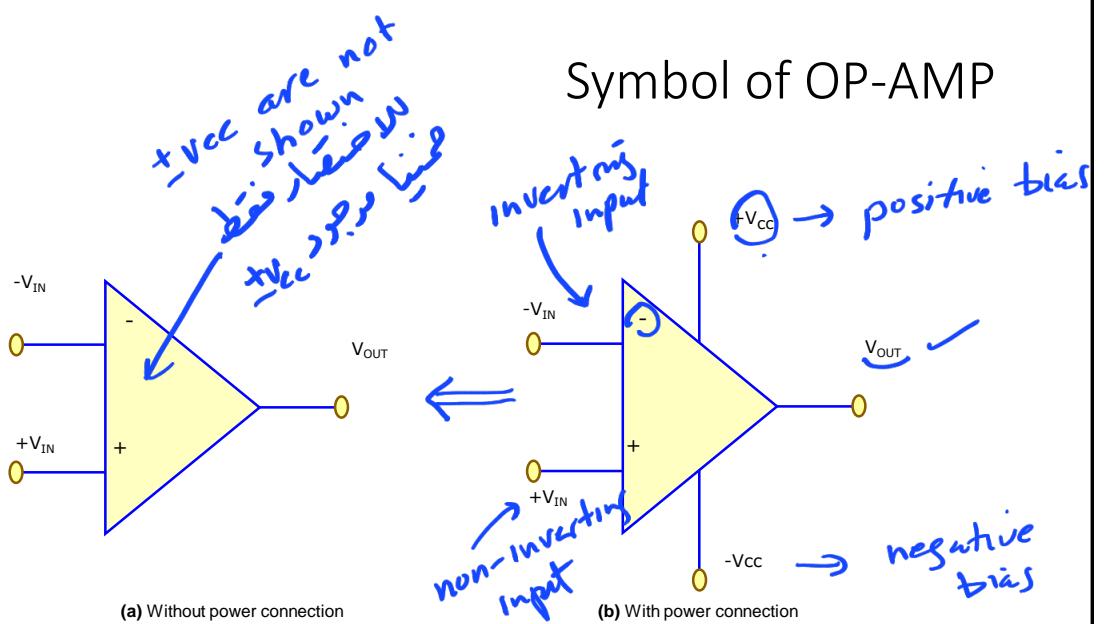


Op Amp Schematic Symbols

Most Op Amps require dual power supply with common ground


Positive Supply +Vcc to pin7 in 741 opamp

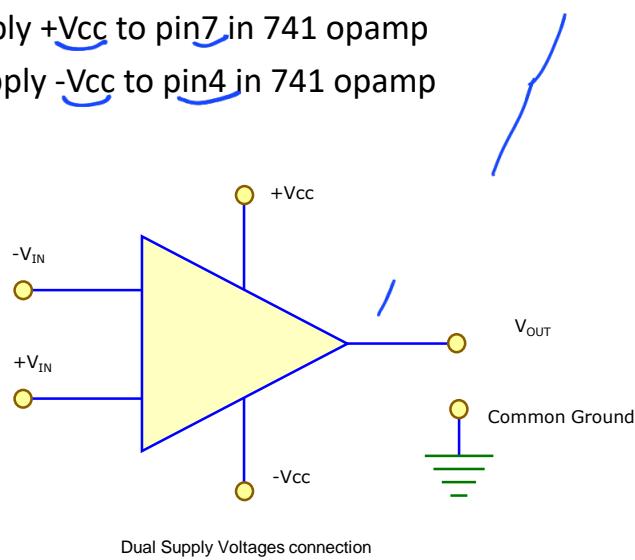Negative Supply -Vcc to pin4 in 741 opamp




Dual Supply Voltages connection

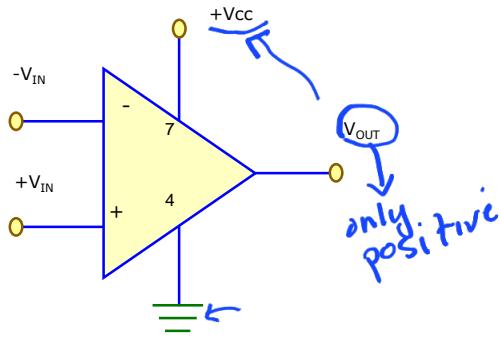Some Op Amps work on single supply
also (with some restrictions)



(a) Single Positive Voltage


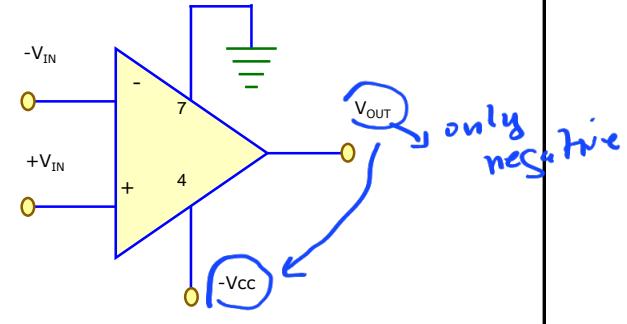


Single Negative Voltage


Single Supply Voltages connection

Advantage of dual power supply

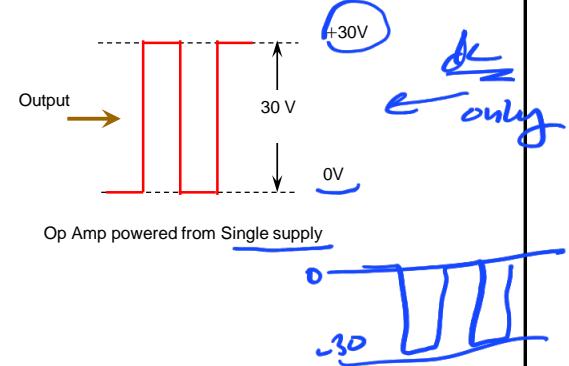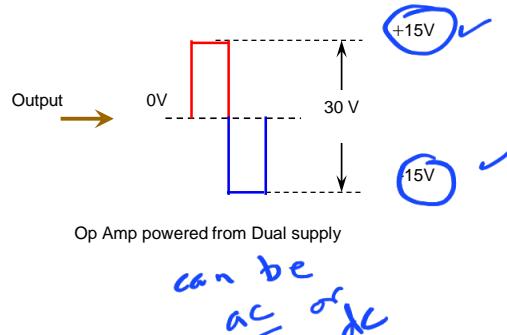Using dual power supply will let the op amp to output true AC voltage.





What is dual power supply?

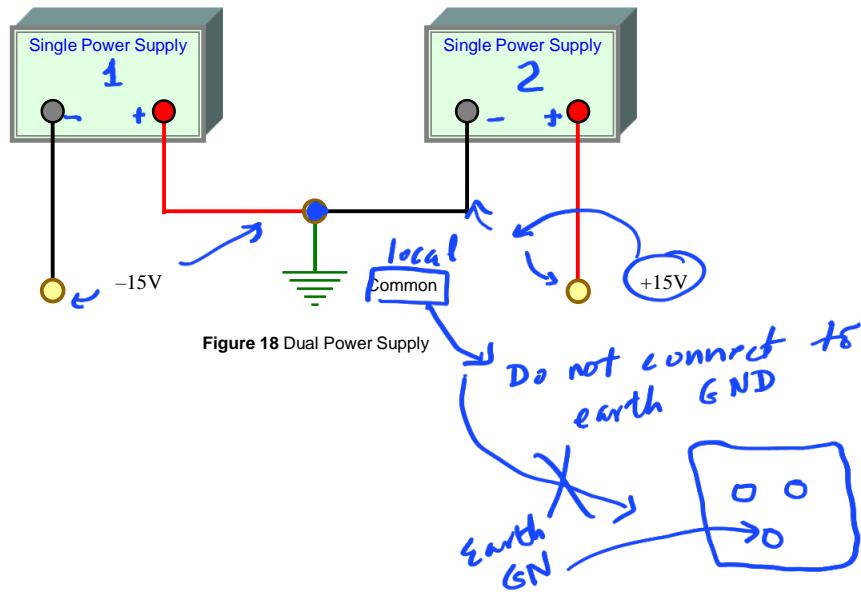


How can you make a dual power supply using two 9V batteries?

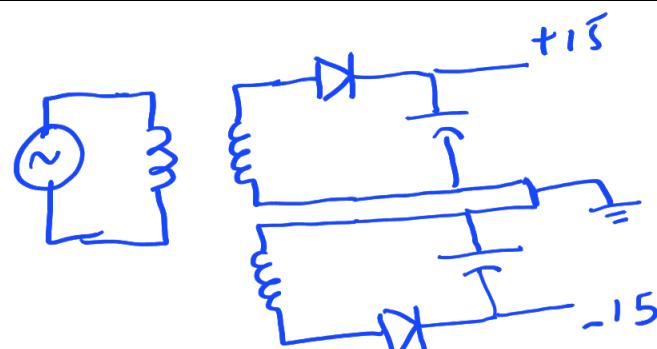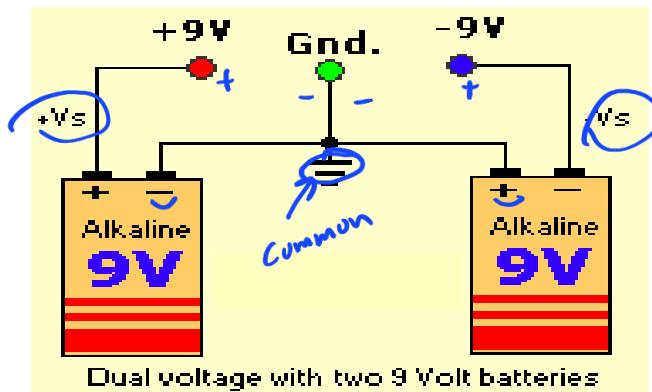What is the voltage between + of first battery and – of second battery?



Operational Amplifiers

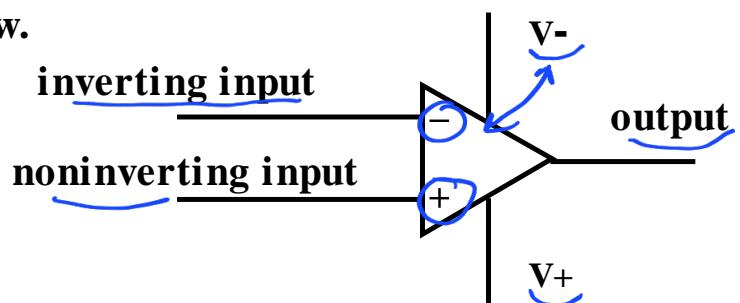The basic op amp with supply voltage included is shown in the diagram below.




In most cases only the two inputs and the output are shown for the op amp.


However, one should keep in mind that supply voltage is required, and a ground.

Operational Amplifiers Model

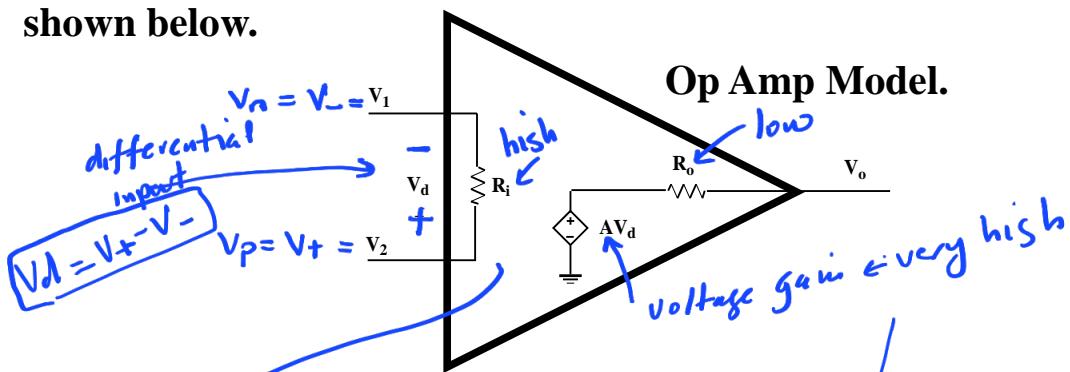A model of the op amp, with respect to the symbol, is shown below.




Working circuit diagram of op amp

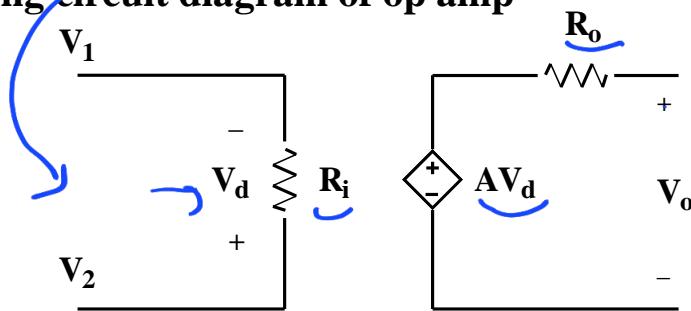



$$+V_{sat} \approx +V_{cc} - 2$$

$$-V_{sat} \approx -V_{cc} + 2$$

to be used
in this course

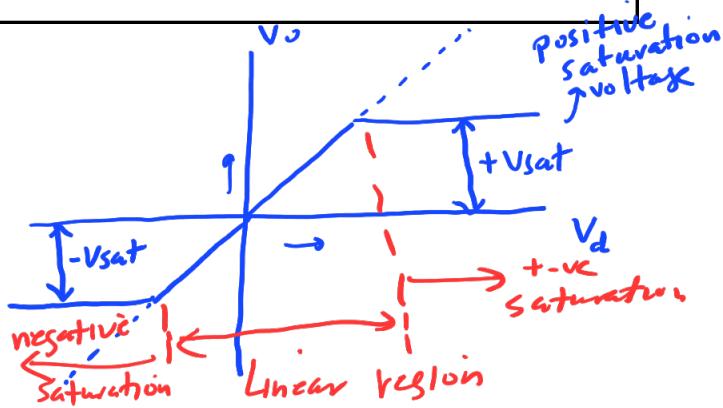

Voltage Transfer Characteristic

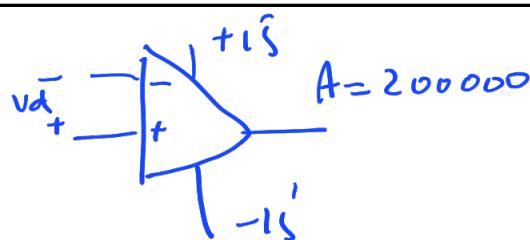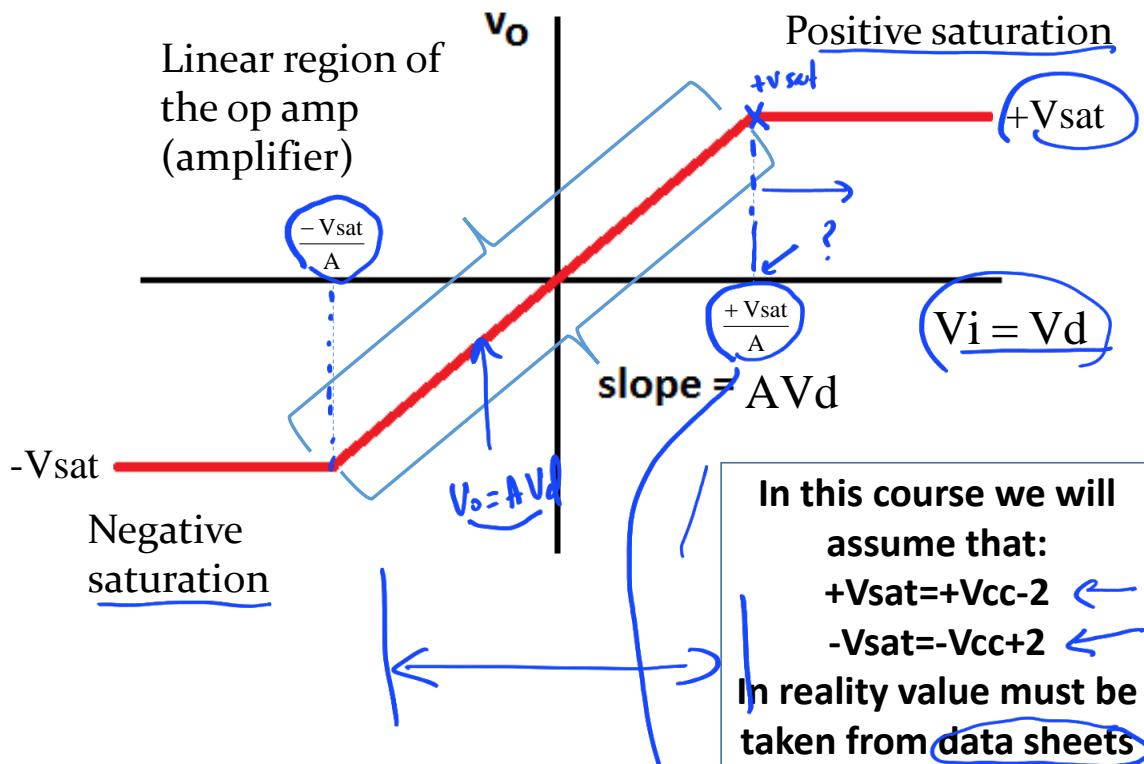


$$\pm V_{sat} = \pm 13$$

$$\frac{+V_{sat}}{A} = \frac{13}{200000} = 65 \mu V$$

$$\frac{-V_{sat}}{A} = -65 \mu V$$

Output Voltage

- Real Op Amp

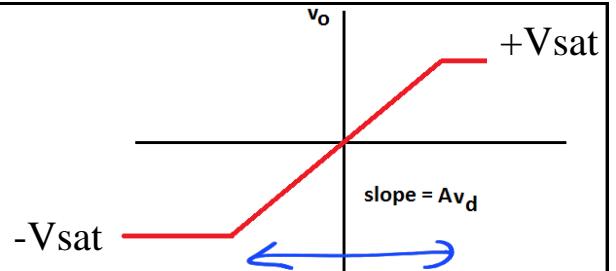


Mode of operation	Voltage Range	Output Voltage
Positive Saturation	$A v_d > +V_{sat}$	$v_o = +V_{sat} = \sim +V_{cc} - 2$
Linear Region	$-V_{sat} < A v_d < +V_{sat}$	$v_o = A v_d$
Negative Saturation	$A v_d < -V_{sat}$	$v_o = -V_{sat} = \sim -V_{cc} + 2$

The voltage produced by the dependent voltage source inside the op amp is limited by the voltage applied to the positive and negative rails and $\pm V_{sat}$ level which is approximated by the formulas above

Operational Amplifiers Analysis (Exact)

As an application of the previous model, consider the following configuration.

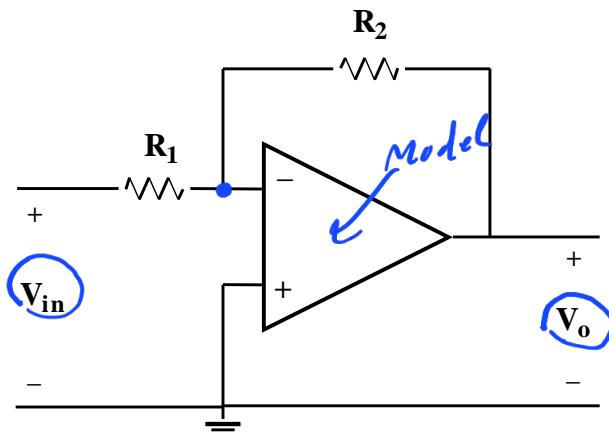Find V_o as a function of V_{in} and the resistors R_1 and R_2 .



Op amp functional circuit.


Operational Amplifiers

$V_i = V_d = V_p - V_n = V_+ - V_-$ differential input voltage

$V_p = V_+$ voltage at the non-inverting input

$V_n = V_-$ voltage at the inverting input

Equivalent circuit

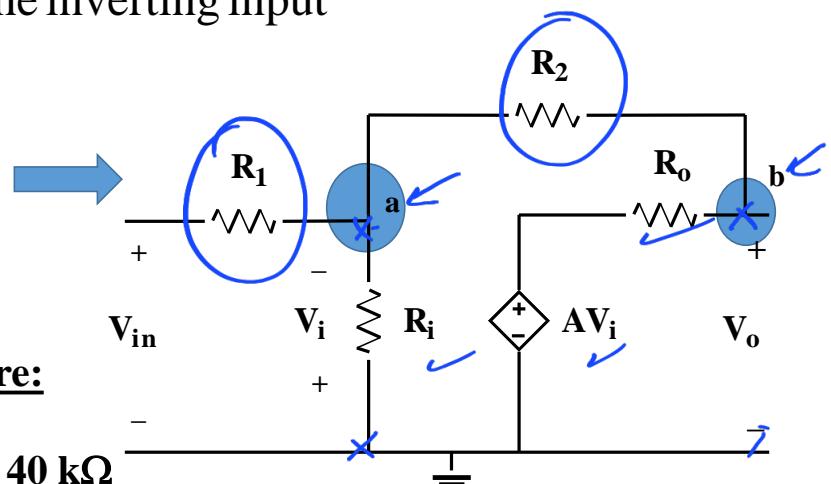

Component values are:

$$\begin{aligned} R_1 &= 10 \text{ k}\Omega & R_2 &= 40 \text{ k}\Omega \\ R_o &= 50 \Omega & A &= 100,000 \\ A &= 100,000 & R_i &= 1 \text{ meg } \Omega \end{aligned}$$

Operational Amplifiers

Exact solution


We can write the following equations for nodes a and b.

KCL at A ✓

$$\frac{V_{in} + V_i}{R_1} = \frac{-V_i}{R_i} - \frac{V_i + V_o}{R_2} \quad (1)$$

KCL at B ✓
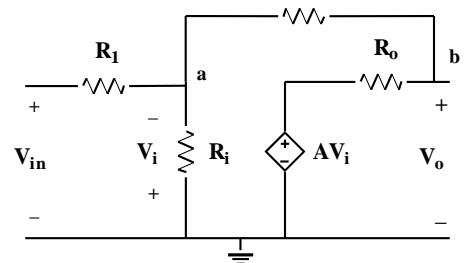
$$V_o = R_o \left[\frac{-(V_i + V_o)}{R_2} \right] + AV_i \quad (2)$$



$$\begin{aligned} R_1 &= 10 \text{ k}\Omega & R_2 &= 40 \text{ k}\Omega \\ R_o &= 50 \Omega & A &= 100,000 \\ & & R_i &= 1 \text{ meg } \Omega \end{aligned}$$

Operational Amplifiers

Equation 1 simplifies to;

$$\frac{V_{in} + V_i}{10k} = \frac{-V_i}{1000k} - \frac{V_i + V_o}{40k}$$

$$-25V_o - 126V_i = 100V_{in} \quad (3) \leftarrow$$

Equation 2 simplifies to;

$$V_o = 50 \left[\frac{-(V_i + V_o)}{40k} \right] + 100,000V_i$$

$$(4.005 \cdot 10^5)V_o - (4 \cdot 10^9)V_i = 0 \quad (4) \leftarrow$$

Operational Amplifiers

From Equations (3) and (4) we find;

$$V_o = -3.99V_{in}$$
 (5)

This is an expected answer.

Fortunately, we are not required to do elaborate circuit analysis, as above, to find the relationship between the output and input of an op amp. Simplifying the analysis is our next consideration.

Operational Amplifiers Models

For most operational amplifiers,

R_i is 1 Meg Ω or larger and

R_o is around 50Ω or less.

The open-loop gain, A , is greater than 100,000.


Ideal Op Amp Model:

The following assumptions are made for the ideal op amp.

1. *Infinite open-loop gain; $\Rightarrow A \approx \infty$*

2. *Zero output ohms; $\Rightarrow R_o = 0$*

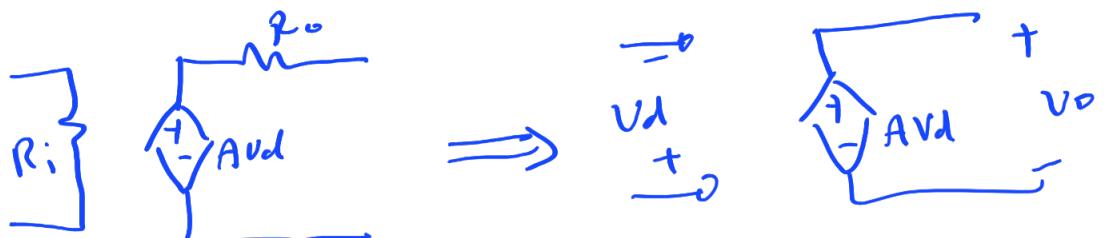
3. *Infinite input ohms; $\Rightarrow R_i = \infty$*



op-amp
ideal-model
* To be used in this
course

Ideal Op Amp Model

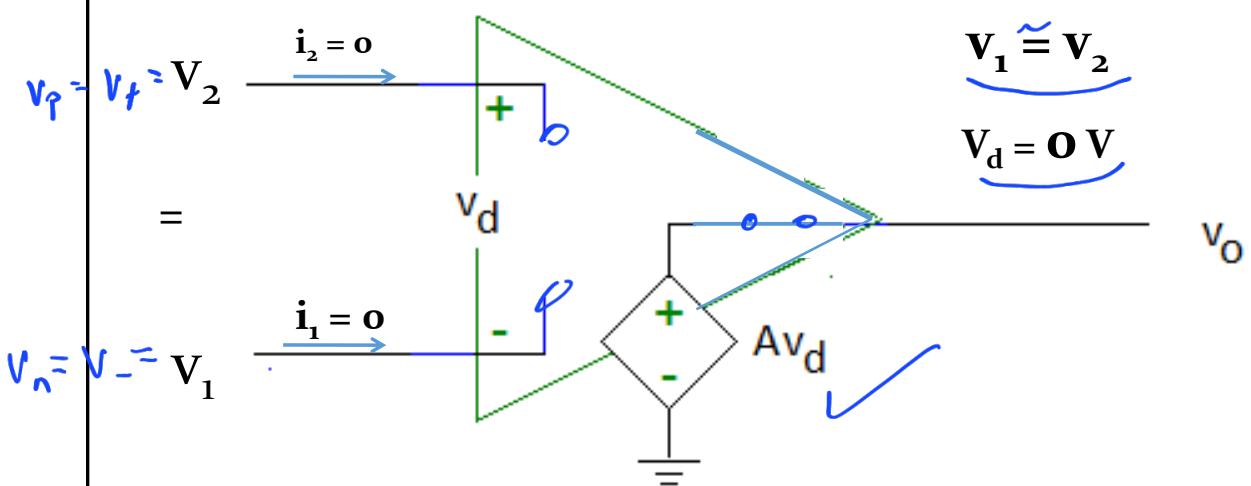
Because R_i is equal to $\infty\Omega$,
the voltage across R_i is 0 V .



Important Note:

Only Ideal Op Amp Model will be used from now on:


$$R_i = \infty \Omega$$

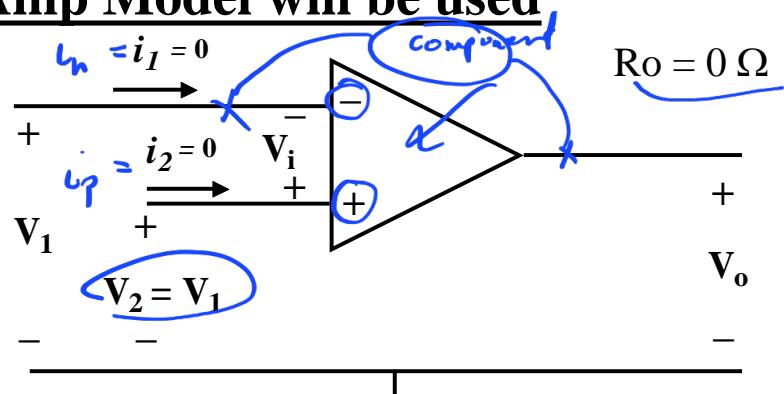

- (a) $i_1 = i_2 = 0$: Due to infinite input resistance. ←
(b) V_i is negligibly small; $V_1 \approx V_2$.


The op amp forces the voltage at the inverting input terminal to be equal to the voltage at the noninverting input terminal if there is some component connecting the output terminal to the inverting input terminal.

OP-AMP CONFIGURATIONS

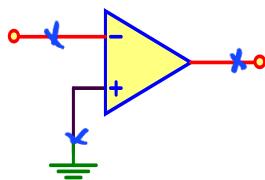


(a) No Feedback
(open loop)
comparator circuit

$V_{out} = -V_{in}$

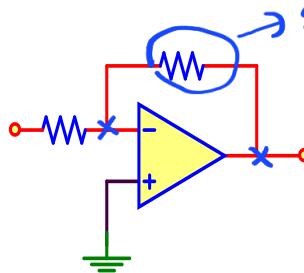

(b) Negative
Feedback

1)

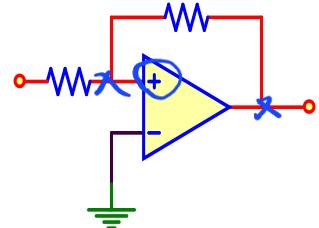

(c) Positive Feedback

- No feedback : Open loop (used in comparators)
- Negative feedback : Feedback to the inverting input (Used in amplifiers)
- Positive feedback : Feedback to the non inverting input (Used in oscillators) and Schmitt triggers (comparators with hysteresis)

**


✓

OP-AMPS WITH NEGATIVE FEEDBACK


The two basic amplifier circuits with negative feedback are:

- The non-inverting Amplifier. ←
- The inverting Amplifier ←

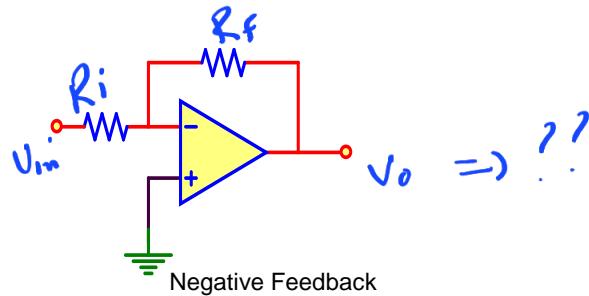
(Note: Negative feedback is used to limit the gain)



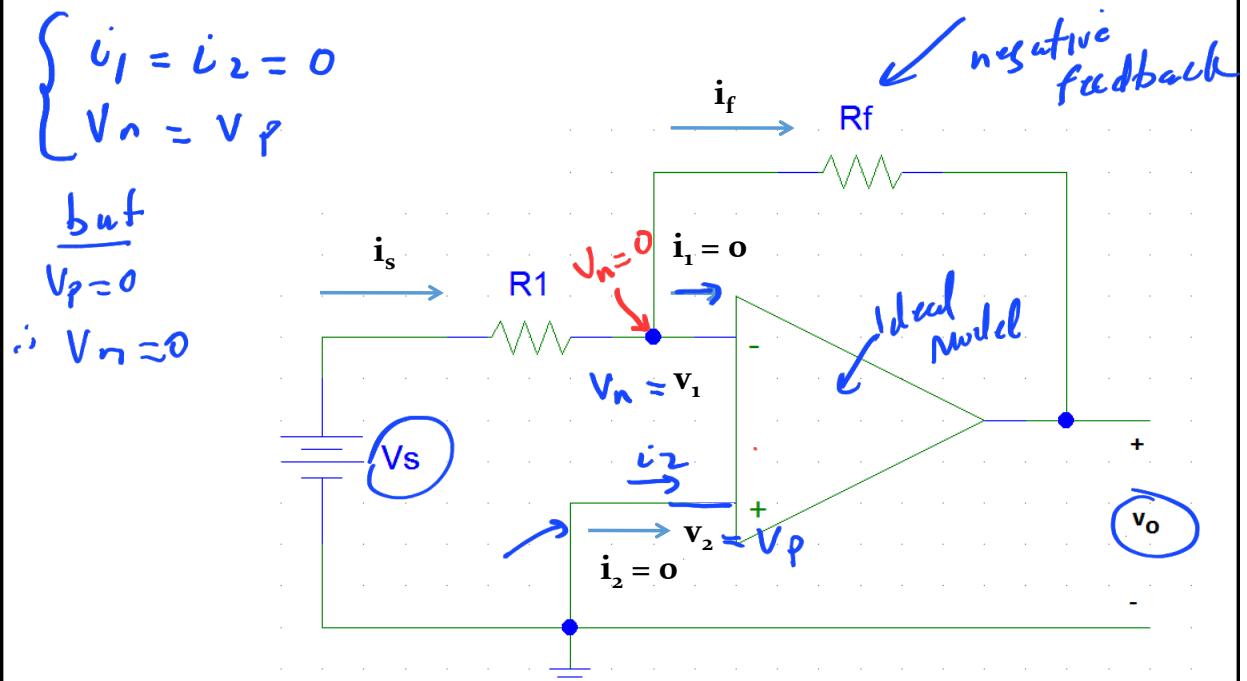Example #2: Closed Loop Gain $\underline{Av} = \frac{V_o}{V_s}$
(inverting amplifier)




Example #2 (con't)

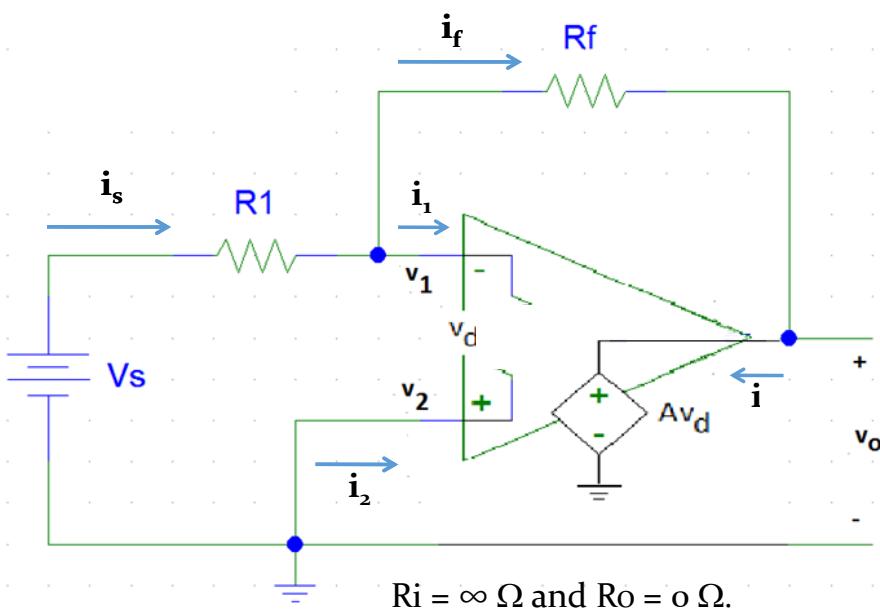

The op amp outputs a voltage V_o such that $V_1 = V_2$.

$$V_2 = V_p = 0 \rightarrow V_1 = V_n = 0$$

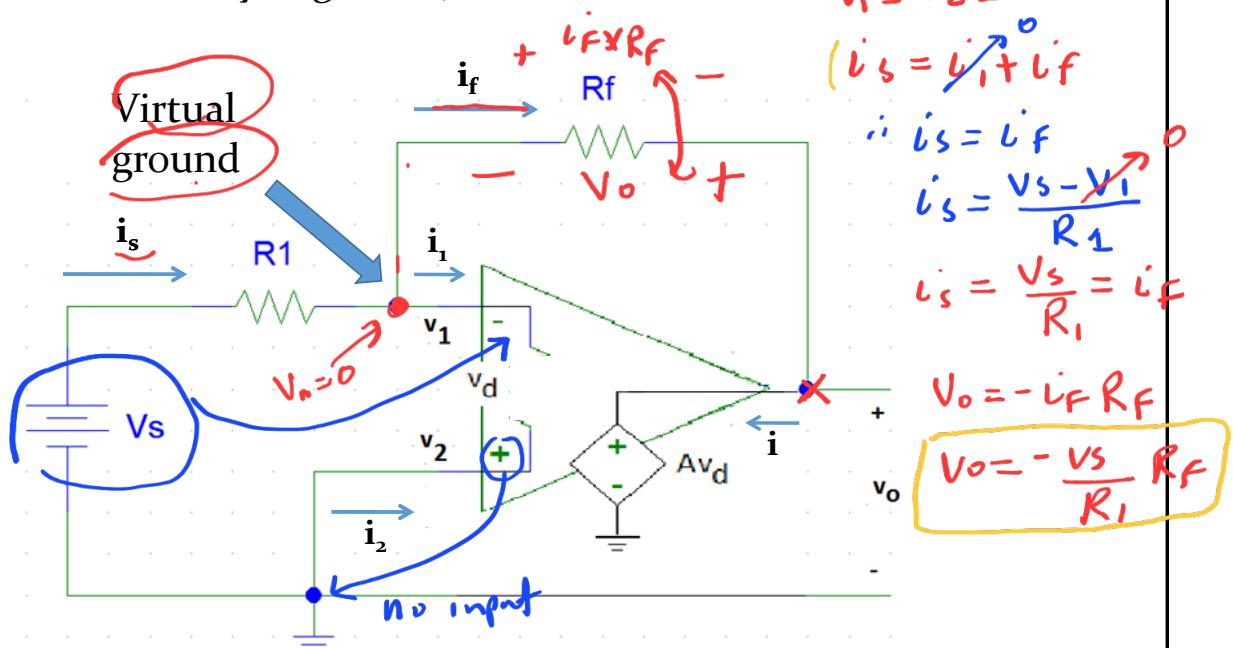(virtual ground - potential equal 0 even though it is not connected really to ground)




$$V_o = -\frac{R_f}{R_1} \cdot V_s \Rightarrow$$

$$A_v = \frac{V_o}{V_s} = -\frac{R_f}{R_1}$$

Inverting Amplifier Gain

Example #2 (con't)

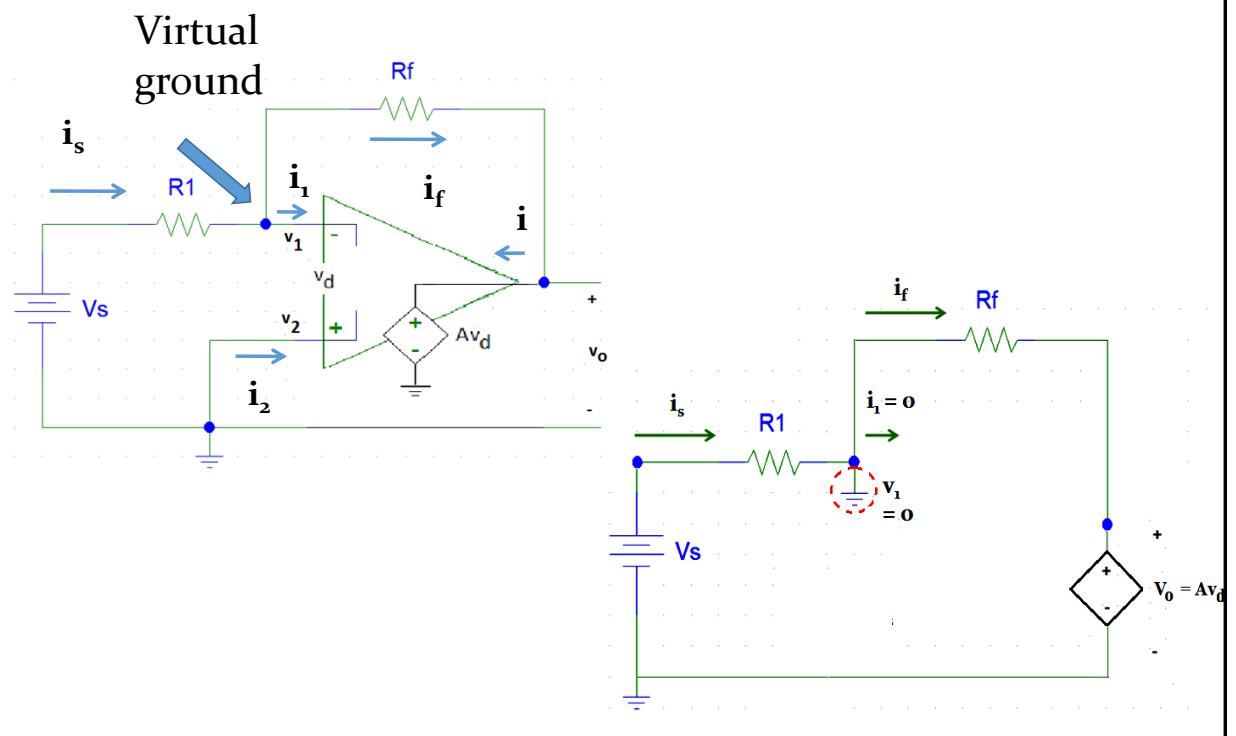


$$V_2 = 0V \Rightarrow V_1 = 0V$$

$$V_s = R_1 i_s$$

$$v_o = -R_f i_f$$

$$i_s = i_f = i$$

Example #2: Closed Loop Gain

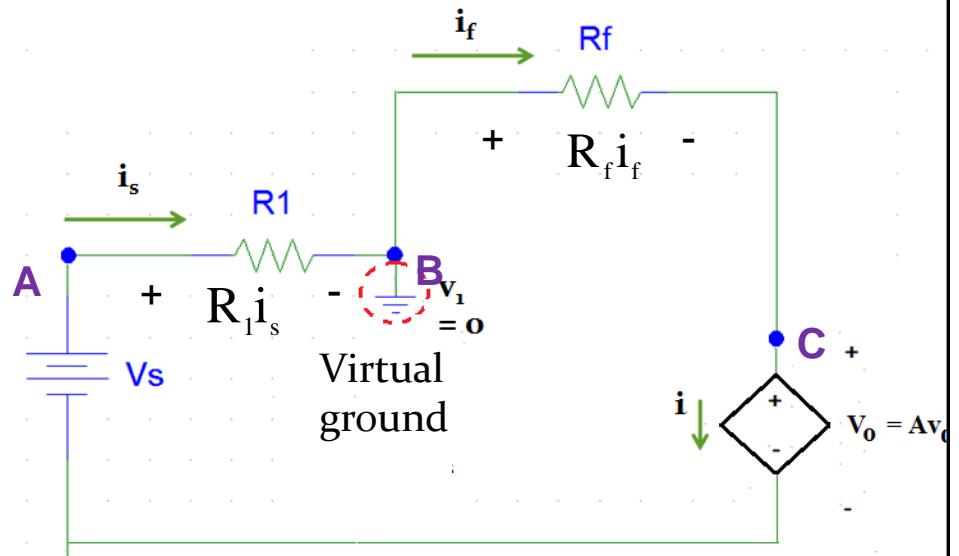


$$A_v = v_o / V_s = \frac{-R_f i_f}{R_1 i_s}$$

$A_v = -R_f / R_1$ → This circuit is known as an inverting amplifier.

Inverting Amplifier (previous example of slide 30)

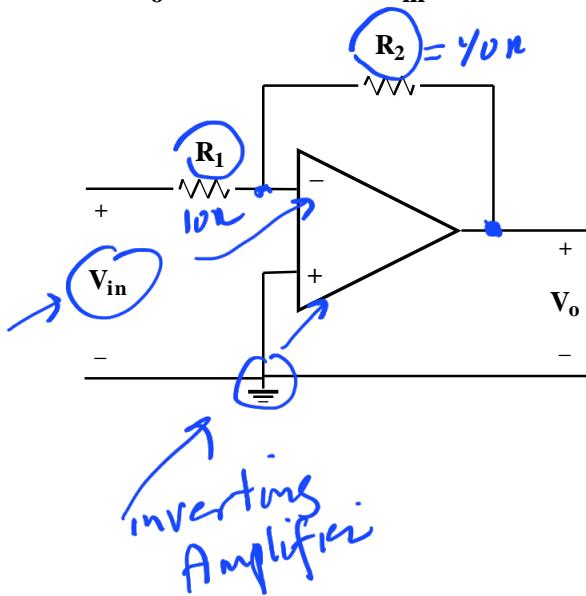Find V_o in terms of V_{in} for the following configuration.



$$V_o = -\frac{R_2}{R_1} V_{in}$$

With $R_2 = 40 \text{ k}\Omega$ and $R_1 = 10 \text{ k}\Omega$, we have

$$V_o = -4V_{in}$$

Earlier
we got


$$V_o = -3.99V_{in}$$

$$\frac{0.01}{4} \times 100\% = 0.25\% \text{ error}$$

Inverting Op Amp:

When $V_i = 0$ in and we apply the Laplace Transform:
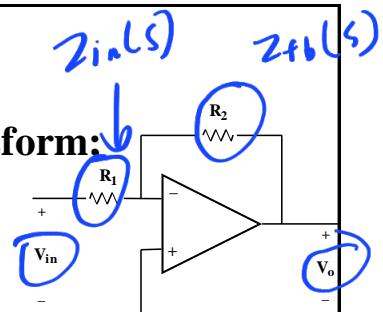
$$\frac{V_o(s)}{V_{in}(s)} = \frac{-R_2}{R_1}$$



In fact, we can replace R_2 with $Z_{fb}(s)$ and R_1 with $Z_1(s)$ and we have the important expression;

$$\frac{V_o(s)}{V_{in}(s)} = \frac{-Z_{fb}(s)}{Z_{in}(s)}$$


At this point in circuits we are not able to appreciate the use of this equation. We will revisit this at a later point in circuits but for now we point out that judicious selections of $Z_{fb}(s)$ and $Z_{in}(s)$ leads to important applications in

- Analog Compensators in Control Systems
- Analog Filters
- Application in Communications

Example

Find the value of V_o and I_o and verify if the opamp is in linear or saturation mode for two values of feedback resistor; assume $I_{o(\max)}=20 \text{ mA}$:

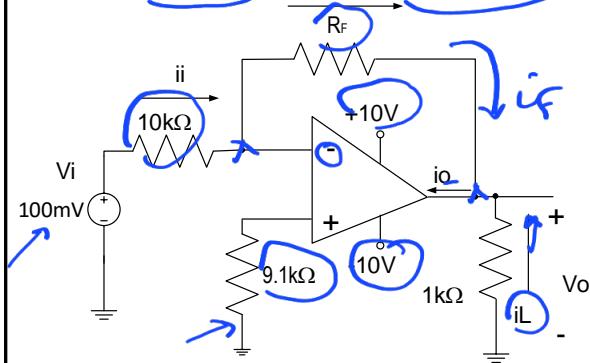1) $R_F=100\text{k}\Omega$ 2) if $R_F=2\text{M}\Omega$



Important

$I_{o(\max)}$ is few mA for most opamps which limits the values of resistors to be used to kohm range

$$V_p = V(+) = 0V$$


$$i_1 = \frac{V_i}{R_1}$$

$$i_i = i_f = \frac{V_i}{10k} = \frac{100 \text{ mV}}{10 \text{ k}\Omega} = 10 \mu\text{A}$$

$$1) V_o = -\frac{R_F}{10 \text{ k}\Omega} V_i = -10 V_i = -1 \text{ V}$$

$$V_o > -V_{sat}$$


Linear mode

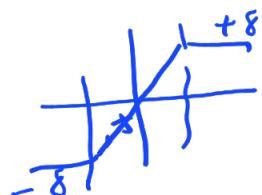

Example

Find the value of V_o and I_o and verify if the opamp is in linear or saturation mode for two values of feedback resistor:

1) $R_F=100k\Omega$ 2) $R_F=2M\Omega$

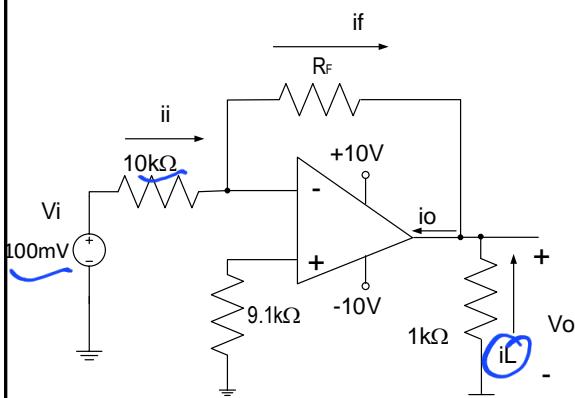

$$i_o = i_f + i_L$$


$$i_L = \frac{1V}{1k} = 1mA$$

$$i_o = 10\mu A + 1mA = 1.01mA < I_o(\max)$$

20mA

Example continued

2) $R_F=2M\Omega$

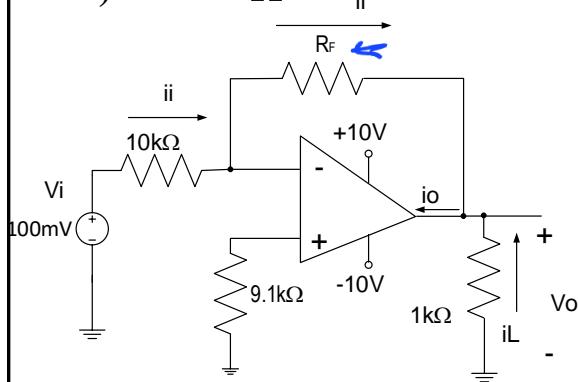

$$i_i = i_f = \frac{V_i}{10k} = \frac{100mV}{10k} = 10 \mu A$$

$$2)V_o = -\frac{R_f}{10k} V_i = -\frac{200}{10k} V_i = -20V$$

$$V_o < -V_{sat}$$

$$-V_{sat} = -8V$$

Saturation mode $\Rightarrow V_o$ is limited to $-V_{sat}$

$$\therefore V_o = -V_{sat} = -8V$$


$$i_L = \frac{8V}{1k} = 8mA$$

$$i_o = 10 \mu A + 8mA = 8.01mA < I_o(\text{max})$$

20mA

End of L22


op-Amp

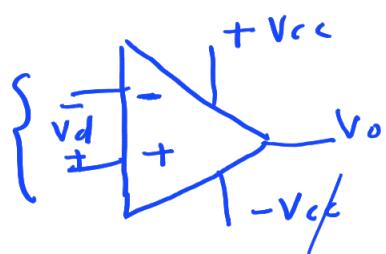


Negative Feedback

1. Inverting Amplifier

$$V_o = -\frac{R_F}{R_i} V_i$$

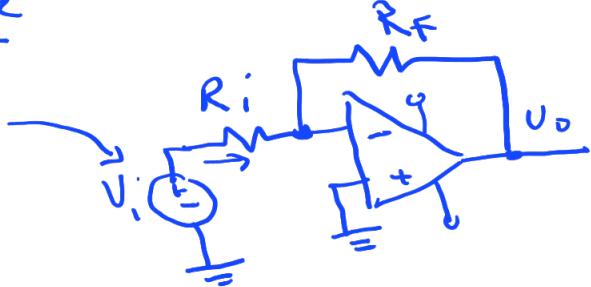Inverting Adder or Summing Amplifier

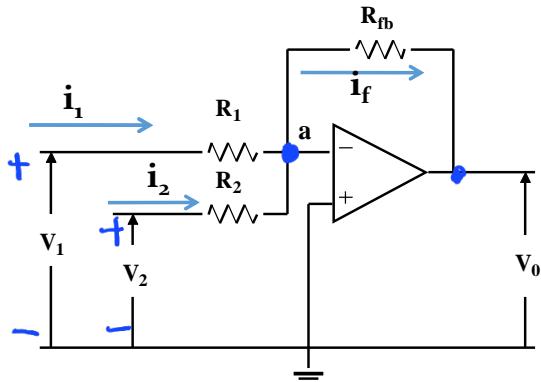Summing Amplifier: This is an application of inverting amplifier



$$V_p = V_{(+)} = 0V$$

$$i_1 = \frac{V_1}{R_1} \quad i_2 = \frac{V_2}{R_2}$$

$$V_o = -R_f i_f$$

$$i_f = i_1 + i_2$$


$$V_o = - \left[\left(\frac{R_{fb}}{R_1} \right) V_1 + \left(\frac{R_{fb}}{R_2} \right) V_2 \right]$$

$$V_o = -R_f [i_1 + i_2]$$

If $R_1 = R_2 = R_{fb}$ then,

$$V_o = -[V_1 + V_2]$$

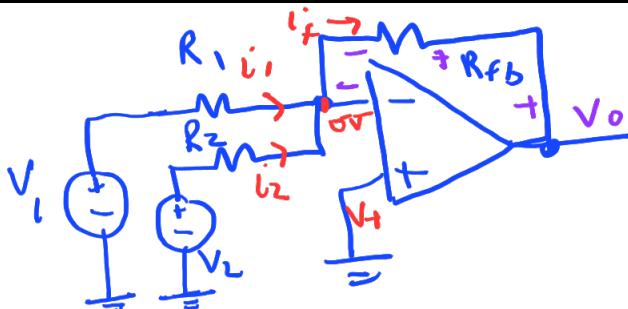Therefore, we can add signals with an op amp



$$V_+ = 0; V_- = V_+ = 0$$

$$i_1 = \frac{V_1}{R_1}; i_2 = \frac{V_2}{R_2};$$

$$i_f = i_1 + i_2$$

$$V_o = -i_f R_{fb} = -(i_1 + i_2) R_{fb}$$

$$V_o = - \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) R_{fb}$$

$$\text{if } R_1 = R_2 = R_{fb} \Rightarrow$$

$$V_o = -(V_1 + V_2)$$


2) Non-Inverting

$$V_+ = V_- ; \text{ but } V_+ = V_i ; \therefore V_- = V_i$$

$$i_i = \frac{V_i}{R_1} = i_f$$

$$V_o = i_f R_f + i_i R_1 = i_f (R_f + R_1)$$
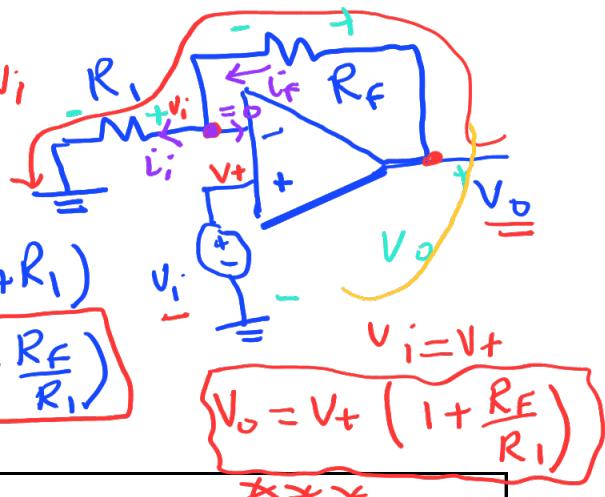
$$V_o = \frac{V_i}{R_1} (R_f + R_1) = V_i \left(1 + \frac{R_f}{R_1} \right)$$



The non-inverting op amp.

The non-inverting op amp has the input voltage connected to its (+) terminal while no voltage at the negative terminal

$$V_n = V_1 = V_p = V_s$$


$$i_+ = i_- = 0$$

$$V_o = V_{R1} + V_{R2}$$

$$V_{R1} = V_1 = i_1 R_1$$

$$V_{R2} = i_2 R_2$$

but

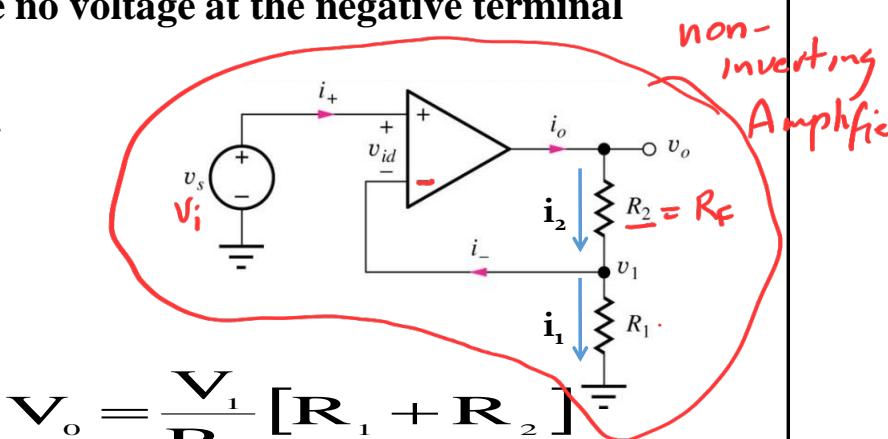

which gives,

$$i_1 = i_2 = \frac{V_1}{R_1}$$

$$V_o = \left(1 + \frac{R_2}{R_1} \right) V_s$$

Example: Non-inverting Amplifiers


Example: Find V_o for the following op amp configuration.

$$V_x = \frac{6k}{6k + 2k} 4V \quad \checkmark$$

$$V_x = 3V \quad \checkmark$$

$$V_o = \left(1 + \frac{R_F}{R_i}\right) V_x \quad \checkmark$$


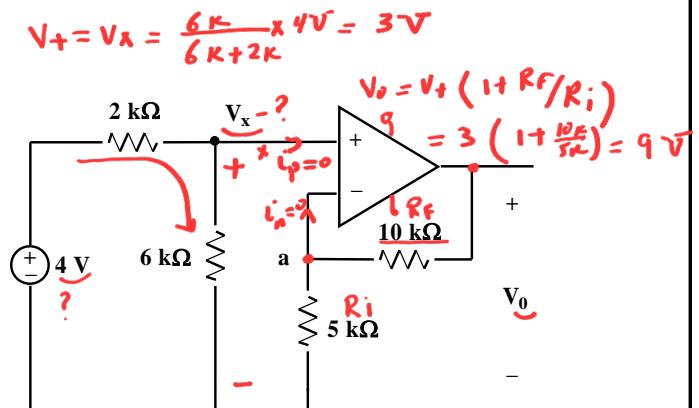
$$V_o = \left(1 + \frac{10k}{5k}\right) 3V \quad \checkmark$$



$$V_o = 9V \quad \stackrel{-V_{cc}+2}{\Rightarrow} \quad \stackrel{+V_{cc}-2}{\Rightarrow}$$

Make sure that: $-V_{sat} < V_o < +V_{sat}$

Non-Inverting Adder

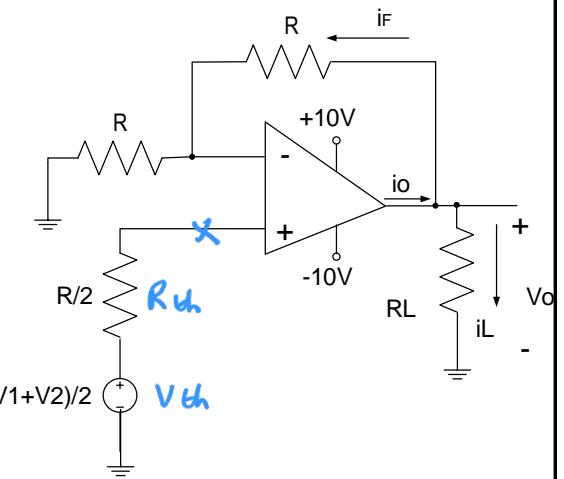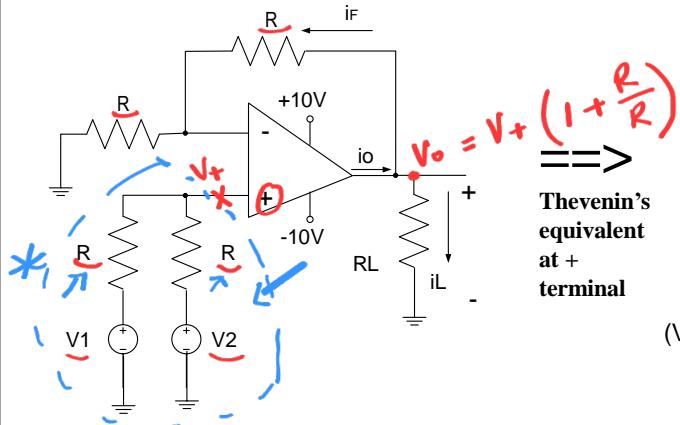


$$V_{TH} = \left(\frac{R}{R+R}\right)V_1 + \left(\frac{R}{R+R}\right)V_2 = \left[\frac{V_1 + V_2}{2}\right]$$

$$V_+ = V_{TH} \quad \Leftarrow \text{(since } i_+ = 0\text{)}$$


$$V_o = \left(1 + \frac{R}{R}\right)V_+ \quad \Rightarrow \quad V_o = \left(1 + \frac{R}{R}\right) \left[\frac{V_1 + V_2}{2}\right] \quad \boxed{V_o = [V_1 + V_2]}$$

$$V_o = 2 \left[\frac{V_1 + V_2}{2}\right]$$

adder

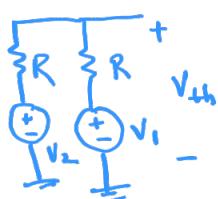

superposition

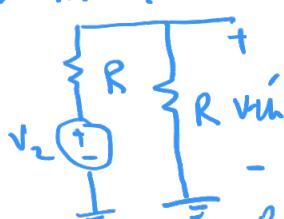


$$\begin{aligned} V_{TH} &= V_+ = \\ &= \frac{R}{R+R} V_1 + \frac{R}{R+R} V_2 \\ &= \frac{R}{R+R} (V_1 + V_2) = \frac{V_1 + V_2}{2} \\ V_{TH}'' &= \frac{R}{R+R} V_1 \end{aligned}$$


Design An Amplifier that have two input voltages V_1 & V_2 such that the output $V_o = 3V_1 + 5V_2$
(use inverting Amplifiers)

Solution → with inverting Amplifier $V_o = -(3V_1 + 5V_2)$

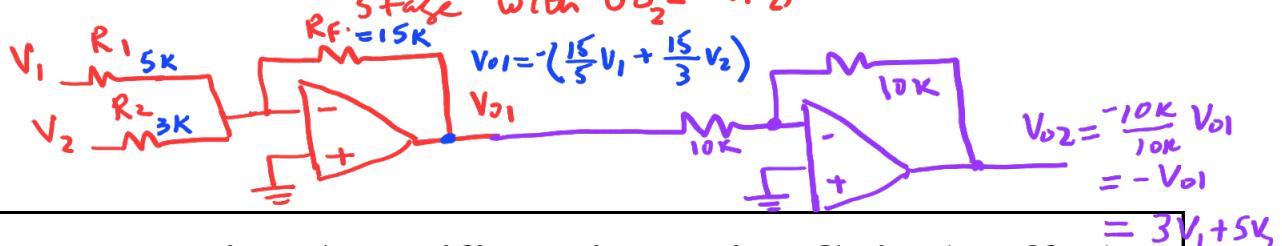→ we can have a second stage with $V_{o2} = -V_{in2}$, $V_{o1} = V_{in2}$



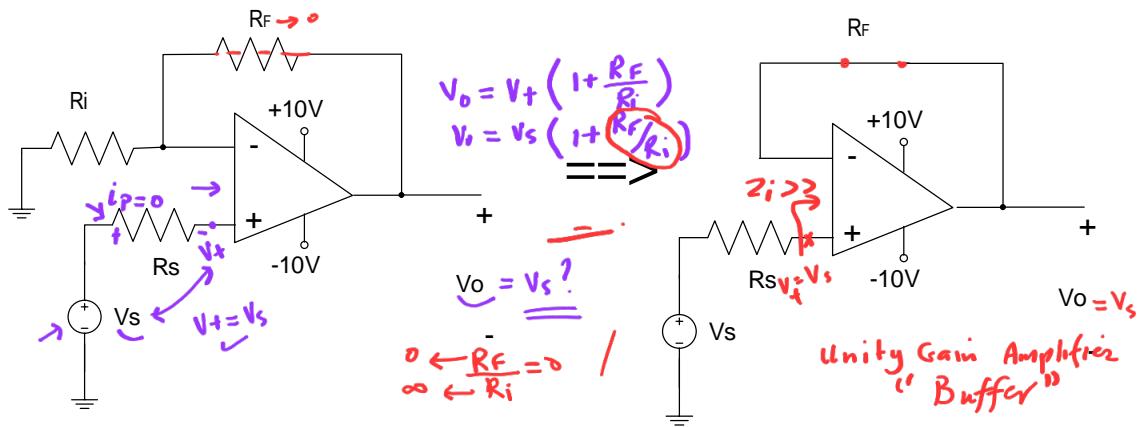Non-Inverting Amplifier with unity Gain (Buffer)



$$V_o = V(-)$$


$$V(-) = V(+) = V_s$$

$$V_o = V_s$$


$$\frac{V_o}{V_s} = 1$$

Buffer or Isolation Amplifier or Voltage Follower

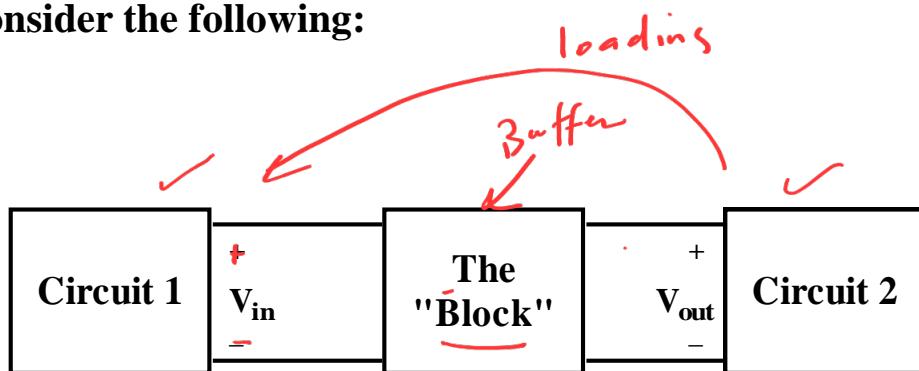- Applications arise in which we wish to connect one circuit to another without the first circuit loading the second.
- This requires that we connect to a “block” that has infinite input impedance and zero output impedance.
- An operational amplifier does a good job of approximating this.
- Consider the following:




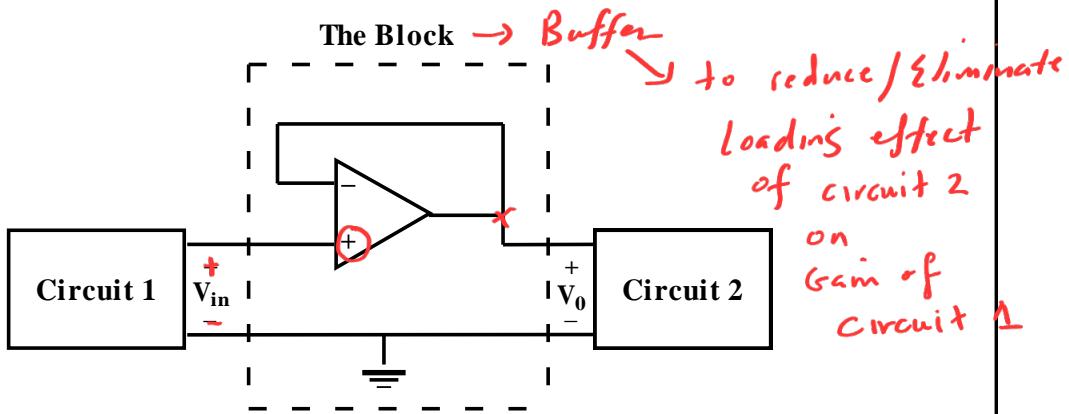
Buffer or Isolation Amplifier or Voltage Follower



Circuit isolation with an op amp.

It is easy to see that: $V_0 = V_{in}$

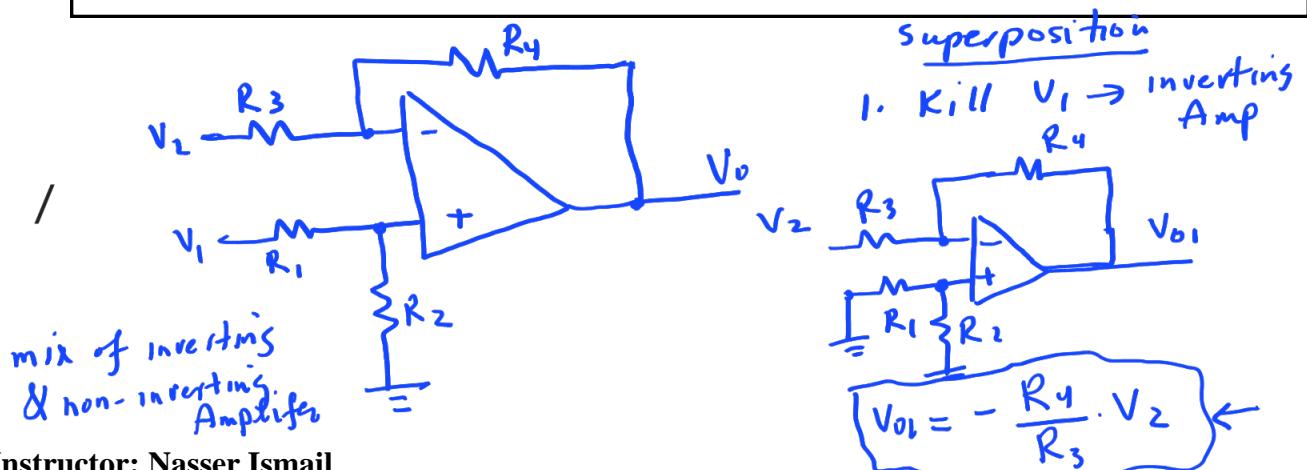

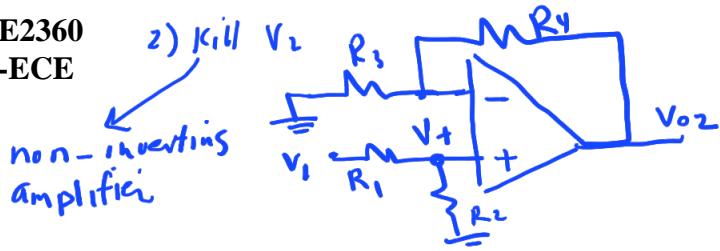

$$V_{o2} = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_1$$

$$V_+ = \frac{R_2}{R_1 + R_2} \cdot V_1$$

$$a = \left(\frac{R_3 + R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right)$$

$$b = \frac{R_4}{R_3}$$

$$V_o = V_{o1} + V_{o2}$$

$$V_o = \left(\frac{R_3 + R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_1 - \frac{R_4}{R_3} V_2$$


$$V_o = a V_1 - b V_2$$

*

Difference Amplifier (Subtractor)

For the following op amp configuration, in order to find V_o we can use

Superposition:

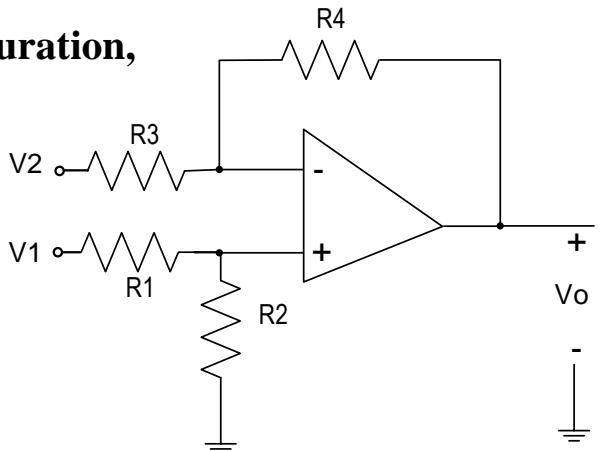

- 1) Short V_2 and find contribution of V_1 to V_o ==> non-inverting amp

$$V_o = V_{o1}$$



- 2) Short V_1 and find contribution of V_2 to V_o ==> inverting amp

$$V_o = V_{o2}$$

- 3) The total output is found by summing the two results above

$$V_o = V_{o1} + V_{o2}$$

Difference Amplifier (Subtractor)

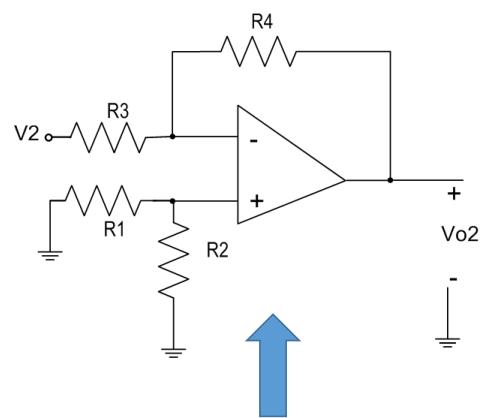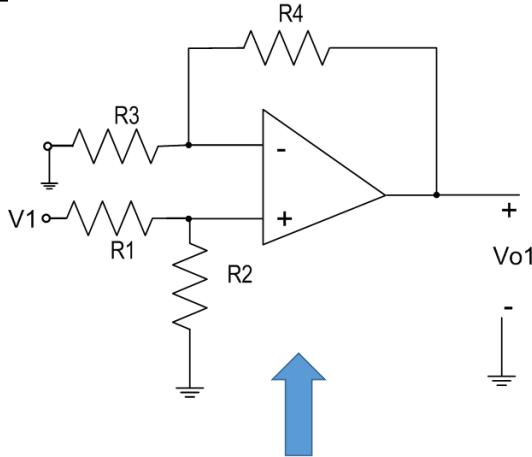

Non-Inverting Amplifier


$$V_{o1} = \left(1 + \frac{R_4}{R_3}\right) V_+$$

$$V_{o1} = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_1$$

Inverting Amplifier

$$V_{o2} = -\frac{R_4}{R_3} V_2$$

Difference Amplifier (Subtractor)

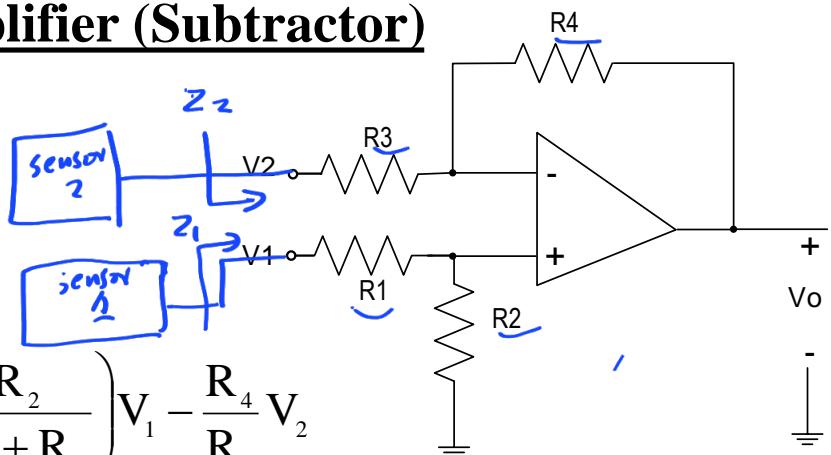

$$V_o = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2} \right) V_1 - \frac{R_4}{R_3} V_2$$

$$V_o = aV_1 - bV_2$$

$$a = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2} \right) = \frac{R_2}{R_3} = m$$

$$b = \frac{R_4}{R_3} = \frac{mR}{R} = m$$

let $R_1 = R_3 = R$
 $R_2 = R_4 = mR$
 $\therefore V_o = m(V_1 - V_2)$

under this condition this is
a difference amplifier ✘


V_1 }
 V_2 } signals
 from
 sensors
 which
 is
 low in
 value

$$V_o = m(V_1 - V_2)$$

amplification factor
« gain »

Example Consider the op amp configuration below.

Assume $V_{in} = 5 \text{ V}$

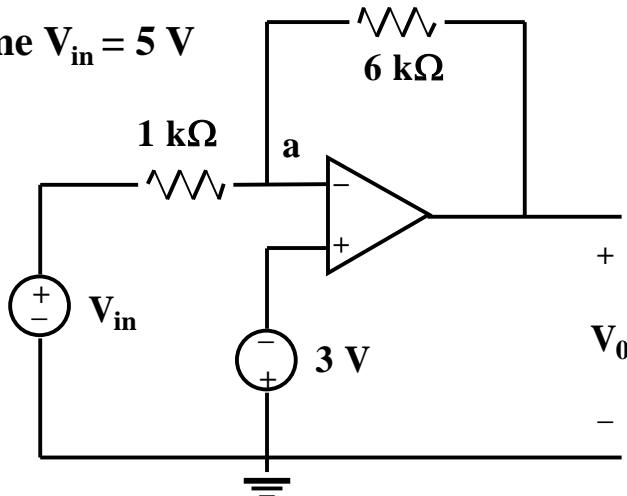


$$V_o = \left(1 + \frac{6k}{1k}\right)(-3) - \left(\frac{6k}{1k}\right)(5)$$

$$= -21 - 30 = -51 \text{ V}$$

Since $V_o = -51 \text{ V}$ (op amp will saturate and V_o will be limited to $-V_{sat}$)

Instrumentation Amplifier

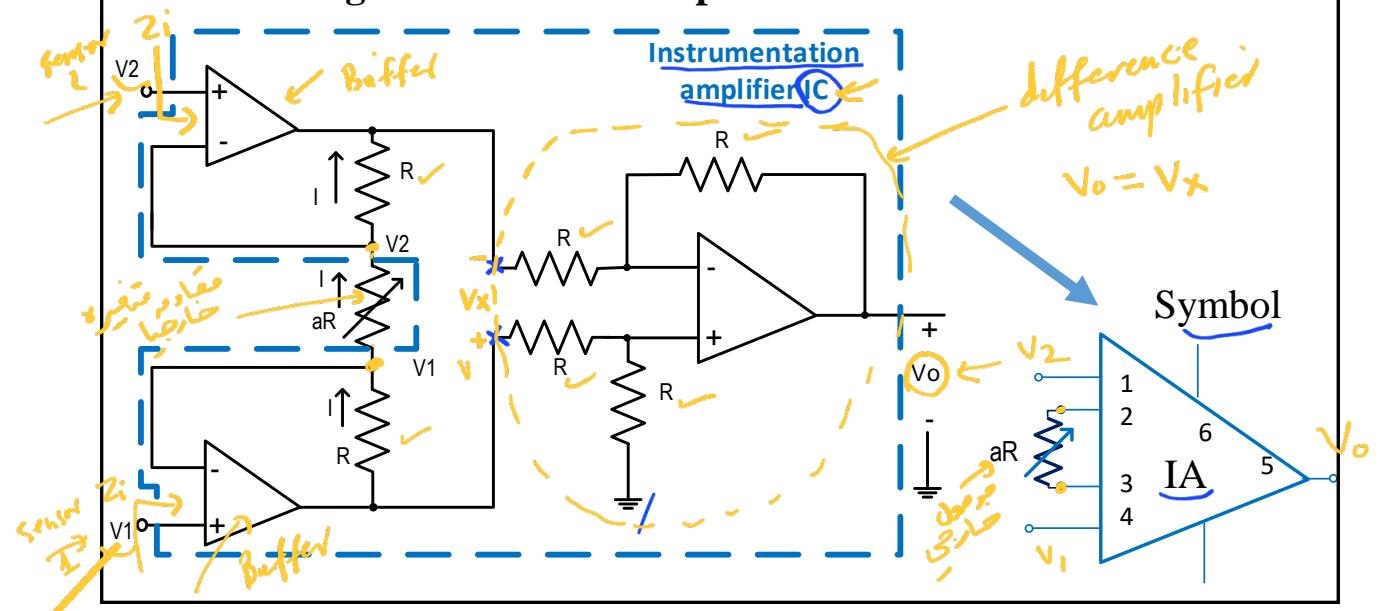- The previous difference amplifier has low input impedance and it is difficult to vary the gain "m"
- The instrumentation amplifier solves this problem by adding a buffer stage and a difference amplifier stage to solve the disadvantages of difference amplifier



$$V_x = I(R + aR + R)$$

$$V_x = I(2R + aR) = I(2 + a)R$$

$$\frac{I}{a} = \frac{V_1 - V_2}{aR}$$


$$V_x = \frac{V_1 - V_2}{aR}(2 + a)R$$

$$= (V_1 - V_2)(2 + a)$$

$$Vo = V_x = (V_1 - V_2)(1 + \frac{2}{a})$$

Instrumentation Amplifier

assume $V_1 > V_2$

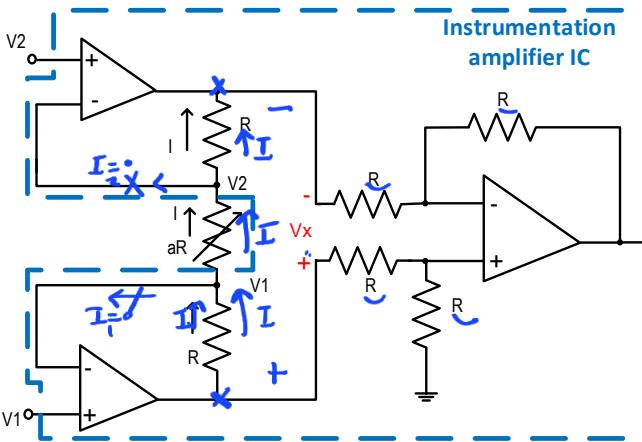

$$I = \frac{V_1 - V_2}{aR}$$

$$V_x = (R + R + aR)V_1 - V_2$$

$$V_x = (R + R + aR)\frac{V_1 - V_2}{aR}$$

$$V_x = \left(\frac{(2+a)R}{aR}\right)(V_1 - V_2)$$

$$V_x = \left(1 + \frac{2}{a}\right)(V_1 - V_2)$$

for $m = 1$


$$V_o = V_x = \left(1 + \frac{2}{a}\right)(V_1 - V_2)$$

- Only by varying the value of potentiometer aR , the output can be adjusted
- R is an internal resistance given in data sheet of "IA" IC

L24 19/8/2021

Instrumentation Amplifier "IA"
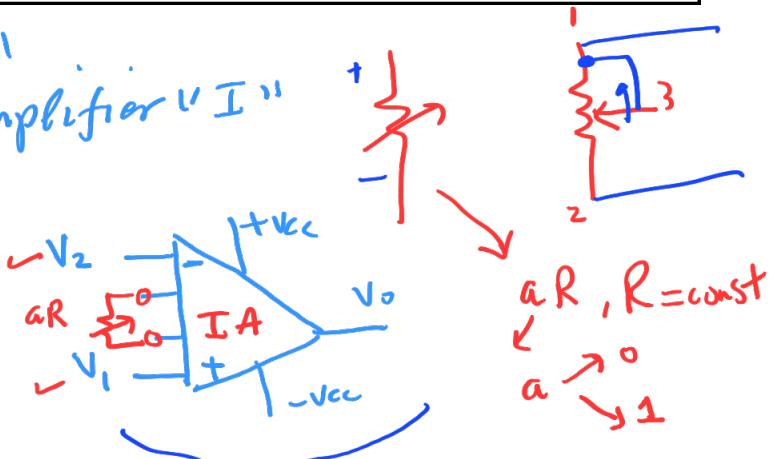
$$V_o = \left(1 + \frac{2}{a}\right)(V_1 - V_2)$$



Wheatstone
Bridge

Example: Instrumentation Amplifier (self study)


$$V_o = \boxed{V_x = \left(1 + \frac{2}{a}\right)(E_1 - E_2)}$$

$$E_1 = \frac{R_1}{R_1 + R_1} E = \frac{1}{2} E$$

$$E_2 = \frac{R_x}{R_x + R_x + \Delta R_x} E$$

$$E_1 - E_2 = \frac{1}{2} E - \frac{R_x}{2R_x + \Delta R_x} E$$
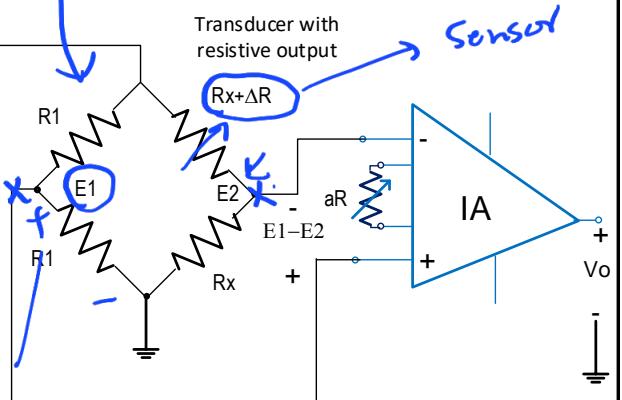
$$= \frac{2R_x + \Delta R_x}{2(2R_x + \Delta R_x)} E - \frac{2R_x}{2(2R_x + \Delta R_x)} E$$



$$E_1 - E_2 = \frac{E}{2} \left(\frac{2R_x + \Delta R_x - 2R_x}{2R_x + \Delta R_x} \right)$$

$$= \frac{E}{2} \left(\frac{\Delta R_x}{2R_x + \Delta R_x} \right)$$

Instrumentation Amplifier

assume $\Delta R_x \ll R_x$



$$V_o = E_1 - E_2 = \left(1 + \frac{2}{a}\right)(E_1 - E_2)$$

$$V_o \propto \Delta R_x = \left(1 + \frac{2}{a}\right) \frac{E}{4R_x} (\Delta R_x)$$

let $R_1 = 10k$; $E = 10V$; $\Delta R_x = 10$;

$$aR = 50.12 \text{ ohm}$$

(potentiometer is set to 50.12 ohms)

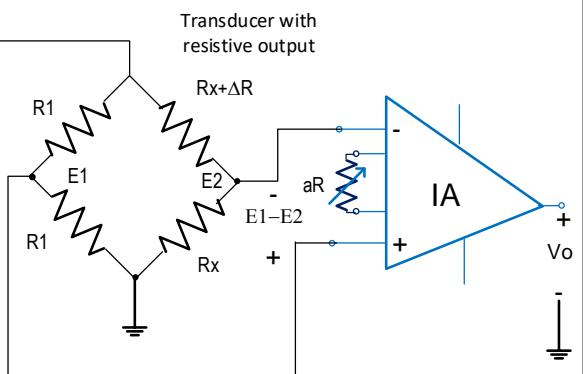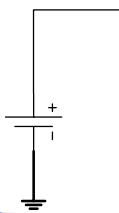

$$a = \left(\frac{aR}{R}\right) = \left(\frac{50.12}{10000}\right) = 0.005013$$

$$\left(1 + \frac{2}{a}\right) = 400$$

$$V_o = (400) \left(\frac{10}{4}\right) * \frac{10}{10000} = 1V$$


Example: Use an instrumentation amplifier in order to get an output $V_o = 5V$ if $V_1 = 15mV$ (sensor 1), $V_2 = 5mV$ (sensor 2) & given that internal IA resistance = $20k\Omega$

$$V_o = \left(1 + \frac{2}{a}\right)(V_1 - V_2)$$


$$5 = \left(1 + \frac{2}{a}\right)(15mV - 5mV)$$

$$5 = \left(1 + \frac{2}{a}\right)(10mV)$$
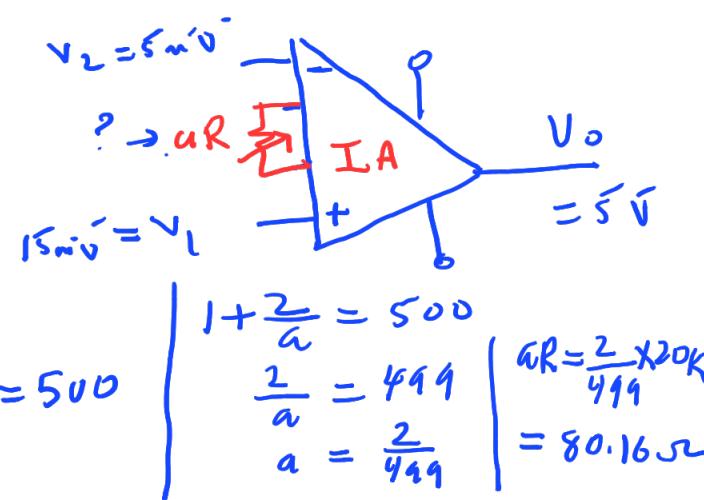
$$1 + \frac{2}{a} = \frac{5V}{10mV} = \frac{500mV}{10mV} = 500$$



Voltage to Current converter

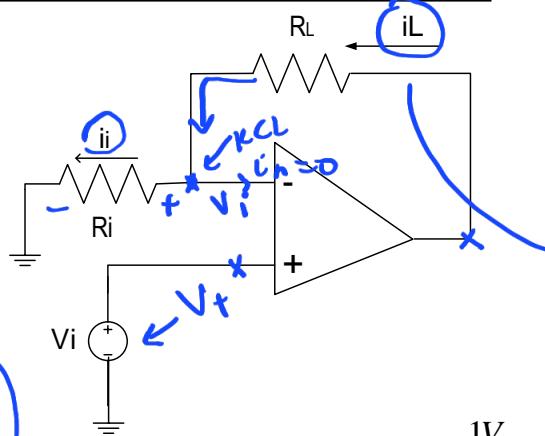

$$i_i = \frac{V_i}{R_i}$$

$$i_i = i_L$$

let $V_i = 1V; R_i = 1k$

$$i_L = \frac{1V}{1k} = +1mA$$

$$V_+ = V_- \\ i_p = i_n = 0$$

replace R_L by current measuring Device



PMMC
 $\pm 1mA = I_M$

$$i_L = \frac{1V}{1k} = +1mA$$

$$\text{let } V_i = -1V; R_i = 1k$$

$$i_L = \frac{-1V}{1k} = -1mA$$



Here we converted $\pm 1V$ to $\pm 1mA$

Voltage to Current converter

PMMC: Permanent magnet moving coil

$$i_i = \frac{V_i}{R_i}$$

$$i_i = i_m$$

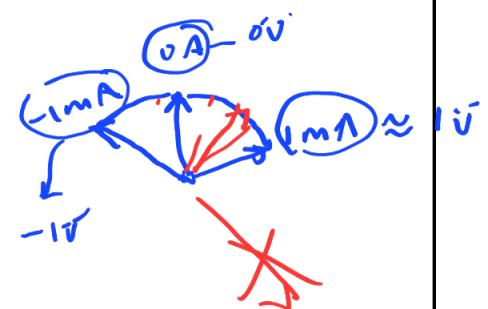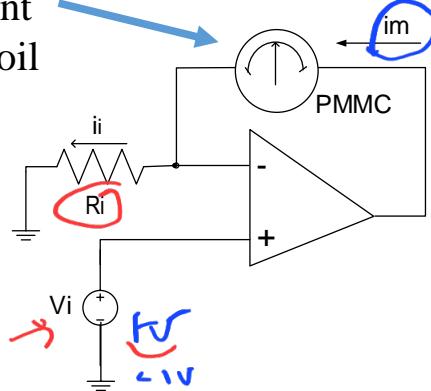


let $V_i = \pm 1V$; $R_i = 1k$

$$i_m = \frac{1V}{1k} = \pm 1mA$$



Current to Voltage converter

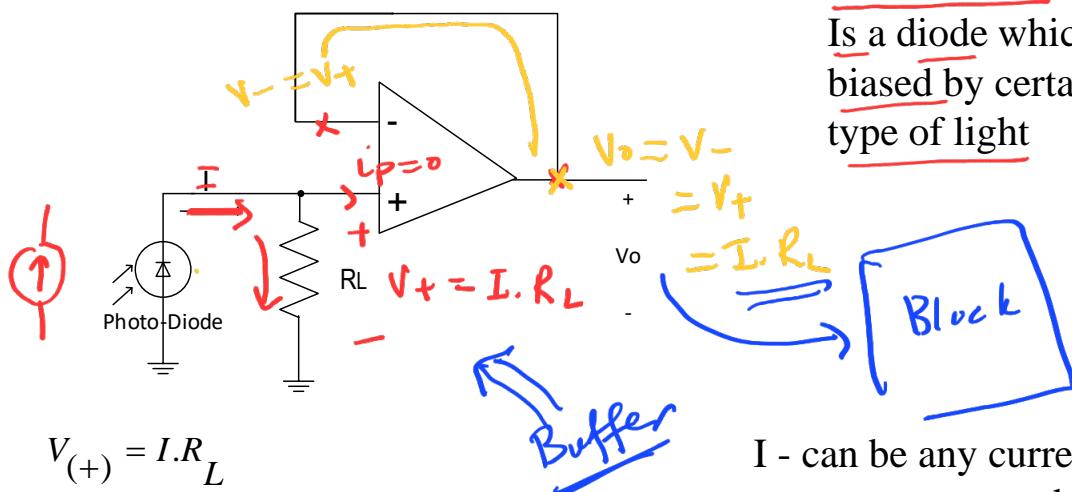


Here we converted current I to voltage V_o

Photo-diode


Is a diode which is biased by certain type of light

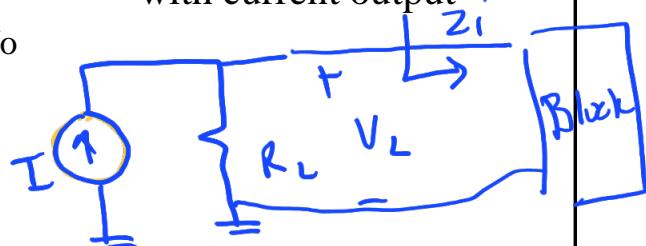I - can be any current source, sensor or device with current output




So far ; Circuits with Negative feedback

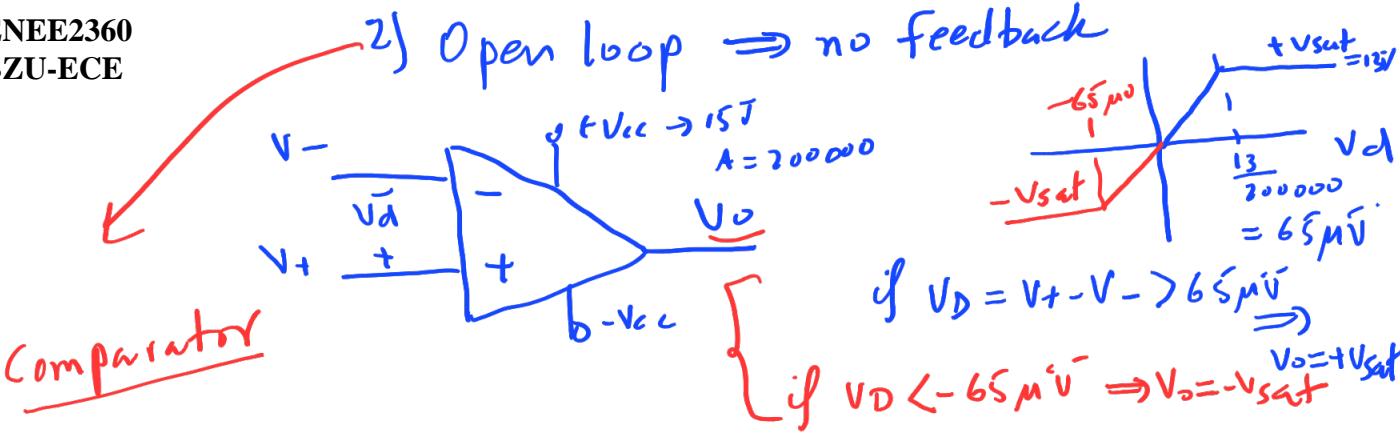- inverting
 - non-inverting
 - Difference
 - Instrumentation
 - Voltage to current
 - current to voltage
-] Amplifiers
-] converters



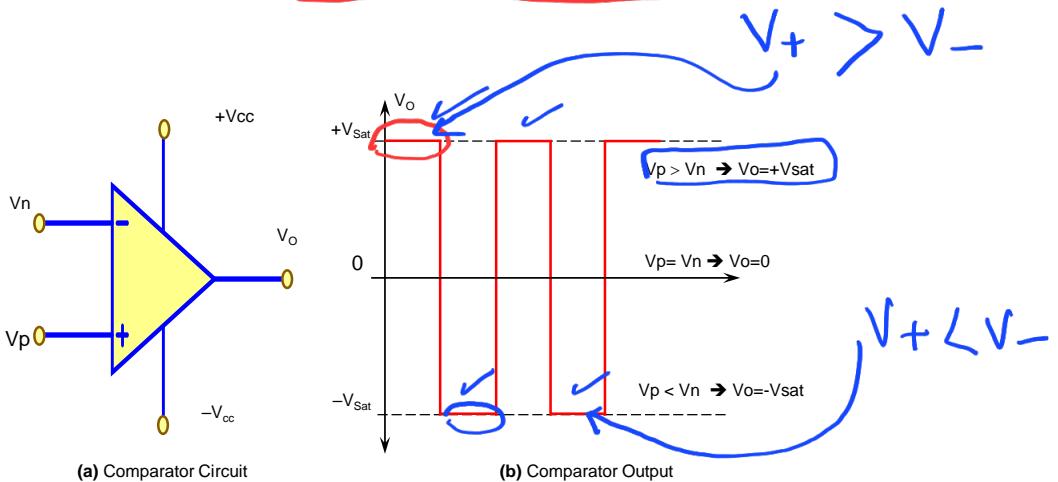OP AMP as a Comparator (compares 2 voltages and produces a signal to indicate which is greater)




Applications of Comparators

- Analog to digital converters (ADC)
- Counters (e.g. count pulses that exceed a certain voltage level).
- Cross Over Detectors


comparator

$$V_+ > V_- \Rightarrow V_o = +V_{sat}$$

$$V_+ < V_- \Rightarrow V_o = -V_{sat}$$

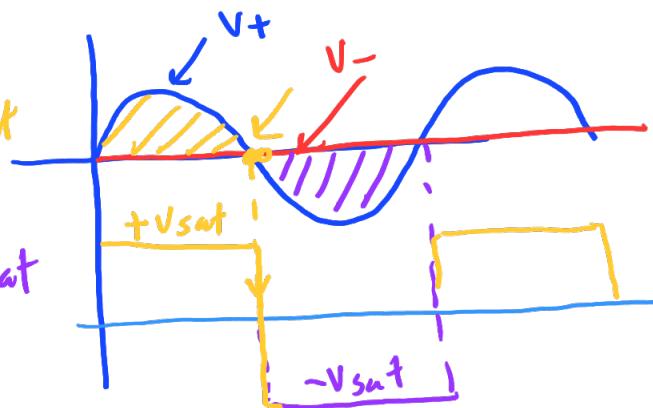


Comparator : Zero -Level detector

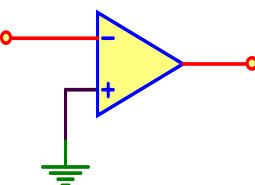

Exact analysis:

When $v_d > 65\mu V$; $V_o = +V_{sat}$

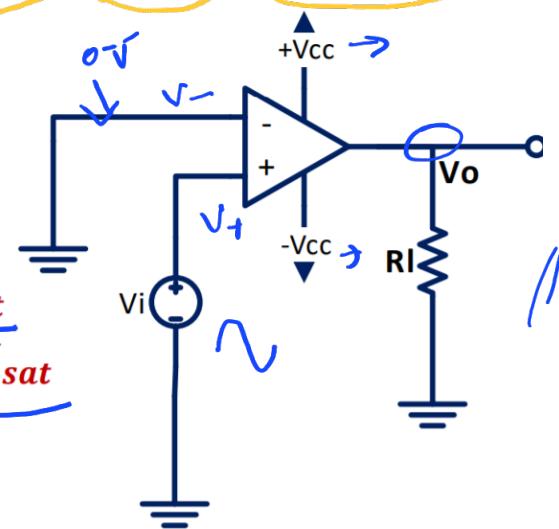When $v_d < -65\mu V$; $V_o = -V_{sat}$ or



Approximate analysis

When $v_d > 0V$; $V_o = +V_{sat}$

When $v_d < 0V$; $V_o = -V_{sat}$



$$v_d = V_+ - V_- \Rightarrow V_+ > V_-$$

$$\Rightarrow V_+ < V_-$$

Comparator : Zero –Level detector

$$V_i(t) = 5 \sin \omega t \text{ v}$$

$$\pm V_{sat} = \pm 13 \text{ v}$$

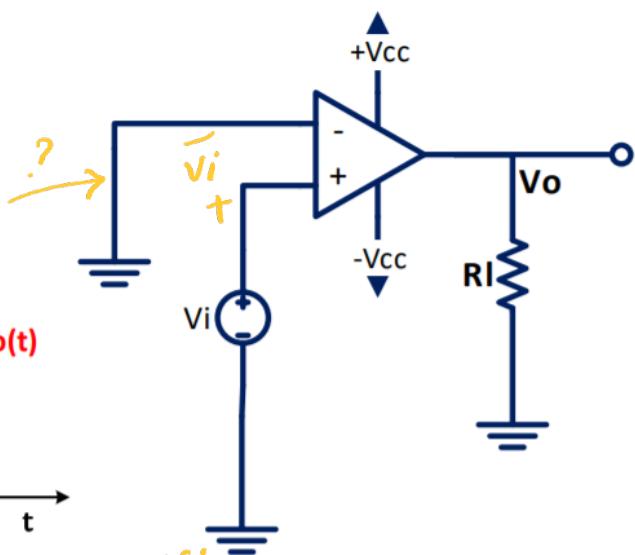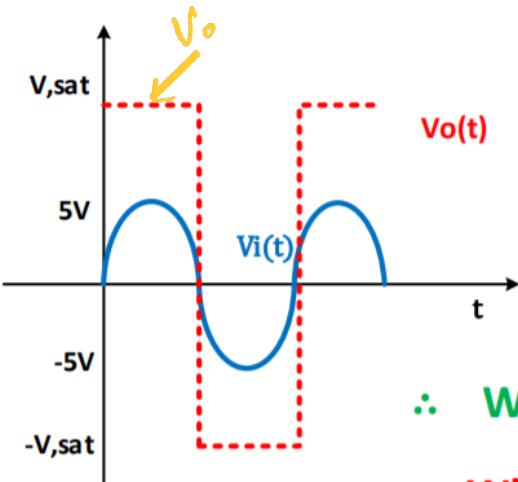

∴ When $V_i > 0V$; $V_o = +V_{sat}$

∴ When $V_i < 0V$; $V_o = -V_{sat}$

Non Zero -Level detector

$$V_i(t) = 5 \sin \omega t \text{ v}$$



$$\pm V_{sat} = \pm 13 \text{ v}$$

When $V_i > 2\text{V}$;

$$V_o = +V_{sat}$$

When $V_i < 2\text{V}$;

$$V_o = -V_{sat}$$

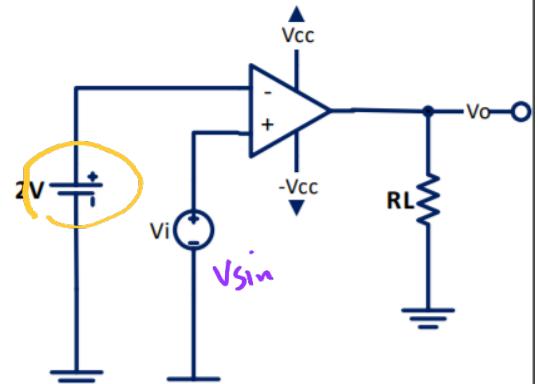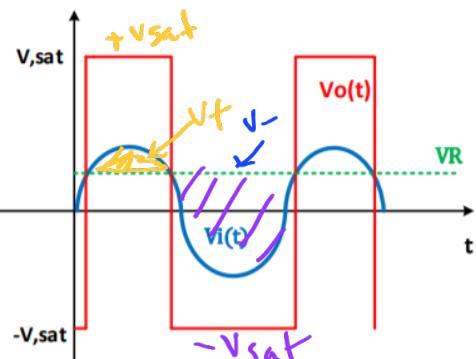

$$V_{sin} - 2 > 0 \rightarrow V_{sin} > 2$$


When $v_d > 0\text{V}$; $V_o = +V_{sat}$

When $v_d < 0\text{V}$; $V_o = -V_{sat}$

$$V_{sin} - 2 < 0 \rightarrow V_{sin} < 2$$


Practical Non Zero -Level detector

Application

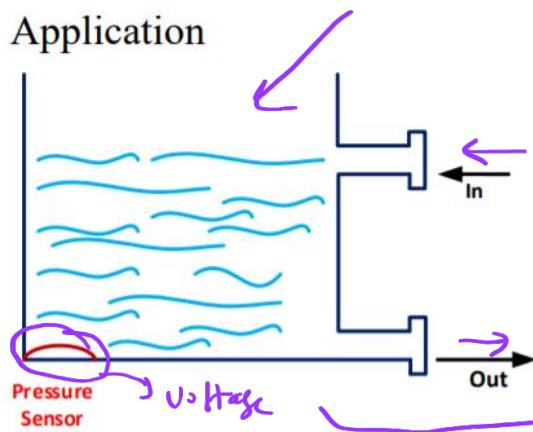

The pressure sensor generates a voltage proportional to the water level in the tank

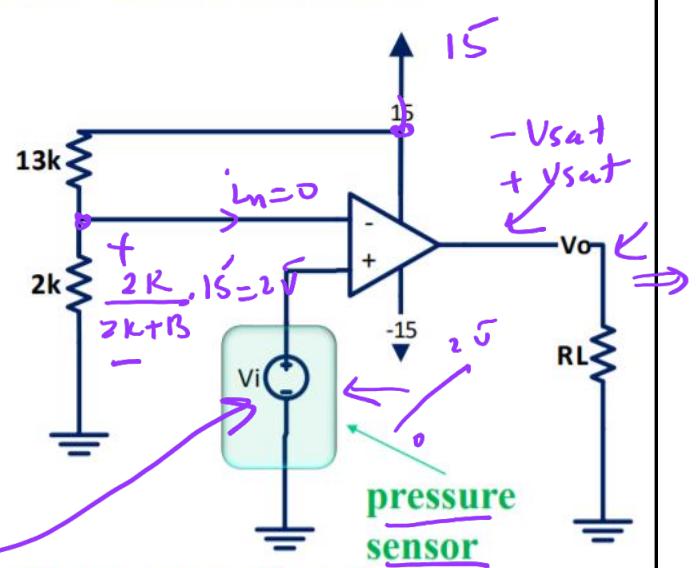When water level reaches the maximum allowable lever
→ $V_i = 2V$



$$V(-) = 2V$$

When $V_i > 2V$; $V_o = +V_{sat}$

When $V_i < 2V$; $V_o = -V_{sat}$

Voltage-Level detector with LEDs:

When $V_i > 2V$; $V_o = +V_{sat}$

\therefore Red LED is ON

\therefore green LED is OFF


When $V_i < 2V$; $V_o = -V_{sat}$

\therefore green LED is ON

$\checkmark \therefore$ Red LED is OFF

When $V_i = 2V$; $V_o = 0$

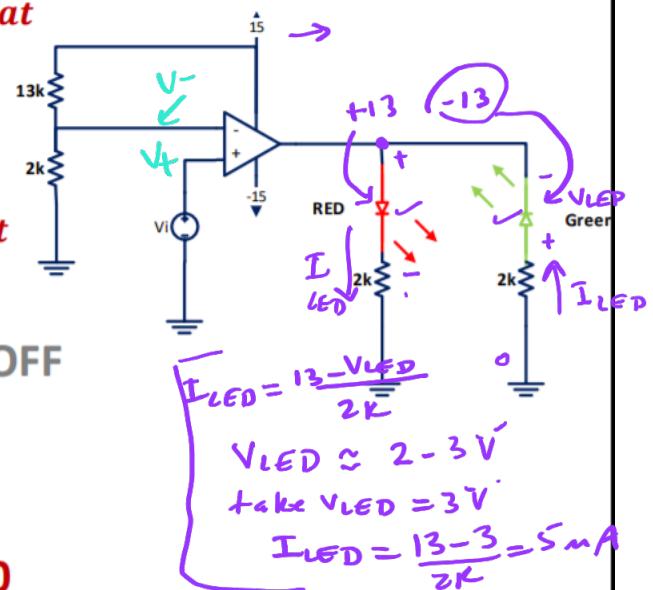\therefore green LED and the Red LED are OFF



Example

- Given how an op amp functions, what do you expect V_o to be if $v_2 = 5V$ when:

1. $V_s = 0V$?


Answer $V_o = +V_{sat}$

2. $V_s = 5V$?


Answer $V_o = 0$ (practically impossible to have both $V_1 = V_2$)

3. $V_s = 6V$?


Answer $V_o = -V_{sat}$

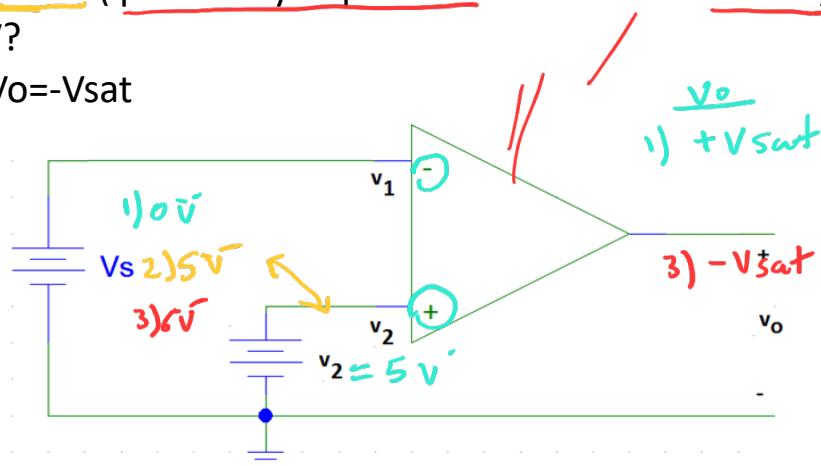


OP-AMP CONFIGURATIONS

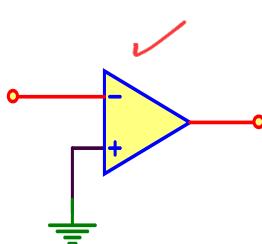

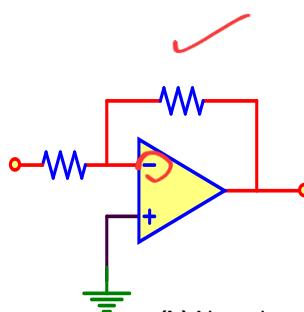(a) No Feedback
(open loop
comparator circuit)



(b) Negative
Feedback

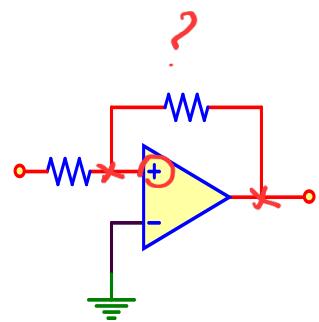

(c) Positive Feedback

- No feedback : Open loop (used in comparators)
- Negative feedback : Feedback to the inverting input (Used in amplifiers)
- Positive feedback : Feedback to the non inverting input (Used in oscillators) and Schmitt triggers (comparators with hysteresis)

a **Schmitt trigger** is a comparator circuit with hysteresis,


Schmitt trigger devices are typically used in signal conditioning applications to remove noise from signals used in digital circuits, particularly mechanical switch bounce.

They are also used in closed loop negative feedback configurations to implement relaxation oscillators, used in function generators and switching power supplies.

The output of a Schmitt trigger (B) and a comparator (A), when a noisy signal (U) is applied.

The green dotted lines are the circuit's switching thresholds.

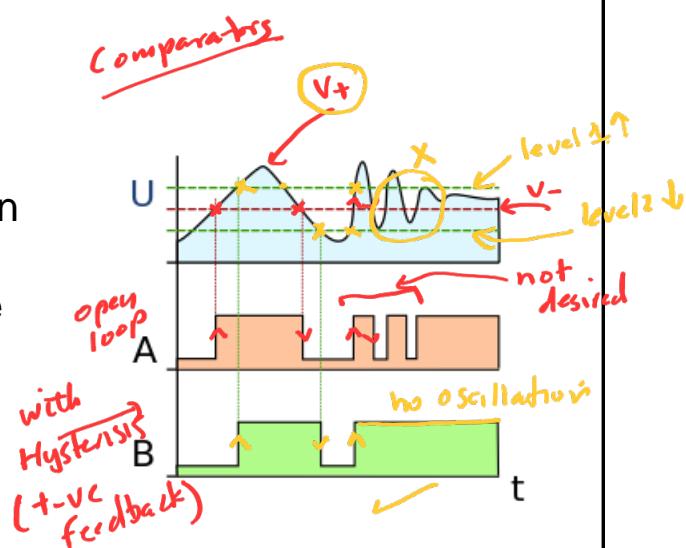The Schmitt trigger tends to remove noise from the signal.



comparator with hysteresis

Schmitt trigger,

This is a comparator circuit
and the output is $V_o = \pm V_{sat}$

Analysis: step 1

let $V_o = +V_{sat}$

$$V_+ = \frac{R_2}{R_1 + R_2} (+V_{sat}) = V_{UT} - \text{upper threshold voltage}$$

in order for V_o to be $+V_{sat}$


$$V_d > 0$$

$$V_d = V(+)-V(-) > 0$$


$$\frac{R_2}{R_1 + R_2} + V_{sat} > V_i$$

$$\text{when } V_{UT} > V_i \Rightarrow V_o = +V_{sat}$$

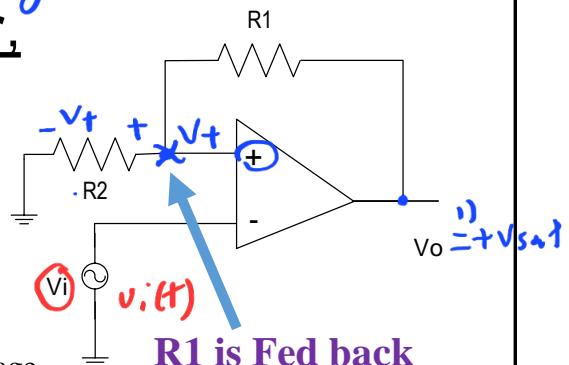
$$\text{But when } V_i > V_{UT} \Rightarrow V_o \text{ switches to } -V_{sat}$$



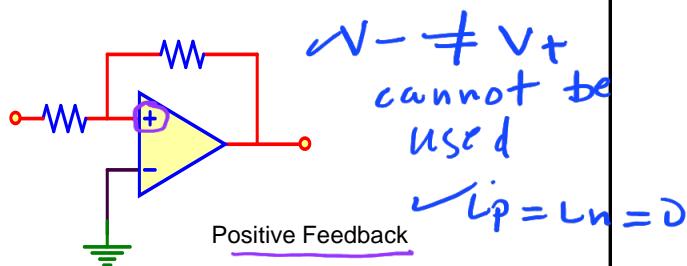R1 is Fed back from output to (+) input
This is called positive feedback




1) let $V_o = +V_{sat}$

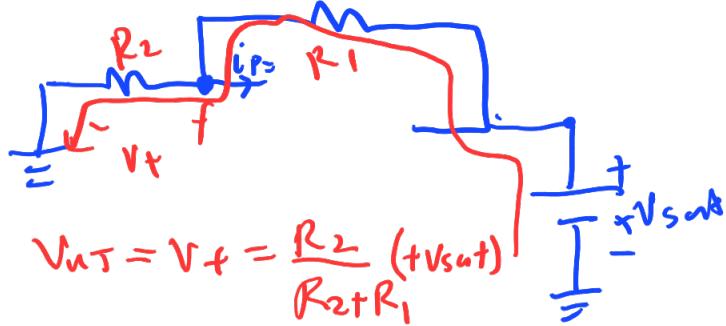

if $V_+ > V_-$

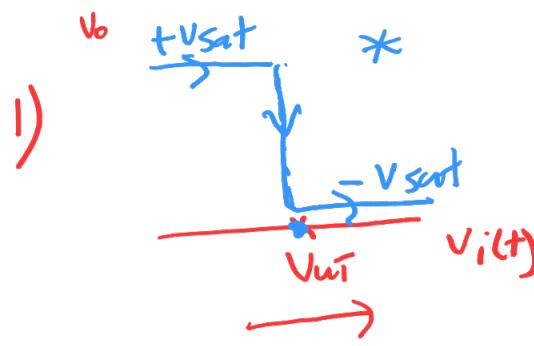$V_{UT} > V_i(t) \Rightarrow V_o = +V_{sat}$
 → as long as $V_i(t) < V_{UT}$
 $V_o = +V_{sat}$
 → if $V_i(t)$ increases such that $V_i(t) > V_{UT}$
 $V_o = -V_{sat}$



Schmitt trigger,

Analysis: step 2

let $V_o = -V_{sat}$

$$V_+ = \frac{R_2}{R_1 + R_2} (-V_{sat}) = V_{LT} \quad \text{- Lower threshold voltage}$$

in order for V_o to be $-V_{sat}$


$$V_d < 0$$

$$V_d = V(+) - V(-) < 0$$

$$\frac{R_2}{R_1 + R_2} - V_{sat} < V_i$$

when $V_i < V_{LT} \Rightarrow V_o = -V_{sat}$

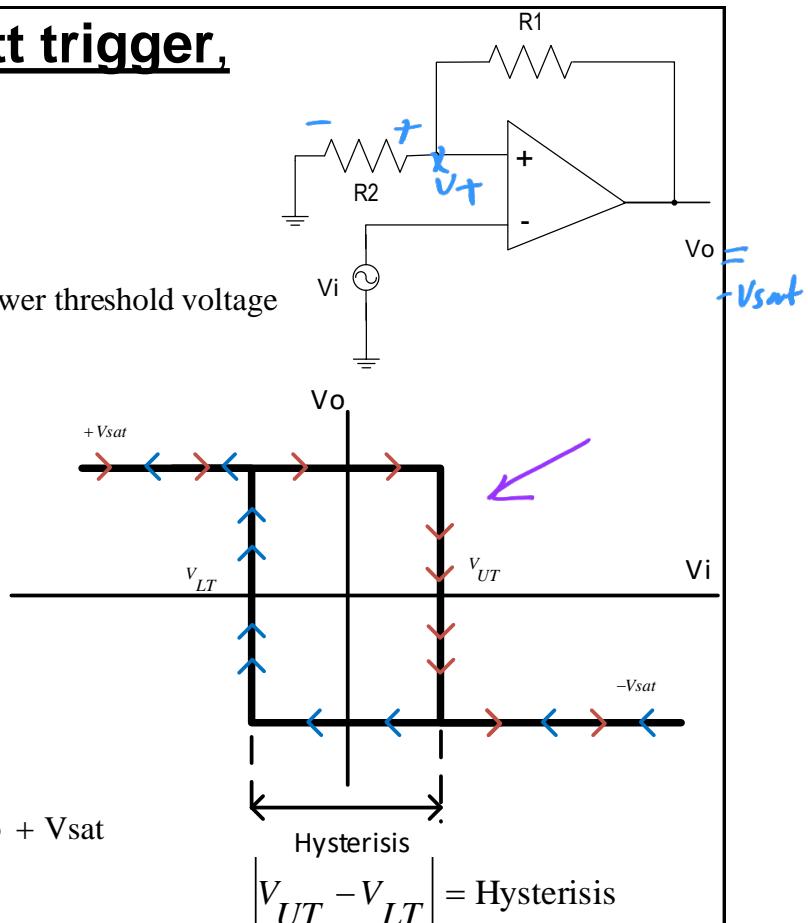But when $V_i < V_{LT} \Rightarrow V_o$ switches to $+V_{sat}$





$$V_+ - V_- < 0 \Rightarrow V_o = -V_{sat}$$



$$V_{LT} - V_{i(t)} < 0 \Rightarrow V_{LT} < V_{i(t)}$$

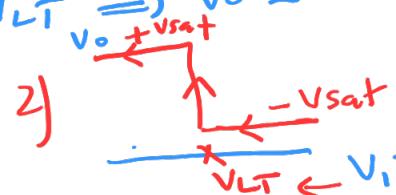- as long as $V_{i(t)} > V_{LT} \Rightarrow V_o = -V_{sat}$
- if $V_{i(t)}$ decreases below $< V_{LT} \Rightarrow V_o = +V_{sat}$



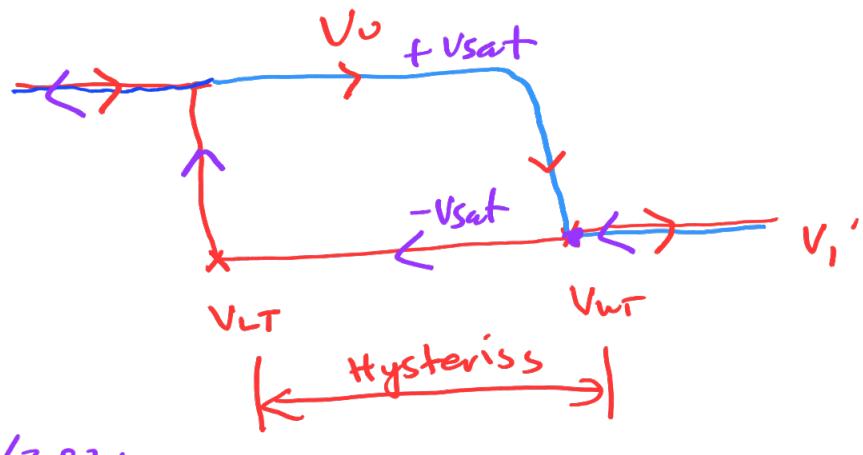

Schmitt trigger,

Example: Find and sketch $V_o(t)$ and the plot of $V_o = f(V_i)$

Solution: this is a Schmitt trigger and

$$\therefore V_o = \pm V_{sat}$$

$$1) \text{ let } V_o = +V_{sat} = 10V$$

in order for V_o to be $+V_{sat}$

$$V_d > 0$$

$$V_d = V(+) - V(-) > 0$$



$$V(+) > V(-)$$

$$V(-) = 4V$$

superposition

$$V(+) = \frac{100k}{(2700 + 100)k} (+V_{sat}) + \frac{2700k}{(2700 + 100)k} (V_i)$$
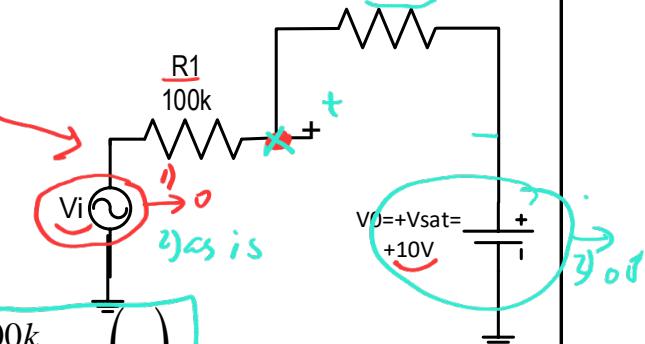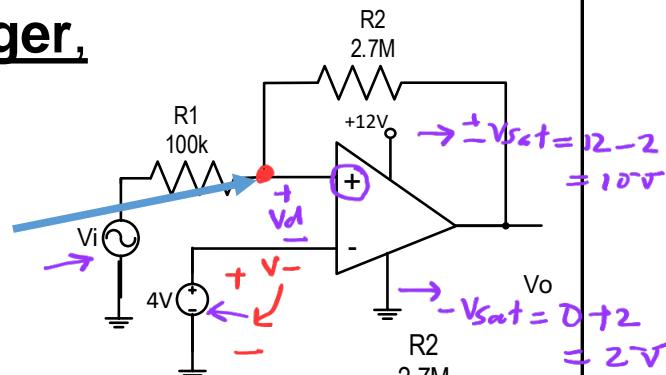
$$= \frac{100k}{(2700 + 100)k} (10) + \frac{2700k}{(2700 + 100)k} (V_i) > 4V$$



$V_i(t) \rightarrow \text{charging voltage}$

Find V_i ?

V_+ V_-

$$\frac{100k}{(2700+100)k}(10V) + \frac{2700k}{(2700+100)k}(V_i) > 4V$$

$$(V_i) > \left[4V - \left(\frac{100k}{(2700+100)k}(10V) \right) \right] \left[\frac{(2700+100)k}{2700k} \right] \Rightarrow V_i > 3.777V$$

when $V_i > 3.777 \Rightarrow V_o = +Vs_{sat}$; But when $V_i < 3.777 \Rightarrow V_o$ switches to $-Vs_{sat}$

2) let $V_o = -Vs_{sat} = (0 + 2) = 2V$


in order for V_o to be $-Vs_{sat}$ $\Rightarrow V_d < 0$; $\therefore V(+)<V(-)$


$$V(+) = \frac{100k}{(2700+100)k}(-Vs_{sat}) + \frac{2700k}{(2700+100)k}(V_i)$$

$$\frac{100k}{(2700+100)k}(-Vs_{sat}) + \frac{2700k}{(2700+100)k}(V_i) < 4V$$

$$(V_i) < \left[4V - \left(\frac{100k}{(2700+100)k}(2V) \right) \right] \left[\frac{(2700+100)k}{2700k} \right] \Rightarrow V_i < 4.074V$$

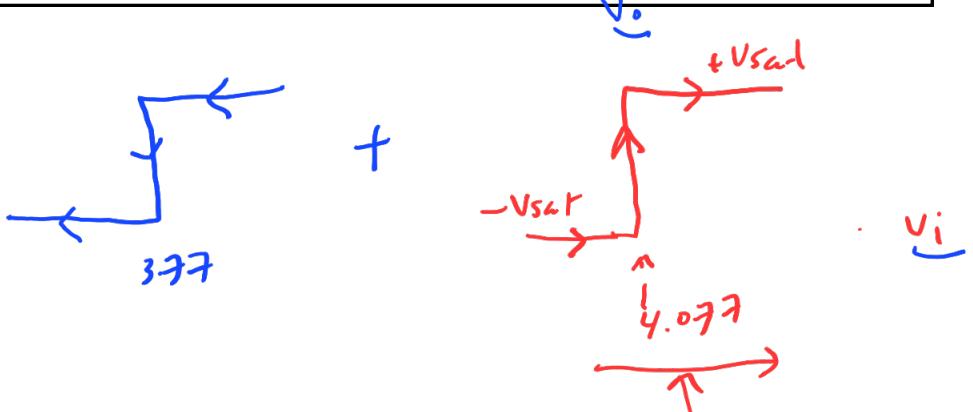when $V_i < 4.074V \Rightarrow V_o = -Vs_{sat}$; But when $V_i > 4.074V \Rightarrow V_o$ switches to $+Vs_{sat}$



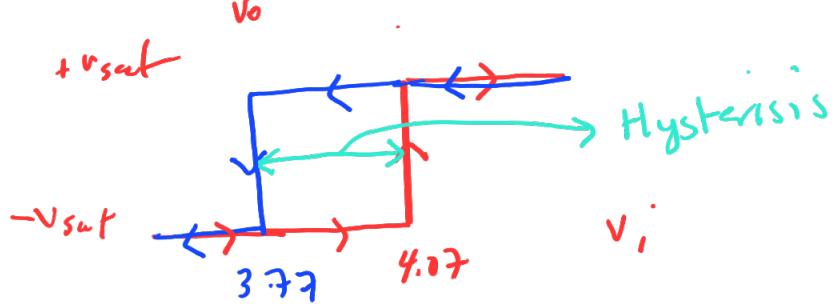


Conclusion

1) when V_i is decreasing , as long as V_i is $> 3.777V \Rightarrow V_o = +Vs_{sat}$;

but when V_i becomes $< 3.777 \Rightarrow V_o$ switches to $-Vs_{sat}$

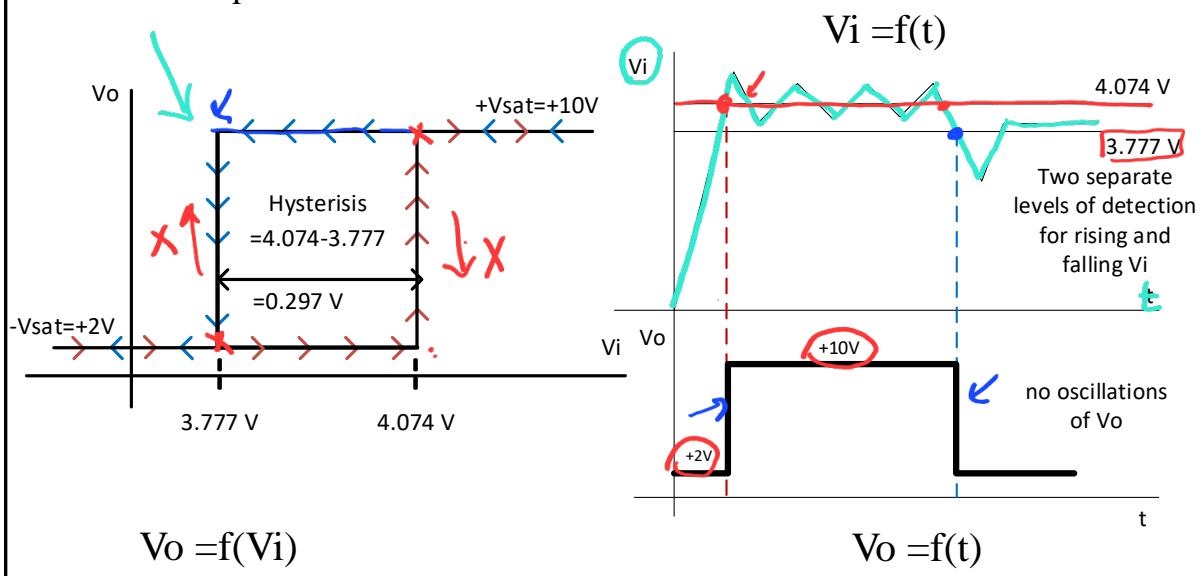2) when V_i is increasing , as long as V_i is $< 4.074V \Rightarrow V_o = -Vs_{sat}$;

but when V_i becomes $> 4.074 \Rightarrow V_o$ switches to $+Vs_{sat}$



Comparator without Hysteresis

Example: Find and sketch $V_o(t)$ and the plot of $V_o = f(V_i)$

Solution: this is a comparator and

$$V_o = \pm V_{sat}$$

1) in order for V_o to be $+ V_{sat}$

$$V_d > 0 \text{ and } V_d = V(+) - V(-) > 0$$

$$V(+) > V(-)$$

$$V(-) = 4V; V(+) = V_i$$



$$V_i > 4V$$

2) in order for V_o to be $- V_{sat} = 2V$

$$V_d < 0 \text{ and } V_d = V(+) - V(-) < 0$$

$$V(+) < V(-)$$

$$V_i < 4V$$

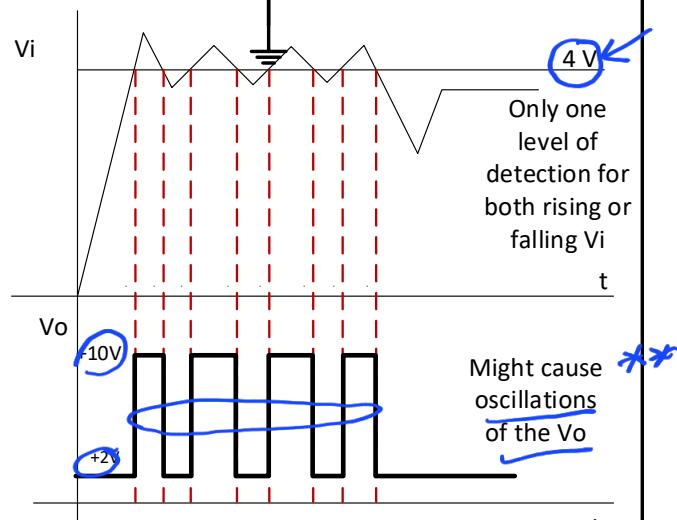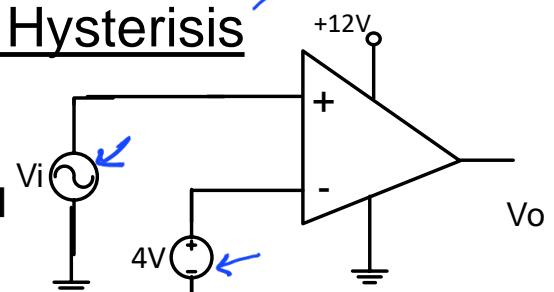

$$\rightarrow i_c(t) = C \frac{dV_c(t)}{dt}$$

Integrator $V_o \propto \int V_i(t)$ \rightarrow time domain


- So far, the input and feedback components have been resistors. If the feedback component used is a capacitor, the resulting connection is called an *integrator*.
- Recall that virtual ground means that we can consider the voltage at the junction of R and X_c to be ground (since $V_+ = 0$ V) but that no current goes into ground at that point.

$$i_i = i_f = \frac{V_i}{R} \leftarrow i_c = C \frac{dV_c(t)}{dt}$$

$$V_c(t) = \frac{1}{C} \int i_f(t) dt$$

$$V_o = -V_c(t) \quad \text{const}$$
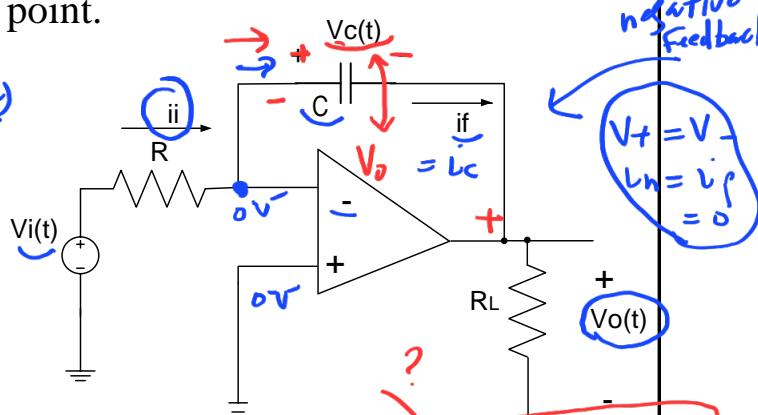
$$V_o = -\frac{1}{C} \int_0^t \frac{V_i(t)}{R} dt = -\frac{1}{RC} \int_0^t V_i(t) dt$$



$$i_c(t) = C \frac{dV_c(t)}{dt} = \frac{V_i(t)}{R}$$

Differentiator → time domain


A differentiator ,while not as useful as the circuit forms covered above, the differentiator does provide a useful operation, the resulting relation for the circuit being


$$i_i = i_f = i_C = C \frac{dV_i(t)}{dt}$$

$$V_C(t) = \frac{1}{C} \int_0^t i_f(t) dt$$


$$V_o = -i_f(t)R$$
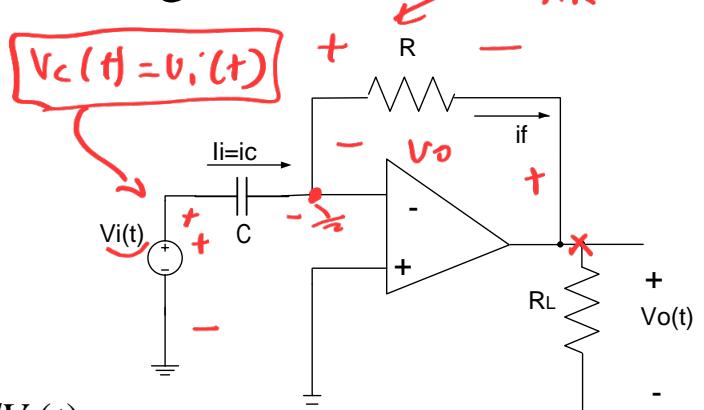
$$V_o = - \left(C \frac{dV_i(t)}{dt} \right) R = -RC \frac{dV_i(t)}{dt}$$



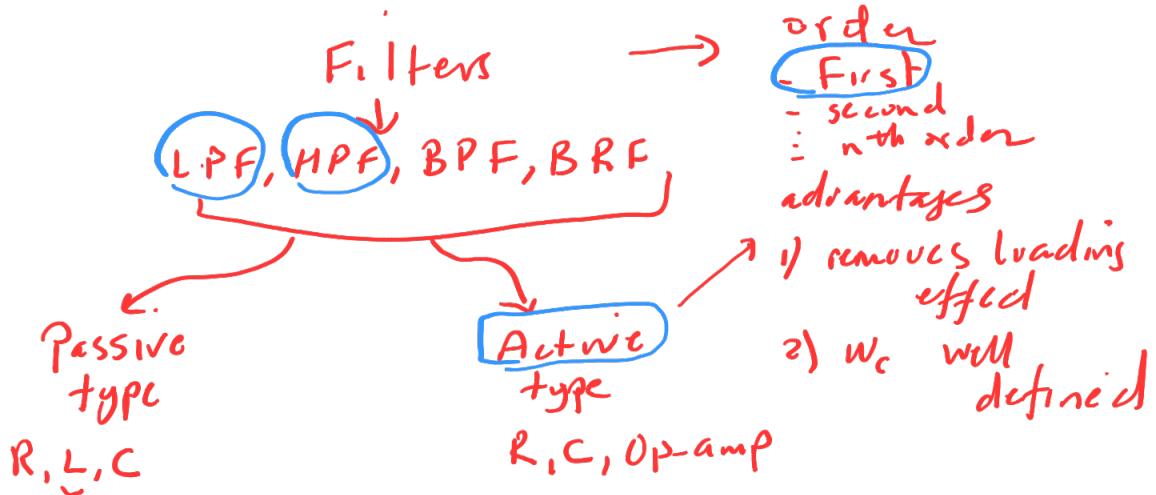

The Active Low-pass Filter

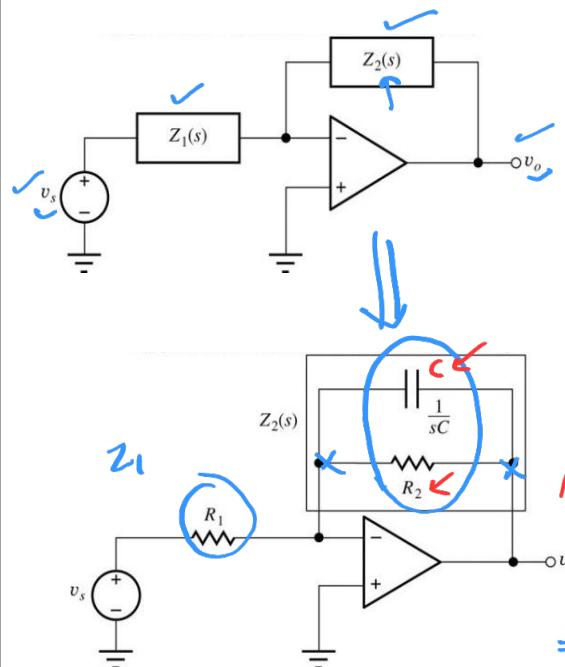

The gain analysis of this inverting amplifier. Note $s = j\omega$.

$$A_v = \frac{\tilde{v}_o(j\omega)}{\tilde{v}_s(j\omega)} = -\frac{Z_2(j\omega)}{Z_1(j\omega)} \quad Z_1(j\omega) = R_1$$

$$Z_2(j\omega) = \frac{1}{R_2 j\omega C} = \frac{R_2}{j\omega C R_2 + 1}$$

$$A_v = -\frac{R_2}{R_1 (1 + j\omega C R_2)}$$

$$A_v = \frac{-K}{1 + j\omega / \omega_c}$$

$$\omega_c = 2\pi f_c = \frac{1}{R_2 C} \therefore f_c = \frac{1}{2\pi R_2 C}$$

& cut-off frequency:

ω
rad/sec
 f (hertz)

$\omega \rightarrow f ?$

$$\omega = 2\pi f$$

$$\omega_c = 2\pi f_c$$

take the Magnitude $\rightarrow A_v = \frac{-K}{1 + j\omega / \omega_c}$ ← complex number
phasor representation

$| \text{mag} | \angle \text{phase} \text{ or}$

exponential

Assume $K=1$

phase



$$|Av| = \frac{1}{\sqrt{1+(\frac{\omega}{\omega_c})^2}} = \frac{1}{\sqrt{1+(\frac{\omega}{\omega_c})^2}}$$

$$\omega_c = \frac{1}{R_2 C} \leftarrow \text{known}$$

$$|Av(j\omega)| \rightarrow \text{drawing}$$

ω

Frequency Response (Bode Plot)


→ log scale ω
→ Decibel scale $| |$

Magnitude Plot (Magnitude in decibels vs log of frequency)

$$A_{dB} = 20 \log |H(j\omega)| = \frac{K}{\sqrt{1+(\frac{\omega}{\omega_c})^2}}$$

$$|H(j\omega)| = |A_v(j\omega)|$$

$$|A_v(j\omega)| = \frac{K}{\sqrt{1+(\frac{\omega}{\omega_c})^2}}$$

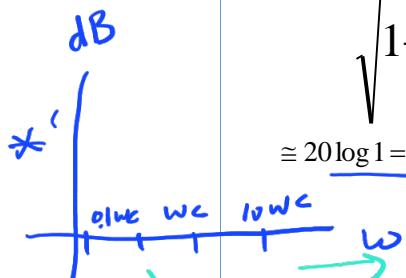

at $\omega = 0.1\omega_c$

$$20 \log \frac{1}{\sqrt{1+(\frac{0.1\omega_c}{\omega_c})^2}} = 20 \log \frac{1}{\sqrt{1+0.01}} \approx 20 \log 1 = 0 \text{dB}$$

at $\omega = \omega_c$

$$20 \log \frac{1}{\sqrt{1+(\frac{\omega_c}{\omega_c})^2}} = 20 \log \frac{1}{\sqrt{1+1}} = \frac{V_o}{V_{in}} = 0.707$$

$$= 20 \log 0.707 = -3 \text{dB}$$

at $\omega = 10\omega_c$

$$20 \log \frac{1}{\sqrt{1+(\frac{10\omega_c}{\omega_c})^2}} = 20 \log \frac{1}{\sqrt{1+100}} = 20 \log 0.1 = -20 \text{dB}$$

cut-off frequency \equiv corner frequency $\equiv -3 \text{dB}$ frequency

@ $\omega = 100\omega_c$



$$= \frac{1}{\sqrt{1+(100)^2}}$$

$$= 20 \log 100 = -40 \text{dB}$$

ω	$ Av $	$= \frac{V_o}{V_i} \Rightarrow V_o = V_i \times Av$
$0.1\omega_c$	0 dB	
ω_c	-3 dB	
$10\omega_c$	-20 dB	0.1
$100\omega_c$	-40 dB	$0.01 = 0.5 \sin \omega t$

$$V_i = 5 \sin 1000t$$

$$V_o = ?$$

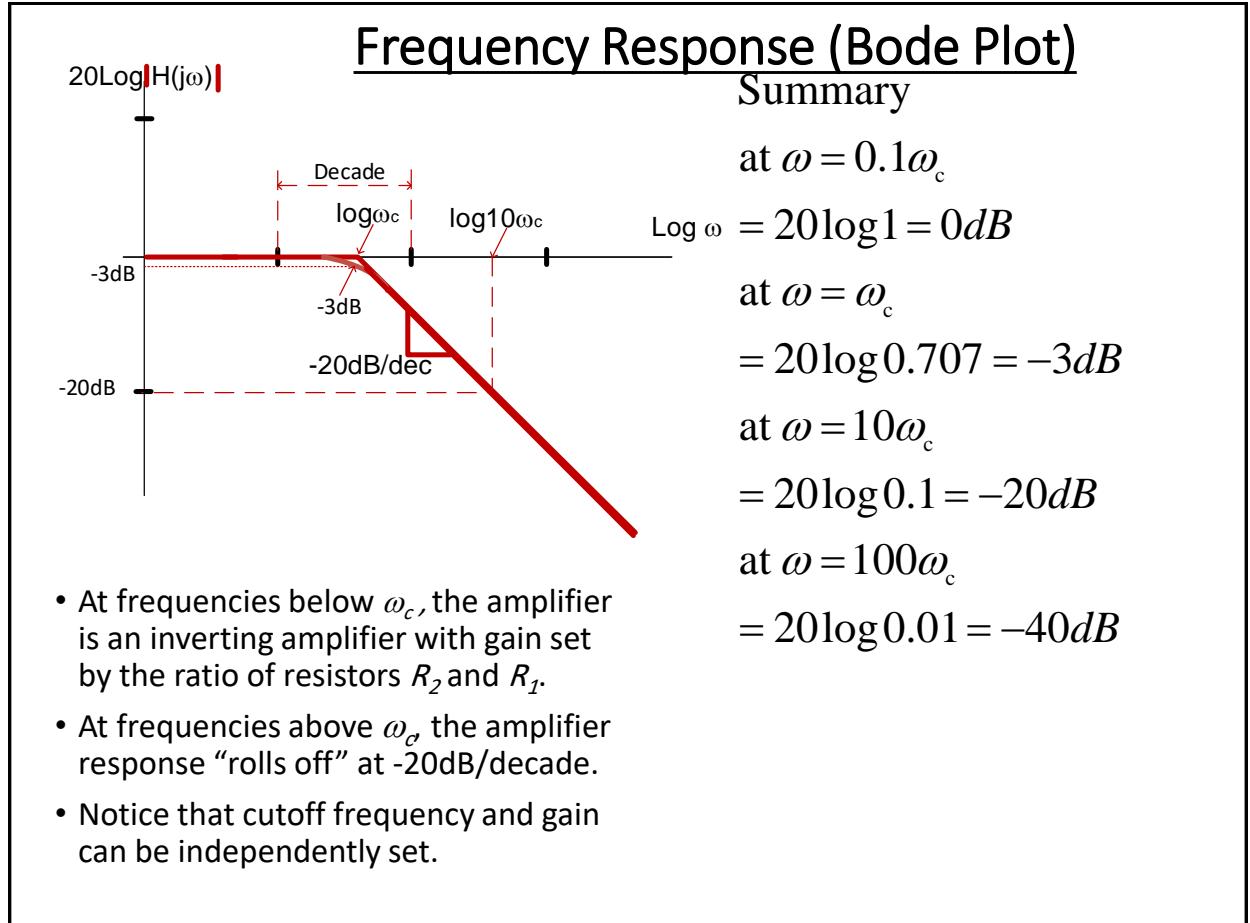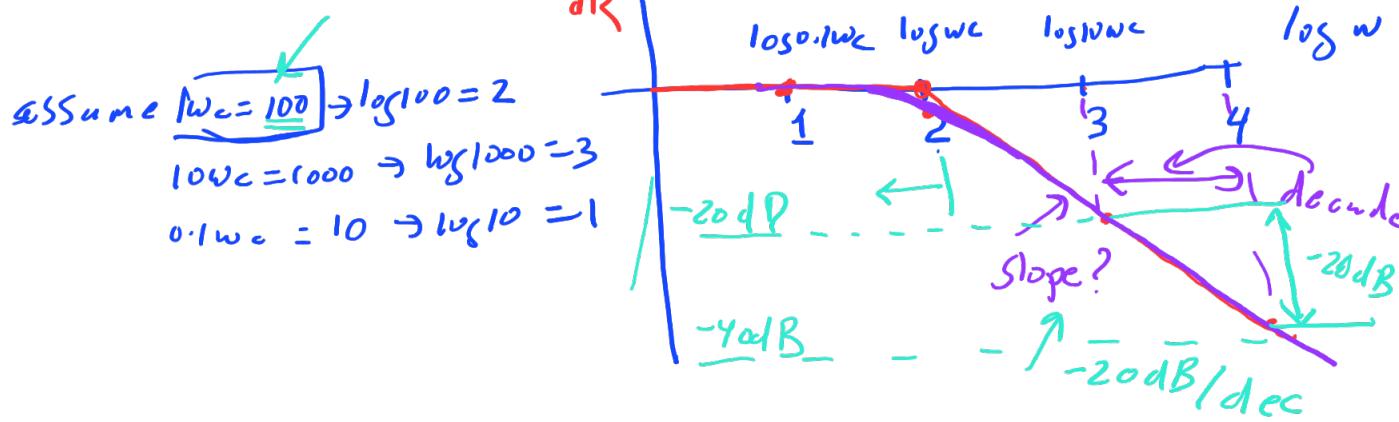

End of L25

$$Q_{\omega=1000} \quad A_{\sqrt{k}} = \left| \frac{V_o}{V_i} \right| = \sqrt{1 + \left(\frac{\omega_c}{\omega} \right)^2} = 0.1$$

$$\frac{V_o}{5} = 0.1 \quad V_o = 5 \times 0.1 = \underline{\underline{0.5}}$$

Active Low-pass Filter: Example



- **Problem:** Design an active low-pass filter
 - **Given Data:** $A_v = 40 \text{ dB}$, $R_{in} = 5 \text{ k}\Omega$, $f_c = 2 \text{ kHz}$
 - **Assumptions:** Ideal op amp, specified gain represents the desired low-frequency gain.
 - **Analysis:** $|A_v| = 10^{40 \text{ dB} / 20 \text{ dB}} = 100$


$w_c = \frac{1}{\sqrt{R_2 C}}$

Input resistance is controlled by R_1 and voltage gain is set by R_2 / R_1 .

The cutoff frequency is then set by C.

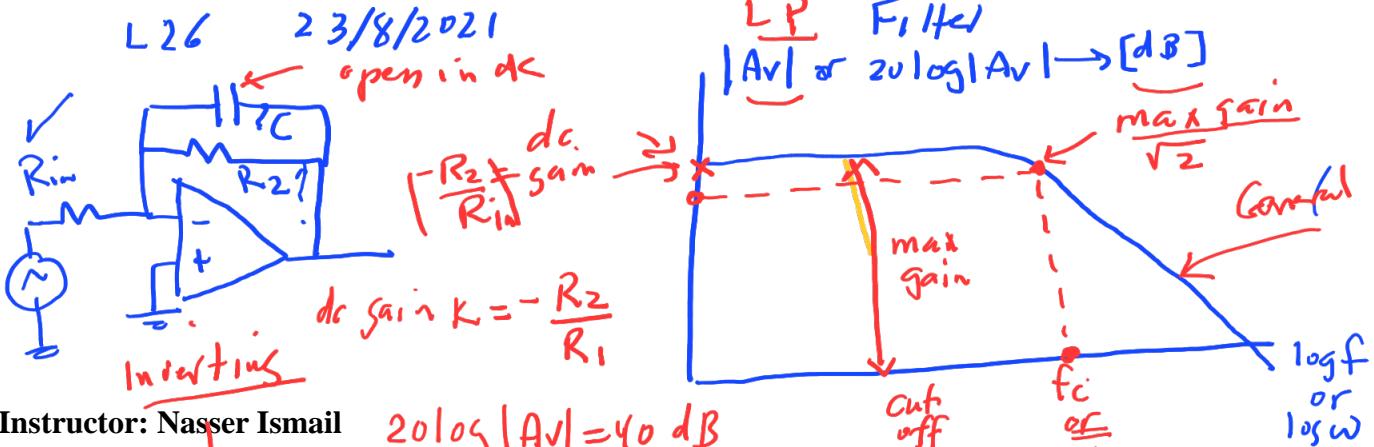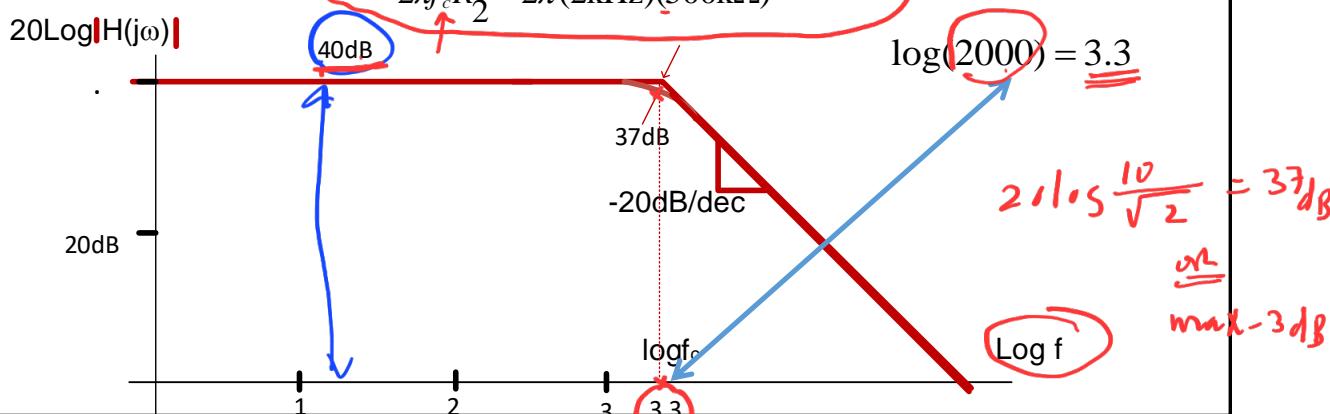
$$C = \frac{1}{2\pi f_c R_2} = \frac{1}{2\pi(2\text{kHz})(500\text{k}\Omega)} = 159\text{pF}$$



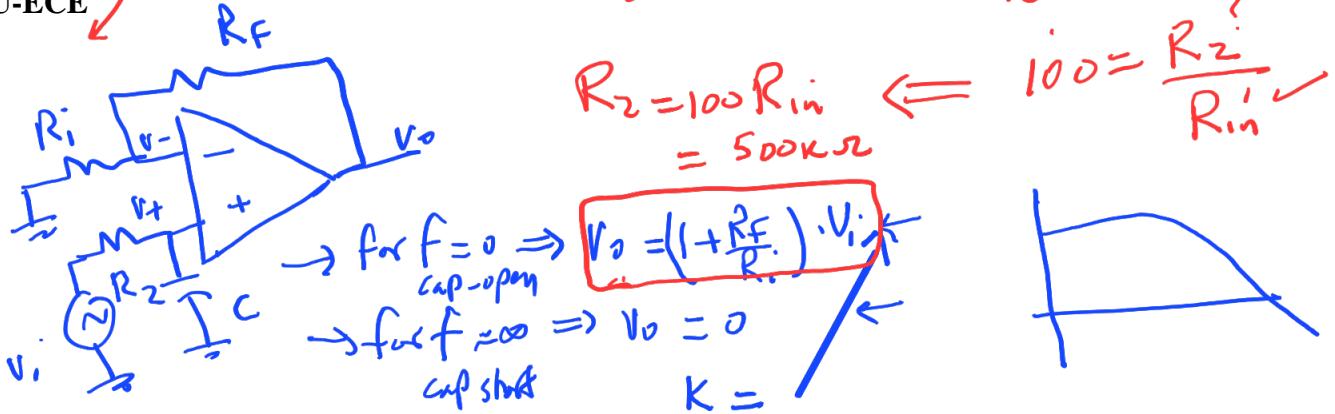

The Active High-pass Filter

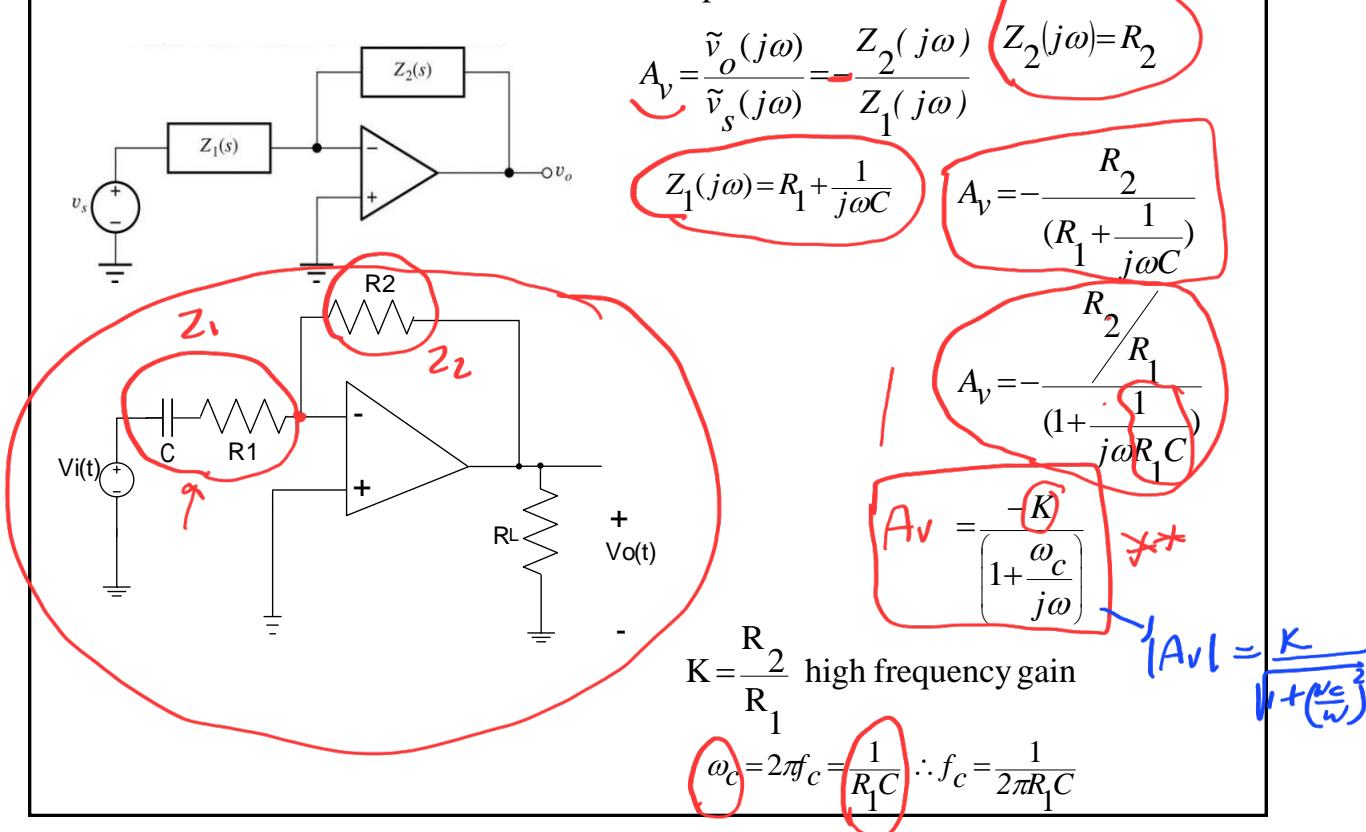The gain analysis of this inverting amplifier.



1st order
LPF

$$|Av| = \frac{K}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

1st order
HPF

$$|Av| = \frac{K}{\sqrt{1 + \left(\frac{\omega_c}{\omega}\right)^2}}$$

assume $K=1$

$$\text{for } \omega = \omega_c \Rightarrow 20 \log |A\omega| = 20 \log \frac{1}{\sqrt{1+1}} = -3 \text{ dB}$$

$$\text{for } \omega = 0.1\omega_c \Rightarrow 20 \log \frac{1}{\sqrt{1+(\frac{\omega_c}{0.1\omega_c})^2}} = 20 \log \frac{1}{\sqrt{101}} = 20 \log 0.1 = -20 \text{ dB}$$

$$\text{for } \omega = 0.01\omega_c \Rightarrow 20 \log \frac{1}{\sqrt{10001}} = 20 \log 0.01 = -40 \text{ dB}$$

$$\text{for } \omega = 10\omega_c \Rightarrow 20 \log \frac{1}{\sqrt{1.001}} = 20 \log 1 = 0 \text{ dB}$$

Frequency Response (Bode Plot)

Magnitude Plot (Magnitude in decibels vs log of frequency)

$$A_{dB} = 20 \log |H(j\omega)|$$

$$|H(j\omega)| = |A_v(j\omega)|$$

$$= \frac{K}{\sqrt{1 + \left(\frac{\omega_c}{\omega}\right)^2}}$$

at $\omega = 0.1\omega_c$

$$20 \log \frac{1}{\sqrt{1 + \left(\frac{\omega_c}{0.1\omega_c}\right)^2}} = 20 \log \frac{1}{\sqrt{1+100}} \\ \approx 20 \log \frac{1}{\sqrt{101}} = -20 \text{ dB}$$


at $\omega = \omega_c$

$$20 \log \frac{1}{\sqrt{1 + \left(\frac{\omega_c}{\omega_c}\right)^2}} = 20 \log \frac{1}{\sqrt{1+1}} \\ = 20 \log |0.707| = -3 \text{ dB}$$

at $\omega = 0.01\omega_c$

$$20 \log \frac{1}{\sqrt{1 + \left(\frac{\omega_c}{0.01\omega_c}\right)^2}} = 20 \log \frac{1}{\sqrt{1+10000}} \\ = 20 \log 0.01 = -40 \text{ dB}$$

ω	$20 \log A \text{ [dB]}$	$K = 10$
$10\omega_c$	0 dB	20 dB
ω_c	-3 dB	17 dB
$0.1\omega_c$	-20 dB	0 dB
$0.01\omega_c$	-40 dB	-20 dB

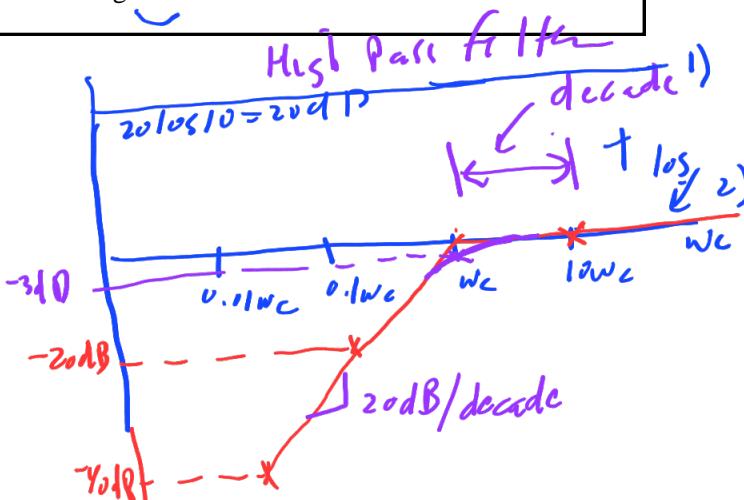

$$20 \log 10 - 20 \log 100$$

for $K = 10$


$$20 \log \frac{10}{100} = 20 dB - 40 dB \\ = -20 dB$$

$$\text{for } \omega = 0.1\omega_c \Rightarrow 20 \log \frac{10}{\sqrt{101}} \times 20 \log 10 \\ = 0 dB$$

$$\omega = 0.01\omega_c \Rightarrow 20 \log \frac{10}{100} \\ = -20 dB$$

$$\omega = \omega_c \Rightarrow 20 \log \frac{10}{\sqrt{2}} \\ = 17 dB$$


Frequency Response (Bode Plot)

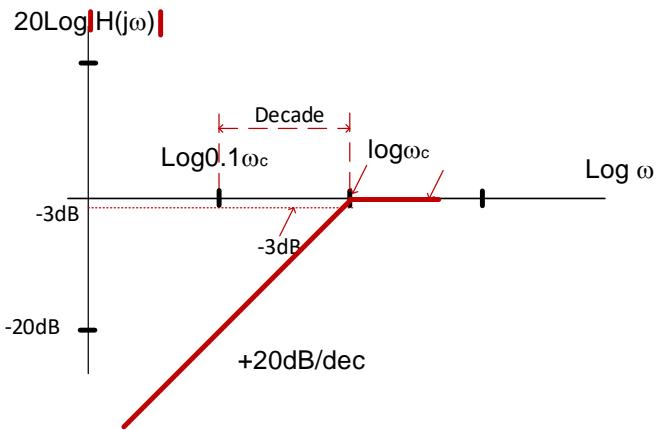


- At frequencies above ω_c , the amplifier is an inverting amplifier with gain set by the ratio of resistors R_2 and R_1 .
- At frequencies below ω_c , the amplifier response "rolls off" at $-20dB/\text{decade}$.
- Notice that cutoff frequency and gain can be independently set.


Summary

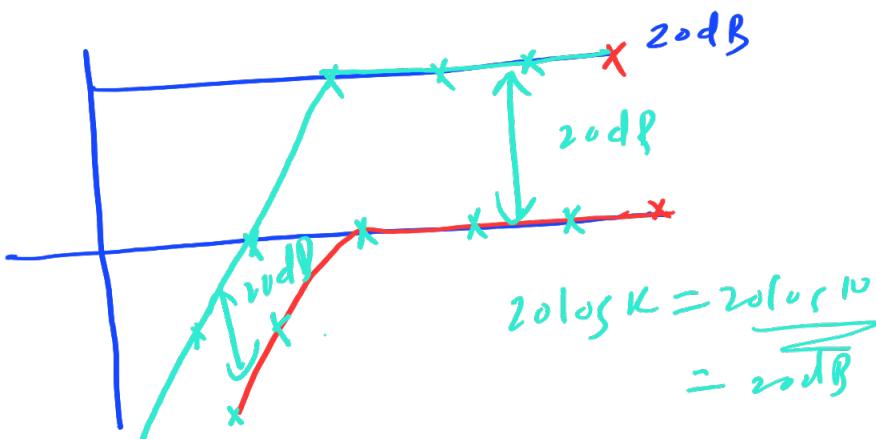- at $\omega = 0.1\omega_c$
 $= 20 \log 0.1 = -20 dB$
- at $\omega = \omega_c$
 $= 20 \log 0.707 = -3 dB$
- at $\omega = 0.01\omega_c$
 $= 20 \log 0.01 = -40 dB$
- at $\omega = 0$
 $= 20 \log 1 = 0 dB$



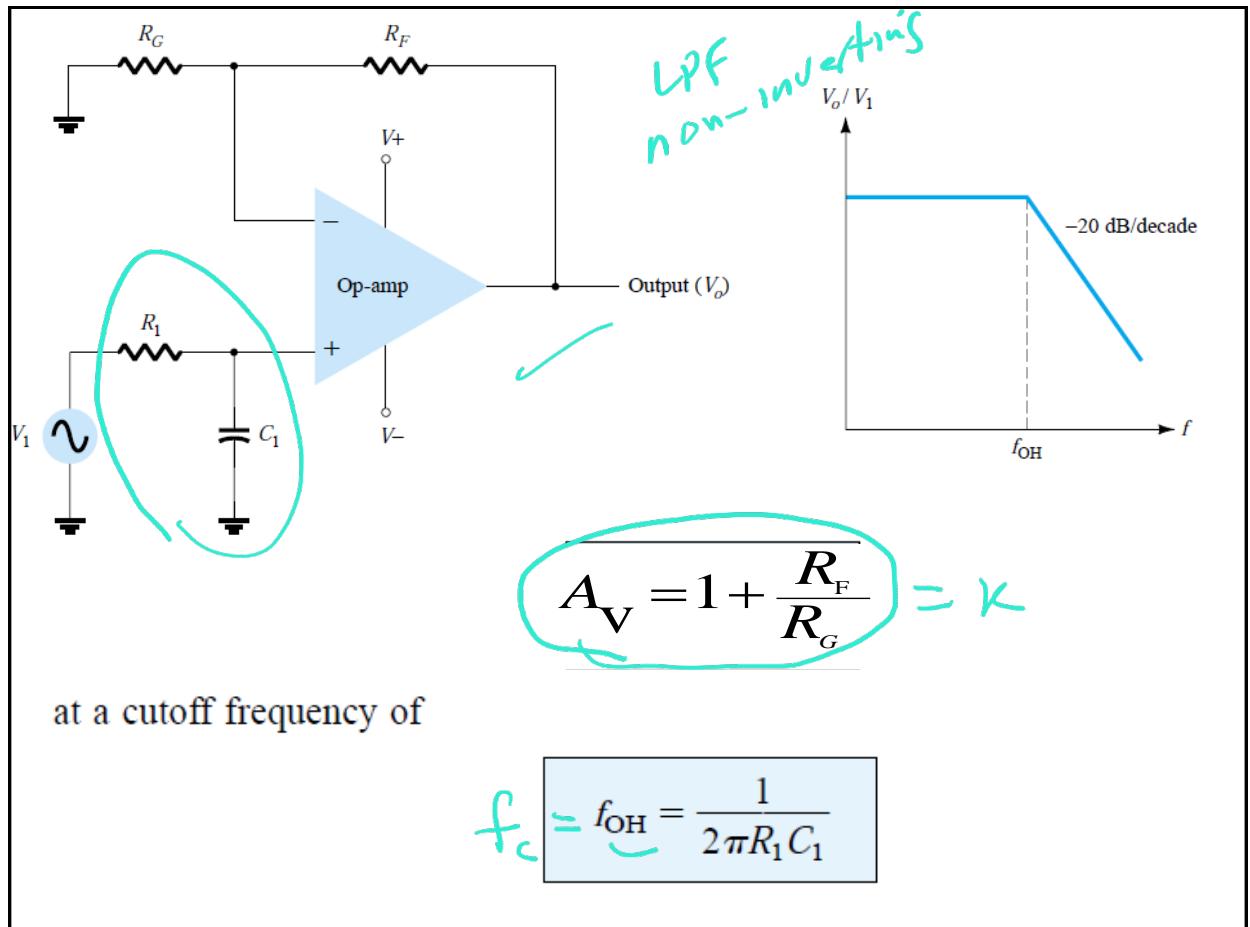


High-Pass Active Filter

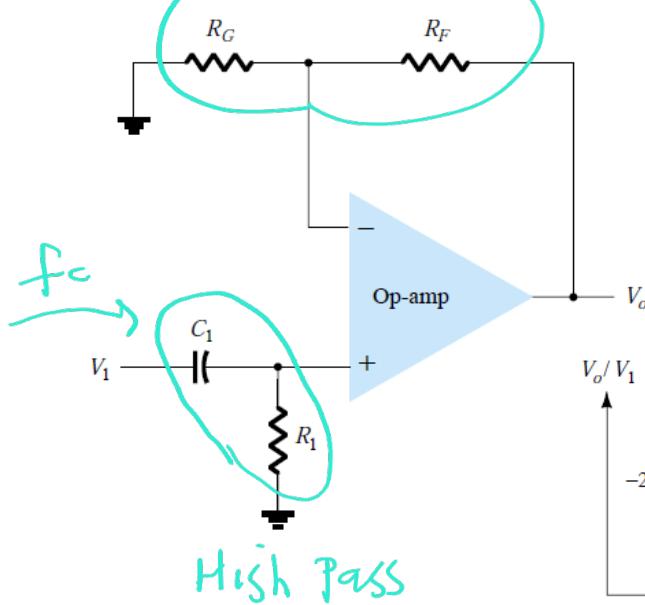


$$f_c = f_{OL} = \frac{1}{2\pi R_1 C_1}$$

$$\kappa = 1 + \frac{R_F}{R_G}$$

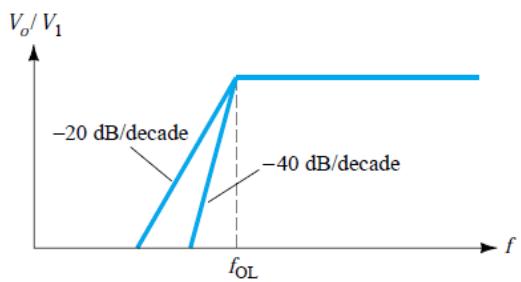


$$A_v = A_{v1} \cdot A_{v2} \cdot A_{v3}$$


Cascaded Amplifiers

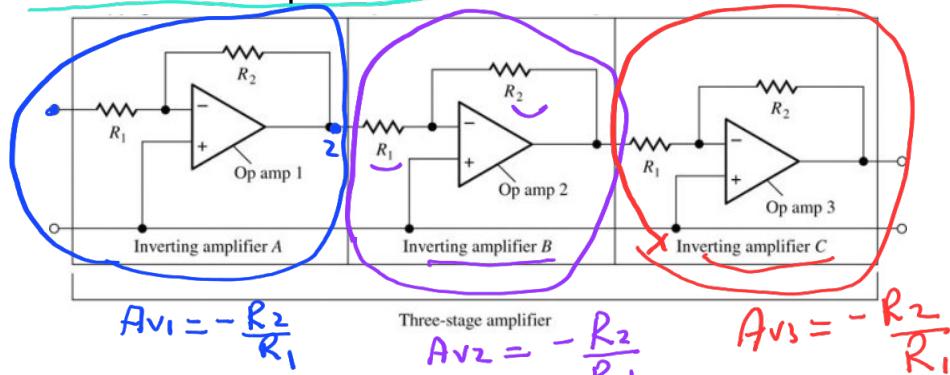



- Connecting several amplifiers in cascade (output of one stage connected to the input of the next) can meet design specifications not met by a single amplifier.
- Each amplifier stage is built using an op amp with parameters A , R_{in} , R_{out} , called open loop parameters, that describe the op amp with no external elements.
- A_v , R_{in} , R_{out} are closed loop parameters that can be used to describe each closed-loop op amp stage with its feedback network, as well as the overall composite (cascaded) amplifier.
- The gain of each stage can be calculated separately, then the total gain is found by multiplying the resulting gains

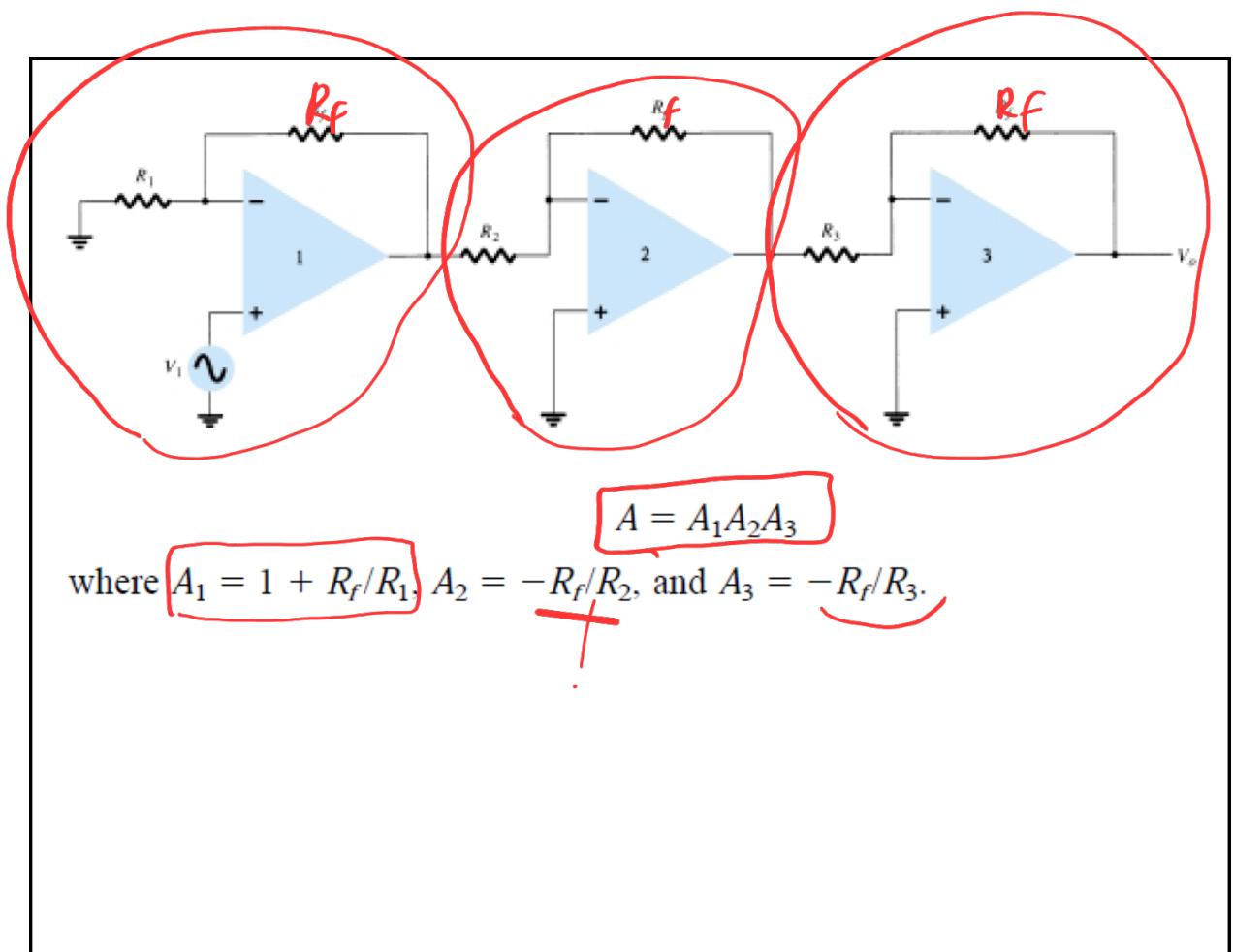


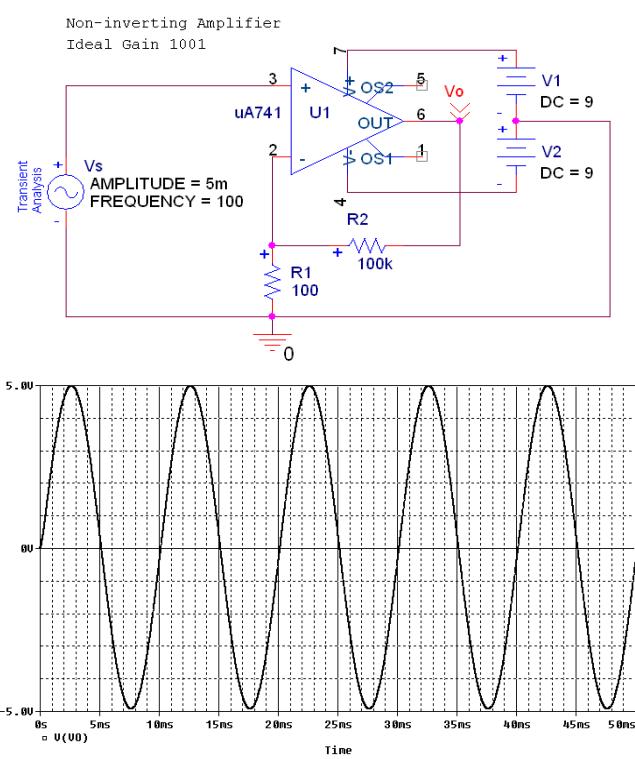
Example PSpice Simulations of Non-inverting Amplifier Circuits




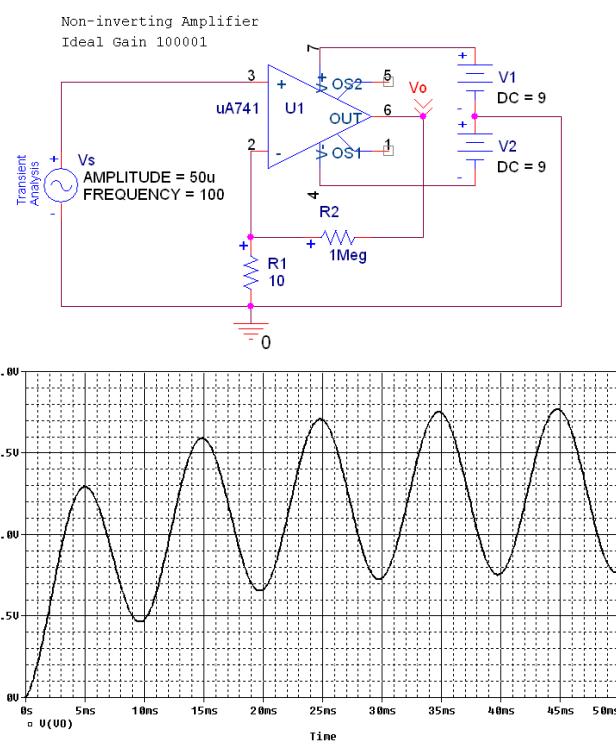

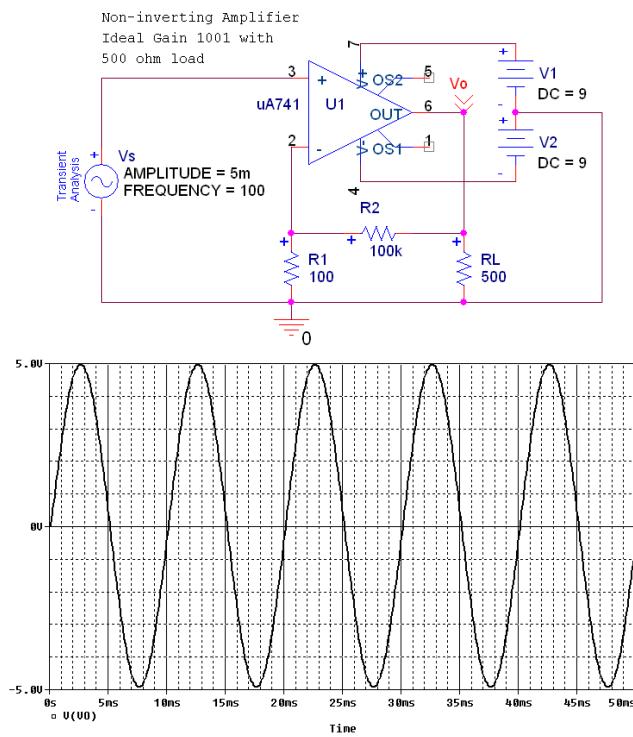


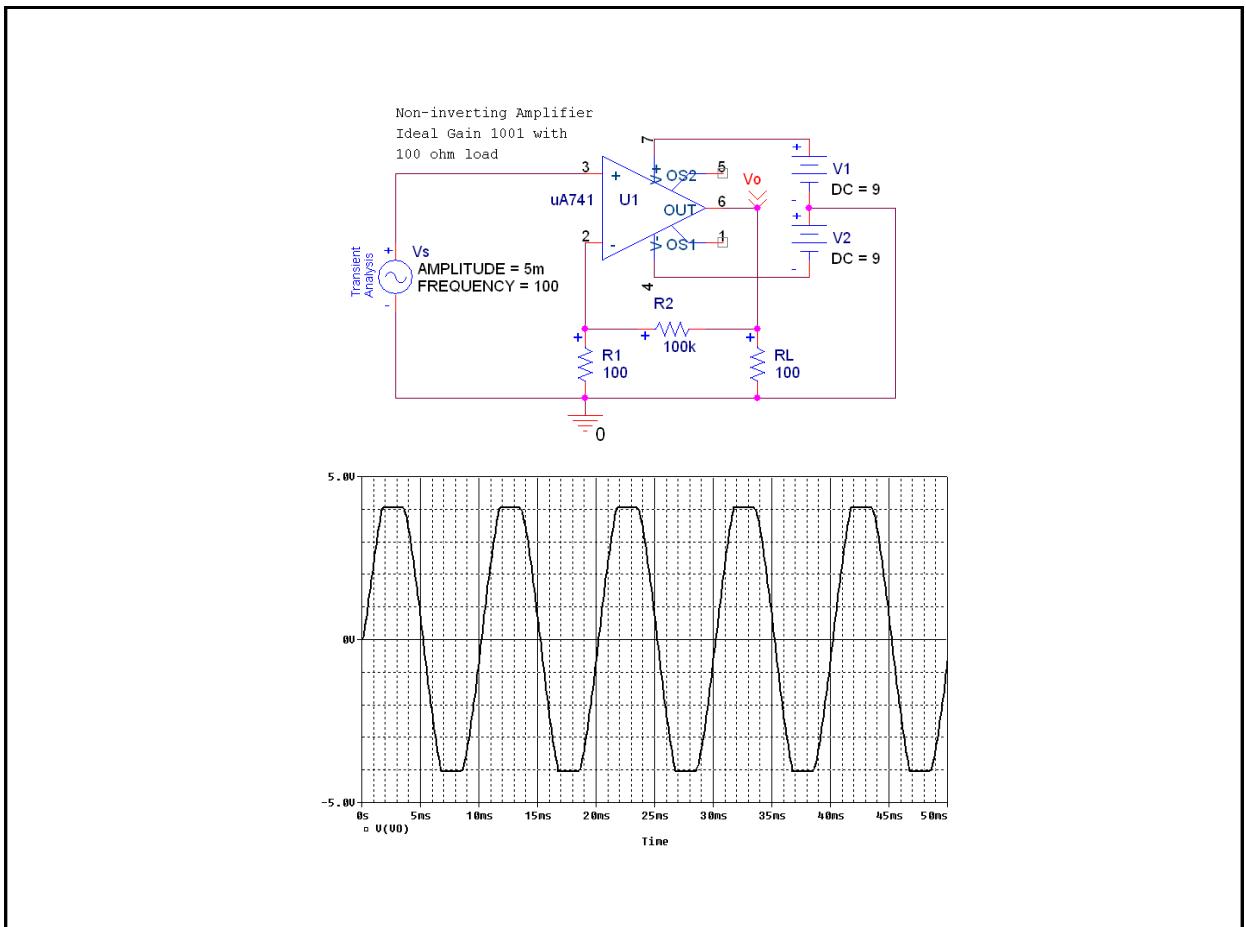

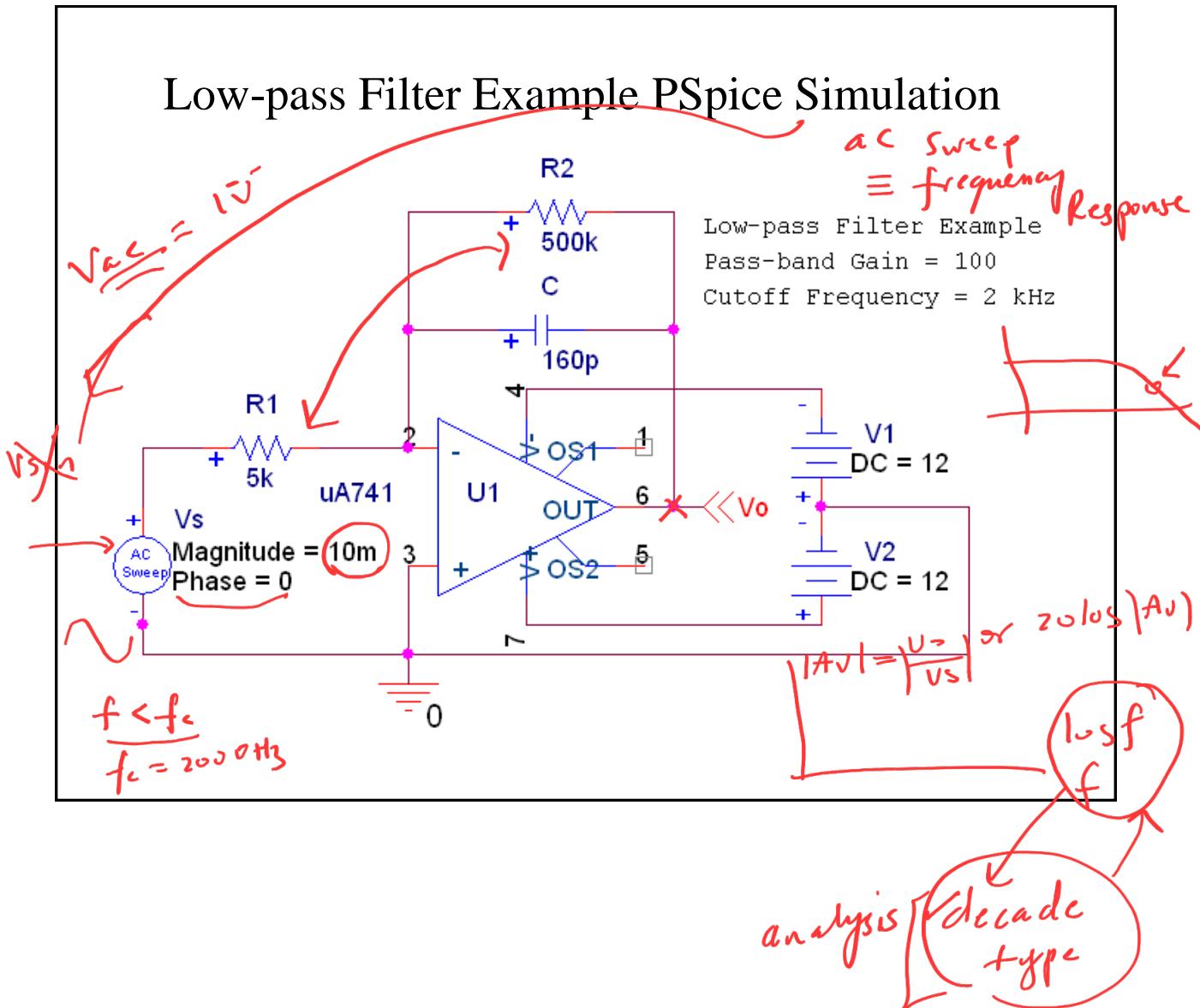


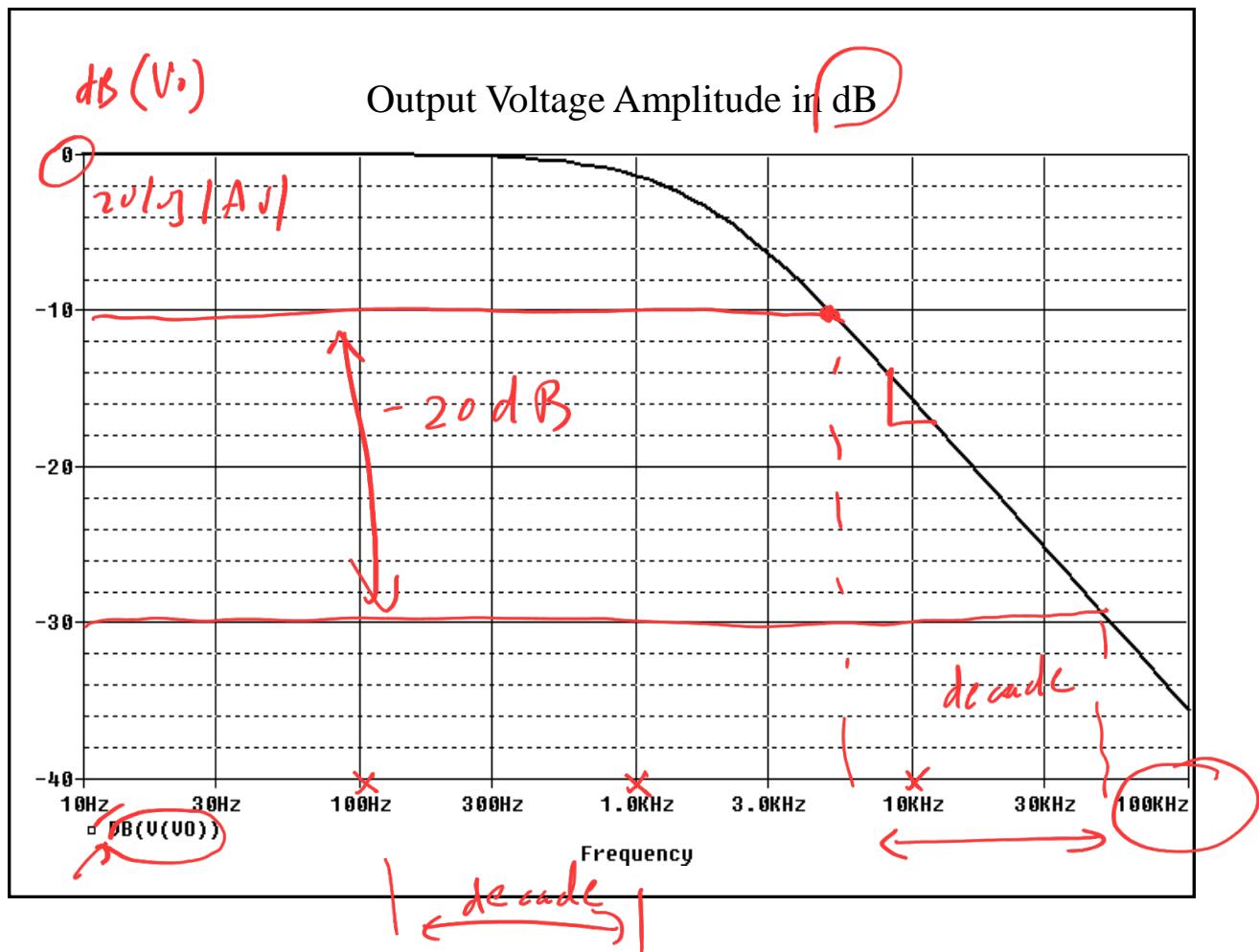

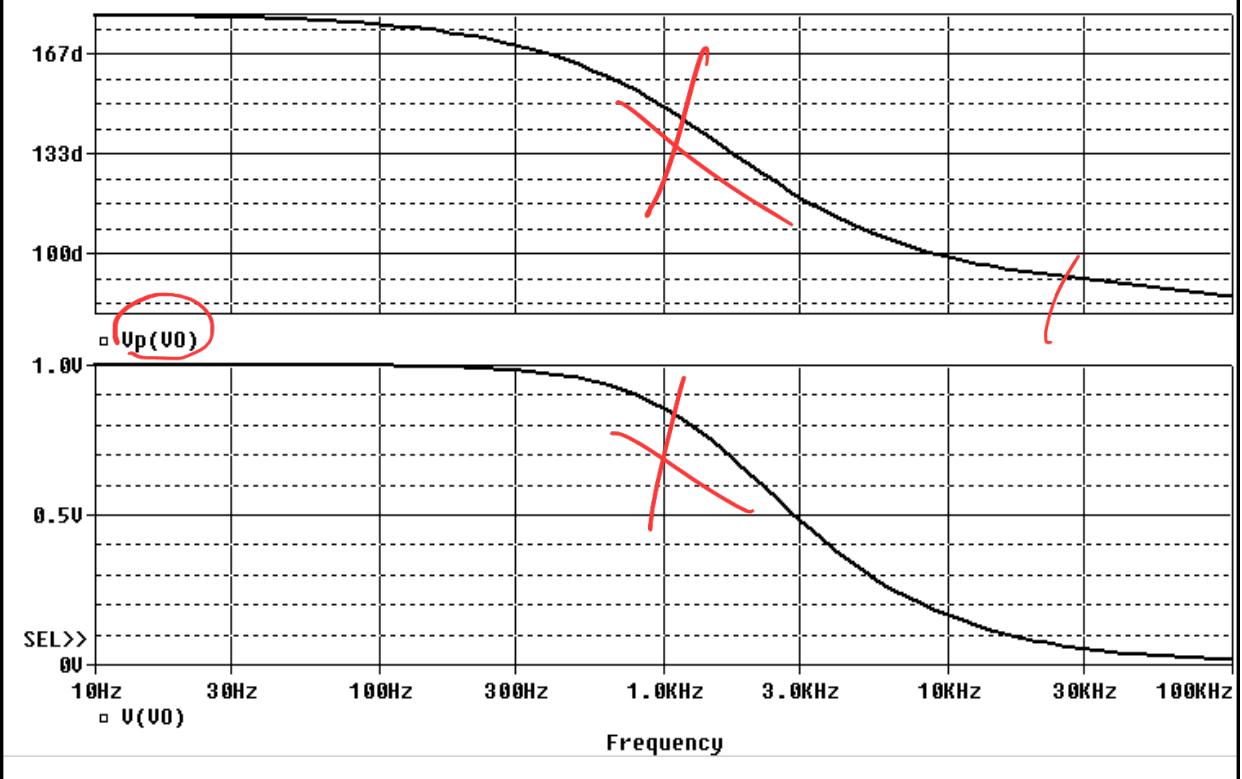Output Voltage Amplitude in Volts (V) and Phase in Degrees (d)




Following Material is for
Reference Only

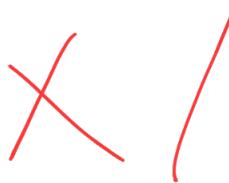

Applications of Op-Amps


Electrocardiogram (EKG) Amplification •

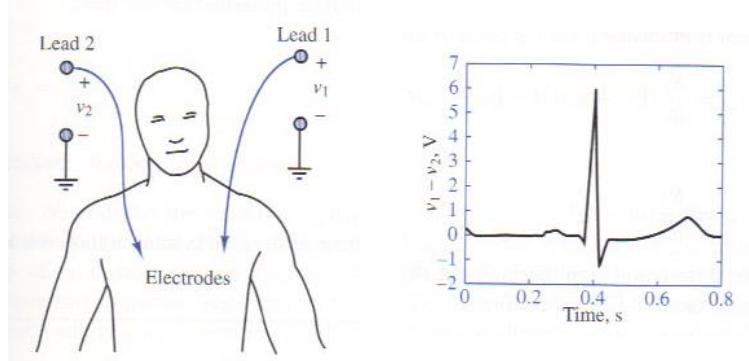- Need to measure difference in voltage from lead 1 and lead 2 •
- 60 Hz interference from electrical equipment •




Applications of Op-Amps


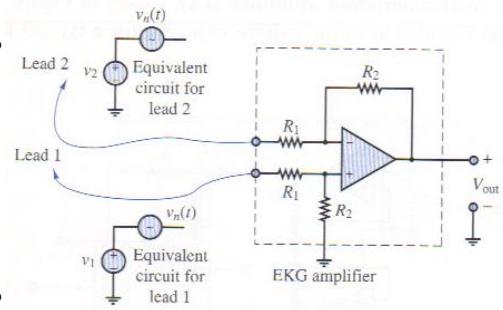
Simple EKG circuit •
Uses differential amplifier •
to cancel common mode
signal and amplify
differential mode signal




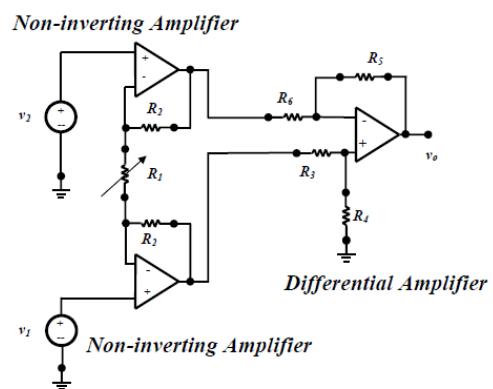
Realistic EKG circuit •
Uses two non-inverting •
amplifiers to first amplify
voltage from each lead,
followed by differential
amplifier
Forms an •
“instrumentation
amplifier”



Strain Gauge

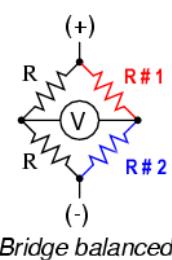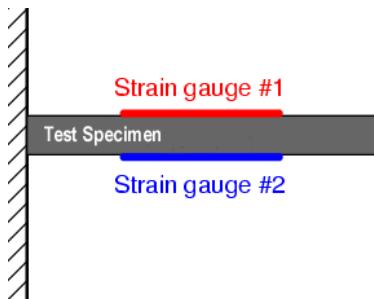

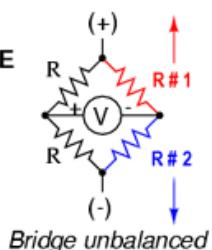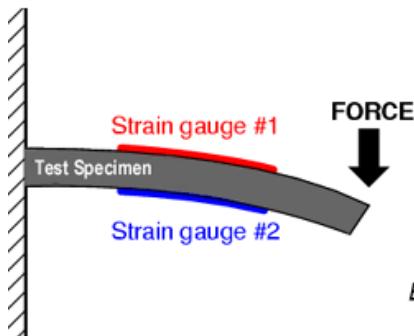Use a Wheatstone bridge to determine the strain of an element by measuring the change in resistance of a strain gauge




(No strain) Balanced Bridge
 $R \#1 = R \#2$

(Strain) Unbalanced Bridge
 $R \#1 \neq R \#2$

Half-Bridge Arrangement

Strain Gauge

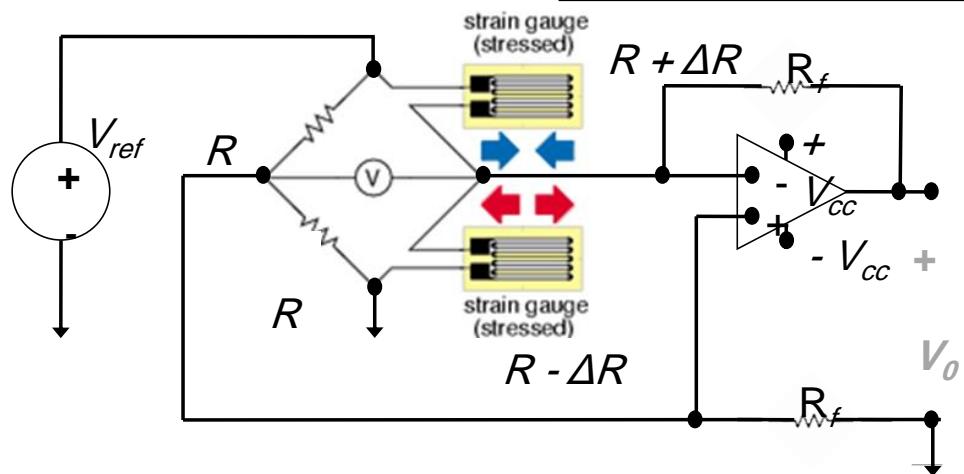Op amp used to amplify output from strain gauge





Using KCL at the inverting and non-inverting terminals of the op amp we find that $\epsilon \sim V_o = 2\Delta R(R_f / R^2)$

Applications of Op-Amps


Piezoelectric Transducer •

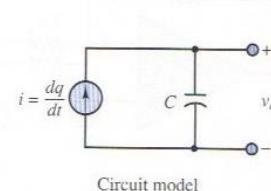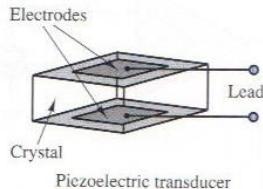- Used to measure force, pressure, acceleration •
- Piezoelectric crystal generates an electric charge in •
response to deformation



Use Charge Amplifier •


Just an integrator op-amp circuit •

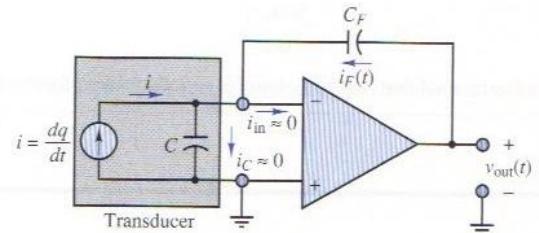

Applications of Op-Amps

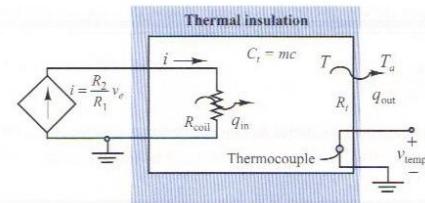- Example of PI Control:
Temperature Control

- Thermal System we wish to automatically control the temperature of:



- Block Diagram of Control System:

