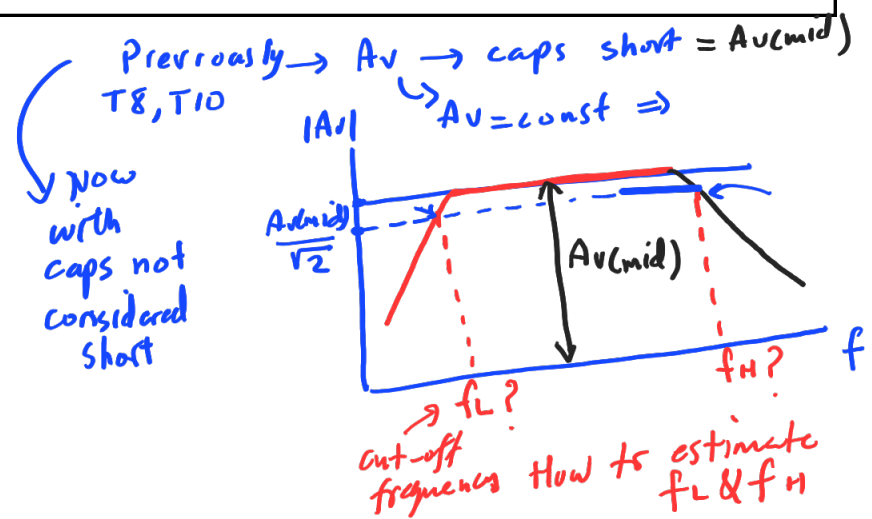


ENEE2360 Analog Electronics

T12: Amplifier Frequency Response




Instructor : Nasser Ismail



Amplifier Frequency Response ?

- Audio frequency signals such as speech and music are combination of many different sine waves, occurring simultaneously with different amplitude and frequency in the following range (20Hz-20kHz (audible noise) , other types of signals have their own range.
- In order for the output to be an amplified version of the input, the amplifier must amplify each and every component in the signal by the same amount
- The Bandwidth must cover the entire range of frequency components if considered amplification is to be achieved

Amplifier Frequency Response

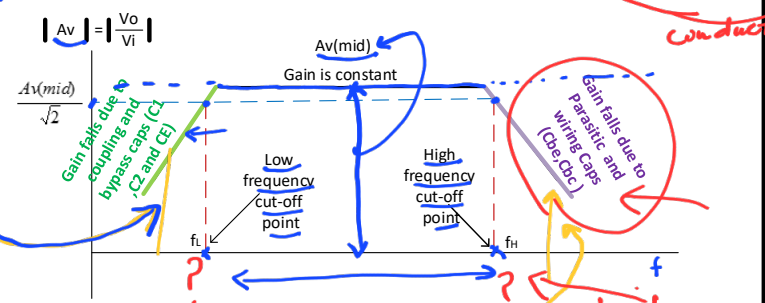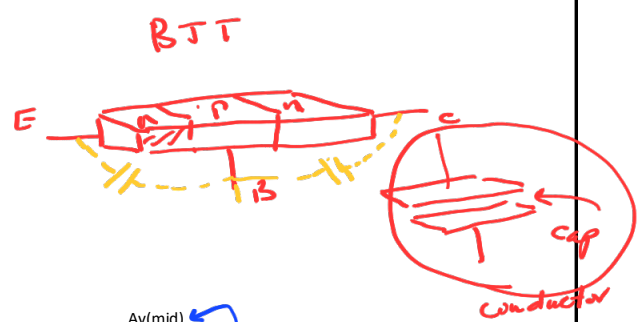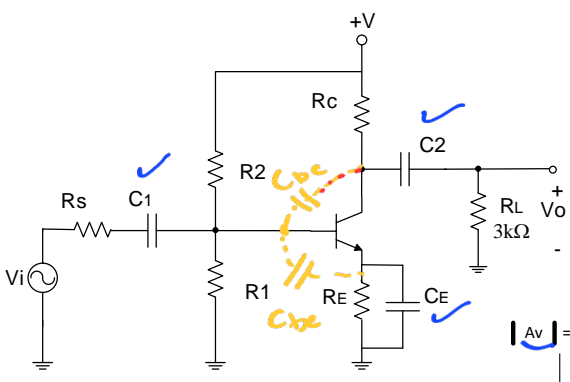


✓ C_1, C_2, C_E ← real (physical) caps

C_{be}, C_{bc}
 C_{gs}, C_{gd} ← hidden (parasitic or stray) cap

Gain falls due to parasitic and wiring caps (C_{be}, C_{bc})

high frequency

Impedance of a cap

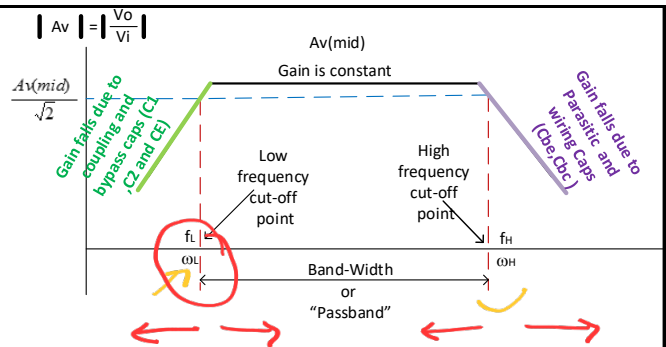

- The impedance of a cap is

$$X_c = \frac{1}{2\pi f C}$$

when $f < f_L$ the coupling caps C_1 and C_2 , and the bypass cap C_E cannot be considered as short circuit since their impedance is not small enough

when $f > f_H$ the internal caps C_{bc} and C_{be} for a BJT (or C_{gs} and C_{gd}), cannot be considered as open circuit since their impedance is not high enough

Corner Frequency

we define the corner (break and cut - off) frequency as :


$$|A(j\omega_L)| = \frac{A_v(mid)}{\sqrt{2}}$$

$$|A(j\omega_H)| = \frac{A_v(mid)}{\sqrt{2}}$$


$$\omega_H - \omega_L = BW \text{ - Bandwidth}$$

$$\text{Midrange} = \text{midband} \cong 10\omega_L - 0.1\omega_H$$

definition

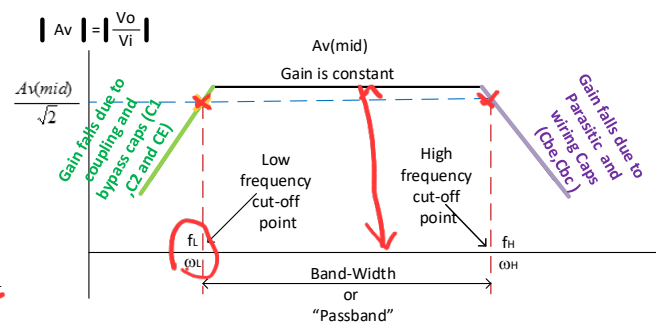

Corner Frequency

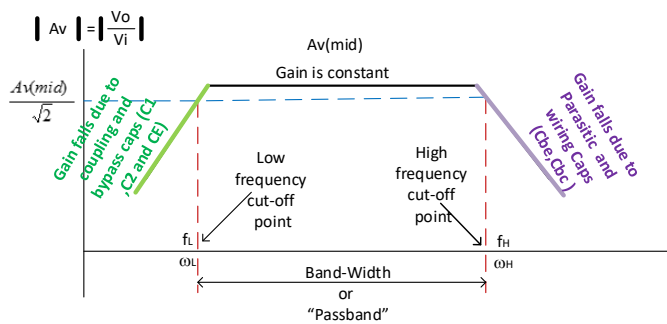


$$\text{Midrange} = \text{midband} \cong 10\omega_L - 0.1\omega_H$$

- This is the range for which the capacitors (C_1 , C_2 and C_E) are considered short circuit while the parasitic caps are considered open circuit (this is the range we have considered so far in previous chapters)


End of L26

$x \left\{ \begin{array}{l} f \rightarrow \omega = 2\pi f \\ \log f, \log \omega \leftarrow [\text{decade}] \end{array} \right.$
 $y \left\{ \begin{array}{l} A_v(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} \\ |A(j\omega)| \\ 20 \log |A(j\omega)| \Rightarrow \text{in decibels [dB]} \end{array} \right.$

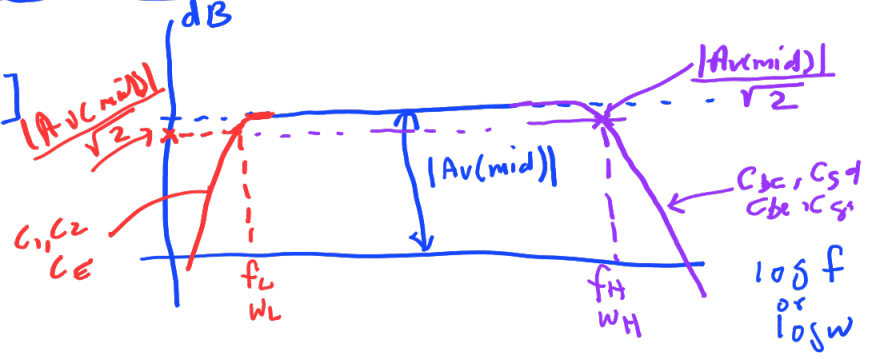

Series Capacitance and low frequency response

consider C1 only

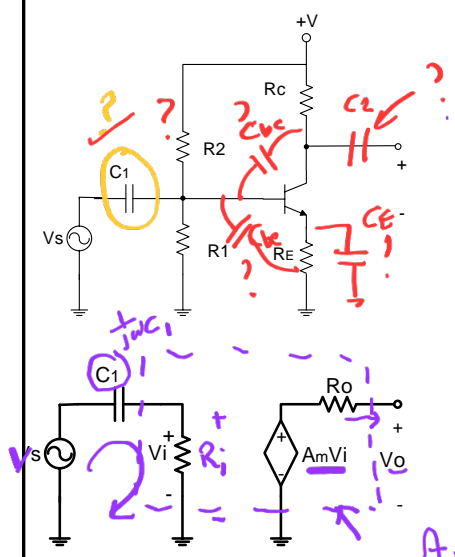

$$V_o = A_m V_i$$


$$V_i = \frac{R_i}{R_i + \frac{1}{j\omega C_1}} V_s \rightarrow V_o = \frac{A_m R_i}{R_i + \frac{1}{j\omega C_1}} V_s$$

$$\frac{V_o}{V_s} = \frac{A_m R_i}{R_i + \frac{1}{j\omega C_1}} = A(j\omega)$$


$$\rightarrow |A(j\omega)| = \frac{A_m R_i}{\sqrt{(R_i)^2 + \left(\frac{1}{\omega C_1}\right)^2}}$$

$A_m = A_v(\text{mid})$

$\frac{V_o}{V_s} = ?$

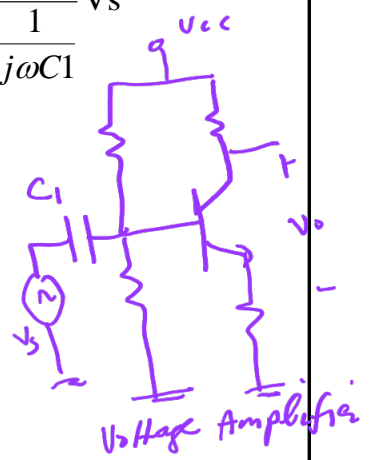

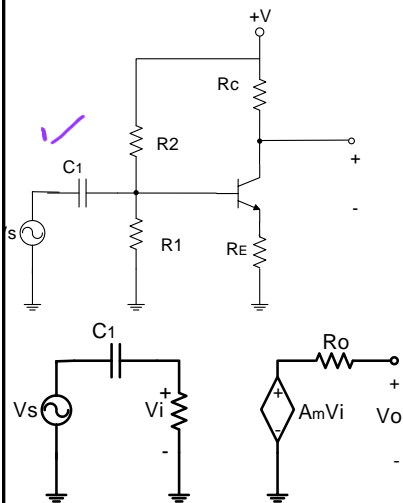Series Capacitance and low frequency response



$$|A(j\omega)| = \frac{A_m R_i}{\sqrt{(R_i)^2 + \left(\frac{1}{\omega C_1}\right)^2}}$$

$$= \frac{A_m}{\sqrt{1 + \left(\frac{\omega_{c1}}{\omega}\right)^2}}$$

where $\omega_{c1} = \frac{1}{R_i C_1}$ is the break frequency due to C1

For $A_m = 1$

for $\omega = \omega_{c1} \rightarrow 20 \log |A(j\omega)| = 20 \log A_m - 20 \log 0.707 = -3 \text{ dB}$

for $\omega = 0.1 \omega_{c1} \rightarrow 20 \log |A(j\omega)| = -20 \log 10 = -20 \text{ dB} \leftarrow \text{High pass filter}$

Handwritten notes:
 $A_m = 1$
 $\omega = 10 \omega_{c1}$ (marked with a checkmark)
 $= \frac{1}{\sqrt{1 + \left(\frac{1}{10}\right)^2}} = \frac{1}{\sqrt{1.01}} \approx 1 = \frac{V_o}{V_i}$
 $\omega = 0.1 \omega_{c1}$
 $= \frac{1}{\sqrt{1 + 10^2}} = \frac{1}{10} = \left(\frac{V_o}{V_i}\right)$
 HPF (High Pass Filter) graph showing a curve that rises from a low value at low frequencies to a high value at high frequencies.



Series Capacitance and low frequency response

$$C_1 \rightarrow \omega_{c1} \rightarrow \left(\frac{A_m}{1 + \frac{\omega_{c1}}{j\omega}} \right) = A(j\omega)$$

Note:

1) If there is only one cap, we find $\omega_{c1} = \frac{1}{R_{th1} \cdot C1}$ and $\omega_L = \omega_{c1}$

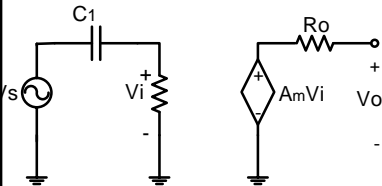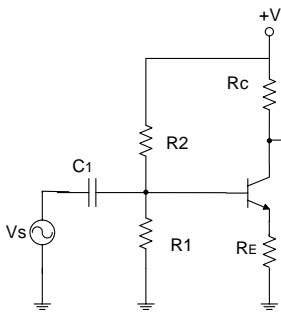2) If there is two caps $C1$ and $C2$ with ω_{c1} and ω_{c2} then




$$A(j\omega) = A_m \left(\frac{1}{1 + \left(\frac{\omega_{c1}}{j\omega} \right)} \right) \left(\frac{1}{1 + \left(\frac{\omega_{c2}}{j\omega} \right)} \right)$$

ω_L ?

$$|A(j\omega_L)| = \frac{A_m}{\sqrt{2}}$$



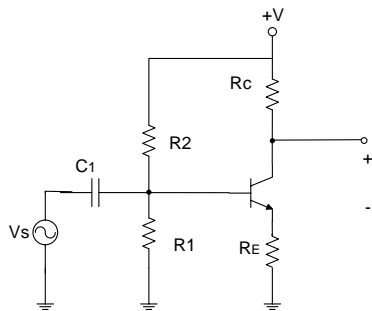Series Capacitance and low frequency response




in order to find ω_L , we find magnitude of the gain at ω_L

$$|A(j\omega_L)| = \frac{A_m}{\sqrt{2}} \rightarrow \omega_L ?$$

solving yields
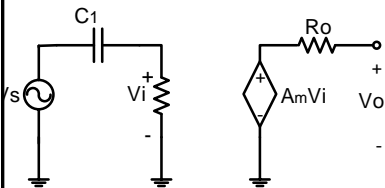
$$\omega_L^2 = \frac{\omega_{C1}^2 + \omega_{C2}^2}{2} + \frac{\sqrt{\omega_{C1}^4 + 6\omega_{C1}^2\omega_{C2}^2 + \omega_{C2}^4}}{2}$$



Series Capacitance and low frequency response

1) let $\omega_{c1} = 616$ rad/sec and $\omega_{c2} = 17.86$ rad/sec

here $\omega_{c1} \gg \omega_{c2}$

$\omega_L = 616.5$ rad/sec

2) let $\omega_{c1} = 200$ rad/sec and $\omega_{c2} = 750$ rad/sec

here $\omega_{c2} \gg \omega_{c1}$

$\omega_L = 798$ rad/sec

$$\omega_L^2 = \frac{\omega_{c1}^2 + \omega_{c2}^2}{2} + \frac{\sqrt{\omega_{c1}^4 + 6\omega_{c1}^2\omega_{c2}^2 + \omega_{c2}^4}}{2}$$

In both cases and in general

if $\omega_{c1} \gg \omega_{c2}$



$$\omega_{c1} < \omega_L < \omega_{c1} + \omega_{c2}$$

Biggest $\omega_{c_i} < \omega_L < \text{sum of all } \omega_{c_i}'s$


$$\max(\omega_i) < \omega_L < \text{sum}(\omega_i) \quad ***$$

Low Frequency Response Example

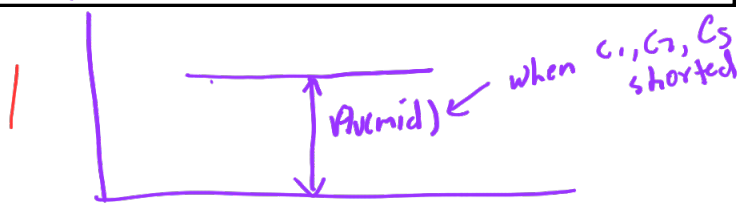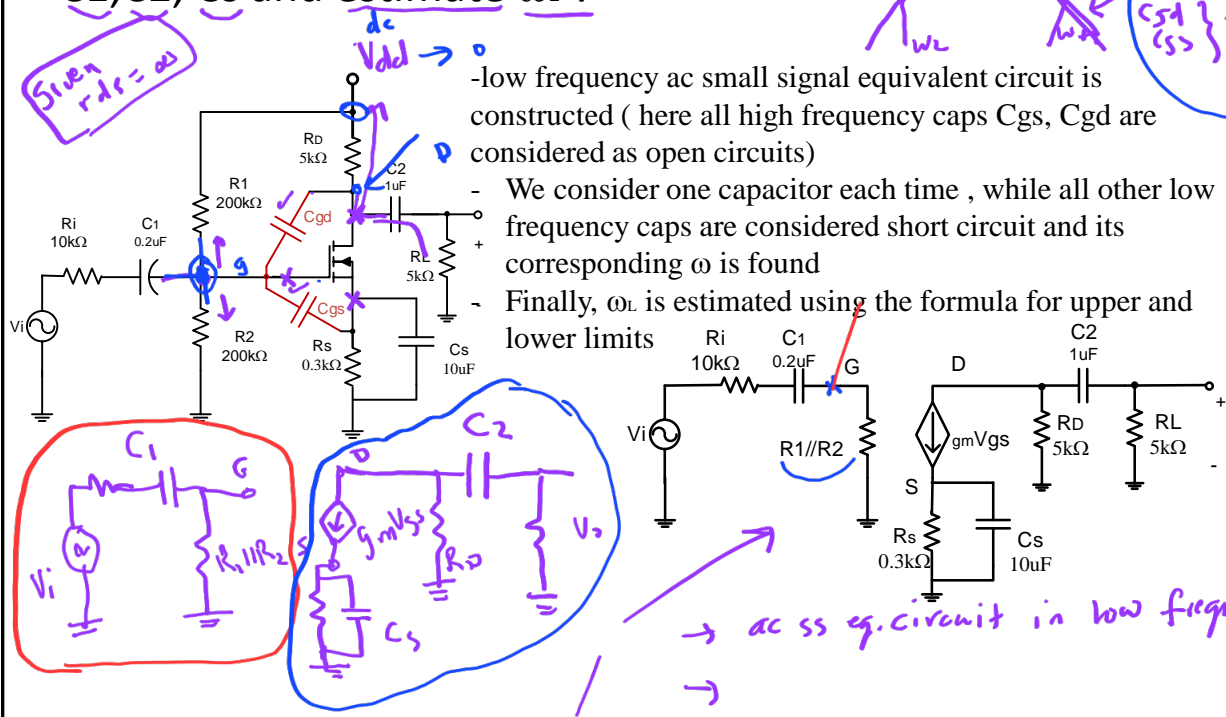- Calculate the low frequency corner frequencies due to C_1, C_2, C_s and estimate ω_L ?




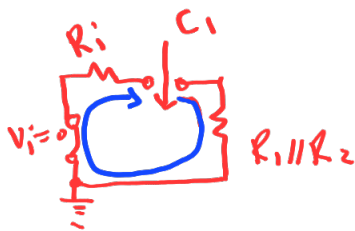Action plan: 1) take C_1 (while C_2 & C_3 shorted)
and find $\omega_{C1} = \frac{1}{C_1 R_{th1}}$;



$R_{th1} \Big|_{\text{seen by } C_1} = (R_1 || R_2) + R_i$

2) take C_2 (while C_1, C_3 shorted)

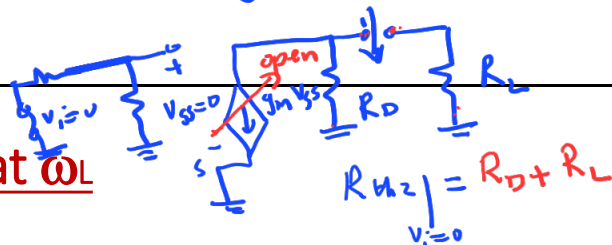

Effect of each Capacitor at ω_L

- We Calculate the low frequency corner frequencies due to each cap acting alone while all others are considered as short circuit

1) consider C_1 (while C_2 and C_3 are shorted)


$$\omega_{C1} = \frac{1}{C_1 R_{th1}} = 45.45 \text{ rad/sec}; \checkmark$$

R_{th1} is the thevenin impedance seen by C_1
while all independant sources are set to zero

$$R_{th1} = R_i + (R_1 || R_2) \checkmark$$

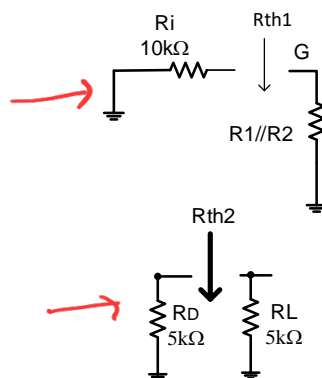2) consider C_2 (while C_1 and C_3 are shorted)


$$\omega_{C2} = \frac{1}{C_2 R_{th2}} = 100 \text{ rad/sec}; \checkmark$$




R_{th1} is the thevenin impedance seen by C_1

$$R_{th2} = R_D + R_L$$


3) consider C_3 (while C_1, C_2 shorted)

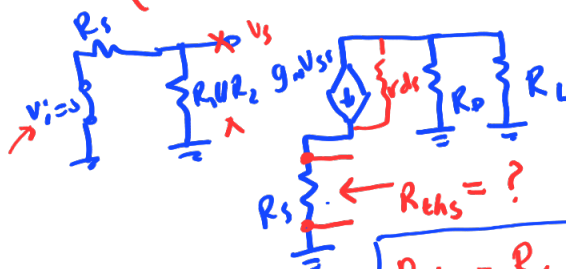

$$R_{th3} = R_s || \frac{1}{g_m}$$

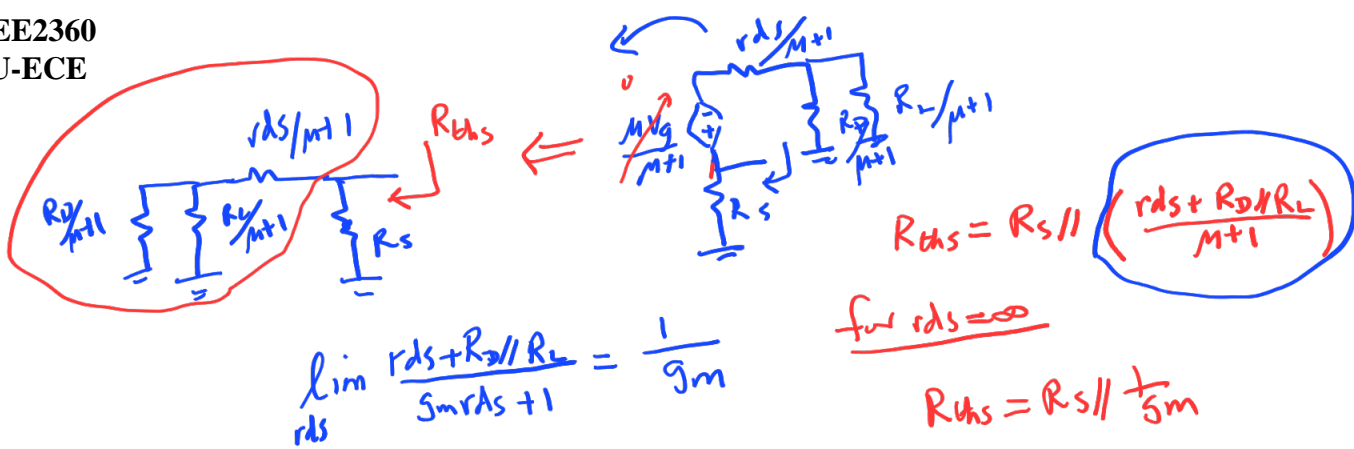

Effect of each Capacitor & ω_L

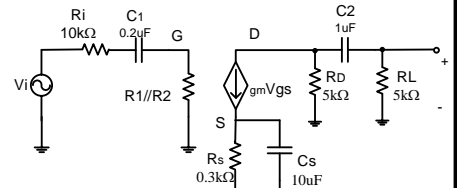

- We Calculate the low frequency corner frequencies due to cap acting alone while all others are considered as short circuit
- 3) consider C_s (while C_1 and C_2 are shorted)


$\omega_{c3} = \frac{1}{C_s \cdot R_{th3}} = 1050 \text{ rad/sec};$

R_{th3} is the thevenin impedance seen by C_s
remember $r_{ds} = \infty$

$R_{th3} = R_s \parallel \frac{1}{g_m}$

4) estimation of the ω_L

$1050 < \omega_L < 1195.5$

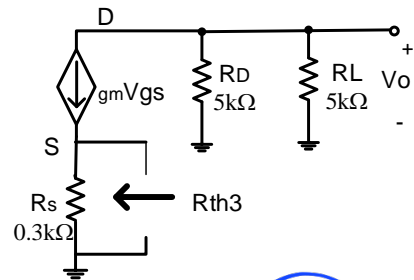

1050
100
45.4 ω_L



Given the following Amplifier, find the unknown Capacitors &/or resistors in order to have $\omega_L = 1000 \text{ rad/sec}$


? $\omega_L \leq \omega_{C1} + \omega_{C2} + \omega_{C3}$

Design Criteria

assume $\omega_{C3} = (0.7 - 0.8)\omega_L$

$\omega_{C1} = \omega_{C2} = (0.1 - 0.15)\omega_L$

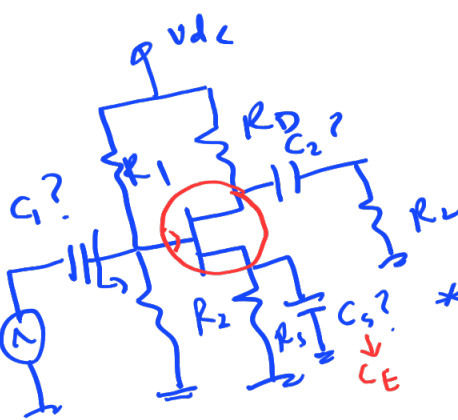always check $\omega_L = \omega_{C1} + \omega_{C2} + \omega_{C3}$



**** always ****
 $\omega_{C3} > \omega_{C1}$
 $\omega_{C3} > \omega_{C2}$

Design of ω_L

$\omega_{C3} = 700 \text{ rad/sec}, \omega_{C1} = \omega_{C2} = 150$

$\omega_{C3} = \frac{1}{R_{th} C_3} = 700 \Rightarrow C_3 =$

- Previous method explained how to estimate value of ω_L in an analysis problem where all capacitor values are given, but what happens if it was desired to design an amplifier with certain ω_L and the task was to find capacitor values?
- Design criteria to be used is:

$\omega_{CE} = (0.7 - 0.8)\omega_L$

$\omega_{C1} = \omega_{C2} = (0.1 - 0.15)\omega_L$

C1, C2 are input and output coupling capacitors

C_E is bypass capacitor // to R_E emitter stabilizing resistor or R_s source resistor

make sure that $\omega_{CE} + \omega_{C1} + \omega_{C3} = \omega_L$

|

parallel
high frequency caps } FET | BJT } in PF $\omega^{-12} f$

C_{gd} | C_{bc}
 C_{ss} | C_{be}

Shunt Capacitance and High frequency response


$$V_o = A_m V_i$$

$$V_i = \frac{R_i // \frac{1}{j\omega C_A}}{\left(R_i // \frac{1}{j\omega C_A}\right) + R_s} V_s \rightarrow \frac{V_o}{V_s} = A(j\omega)$$

$$A(j\omega) = A_m \frac{R_i // \frac{1}{j\omega C_A}}{\left(R_i // \frac{1}{j\omega C_A}\right) + R_s}$$

$$= A_m \left(\frac{R_i}{R_i + R_s}\right) \left(\frac{1}{1 + j\omega C_A (R_s // R_i)}\right)$$

$$\rightarrow |A(j\omega)| = A_m \frac{R_i}{R_i + R_s} \cdot \frac{1}{\sqrt{1 + [\omega C_A (R_s // R_i)]^2}}$$

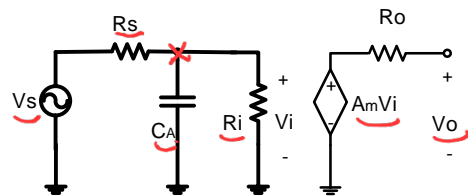

$$\rightarrow |A(j\omega)| = A_v(\text{mid}) \frac{1}{\sqrt{1 + [\omega C_A (R_s // R_i)]^2}}$$

$$\rightarrow |A(j\omega)| = A_v(\text{mid}) \frac{1}{\sqrt{1 + \left[\frac{\omega}{\omega_{CA}}\right]^2}} \quad \leftarrow \text{LPF}$$


$$\rightarrow \text{at } \omega = \omega_H = \omega_{CA}$$

$$\therefore |A(j\omega_H)| = A_v(\text{mid}) \frac{1}{\sqrt{2}}$$

$$\rightarrow \omega_H C_A (R_s // R_i) = 1$$

End of L27

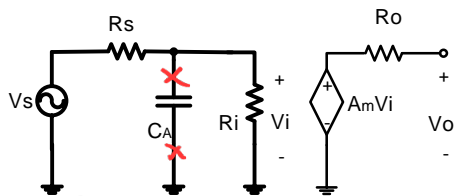
Shunt Capacitance and High frequency response



$$\rightarrow \omega_H C_A (R_s // R_i) = 1$$


$$\therefore \omega_H = \frac{1}{C_A (R_s // R_i)}$$

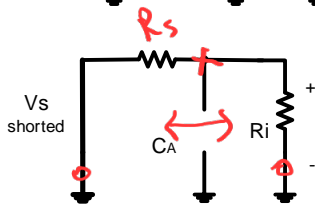where R_{th_A} is thevenin impedance seen by capacitor C_A




For $A_v(\text{mid}) = 1$

for $\omega = \omega_{CA} \rightarrow 20 \log |A(j\omega)| = 20 \log A_v(\text{mid}) - 20 \log 0.707 = -3 \text{ dB}$

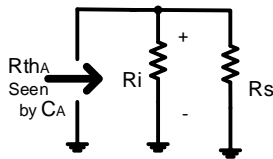

for $\omega = 10\omega_{CA} \rightarrow 20 \log |A(j\omega)| = -20 \log 10 = -20 \text{ dB} \leftarrow \text{low pass filter}$

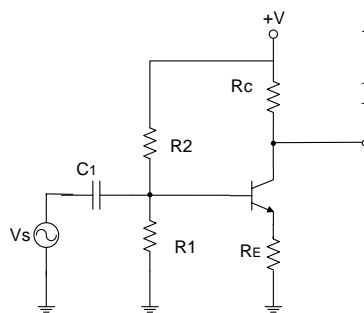Shunt Capacitance and High frequency response



Note :


1) If there is only one cap, we find $\omega_{CA} = \frac{1}{R_{thA} \cdot C1}$ and $\omega_H = \omega_{CA}$

2) If there is two caps C_A and C_B with ω_{CA} and ω_{CB} , then

$$A(j\omega) = Av(mid) \frac{1}{1 + \left(\frac{j\omega}{\omega_{CA}}\right)} \frac{1}{1 + \left(\frac{j\omega}{\omega_{CB}}\right)}$$


in order to find ω_H , we find magnitude of the gain at ω_H

$$|A(j\omega_H)| = \frac{Av(mid)}{\sqrt{2}} = \frac{Av(mid)}{\left[\left(1 + \left(\frac{j\omega}{\omega_{CA}}\right)\right) \left(1 + \left(\frac{j\omega}{\omega_{CB}}\right)\right) \right]}$$

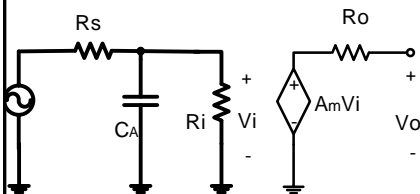

Shunt Capacitance and High frequency response

By solving for the magnitude of the gain $A(j\omega)$ at $\omega = \omega_H$
yields for an approximation for the lower and upper limit to estimate ω_H
for $\omega_{CA} \gg \omega_{CB}$


$$\frac{1}{\frac{1}{\omega_{CA}} + \frac{1}{\omega_{CB}}} < \omega_H < \omega_{CB}$$

$$\frac{\omega_{CA} \cdot \omega_{CB}}{\omega_{CA} + \omega_{CB}} < \omega_H < \omega_{CB}$$



$$\text{lower limit} < \omega_H < \text{Smallest } \omega$$

High Frequency Response Example

- Calculate the high frequency corner frequencies due to C_{gs} , C_{gd} and estimate ω_H ?

-High frequency ac small signal equivalent circuit is constructed (here all low frequency caps C_1 , C_2 and C_3 are considered as short circuits)

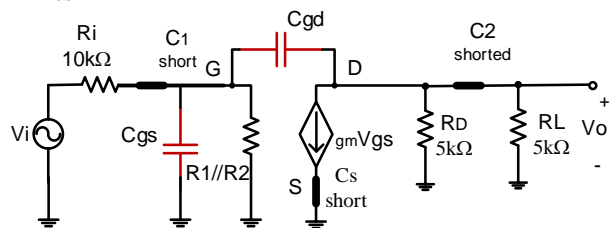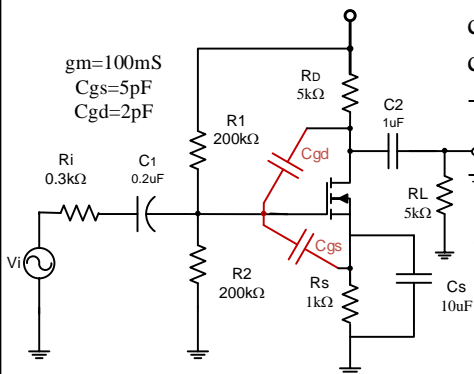- We consider one capacitor each time , while all others are considered open circuit and its corresponding ω is found Finally, ω_H is estimated using the formula for upper and lower limits



Effect of each Capacitor & ω_H

- We Calculate the high frequency corner frequencies due to each high frequency cap acting alone while all others are considered as open circuit


1) Consider C_{gs} (while C_{gs} is open , C_1, C_2 & C_s are shorted)

$$\omega_{C_{gs}} = \frac{1}{C_{gs} \cdot R_{gs}}$$

R_{gs} is the thevenin impedance seen by C_{gs}

$$R_{gs} = R_1 // R_2 // R_i$$

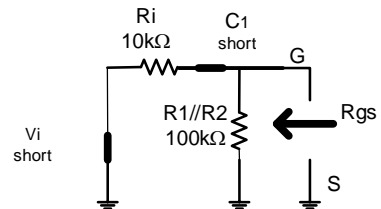
$$\omega_{C_{gs}} = 668.45 \text{ Mrad/sec;}$$



Effect of each Capacitor & ω_H


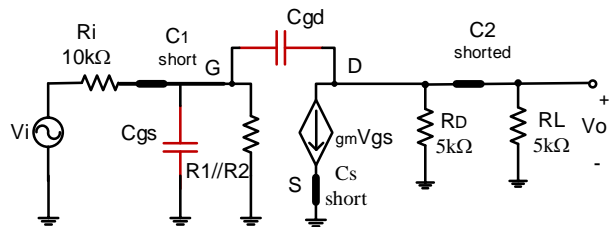
2) Consider C_{gd} (while C_{gs} is open , C_1, C_2 & C_s are shorted)

$$\omega_{C_{gd}} = \frac{1}{C_{gd} \cdot R_{gd}}$$



Effect of Capacitor Cgd

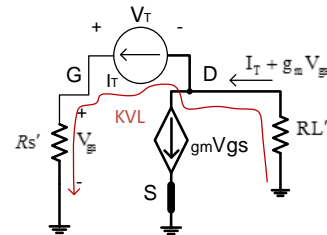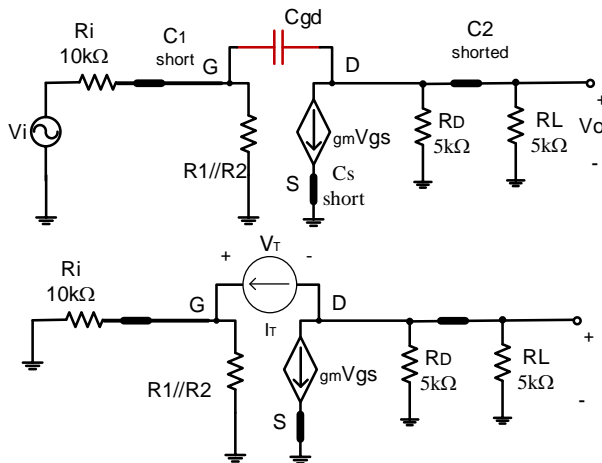- Calculation of Rgd is done through test current /voltage method



KVL :

$$R_L'(I_T + g_m V_{gs}) + I_T R_s' = V_T$$

$$\text{but } V_{gs} = V_g - V_s = R_s' I_T$$

substituting yeilds

$$R_L'(I_T + g_m R_s' I_T) + I_T R_s' = V_T$$

$$R_{gd} = \frac{V_T}{I_T} = R_L' + R_s' + g_m R_L' R_s'$$

$$R_L' = R_D // R_L \quad \text{and} \quad R_s' = R_i // R_1 // R_2$$

Effect of each Capacitor & ω_H

Now

$$\omega_{Cgd} = \frac{1}{Cgd.Rgd} = 48.54 \text{ Mrad/sec;}$$





3) Estimation of the ω_H

$$\frac{(\omega_{gd} \bullet \omega_{gs})}{(\omega_{gd} + \omega_{gs})} < \omega_H < 48.45$$

$$45.25 < \omega_H < 48.45$$

Effect of each Capacitor & ω_H

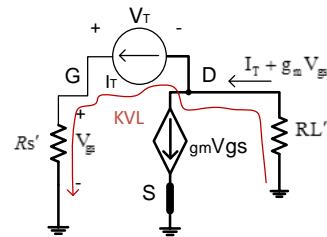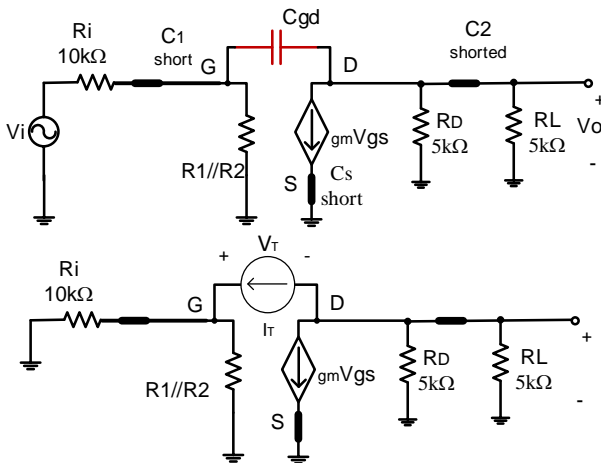- Calculation of R_{gd} is done through
- test current /voltage method



$$\text{KVL : } RL'(I_T + g_m V_{gs}) + I_T R_{s'} = V_T$$

$$\text{but } V_{gs} = V_g - V_s = R_{s'} I_T$$

substituting yeilds


$$RL'(I_T + g_m R_{s'} I_T) + I_T R_{s'} = V_T$$

$$R_{gd} = \frac{V_T}{I_T} = RL' + R_{s'} + g_m RL' R_{s'}$$


$$RL' = R_D // R_L \quad \text{and} \quad R_{s'} = R_i // R_1 // R_2$$

BJT High Frequency Response

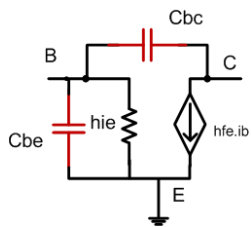
- Capacitors Cbe and Cbc
- CE and CC model



Convert to
 a form
 similar to
 FET

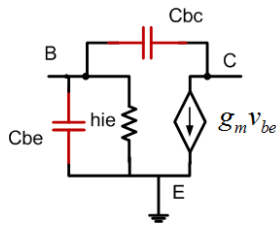

CB model

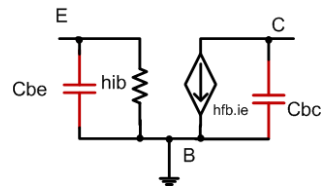

$hfb = \alpha = -1$

$$h_{fe} \cdot i_b = h_{fe} \frac{v_{be}}{h_{ie}} = g_m v_{be};$$

where

$$\frac{h_{fe}}{h_{ie}} = g_m$$

CE Example:


- Estimate the high corner frequency for the following BJT amplifier

1) Effect of Cbe (Cbc is considered open) High Frequency Small Signal equivalent Circuit

$$\omega_{be} = \frac{1}{C_{be} \cdot R_{be}};$$

where R_{be} is the thevenin impedance seen by C_{be}
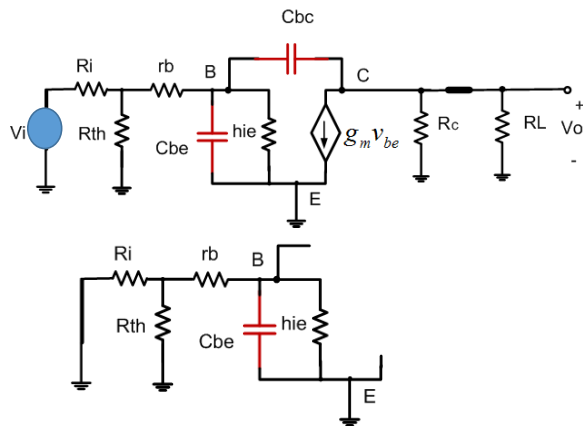
$$R_{be} = ((R_i // R_{th}) + r_b) // h_{ie}$$





CE Example:

2) Effect of C_{bc} (C_{be} is considered open)

$$\omega_{bc} = \frac{1}{C_{bc} \cdot R_{bc}};$$

where R_{bc} is the thevenin

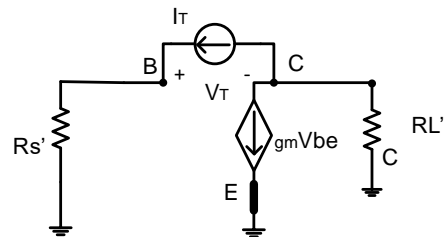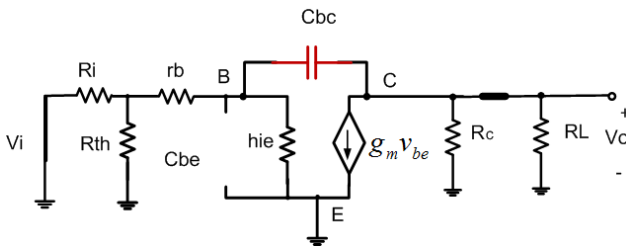impedance seen by C_{bc} and it is found by V_T/I_T method



$$RL'(I_T + g_m V_{be}) + I_T R_s' = V_T$$

$$\text{but } V_{be} = V_b - V_e = R_s' I_T$$

substituting yeilds

$$RL'(I_T + g_m R_s' I_T) + I_T R_s' = V_T$$

$$R_{bc} = \frac{V_T}{I_T} = RL' + R_s' + g_m RL' R_s'$$

$$R_s' = (R_i / R_{th} + r_b) // h_{ie}$$

CE Example:

- Given the following values in previous example

$$g_m = 33.5 \text{ mS}$$

$$h_{ie} = 8.77 \text{ k}\Omega$$

$$h_{fe} = 294$$

$$R_s = 1 \text{ k}\Omega, R_1 // R_2 = 16.67 \text{ k}\Omega$$

$$r_b = 20 \text{ }\Omega; C_{bc} = 1.8 \text{ pF}; C_{be} = 17.25 \text{ pF}$$

$$R_c = 5 \text{ k}\Omega; R_L = 2 \text{ k}\Omega$$

calculate :

$$\omega_{bc} = \frac{1}{C_{bc} \cdot R_{bc}} = 66.7 \text{ Mrad/sec}$$

$$\omega_{be} = \frac{1}{C_{be} \cdot R_{bc}} = 12.67 \text{ Mrad/sec}$$

Estimate ω_H

$$\frac{(\omega_{be} \cdot \omega_{bc})}{(\omega_{be} + \omega_{bc})} < \omega_H < \omega_{be}$$

$$10.65 < \omega_H < 12.67$$

CB Example :

- Estimate the high corner frequency ω_H for the following BJT amplifier

1) Effect of C_{be} (C_{bc} is considered open)

$$\omega_{be} = \frac{1}{C_{be} \cdot R_{be}}; \text{ where } R_{be} \text{ is the thevenin}$$


impedance seen by C_{be}

$$R_{be} = ((R_s // R_E)) // h_{ib}$$

2) Effect of C_{bc}


$$\omega_{bc} = \frac{1}{C_{bc} \cdot R_{bc}};$$

$$\text{where } R_{bc} = R_L // R_C$$

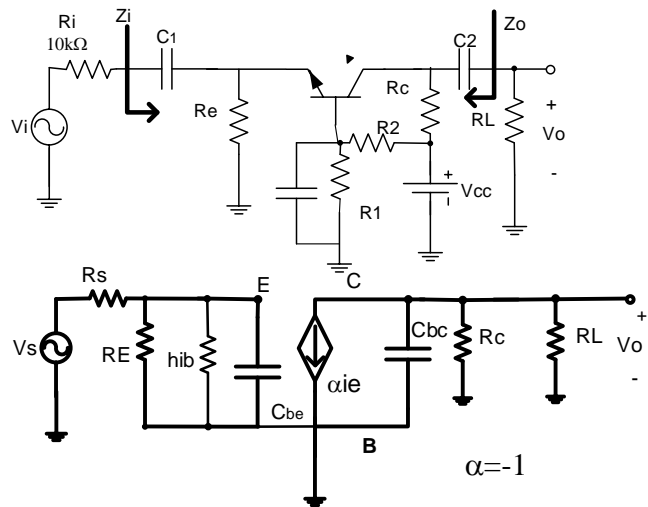



Practice Question : Amplifier Frequency Response

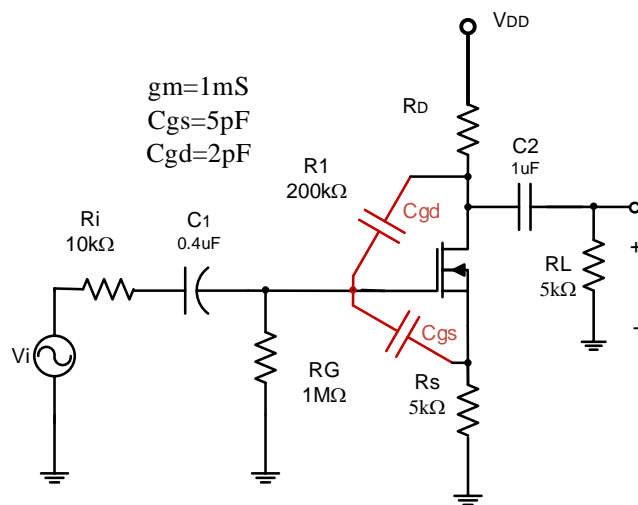- Estimate the value of **low** and **high** frequency corner frequencies and calculate the mid-range voltage gain of the following amplifier



Miller Theorem (another method to solve previous example)

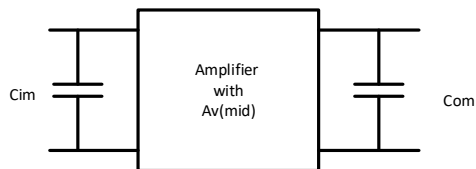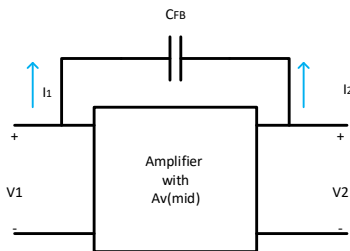- Miller theorem is used to simplify the analysis of inverting amplifiers only at high frequencies
- The feedback capacitor C_{bc} or C_{gd} is decomposed into two capacitors, one at the input C_{im} and one at the output C_{om} , whose values are found using the following formulas:



Input Miller Capacitance

$$C_{IM} = C_{FB} \left[1 - A_v(mid) \right]$$

Output Miller Capacitance

$$C_{OM} = C_{FB} \left[1 - \frac{1}{A_v(mid)} \right]$$

CE Example using Miller Theorem:

- Estimate the high corner frequency for the following BJT amplifier using miller theorem

- Calculate $A_v(\text{mid}) = \frac{V_y}{V_x}$

- Calculate $C_{IM} = C_{FB} [1 - A_v(\text{mid})]$;

$C_{FB} = C_{BC}$

- Calculate $C_{OM} = C_{FB} \left[1 - \frac{1}{A_v(\text{mid})} \right]$

- Calculate $\omega_{IM} = \frac{1}{(C_{IM} + C_{be})R_{be}}$

- Calculate $\omega_{OM} = \frac{1}{C_{OM}R_{ce}}$

- Estimate ω_L

