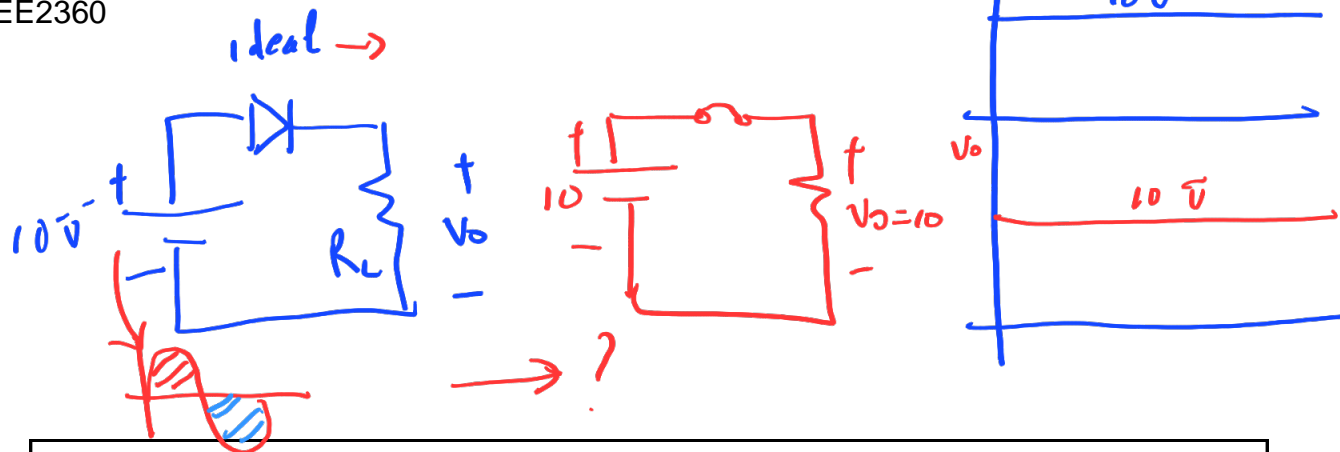


*L4 - Part 2
13/7/2021*

ENEE236
Analog Electronics

T3:
Diode Applications



Diode large – signal application

1) Diode clipper circuit ≡ Limiter


a) assume the diode is on
replace it with short circuit

$$i_D(t) > 0$$

$$i_D(t) = \frac{V_i(t)}{R_L} > 0$$


$\therefore V_i(t) > 0$ always positive

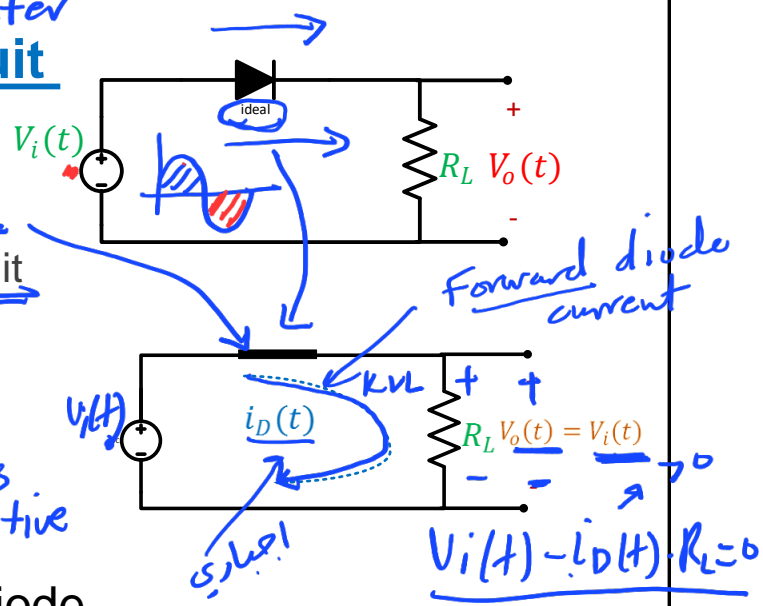\therefore when $V_i(t) > 0$, the diode is on and $V_o(t) = V_i(t)$





$$V_i(t) - i_D(t) \cdot R_L = 0$$

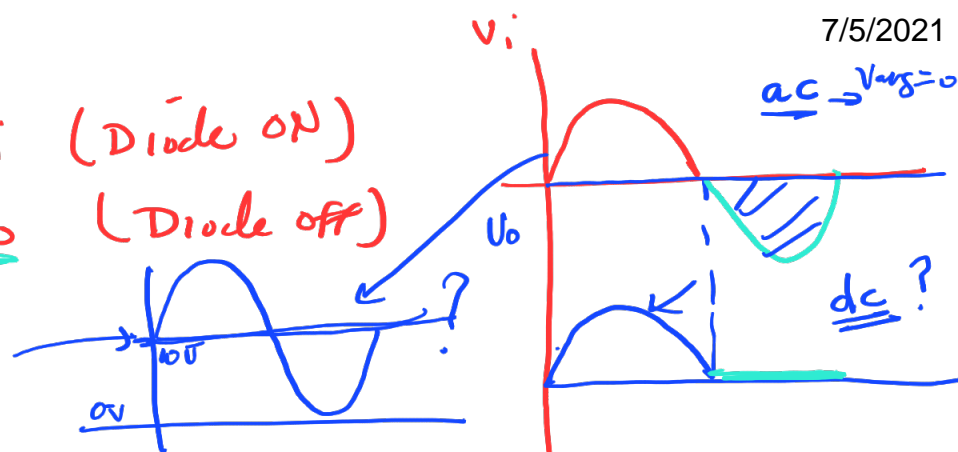$V_i(t) > 0 \rightarrow V_o = V_i$ (Diode ON)
 $V_i(t) < 0 \rightarrow V_o = 0$ (Diode OFF)



\therefore when $V_i(t) < 0$, the diode is off and $V_o(t) = 0$. $= i_D \cdot R_L$

$V_o(t) = 0$.

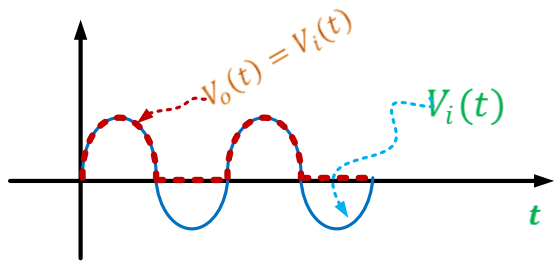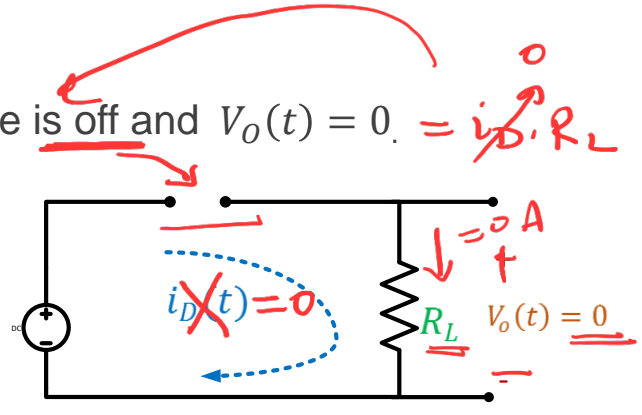




\therefore the clipper circuit used to eliminate portion of the input signal .

Example

a) assume that the diode is on

→ replace it with short circuit

$$i_D > 0$$

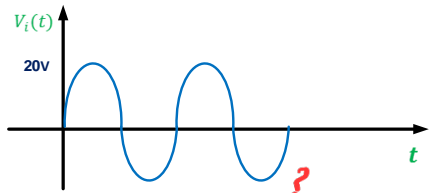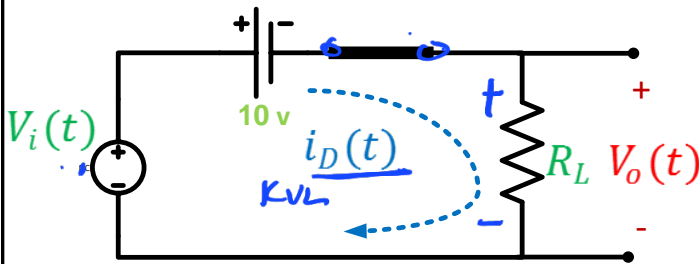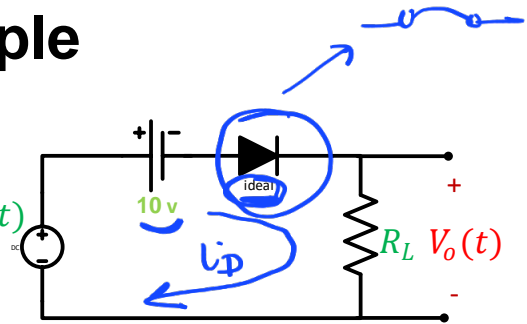

$$i_D(t) = \frac{V_i(t) - 10}{R_L} \geq 0$$

$$V_i(t) - 10 - \underbrace{i_D(t) \cdot R_L}_{V_o(t)} = 0$$

$$\left. \begin{array}{l} V_i - 10 > 0 \\ V_i > 10 \end{array} \right\} \begin{array}{l} \rightarrow \text{Diode ON} \\ \rightarrow \boxed{V_o = V_i(t) - 10} \end{array}$$

$$i_D(t) = \frac{V_i(t) - 10}{R_L} > 0$$



$$\therefore V_i(t) - 10 > 0$$

$$\therefore V_i(t) > 10$$

\therefore when $V_i(t) > 10$ V , the diode is on and $V_o(t) = V_i - 10$

and also we can prove that when $V_i(t) < 10$ V , the diode is off


$$\therefore V_o(t) = 0$$

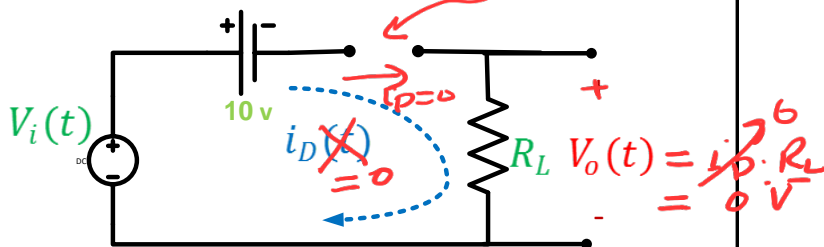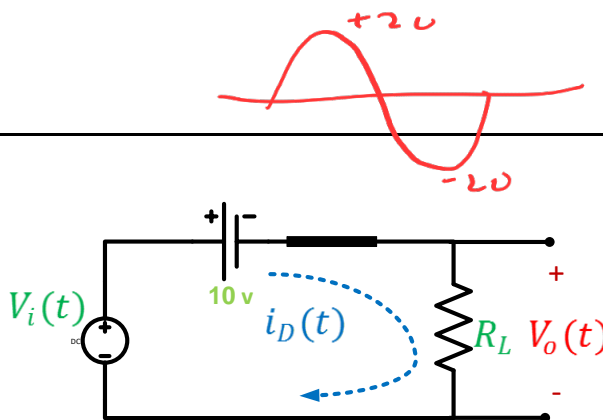




$V_i(t) > 10$ Diode ON
 $V_i(t) < 10$ Diode OFF

$$V_o = V_i(t) - 10$$

$$V_o = 0$$

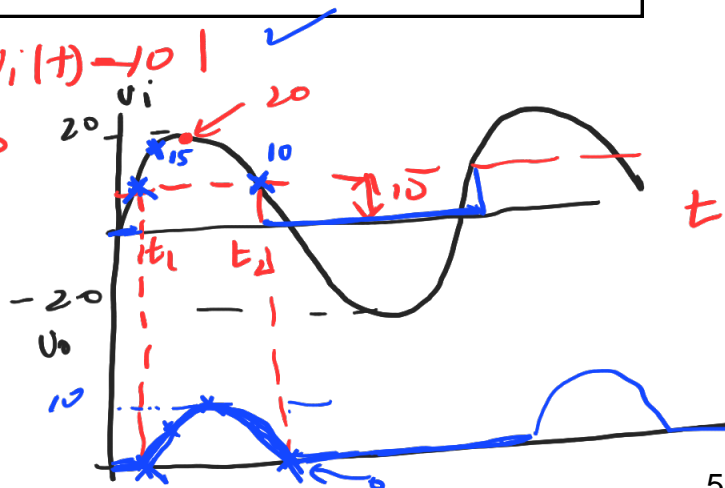

The output

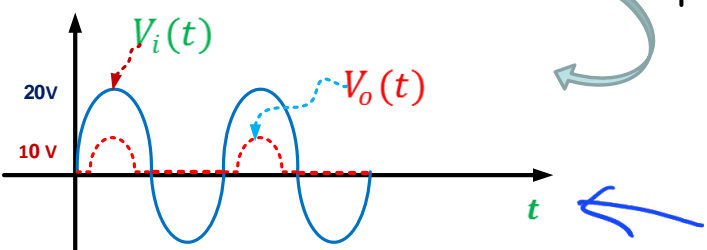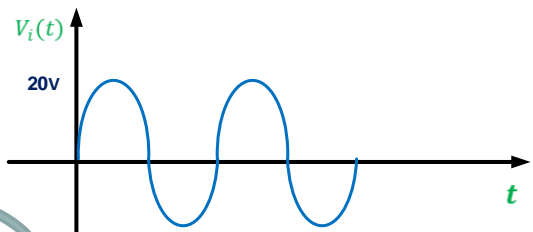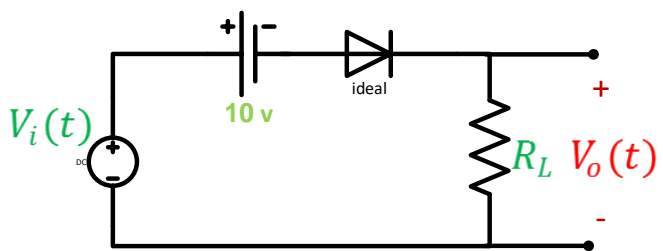


Second Method

assume that the diode is off, replace it with open circuit

$$V_D(t) < 0$$

$$V_D(t) = -10 + V_i$$

$$V_i(t) < 10 \text{ V}$$

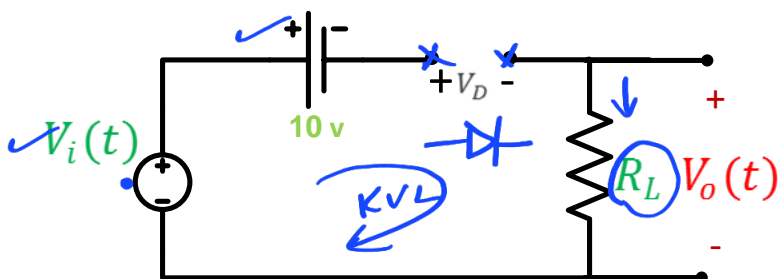

$$V_i - 10 - V_D = 0$$

$$V_D = V_i - 10$$



\therefore when $V_i(t) < 10 \text{ V}$, the diode is off and $V_o(t) = 0$

$V_i > 10$, " ON $V_o = V_i - 10$ ← see previous solution

ENEE236 – Analog Electronics


Limiters (=Clipping circuits) (1)

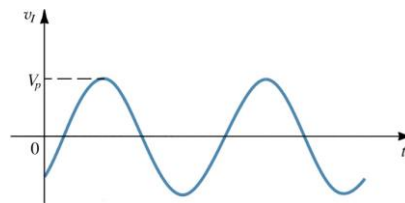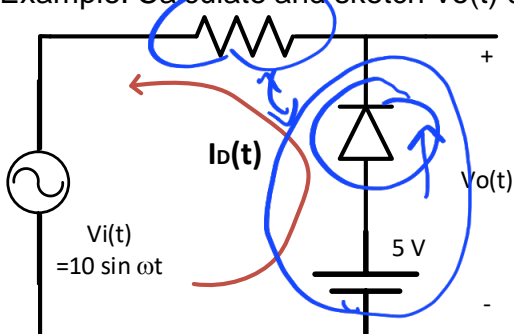Example: Calculate and sketch $V_o(t)$ using simplified diode model



$$5 = 0.7 + i_D R + V_i(t)$$

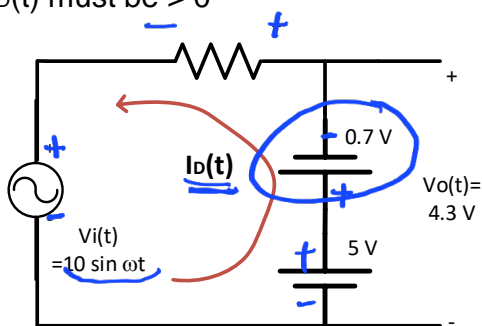1) Assume diode is ON, so we replace it by 0.7 V and $i_D(t)$ must be > 0




$$5V - 0.7V - i_D(t) \cdot R - V_i(t) = 0$$

$$i_D(t) \cdot R = 4.3V - V_i(t)$$

$$i_D(t) = \frac{4.3V - V_i(t)}{R} > 0$$

ENEE236 – Analog Electronics

Limiters (=Clipping circuits) (2)

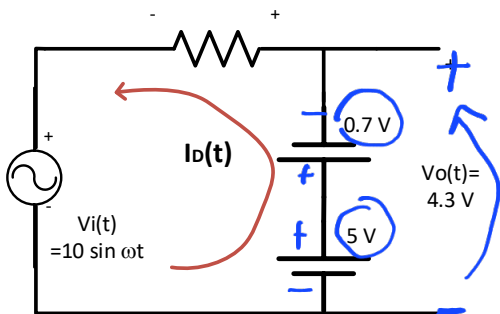


$$\therefore 4.3\text{V} - V_i(t) > 0$$

$$\Rightarrow \underline{V_i(t) < 4.3\text{V}}$$

when $V_i(t) < 4.3\text{V}$ diode is ON and
 $V_o(t) = 4.3\text{V}$

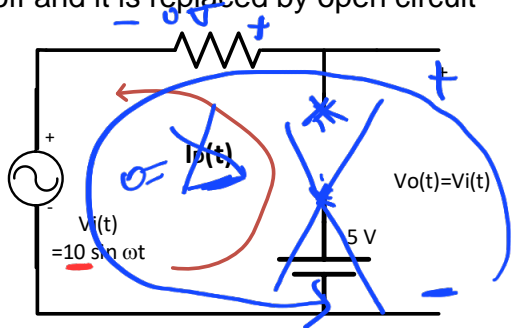2) Otherwise, When $V_i(t)$ is $> 4.3\text{V}$, Diode will be off and it is replaced by open circuit




$$\Rightarrow V_i(t) > 4.3\text{V}$$

$$V_o(t) = V_i(t)$$

$$V_o(t) - V_i(t) = 0$$

$$\boxed{V_o(t) = V_i(t)}$$

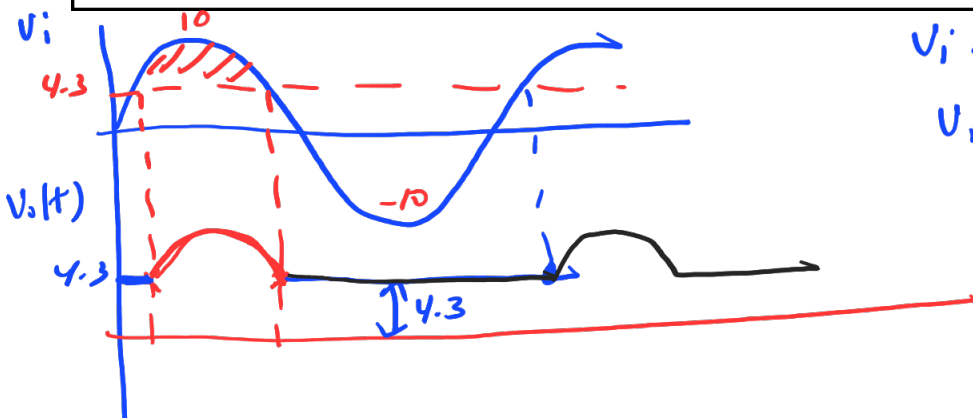


$$V_i < 4.3 \rightarrow \underline{V_o = 4.3}$$

$$V_i > 4.3 \rightarrow \underline{V_o = V_i}$$

ENEE236 – Analog Electronics

Limiters (=Clipping circuits) (3)

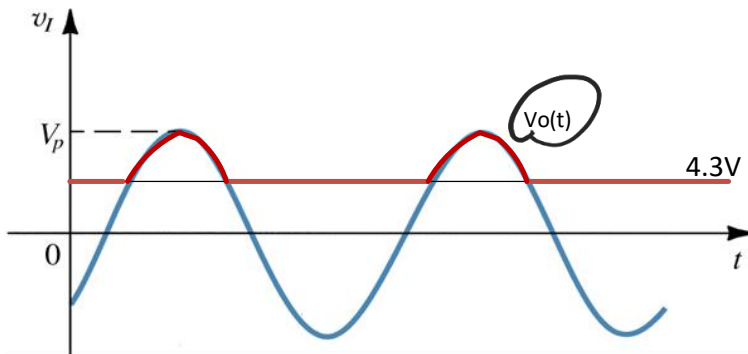when $V_i(t) < 4.3V$, diode is ON & $V_o(t) = 4.3V$
when $V_i(t) > 4.3V$, diode is off & $V_o(t) = V_i(t)$





✓
summary
↓
sketch

ENEE236 – Analog Electronics

Circuit Containing Two diodes

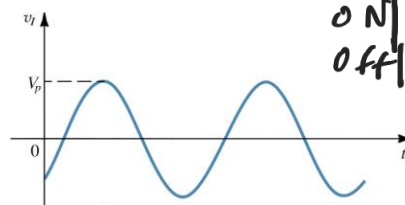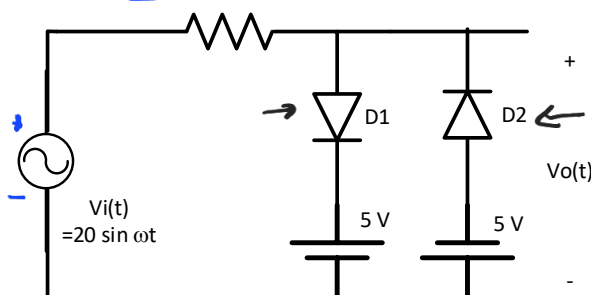Example: Calculate and sketch $V_o(t)$ using ideal diode model



D1	D2
ON	OFF
OFF	ON
ON	ON
OFF	OFF

Since the circuit contains two diodes, each of them can be either On or Off,

→ then there is 4 possible combinations for the states of D1 and D2


L5
14/7/2021

ENEE236 – Analog Electronics

- 1) Assume D1 is ON and D2 is OFF
 $i_{D1}(t) > 0$

$$i_{D1}(t) = \frac{V_i(t) - 5}{R} > 0$$

when $V_i(t) > 5 \text{ V}$, $V_o(t) = 5 \text{ V}$

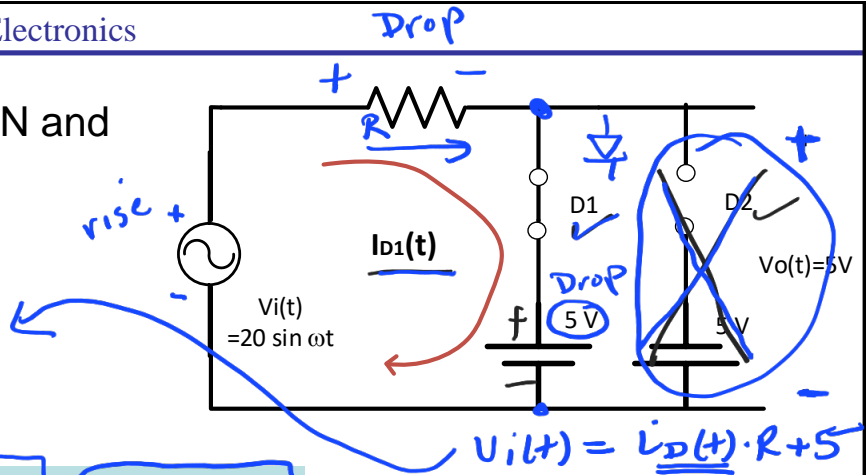


ENEE236 – Analog Electronics

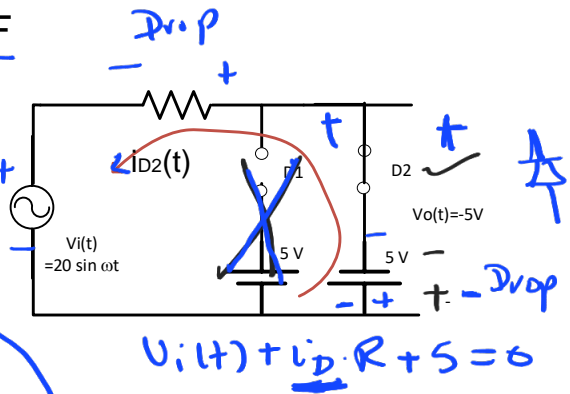
2) Assume D2 is ON and D1 is OFF

$$i_{D2}(t) > 0$$

$$i_{D2}(t) = \frac{-V_i(t) - 5}{R} > 0$$



when $V_i(t) < -5V$, $V_o(t) = -5V$ ✓

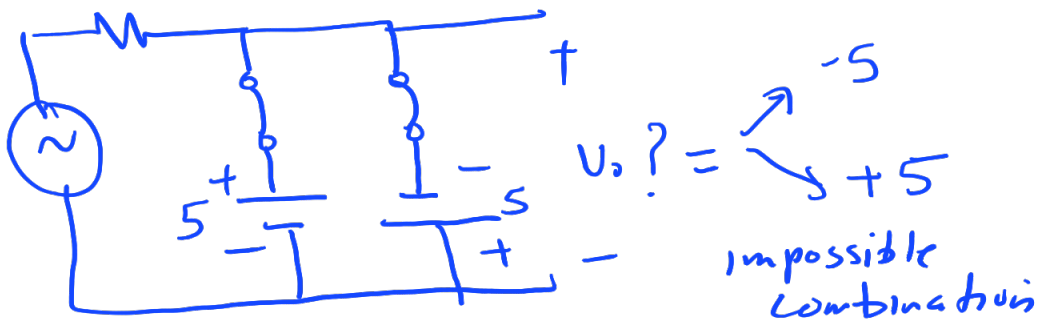


ENEE236 – Analog Electronics

3) Assume D1 & D2 are ON

$V_o = +5V$??

$V_o = -5V$??

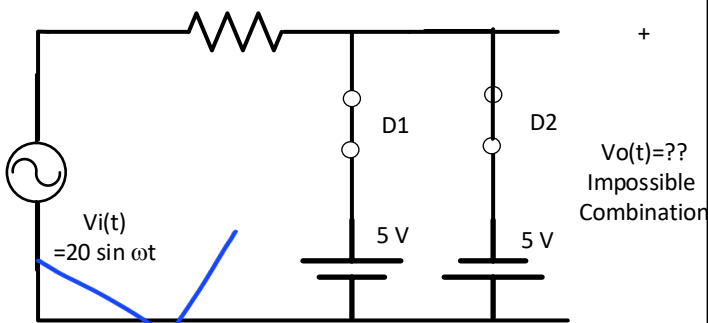



This is invalid configuration and impossible to occur

$$V_i > 5 \rightarrow V_o = 5$$

$$V_i < -5 \rightarrow V_o = -5$$

$-5 < V_i < 5$?

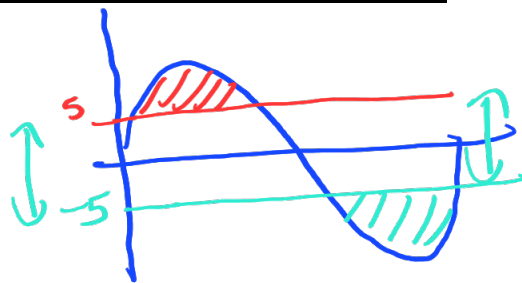


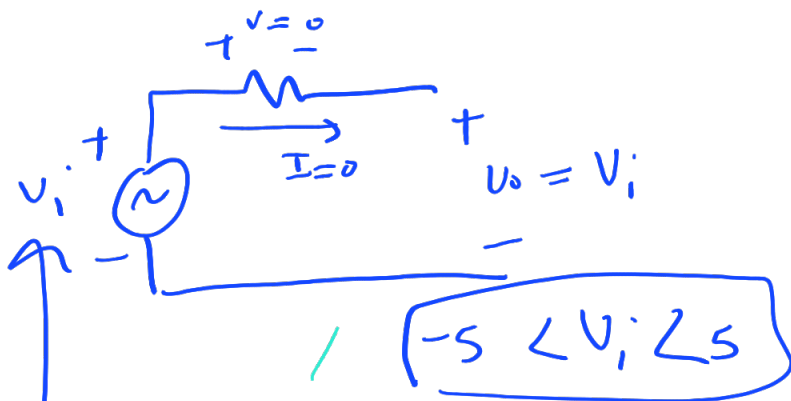

ENEE236 – Analog Electronics


4) Assume D1 & D2 are both OFF

$V_o(t) = V_i(t)$

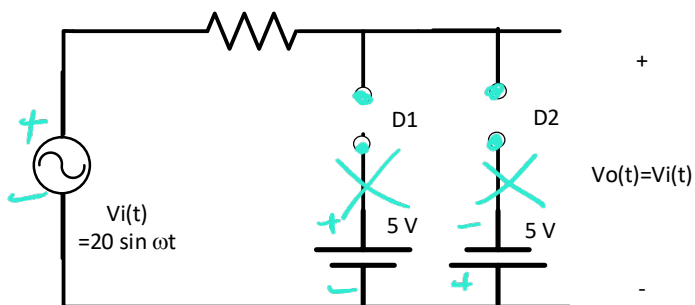



This occurs for the remaining part of the input voltage waveform:

$-5V < V_i(t) < 5V$

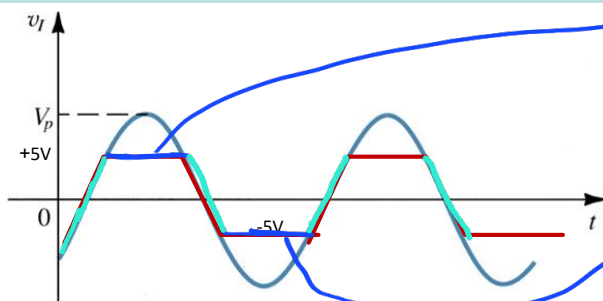

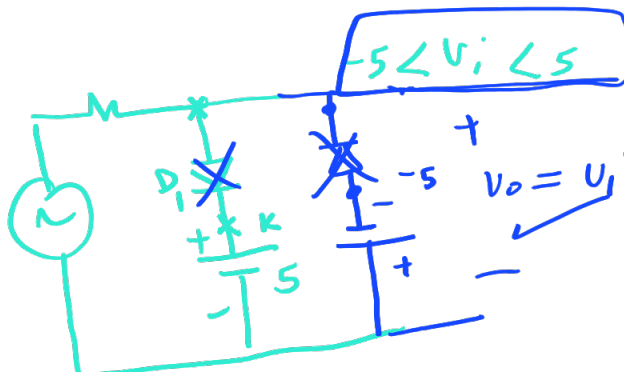$V_o = 5, V_i > 5$
 $V_o = -5, V_i < -5$
 $V_o = V_i, -5 < V_i < 5$



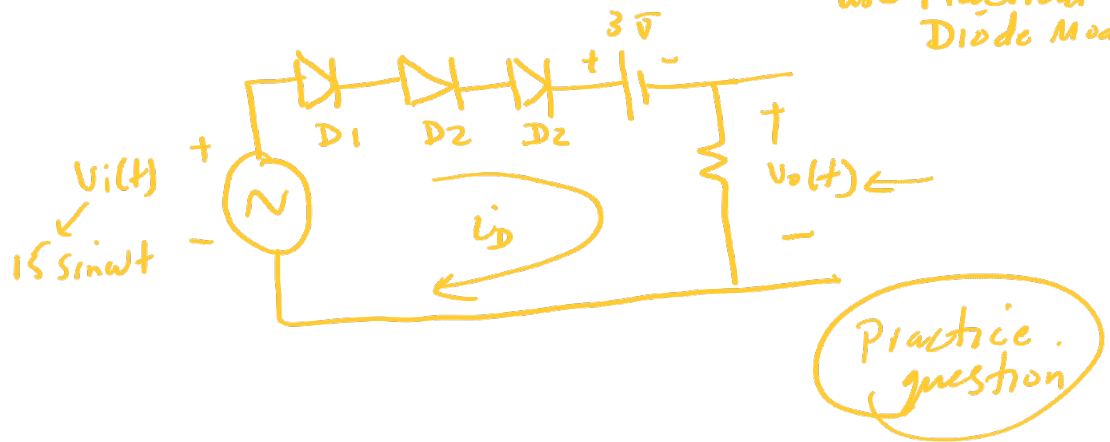

Summary of Clipper Circuits

HW for Practice

Simple Series Clippers (Ideal Diodes)

POSITIVE

NEGATIVE

Biased Series Clippers (Ideal Diodes)






POSITIVE

NEGATIVE











Summary of Clipper Circuits


HW for Practice

Simple Parallel Clippers (Ideal Diodes)

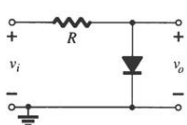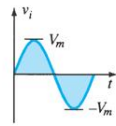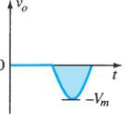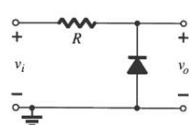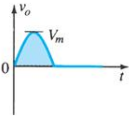Biased Parallel Clippers (Ideal Diodes)

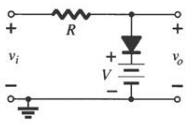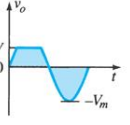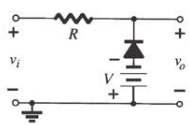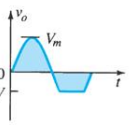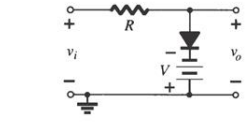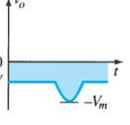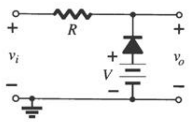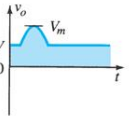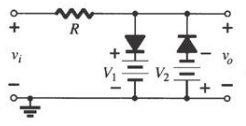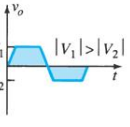



ENEE236 – Analog Electronics

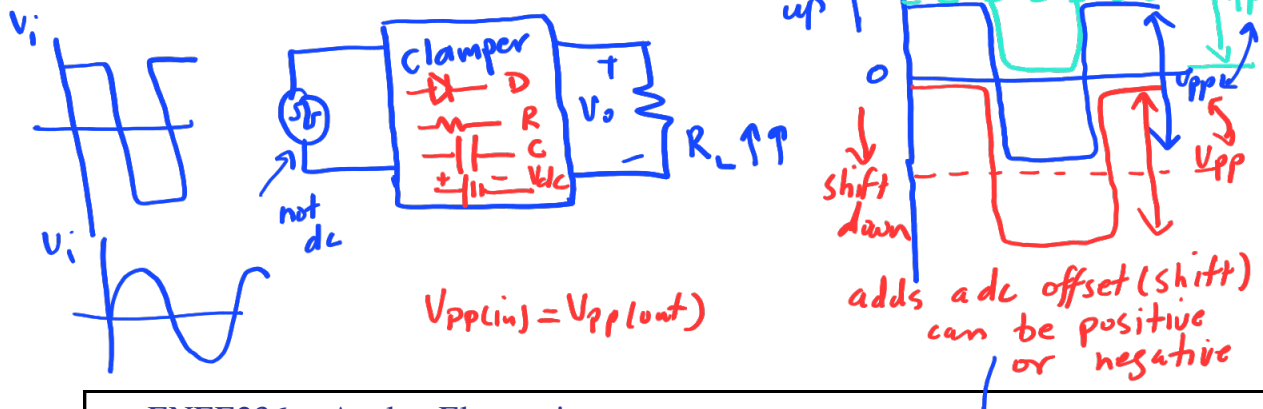Clampers

Function: A Clamper shifts the input waveform up or down (adds a dc offset) while keeping its shape and peak to peak value unchanged.

It consists of a diode and capacitor (and maybe a series dc source) that can be combined to “clamp” an AC signal to a specific DC level and supply it to the load R


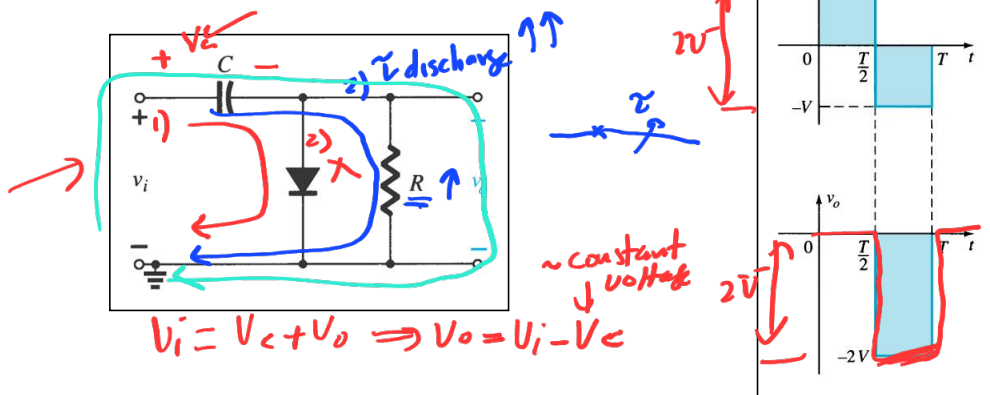


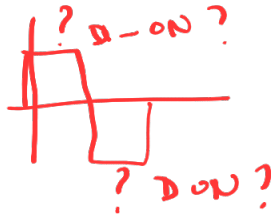

ENEE236 – Analog Electronics

Steps for Clamper Circuit Analysis


- ** 1) Start analysis by examining the portion of input that will forward bias the diode**
- 2) During diode On period, assume that the cap is charged instantaneously to a voltage level defined by surrounding network**
- 3) During OFF period, assume the cap holds the established voltage level (i.e. it behaves as constant dc voltage source)**
- 4) Consider value and polarity of V_o ←**
- * 5) Check that total swing (peak to peak) of output equal swing of input.**

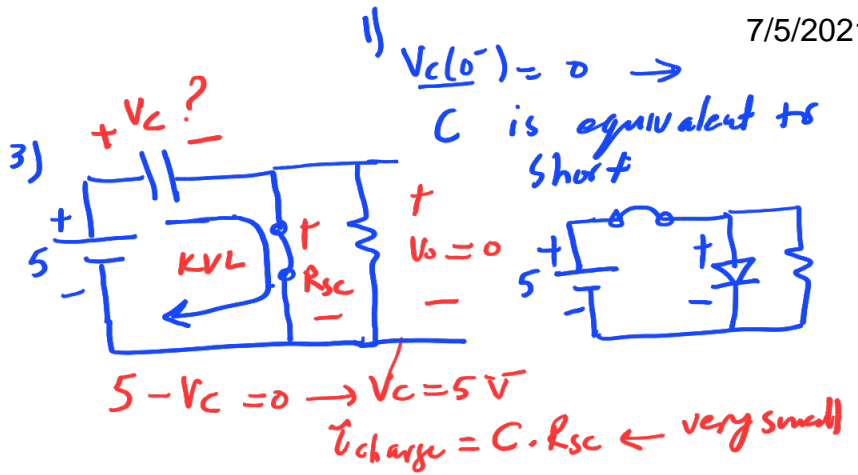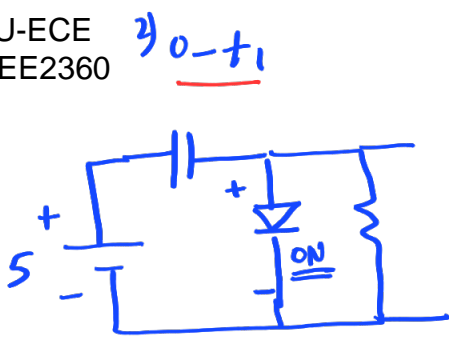

ENEE236 – Analog Electronics


Example

Find and sketch $V_o(t)$?

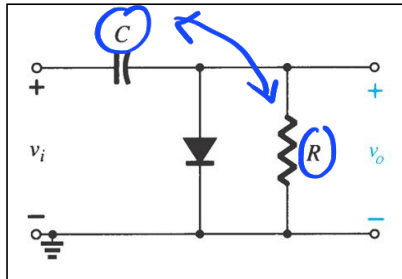

in steady state

clamping action

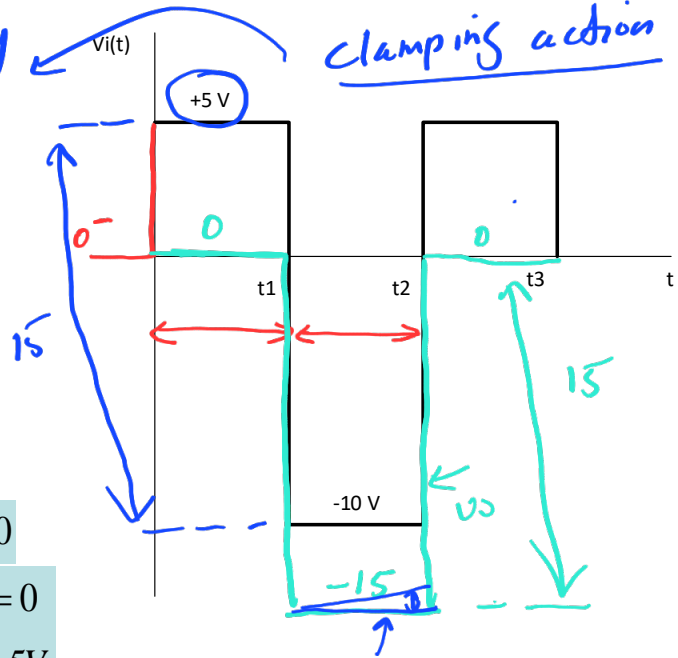

1) For $t < 0$ ($t = 0^-$) $V_C(0^-) = 0$


2) For $t > 0$ ($t = 0^+$) $V_C(0^+) = 0$

$V_i(0^+) = 5V$

$\Rightarrow D1$ is ON and it is replaced by short circuit


3) for $0^+ < t < t_1$ equivalent circuit is \Rightarrow see next page

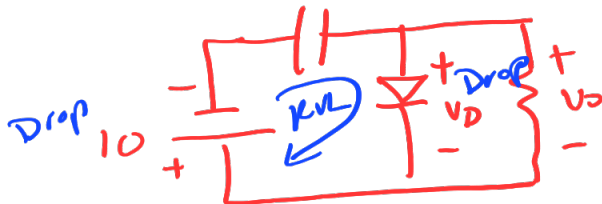4) $t_1 - t_2 \rightarrow V_i = -10, V_C = 5V^-, \text{ Diode ?!}$
Drop +5 -





$10 + 5 + V_D = 0$

$V_D = -15 < 0 \rightarrow D$ is off

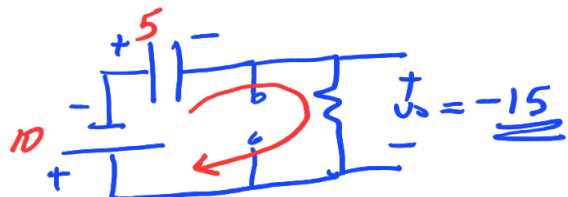


ENEE236 – Analog Electronics

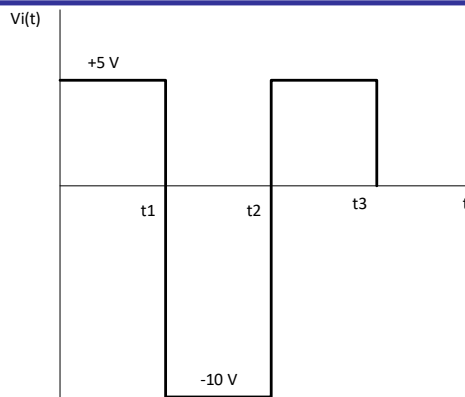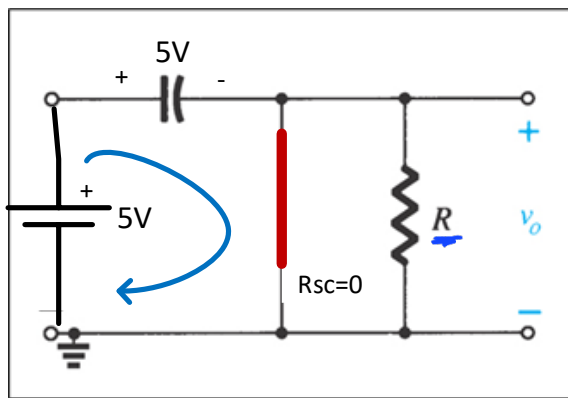

⇒ $D1$ is ON, Cap charges instantously to +5V with shown polarity since $\tau_{\text{charge}} = R_{sc} \cdot C \cong 0$ and $V_o(t) = 0\text{ V}$ ✓



4) for $t_1 < t < t_2$ voltage source reverses polarity, $V_i(t) = -10\text{V}$ while Cap keeps its charge $V_c = 5\text{V}$ since $\tau_{\text{discharge}} = R \cdot C$ is large

ENEE236 – Analog Electronics

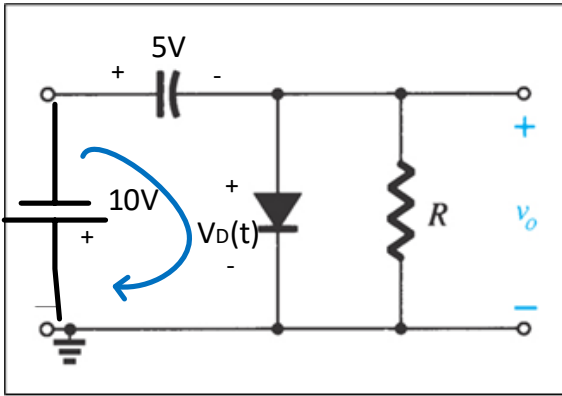


KVL around the loop: $-10 - 5 - V_D(t) = 0$
 $\Rightarrow V_D(t) = -15 \text{ V} < 0, \therefore \text{diode is OFF}$

$V_i(t)$

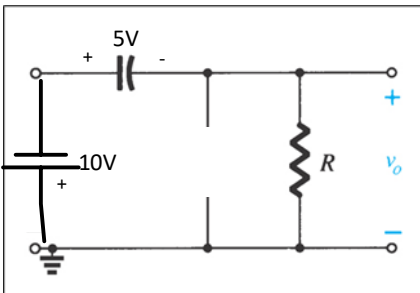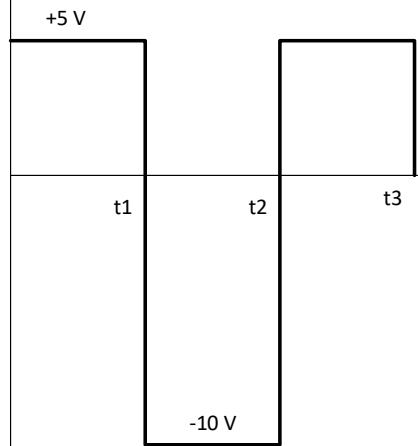


$V_o(t) = V_D(t) = -15 \text{ V}$


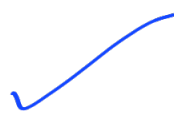


ENEE236 – Analog Electronics

5) for $t_2 < t < t_3$, $V_i(t) = 5V$
 while $V_C = 5V$
 $V_D(t) = 5 - 5 = 0$

Diode is OFF and it will remain always off no matter what happens to $V_i(t)$
 $V_o(t) = V_D(t) = V_i(t) - 5$


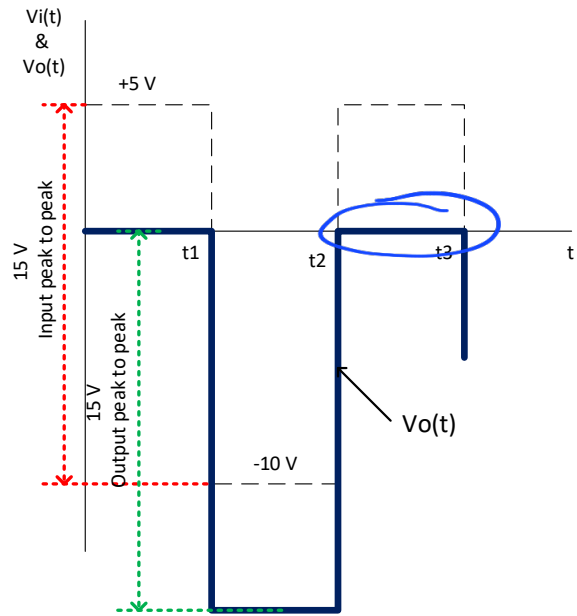


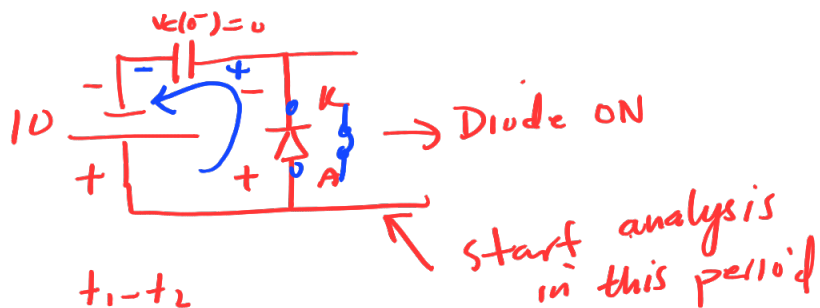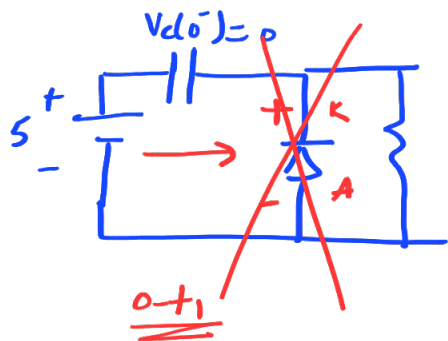

ENEE236 – Analog Electronics

Example




What happens if the diode was inverted

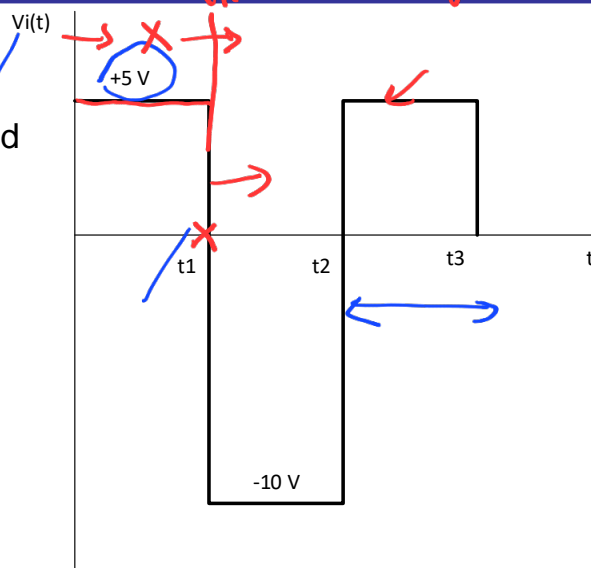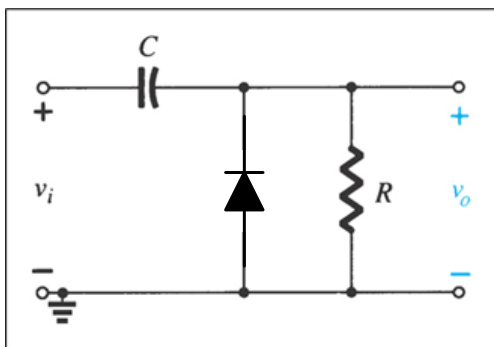


1) Consider $t_1 < t < t_2$ which makes the diode ON

$\Rightarrow D$ is ON and it is replaced by short circuit



$V_o(t) = 0V$

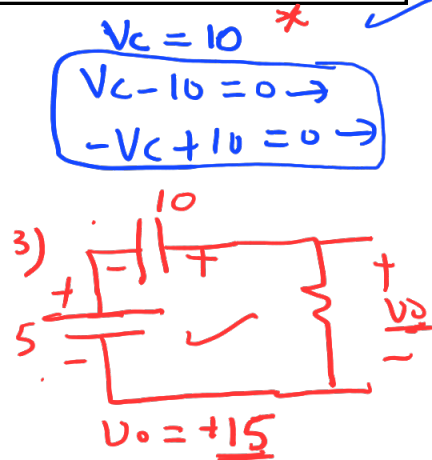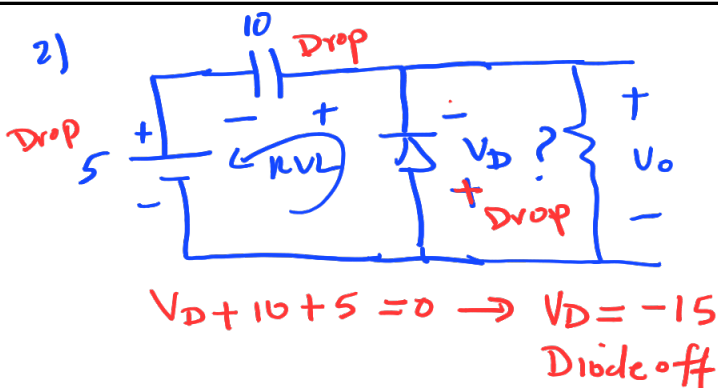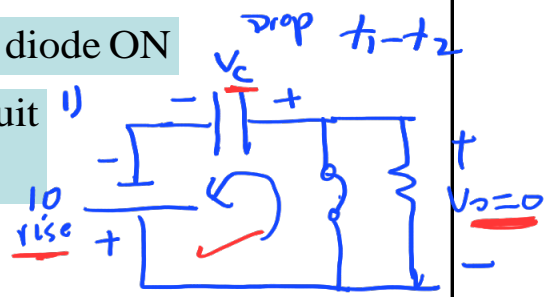

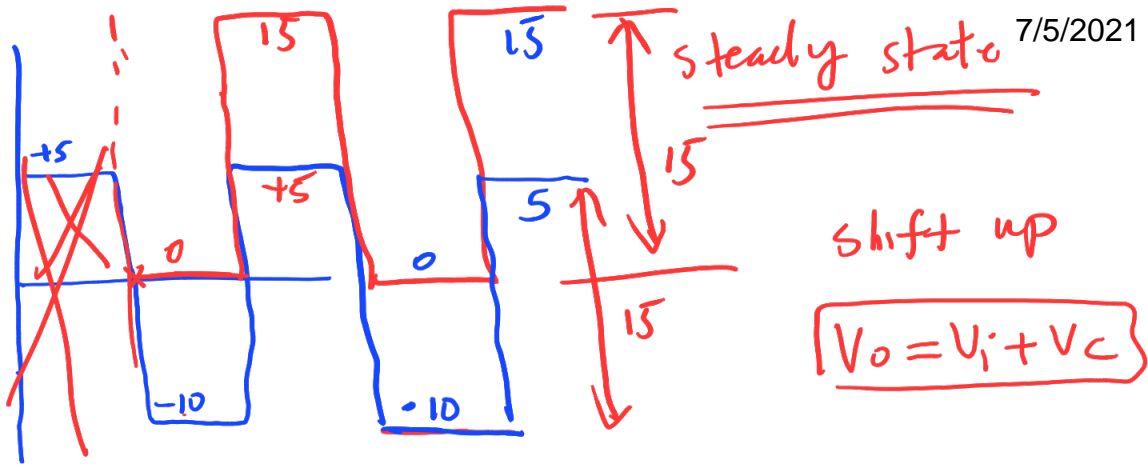


ENEE236 – Analog Electronics

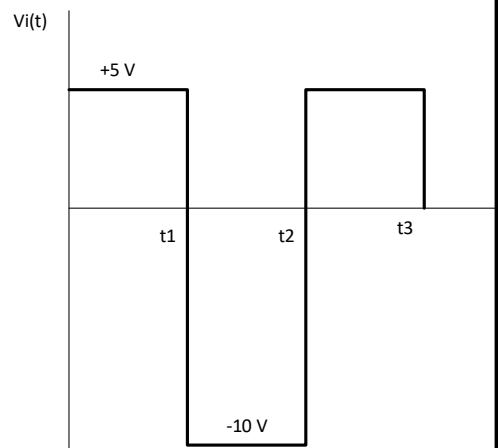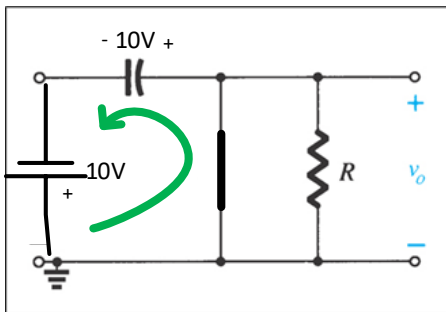Cap is charged to 10V with shown polarity due to diode forward current $V_o(t) = 0$ V





2) for $t_2 < t < t_3$ voltage source reverses polarity, $V_i(t) = +5$ V while Cap keeps its charge $V_c = 10$ V

ENEE236 – Analog Electronics

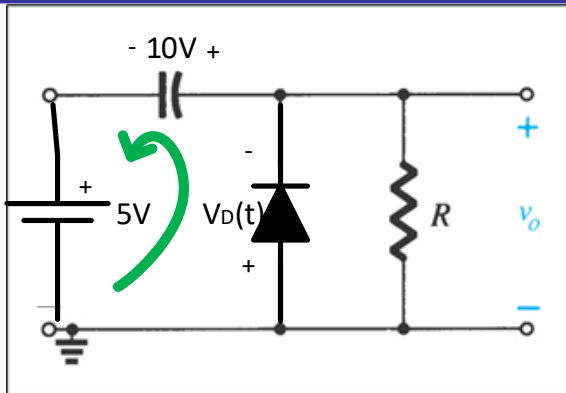

KVL around the loop: $10 + 5 + V_D(t) = 0$
 $\Rightarrow V_D(t) = -15 \text{ V} < 0, \therefore$ diode is OFF

$V_i(t)$

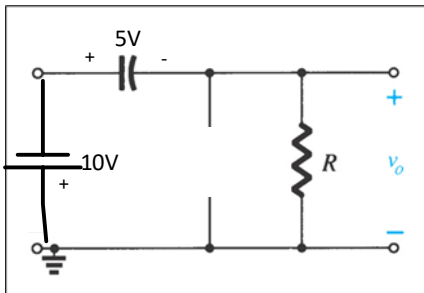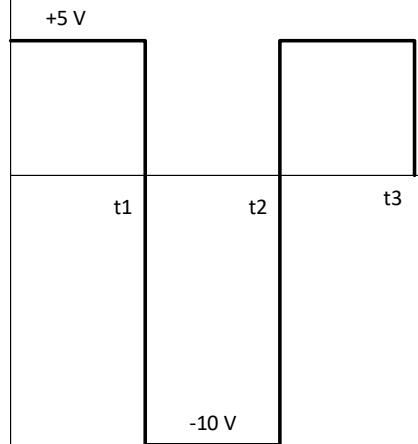

$V_o(t) = -V_D(t) = 15 \text{ V}$

ENEE236 – Analog Electronics


Afterwards for any value of the given $V_i(t)$ diode remains OFF and $V_o(t) = V_i(t) + 10$


∴ the clamper charges a cap and uses this charge to add up to the input to shift it up or down (i.e. add dc offset)

Important Note *

For Proper Clamping action, $\tau_{discharge}$ must be large enough (at least 10 times the period of the input waveform)



$$\tau_{discharge} = R.C > 10 (t_1 + t_2)$$

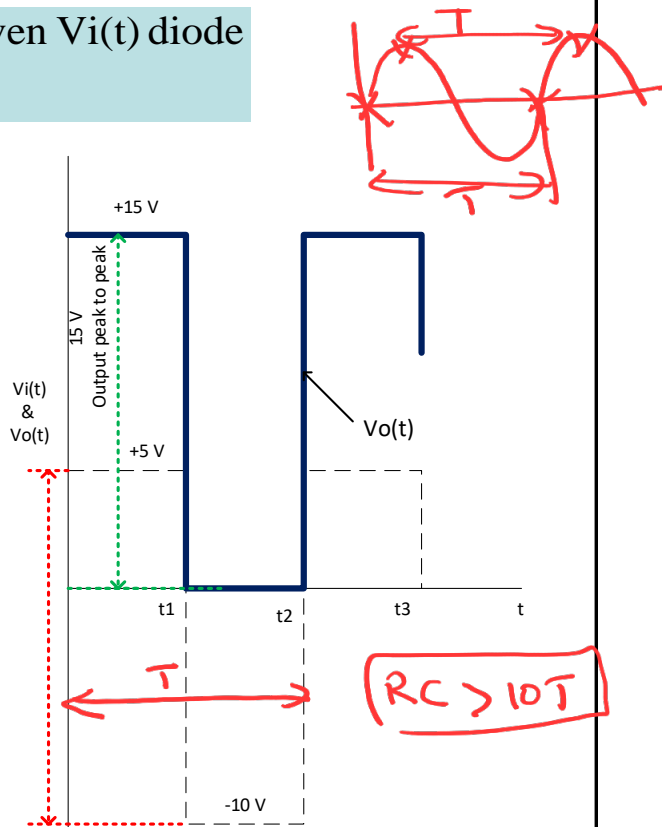

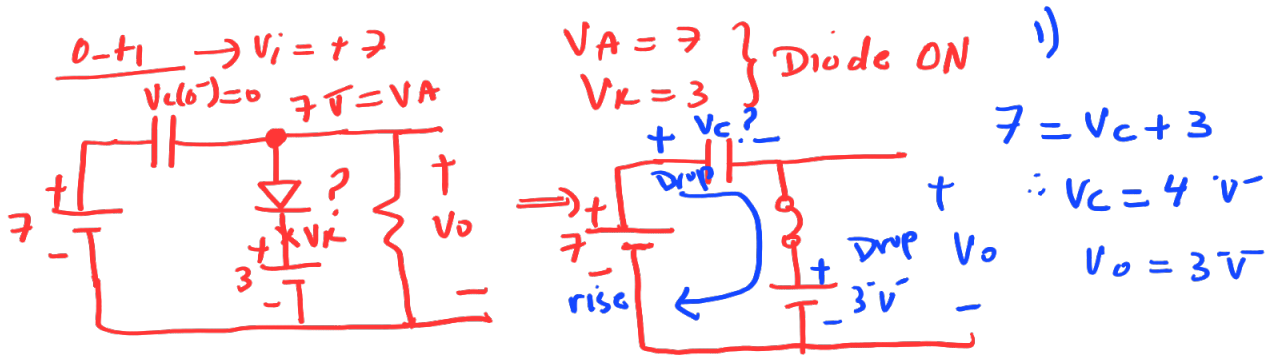

ENEE236 – Analog Electronics

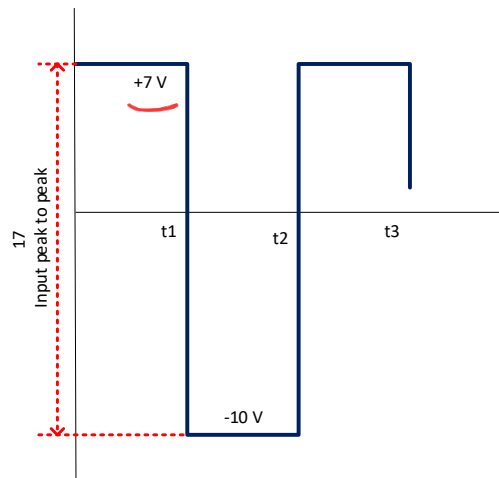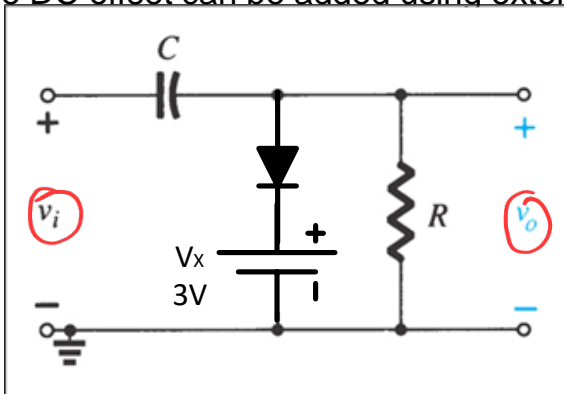
More DC offset can be added using external voltage source



1) When $V_i = +7 \text{ V}$
 $7 - V_C(t) - V_X = 0$
 $\therefore V_C(t) = 7 - 3 = 4 \text{ V}$
 $\Rightarrow V_O(t) = V_X = 3 \text{ V}$


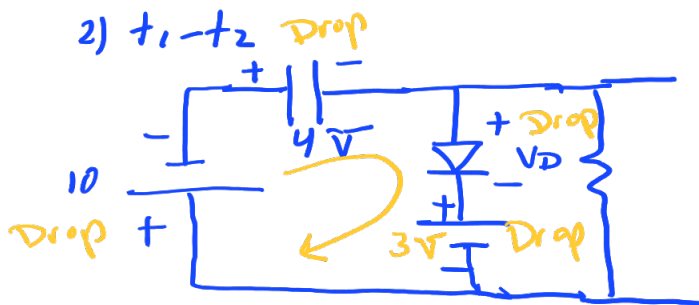
2) for $V_i = -10 \text{ V}$
 $-10 - 4 - V_D(t) - 3 = 0$
 $\Rightarrow V_D(t) = -17 \text{ V} < 0$ and diode is OFF

$\Rightarrow V_O(t) = V_i(t) - V_C(t)$
 $= V_i(t) - 4$
 $= -10 - 4 = -14 \text{ V}$



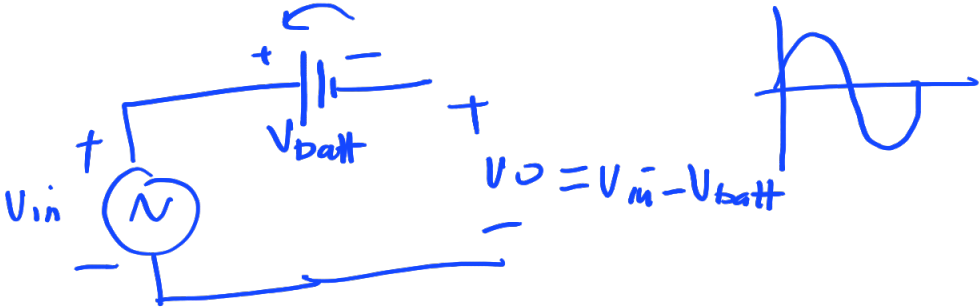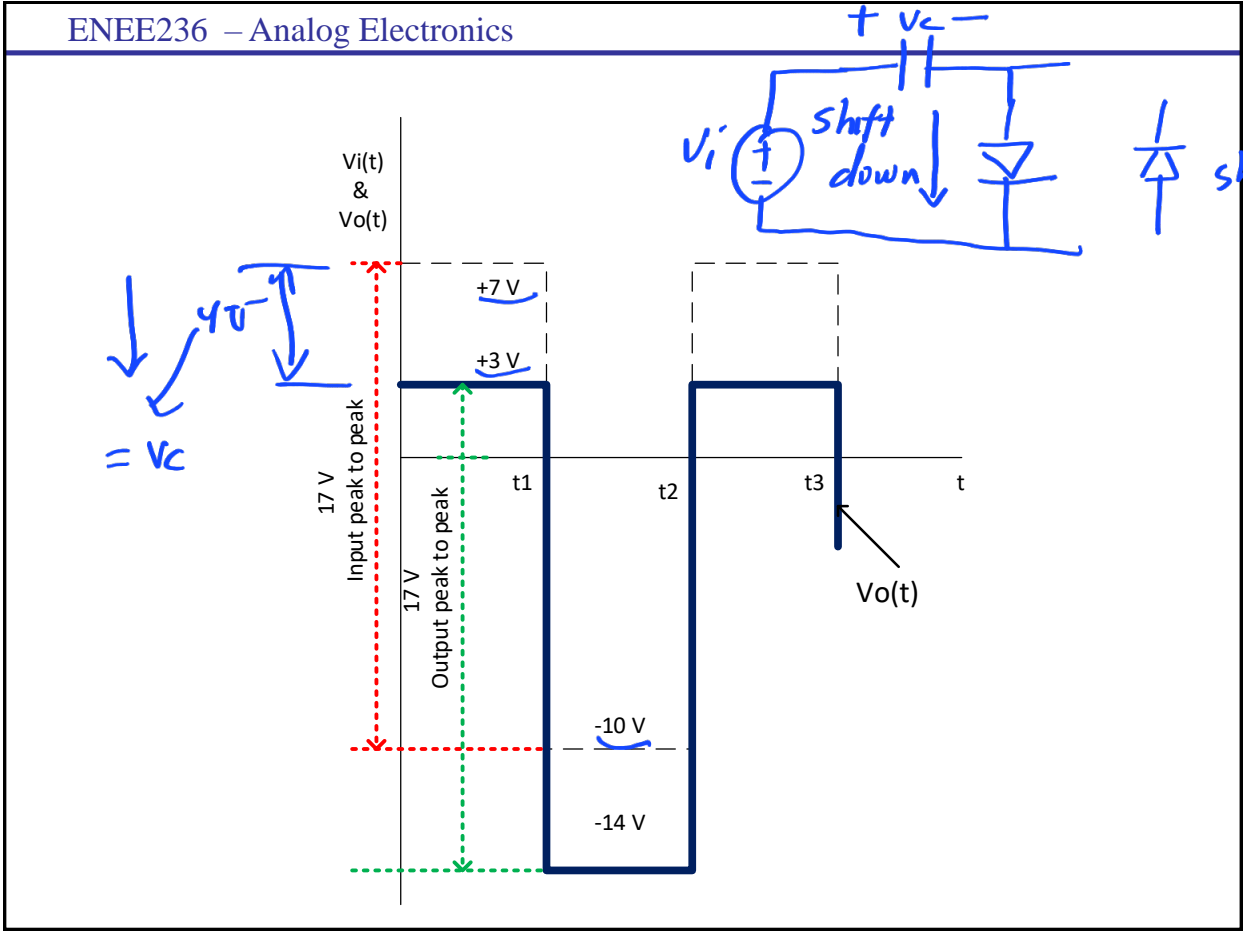$10 + 4 + V_D + 3 = 0$
 $\therefore V_D = -17 \text{ V} < 0$
Diode off







//

Biased Clamper Circuits

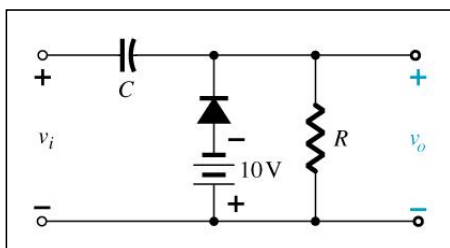The input signal can be any type of waveform such as a sine, square, or triangle wave.




The DC source lets you adjust the DC clamping level.

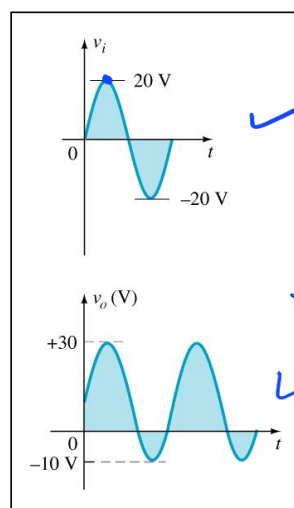

ENEE236 – Analog Electronics

Practice solve

Summary of Clamper Circuits

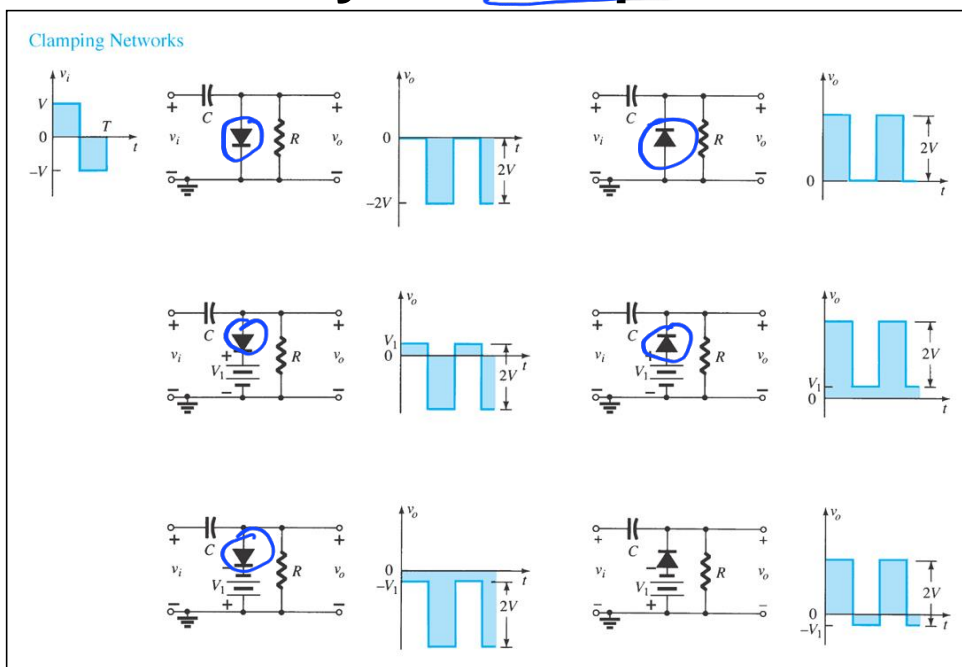

*End of L5
End of T3
عاده الكورس لغاية هنا
يوم السبت*