

LS
26/7/2021

ENEE2360

Analog Electronics

T5: Zener Diode

INSTRUCTOR: NASSER ISMAIL


ENEE236 – Analog Electronics

Zener Diode Simple Voltage Regulator ?


- * *The Zener is used as a voltage regulator to ^{keep} maintain a constant dc output under variations in load current and ac line voltage*
- *It can also be used as protection device against overvoltage*
- *Analysis starts by defining state of diode followed by using appropriate model, then find unknown quantities*


EENEE236 – Analog Electronics

Voltage Regulator

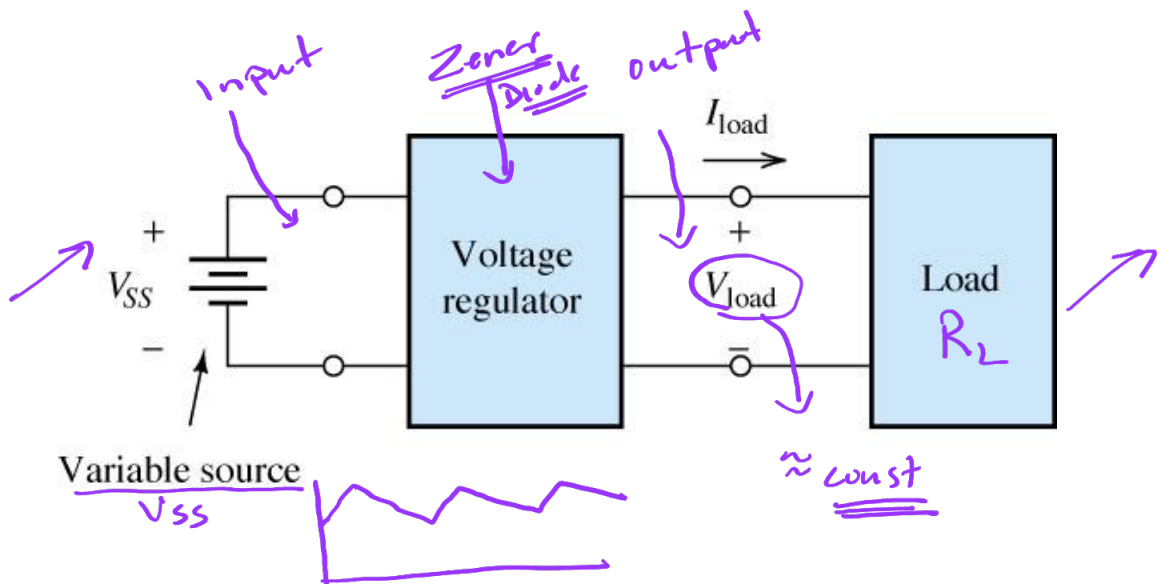


A voltage regulator supplies constant voltage to a load.

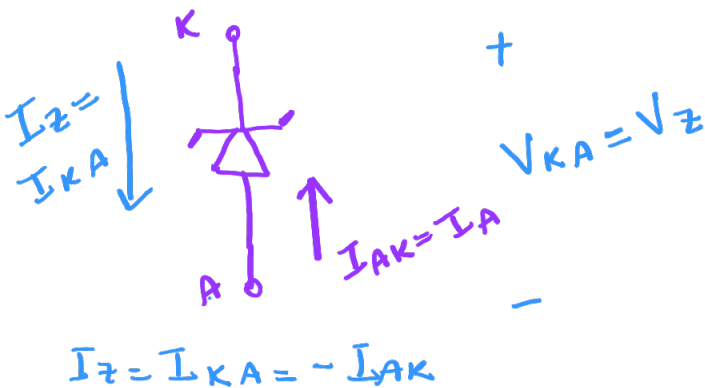

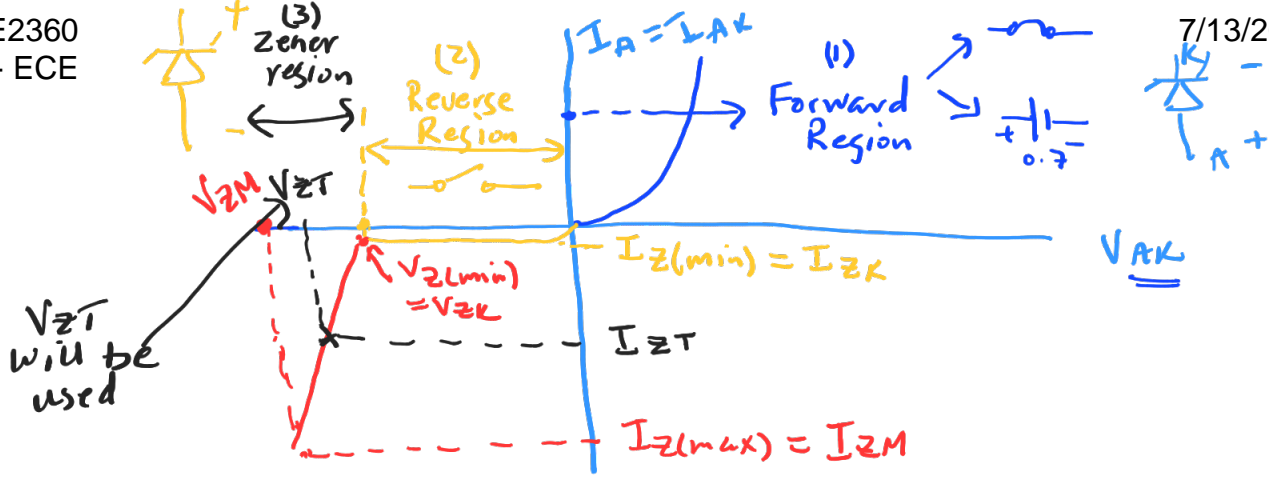

ENEE236 – Analog Electronics

Zener Diode V-I Curve

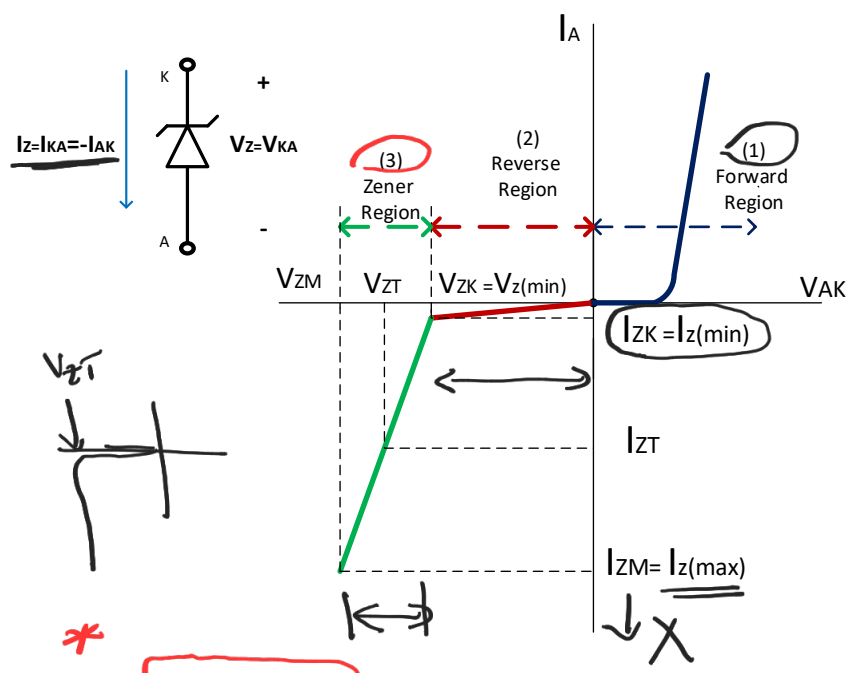


- In data sheet , we have I_{ZT} , V_{ZT}
- Zener currents will be assumed positive if passing from cathode to Anode
- If $I_Z < I_{ZK}$ zener will act as an open circuit
- If $I_Z > I_{Zmax}$ zener will be damaged

* If $I_{ZK} < I_Z < I_{Zmax}$ zener will be in voltage regulation (zener) region

ENEE236 – Analog Electronics

Zener Diode Operation Regions

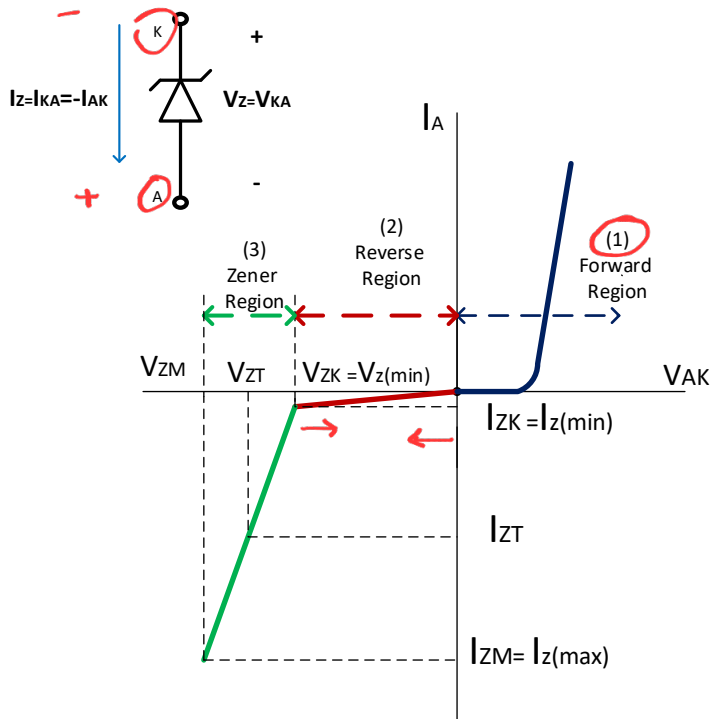

Region (1)

➤ When $V_{AK} > 0$, zener acts as regular diode
ON → short



➤ Region (2)

When $0 < V_{KA} < V_{ZK}$, zener acts as regular diode
OFF



➤ Region (3)

When $V_{KA} > V_{ZK}$, This is the intended operating region, and the zener acts as a voltage regulator

? Model

ENEE236 – Analog Electronics

Zener Diode Operation & Models


The Zener is a diode that is operated in reverse bias at the Zener Voltage (V_Z).

Conditions for zener diode to operate in the breakdown (Zener/ON) region When

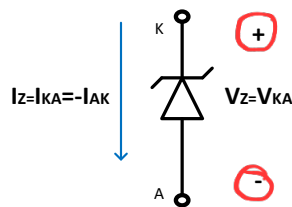
1. Cathode is more positive than anode
2. $V_{th} \geq V_Z$ ← *data sheet*
3. $I_Z > I_Z(\min)$
4. $I_Z < I_Z(\max)$

==> Voltage across the Zener is V_Z


- Zener current: $I_Z = I_S - I_L$
- The Zener Power: $P_Z = V_Z I_Z$



Model ??



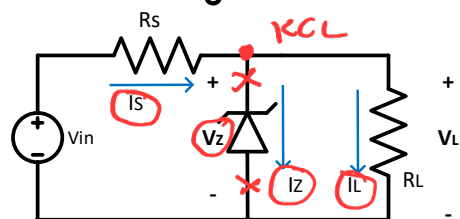


$I_S = I_Z + I_L$

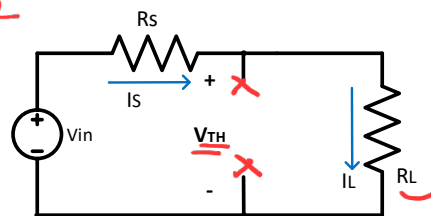

Zener Diode Models

1. Ideal Model

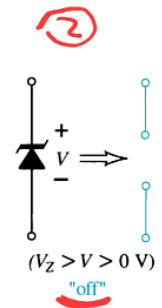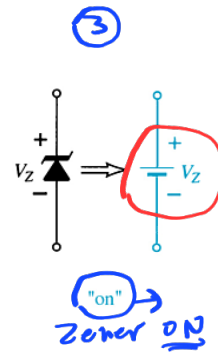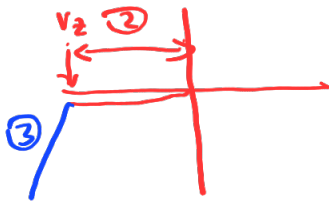


2. Simplified Model


$$A \left(\frac{\Delta V_Z}{\Delta I_Z} = r_Z \right)$$

$$I_Z = I_{KA} = -I_{AK}$$



$$V_Z = V_{KA}$$

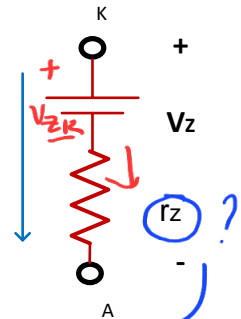

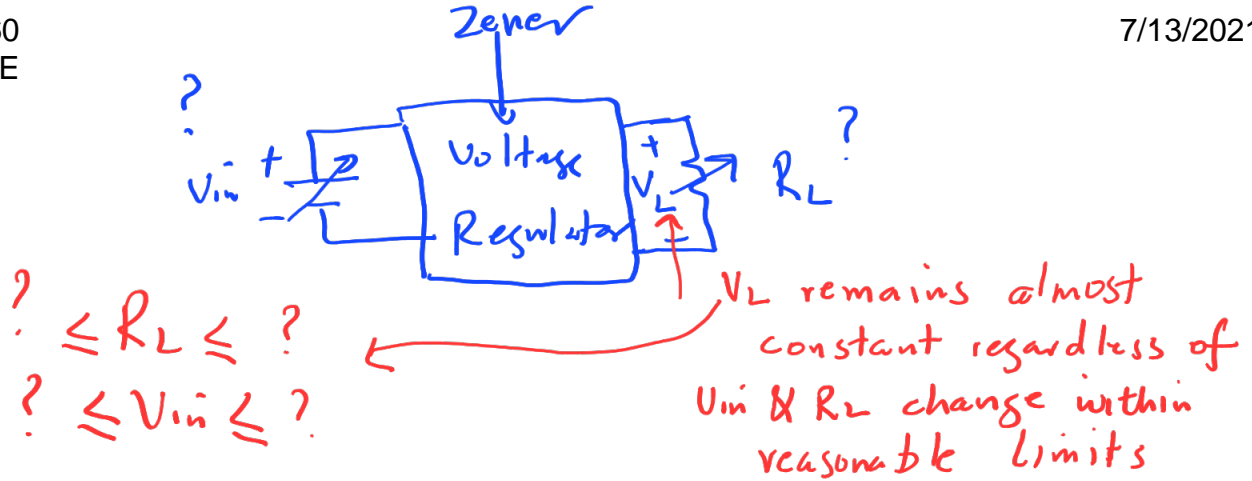

ENEE236 – Analog Electronics

Fixed Vin, Variable RL

$R_{L(min)} \leq R_L \leq R_{L(max)}$
 $I_{Z(max)}$


- Due to the value of V_Z , there is specific values of R_L (I_L) that ensure the zener is in the ON (regulation) state
- Too small values of R_L can result in zener being OFF

1) $V_L = V_Z = \frac{R_L}{R_L + R_S} V_{in}$

$V_{th} \geq V_Z$

$R_{L(min)} = \frac{R_S \cdot V_Z}{V_{in} - V_Z}$

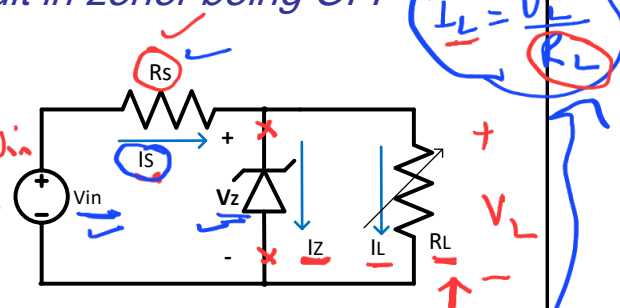$V_{th} = \frac{R_L \cdot V_{in}}{R_L + R_S}$



$I_L = \frac{V_L}{R_L}$

$R_L \geq R_{L(min)} \Rightarrow I_{L(max)} = \frac{V_L}{R_L} = \frac{V_Z}{R_{L(min)}}$


2) Also, values of $R_L \geq R_{L(max)}$ can result in $I_Z > I_{Z(max)}$

$I_{L(min)} = I_S - I_{Z(max)}$

$R_{L(max)} = \frac{V_Z = V_L}{I_{L(min)}}$

$I_S = I_Z + I_L$
 $I_L = I_S - I_Z$
 $I_{L(min)} = I_{S(min)} - I_{Z(max)}$

? $\rightarrow I_S$

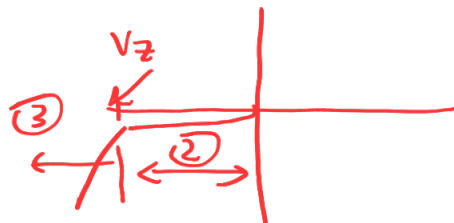

ENEE236 – Analog Electronics

Example

Given the following values of R_L , find the mode of operation of the zener and the voltage V_L , I_Z, I_Z

- a) $R_L = 0.1 \text{ k}\Omega$ ✓
- b) $R_L = 0.5 \text{ k}\Omega$ ✓
- c) $R_L = 5 \text{ k}\Omega$ ✓
- d) $R_L = \infty$ ✓

SOLUTION



a) $R_L = 0.1 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_s} V_{in} = \frac{0.1}{0.1 + 1} 35 \text{ V} = 3.18 \text{ V}$$

Zener works in region 2, it acts as open circuit

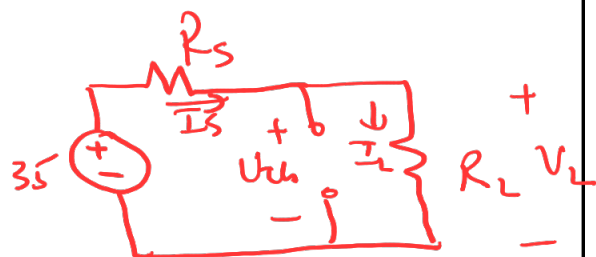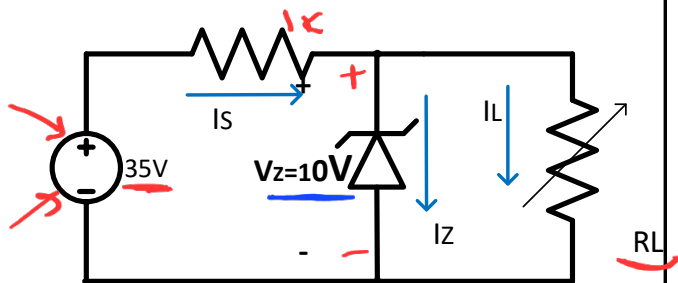$V_L = 3.18 \text{ V}$ (it is not regulated)



1)
$$V_{th} = \frac{R_L}{R_L + R_s} \cdot V_{in}$$

$$V_{th} = \frac{0.1 \text{ k}\Omega}{0.1 \text{ k}\Omega + 1 \text{ k}\Omega} \cdot 35 = 3.18 < V_z$$


region 2 → open circuit

$$\therefore V_L = V_{th} = 3.18 \text{ V}$$

$$I_Z = 0, I_L = \frac{3.18}{0.1 \text{ k}\Omega}$$

2)
$$V_{th} = \frac{0.5 \text{ k}\Omega}{0.5 \text{ k}\Omega + 1 \text{ k}\Omega} \cdot 35$$


$$= 11.67 > V_z = 10 \rightarrow \text{region 3}$$

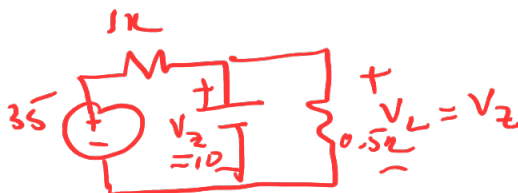



ENEE236 – Analog Electronics

Example

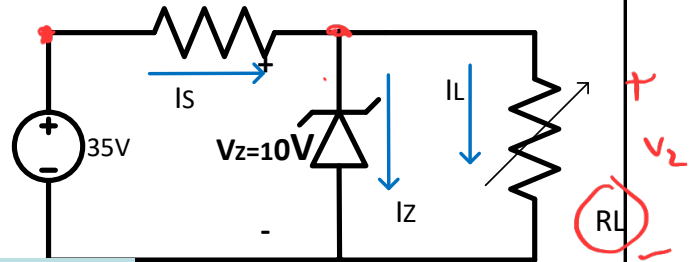

b) $R_L = 0.5 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_S} V_{in} = \frac{0.5}{0.5 + 1} 35 \text{ V} = 11.67 \text{ V}$$

$$V_{th} > V_Z$$

Zener works in region 3, it works as voltage regulator

$$V_L = V_Z = 10 \text{ V}$$


$$I_S = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{0.5 \text{ k}\Omega} = 20 \text{ mA}$$

$$I_Z = I_S - I_L = 5 \text{ mA}$$

ENEE236 – Analog Electronics

Example

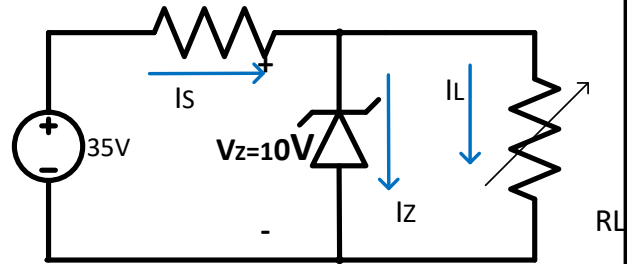

c) $R_L = 5\text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_s} V_{in} = \frac{5}{5+1} 35\text{ V} = 29.17\text{ V} > V_z = 10$$

$V_{th} > V_z$


Zener works in region 3, it works as voltage regulator

$V_L = V_z = 10\text{ V}$

$$I_s = \frac{35\text{ V} - 10\text{ V}}{1\text{ k}\Omega} = 25\text{ mA}$$


$$I_L = \frac{V_L}{R_L} = \frac{10}{5\text{ k}\Omega} = 2\text{ mA}$$

$$I_z = I_s - I_L = 23\text{ mA}$$

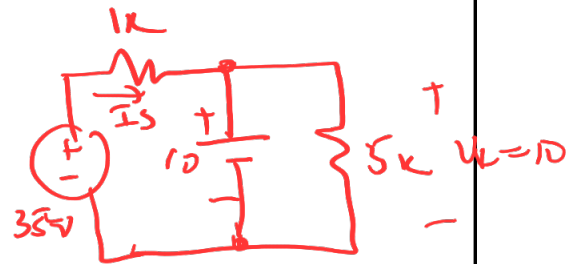

ENEE236 – Analog Electronics

Example

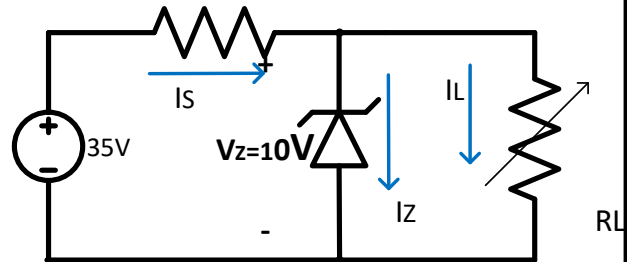

d) $R_L = \infty$

using ideal model

$$V_{th} = \frac{\infty}{\infty + R_s} V_{in} = 35 \text{ V}$$

$$V_{th} > V_Z$$


Zener works in region 3, it works as voltage regulator

$$V_L = V_Z = 10 \text{ V}$$

$$I_s = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{\infty} = 0$$


$$I_Z = I_s - I_L = 25 \text{ mA}$$

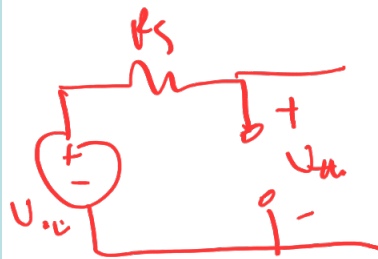

ENEE236 – Analog Electronics

Example

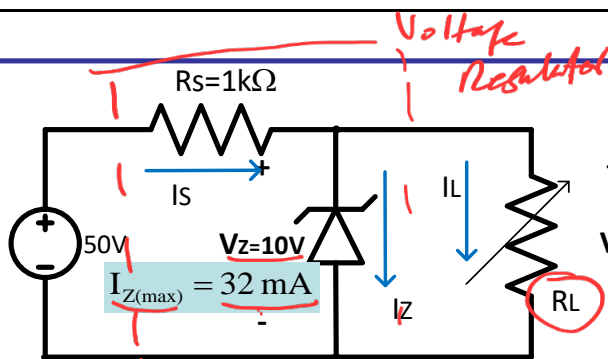- 1) Determine Range of R_L & I_L that will result in V_L being maintained at 10V
- 2) Determine the power rating of the zener diode $P_Z = V_Z \cdot I_Z$



SOLUTION

1) To find $R_{L(min)}$ that will turn the zener diode ON :

$$V_L = V_Z = \frac{R_L}{R_L + R_S} V_i \Rightarrow$$

$$R_L = \frac{R_S}{V_i - V_Z} V_Z$$

$$R_{L(min)} = \frac{1 \text{ k}\Omega}{50 - 10} 10 = 250 \Omega$$

$$250 \Omega \leq R_L \leq 1.25 \text{ k}\Omega$$

2) To find $R_{L(max)} \Rightarrow$ we need $I_{L(min)}$

$$I_{L(min)} = I_S - I_{Z(max)}$$

$$I_S = \frac{V_i - V_Z}{R_S} = \frac{50 - 10}{1 \text{ k}\Omega} = 40 \text{ mA}$$

$$I_{L(min)} = 40 - 32 = 8 \text{ mA}$$

$$R_{L(max)} = \frac{V_L}{I_{L(min)}} = \frac{10 \text{ V}}{8 \text{ mA}} = 1.25 \text{ k}\Omega$$

$$3) P_{Z(max)} = V_Z \cdot I_{Z(max)} = 10 \text{ V} \cdot 32 \text{ mA} = 320 \text{ mW}$$

The zener diode is chosen with power rating $\geq P_{Z(max)}$

$$40 \text{ mA} \geq I_L \geq 8 \text{ mA}$$


$$\frac{10 \text{ V}}{250}$$

$$\frac{10 \text{ V}}{1.25 \text{ k}}$$

End of L8

1183336

La
 27/7/2021

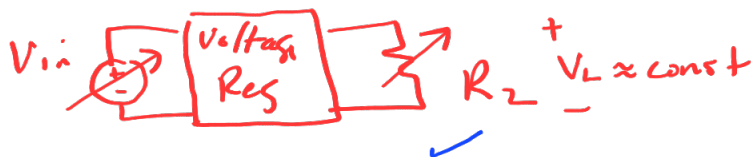

ENEE236 – Analog Electronics

Fixed R_L , Variable V_{in}

For Fixed R_L , the voltage V_{in} must be large enough to turn the zener diode on (regulation region (3)) $? \leq V_{in} \leq ?$

$$V_{in} = V_{in(min)} = \frac{R_L + R_S}{R_L} V_Z$$

$V_{in(max)}$ is limited by maximum zener current $I_{Z(max)}$


$$I_S = I_Z + I_L$$

$$I_{S(max)} = I_{Z(max)} + I_L$$

$$V_{i(max)} = I_{S(max)} \cdot R_S + V_Z$$

⇓
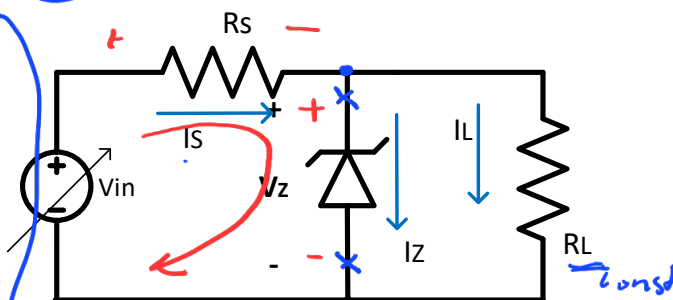
$$V_{in(min)} \leq V_{in} \leq V_{in(max)}$$



$$V_{th} = \frac{R_L}{R_L + R_S} \cdot V_{in} \geq V_Z$$

$$V_{in} \geq V_Z \frac{(R_L + R_S)}{R_L}$$

EENEE236 – Analog Electronics

Example

Find the range of values of V_i that will maintain the zener in the ON (regulation) State

$$V_{in(min)} = \frac{R_L + R_S}{R_L} V_Z$$

$$= \frac{1200 + 220}{1200} 20 = 23.07 \text{ V}$$

$$I_S = I_Z + I_L$$


$$I_{S(max)} = I_{Z(max)} + I_L$$

$$I_L = \frac{V_L}{R_L} = \frac{20 \text{ V}}{1200 \Omega} = 16.67 \text{ mA}$$


$$I_{S(max)} = 60 \text{ mA} + 16.67 \text{ mA} = 76.67 \text{ mA}$$

$$V_{i(max)} = (76.67 \text{ mA}) \cdot (220 \Omega) + 20 \text{ V} = 36.87 \text{ V}$$

$$= I_{S(max)} \cdot R_S + V_Z$$

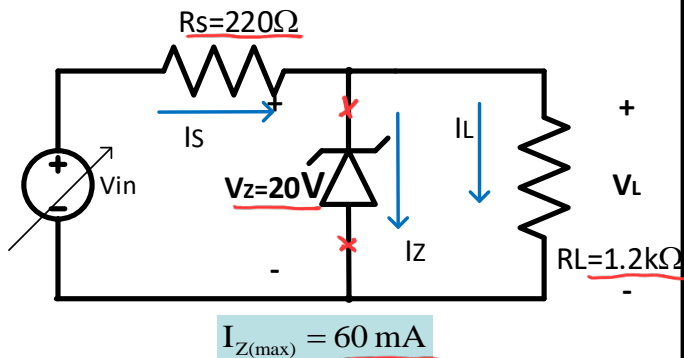

$$\therefore 23.07 \text{ V} \leq V_{in} \leq 36.87 \text{ V}$$

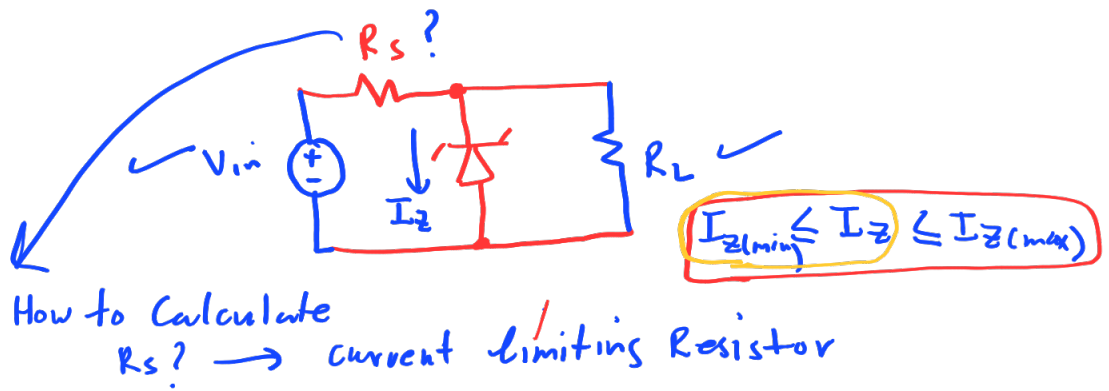

EENEE236 – Analog Electronics

Design of R_s (Current limiting Resistor)

Given : $V_Z, I_{Z(min)}, I_{Z(max)}, V_{in(min)}, V_{in(max)}, R_{L(min)}, R_{L(max)}$

Find range of acceptable R_s in the voltage regulator

$$1) I_Z = I_S - I_L \geq I_{Z(min)}$$

Worst Case : the smallest value of

$$(I_S - I_L)$$


must be always higher than $> I_{Z(min)}$

$$I_{S(min)} - I_{L(max)} \geq I_{Z(min)}$$

$$\frac{V_{S(min)} - V_Z}{R_S} - I_{L(max)} \geq I_{Z(min)}$$

$$I_{Z(min)} + I_{L(max)} \leq \frac{V_{S(min)} - V_Z}{R_S}$$
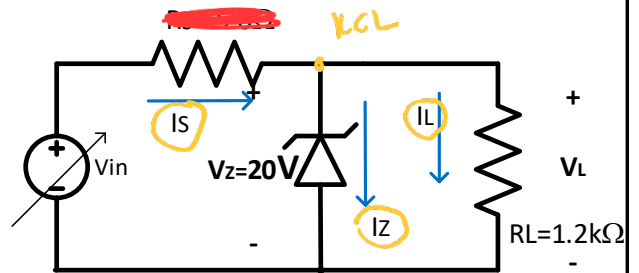
$$R_S \leq \frac{V_{S(min)} - V_Z}{I_{Z(min)} + I_{L(max)}}$$



$$I_S = \frac{V_{in} - V_Z}{R_S}$$

Design of R_s (Current limiting Resistor)

Given : $V_Z, I_{Z(\min)}, I_{Z(\max)}, V_{in(\min)}, V_{in(\max)}, R_{L(\min)}, R_{L(\max)}$

Find range of acceptable R_s in the voltage regulator

2) $I_Z \leq I_{Z(\max)}$

Worst Case : the largest value of $(I_S - I_L)$ must be always smaller than $I_{Z(\max)}$

$$I_{S(\max)} - I_{L(\min)} \leq I_{Z(\max)}$$

$$\frac{V_{S(\max)} - V_Z}{R_s} - I_{L(\min)} \leq I_{Z(\max)}$$

$$I_{Z(\max)} + I_{L(\min)} \geq \frac{V_{S(\max)} - V_Z}{R_s}$$

$$R_s \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Note That

$$I_{L(\min)} = \frac{V_Z}{R_{L(\max)}}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}}$$

**

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_s \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

ENEE236 – Analog Electronics

Design of R_s (Current limiting Resistor)

Given :

$$V_Z = 10 \text{ V},$$

$$I_{Z(\min)} = 5 \text{ mA}, I_{Z(\max)} = 200 \text{ mA},$$

$$V_{in(\min)} = 15 \text{ V}, V_{in(\max)} = 20 \text{ V},$$

$$R_{L(\min)} = 500, R_{L(\max)} = \infty$$

Find R_s ?

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_s \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Solution

$$I_{L(\min)}^{\max} = \frac{V_Z}{R_{L(\max)}^{\min}} = \frac{10 \text{ V}}{500 \Omega} = 20 \text{ mA}$$

$$I_{L(\max)}^{\min} = \frac{V_Z}{R_{L(\min)}^{\max}} = \frac{10 \text{ V}}{\infty} = 0$$

$$200 \Omega \geq R_s \geq 50 \Omega$$

$$\text{let } R_s = 100 \Omega$$

Variation of V_Z (using simplified model)


للعلم فقط

$$r_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

If V_{ZT} , I_{ZT} & r_Z are known

$$\begin{aligned} V_{Z(\max)} = V_{ZM} &= V_{ZT} + \Delta I_Z \cdot r_Z \\ &= V_{ZT} + (I_{Z(\max)} - I_{ZT}) \cdot r_Z \end{aligned}$$

$$\begin{aligned} V_{Z(\min)} = V_{ZK} &= V_{ZT} - \Delta I_Z \cdot r_Z \\ &= V_{ZT} - (I_{ZT} - I_{Z(\min)}) \cdot r_Z \end{aligned}$$

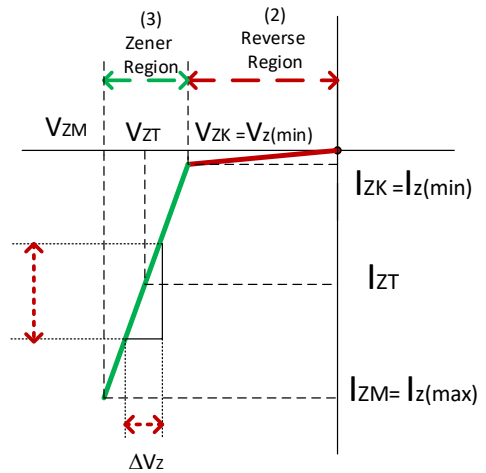

ENEE236 – Analog Electronics

Example

If $V_{ZT} = 15V$ at $I_{ZT} = 17mA$

& $r_{ZT} = 14\Omega$

$I_{ZK} = 0.25 mA$

$P_{Zmax} = 1 Watt$

Find :

1) Minimum and Maximum Values of V_Z



2) Value of R_S

3) Value of $R_{L(min)}$

$$1) I_{Z(max)} \cong \frac{P_{Z(max)}}{V_Z} = \frac{1 Watt}{15} = 66.7 mA$$

$$\begin{aligned} V_{Z(max)} = V_{ZM} &= V_{ZT} + \Delta I_Z \cdot r_Z \\ &= V_{ZT} + (I_{Z(max)} - I_{ZT}) \cdot r_Z \\ &= 15 + (66.7 - 17) mA (14\Omega) = 15.7 V \end{aligned}$$


$$\begin{aligned} V_{Z(min)} = V_{ZK} &= V_{ZT} - \Delta I_Z \cdot r_Z \\ &= V_{ZT} - (I_{ZT} - I_{Z(min)}) \cdot r_Z \end{aligned}$$

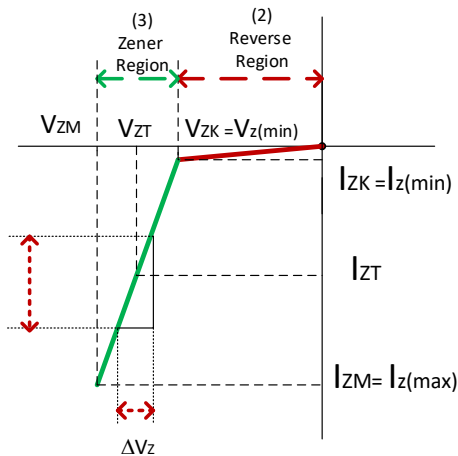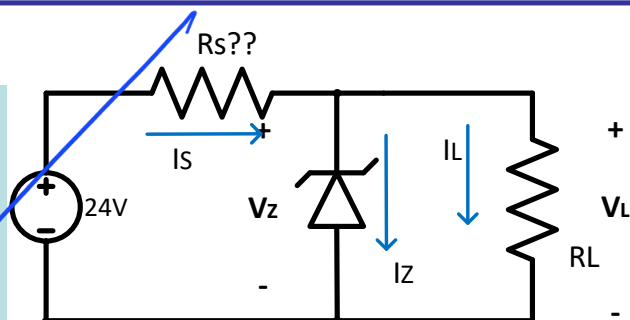

EENEE236 – Analog Electronics

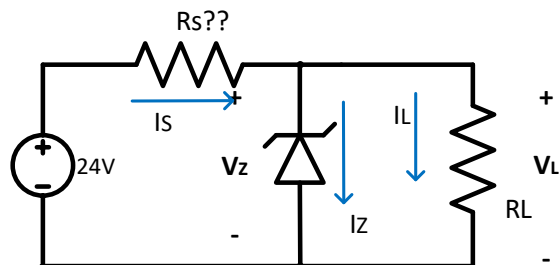Example

$$\begin{aligned}
 V_{Z(\min)} &= V_{ZK} = V_{ZT} - \Delta I_Z \cdot r_Z \\
 &= V_{ZT} - (I_{ZT} - I_{Z(\min)}) \cdot r_Z \\
 &= 15 - (17 - 0.25) \text{ mA} (14 \Omega) = 14.76 \text{ V}
 \end{aligned}$$



2) R_S


$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Here $V_{IN} = V_S$ is fixed \Rightarrow

$$R_S \geq \frac{V_S - V_{Z(\max)}}{I_{Z(\max)} + I_{L(\min)}} = \frac{24 - 15.7}{66.7 \text{ mA} + 0} = 124 \Omega$$

$$R_S \leq \frac{V_S - V_{Z(\min)}}{I_{Z(\min)} + I_{L(\max)}} = \frac{24 - 14.76}{0.25 \text{ mA} + ???}$$

we choose $R_S = 124 \Omega$

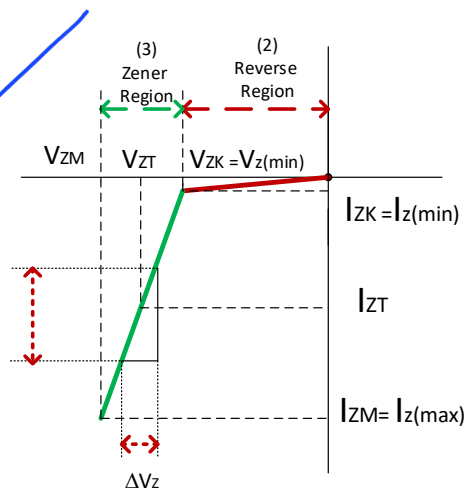

ENEE236 – Analog Electronics



Example


$$3) R_{L(\min)} \Rightarrow I_{L(\max)}$$

$$I_{L(\max)} = I_S - I_{L(\min)}$$

$$= 66.7 \text{ mA} - 0.25 \text{ mA} = 66.45 \text{ mA}$$

$$\therefore R_{L(\min)} = \frac{V_{Z(\min)}}{I_{L(\max)}} = \frac{14.76 \text{ V}}{66.45 \text{ mA}} \cong 222 \Omega$$

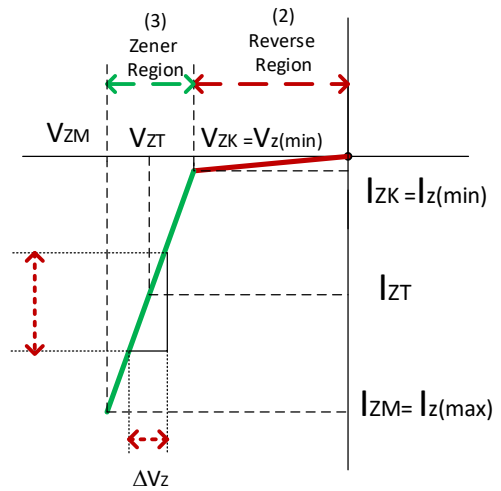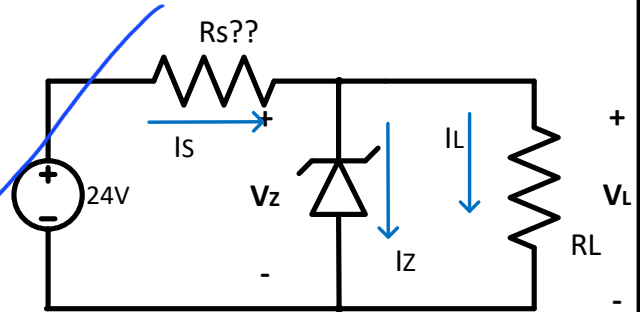

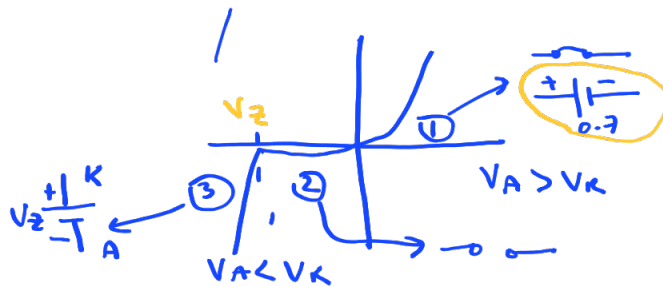

ENEE236 – Analog Electronics

Clipper circuits using Zeners

a) When $V_i(t) < -0.7$ V, Zener works in region (1) as regular diode ON

$$0.7 + i_D(t) \cdot R + V_i(t) = 0$$




$$i_D(t) = \frac{-V_i(t) - 0.7}{R} > 0$$

$$V_i(t) < -0.7$$

$$\therefore V_o(t) = -0.7$$

b) When $V_Z > V_i(t) > -0.7$ V, Zener works in region (2) as regular diode OFF $\therefore V_o(t) = V_i(t)$ ✓

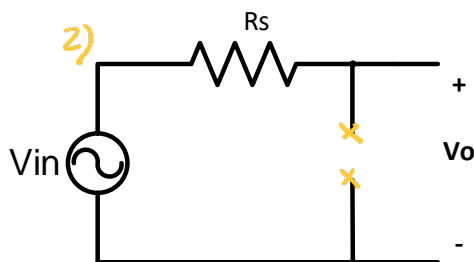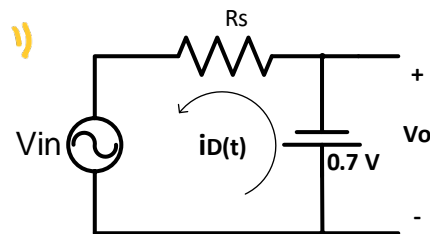
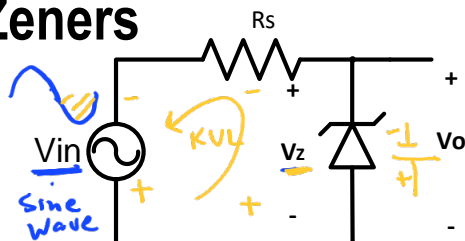
c) When $V_i(t) > V_Z$, Zener works in region (3) as voltage regulator $\therefore V_o(t) = V_Z$




Clipper circuits using Zeners

c) When $V_i(t) > V_z$, Zener works in region (3) as voltage regulator

$$\therefore V_o(t) = V_z$$

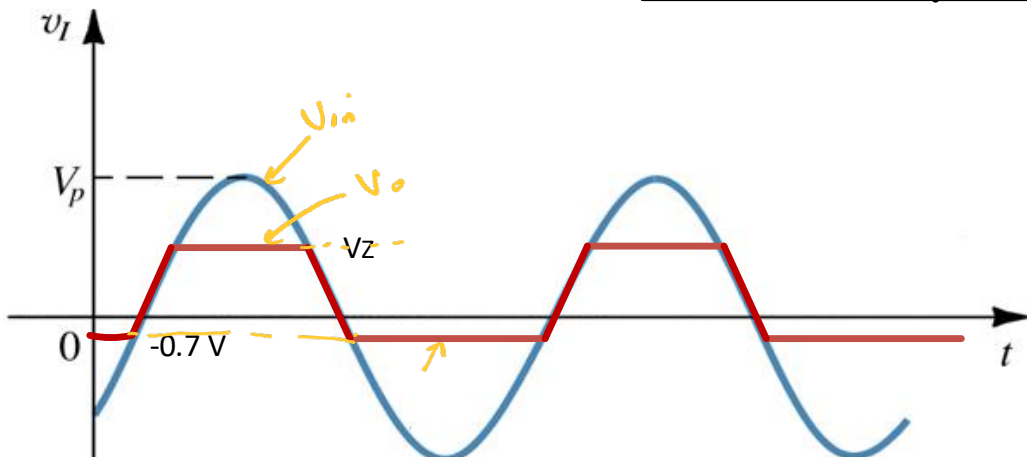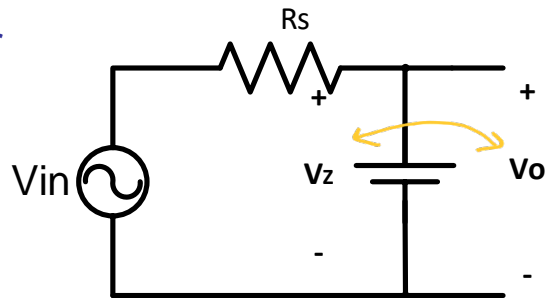

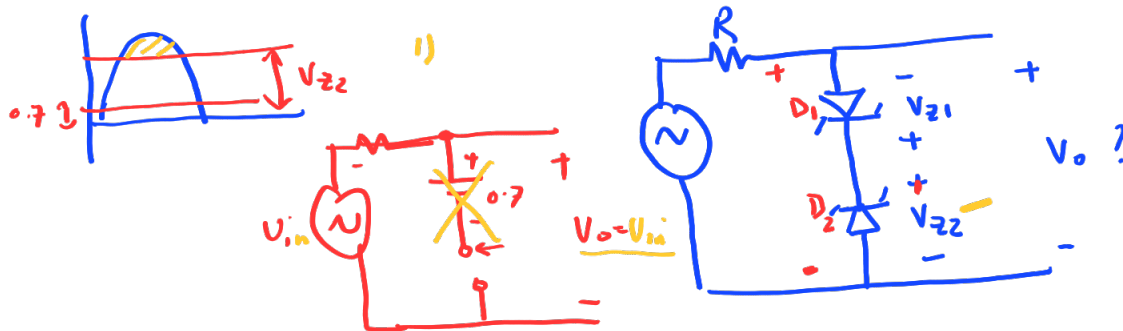



ENEE236 – Analog Electronics

Clipper circuits using Zeners

Find and sketch $V_o(t)$


- a) When $0.7V < V_i(t) < V_{z2}$,
 D1- regular diode ON ✓ (1)
 D2- regular diode OFF ✓ (2)

$\therefore V_o(t) = V_i(t)$

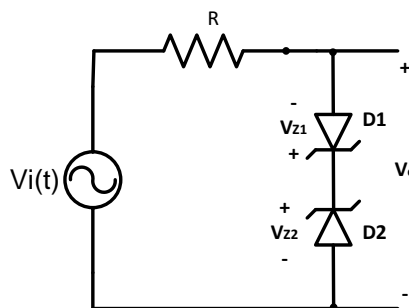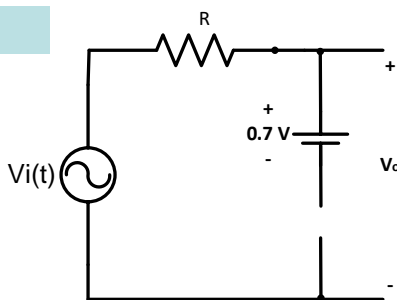

- b) When $V_i(t) > V_{z2}$
 D1 – ON (region 1) ✓
 D2- Zener ON (region 3) ✓

$\therefore V_o(t) = V_{z2} + 0.7$


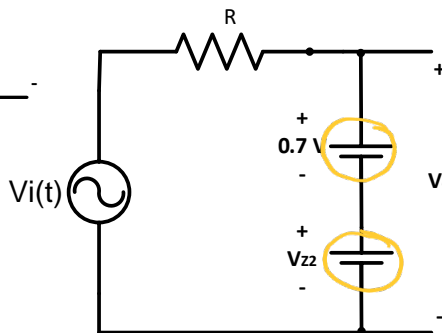


ENEE236 – Analog Electronics




Clipper circuits using Zeners

c) When $-0.7V > V_i(t) > -V_{Z1}$,
 D1- regular diode OFF
 D2- regular diode ON

$\therefore V_o(t) = V_i(t)$

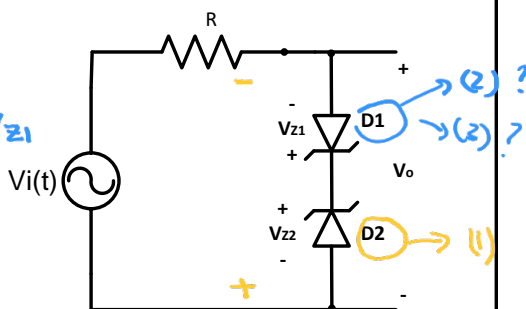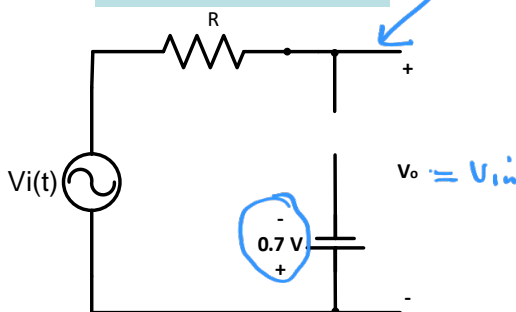

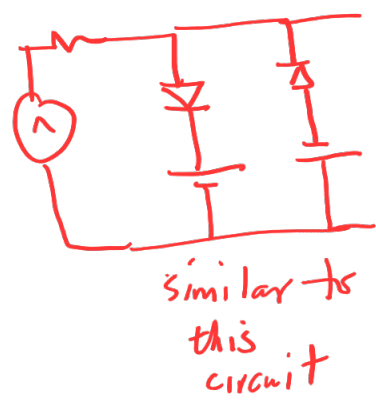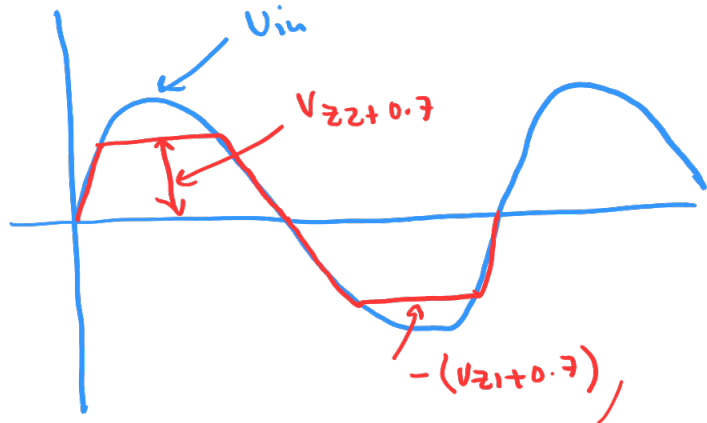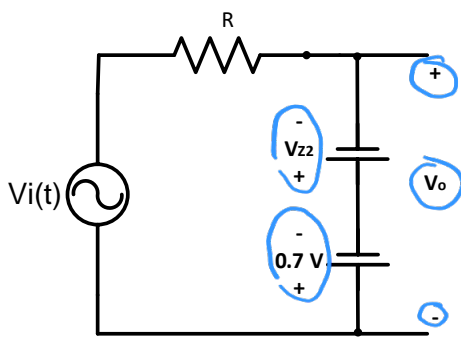d) When $V_i(t) < -V_{Z1}$
 D2 – ON (region 1) ✓
 D1- Zener ON (region 3) ✓
 $\therefore V_o(t) = -V_{Z1} - 0.7$




Voltage-Multiplier Circuits

Voltage multiplier circuits use a combination of diodes and capacitors to step up the output voltage of rectifier circuits. Three common voltage multipliers are the:

Voltage Doubler → $\times 2$



Voltage Tripler → $\times 3$

Voltage Quadrupler → $\times 4$

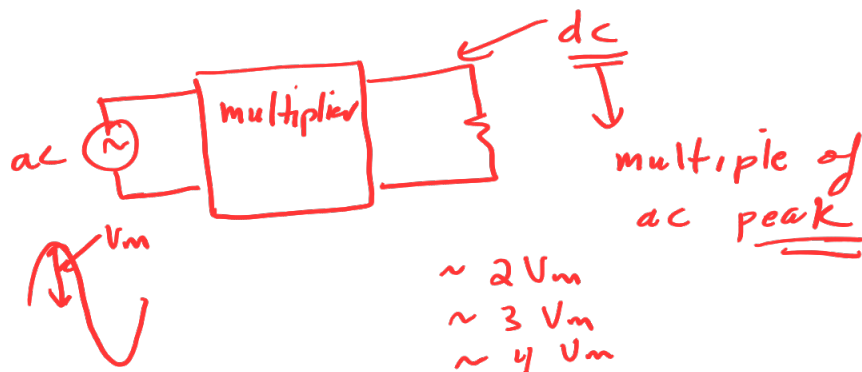

ENEE236 – Analog Electronics

Voltage Doubler

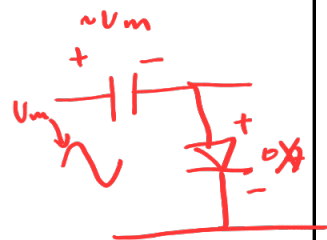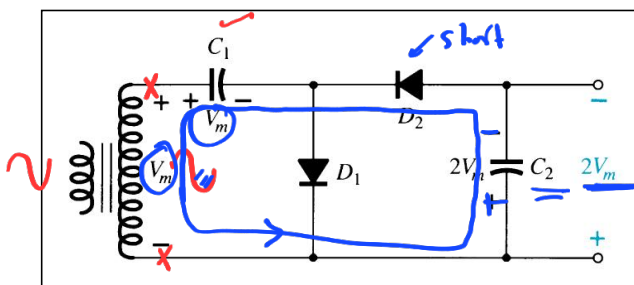

This half-wave voltage doubler's output can be calculated using:

$$V_{out} = V_{C2} = 2V_m$$

where V_m = peak secondary voltage of the transformer

Voltage Doubler

Similar to clamper circuit


Positive Half-Cycle

D_1 conducts
 D_2 is switched off
 Capacitor C_1 charges to V_m

Negative Half-Cycle


D_1 is switched off
 D_2 conducts
 Capacitor C_2 charges to V_m

$$V_{out} = V_{C2} = 2V_m$$

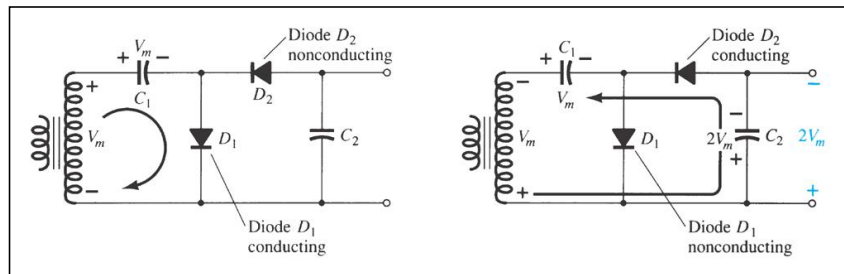

Voltage Tripler and Quadrupler

Test in the Lab
ENEE2103

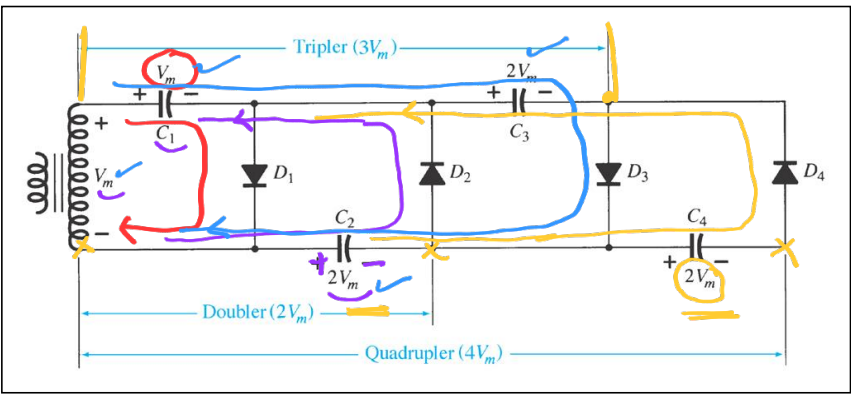

End of Diodes