



Faculty Of Information Technology
Electrical and Computer Engineering Department
CIRCUITS AND ELECTRONICS LABORATORY (ENEE2103)

Prelab Experiment#2
“Circuit Laws & Theorems”

Instructor: Dr. Wael Hashlamoun

Teacher: Eng. Mostafa Helal

Student Name: Mays Sbaih

Student Number:1160006

Section 3

Due to:17-2-2019

Part A: KVL & KCL

Bias simulation:

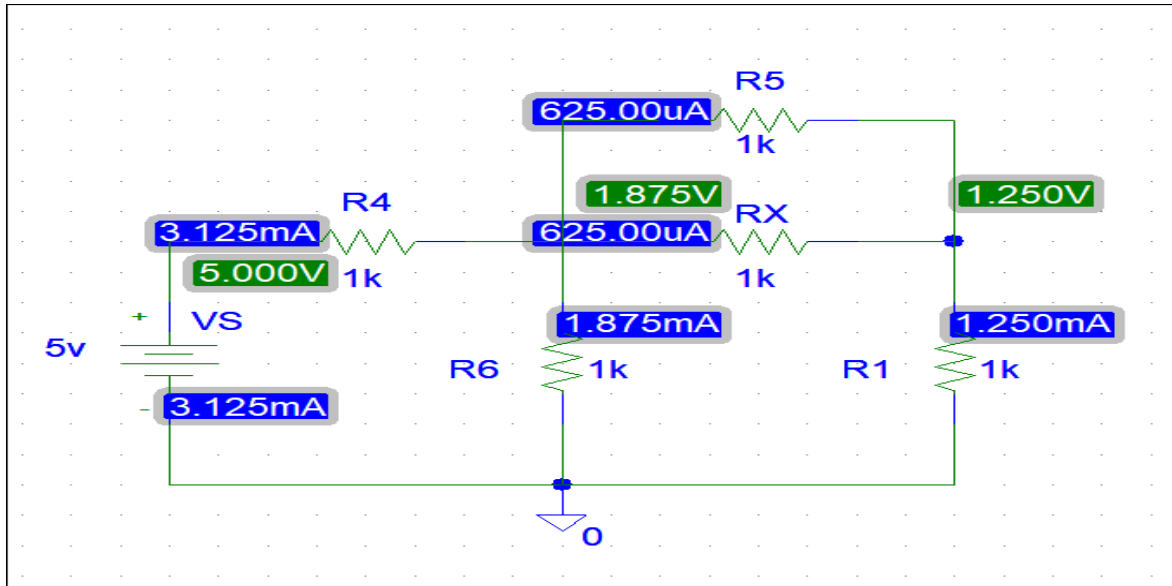


Fig A

Part B: Voltage & Current Division

- Current Division

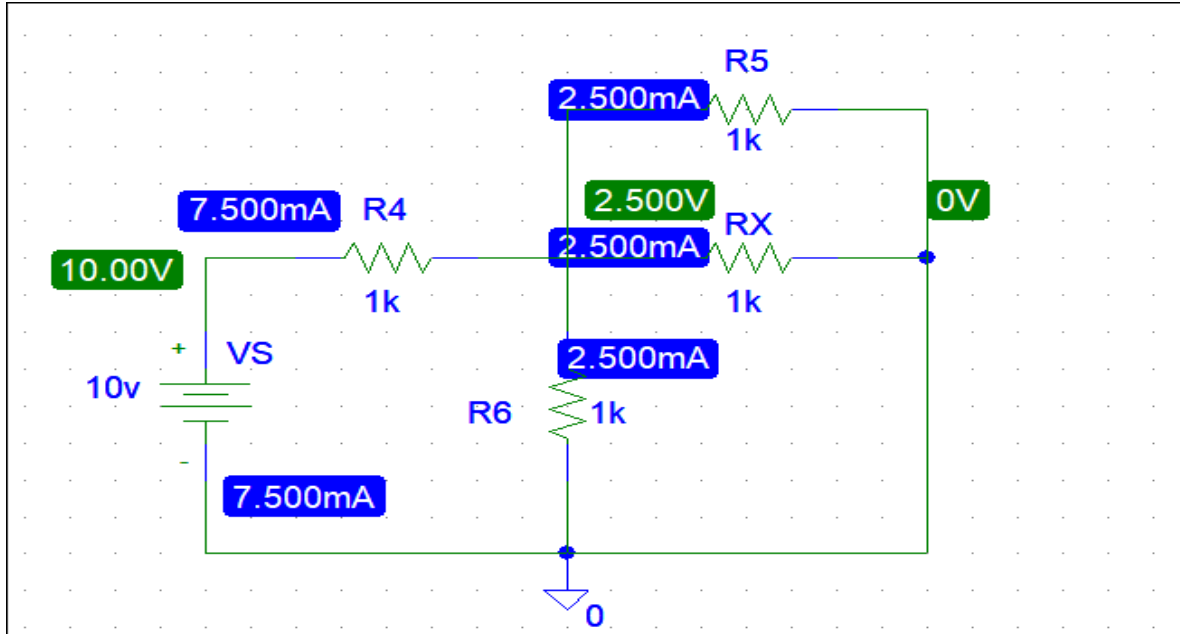


Fig B

Part C: Superposition

- $V_{s1} = 5v, V_{s2} = 10v \gg V_{R6} = 4v \ \& \ I_{R6} = 4mA$

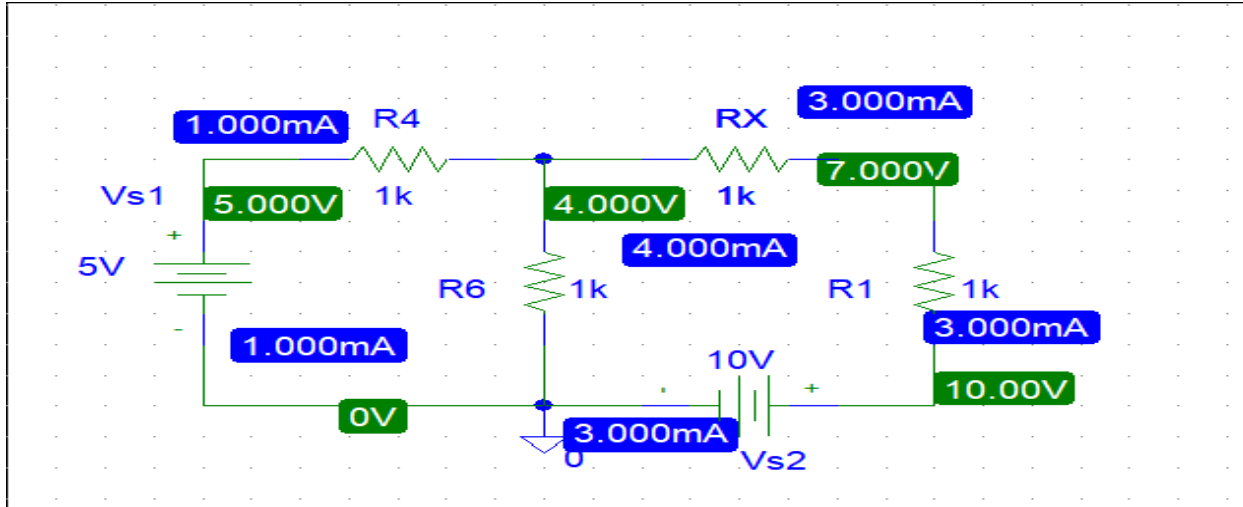


Fig C.1

- $V_{s1} = 0v, V_{s2} = 10v \gg V_{R6} = 2v \ \& \ I_{R6} = 2mA$

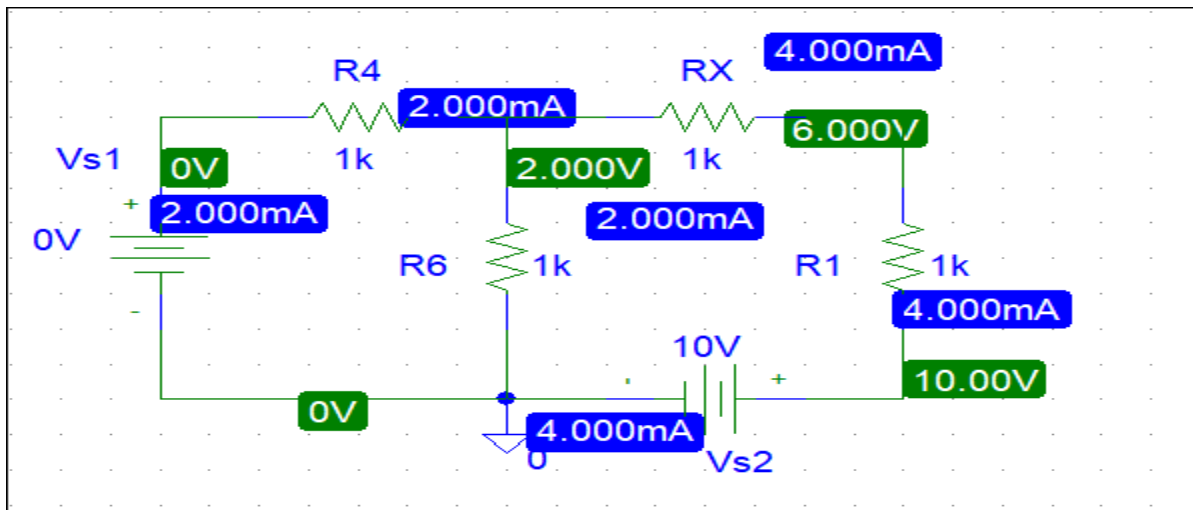


Fig C.2

- $V_{s1} = 5v, V_{s2} = 0v \gg V_{R6} = 2v$ & $I_{R6} = 2mA$

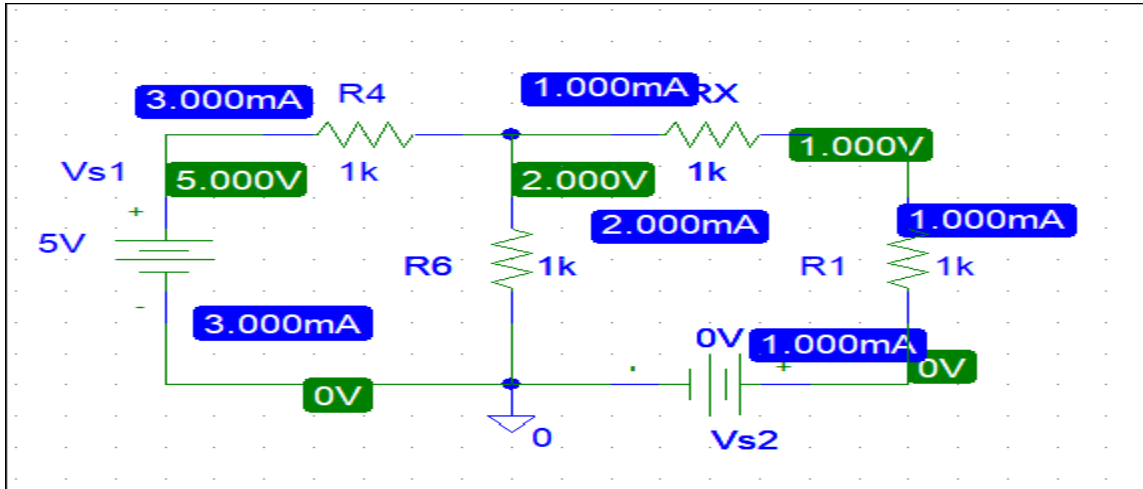


Fig C.3

Part D: Thevinin and Norton equivalent circuits.

Current on $R_1 = 3mA$, and the voltage across $R_1 = 7v - 10v = -3v$.

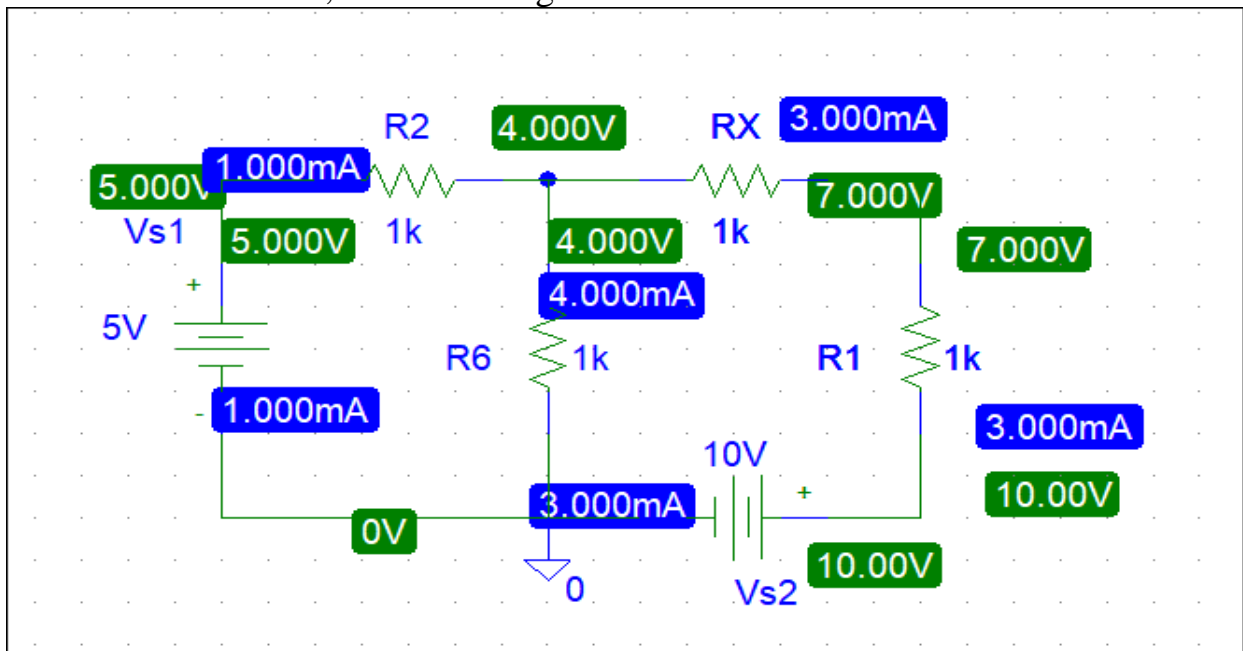


Fig D.1

- Open Circuit:

To measure R_{oc} , I set the resistance on high value, $R_{oc} = 2.5 - 10 = -7.5v$.

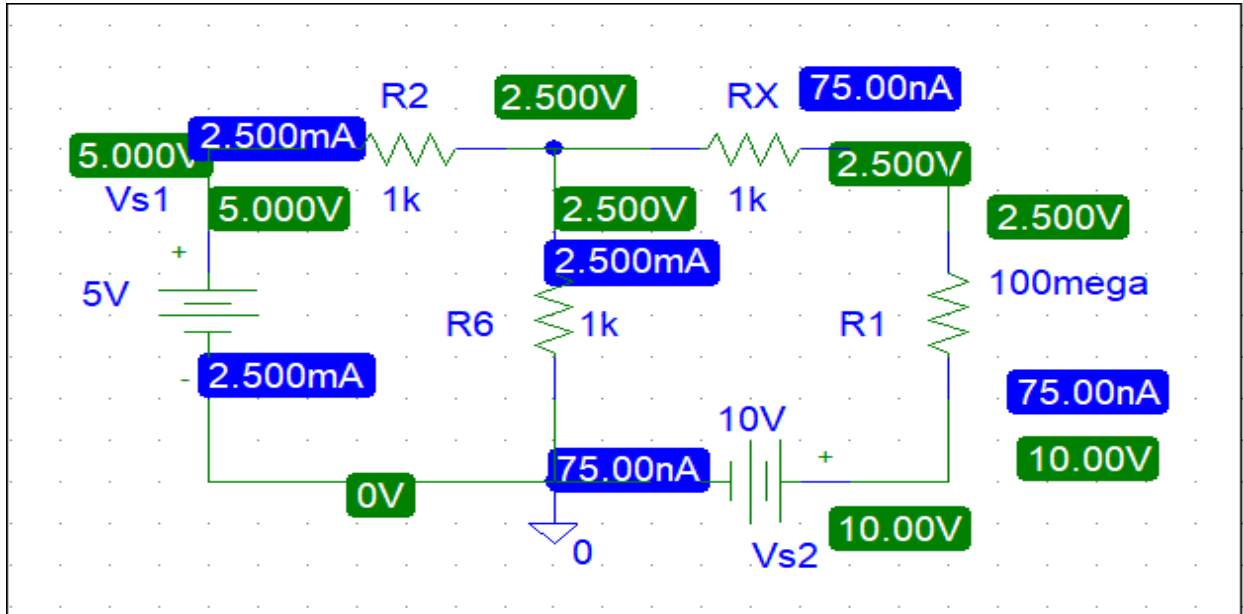


Fig D.2

- Short circuit:

$I_{sc} = -5mA$.

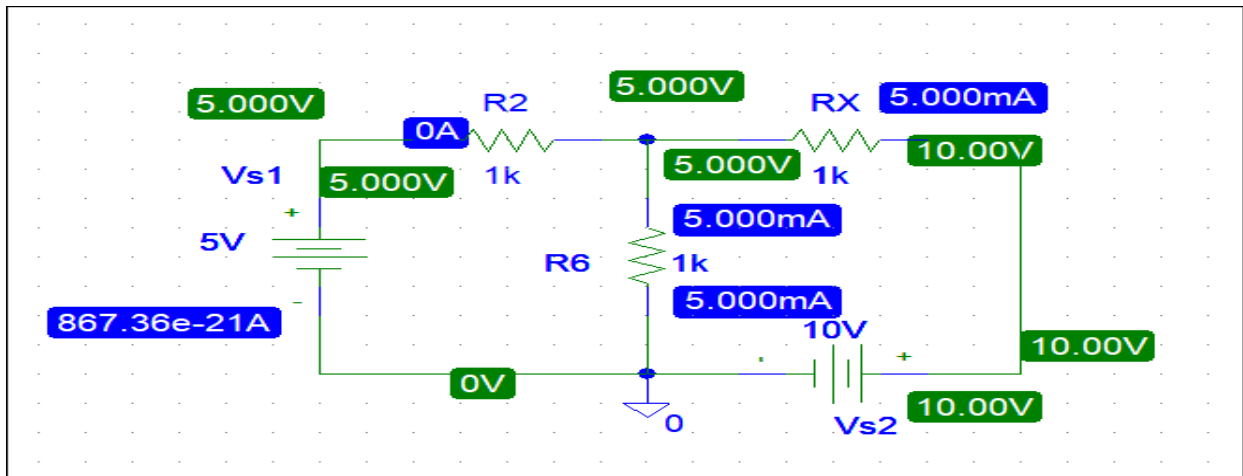


Fig D.3

- without terminals:

$$R_{th} = (R2 // R6) + R_x = 1.5k.$$

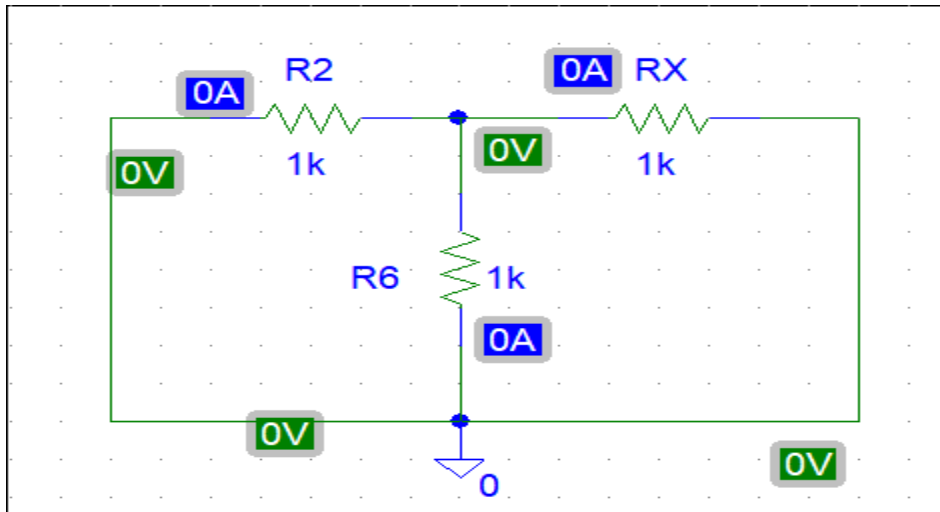


Fig D.4

- Equivalent Thevenin Circuit:

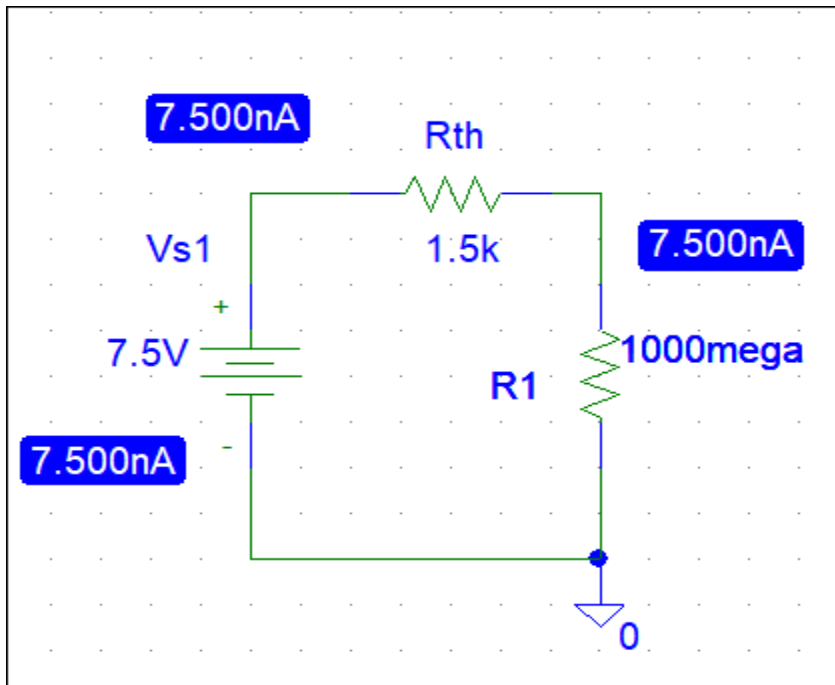


Fig D.5

- After connect R1:

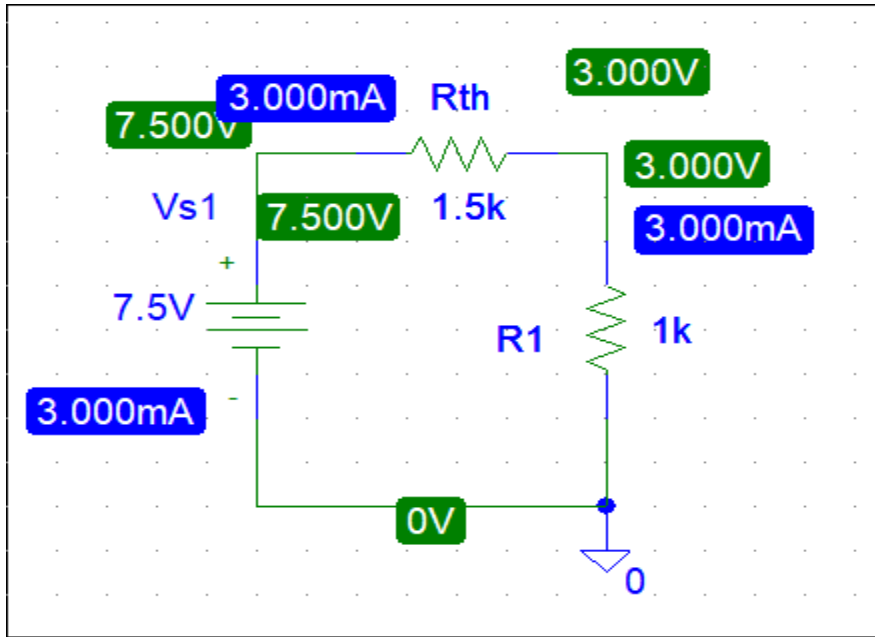


Fig D.6

The voltage across R1 =3 volt and this value is equal to the value we measured o step 2.

- After this comparison we conclude that the relationship between the two circuits is equivalent circuits but with different design.