



Faculty of Engineering & Technology
Electrical & Computer Engineering Department

ENEE2103

PreLab#2

First and Second Order Circuit

Prepared by : Tareq Shannak

ID Number : 1181404



Instructor : Dr. Alhareth Zyoud

Teaching Assistant : Mahdi Salem

Section : 5

Date : 3/3/2021

Part A: RC Circuit

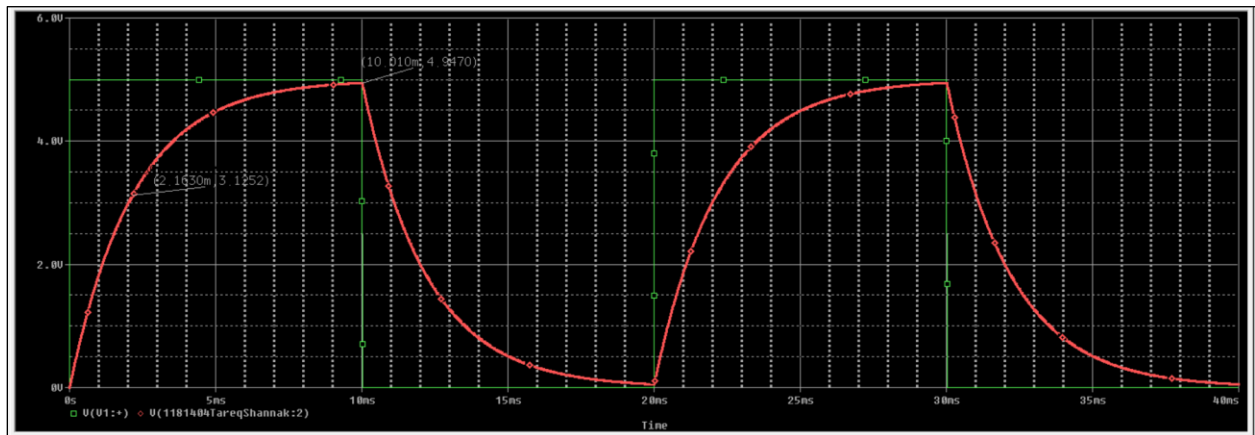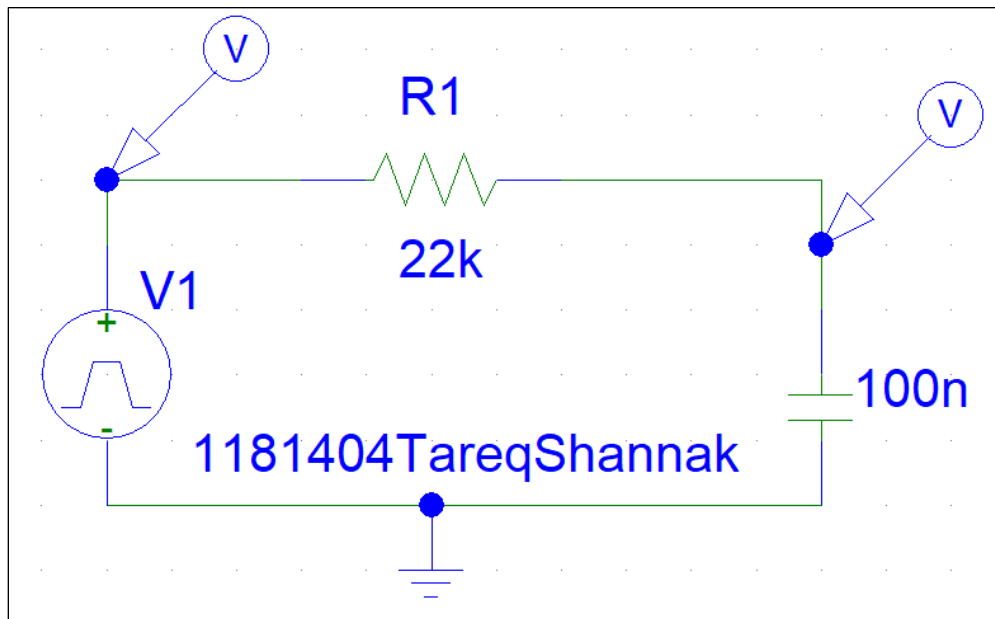



$$V_{\text{charging}} = 4.947 * 0.63 = 3.11661\text{v}$$

When $V = 3.1252\text{v}$, $t = T = 2.163\text{ms}$ from graph

$$T = RC = 22\text{k} * 100\text{nF} = 2.2\text{ms} \text{ (theoretical)}$$

$$C = T/R = 2.163\text{ms}/22\text{k} = 98.3 \text{ nF} \text{ (too close from } 100\text{nF)}$$

Part B: RL Circuit

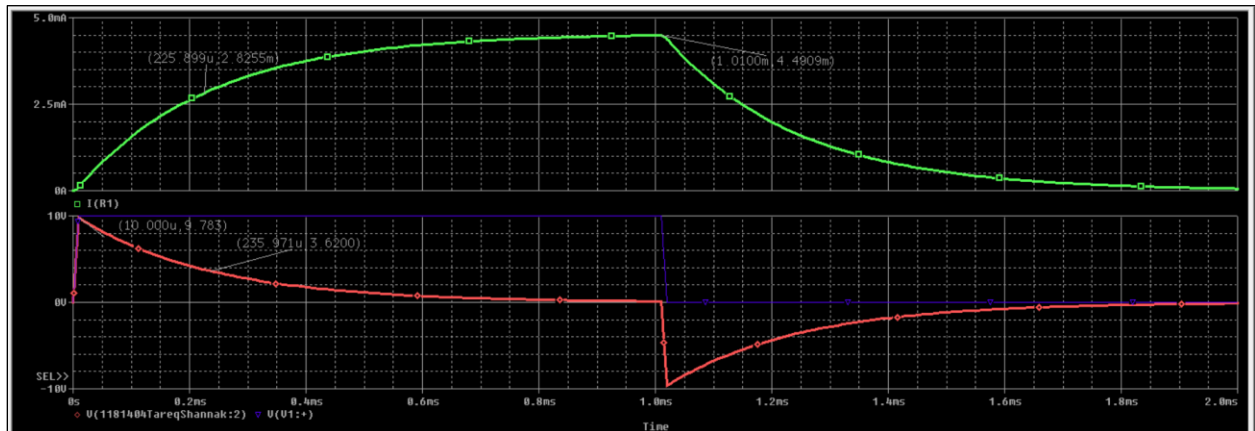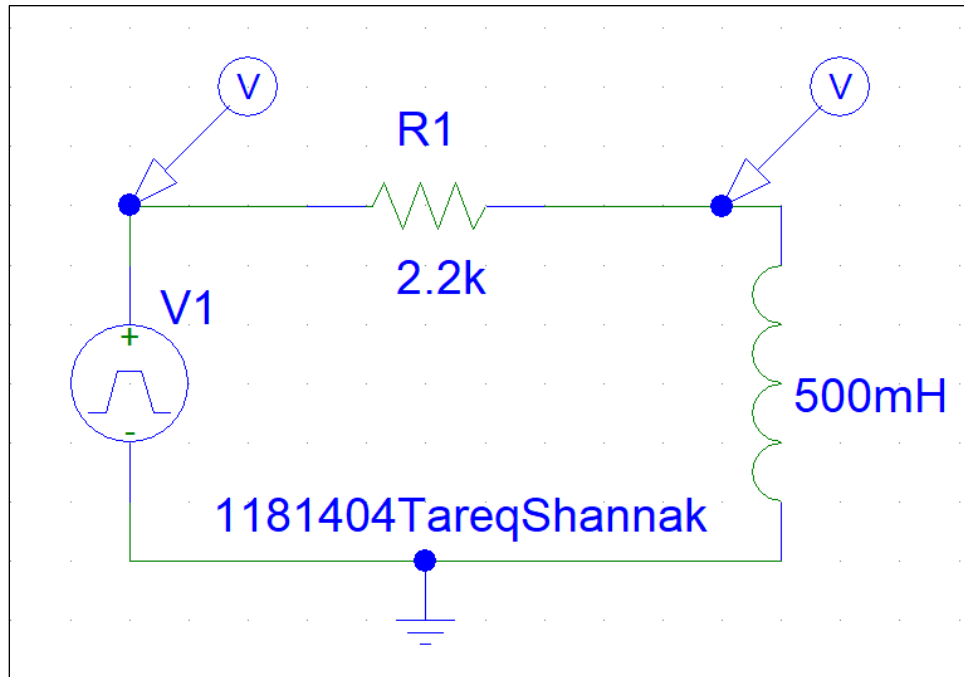

Since it's charging in the current response, $I_{\text{charging}} = 0.63 * 4.4909\text{mA} = 2.829\text{ m}$, $t = T = 226\text{us}$



Since it's discharging in the voltage response, $V_{\text{Discharging}} = 0.37 * 9.783 = 3.62\text{v}$, $t = T = 236\text{us}$

$t = T = L/R = 500\text{mH}/2.2\text{k} = 227\text{us}$ (Theoretical)

The practical results are too close from the theoretical results.

$$T = 2\tau L = 2 * L / R?$$

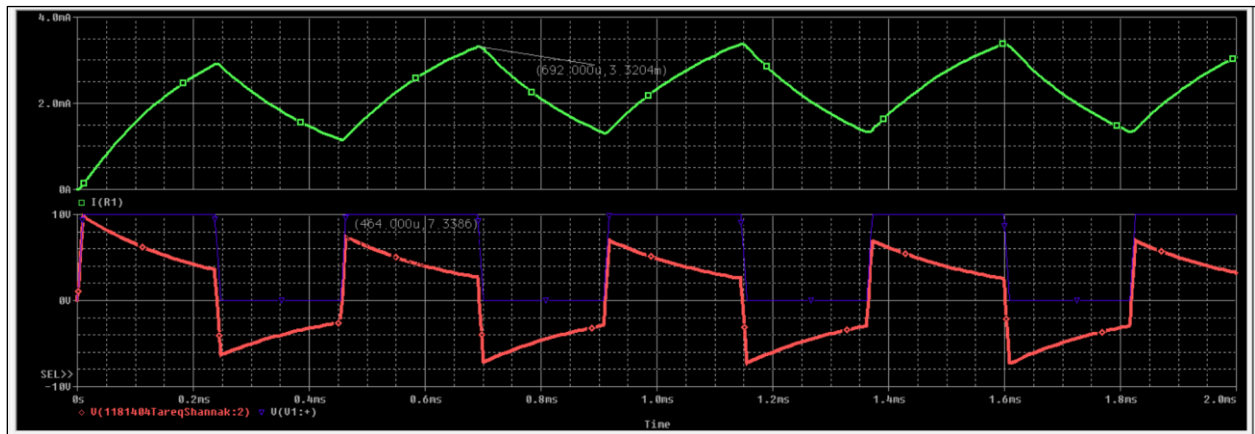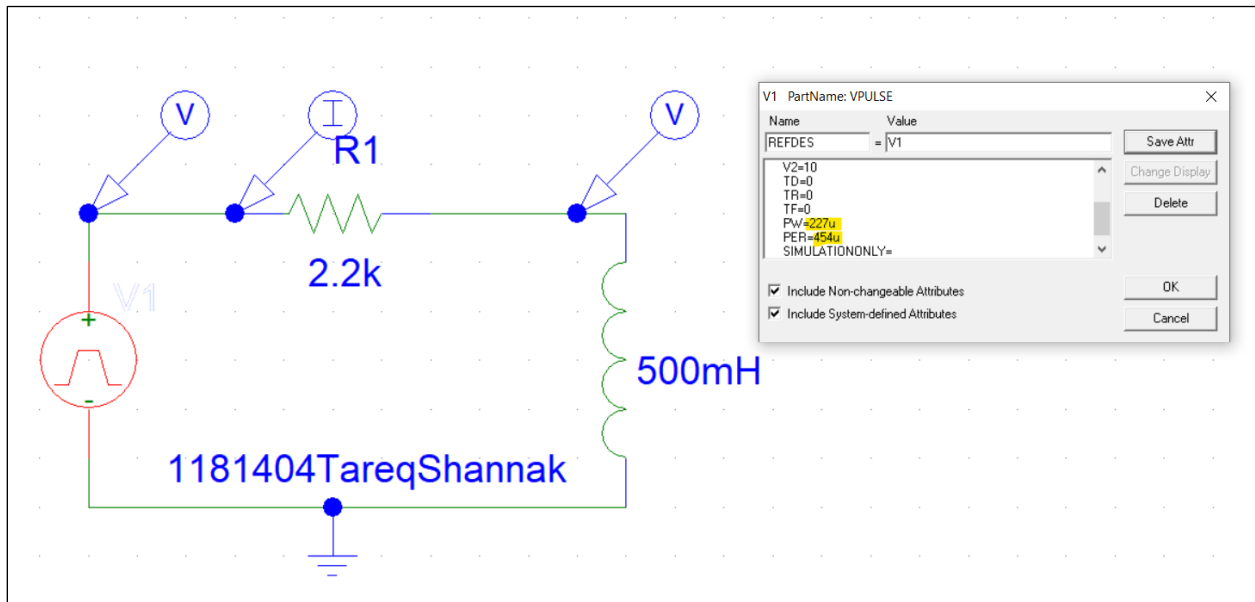$T = 2 * 500\text{m} / 2.2\text{k} = 454\text{us} =$ the period of the periodic square wave.



The period is too small and not enough to charging.



Part C: RLC Circuit

Response Type

$$a = R/2L = 22k/1H = 22000$$

$$\omega = 1/\sqrt{LC} = 4472$$

$a > \omega$? Overdamped

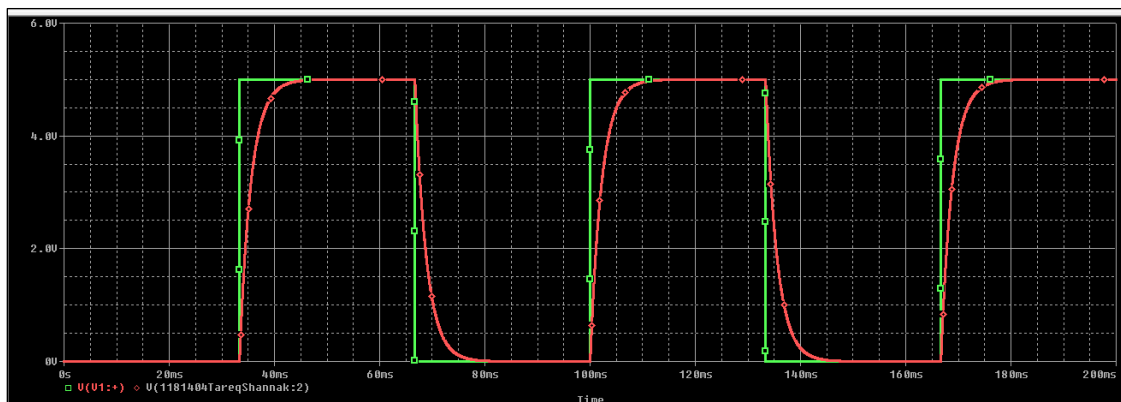
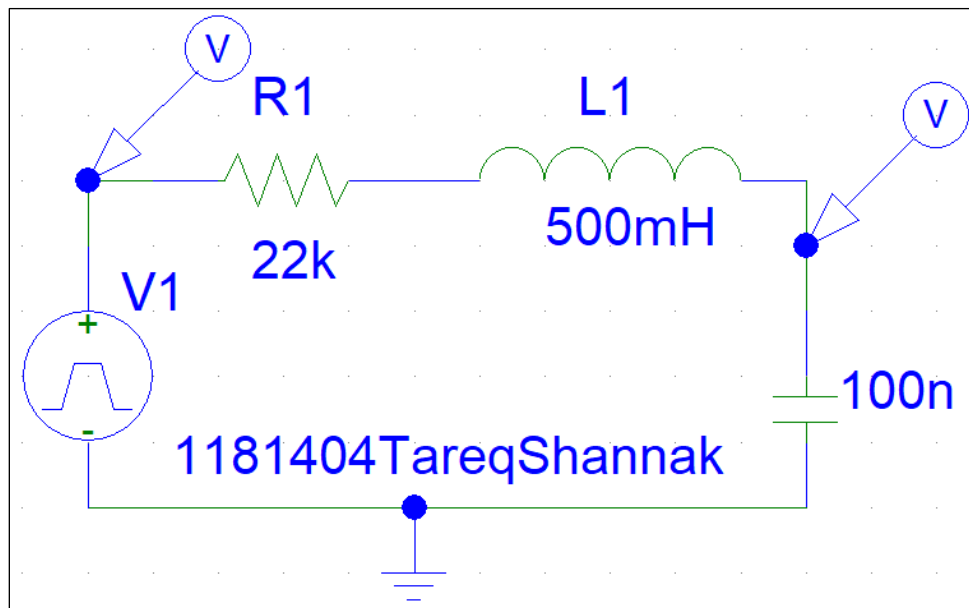


To be underdamped: $a < \omega \rightarrow R / 2L < 1 / \sqrt{LC} \rightarrow R < 2L / \sqrt{LC} \rightarrow R < 4.47 \text{ K ohm}$



To be overdamped: $R > 4.47 \text{ K ohm}$

To be critical damped: $R = 4.47 \text{ K ohm}$



Critical damping: $R = 4.47\text{ K}$

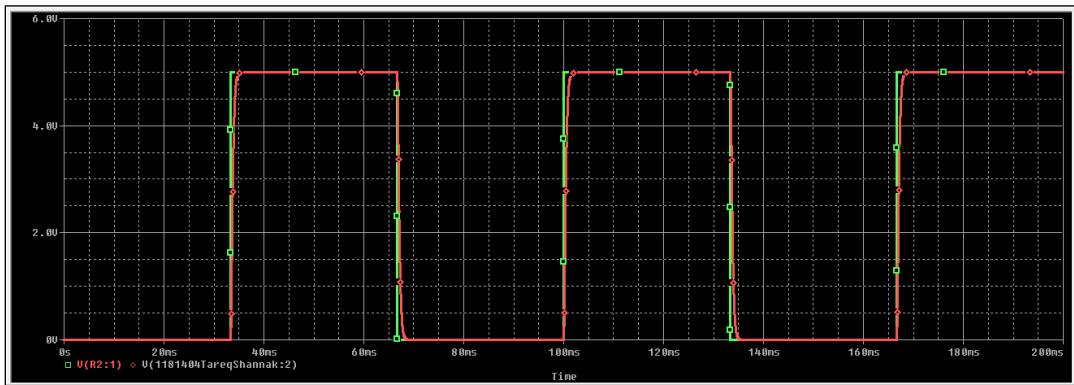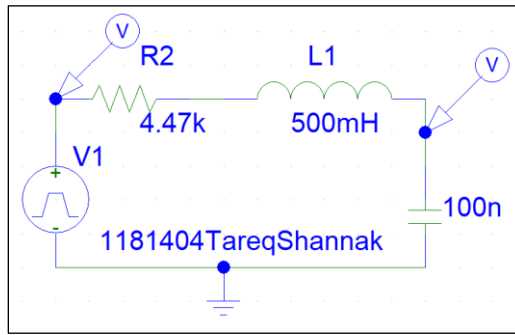

Underdamping: $R = 750$

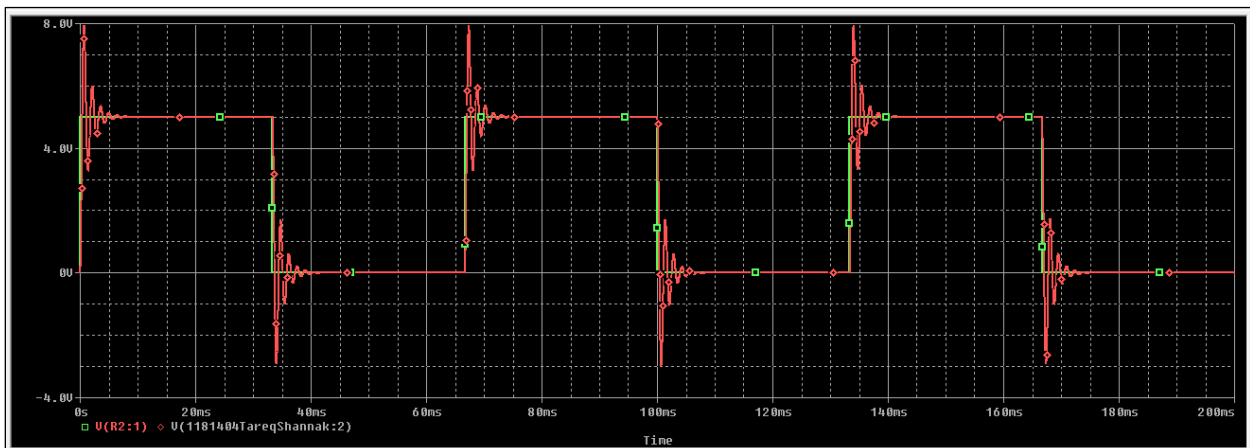
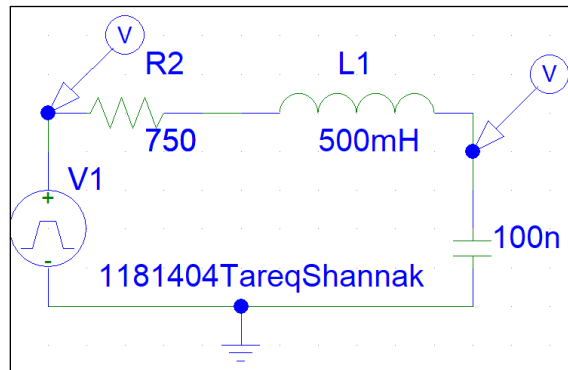


Using PARAM Element

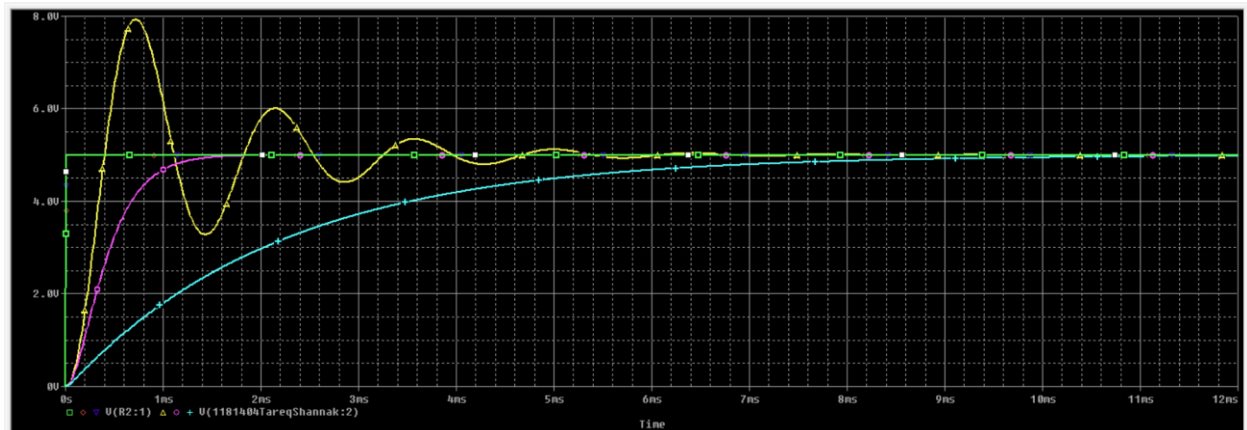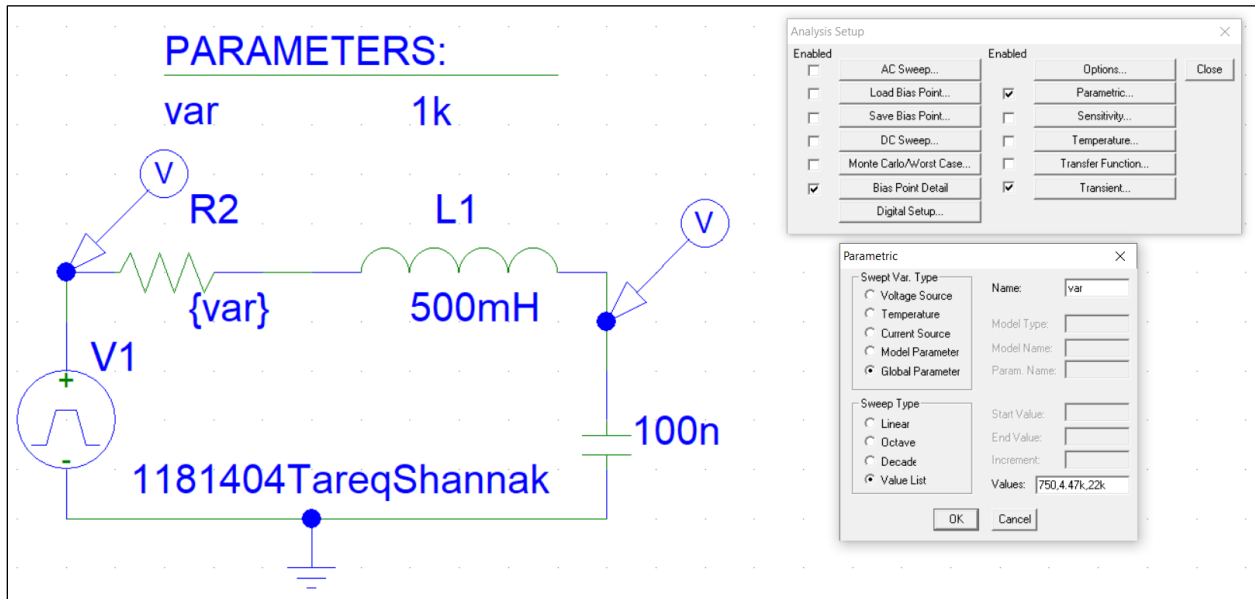

We can notice that when $R=4.47k$ (Critical Damping – the pink curve), the output voltage is near from the input voltage (the green curve).

Response Parameters

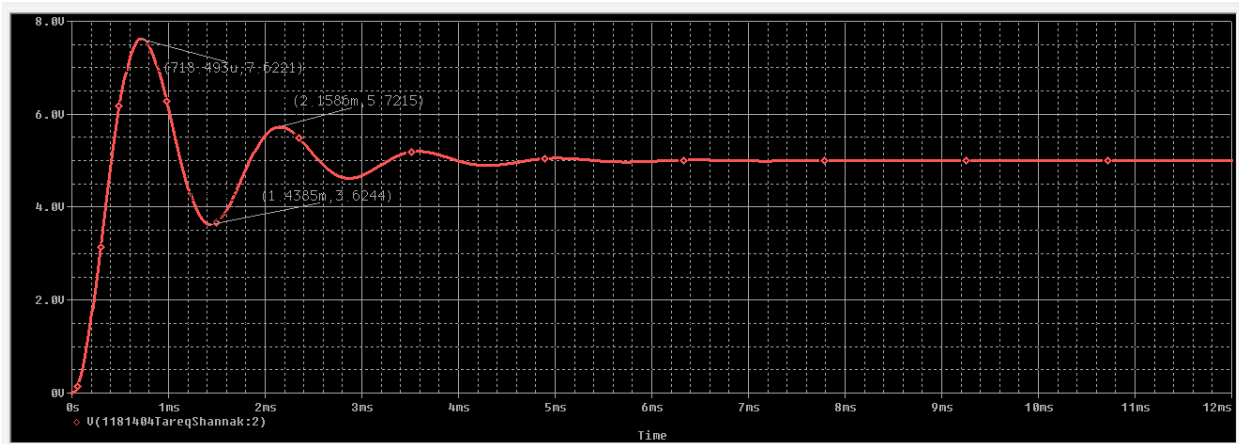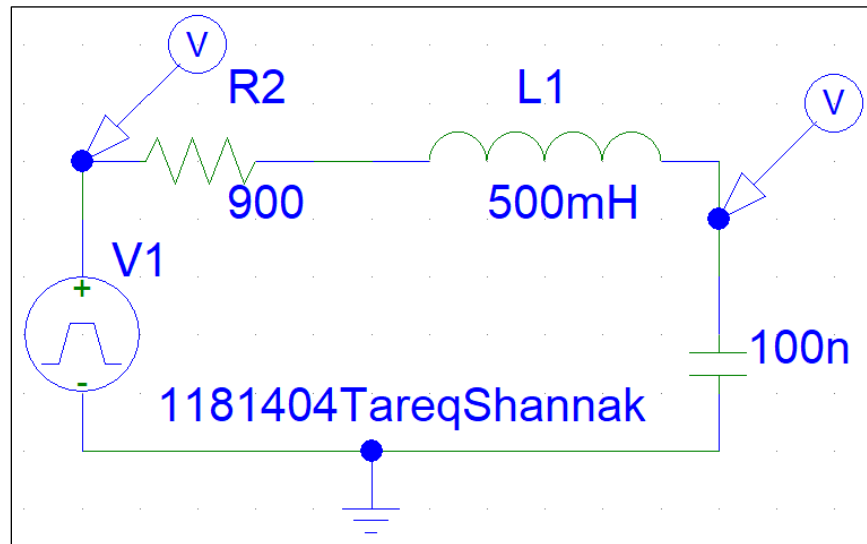


$$V_a = 7.6221, V_b = 5.7215, T_a = 718.493\mu\text{s}, T_b = 2.1586\text{ms}, V_\infty = 5\text{v}$$

$$\tau = (T_b - T_a) / \ln((V_a - V_\infty) / (V_b - V_\infty)) = 1116\mu\text{s}$$

$$\alpha = 1/\tau = 896 \text{ rad/sec}$$

$$\omega d = 2 * \pi / (T_b - T_a) = 4.36\text{k rad/sec}$$

C = 200nF?

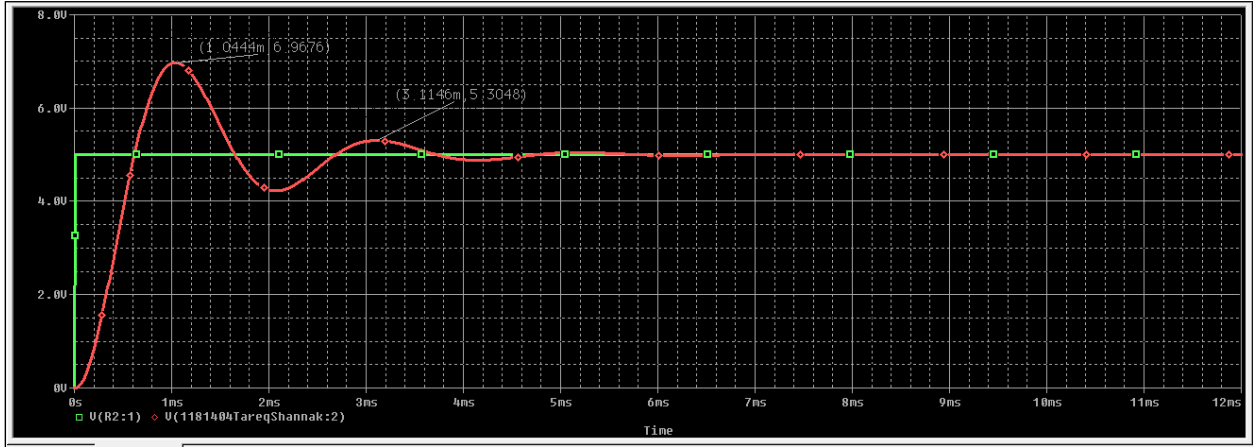


$V_a = 6.9676$, $V_b = 5.3048$, $T_a = 1.0444\text{ms}$, $T_b = 3.3146\text{ms}$, $V_\infty = 5\text{v}$

$$\tau = (T_b - T_a) / \ln((V_a - V_{\infty}) / (V_b - V_{\infty})) = 1.217\text{ms}$$

$$\alpha = 1/\tau = 821 \text{ rad/sec}$$

$$\omega d = 2 * \pi / (T_b - T_a) = 2.766\text{k rad/sec}$$

L = 250mH?

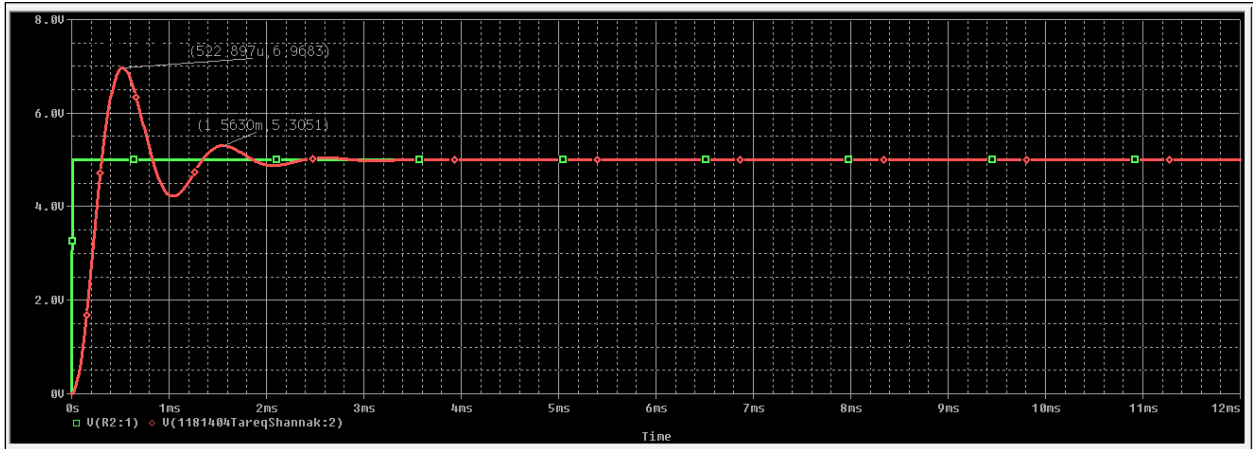

$V_a = 6.9683$, $V_b = 5.3051$, $T_a = 522.897\text{us}$, $T_b = 1.563\text{ms}$, $V_\infty = 5\text{v}$

$$\tau = (T_b - T_a) / \ln((V_a - V_{\infty}) / (V_b - V_{\infty})) = 557.909\text{us}$$

$$\alpha = 1/\tau = 1792 \text{ rad/sec}$$

$$\omega d = 2 * \pi / (T_b - T_a) = 6.037\text{k rad/sec}$$