



Faculty of Information Technology
Electrical and Computer Engineering Department
CIRCUITS AND ELECTRONICS LABORATORY (ENEE2103)

Prelab Experiment#3
“First and Second Order Circuit”

Instructor: Dr. Wael Hashlamoun

Teacher: Eng. Mostafa Helal



Student Name: Mays Sbaih

Student Number:1160006

Section 3

Due to:25-2-2019


Part A. RC Circuit:

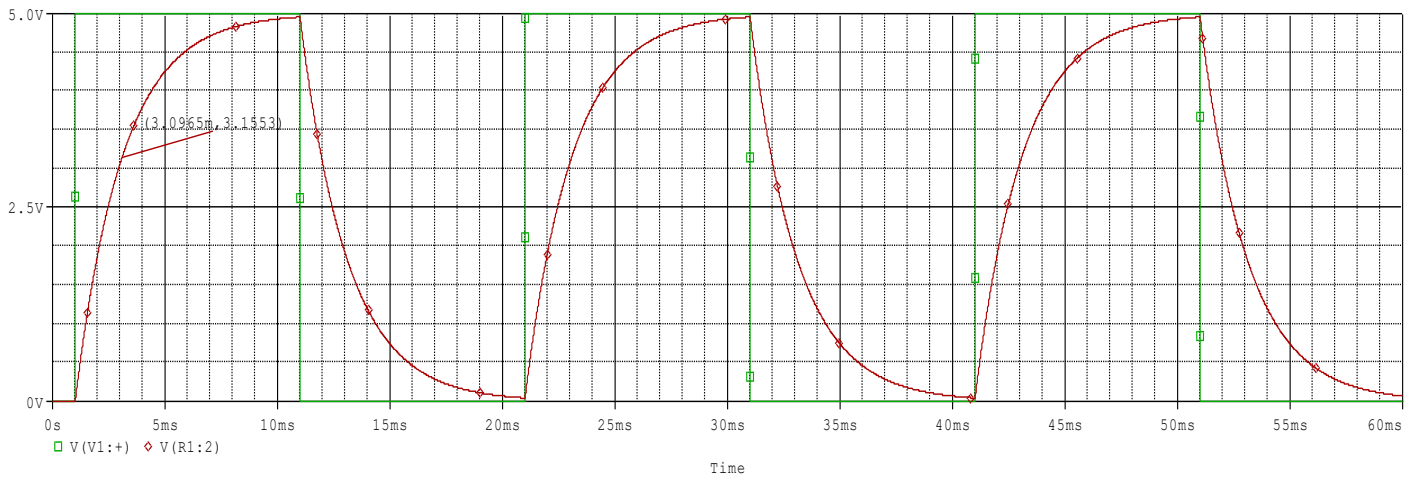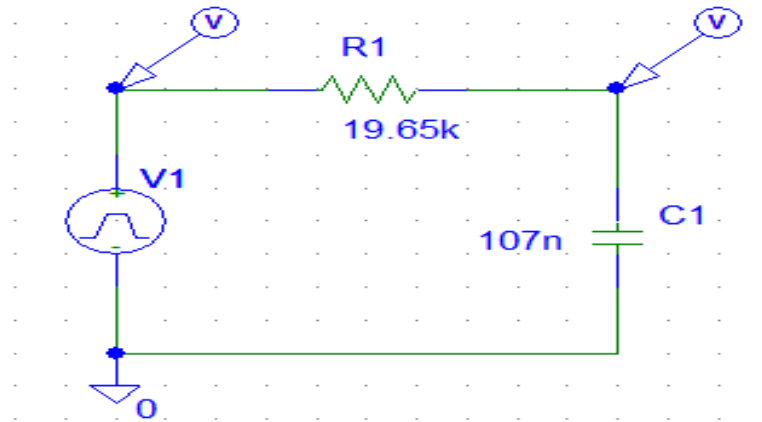

Steady state voltage value on the capacitor = 5 volt. To calculate time constant, we use the assumption that it is at charging when $V(t) = 0.63 * V_{max} = 0.63 * 5 = 3.15v$


- Time constant from Simulation ≈ 3.0965 ms.
- Time Constant time from calculation (τ) = $RC = (19.65k)(107nF) = 2.103$ ms.

Part B. RL Circuit:

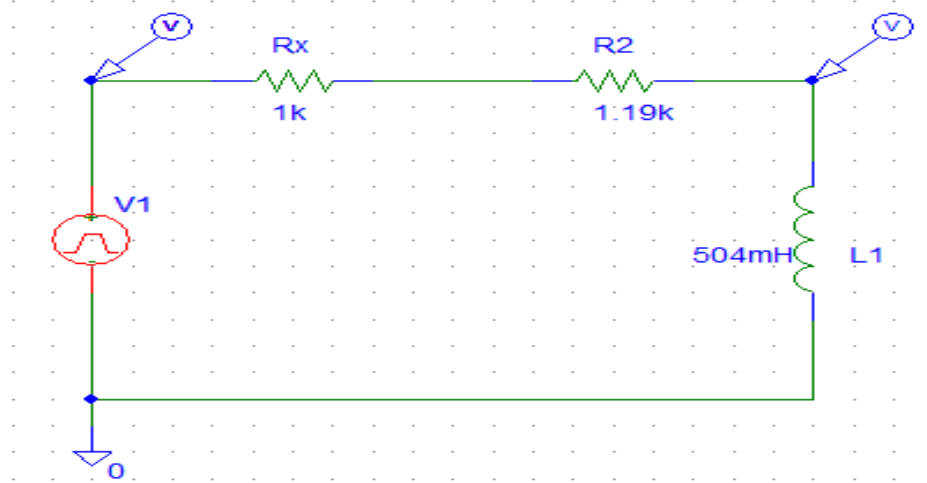

- When frequency = 500Hz.


Voltage response

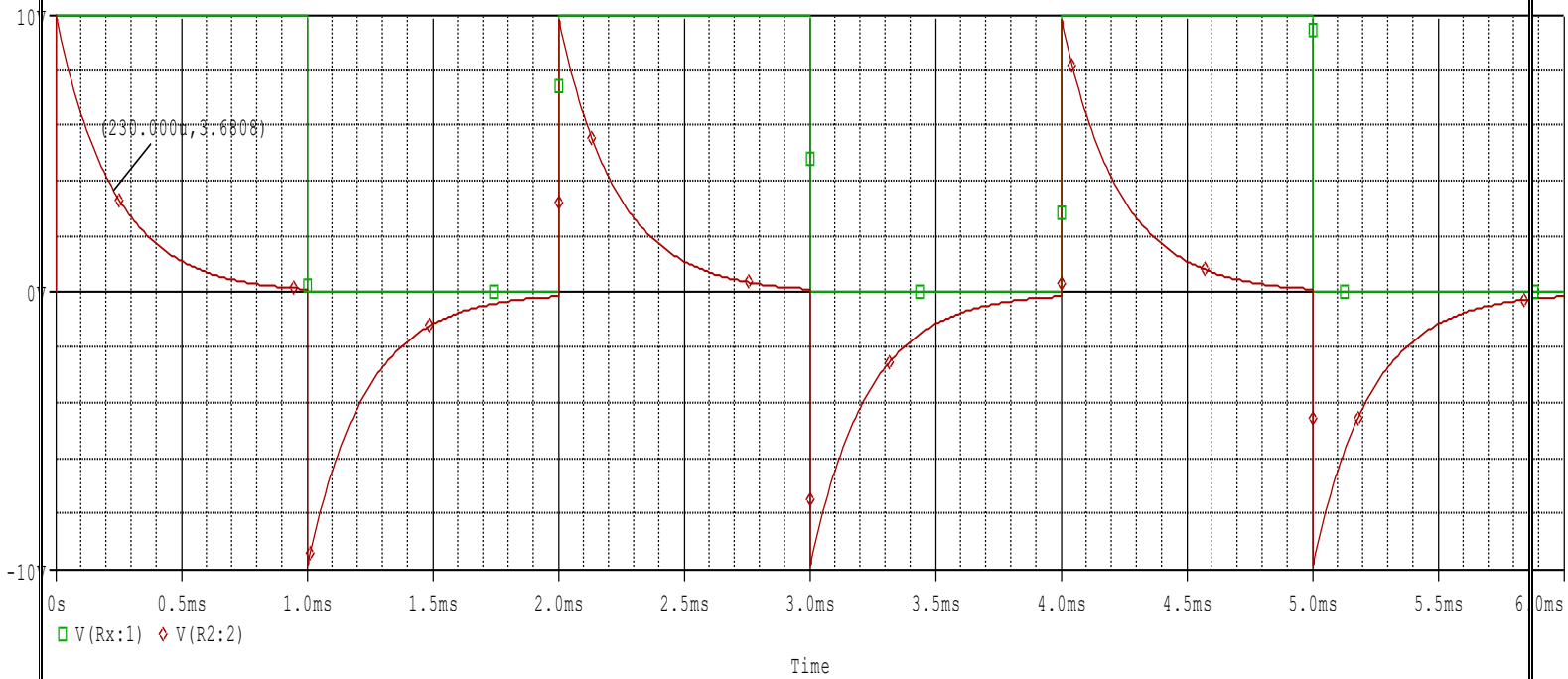

To calculate time constant, we use the assumption that it is at discharging when $V(t) = 0.37 V_{max} = 0.37 * 10 = 3.7$ volt


- Time constant from Simulation ≈ 230.0 us.
- Time Constant from calculation $= L/R = (504\text{mH}) / (2.19\text{k}) = 230.137$ us.

Current response

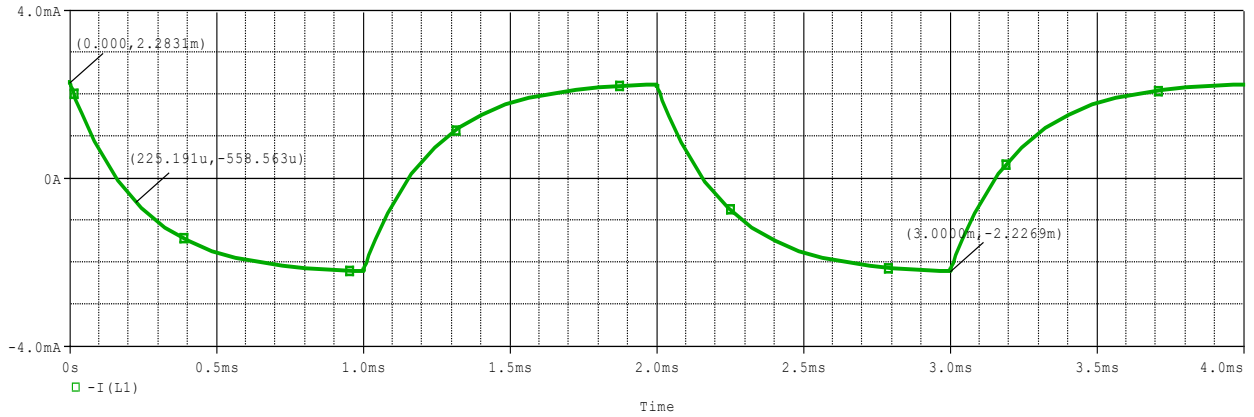


- When $T = 2 \cdot \text{Time constant}$.
 - Period $T = 2 \cdot 230.137 \approx 460 \mu\text{s}$.
 - Frequency $= 1/T = 2.17 \text{ MHz}$.



Current response

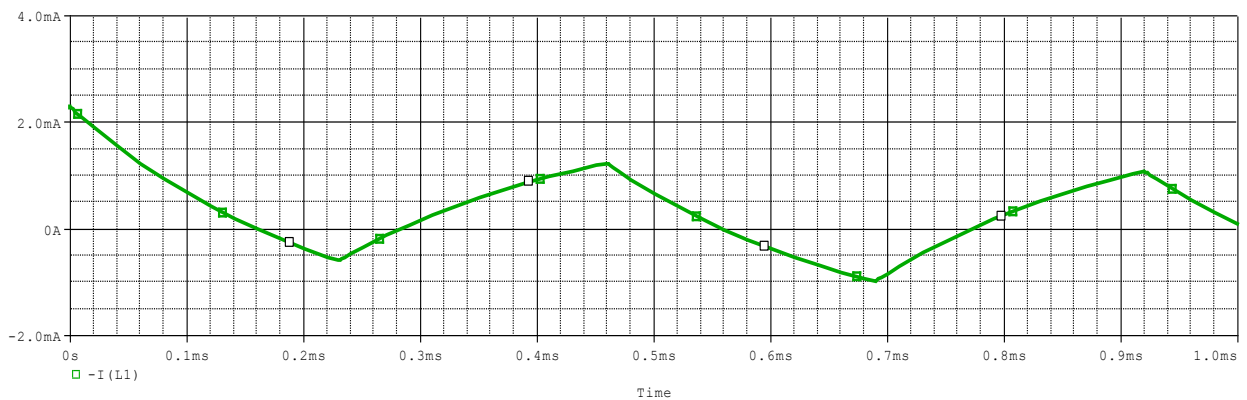

Voltage Response

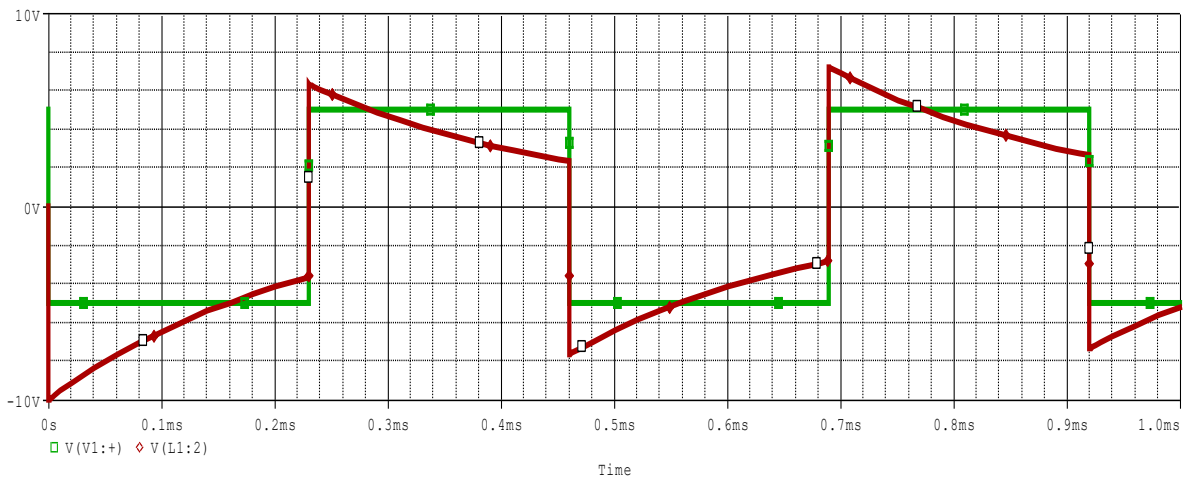

C. RLC Circuit:

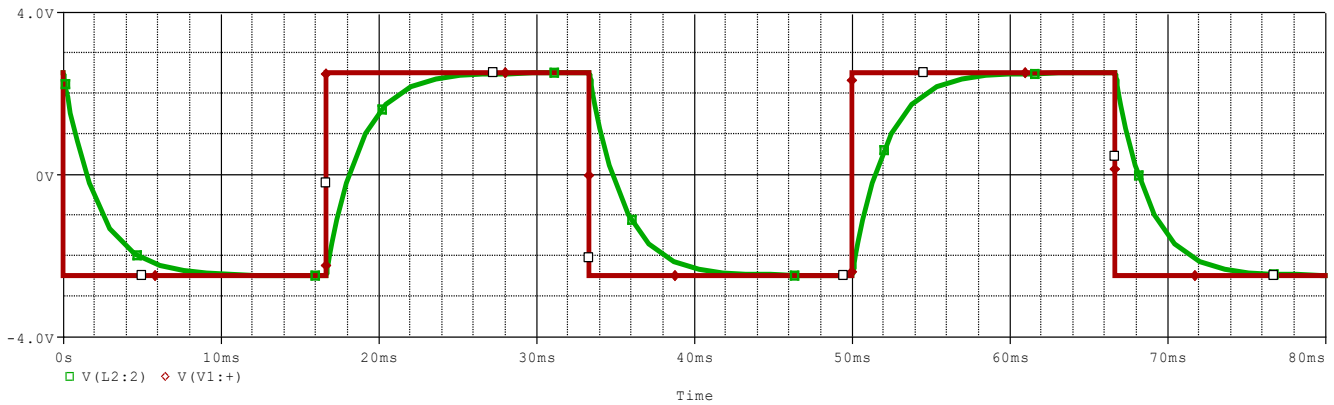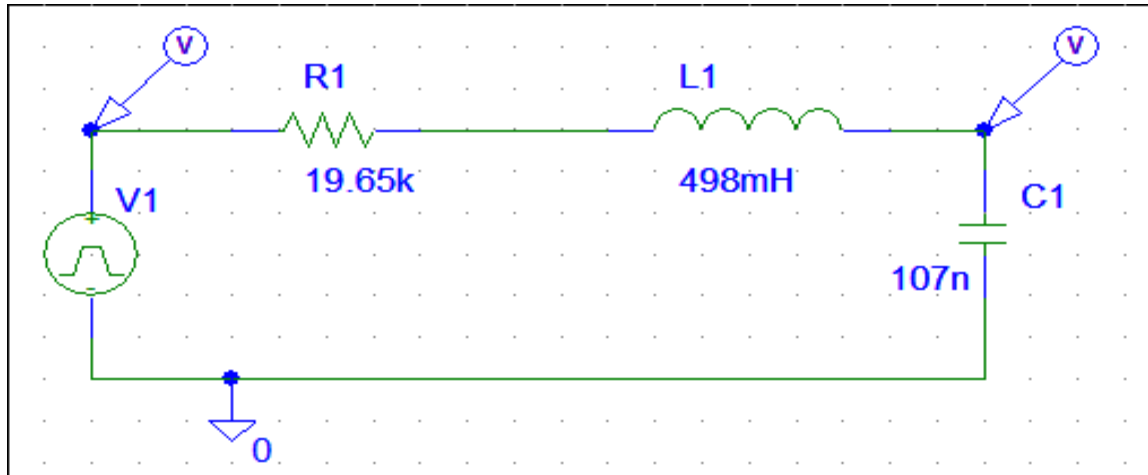


- Type of response is overdamping.

To find R that causes critical damping numerically:

Neper frequency (α) = $R/2L$, $\omega_o = 1/\sqrt{LC}$.

Critical damping when $\alpha^2 = \omega_o^2 \rightarrow R = 2 \sqrt{L/C} = 4314.7216 \text{ Ohm}$

• Critical Damping:

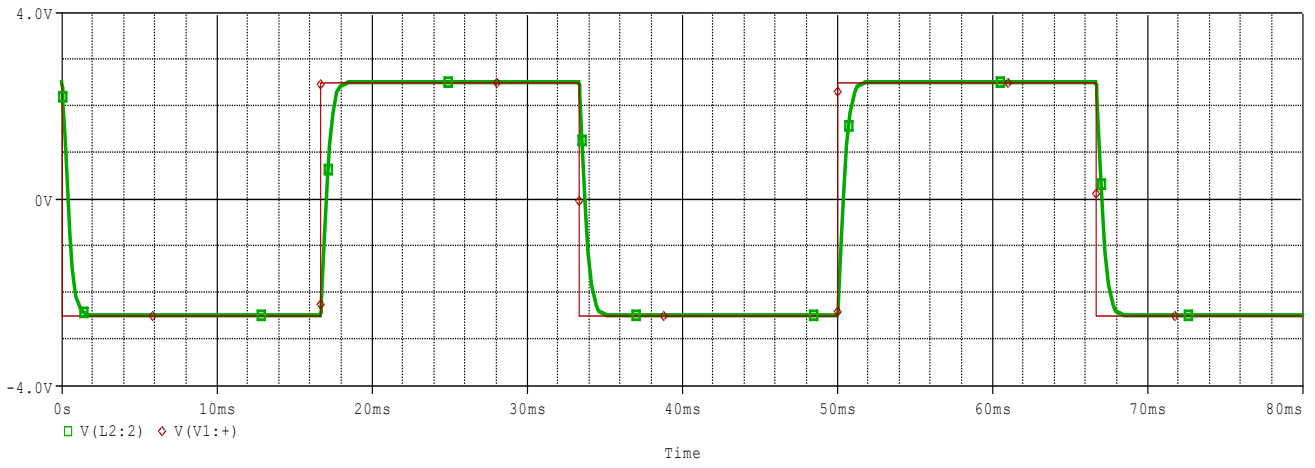

• Underdamping (R=500 Ohm)

