



Faculty of Engineering & Technology
Electrical & Computer Engineering Department

ENEE2103

PreLab#03

Sinusoidal Steady State Circuit Analysis

Prepared by : Tareq Shannak

ID Number : 1181404

Instructor : Dr. Alhareth Zyoud


Teaching Assistant : Mahdi Salem

Section : 5


Date : 14/3/2021

Part A: Impedance

Simple AC Circuit

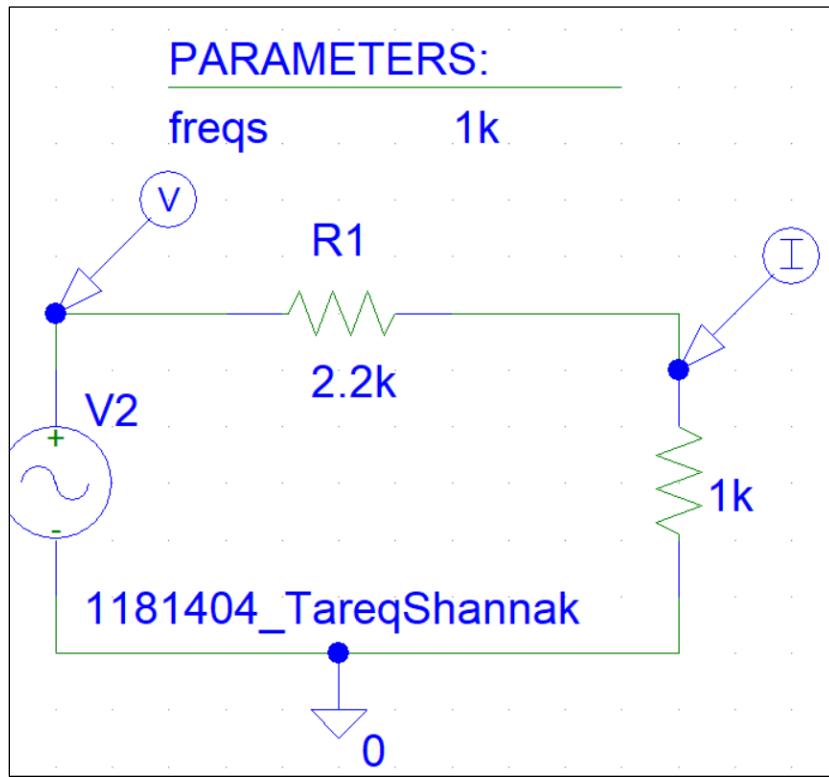

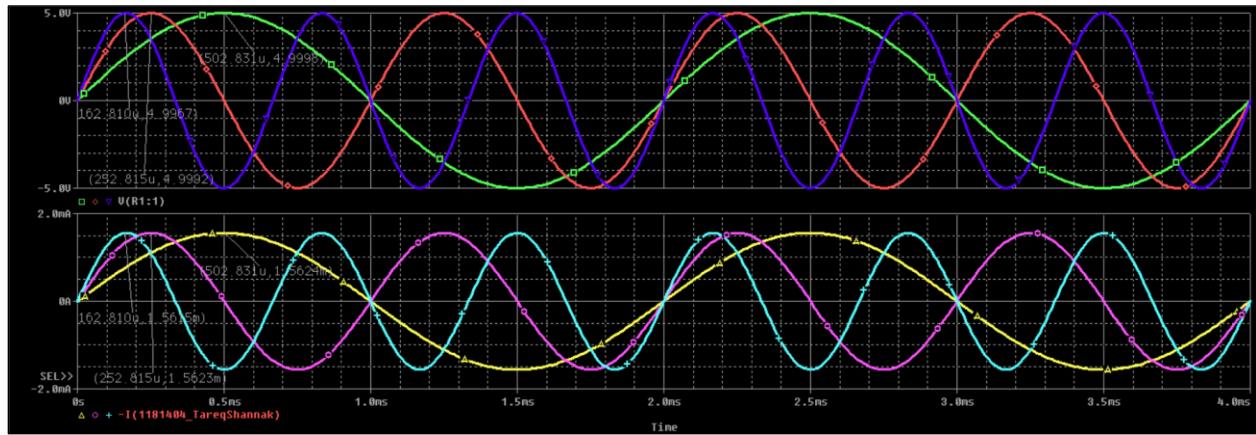{Freqs} is a variable has a list: 0.5k, 1k, 1.5k.





In three frequency cases, there are in-phase and the impedance is almost the same:

$$Z = \frac{V_{max}}{I_{max}} = \frac{4.99}{1.562m} = 3.196k\Omega \text{ from graph}$$

$$Z = R = (2.2 + 1)k\Omega = 3.2k\Omega \text{ from theory (Too Close)}$$

RC Circuit

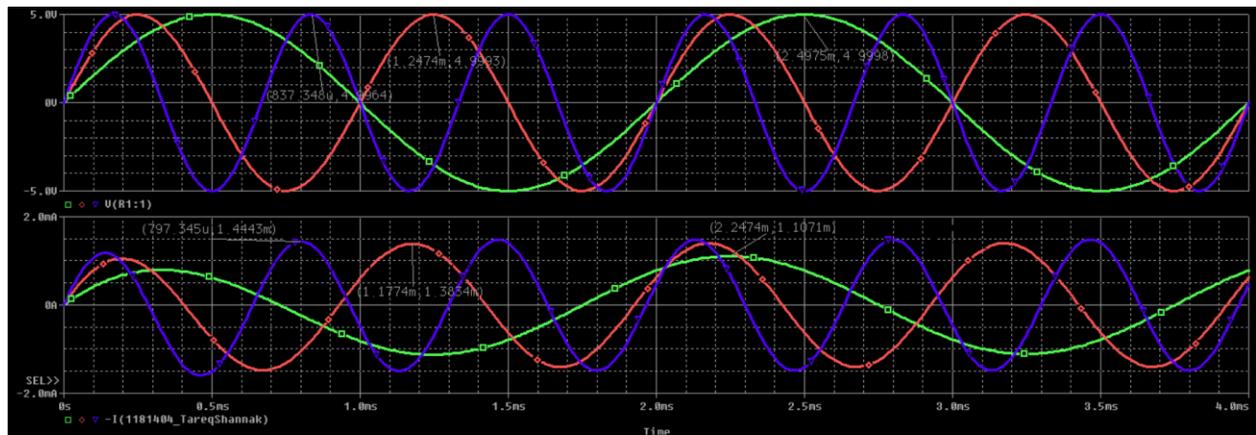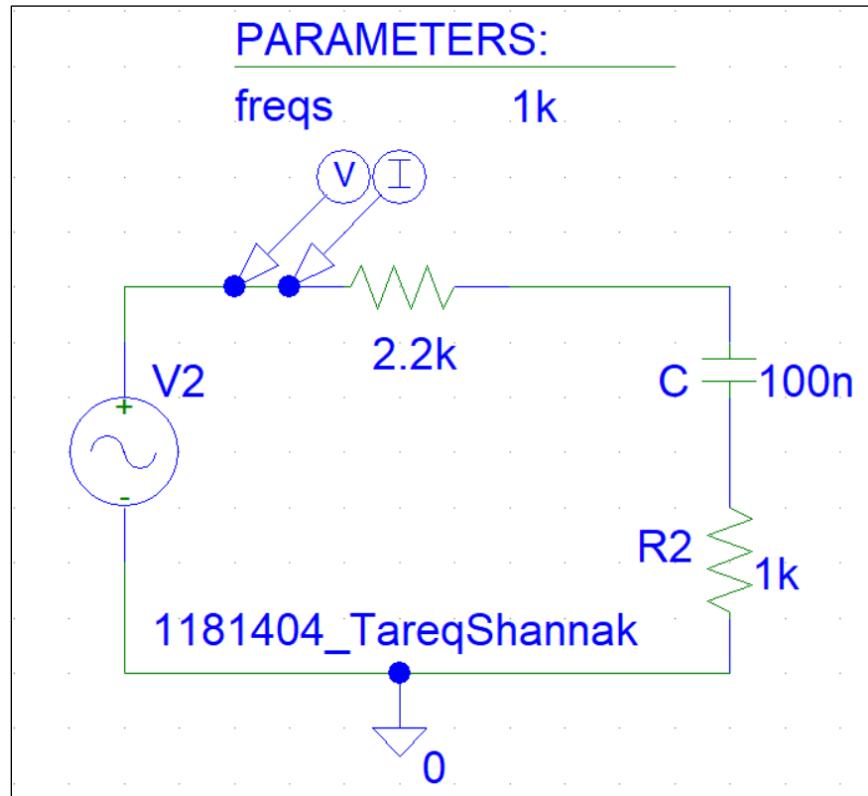

Because it's a capacitive circuit, current in all cases leads the voltage by a phase shift

Note: when a phase shift is positive, then voltage leads current (inductive), otherwise is the opposite.

F=0.5KHZ

$$\text{From Graph: } Z = \frac{V_{max}}{I_{max}} = \frac{4.999}{1.1071m} = \textcolor{red}{4.515k\Omega}$$

$$\text{Phase Shift} = \frac{T_{app} \times 360}{Period} = \frac{(2.2474m - 2.4975m) \times 360}{2m} = \textcolor{green}{-45.018 \text{ degrees}}$$

$$\text{From Theory: } Z = R_1 + R_2 + \frac{1}{j2\pi fc} = 2.2k + 1k + \frac{1}{j2\pi(0.5k)(100n)} = 3.2 - j(3.183) k\Omega$$

$$|Z| = \sqrt{(R^2 + X^2)} = \sqrt{(3.2^2 + 3.183^2)} k\Omega = \textcolor{red}{4.513k\Omega}$$

$$\text{Phase Shift} = \tan^{-1} \frac{X_c}{R} = \tan^{-1} \frac{-3.183k}{3.2k} = \textcolor{green}{-44.847 \text{ degrees}}$$

F=1KHZ

$$\text{From Graph: } Z = \frac{V_{max}}{I_{max}} = \frac{4.999}{1.3834m} = \textcolor{red}{3.614k\Omega}$$

$$\text{Phase Shift} = \frac{T_{app} \times 360}{Period} = \frac{(1.1774m - 1.2474m) \times 360}{1m} = \textcolor{green}{-25.2 \text{ degrees}}$$

$$\text{From Theory: } Z = R_1 + R_2 + \frac{1}{j2\pi fc} = 2.2k + 1k + \frac{1}{j2\pi(1k)(100n)} = 3.2 - j(1.5915) k\Omega$$

$$|Z| = \sqrt{(R^2 + X^2)} = \sqrt{(3.2^2 + 1.5915^2)} k\Omega = \textcolor{red}{3.574k\Omega}$$

$$\text{Phase Shift} = \tan^{-1} \frac{X_c}{R} = \tan^{-1} \frac{-1.5915k}{3.2k} = \textcolor{green}{-26.443 \text{ degrees}}$$

F=1.5KHZ

$$\text{From Graph: } Z = \frac{V_{max}}{I_{max}} = \frac{4.999}{1.4443m} = \textcolor{red}{3.461k\Omega}$$



$$\text{Phase Shift} = \frac{T_{app} \times 360}{Period} = \frac{(0.7973m - 0.8373m) \times 360}{0.6667m} = \textcolor{green}{-21.6 \text{ degrees}}$$

$$\text{From Theory: } Z = R_1 + R_2 + \frac{1}{j2\pi fc} = 2.2k + 1k + \frac{1}{j2\pi(1.5k)(100n)} = 3.2 - j(1.061) k\Omega$$

$$|Z| = \sqrt{(R^2 + X^2)} = \sqrt{(3.2^2 + 1.061^2)} k\Omega = \textcolor{red}{3.371k\Omega}$$

$$\text{Phase Shift} = \tan^{-1} \frac{X_c}{R} = \tan^{-1} \frac{-1.061k}{3.2k} = \textcolor{green}{-18.344 \text{ degrees}}$$

RL Circuit

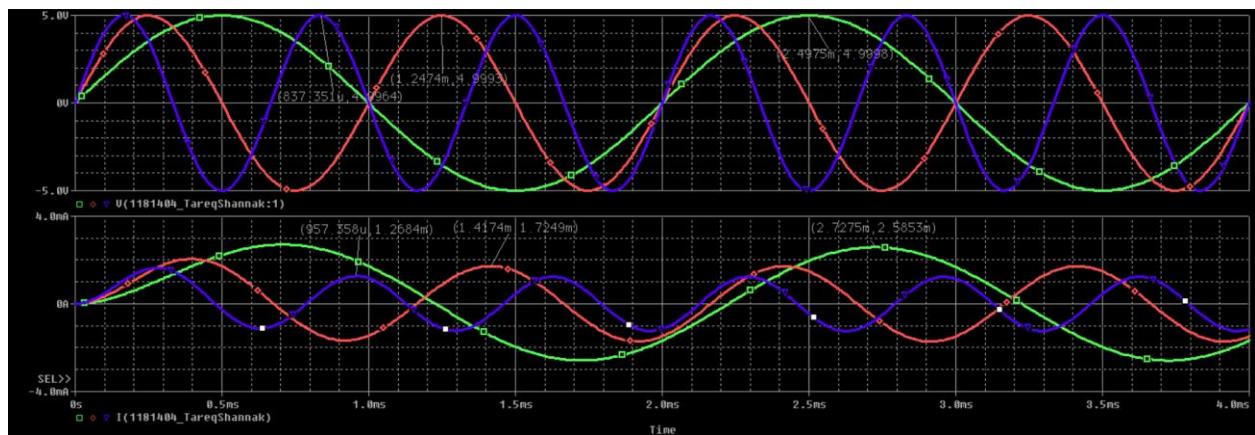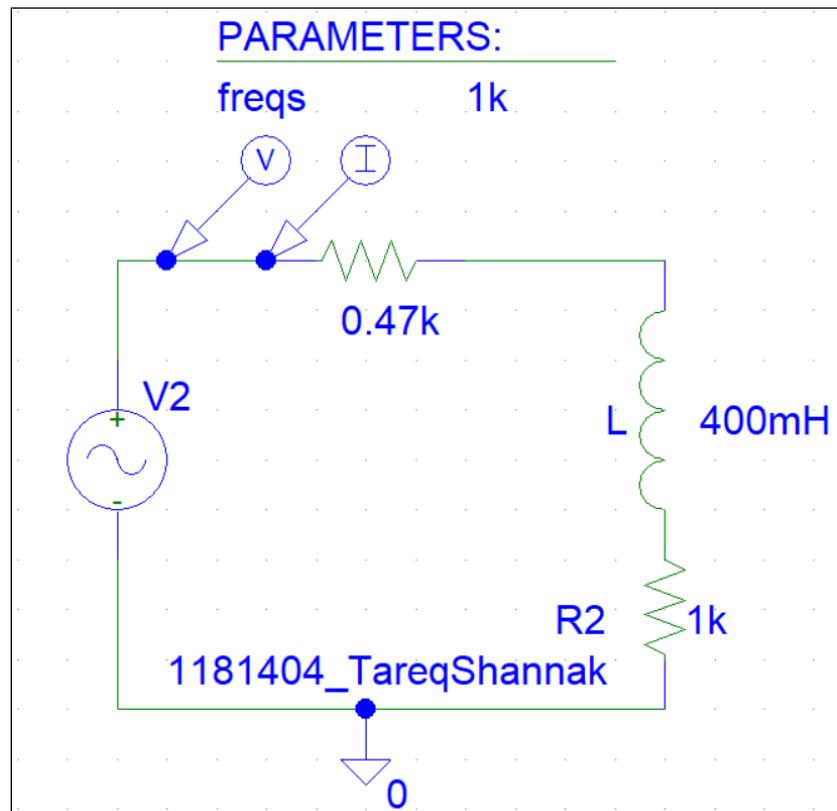

Because it's an inductive circuit, voltage in all cases leads the current by a phase shift

V

F=0.5KHZ

$$\text{From Graph: } Z = \frac{V_{max}}{I_{max}} = \frac{4.999}{2.5853\text{m}} = \text{1.934k}\Omega$$

$$\text{Phase Shift} = \frac{T_{app} \times 360}{\text{Period}} = \frac{(2.7275\text{m} - 2.4975\text{m}) \times 360}{2\text{m}} = \text{41.4 degrees}$$

From Theory: $Z = R_1 + R_2 + j2\pi fl = 0.47k + 1k + j2\pi(0.5k)(400\text{m}) = 1.47 + j(1.257)\text{k}\Omega$

$$|Z| = \sqrt{(R^2 + X^2)} = \sqrt{(1.47^2 + 1.257^2)} \text{k}\Omega = \text{1.934k}\Omega$$

$$\text{Phase Shift} = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{1.257k}{1.47k} = \text{40.534 degrees}$$

F=1KHZ

$$\text{From Graph: } Z = \frac{V_{max}}{I_{max}} = \frac{4.999}{1.7249\text{m}} = \text{2.898k}\Omega$$

$$\text{Phase Shift} = \frac{T_{app} \times 360}{\text{Period}} = \frac{(1.4174\text{m} - 1.2474\text{m}) \times 360}{1\text{m}} = \text{61.2 degrees}$$

From Theory: $Z = R_1 + R_2 + j2\pi fl = 0.47k + 1k + j2\pi(1k)(400\text{m}) = 1.47 + j(2.514)\text{k}\Omega$

$$|Z| = \sqrt{(R^2 + X^2)} = \sqrt{(1.47^2 + 2.514^2)} \text{k}\Omega = \text{2.912k}\Omega$$

$$\text{Phase Shift} = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{2.514k}{1.47k} = \text{59.684 degrees}$$

F=1.5KHZ


$$\text{From Graph: } Z = \frac{V_{max}}{I_{max}} = \frac{4.999}{1.2684\text{m}} = \text{3.939k}\Omega$$

$$\text{Phase Shift} = \frac{T_{app} \times 360}{\text{Period}} = \frac{(0.9574\text{m} - 0.8374\text{m}) \times 360}{0.6667\text{m}} = \text{64.8 degrees}$$


From Theory: $Z = R_1 + R_2 + j2\pi fl = 0.47k + 1k + j2\pi(1.5k)(400\text{m}) = 1.47 + j(3.77)\text{k}\Omega$

$$|Z| = \sqrt{(R^2 + X^2)} = \sqrt{(1.47^2 + 3.77^2)} \text{k}\Omega = \text{4.046k}\Omega$$
$$\text{Phase Shift} = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{3.77k}{1.47k} = \text{68.698 degrees}$$

Capacitive and inductive behavior

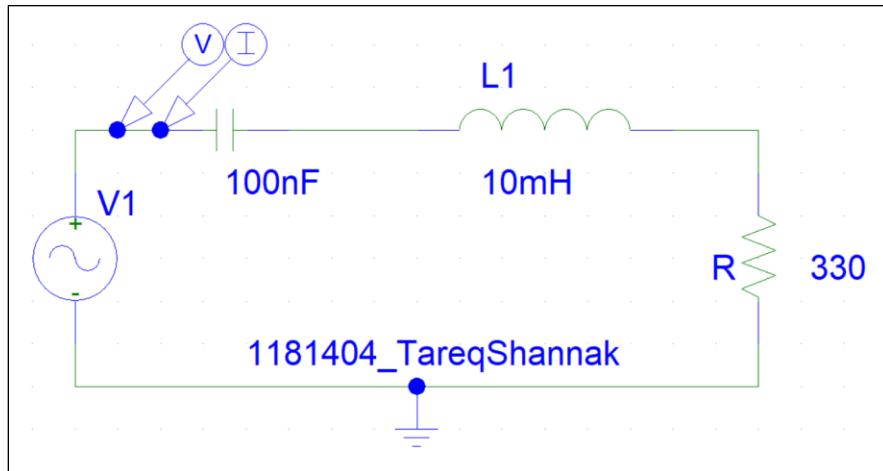

F=1KHZ

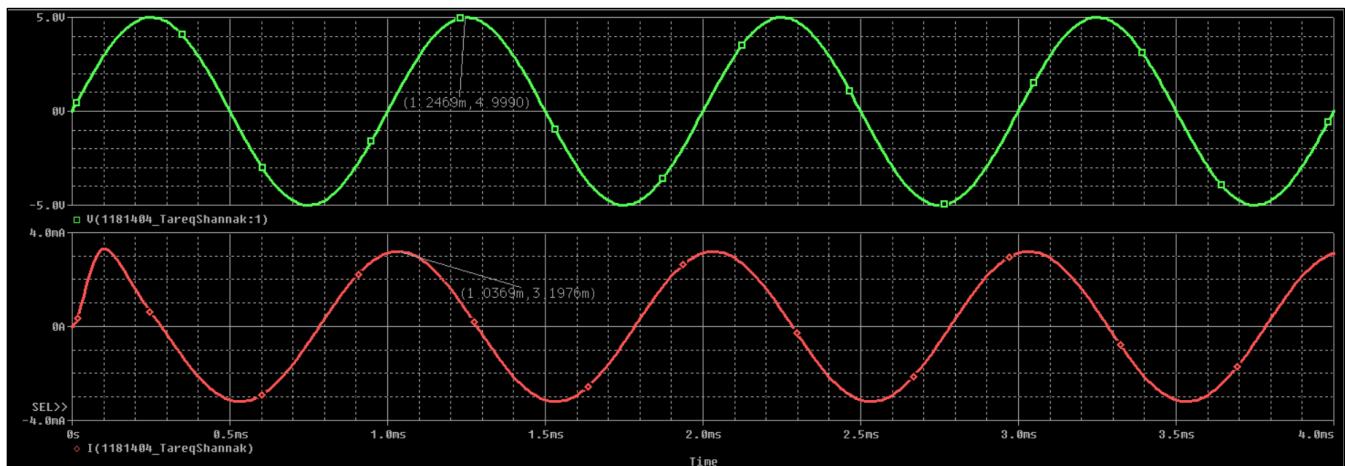

$$\text{From Graph: Phase Shift} = \frac{T_{\Delta pp} \times 360}{\text{Period}} = \frac{(1.0369\text{m} - 1.2469\text{m}) \times 360}{1\text{m}} = -75.6 \text{ degrees}$$


$$\begin{aligned} \text{From Theory: } X &= j2\pi fL + \frac{1}{j2\pi fC} = j2\pi(1k)(10m) - \frac{j}{2\pi(1k)(100n)} \\ &= j(62.832 - 1591.5) = -j 1528.7 \end{aligned}$$

$$R = 330\Omega$$

$$\text{Phase Shift} = \tan^{-1} \frac{X}{R} = \tan^{-1} \frac{-1528.7}{330} = -77.82 \text{ degrees}$$

Where current leads the voltage by 77.82 degrees, so it's a capacitive circuit.

F = F_o (Resonance Frequency)

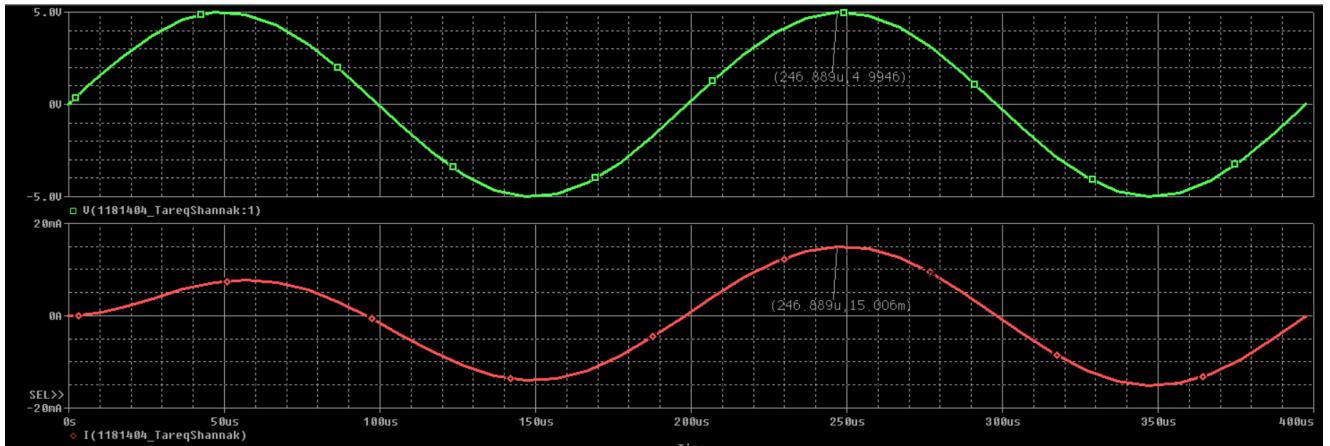

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(10m)(100n)}} \cong 5033\text{Hz}$$


From Graph: Phase Shift = $\frac{T_{app} \times 360}{Period} = \frac{(0.2469\text{m} - 0.2469\text{m}) \times 360}{0.1987\text{m}} = 0 \text{ degree}$

$$\begin{aligned} \text{From Theory: } X &= j2\pi f L + \frac{1}{j2\pi f c} = j2\pi(5.033k)(10m) - \frac{j}{2\pi(5.033k)(100n)} \\ &= j(316.232 - 316.232) = 0 \end{aligned}$$

$$\text{Phase Shift} = \tan^{-1} \frac{X}{R} = \tan^{-1} \frac{0}{330} = 0 \text{ degree}$$

The current and voltage signals are in phase.

F = 2F_o

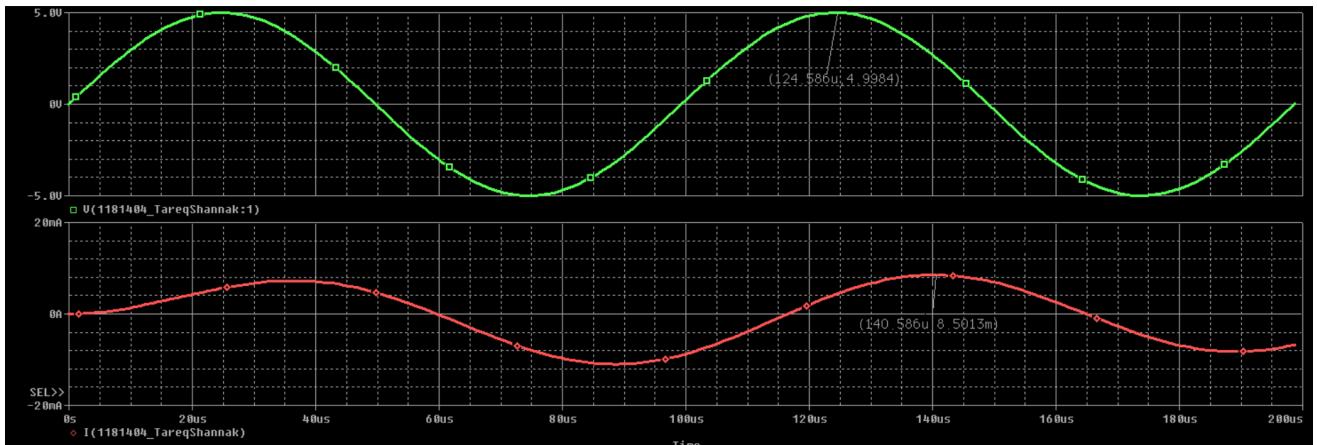


From Graph: Phase Shift = $\frac{T_{app} \times 360}{Period} = \frac{(140.6\mu - 124.6\mu) \times 360}{99.344\mu} = 57.98 \text{ degrees}$

$$\begin{aligned} \text{From Theory: } X &= j2\pi f L + \frac{1}{j2\pi f c} = j2\pi(10.066k)(10m) - \frac{j}{2\pi(10.066k)(100n)} \\ &= j(632.465 - 158.111) = j 474.354 \end{aligned}$$


$$\text{Phase Shift} = \tan^{-1} \frac{X}{R} = \tan^{-1} \frac{474.354}{330} = 55.17 \text{ degrees}$$

Where voltage leads the current by 55.17 degrees, so it's an inductive circuit.

Double the value of the capacitor

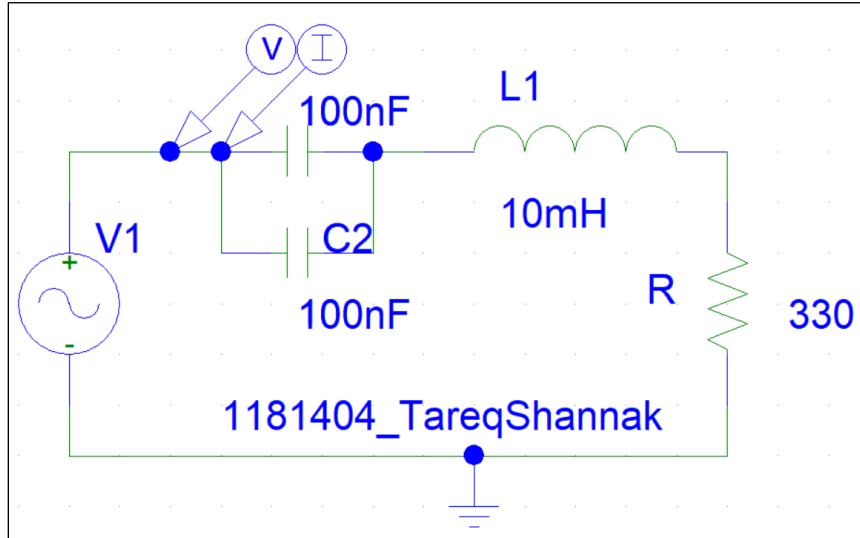

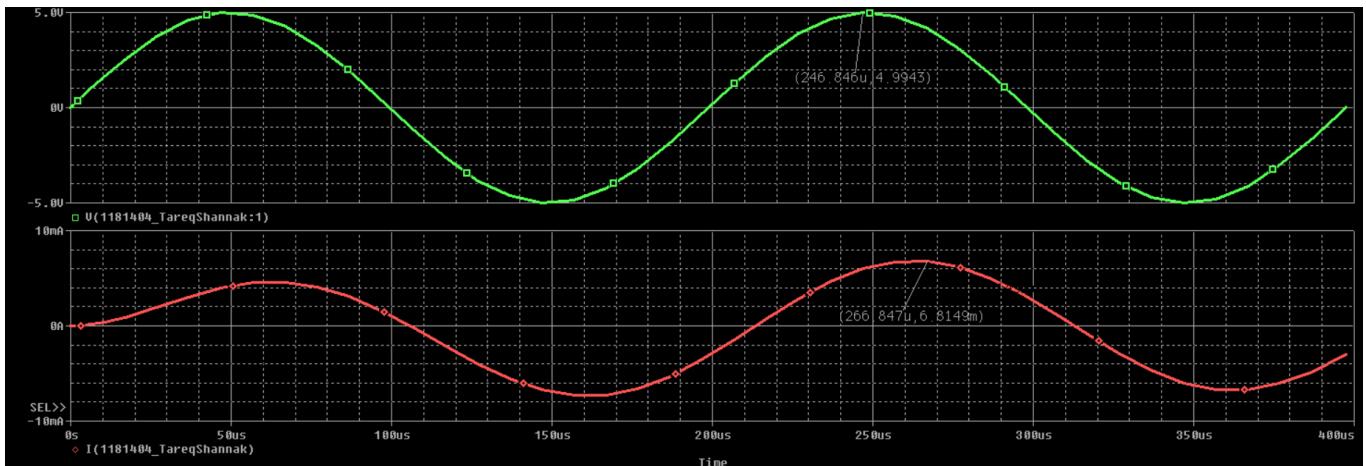When we add a capacitor with value 100nF in a parallel with the old one, the total capacitance = 200nF .



$$\text{From Graph: Phase Shift} = \frac{T_{\Delta pp} \times 360}{\text{Period}} = \frac{(266.847\mu - 246.846\mu) \times 360}{198.689\mu} = 36.24 \text{ degrees}$$



$$\begin{aligned} \text{From Theory: } X &= j2\pi fL + \frac{1}{j2\pi fc} = j2\pi(5.033k)(10m) - \frac{j}{2\pi(5.033k)(200n)} \\ &= j(316.233 - 158.111) = j 158.122 \end{aligned}$$

$$R = 330\Omega$$

$$\text{Phase Shift} = \tan^{-1} \frac{X}{R} = \tan^{-1} \frac{158.122}{330} = 25.6 \text{ degrees}$$

Where voltage leads the current by 25.6 degrees, so it's an inductive circuit.

Double the value of the inductor

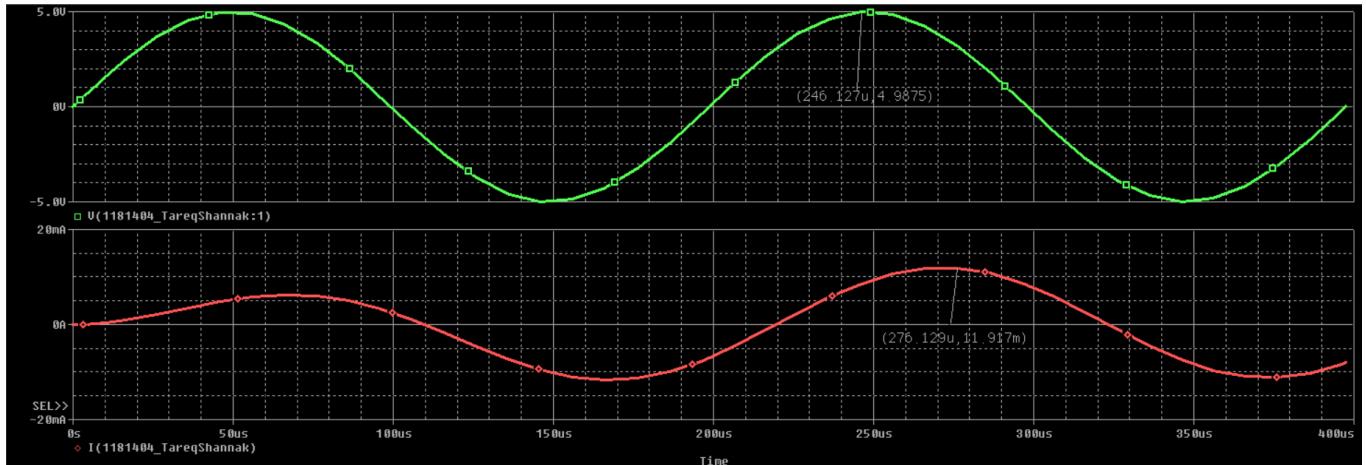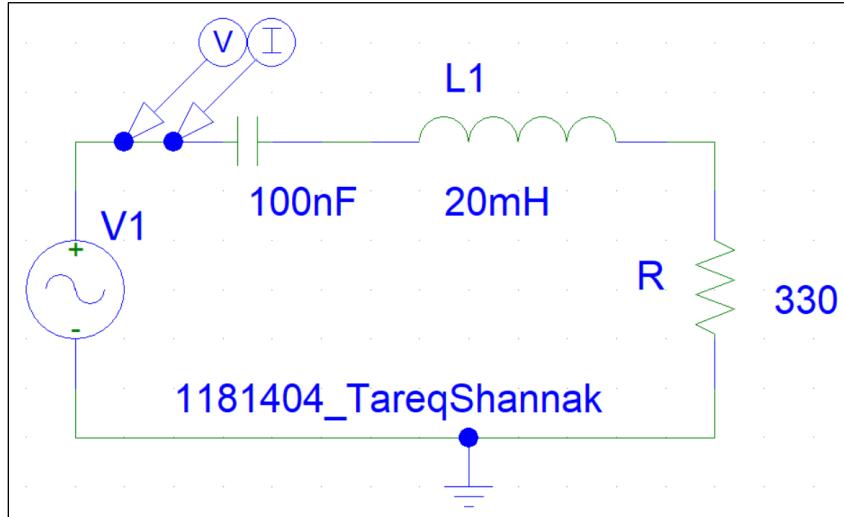

$$\text{From Graph: Phase Shift} = \frac{T_{\Delta pp} \times 360}{\text{Period}} = \frac{(276.129\mu - 246.127\mu) \times 360}{198.689\mu} = \mathbf{54.36 \text{ degrees}}$$

$$\begin{aligned} \text{From Theory: } X &= j2\pi fL + \frac{1}{j2\pi fc} = j2\pi(5.033k)(20m) - \frac{j}{2\pi(5.033k)(100n)} \\ &= j(632.466 - 316.233) = j 316.233 \end{aligned}$$

$$R = 330\Omega$$



$$\text{Phase Shift} = \tan^{-1} \frac{X}{R} = \tan^{-1} \frac{316.233}{330} = \mathbf{43.78 \text{ degrees}}$$

Where voltage leads the current by 43.78 degrees, so it's an inductive circuit.

X

Sinusoidal steady state power

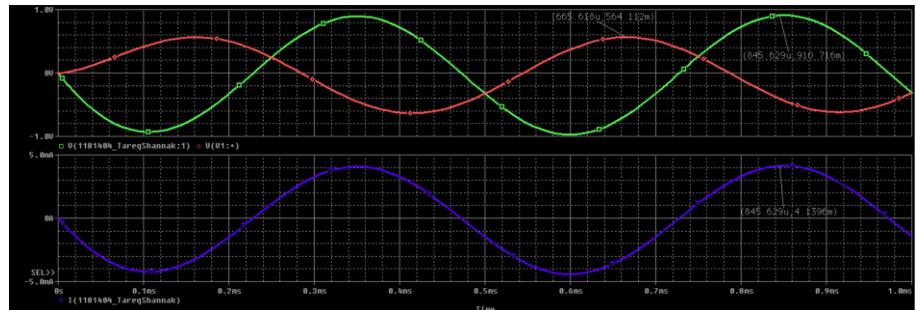
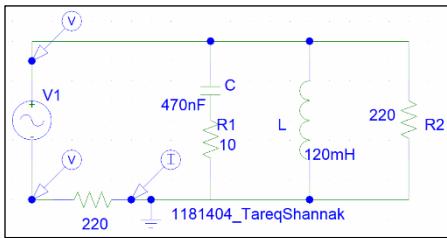
$$V_{RMS} = \frac{V_{Peak}}{\sqrt{2}} \rightarrow V_{Peak} = \sqrt{2} \times 1 = 1.4142v$$



$$V_s = 564.112m, I_s = 4.1396mA, V_{220\Omega} = 910.716mv$$

From Graph: Phase Shift = $\frac{T_{App} \times 360}{Period} = \frac{(845.629u - 845.629u) \times 360}{198.689u} = 0 \text{ degree}$

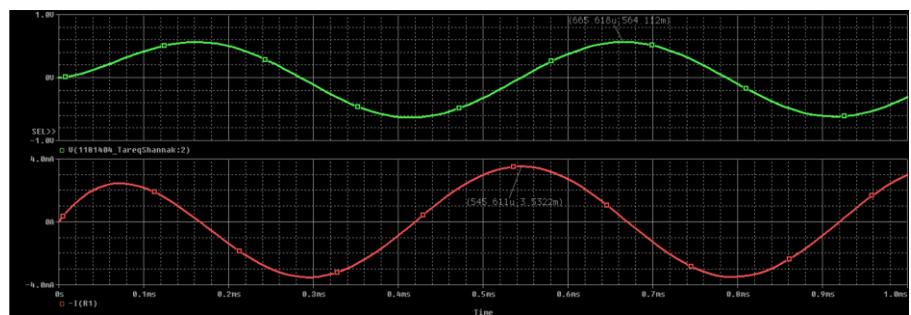
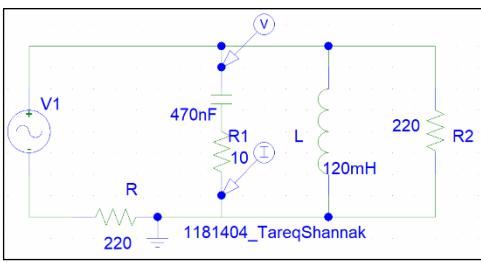
$$R = \frac{V_{220\Omega}}{I_s} = \frac{910.716mv}{4.1396mA} = 220\Omega$$



$$V_c = 564.112mv, I_c = 3.5322mA$$

From Graph: Phase Shift = $\frac{T_{App} \times 360}{Period} = \frac{(545.611u - 665.618u) \times 360}{198.689u} = -217.44 \text{ degrees}$

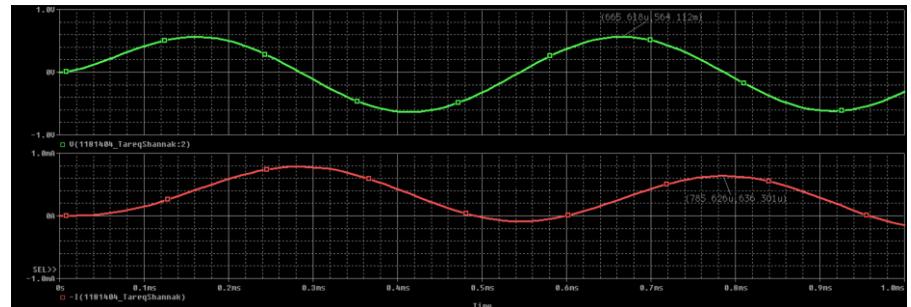
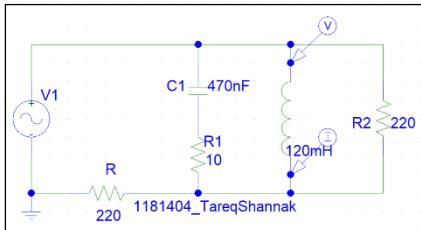
$$X = \frac{V_c}{I_c} = \frac{564.112mv}{3.5322mA} = \frac{1}{2\pi f c} + 10(3.5322mA) \rightarrow c = 499nF$$



$$V_L = 564.112mv, I_L = 636.301uA$$

From Graph: Phase Shift = $\frac{T_{\Delta pp} \times 360}{Period} = \frac{(785.626u - 665.618u) \times 360}{198.689u} = 217.44 \text{ degrees}$
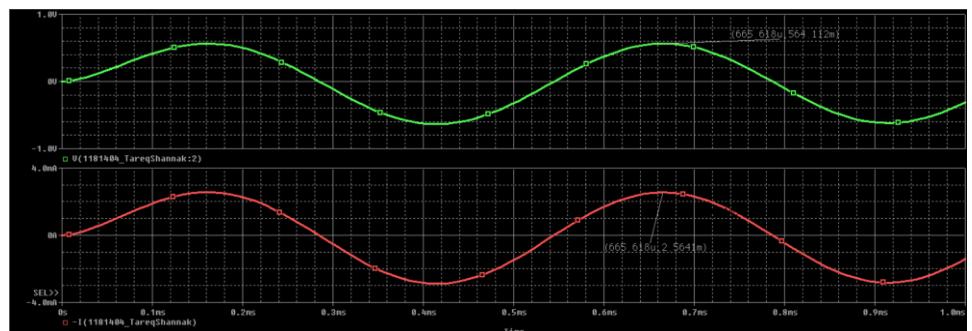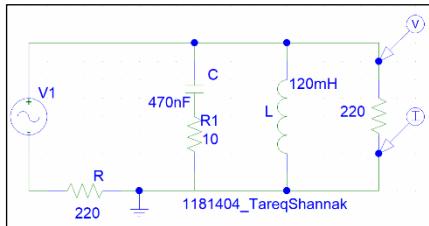
$$X = \frac{V_c}{I_c} = \frac{564.112mv}{636.301uA} = 2\pi f l \rightarrow l = 70mH$$



$$V_L = 564.112mv, I_L = 2.5641mA$$

From Graph: Phase Shift = $\frac{T_{\Delta pp} \times 360}{Period} = \frac{(665.618u - 665.618u) \times 360}{198.689u} = 0 \text{ degree}$

$$R = \frac{V_{220\Omega}}{I_s} = \frac{564.112mv}{2.5641mA} = 220\Omega$$

	V	I	Practical Value	Phase Shift
S	564.112mv	4.1396mA	-	0
C	564.112mv	3.5322mA	499nF	-217.44
L	564.112mv	636.301uA	70mH	217.44
R	564.112mv	2.5641mA	220Ω	0
$R_{220\Omega}$	910.716mv			