



Faculty of Engineering & Technology  
Electrical & Computer Engineering Department

**ENEE2103**

**PreLab#04**

**Filters**

---

**Prepared by : Tareq Shannak**

**ID Number : 1181404**

**Instructor : Dr. Alhareth Zyoud**


**Teaching Assistant : Mahdi Salem**

**Section : 5**

**Date : 21/3/2021**


## Passive Filters

### First Order Circuits

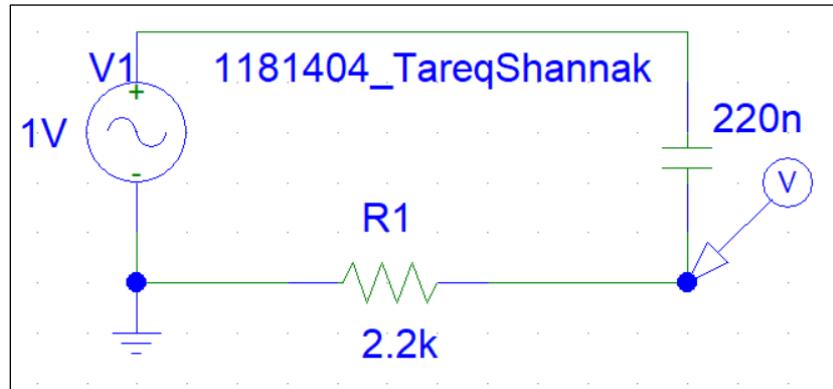


$$\text{From Theory: } f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(2.2k)(220n)} \text{ HZ} \cong 328.833 \text{ HZ}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = v_{out} = \text{magnitude of } v_c + v_l = \text{magnitude of } v_r \rightarrow v_{out} = 0 \text{ db}$$

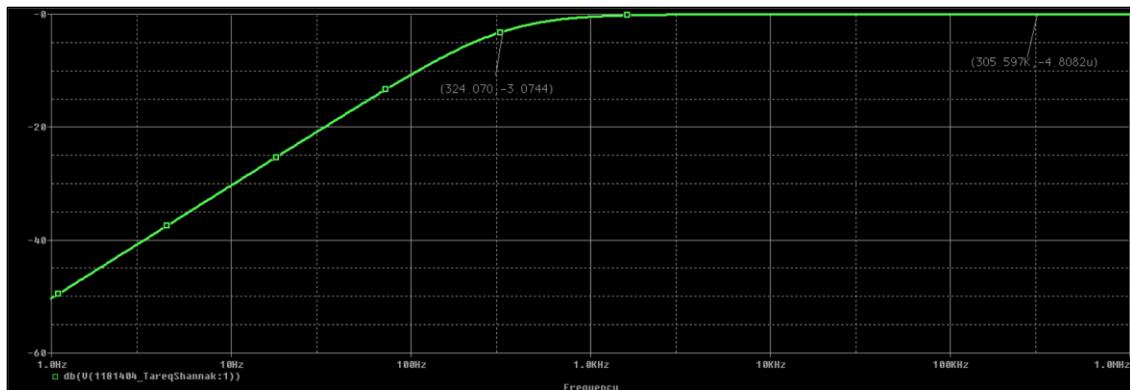


From Graph: magnitude of  $v_r = -4.8082u \text{ db}$

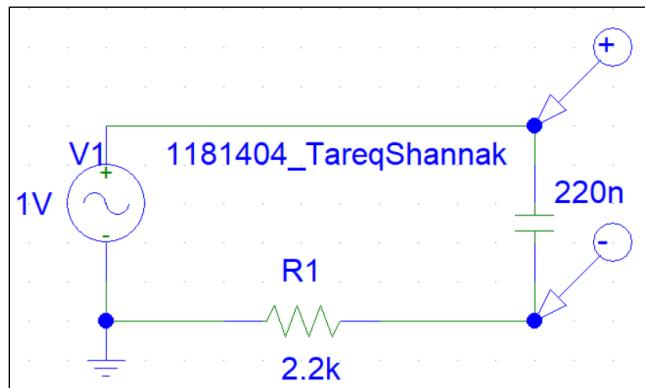
When  $v = (-4.8082u - 3) \text{ db} \approx -3 \text{ db}$ ,  $f_c \cong 324.070 \text{ HZ}$ , High Pass Filter



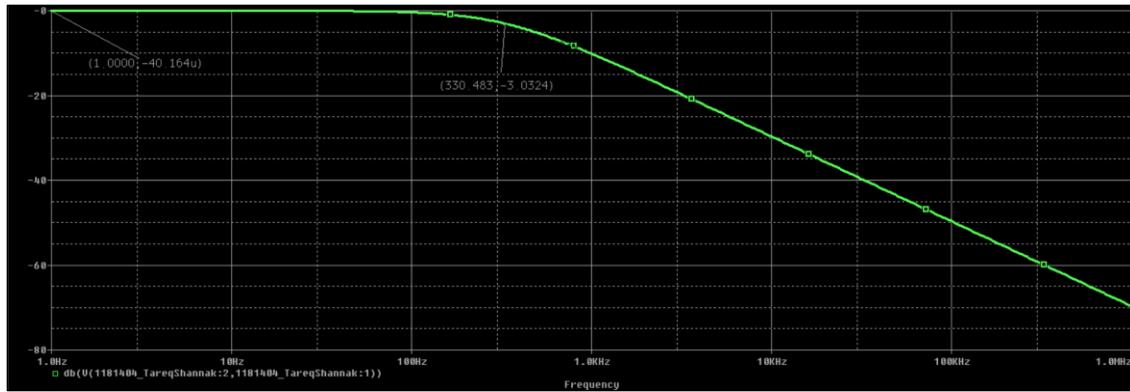
$$\text{From Theory: } f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(2.2k)(220n)} \text{ HZ} \cong 328.833 \text{ HZ}$$



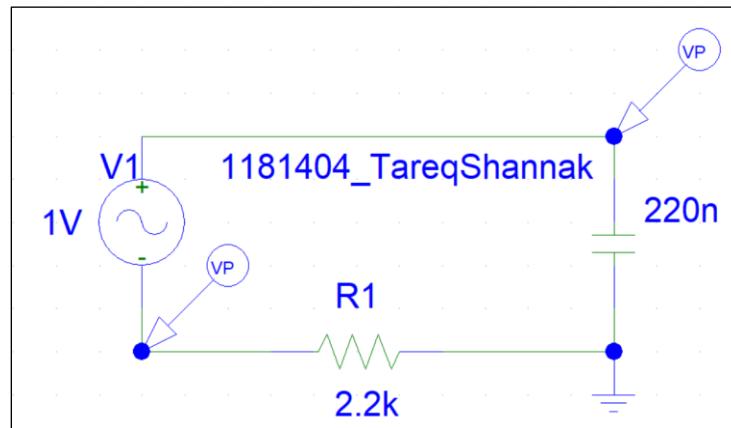From Graph: magnitude of  $v_c = -40.164u \text{ db}$   
When  $v = (40.164u - 3)\text{db} \approx -3\text{db}, f_c \cong 330.483 \text{ HZ, Low Pass Filter}$


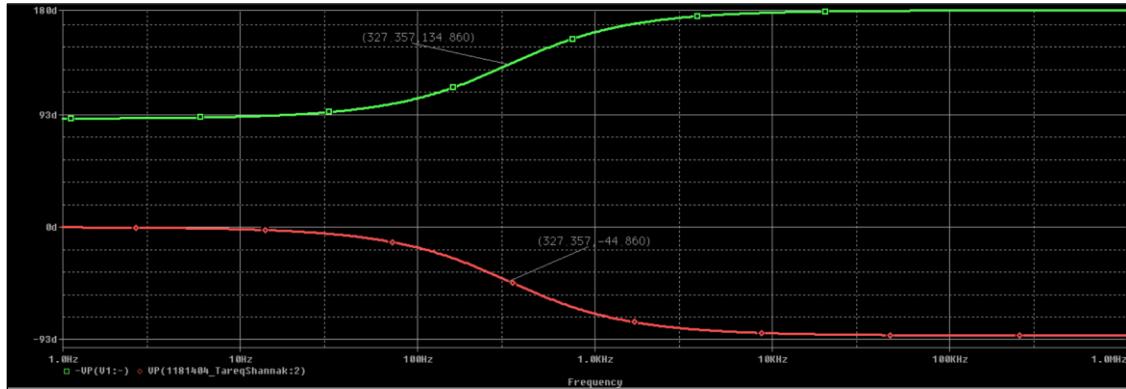
$$\varphi_c = -\tan^{-1} 2\pi f RC = -\tan^{-1} 2\pi(328.833)(2200)(220n) = -\tan^{-1} 1 = -45 \text{ degrees}$$




From Graph:  $\varphi_r \text{ when } f=f_c, \varphi = 135 \text{ degrees} = -45 \text{ in } \tan \varphi$

$\varphi_c \text{ when } f=f_c, \varphi = -45 \text{ degrees}$

## Second Order Circuits

### Band Pass Filter

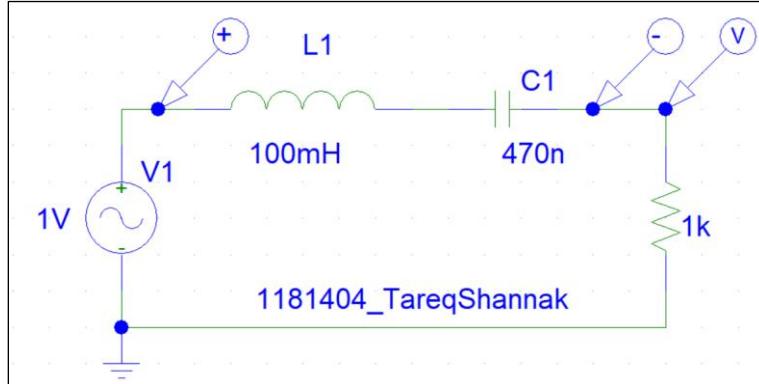


$$\text{From Theory: } f_c = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(100\text{m})(470\text{n})}} \text{ HZ} \cong 734.127 \text{ HZ}$$

$$f_{c1} = \frac{1}{2\pi} \left( \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} - \frac{R}{2L} \right) = \frac{1}{2\pi} \left( \sqrt{(5000)^2 + \frac{1}{(0.1)(470\text{n})}} - 5000 \right) \text{ HZ} \cong 286.907 \text{ HZ}$$

$$f_{c2} = \frac{1}{2\pi} \left( \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} + \frac{R}{2L} \right) = \frac{1}{2\pi} \left( \sqrt{(5000)^2 + \frac{1}{(0.1)(470\text{n})}} + 5000 \right) \text{ HZ} \cong 1878.457 \text{ HZ}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = v_{out} = \text{magnitude of } v_c + v_l = \text{magnitude of } v_r \rightarrow v_{out} = 0\text{db}$$

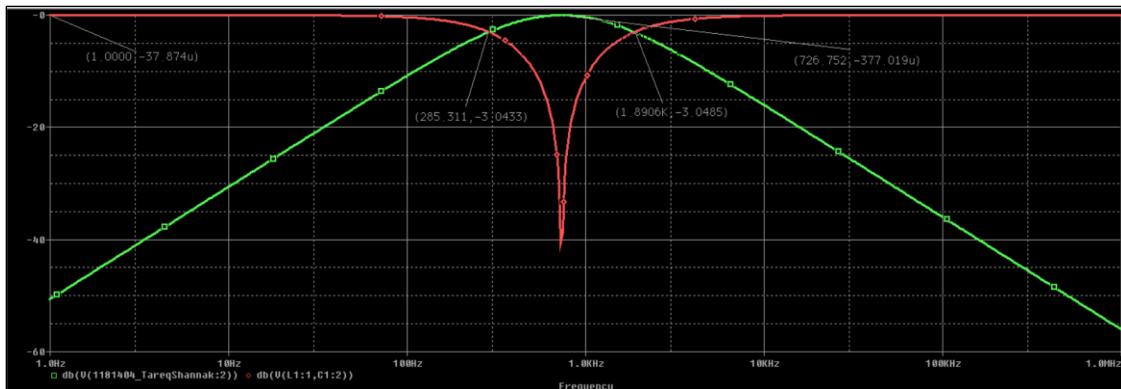

From Red Graph: For  $v_c + v_l$ , magnitude =  $-37.874u$  db


When  $v = (-37.874u - 3)$  db  $\approx -3$  db,  $f_c \cong 726.752 \text{ HZ}$ ,  $f_{c1} \cong 285.311\text{HZ}$ ,  $f_{c2} \cong 1890.6 \text{ HZ}$

### Band Pass Filter

From Green Graph: For  $v_r$ , magnitude =  $-377.019u$  db

When  $v = (-377.019u - 3)$  db  $\approx -3$  db,  $f_c \cong 726.752 \text{ HZ}$ ,  $f_{c1} \cong 285.311\text{HZ}$ ,  $f_{c2} \cong 1890.6 \text{ HZ}$


### Band Reject Filter

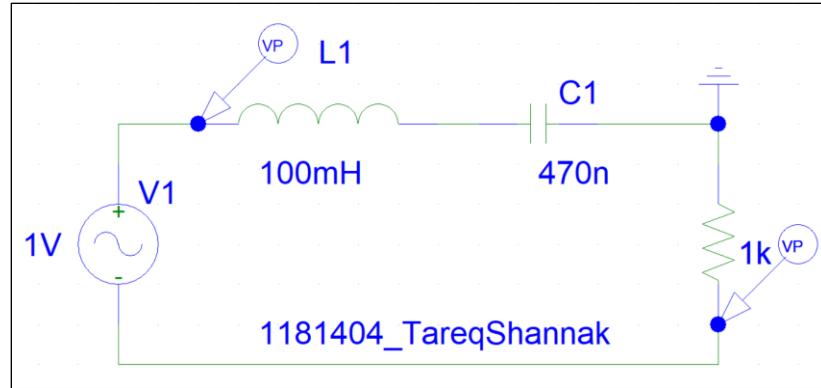

$$\varphi_c = -\tan^{-1} \left( \frac{\frac{1}{LC} - (2\pi f_c)^2}{\frac{2\pi f_c R}{L}} \right) = -\tan^{-1} \left( \frac{\frac{1}{(0.1)(470n)} - (2\pi(734.127))^2}{\frac{2\pi(734.127)(1000)}{(0.1)}} \right) = 0 \text{ degree}$$

$$\varphi_{c1} = -\tan^{-1} \left( \frac{\frac{1}{LC} - (2\pi f_{c1})^2}{\frac{2\pi f_{c1} R}{L}} \right) = -\tan^{-1} \left( \frac{\frac{1}{(0.1)(470n)} - (2\pi(286.907))^2}{\frac{2\pi(286.907)(1000)}{(0.1)}} \right) = -45 \text{ degrees}$$
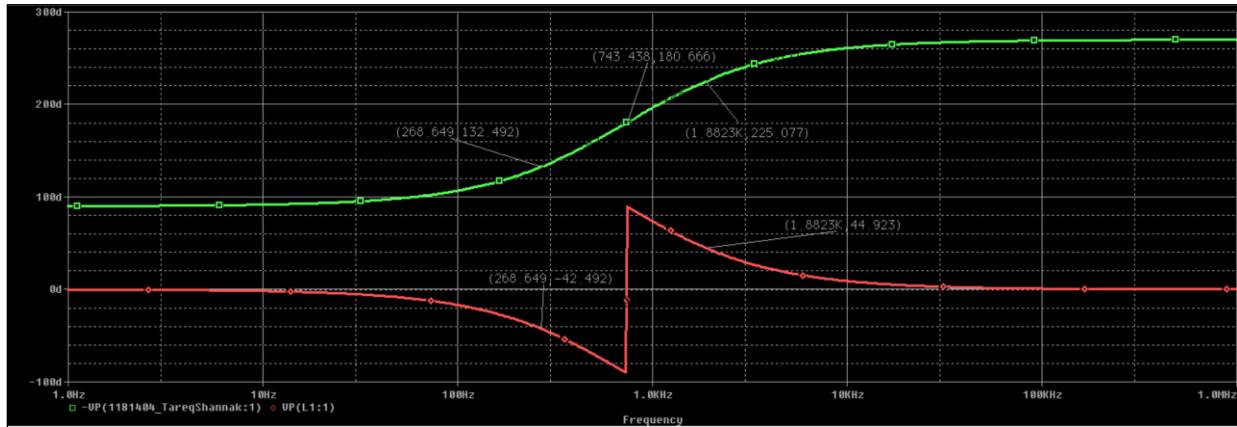
$$\varphi_{c2} = -\tan^{-1} \left( \frac{\frac{1}{LC} - (2\pi f_{c2})^2}{\frac{2\pi f_{c2} R}{L}} \right) = -\tan^{-1} \left( \frac{\frac{1}{(0.1)(470n)} - (2\pi(1878.457))^2}{\frac{2\pi(1878.457)(1000)}{(0.1)}} \right) = 45 \text{ degrees}$$



From Green Graph:  $\varphi_{\text{when } f=f_c} = 180 \text{ degrees} = 0 \text{ in } \tan \varphi$ ,

$\varphi_{\text{when } f=f_{c1}} = 132 \text{ degrees} = -48 \text{ in } \tan \varphi$ ,


$\varphi_{\text{when } f=f_{c2}} = 225 \text{ degrees} = 45 \text{ in } \tan \varphi$

From Red Graph:  $\varphi_{\text{when } f=f_c} = 0 \text{ degree}$ ,

$\varphi_{\text{when } f=f_{c1}} = -42.492 \text{ degrees}$ ,  $\varphi_{\text{when } f=f_{c2}} = 44.932 \text{ degrees}$

## Active Filters

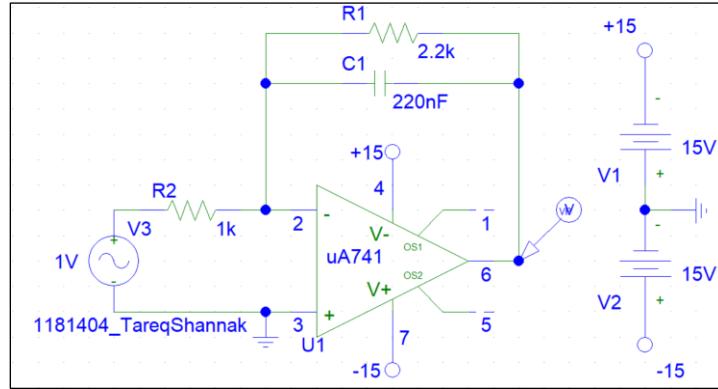
### Simplified Inverting Amplifier Filter



$$From\ Theory: f_c = \frac{1}{2\pi R_1 C} = \frac{1}{2\pi(2.2k)(220n)} = 328.833\ Hz$$

$$v_o = \left| \frac{v_{out}}{v_{in}} \right| = \left| \frac{-\frac{R_1}{R_2} v_{in}}{v_{in}} \right| = \frac{R_1}{R_2} = \frac{2.2k}{1k} = 2.2v = 20 \log 2.2 \text{ db} = 6.8485 \text{ db}$$
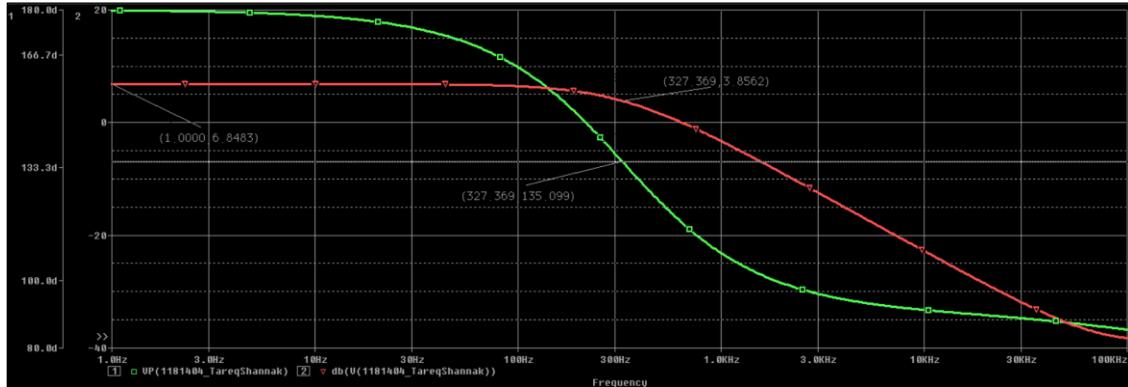
$$\varphi_c = -\tan^{-1} 2\pi f RC = -\tan^{-1} 2\pi(328.833)(2200)(220n) = -\tan^{-1} 1 = -45 \text{ degrees}$$



From Graph: For  $v_o$ , magnitude = 6.8483 db

When  $v = (6.8483 - 3) \text{ db} \approx 3.8483 \text{ db}$ ,  $f_c \cong 327.369 \text{ Hz}$ , Low Pass Filter

$\varphi_{\text{when } f=f_c} = 135.009 \text{ degrees} \approx 135 \text{ degrees} = -45 \text{ in } \tan \varphi$