

Experiment #5 Prelab Procedure**ENEE2103****Filters****Pre-lab Work:**

1. Simulate the given circuits using ac sweep analysis, plot the Magnitude, and phase frequency response.
2. Compare the cutoff frequencies obtained from simulation with those computed theoretically.

Procedure:**A. Passive filters:****I. First order circuits:**

1. Simulate the circuit of Fig (5.1) using **ac sweep ANALYSIS**.
2. **The voltage source must be replaced with an ac source Vac with magnitude =1V**

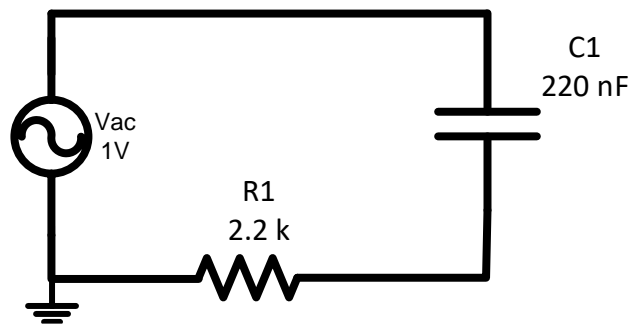


Fig (5.1)

3. Perform **ac sweep/ decade type** with suitable range of frequencies from 1Hz-1MHz
 4. Plot magnitude of V_{R1} in decibels: i.e. : db(V_{R1})
 5. Plot magnitude of V_{C1} note that this is differential voltage across C1 in decibels
- From 5 and 6 indicate location and value of cutoff frequency f_c**
6. Plot phase of V_R and V_c in degrees: i.e. : p(V_R) and p(V_c).

II. Second Order Filters:

1. Simulate the circuit of Fig (5.2) using ac sweep.
2. The voltage source must be replaced with an ac source V_{ac} with magnitude =1V, make sure to add a ground reference connection in the circuit

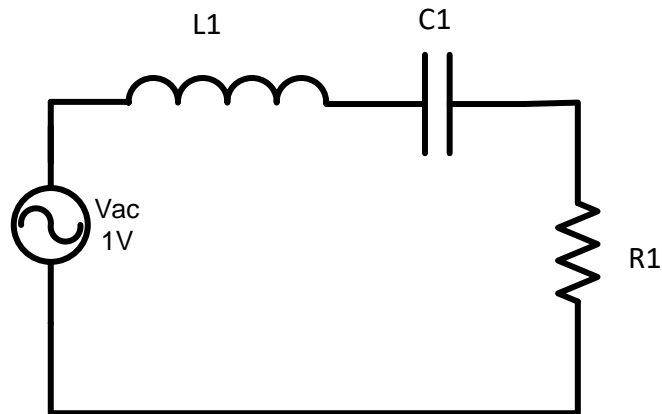


Fig (5.2)

3. Perform ac sweep/ decade type from 1Hz to 1MHz
4. Plot magnitude of V_R and (V_C+V_L) in decibels.
5. Plot phase of V_R and (V_C+V_L)
6. From the magnitude-frequency plots of (V_R/V_i) and $((V_C + V_L)/V_i)$ determine the filter type in each case.
7. From the plots of step 6. Determine approximately the 3db cut-off frequency in each of the two cases.

B. Active filters:

1. Simulate Circuit of Fig. 5.3

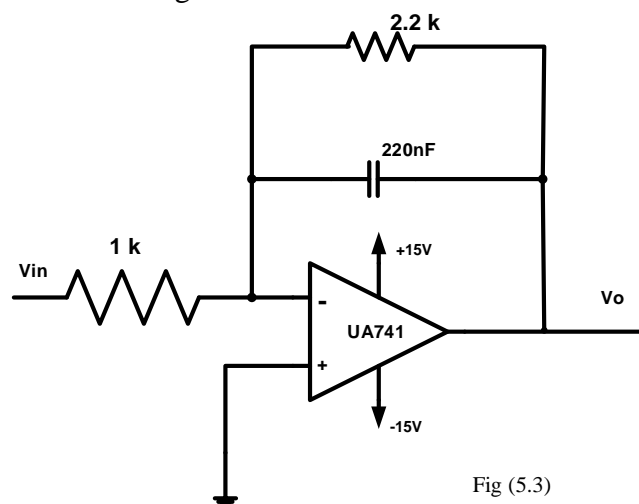


Fig (5.3)

2. Make sure to connect +15 V bias source to V+ terminal and -15 V to V- terminal.
3. Perform ac sweep/ decade type with range of frequencies from 1Hz-100kHz
4. Plot magnitude of V_o in decibels.
5. Plot phase of V_o .
6. From the magnitude-frequency plot, determine the filter type.
7. From the plots of step 6. Determine approximately the 3db cut-off frequency.
8. Compare theoretical and simulation values of f_c