



**Faculty of Information Technology**  
**Electrical and Computer Engineering Department**  
**CIRCUITS AND ELECTRONICS LABORATORY (ENEE2103)**

**Prelab Experiment#5**  
**“Filters”**

**Instructor: Dr. Wael Hashlamoun**

**Teacher: Eng. Mostafa Helal**

**Student Name: Mays Sbaih**


**Student Number:1160006**

**Section 3**


**Due to:11-3-2019**

## A. Passive filters:

### I. First order circuits:

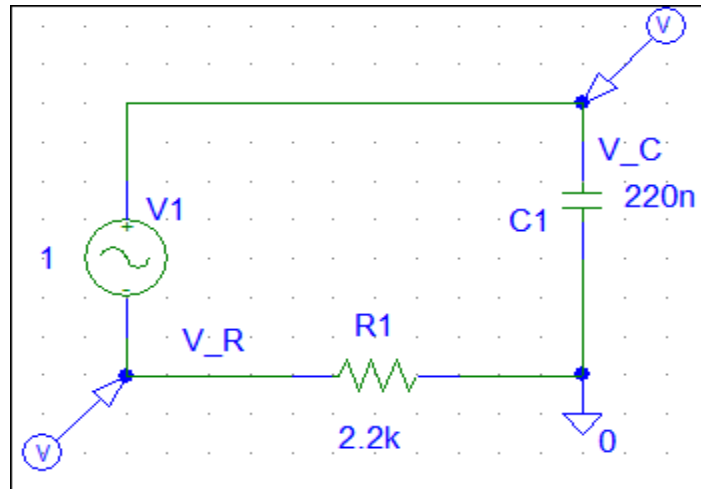

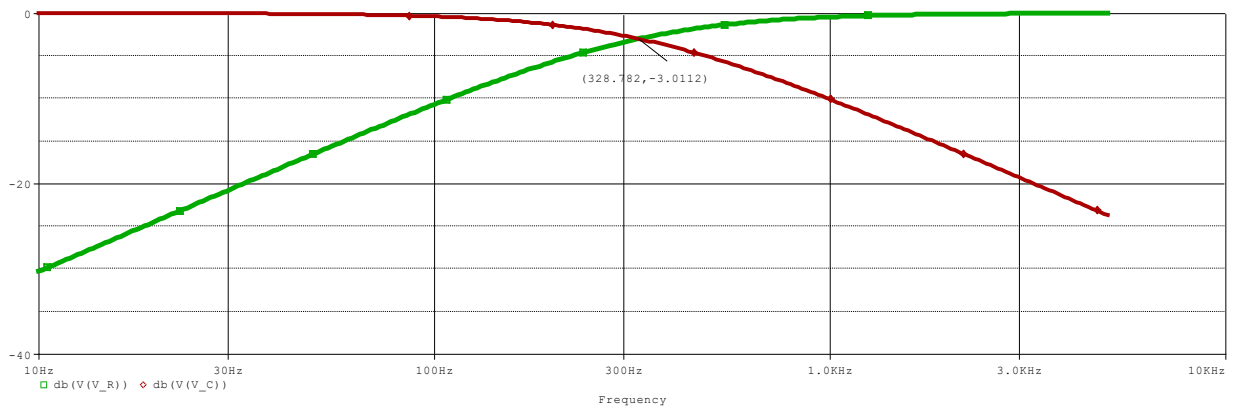
- Magnitude of  $V_R$  and  $V_C$  in decibels:




➤ From the above plot, 3db cut-off frequency  $\approx 328.782$  Hz.

Theoretically, 3db cut-off frequency =  $1 / (2\pi RC) = 1 / (2\pi * 2.2k * 220n) = 328.833$  Hz.

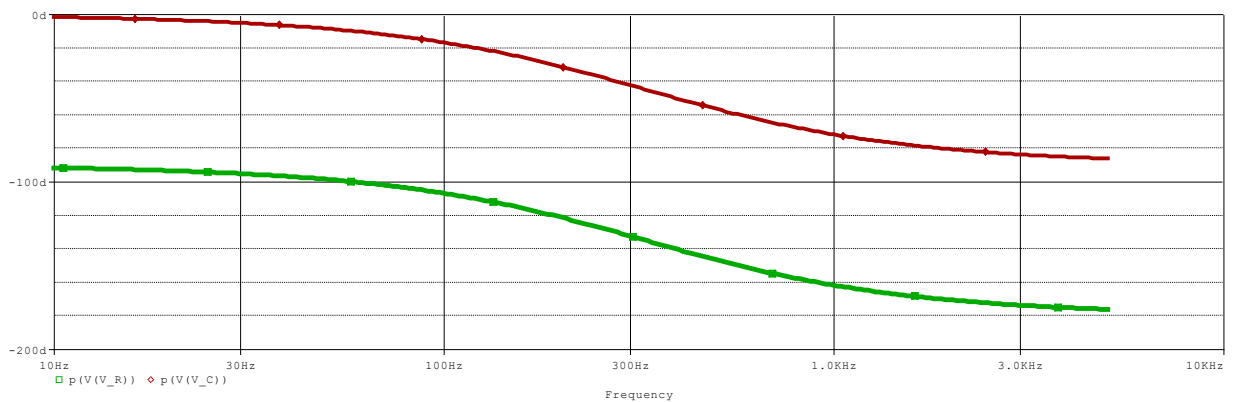
- Phase of  $V_R$  and  $V_C$  in decibels:




## II. Second Order Filters:

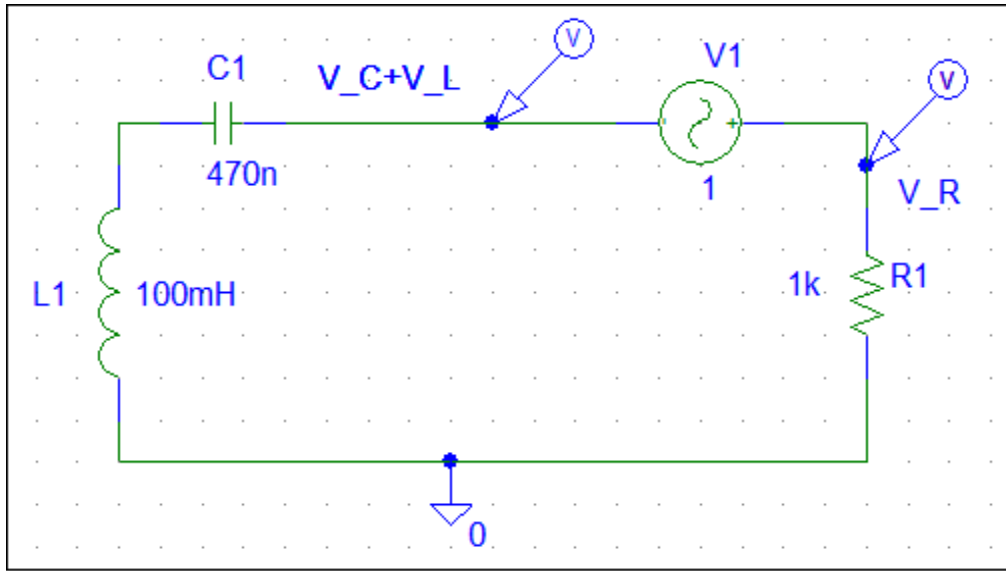

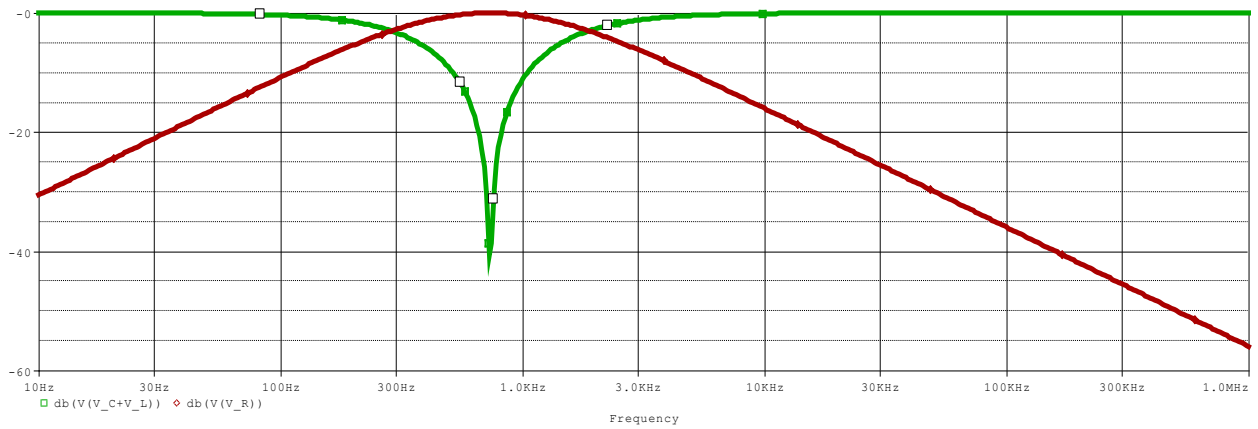
- Magnitude of  $V_R$  and  $(V_C + V_L)$  in decibels.



- Phase of  $V_R$  and  $(V_C + V_L)$ .

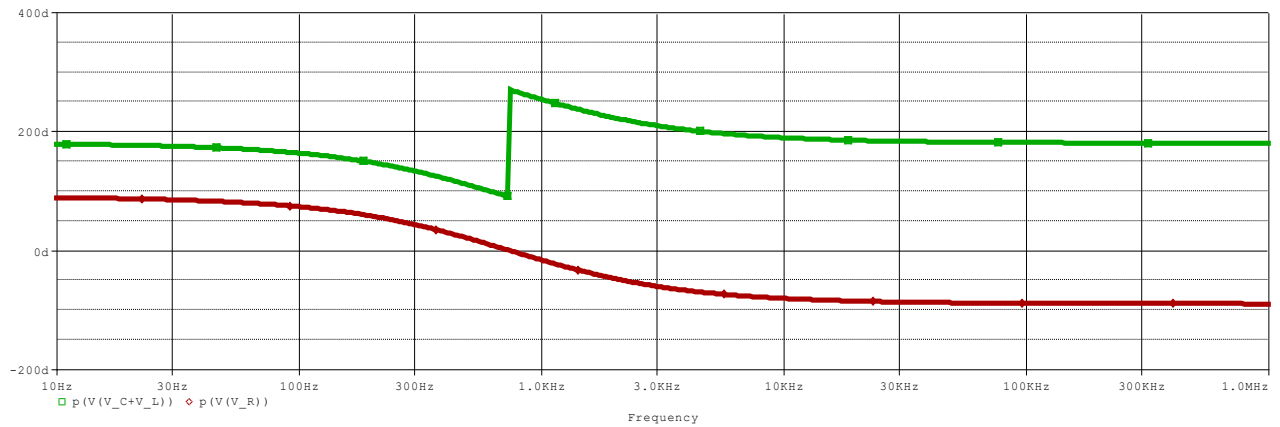


• Plot of  $(V_R/V_I)$ .

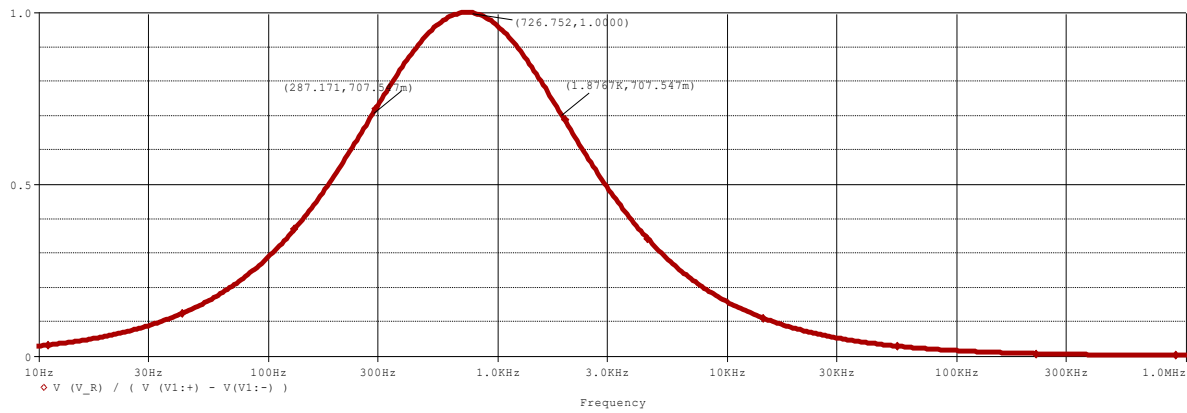

From plot above:

- Filter type is band-pass filter.
- $f_{c1} = 287.171$  Hz
- $f_{c2} = 1876.7$  Hz
- $f_o = 726.752$  Hz.


• Plot of  $((V_C + V_L)/ V_i)$ .

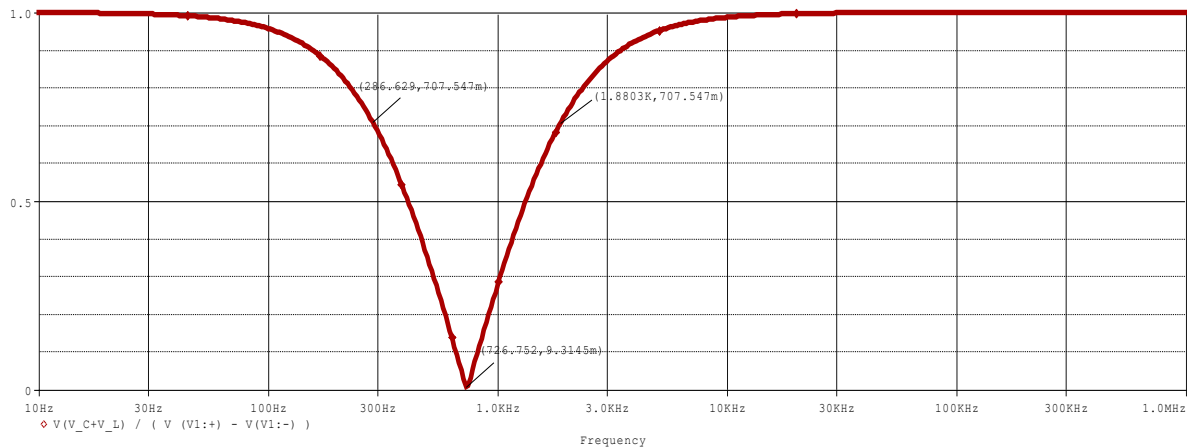

From plot above:

- Filter type is band-reject filter.
- $f_{c1} = 286.629$  Hz
- $f_{c2} = 1880.3$  Hz
- $f_o = 726.752$  Hz.

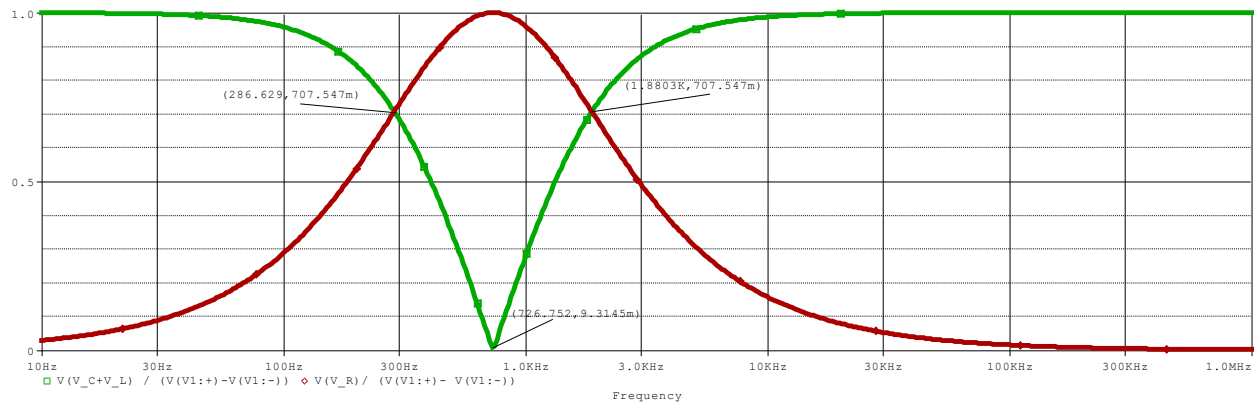- Both plots of  $(V_R / V_i)$  and  $((V_C + V_L) / V_i)$ .




- Theoretically:

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{100 \text{ mH} \times 470 \text{ nF}}} = 734.13 \text{ Hz.}$$


$$f_{c1} = \frac{-\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}}{2\pi} = 286.907 \text{ Hz.}$$

$$f_{c2} = \frac{\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}}{2\pi} = 1878.456 \text{ Hz.}$$


**B. Passive filters:**

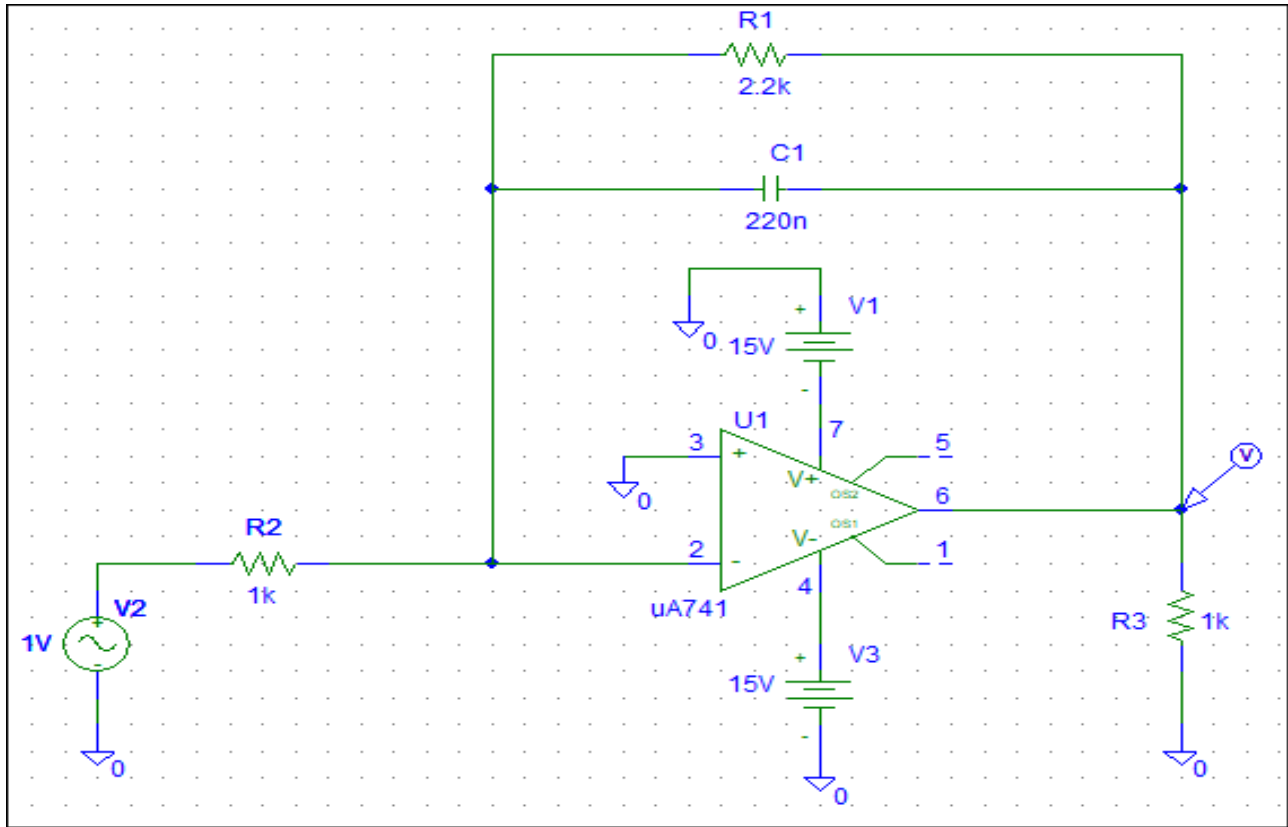


- Magnitude of  $V_o$  in decibels.

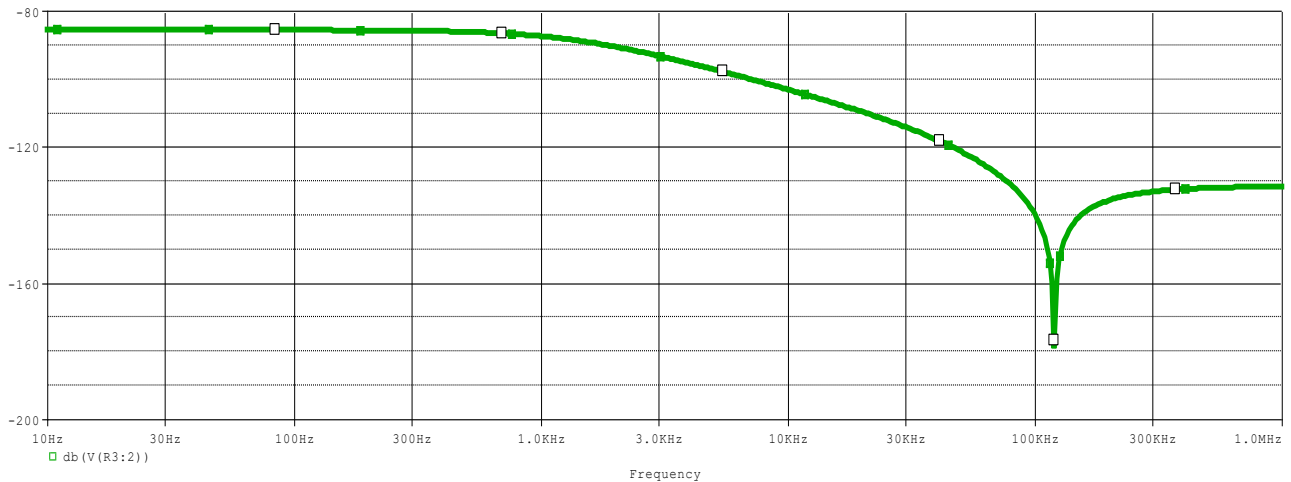

- Phase of Vo.

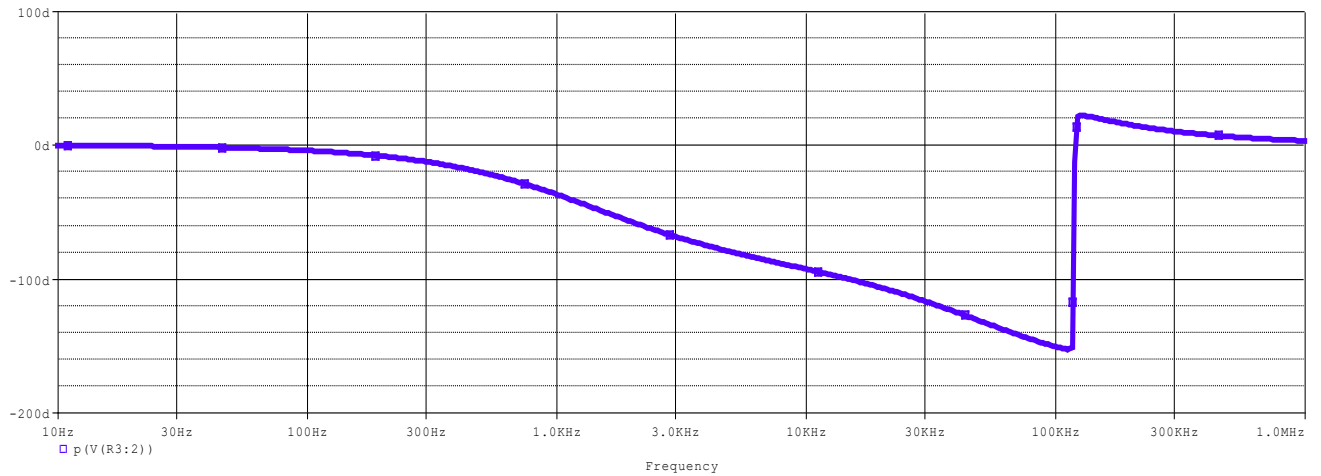

- Magnitude-frequency Plot.

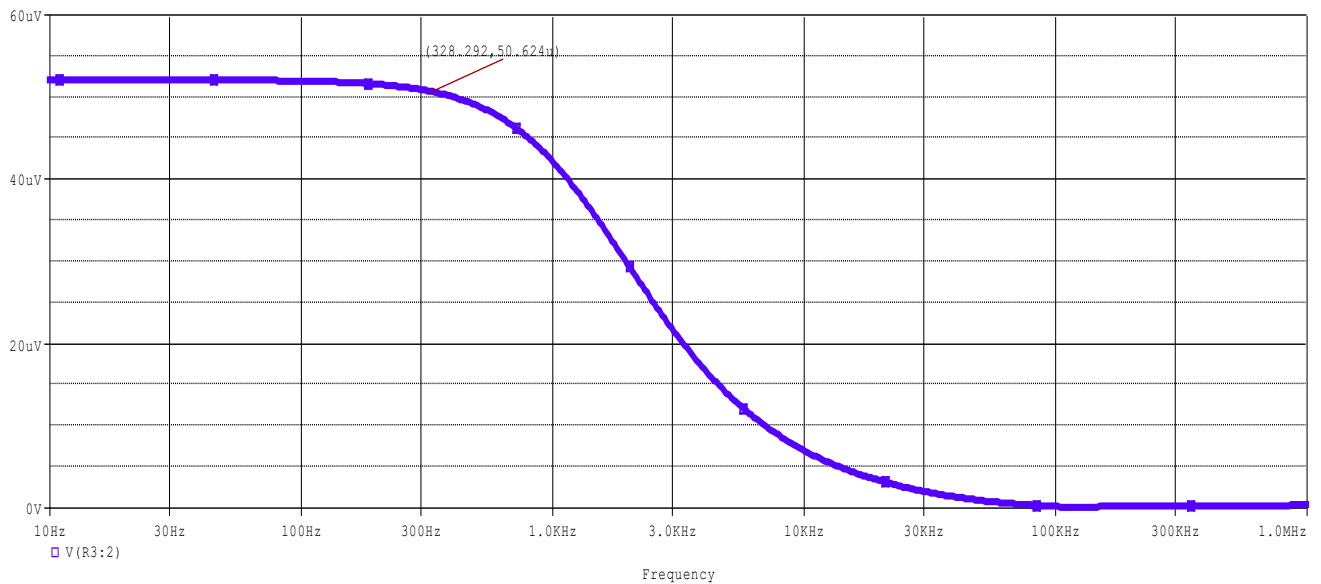

- o From plot above:

- Filter type is low-pass filter.
- 3db cut-off ( $f_c$ )= 328.292 Hz.

- o Theoretically:

$f_c = 1/2\pi RC = 328.833\text{Hz}.$