



Faculty of Engineering & Technology
Electrical & Computer Engineering Department

ENEE2103

PreLab#06

BJT Transistor As an Amplifier, CE, CC, CB Connection

Prepared by : Tareq Shannak

ID Number : 1181404

Instructor : Dr. Alhareth Zyoud


Teaching Assistant : Mahdi Salem

Section : 5

Date : 7/4/2021

Part One

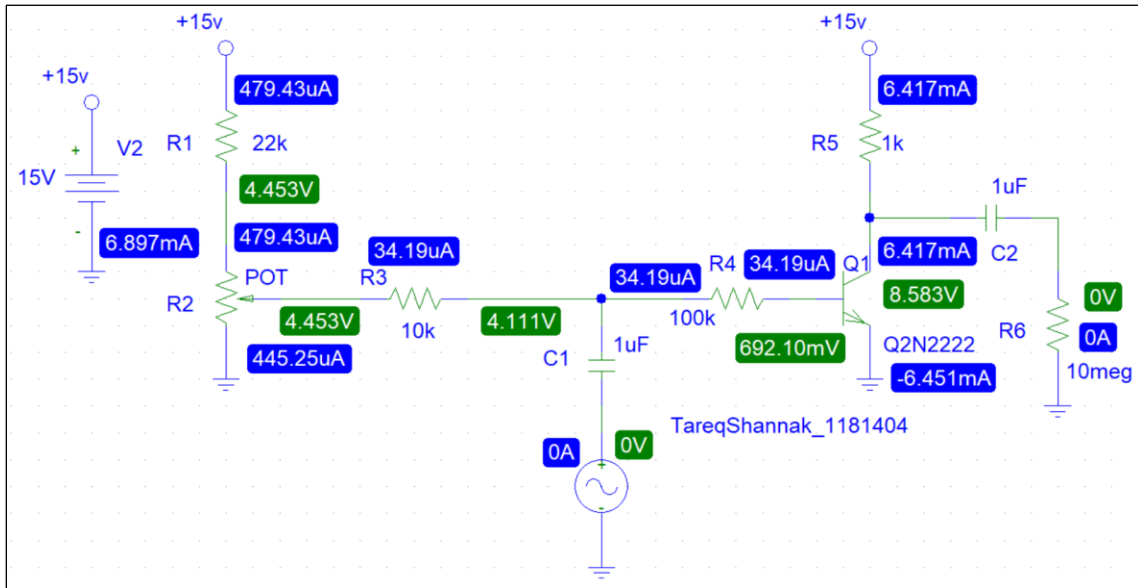
Initially set $V_i(t)$ amplitude to 0, set the potentiometer value to 10 k and its set value to 0. Set sinusoidal source to 1 kHz and amplitude to zero.



Measure V_C , V_{BE} , V_{CE} , I_C , I_B

V_C	8.583 V
V_{BE}	692.1 mV
V_{CE}	8.583 V
I_C	6.417 mA
I_B	34.19 μA

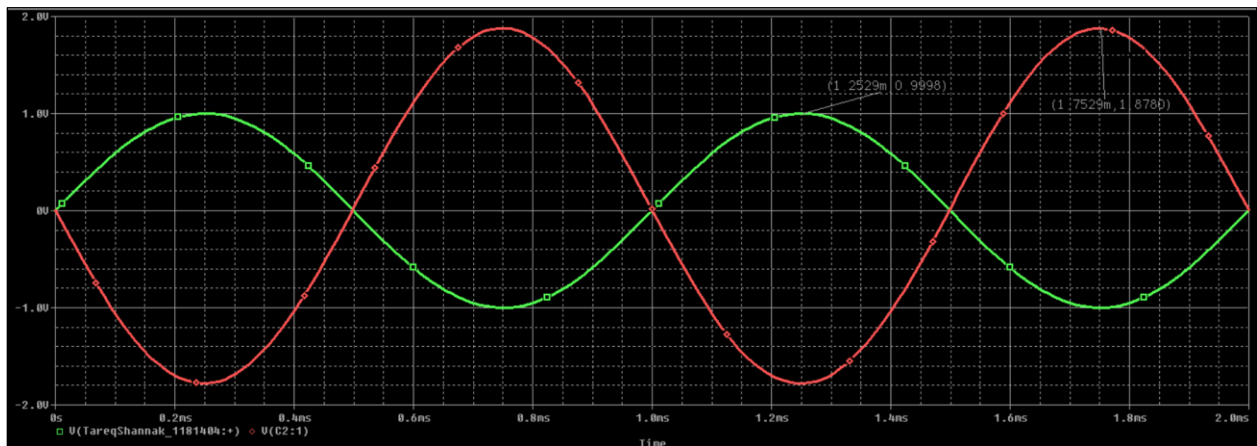Adjust amplitude of $V_i(t)$ to 1 V and measure $V_o(t)$




$$V_o(t) = 1.878 \text{ V}, \text{ Voltage Gain } A_V = \frac{1.878}{0.9998} = 1.8784$$

Change peak of $V_i(t)$ such that $V_o(t) = 4V$

$$\text{Voltage Gain } A_V = 1.8784 \rightarrow 1.8784 = \frac{V_o(t)}{V_i(t)}$$

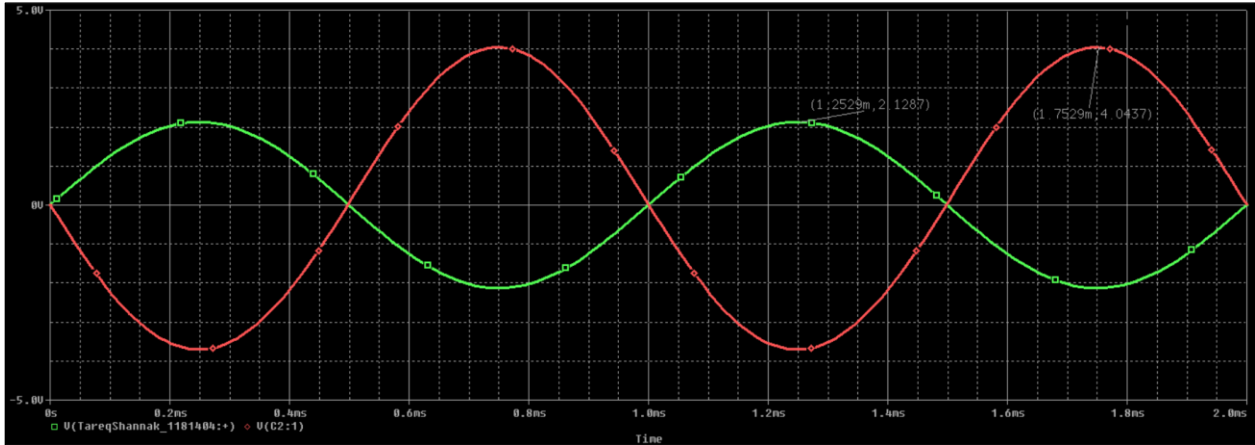
$$\rightarrow V_i(t) = \frac{4}{1.8784} V = 2.129 V$$



Calculate the voltage gain of the transistor


$$\text{Voltage Gain } A_V = \frac{1.878}{0.9998} = 1.8784$$

Calculate $A_{V1} = V_o(t) / V_B(t)$

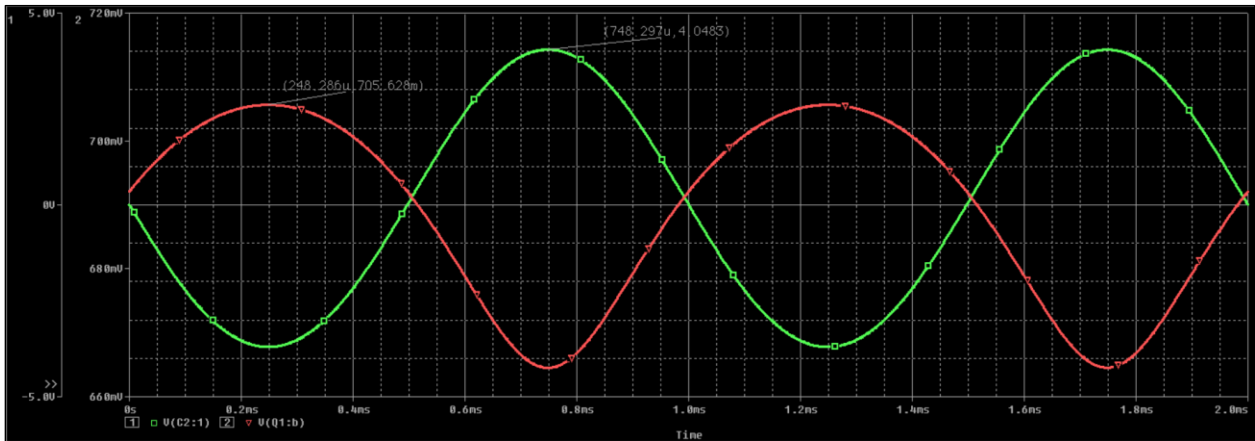


$$A_{V1} = \frac{V_o(t)}{V_B(t)} = \frac{4.0483}{705.628m} = 5.737$$

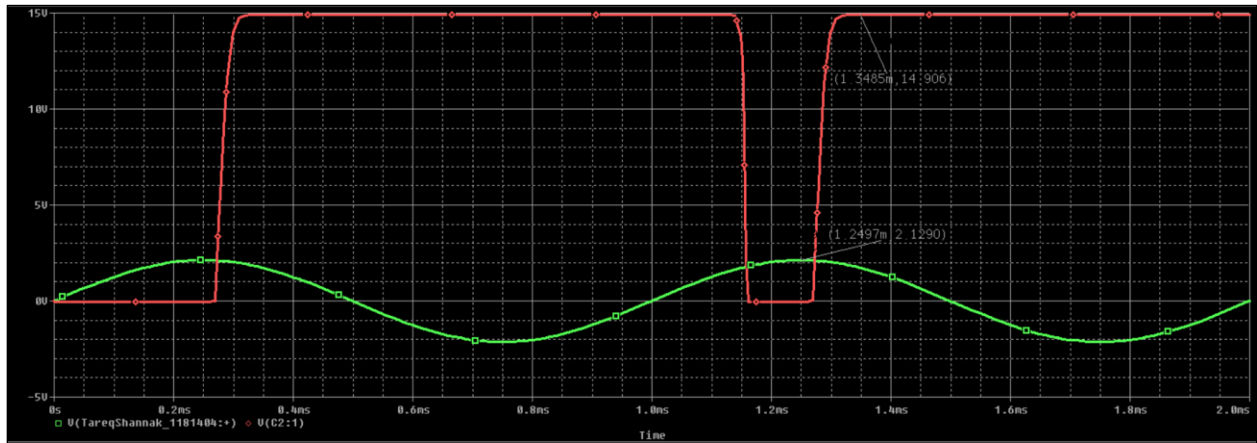Remove the 100k resistor and see what happens to voltage gain



$$A_V = \frac{V_O}{V_i} = \frac{14.906}{2.129} \approx 7$$

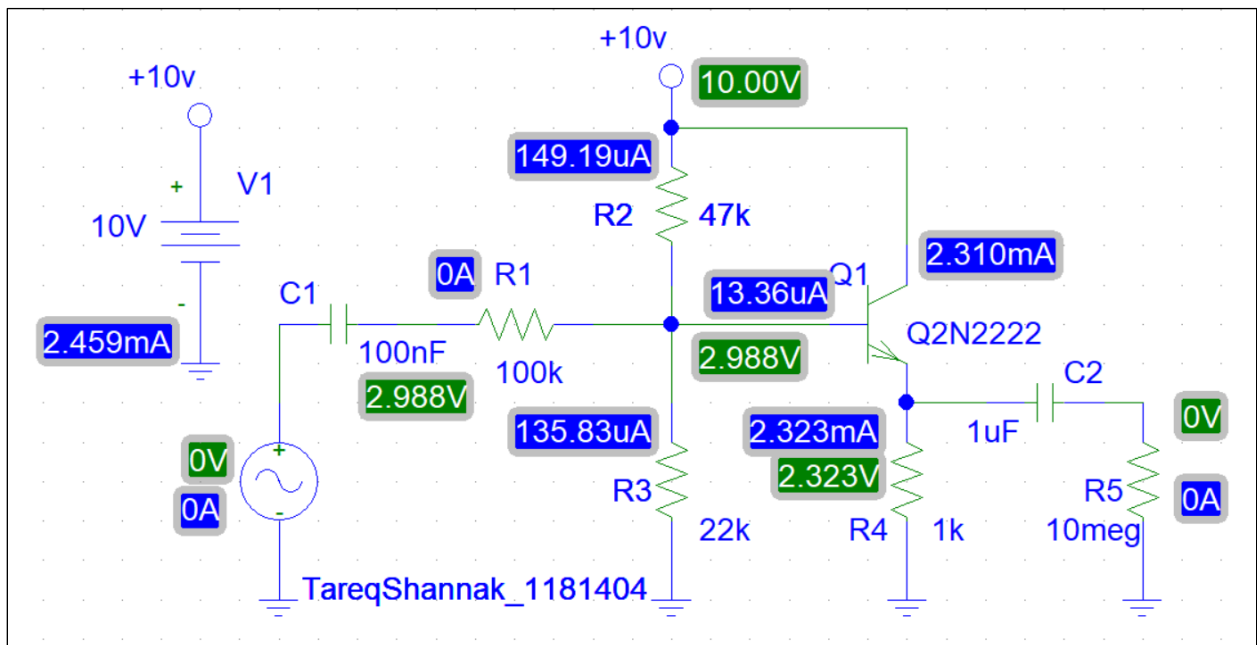Part Two: Common Collector Transistor Amplifier




Measure V_B , V_C , I_B , I_C

V_B	2.988 V
V_C	10 V
I_B	13.36 μ A
I_C	2.31 mA


Adjust the amplitude of the sine wave generator until an output amplitude from the amplifier is about 2 volts peak-to-peak. (Make sure the waveform is undistorted).

$$\text{Let } V_{in} = 5 \text{ V} \rightarrow V_{out} = 594.77 \text{ mV}$$
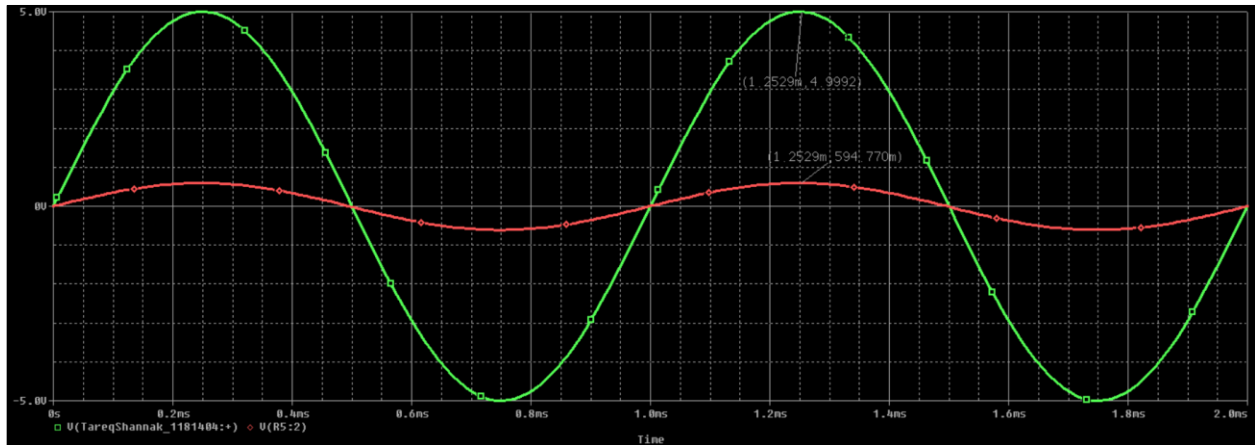
$$A_V = \frac{594.77 \text{ m}}{4.9992} = 0.119$$


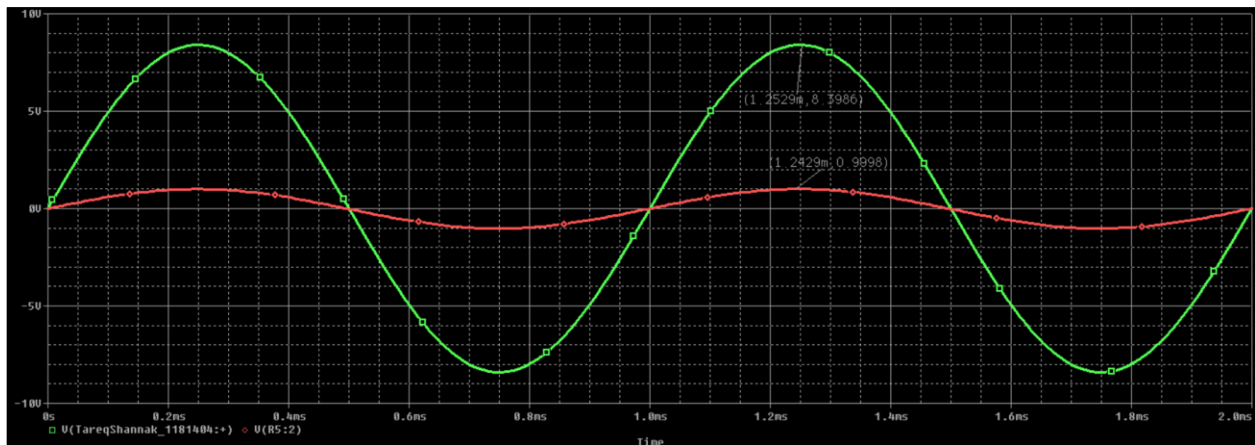
$$\text{If we need } V_{out} = 1, V_{in} = \frac{V_{out}}{A_V} = \frac{1}{0.119} \approx 8.4 \text{ V}$$



$$V_{out} = 0.9998 \text{ V} \approx 1 \text{ V} \rightarrow V_{out} = 2 \text{ V peak to peak}$$


Measure the ac input voltage needed to achieve this output

$$V_{in} \approx 8.4 \text{ V}$$

Calculate the voltage gain A_V

$$A_V = 0.119$$

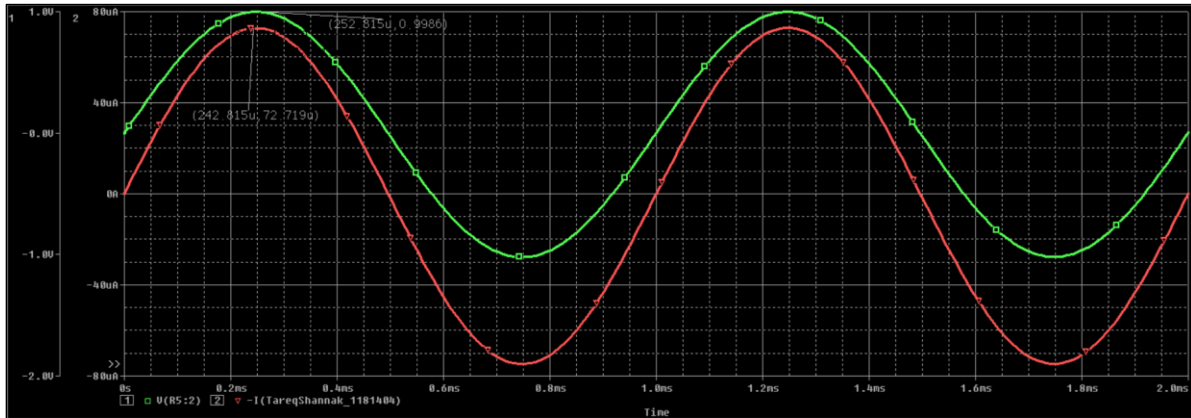Measure the input and output currents and calculate A_i



$$I_{in} = 72.719 \mu A, V_{out} = 0.9986 V \rightarrow I_{out} = 0.9986 mA$$

$$A_i = \frac{I_{out}}{I_{in}} = \frac{0.9986 mA}{72.719 \mu A} = 13.732$$


Calculate the current gain A_i


$$A_i = \frac{I_{out}}{I_{in}} = 13.732$$

Estimate Z_i from I_i and V_i values

$$Z_i = \frac{V_i}{I_i} = \frac{8.4 V}{72.719 \mu A} = 115.513 k\Omega$$

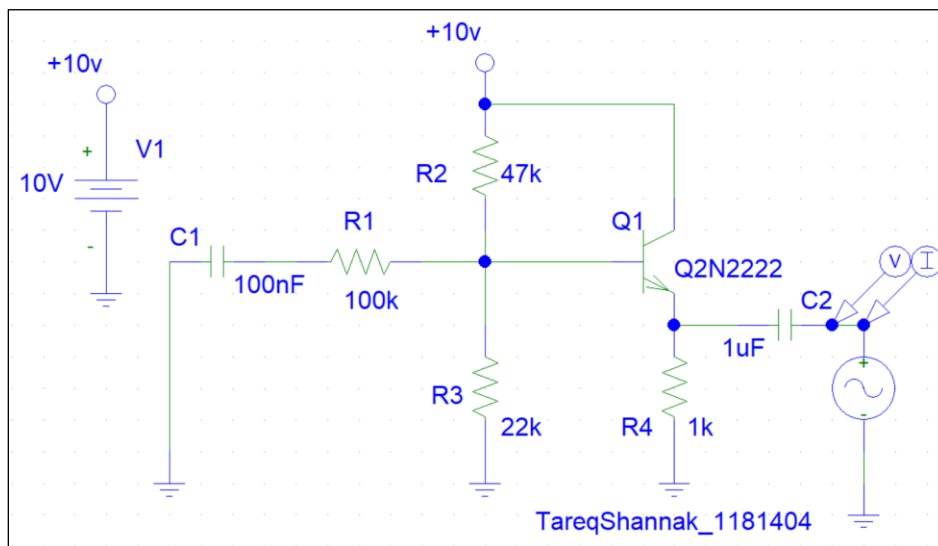To find the output impedance of the amplifier, you should take off the input sine wave generator and replace it with a short circuit, then you have to connect the generator to the output (emitter) via a capacitor, and measure its output voltage and current.



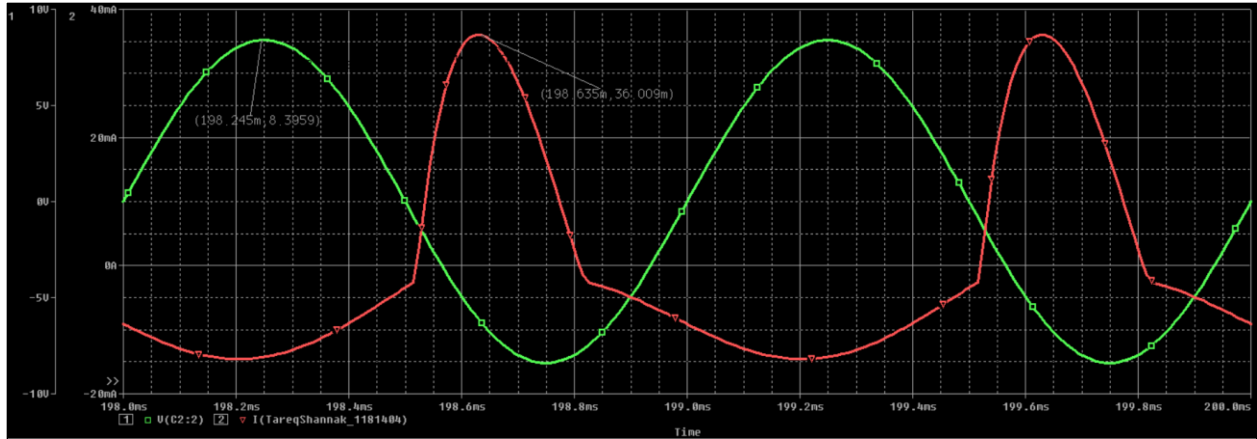

$$V_o = 8.3959 \text{ V}$$

$$I_o = 36.009 \text{ mA}$$

$$Z_o = \frac{V_o}{I_o} = \frac{8.3959 \text{ V}}{36.009 \text{ mA}} = 233.16 \Omega$$

Quantity	Measured Values
V_{in}	8.4 V
V_{out}	0.9986 V
I_{in}	72.719 μA
I_{out}	0.9986 mA
	Calculated Values
A_V	0.119 (< 1)
A_i	13.732 (> 1)
Z_{in}	115.513 $\text{k}\Omega$ (High)
Z_{out}	233.16 Ω (Low)