

Revision Chapter 8

How to solve RLC Circuit ?

- ① Find initial condition ($V_c(0)$ $i_L(0)$)
- ② After changing the switch, determine if it's Parallel or Series

Parallel RLC Circuit :-

$$\mu_{pp} \leftarrow \leftarrow s_{ib}$$

$$\alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

if $\alpha^2 > \omega_0^2 \Rightarrow$ overdamping

$$V(t) = Ae^{s_1 t} + Be^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

② if $\omega_0^2 = \alpha^2 \Rightarrow$ critically damped

$$V(t) = Ae^{-\alpha t} + Bte^{-\alpha t}$$

③ if $\alpha^2 < \omega_0^2 \Rightarrow$ under damping


$$V(t) = e^{-\alpha t} [A \cos \omega_d t + B \sin \omega_d t]$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Series RLC circuit

$\alpha = \frac{R}{2L}$, the equations depend on $i(t)$

Ex

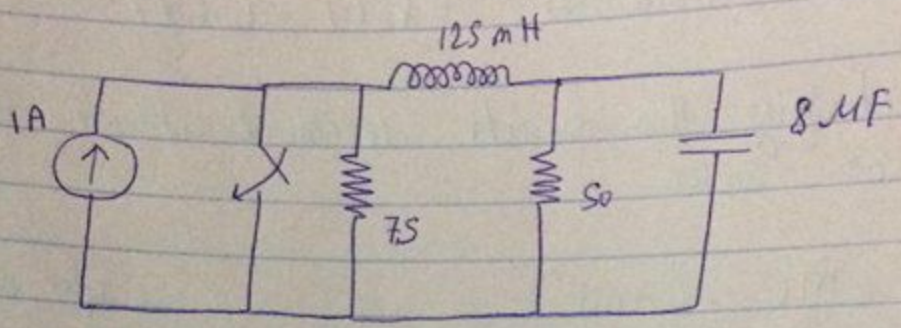


Find $i_L(t)$?

Solution

* نكتب المعادلات الكهربية ونحلها
 الاستجابة الأولية $i_L(t), V_C(t)$

At $t < 0$, $t = 0^-$

Inductor: short CKT
 Capacitor: open CKT

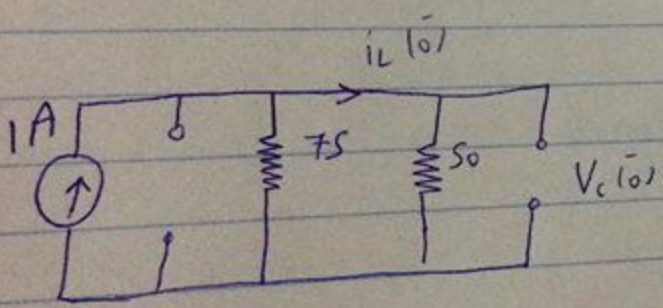


$$i_L(0^-) = \frac{75}{125} * 1 = 0.6 A$$


$$V_C(0^-) = 8 * \frac{6}{10} = 30 V$$

②

Parallel or series
 نكتب $i(t)$ or $V(t)$ ونحلها
 بعد $t > 0$

At $t > 0$

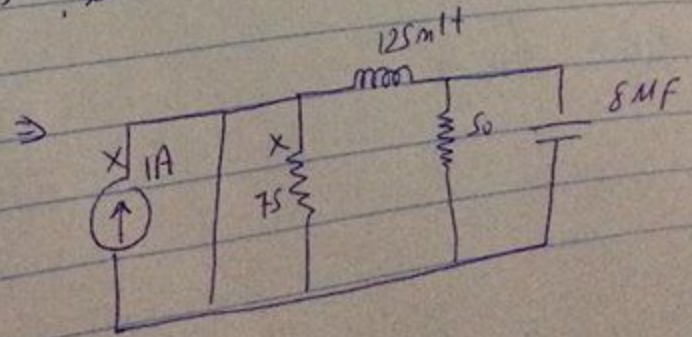

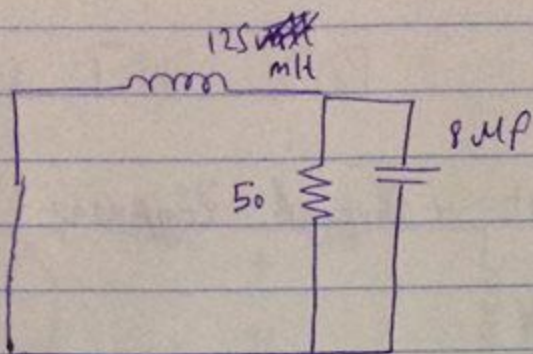

Parallel \Rightarrow find $V(t)$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 * 50 * 8 * 10^{-6}} = 1250$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{125 * 10^{-3} * 8 * 10^{-6}}} = 1000$$

$\alpha^2 > \omega^2 \Rightarrow$ overdamp

$$V(t) = A e^{\frac{s_1 t}{\tau}} + B e^{\frac{s_2 t}{\tau}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega^2} \Rightarrow -1250 \pm \sqrt{1562500 - 1000000} = -1250 \pm 750$$

المخرج

$$s_1 = -2000, s_2 = -500$$

خطأ

$$\Rightarrow -2500, -10000$$

خطأ

$$V(t) = A e^{-2500t} + B e^{-1000t}$$

$$V(0) = 30 \Rightarrow A + B = 30$$

$$L \frac{di}{dt} = V_L(t)$$

$$i(t) = \frac{1}{L} \int V(t) dt - i(0)$$

1st equation

$$0 = i_L + i_C + i_R$$

$$0 = C \frac{dV(t)}{dt} + \frac{V(t)}{R} + \frac{1}{L} \int_0^t V(t) dt - i(0)$$

$$0 = C \frac{dV(0)}{dt} + \frac{V(0)}{R} + 0 - 0.6$$

$$0 = C \frac{dV(0)}{dt} \Rightarrow \frac{dV(0)}{dt} = 0$$

$$\frac{dV(t)}{dt} = -2500A - 10000B = 0$$

$$A = 10$$

$$B = -10$$

$$V(t) = 40 e^{-2500t} - 10 e^{-10000t}$$



$i(t) =$ Natural component + forced component

$$i_L(t) = \frac{1}{L} \int_0^t V(t) dt$$


$$= \frac{1}{L} \left[\frac{-40}{4000} e^{-2500t} + \frac{10}{10000} e^{-10000t} \right]$$

$$i_L(t) = -0.64 e^{-2500t} + 0.04 e^{-10000t}$$

Series RLC CKT

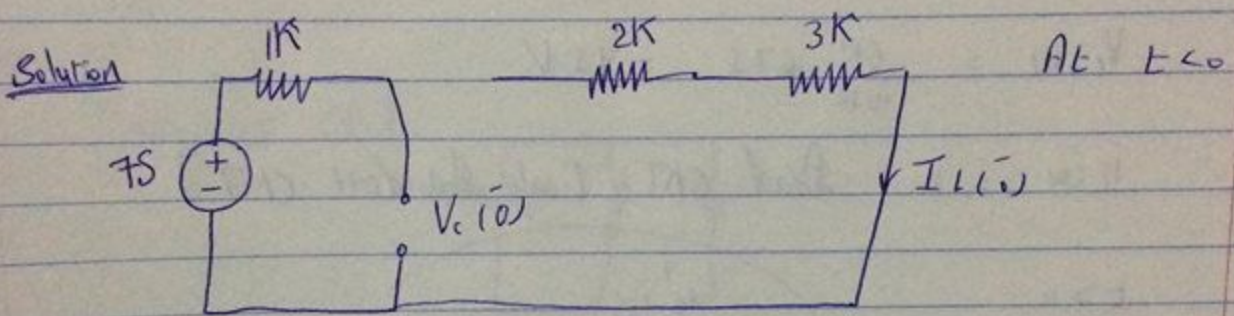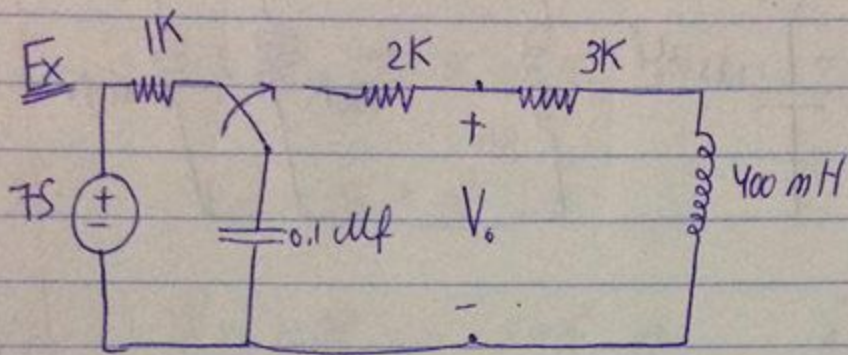
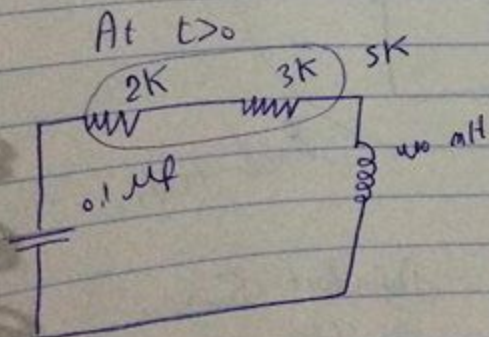
$$I_L(\bar{0}) = 0 \quad V_c(\bar{0}) = 75 \text{ V}$$




Series

$$\alpha = \frac{R}{2L} = 6250$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{5000}{\sqrt{0.1 \times 0.4}} \quad \text{overdamp}$$

$$i(t) = \dots$$

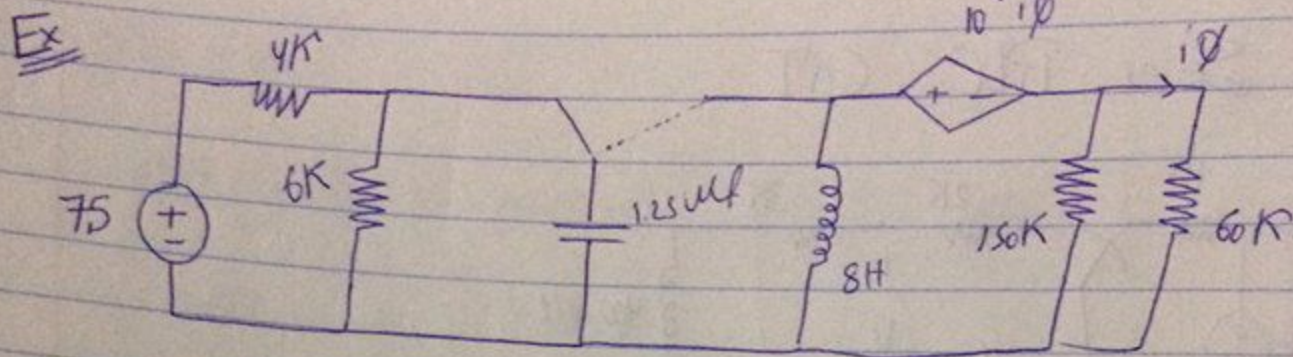


Solution


$$t < 0, \quad t = 0$$

$$V_c(0) = \frac{6k}{10k} * 75 = 45V$$
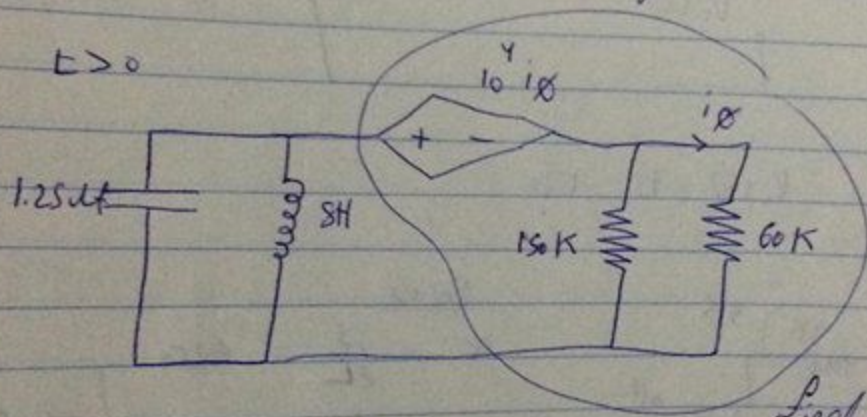
$$i_L(0) = 0 \quad \text{Dead CKT [Only dependent CKT]}$$



Note to solve Pth CKT

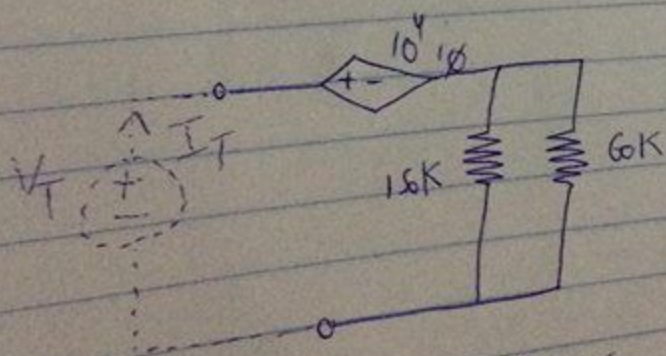

Dependent Source
 \Rightarrow Use Test Source

$$-V_T + 10^4 i_φ + 150 * 10^3 (I_T - i_φ) = 0$$

$$i_φ = \frac{150}{210} I_T \quad \text{COP}$$

$$V_T = 10^4 I_\phi + 150 * 10^3 (I_T - I_\phi)$$

$$\Rightarrow V_T = 7.1 * 10^3 I_T + (0.28 I_T) (150 * 10^3)$$

$$V_T = 50 * 10^3 I_T$$

$$\frac{V_T}{I_T} = R = 50 * 10^3 \Omega$$

\Rightarrow our CKT

