
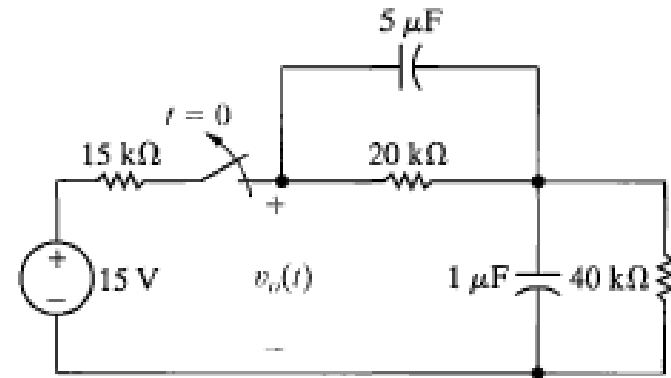


Assessment 7.4

The switch in the circuit shown has been closed for a long time before being opened at $t = 0$. Find $v_o(t)$ for $t > 0$.

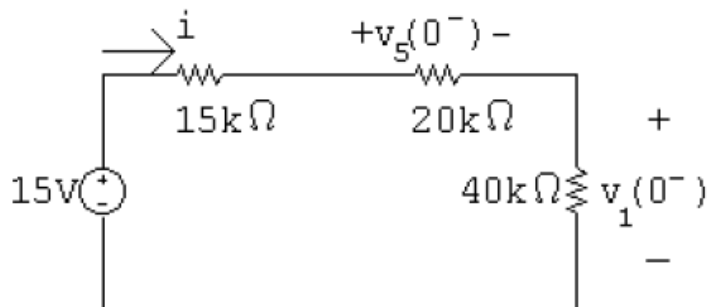**Solution**

This circuit is actually two RC circuits in series, and the requested voltage, v_o , is the sum of the voltage drops for the two RC circuits. The circuit for $t < 0$ is shown below:



Find the current in the loop and use it to find the initial voltage drops across the two RC circuits:

$$i = \frac{15}{75,000} = 0.2 \text{ mA}, \quad v_5(0^-) = 4 \text{ V}, \quad v_1(0^-) = 8 \text{ V}$$

There are two time constants in the circuit, one for each RC subcircuit. τ_5 is the time constant for the $5 \mu\text{F} - 20 \text{ k}\Omega$ subcircuit, and τ_1 is the time constant for the $1 \mu\text{F} - 40 \text{ k}\Omega$ subcircuit:

$$\tau_5 = (20 \times 10^3)(5 \times 10^{-6}) = 100 \text{ ms}; \quad \tau_1 = (40 \times 10^3)(1 \times 10^{-6}) = 40 \text{ ms}$$

Therefore,


$$v_5(t) = v_5(0^-)e^{-t/\tau_5} = 4e^{-t/0.1} = 4e^{-10t} \text{ V}, \quad t \geq 0$$

$$v_1(t) = v_1(0^-)e^{-t/\tau_1} = 8e^{-t/0.04} = 8e^{-25t} \text{ V}, \quad t \geq 0$$

Finally,

$$v_o(t) = v_1(t) + v_5(t) = [8e^{-25t} + 4e^{-10t}] \text{ V}, \quad t \geq 0$$

Assessment 7.5

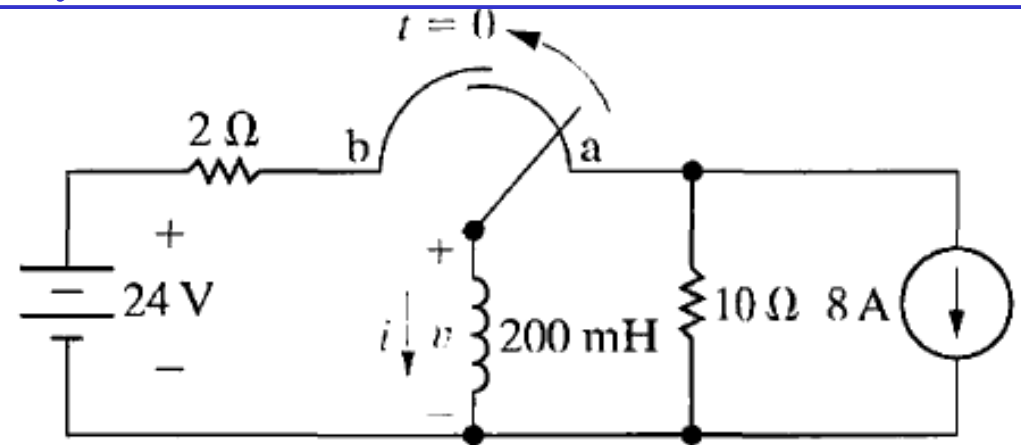


Assume that the switch in the circuit shown has been in position b for a long time, and at $t = 0$ it moves to position

Find : $i(t)$, $t > 0$; and $v(t)$, $t > 0_+$.

Solution

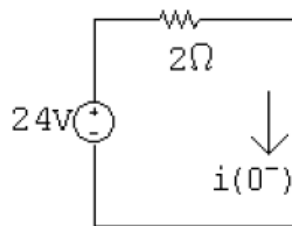
Use the circuit at $t < 0$, shown below, to calculate the initial current in the inductor:



$$i(0^-) = 24/2 = 12 \text{ A} = i(0^+)$$

Note that $i(0^-) = i(0^+)$ because the current in an inductor is continuous.

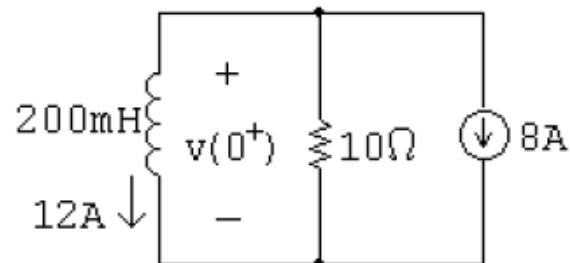Use the circuit at $t = 0^+$, shown below, to calculate the voltage drop across the inductor at 0^+ . Note that this is the same as the voltage drop across the $10\ \Omega$ resistor, which has current from two sources — $8\ \text{A}$ from the current source and $12\ \text{A}$ from the initial current through the inductor.




$$v(0^+) = -10(8 + 12) = -200\ \text{V}$$

To calculate the time constant we need the equivalent resistance seen by the inductor for $t > 0$. Only the $10\ \Omega$ resistor is connected to the inductor for $t > 0$. Thus,

$$\tau = L/R = (200 \times 10^{-3}/10) = 20\ \text{ms}$$

To find $i(t)$, we need to find the final value of the current in the inductor.

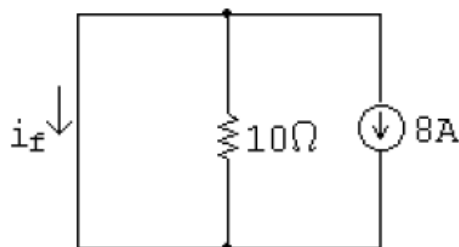When the switch has been in position a for a long time, the circuit reduces to the one below:



Note that the inductor behaves as a short circuit and all of the current from the 8 A source flows through the short circuit. Thus,

$$i_f = -8 \text{ A}$$

Now,

$$\begin{aligned} i(t) &= i_f + [i(0^+) - i_f]e^{-t/\tau} = -8 + [12 - (-8)]e^{-t/0.02} \\ &= -8 + 20e^{-50t} \text{ A}, \quad t \geq 0 \end{aligned}$$


To find $v(t)$, use the relationship between voltage and current for an inductor:

$$v(t) = L \frac{di(t)}{dt} = (200 \times 10^{-3})(-50)(20e^{-50t}) = -200e^{-50t} \text{ V}, \quad t \geq 0^+$$

Problem 7.6


The switch in the circuit has been closed a long time. At $t = 0$ it is opened.

Find $i_o(t)$ for $t > 0$.

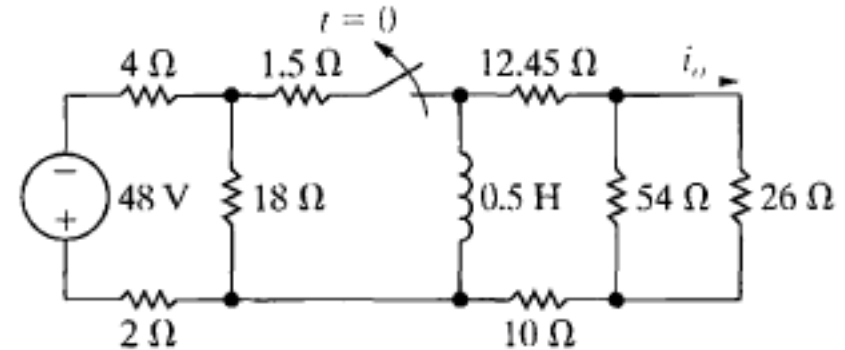

Solution


For $t < 0$

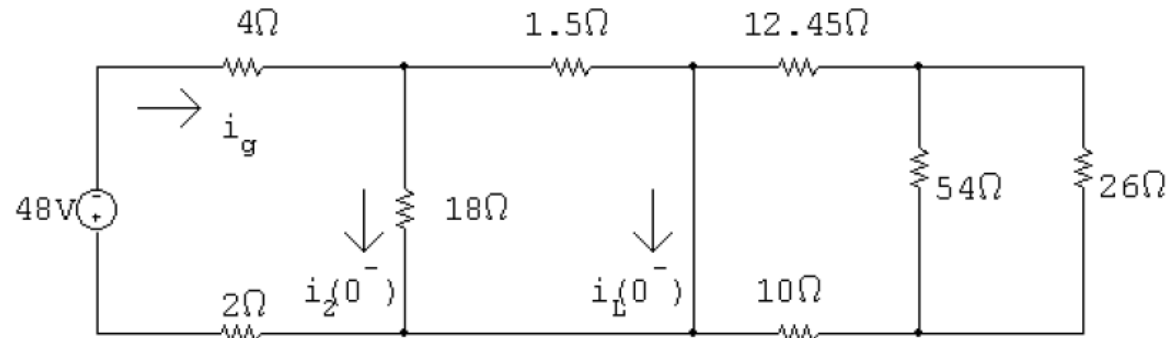

$$i_g = \frac{-48}{6 + (18 \parallel 1.5)} = -6.5 \text{ A}$$

$$i_L(0^-) = \frac{18}{18 + 1.5}(-6.5) = -6 \text{ A} = i_L(0^+)$$

For $t > 0$

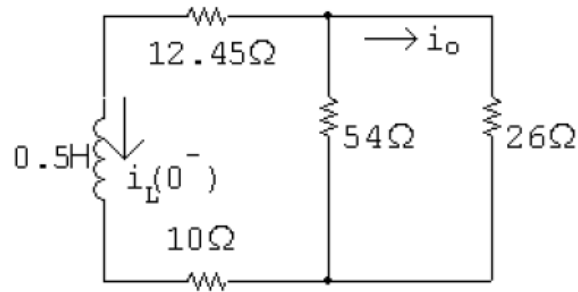

$$i_L(t) = i_L(0^+)e^{-t/\tau} \text{ A}, \quad t \geq 0$$

$$\tau = \frac{L}{R} = \frac{0.5}{10 + 12.45 + (54 \parallel 26)} = 0.0125 \text{ s}; \quad \frac{1}{\tau} = 80$$


$$i_L(t) = -6e^{-80t} \text{ A}, \quad t \geq 0$$

$$i_o(t) = \frac{54}{80}(-i_L(t)) = \frac{54}{80}(6e^{-80t}) = 4.05e^{-80t} \text{ V}, \quad t \geq 0^+$$

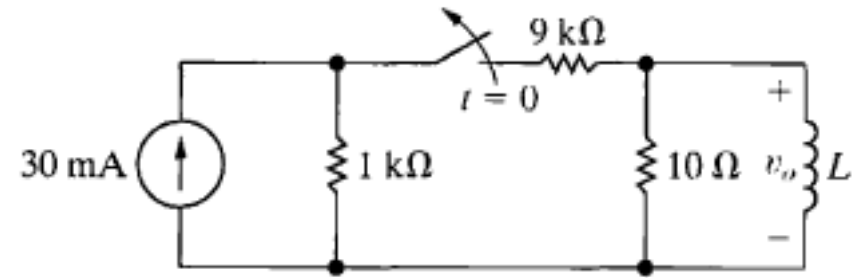Problem 7.10

In the circuit, the switch has been closed for a long time before opening at $t = 0$.

Find the value of L so that $v_o(t)$ equals to $0.5 v_o(0^+)$ when $t = 1$ ms



Solution

$$v_o(t) = v_o(0^+)e^{-t/\tau}$$

$$\therefore v_o(0^+)e^{-10^{-3}/\tau} = 0.5v_o(0^+)$$

$$\therefore e^{10^{-3}/\tau} = 2$$

$$\therefore \tau = \frac{L}{R} = \frac{10^{-3}}{\ln 2}$$


$$\therefore L = \frac{10 \times 10^{-3}}{\ln 2} = 14.43 \text{ mH}$$

Problem 7.23

The switch in the circuit has been in position a for a long time and $v_2 = 0$ V. At $t = 0$, the switch is thrown to position b.

Calculate


i , v_1 and v_2 for $t > 0+$.

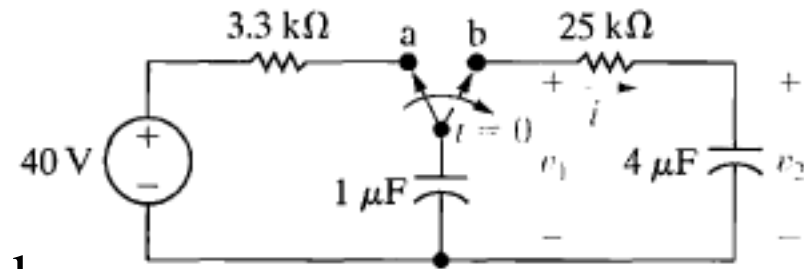

Solution


$$\text{P 7.23 [a] } v_1(0^-) = v_1(0^+) = 40 \text{ V} \qquad v_2(0^+) = 0$$
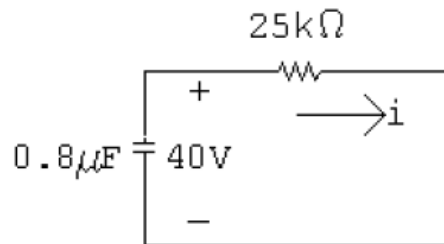
$$C_{\text{eq}} = (1)(4)/5 = 0.8 \mu\text{F}$$



$$\tau = (25 \times 10^3)(0.8 \times 10^{-6}) = 20\text{ms}; \qquad \frac{1}{\tau} = 50$$
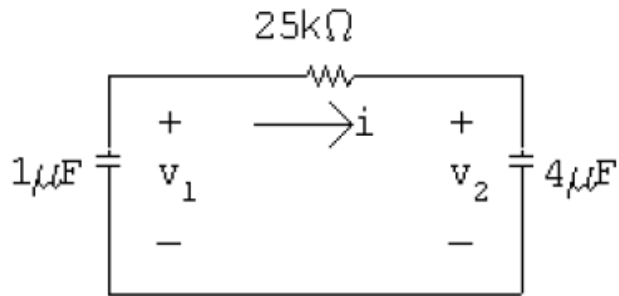
$$i = \frac{40}{25,000} e^{-50t} = 1.6e^{-50t} \text{ mA}, \quad t \geq 0^+$$



$$v_1 = \frac{-1}{10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 40 = 32e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

$$v_2 = \frac{1}{4 \times 10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 0 = -8e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

Answer

$$i(t) = 1.6e^{-50t} \text{ mA}, \quad t \geq 0^+$$


$$V_1(t) = 32e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

$$V_2(t) = -8e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

Problem 7.30


The switch in the circuit has been in position 1 for a long time before moving to position 2 at $t = 0$.

Find $i_o(t)$ for $t > 0+$.

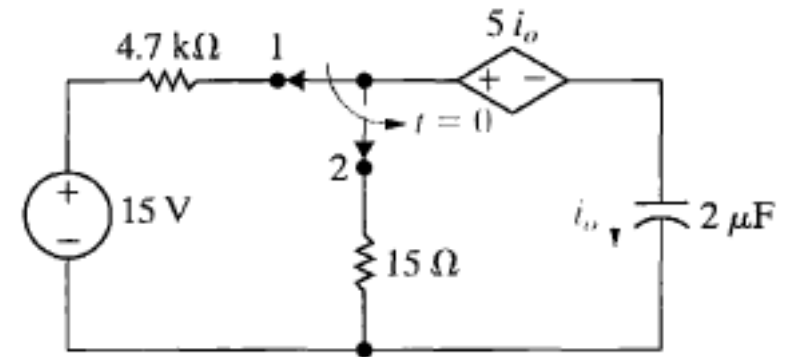


Solution


$t < 0$

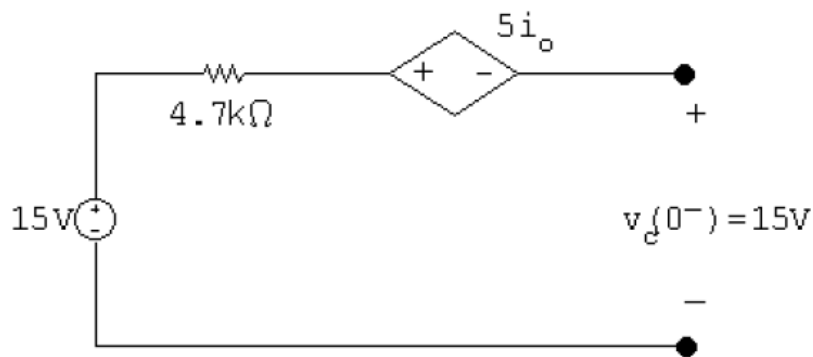

$t > 0$

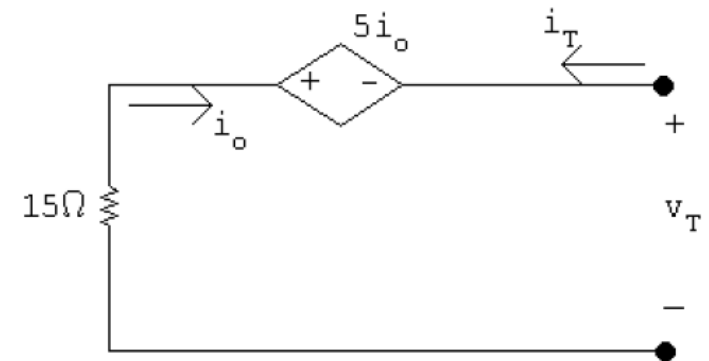
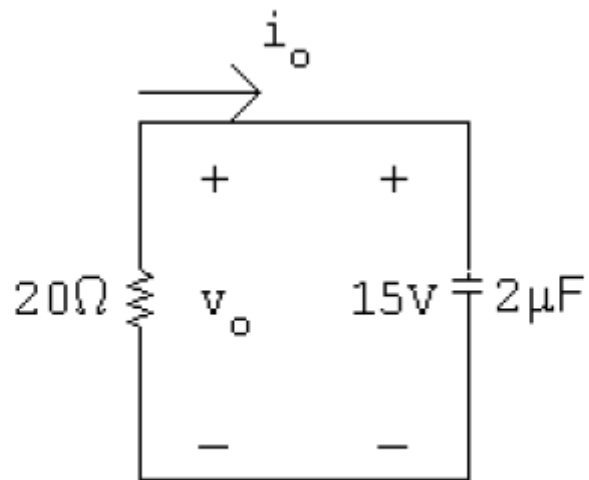
$$v_T = -5i_o - 15i_o = -20i_o = 20i_T \quad \therefore \quad R_{Th} = \frac{v_T}{i_T} = 20 \Omega$$




$$\tau = RC = 40 \mu s; \quad \frac{1}{\tau} = 25,000$$

$$v_o = 15e^{-25,000t} \text{ V}, \quad t \geq 0$$

$$i_o = -\frac{v_o}{20} = -0.75e^{-25,000t} \text{ A}, \quad t \geq 0^+$$

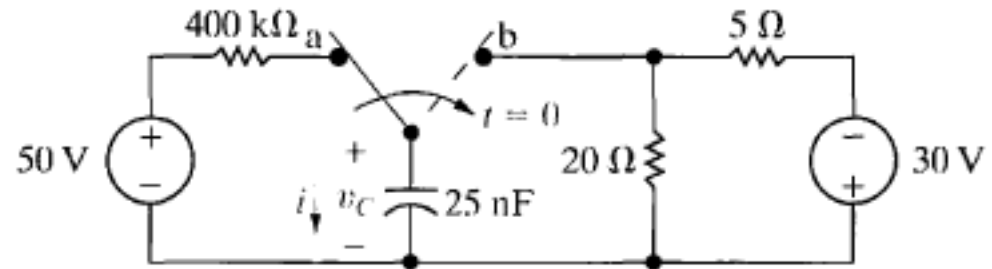Problem 7.55

Assume that the switch in the circuit has been in position a for a long time and that at $t = 0$ it is moved to position b.



Find

- (a) $v_c, t > 0$;
- (b) $i, t > 0+$.

$$v_c(0^+) = 50 \text{ V}$$

Use voltage division to find the final value of voltage:


$$v_c(\infty) = \frac{20}{20 + 5}(-30) = -24 \text{ V}$$

Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$V_{\text{Th}} = -24 \text{ V}, \quad R_{\text{Th}} = 20 \parallel 5 = 4 \Omega,$$

$$\text{Therefore } \tau = R_{\text{eq}}C = 4(25 \times 10^{-9}) = 0.1 \mu\text{s}$$

The simplified circuit for $t > 0$ is:

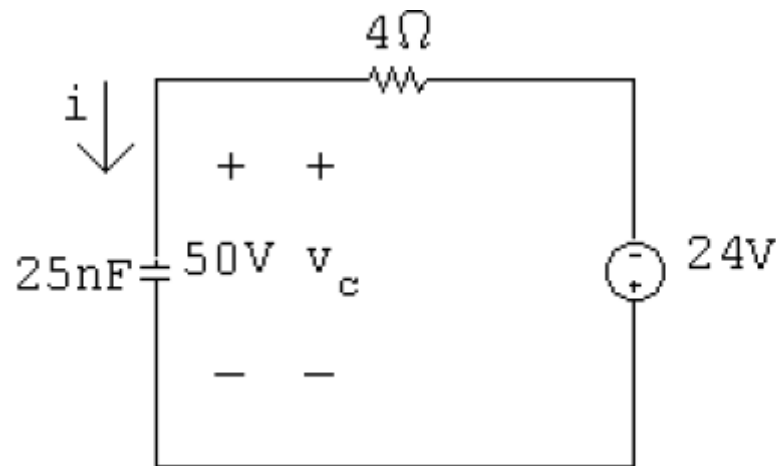


$$i(0^+) = \frac{-24 - 50}{4} = -18.5 \text{ A}$$

$$v_c = v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-t/\tau}$$

$$= -24 + [50 - (-24)]e^{-t/\tau} = -24 + 74e^{-10^7 t} \text{ V}, \quad t \geq 0$$

$$i = C \frac{dv_c}{dt} = (25 \times 10^{-9})(-10^7)(74e^{-10^7 t}) = -18.5e^{-10^7 t} \text{ A}, \quad t \geq 0^+$$


Problem 7.71

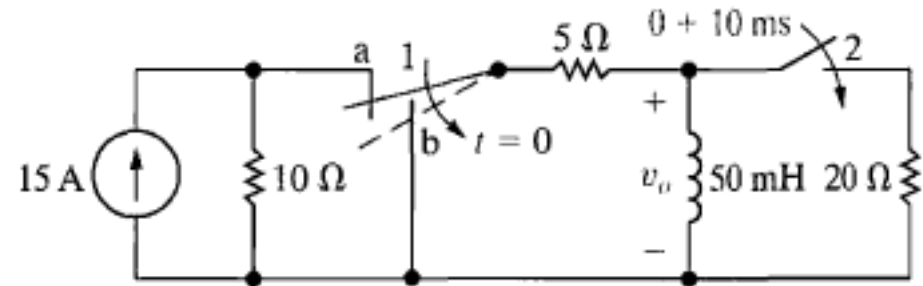

The action of the two switches in the circuit seen in is as follows. For $t < 0$, switch 1 is in position a and switch 2 is open. This state has existed for a long time. At $t = 0$, switch 1 moves instantaneously from position a to position b, while switch 2 remains open. Ten milliseconds after switch 1 operates, switch 2 closes, remains closed for 10 ms and then opens.


Find $v_o(t)$ for $t > 20$ ms.

For $t < 0$:

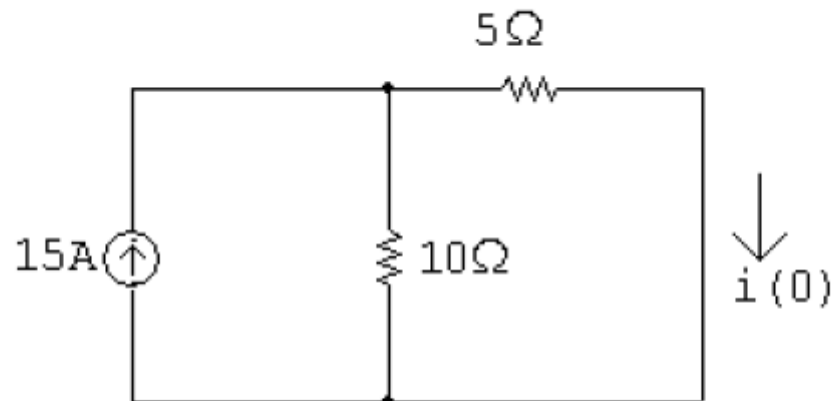

$$i(0) = \frac{10}{15}(15) = 10 \text{ A}$$


$0 \leq t \leq 10 \text{ ms}$:

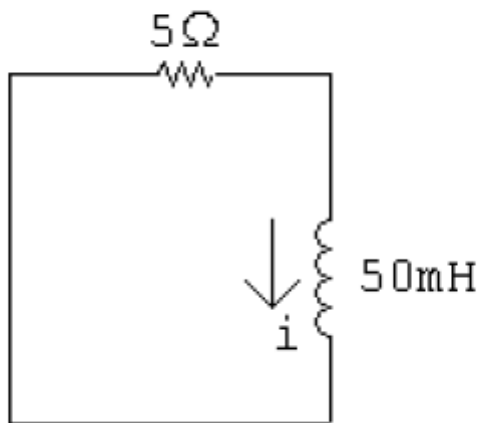

$$i = 10e^{-100t} \text{ A}$$

$$i(10 \text{ ms}) = 10e^{-1} = 3.68 \text{ A}$$

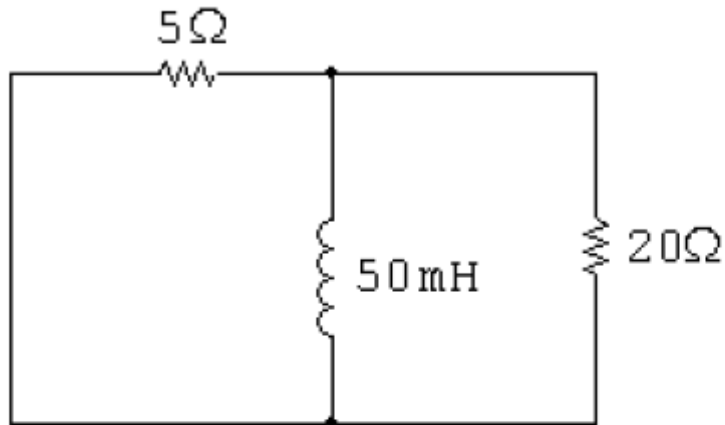$10 \text{ ms} \leq t \leq 20 \text{ ms}$:



$$R_{\text{eq}} = \frac{(5)(20)}{25} = 4 \Omega$$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{4}{50 \times 10^{-3}} = 80$$

$$i = 3.68e^{-80(t-0.01)} \text{ A}$$

$20 \text{ ms} \leq t < \infty$:

$$i(20 \text{ ms}) = 3.68e^{-80(0.02-0.01)} = 1.65 \text{ A}$$

$$i = 1.65e^{-100(t-0.02)} \text{ A}$$

$$v_o = L \frac{di}{dt}; \quad L = 50 \text{ mH}$$

$$\frac{di}{dt} = 1.65(-100)e^{-100(t-0.02)} = -165e^{-100(t-0.02)}$$

$$v_o = (50 \times 10^{-3})(-165)e^{-100(t-0.02)}$$

$$= -8.26e^{-100(t-0.02)} \text{ V}, \quad t > 20^+ \text{ ms}$$

$$v_o(25 \text{ ms}) = -8.26e^{-100(0.025-0.02)} = -5.013 \text{ V}$$