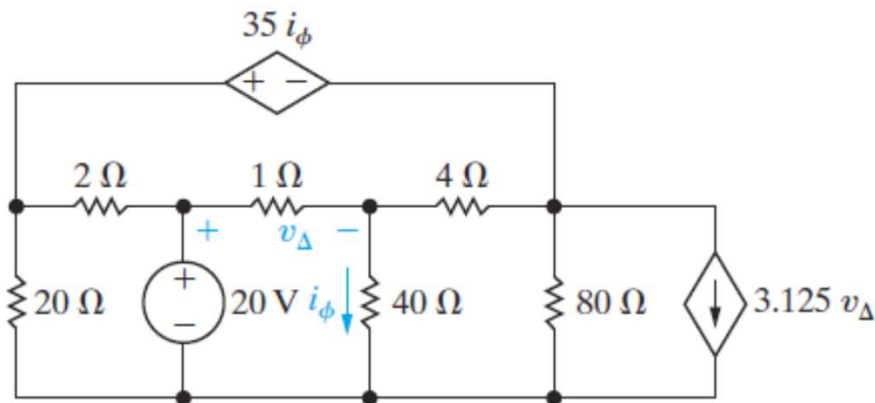


4.30 Use the node-voltage method to find the power developed by the 20 V source in the circuit in Fig. P4.30.

PSPICE
MULTISIM

Figure P4.30



Let i_g be the current delivered by the 20 V source, then

$$i_g = \frac{20 - (20.25)}{2} + \frac{20 - 10}{1} = 30.125 \text{ A}$$

$$p_g \text{ (delivered)} = 20(30.125) = 602.5 \text{ W}$$

Node equations:

$$\frac{v_1}{20} + \frac{v_1 - 20}{2} + \frac{v_3 - v_2}{4} + \frac{v_3}{80} + 3.125v_\Delta = 0$$

$$\frac{v_2}{40} + \frac{v_2 - v_3}{4} + \frac{v_2 - 20}{1} = 0$$

Constraint equations:

$$v_\Delta = 20 - v_2$$

$$v_1 - 35i_\phi = v_3$$


$$i_\phi = v_2/40$$

$$\text{Solving, } v_1 = -20.25 \text{ V; } v_2 = 10 \text{ V; } v_3 = -29 \text{ V}$$

4.42 Use the mesh-current method to find the power developed in the dependent voltage source in the circuit in Fig. P4.42.

PSPICE
MULTISIM

Figure P4.42

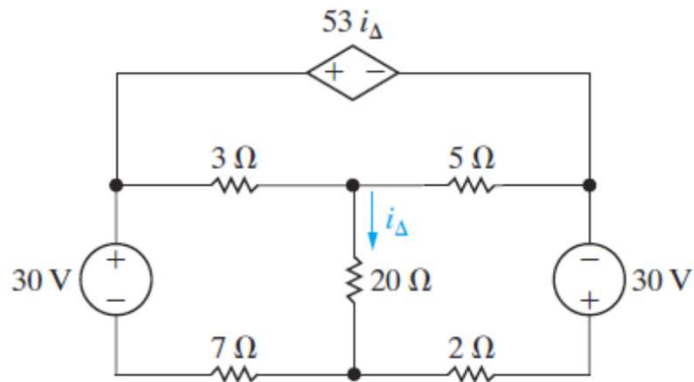

Mesh equations:

$$53i_{\Delta} + 8i_1 - 3i_2 - 5i_3 = 0$$

$$i_{\Delta} - 3i_1 + 30i_2 - 20i_3 = 30$$

$$i_{\Delta} - 5i_1 - 20i_2 + 27i_3 = 30$$

Constraint equations:

$$i_{\Delta} = i_2 - i_3$$


Solving, $i_1 = 110 \text{ A}$; $i_2 = 52 \text{ A}$; $i_3 = 60 \text{ A}$; $i_{\Delta} = -8 \text{ A}$

$$p_{\text{depsource}} = 53 i_{\Delta} i_1 = (53)(-8)(110) = -46,640 \text{ W}$$

PSPICE
MULTISIM

4.74 Determine the Thévenin equivalent with respect to the terminals a,b for the circuit shown in Fig. P4.74.

Figure P4.74

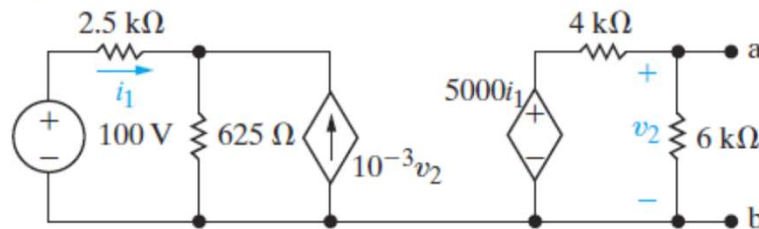

OPEN CIRCUIT

$$100 = 2500i_1 + 625(i_1 + 10^{-3}v_2)$$

$$v_2 = \frac{6000}{10,000} (5000i_2)$$

Solving,

$$I_1 = 0.02A; V_2 = V_{oc} = 60V$$

SHORT CIRCUIT

$$V_2 = 0;$$

$$i_{sc} = \frac{5000}{4000} (i_1)$$

$$i_1 = \frac{100}{2500+625} = 0.032A$$

$$\text{Thus, } i_{sc} = 0.04A$$

$$R_{Th} = 1.5 \text{ k}$$

4.81 Find the Norton equivalent with respect to the terminals a,b for the circuit seen in Fig. P4.81.

Figure P4.81


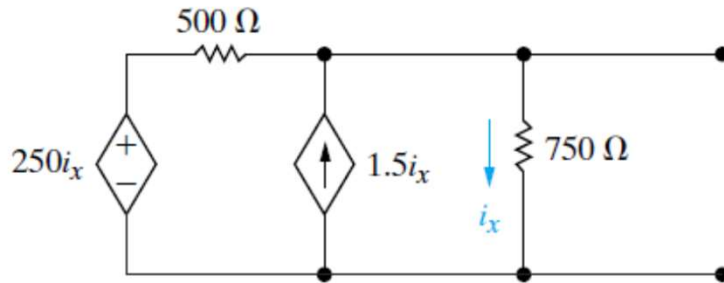


Figure P4.81

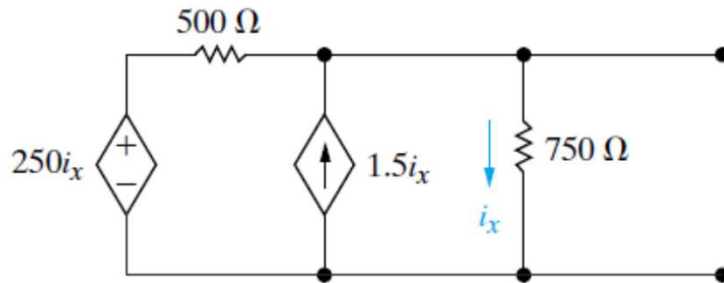


$$\frac{v - 250i_x}{500} - 1.5i_x + \frac{v}{750} - 1 = 0$$

$$i_x = \frac{v}{750}$$

Solving,


$$v = 1500 \text{ V}; \quad i_x = 2 \text{ A}$$
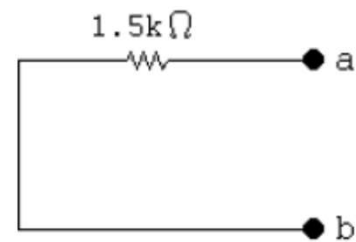
$$R_{Th} = \frac{v}{1 \text{ A}} = 1500 = 1.5 \text{ k}\Omega$$




4.97 Use the principle of superposition to find v_o in the circuit in Fig. P4.97.


Figure P4.97

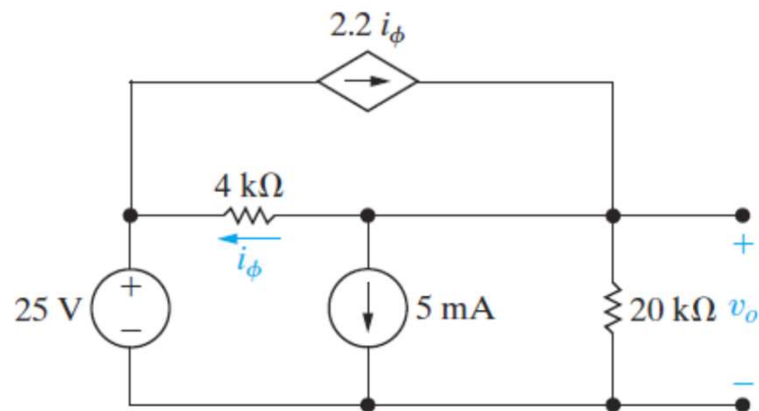

Current source acting alone:

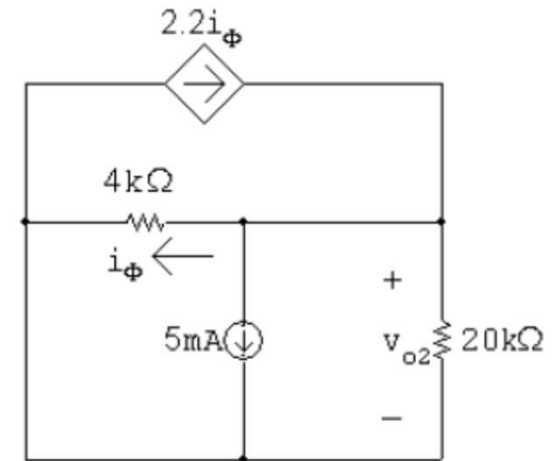

Voltage source acting alone:

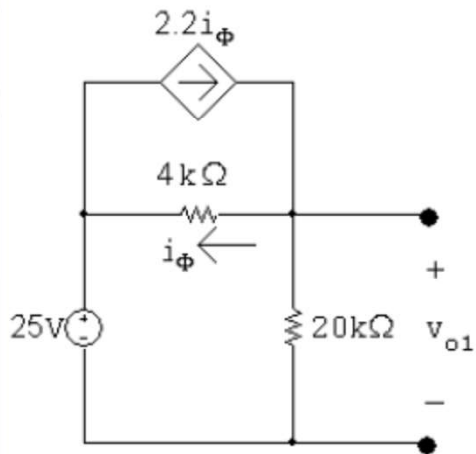

$$\frac{v_{o1} - 25}{4000} + \frac{v_{o1}}{20,000} - 2.2 \left(\frac{v_{o1} - 25}{4000} \right) = 0$$


Simplifying $5v_{o1} - 125 + v_{o1} - 11v_{o1} + 275 = 0 \quad \therefore v_{o2} = 20 \text{ V}$

$\therefore v_{o1} = 30 \text{ V}$

$$\frac{v_{o2}}{4000} + \frac{v_{o2}}{20,000} + 0.005 - 2.2 \left(\frac{v_{o2}}{4000} \right) = 0$$

Simplifying $5v_{o2} + v_{o2} + 100 - 11v_{o2} = 0$
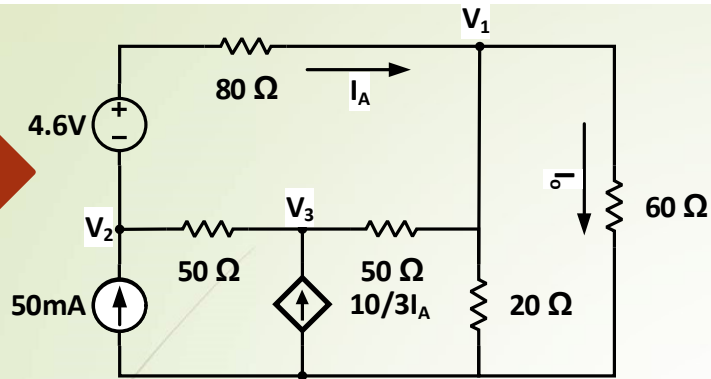
$$v_o = v_{o1} + v_{o2} = 30 + 20 = 50 \text{ V}$$



$$\frac{V_1 - 4.6 - V_2}{80} + \frac{V_1}{20} + \frac{V_1}{60} + \frac{V_1 - V_3}{50} = 0$$

$$119V_1 - 15V_2 - 24V_3 = 69$$

$$\frac{V_2 + 4.6 - V_1}{80} + \frac{V_2 - V_3}{50} - 50m = 0$$

$$-5V_1 + 13V_2 - 8V_3 = -3$$


$$\frac{V_3 - V_2}{50} + \frac{V_3 - V_1}{50} - \frac{10}{3}I_A = 0$$

$$\frac{V_3 - V_2}{50} + \frac{V_3 - V_1}{50} - \frac{10}{3} \left(\frac{V_2 + 4.6 - V_1}{80} \right) = 0$$

$$13V_1 - 37V_2 + 24V_3 = 115$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 36.75 \\ 89.75 \\ 123.25 \end{bmatrix}$$
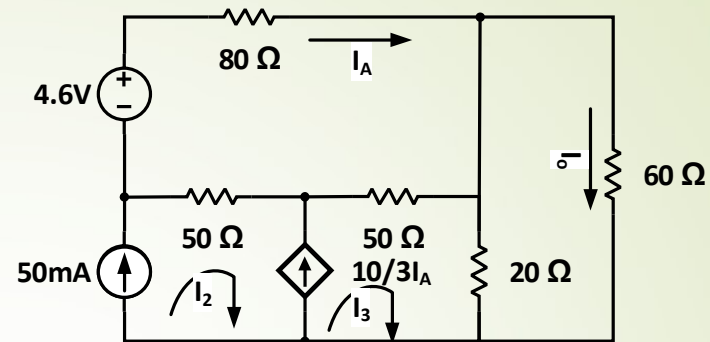
$$I_o = \frac{V_1}{60} = \frac{36.75}{60} = 0.61A$$



$$(I_2 = 0.05)$$

$$(I_3 - 0.05 = \frac{10}{3}I_A) \text{ Or } (0.3I_3 - 0.015) = I_A$$

$$-4.6 + 80I_A + 50(I_A - I_3) + 50(I_A - 0.05) = 0$$

$$-7.1 + 180I_A - 50I_3 = 0$$

$$-7.1 + 180(0.3I_3 - 0.015) - 50I_3 = 0$$


$$I_3 = 2.45A;$$

$$60I_o + 20(I_o - I_3) = 0$$

$$80I_o - 20 * 2.45 = 0$$

$$I_o = 0.61mA$$

Find R_L that dissipate maximum power?


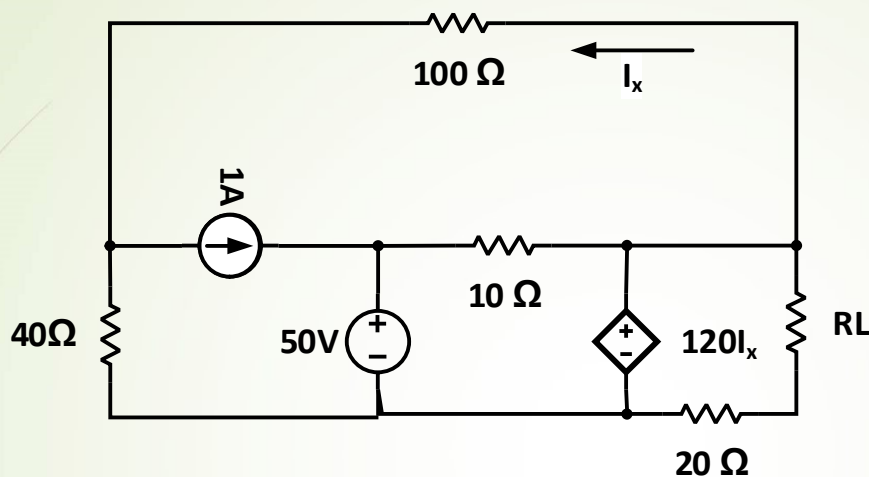


$$\begin{aligned}
 V_{oc} &= 120I_x \\
 40(1 - I_x) - 100I_x + 120I_x &= 0 \\
 20I_x &= 1 \\
 I_x &= \frac{1}{20} A \\
 V_{oc} &= \frac{120}{20} = 6A
 \end{aligned}$$

$$\begin{aligned}
 I_{sc} &= \frac{120I_x}{20} = 6I_x \\
 40(1 - I_x) - 100I_x + 120I_x &= 0 \\
 20I_x &= 1 \\
 I_x &= \frac{1}{20} A \\
 I_{sc} &= 6I_x = \frac{3}{10} A
 \end{aligned}$$

$$R_L = R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{120 * 10}{3} = 400\Omega$$


Use Superposition method to find V_o ?

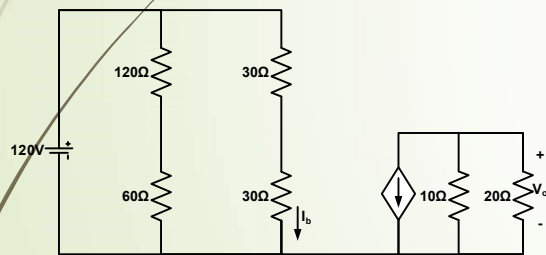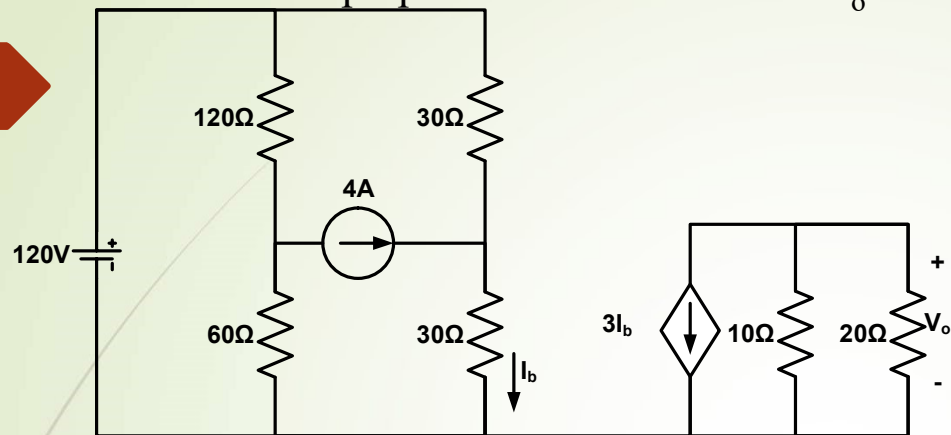

For 120V on

$$I_b = \frac{120}{60} = 2A$$
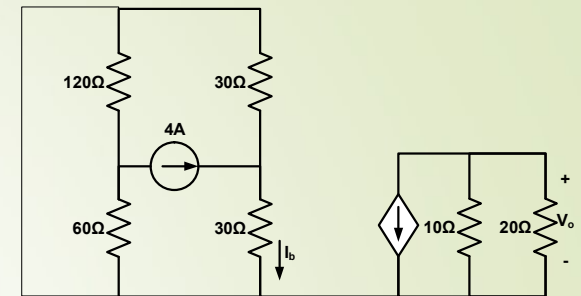
$$V_{o1} = - \left[\frac{10}{10 + 20} 3I_b \right] * 20 = -40V$$




For 4A on

$$I_b = \frac{30}{60} * 4 = 2A$$

$$V_{o2} = - \left[\frac{10}{10 + 20} 3I_b \right] * 20 = -40V$$

$$V_o = V_{o1} + V_{o2} = -80$$

Use Node Voltage method to find I?

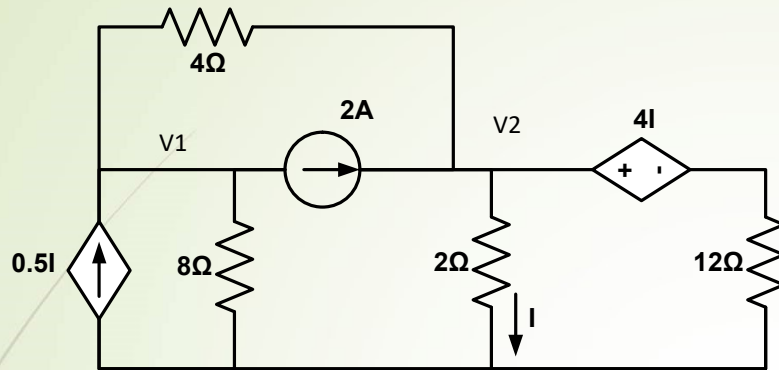

$$I = \frac{V_2}{2}$$

$$-0.5I + 2 + \frac{V_1}{8} + \frac{V_1 - V_2}{4} = 0$$

$$3V_1 - 4V_2 = -16$$

$$\frac{V_2 - 4I}{12} + \frac{V_2}{2} - 2 + \frac{V_2 - V_1}{4} = 0$$

$$10V_2 - 4I - 3V_1 = 24$$

$$8V_2 - 3V_1 = 24$$

$$1 + 2 - 4V_2 = 8$$

$$I = \frac{V_2}{2} = 1A$$