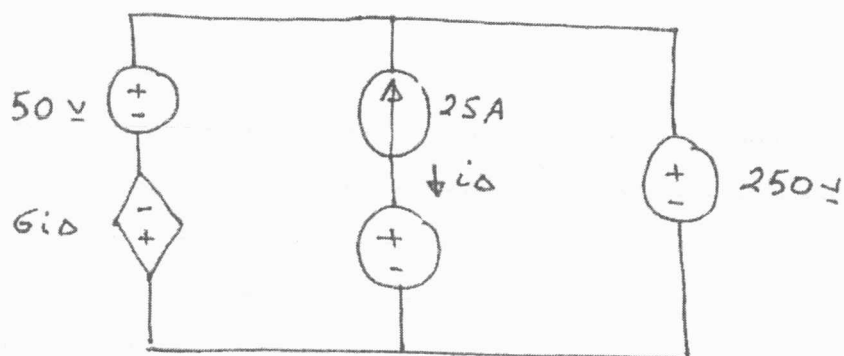


Ch 2 Homework Solutions Circuit Analysis EE 231

2.7




$$i_{\Delta} = -25A, \therefore 6i_{\Delta} = -150V$$


Since  $50 - (-150) \neq 250$

$\therefore$  The connection is invalid.

2.8

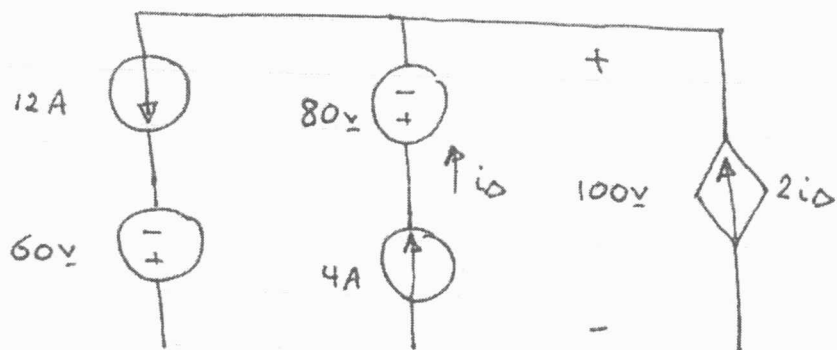

$$i_{\Delta} = 4A$$

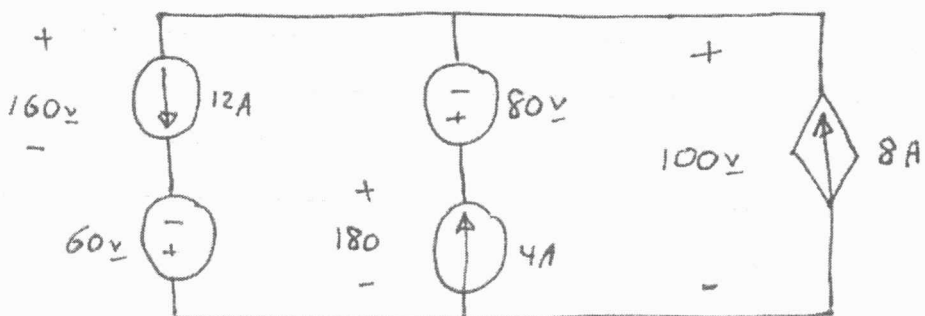

$$P_{12A} = (160)(12) = 1920 \text{ W absorb}$$

$$P_{60V} = (60)(12) = 720 \text{ W supply}$$


$$P_{80V} = (80)(4) = 320 \text{ W absorb}$$

$$P_{4A} = (4)(180) = 720 \text{ W supply}$$

$$P_{210} = (8)(100) = 800 \text{ W supply}$$

$$\Sigma \text{ Power supply} = \Sigma \text{ Power absorb}$$

2.21

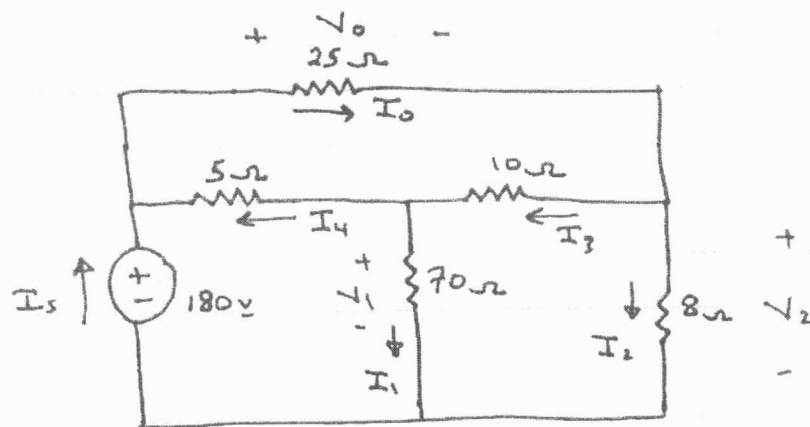

Since  $I_0 = 4A$  ,  $V_0 = 100V$

$$V_2 = -V_0 + 180 = 80V$$

$$I_2 = \frac{V_2}{8} = 10A$$

$$I_3 = I_0 - I_2 = -6A$$

$$V_1 = -10 I_3 + V_2 = 140V$$

$$I_1 = \frac{V_1}{70} = 2A$$

$$I_4 = I_3 - I_1 = -8A$$

$$I_5 = I_0 - I_4 = 12A$$

$$P_{5\Omega} = (8)^2 \cdot 5 = 320 \text{ W}$$

$$P_{25\Omega} = (4)^2 \cdot 25 = 400 \text{ W}$$

$$P_{70\Omega} = (2)^2 \cdot 70 = 280 \text{ W}$$


$$P_{10\Omega} = (6)^2 \cdot 10 = 360 \text{ W}$$

$$P_{8\Omega} = (10)^2 \cdot 8 = 800 \text{ W}$$

$$P_{180V} = (180)(12) = 2160$$

$$\Sigma P_{\text{dissipated}} = \Sigma \text{ Power supply}$$

2.27

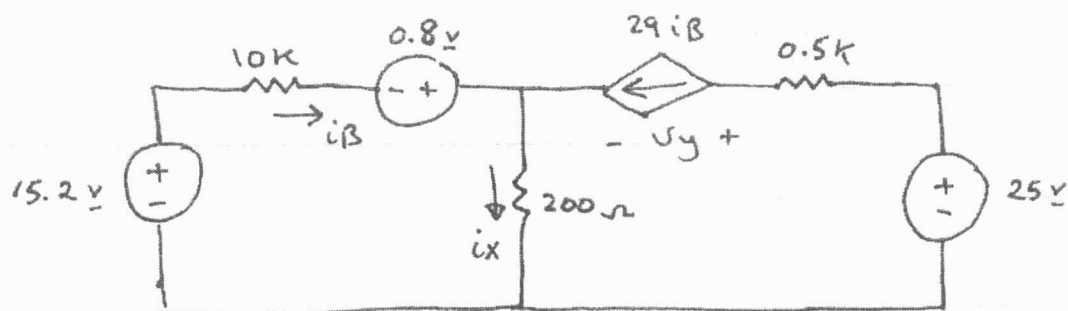

$$i_X = 30 i_B$$

$$i_B = \frac{15.2 + 0.8}{16k} = 1 \text{ mA}$$

$$V_Y = -(0.5k)(29 i_B) + 25 - (0.2k)(30 i_B) = 4.5 \text{ V}$$

$$P_{15.2V} = (15.2)(1 \text{ mA}) = 15.2 \text{ mW supply}$$

$$P_{0.8V} = (0.8)(1 \text{ mA}) = 0.8 \text{ mW supply}$$

$$P_{25V} = (25)(29mA) = 725 \text{ mW} \quad \text{supply}$$

$$P_{29mA} = (29mA)(4.5) = 130.5 \text{ mW} \quad \text{absorb}$$


$$P_{10K} = (10K)(1mA)^2 = 10 \text{ mW} \quad \text{dissipated}$$

$$P_{200\Omega} = (30mA)^2(200) = 180 \text{ mW} \quad \text{dissipated}$$

$$P_{0.5K} = (29mA)^2(500) = 420.5 \text{ mW} \quad \text{dissipated}$$

$$\underline{\underline{\sum \text{power supplied} = \sum \text{power absorbed} + \sum \text{power dissipated}}}$$

2.30

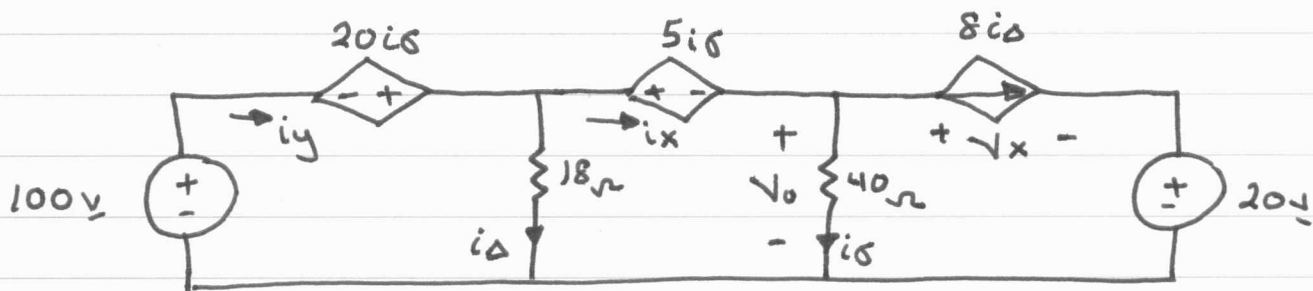

$$100 = -20i_Ω + 18i_Δ$$

$$0 = 5i_Ω + 40i_Ω - 18i_Δ$$

$$\therefore i_Ω = 4A \quad \text{and} \quad i_Δ = 10A$$

$$V_0 = 40i_Ω = 160V, \quad V_x = V_0 - 20 = 140V$$

$$i_x = i_Ω + 8i_Δ = 84A$$

$$i_y = i_x + i_Δ = 94A$$

$$P_{100V} = (100)(i_y) = 9400 \text{ W} \quad \text{supply}$$

$$P_{20Ω} = (20)(i_y) = 7520 \text{ W} \quad \text{supply}$$

$$P_{20V} = (20)(8i_Δ) = 1600 \text{ W} \quad \text{absorb}$$

$$P_{8\Omega} = (8i_D)(-ix) = 11200 \text{ w absorb}$$

$$P_{5\Omega} = (5i_D)(ix) = 1680 \text{ w absorb}$$

$$P_{18\Omega} = (18)(i_D)^2 = 1800 \text{ w dissipated}$$

$$P_{40\Omega} = (40)(i_D)^2 = 640 \text{ w dissipated}$$


$$\Sigma \text{ power supplied} = \Sigma \text{ power absorbed} + \Sigma \text{ Power dissipated}$$

Ch. 3

Homework Solutions

EE 231


3.6 c

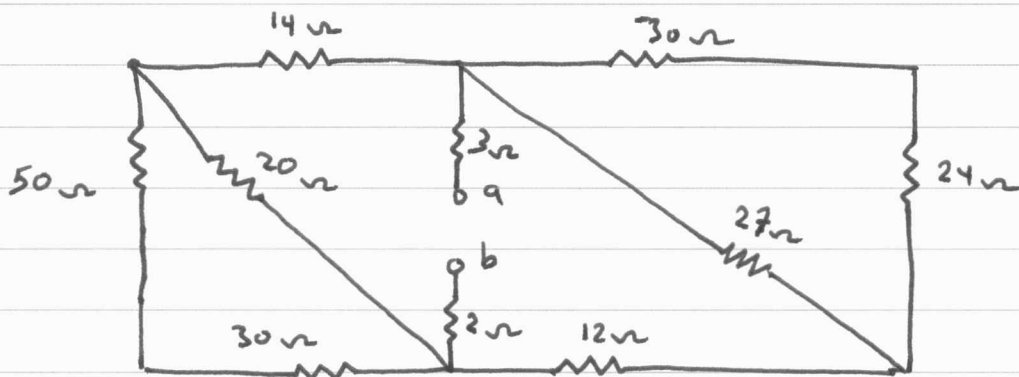

$$R_{eq} = 2 + 3 + \left[ \left( (30 + 24) \parallel 27 \right) + 12 \right] \parallel \left( 14 + (50 + 30) \parallel 20 \right)$$

$$R_{eq} = 20 \Omega$$

3.11

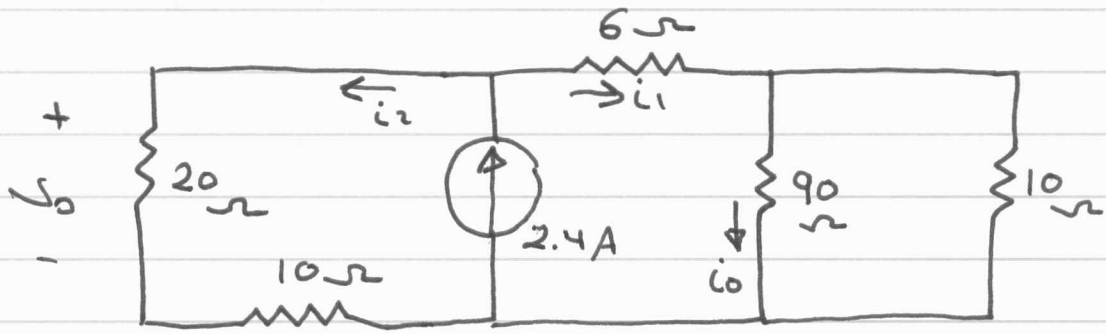

$$i_1 = \frac{(20+10)}{(20+10) + (6+90\parallel 10)} (2.4A)$$

$$i_1 = 1.6A$$

$$i_2 = 2.4A - 1.6A = 0.8A$$

$$i_0 = \left(\frac{10}{10+90}\right)(1.6A) = 0.16A$$


$$V_0 = 20 i_2 = 16V$$

$$V_{2.4A} = (20+10) i_2 = 24V$$

$$P_{2.4A} = (24)(2.4) = 57.6W \text{ (supply)}$$

$$P_{6\Omega} = 6 i_1^2 = 15.36W \text{ (dissipate)}$$


3.14

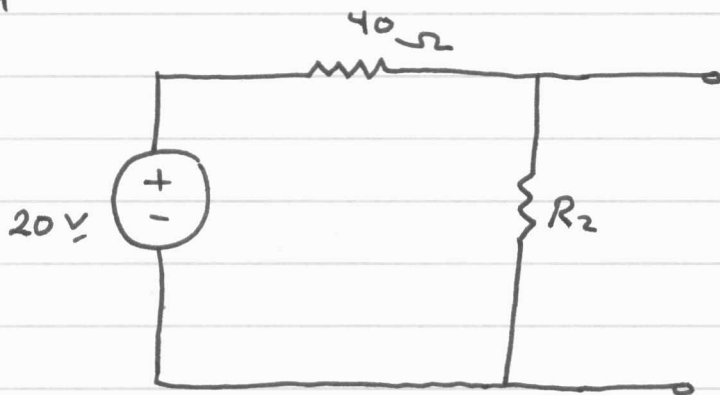

$$4 = \frac{R_2}{R_2 + 40} (20) \rightarrow R_2 = 10\Omega$$

$$3 = \frac{R_2 \parallel R_L}{R_2 \parallel R_L + 40} (20) \rightarrow R_L = 24\Omega$$

3.25

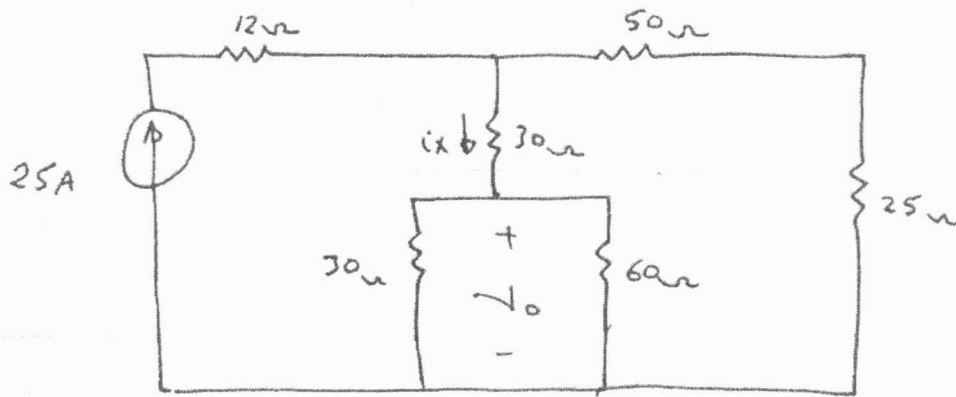


$$i_x = 25 \frac{75}{75 + 30 + 60 \parallel 30} = 15 \text{ A}$$

$$V_o = i_x (30 \parallel 60) = 300 \text{ V}$$

$$V_s = (12)(25) + 30 i_x + V_o = 1050 \text{ V}$$

3.26

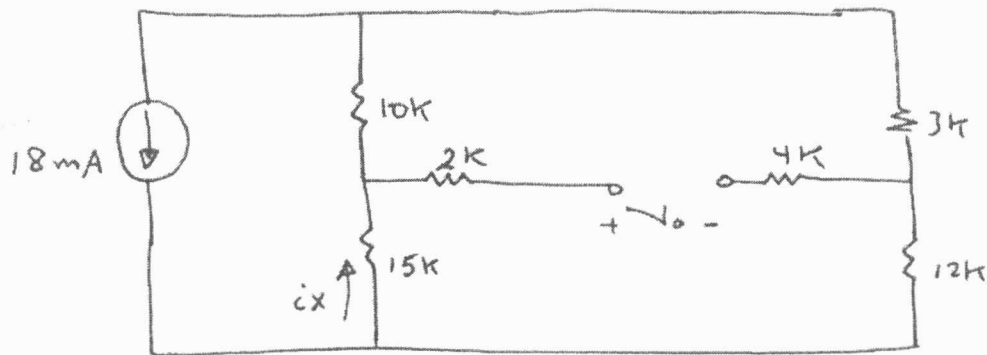


$$i_x = (18 \text{ mA}) \frac{15}{15 + 25} = 6.75 \text{ mA}$$


$$V_o = - (15 \text{ k}) i_x + (12 \text{ k})(18 - i_x)$$

$$V_o = 33.75 \text{ V}$$

3.49

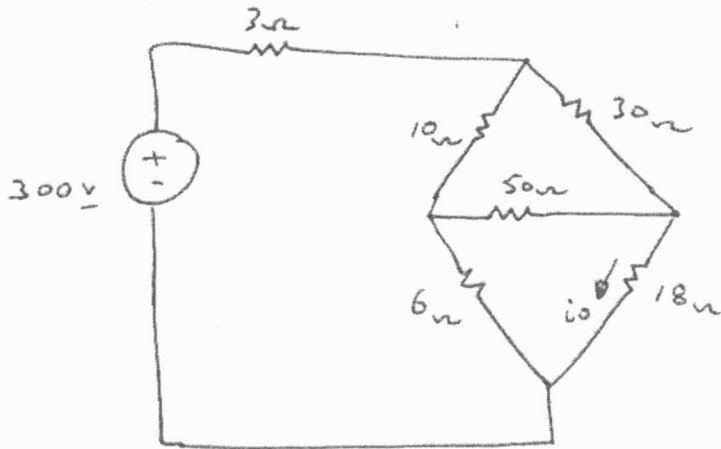

$\Delta$ -Y Transformation

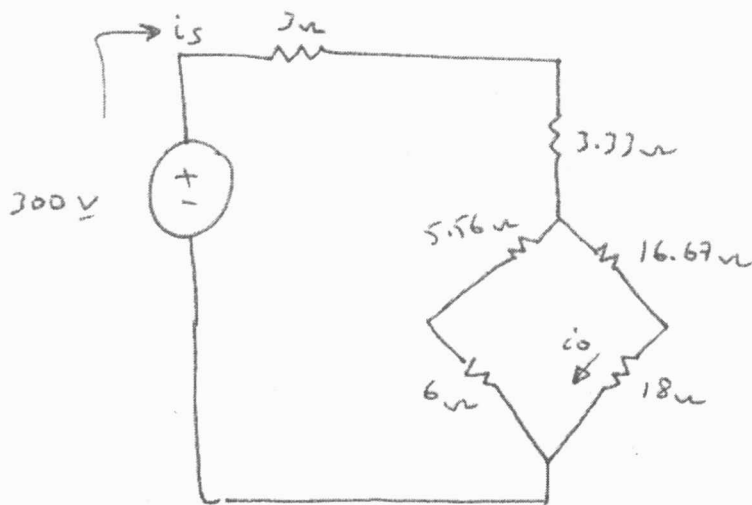


$$i_s = \frac{300}{3 + 3.33 + (5.56 + 6) \parallel (18 + 16.67)} = 20 \text{ A}$$

$$i_o = 20 \frac{11.56}{11.56 + 34.67} = 5 \text{ A}$$



$$P_{18\Omega} = (5)^2 \cdot 18 = 450 \text{ dissipated}$$



3.54

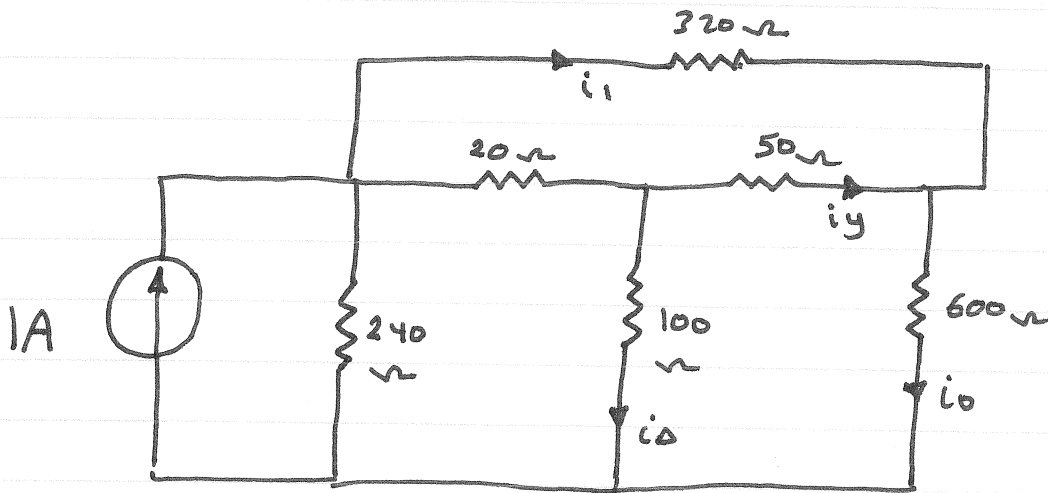

Y-Δ Transformation

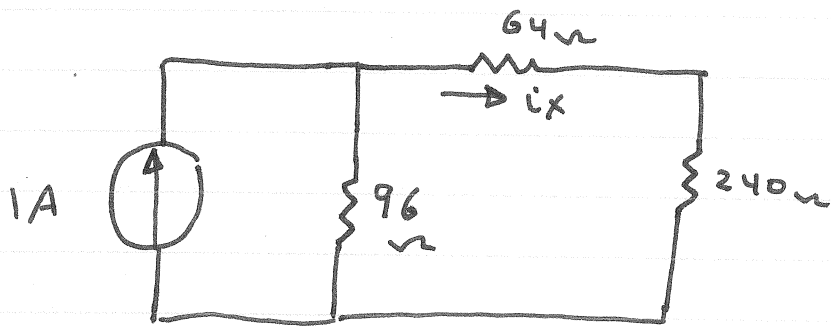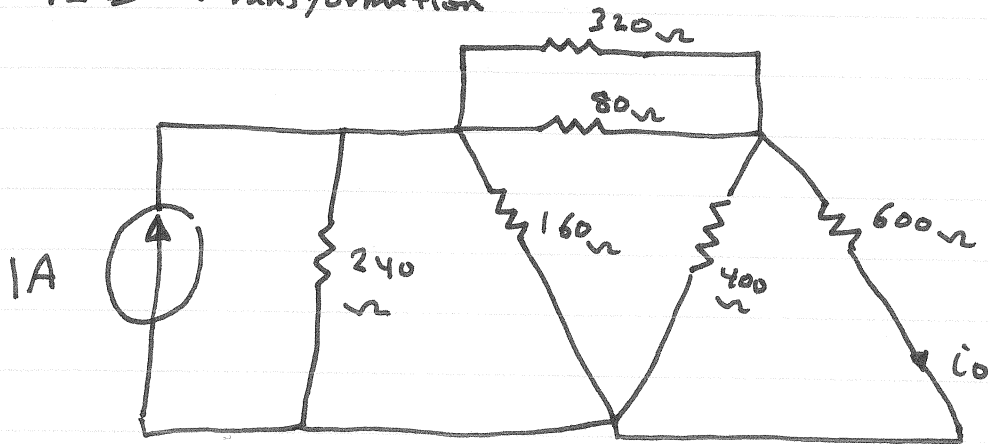

$$i_X = 1A \frac{96}{96+304} = 0.24A$$

$$i_1 = \frac{80}{80+320} i_X = 0.048A$$

$$i_O = \frac{400}{400+600} i_X = 0.096A$$

$$i_Y = i_O - i_1 = 0.048A$$

$$i_D = \frac{50i_Y + 600i_O}{100} = 0.6A$$