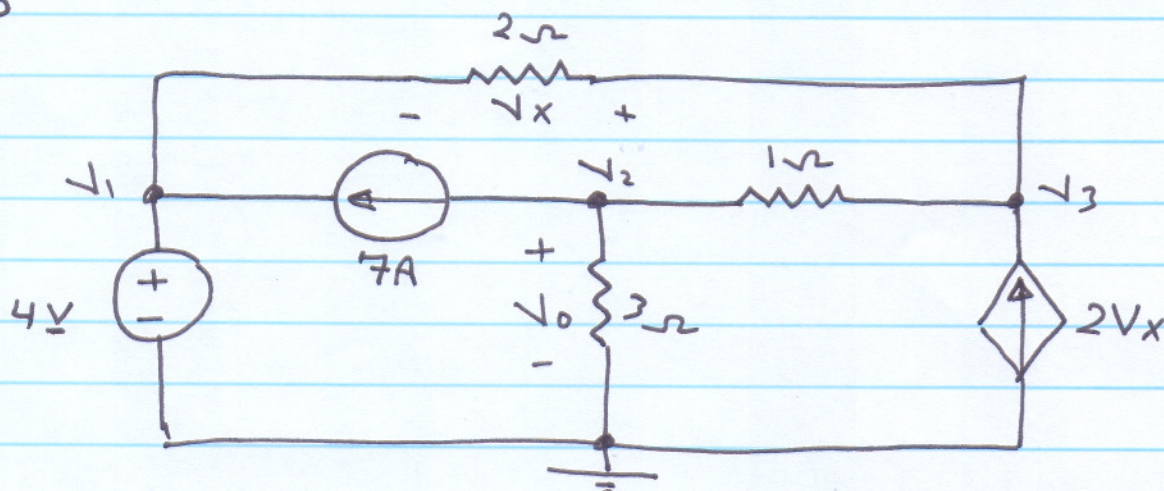


4.25



$$v_1 = 4$$

Constraint equation

$$-7 = \left(1 + \frac{1}{3}\right)v_2 - v_3$$

$$2V_x = -\frac{1}{2}v_1 - v_2 + \left(1 + \frac{1}{2}\right)v_3$$


$$v_x = v_3 - v_1$$

Solving

$$v_0 = v_2 = 1.5 \text{ V}$$



4.28

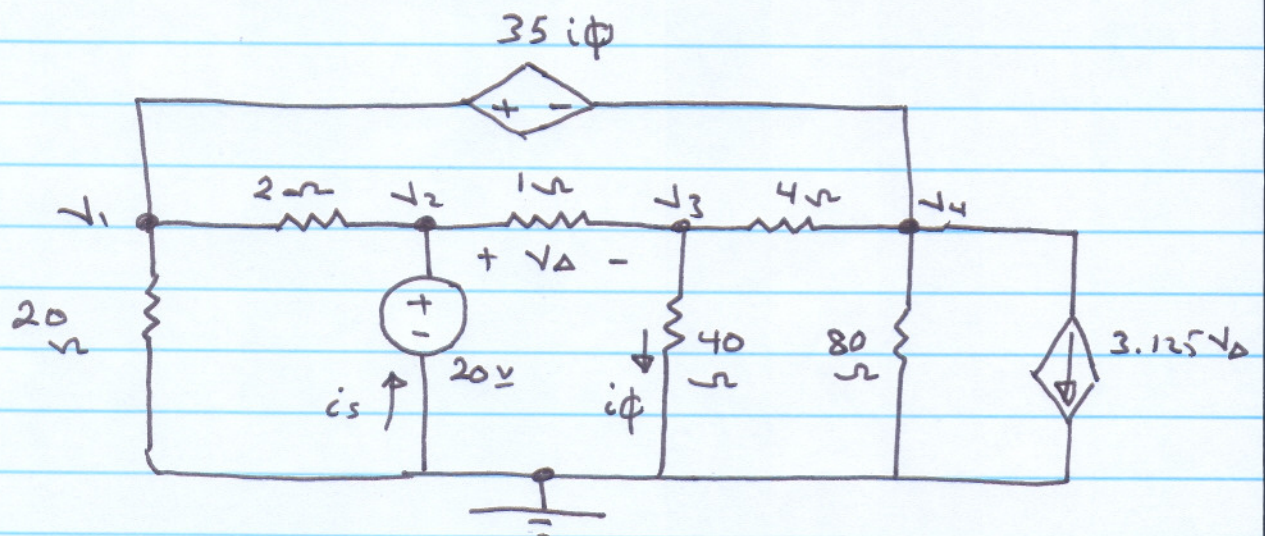

$$v_2 = 20 \quad \text{Constrain equation}$$

$$v_1 - v_4 = 35i\phi \quad \text{Constrain equation}$$

$$i\phi = \frac{v_3}{40}$$

$$0 = -v_2 + \left(1 + \frac{1}{4} + \frac{1}{40}\right)v_3 - \frac{1}{4}v_4$$

$$-3.125v_\Delta = \left(\frac{1}{2} + \frac{1}{20}\right)v_1 - \frac{1}{2}v_2 - \frac{1}{4}v_3 + \left(\frac{1}{4} + \frac{1}{80}\right)v_4$$

$$v_\Delta = v_2 - v_3$$


Solving:

$$v_1 = -20.25 \text{ V} ; \quad v_3 = 10 \text{ V} , \quad \text{and} \quad v_4 = -29 \text{ V}$$

$$i_s = \frac{v_2 - v_1}{2} + \frac{v_2 - v_3}{1} = 30.125 \text{ A}$$

$$P_{20\text{V}} = 20i_s = 602.5 \text{ Watt Supply}$$

4.42

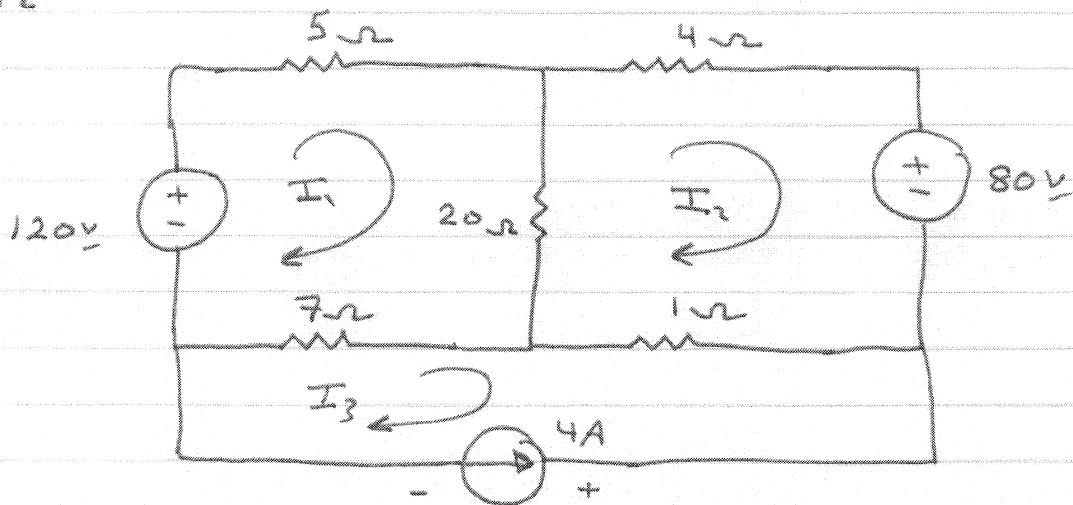

$$I_3 = -4A \quad \text{Constraint equation}$$

$$120 = 32 I_1 - 20 I_2 - 7 I_3$$

$$-80 = -20 I_1 + 25 I_2 - I_3$$

Solving:

$$I_1 = 1.55 A, \text{ and } I_2 = -2.12 A$$

$$V_{4A} = 1(I_2 - I_3) + 7(I_1 - I_3) = 40.73 \text{ V}$$

$$P_{4A} = 162.92 \text{ W (Supply)}$$

$$P_{120V} = (120)(I_1) = 186 \text{ Watt Supply}$$


$$P_{80V} = (80)(I_2) = 169.6 \text{ Watt Supply}$$

$$\Sigma P_{\text{supply}} = 518.52 \text{ Watt.}$$


$$\begin{aligned} \Sigma P_{\text{resistances}} &= 5(1.55)^2 + 4(2.12)^2 + 20(3.67)^2 + 7(5.55)^2 + 1(1.88)^2 \\ &= 518.52 \text{ Watt (dissipated)} \end{aligned}$$

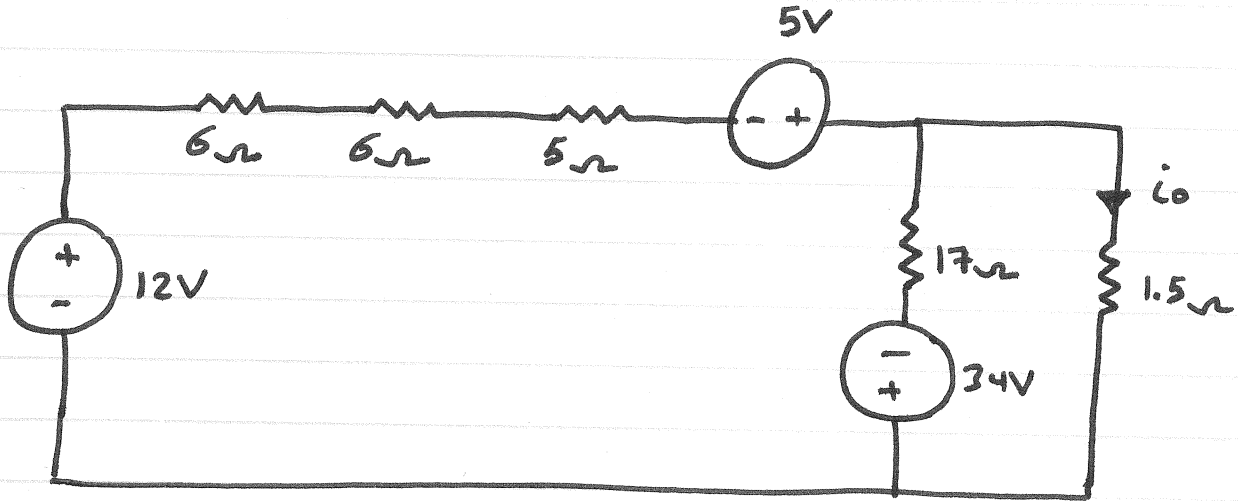4.60

Applying source transformation to both current sources yields:



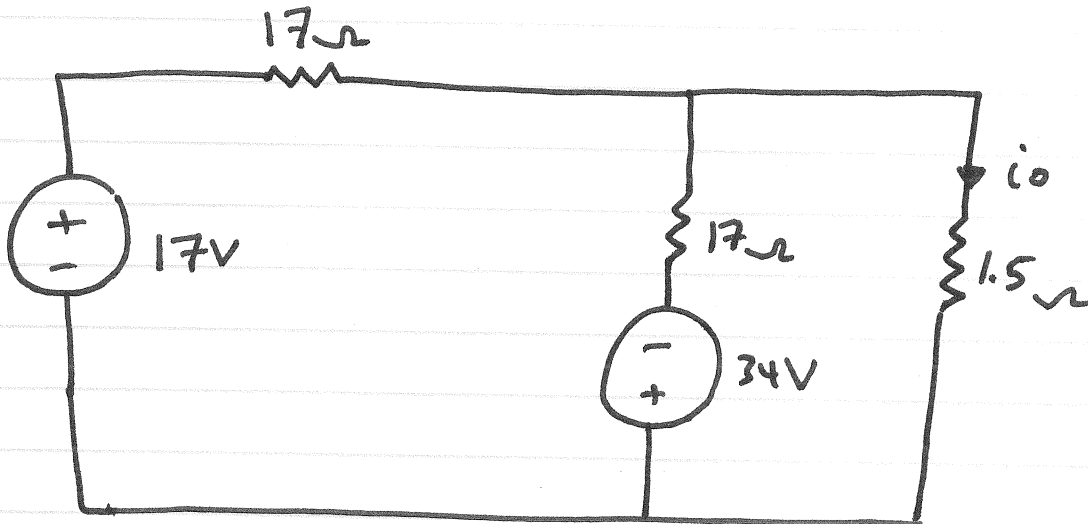
Combining the 12V and 5V into one source and adding the 3 resistors ( $6\Omega$ ,  $6\Omega$ , and  $5\Omega$ ) in series



Now source transformation for both voltage sources



4.42

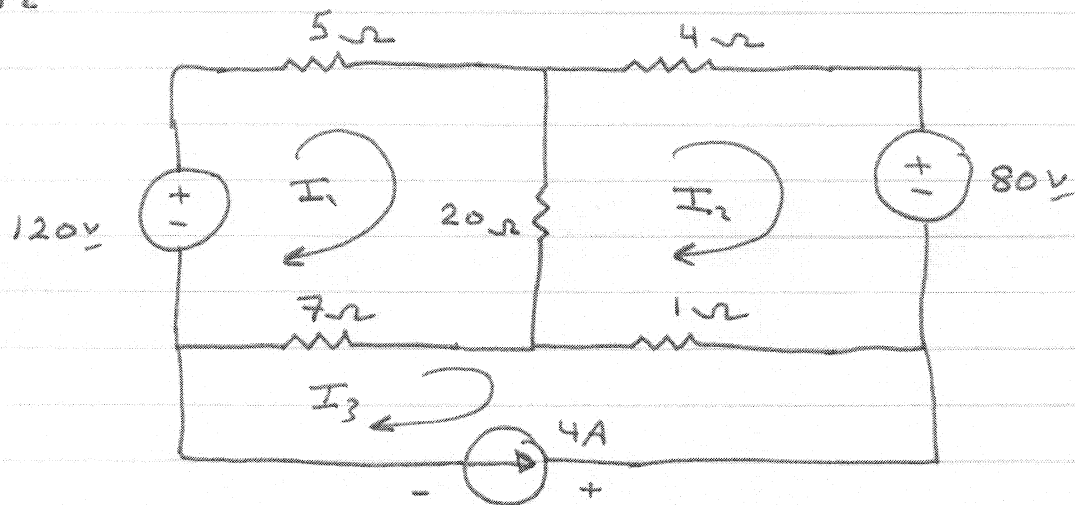

$$I_3 = -4A \quad \text{Constraint equation}$$

$$120 = 32 I_1 - 20 I_2 - 7 I_3$$

$$-80 = -20 I_1 + 25 I_2 - I_3$$

Solving:

$$I_1 = 1.55 A, \text{ and } I_2 = -2.12 A$$

$$V_{4A} = 1(I_2 - I_3) + 7(I_1 - I_3) = 40.73 \text{ V}$$


$$P_{4A} = 162.92 \text{ W (Supply)}$$

$$P_{120V} = (120)(I_1) = 186 \text{ Watt Supply}$$


$$P_{80V} = (80)(I_2) = 169.6 \text{ Watt Supply}$$

$$\Sigma P_{\text{supply}} = 518.52 \text{ Watt}$$
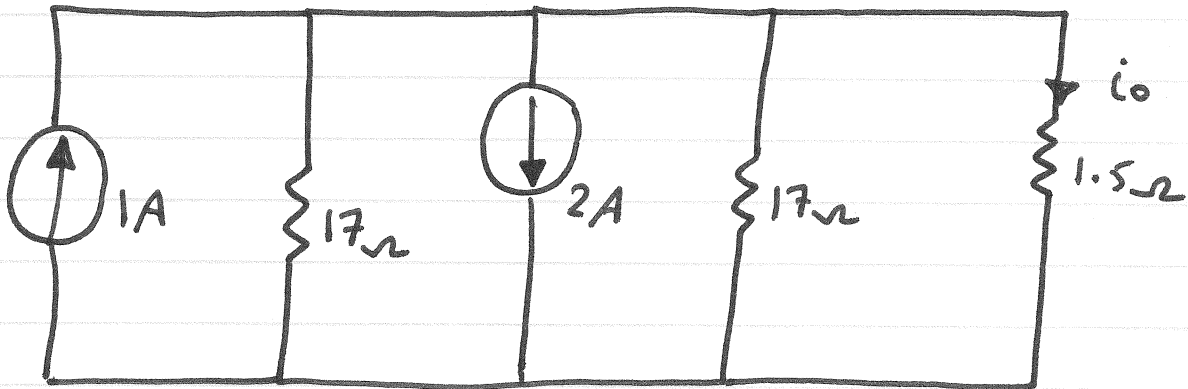
$$\begin{aligned} \Sigma P_{\text{resistances}} &= 5(1.55)^2 + 4(2.12)^2 + 20(3.67)^2 + 7(5.55)^2 + 1(1.88)^2 \\ &= 518.52 \text{ Watt (dissipated)} \end{aligned}$$



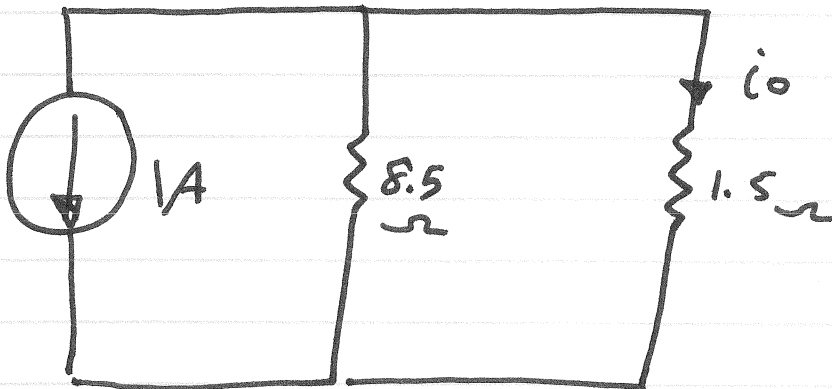Combining 1A, 2A sources and the  
 $17\Omega$ ,  $17\Omega$  resistors




$$i_o = - \frac{8.5}{8.5 + 1.5} 1A$$

$$i_o = - 0.85A$$



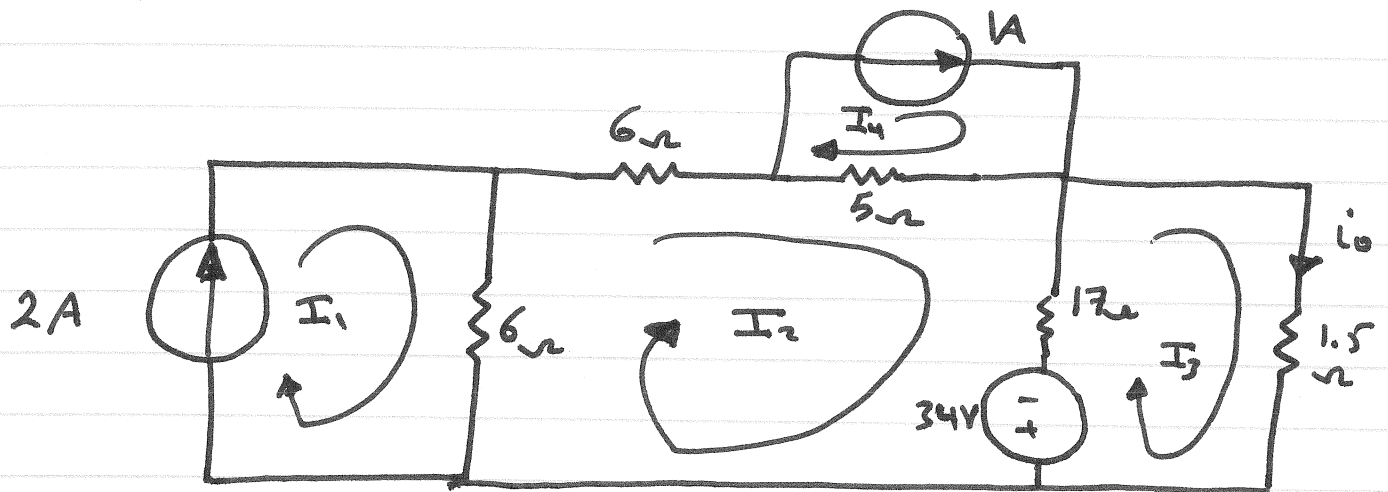b) Verification by mesh - Current method.



$$I_1 = 2A \quad \text{Constrain equation}$$

$$I_4 = 1A \quad \text{Constrain equation}$$

mesh 2 KVL :

$$34 = -6I_1 + 34I_2 - 17I_3 - 5I_4$$

mesh 3 KVL :

$$-34 = -17I_2 + 18.5I_3$$


Solving for  $I_2$  and  $I_3$  yields :

$$I_3 = -0.85A$$

$$I_2 = 1.075A$$

$$\therefore i_o = I_3 = -0.85A$$

4.67

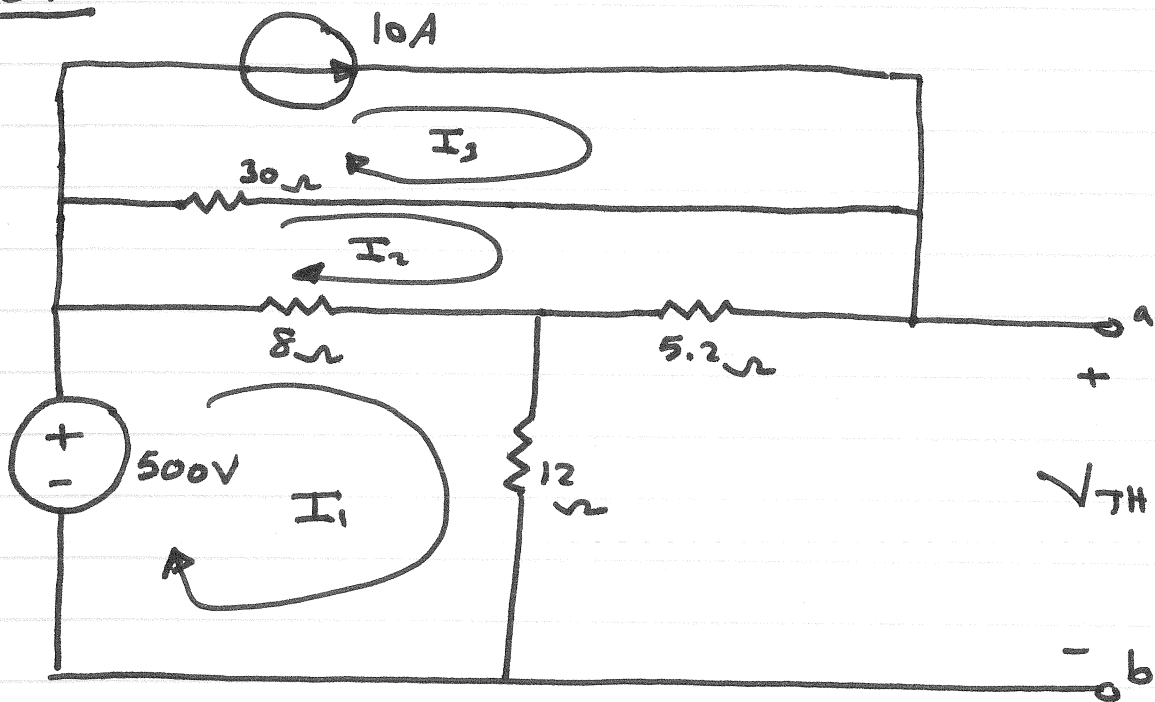

$$V_{TH} = (5.2\Omega) I_2 + (12\Omega) I_1$$

$$I_3 = 10A \quad \text{Constraint equation}$$

KVL for mesh 1 :

$$500 = 20 I_1 - 8 I_2$$

KVL for mesh 2 :

$$0 = 43.2 I_2 - 30 I_3 - 8 I_1$$

Solving for  $I_1$  and  $I_2$  yields :


$$I_1 = 30A$$

$$I_2 = 12.5A$$

$$\therefore V_{TH} = (5.2)(12.5) + (12)(30) = 425V$$




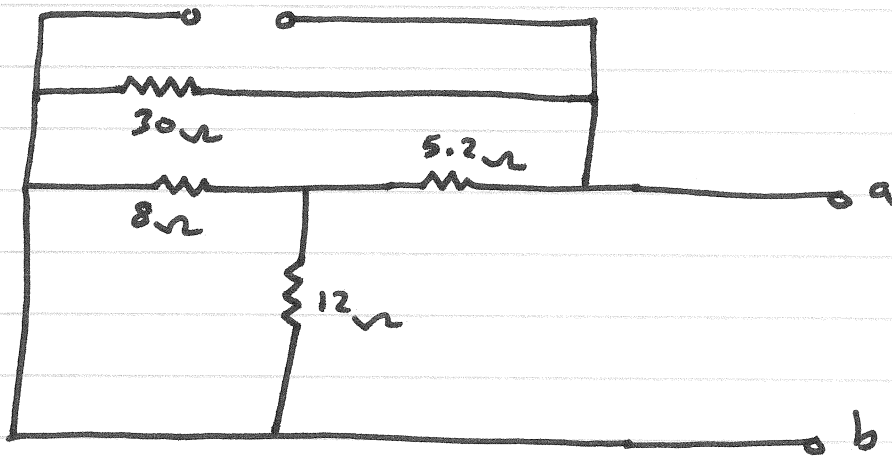To find  $R_{TH}$ , set all the independent sources to zero.




$$R_{TH} = 30\ \Omega \parallel \left( 5.2\ \Omega + 8\ \Omega \parallel 12\ \Omega \right)$$

$$R_{TH} = 7.5\ \Omega$$

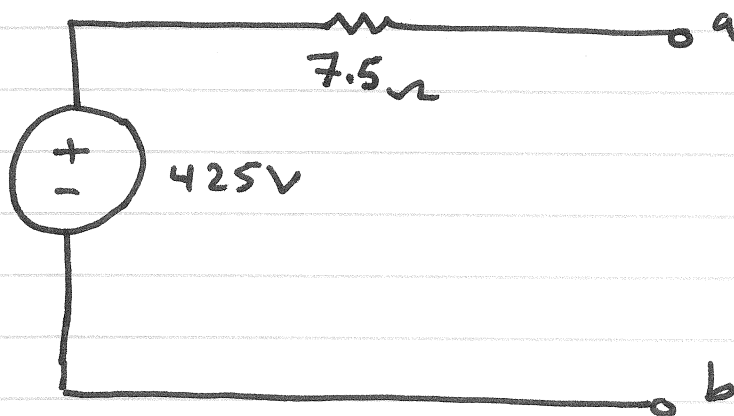

4.73

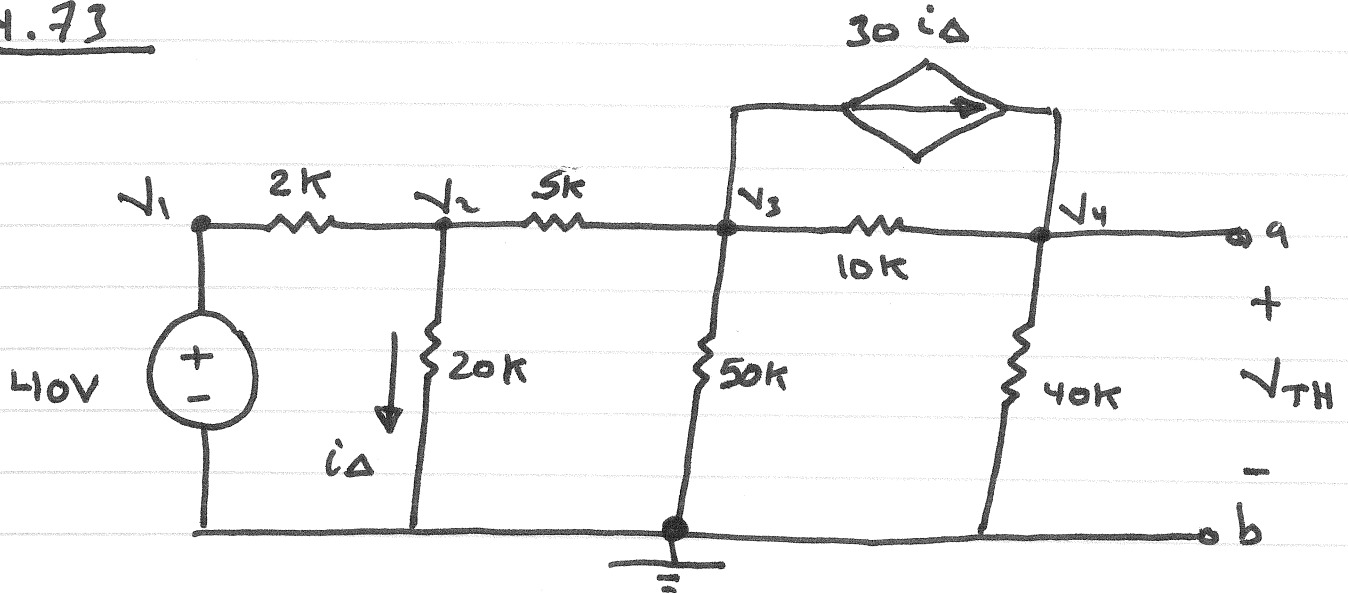

$$V_{TH} = V_4$$

KCL at node 2 :

$$\left( \frac{1}{2k} + \frac{1}{20k} + \frac{1}{5k} \right) V_2 - \frac{1}{2k} V_1 - \frac{1}{5k} V_3 = 0$$

KCL at node 3 :

$$-30 i_D = -\frac{1}{5k} V_2 + \left( \frac{1}{5k} + \frac{1}{50k} + \frac{1}{10k} \right) V_3 - \frac{1}{10k} V_4$$

$$i_D = \frac{V_2}{20k}$$

KCL at node 4 :

$$30 i_D = -\frac{1}{10k} V_3 + \left( \frac{1}{10k} + \frac{1}{40k} \right) V_4$$


$V_1 = 40V$  constrain equation

solving for  $V_4$

$$V_4 = 280V, \therefore V_{TH} = 280V$$



To find  $R_{TH} = \frac{V_{TH}}{I_N}$

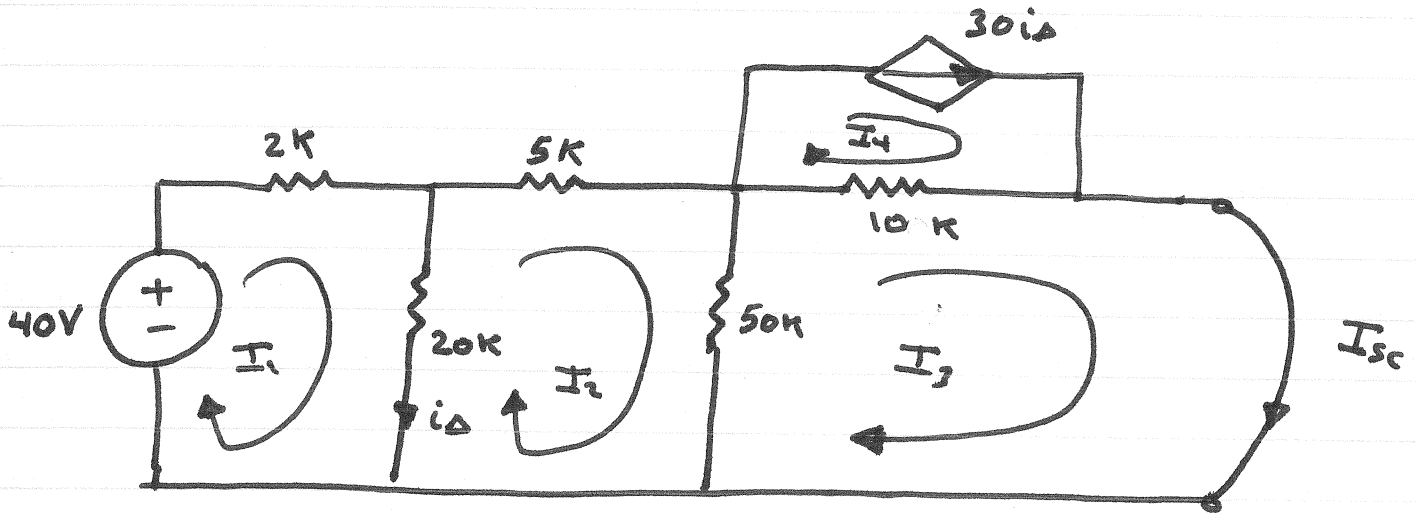

$$I_{sc} = I_N = I_3$$

KVL for mesh 1 :

$$40 = 22k I_1 - 20k I_2$$

KVL for mesh 2 ,

$$0 = -20k I_1 + 75k I_2 - 50k I_3$$

KVL for mesh 3 :

$$0 = -50k I_2 + 60k I_3 - 10k I_4$$


$$I_4 = 30 \text{ mA} \quad \text{Constraint equation}$$

$$i_{\Delta} = I_1 - I_2$$


Solving for  $I_3 = I_{sc} = I_N = 14 \text{ mA}$

$$\therefore R_{TH} = \frac{V_{TH}}{I_N} = 20k \Omega$$

4.88

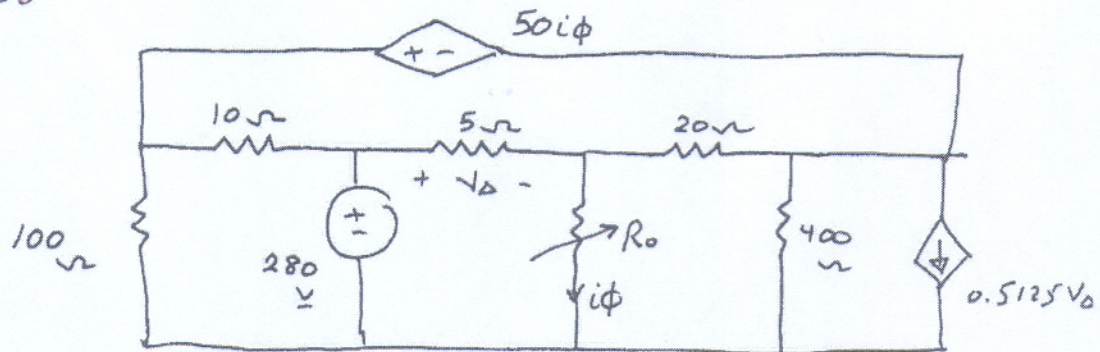

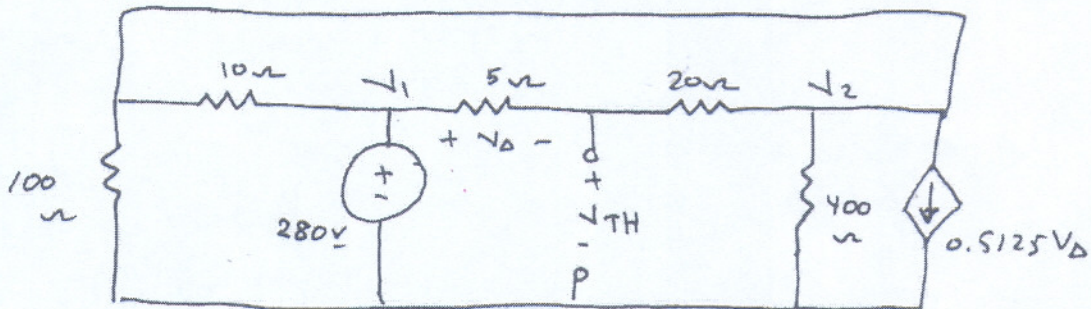1) To find  $V_{TH}$  ;  $i_{\phi} = 0 \rightarrow 50i_{\phi} = 0 \rightarrow$  Short Circuit



Supernode

$$V_2 \left( \frac{1}{100} + \frac{1}{10} + \frac{1}{400} + \frac{1}{25} \right) - \left( \frac{1}{10} + \frac{1}{25} \right) V_1 = -0.5125 V_{\Delta}$$

$$V_1 = 280 \text{ Constrain equation}$$


$$V_{\Delta} = \frac{5}{5+20} (V_1 - V_2)$$

$$\therefore V_2 = 210 \text{ V} ; V_{\Delta} = \frac{5}{25} (280 - 210) = 14 \text{ V}$$

$$V_{TH} = -V_{\Delta} + 280 = 266 \text{ V}$$



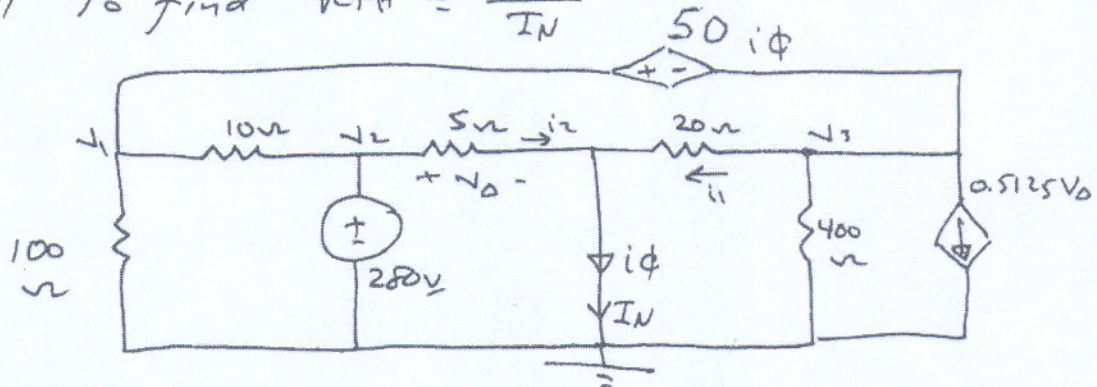2) To find  $R_{TH} = \frac{V_{TH}}{I_N}$



$$V_1 - V_3 = 50 i_\phi = 50 I_N$$

$$V_2 = 280V$$


Supernode equation

$$V_3 \left( \frac{1}{400} + \frac{1}{20} \right) + V_1 \left( \frac{1}{100} + \frac{1}{10} \right) - \frac{1}{10} V_2 = -0.5125 V_A$$

$$V_A = 280V \quad ; \quad V_3 = -968V$$

$$I_N = i_1 + i_2 = \frac{-968}{20} + \frac{280}{5} = 7.6 A$$

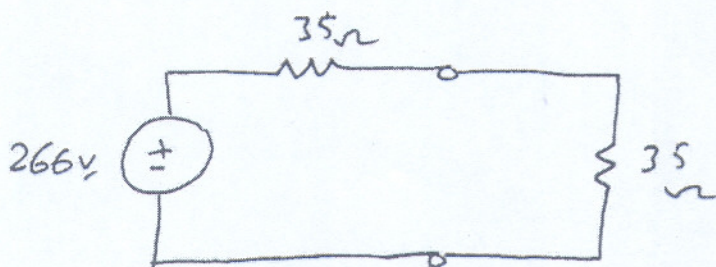
$$\therefore R_{TH} = \frac{266}{7.6} = 35 \Omega$$



$$P_{max} = \frac{V_{TH}^2}{4 R_{TH}} = 505.4 W$$



c)

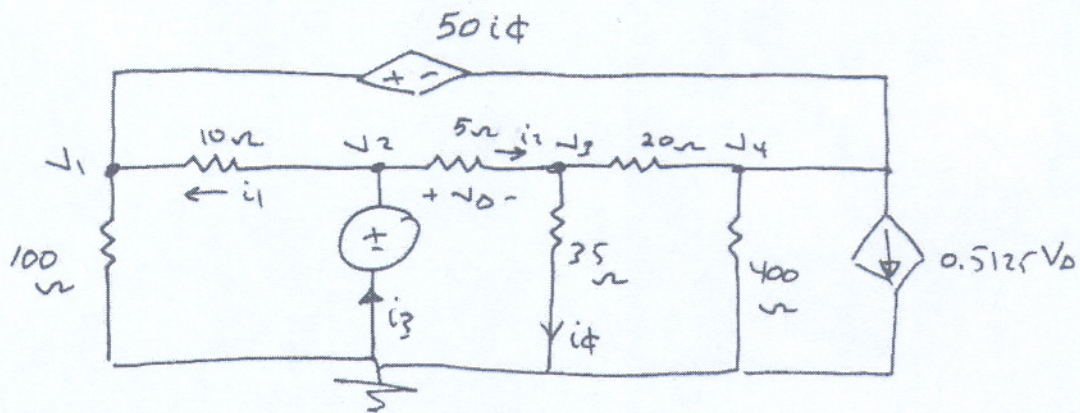

$$v_1 - v_4 = 50i_\phi \quad ; \quad i_\phi = \frac{v_3}{35}$$

$$v_2 = 280 \text{ V}$$

$$v_3 \left( \frac{1}{5} + \frac{1}{35} + \frac{1}{20} \right) - \frac{1}{5} v_2 - \frac{1}{20} v_4 = 0$$

Supernode

$$v_1 \left( \frac{1}{10} + \frac{1}{100} \right) + v_4 \left( \frac{1}{400} + \frac{1}{20} \right) - \frac{1}{10} v_2 - \frac{1}{20} v_3 = -0.5i_\phi \text{ V}$$

$$v_4 = v_2 - v_3 \quad ; \quad v_3 = 133 \text{ V}$$

$$\therefore v_1 = -189 \text{ V}$$

$$i_1 = \frac{280 - 189}{10} = 46.9 \text{ A}$$


$$i_2 = \frac{280 - 133}{5} = 29.4 \text{ A}$$

$$i_g = i_3 = i_1 + i_2 = 76.3 \text{ A}$$


$$P_{\downarrow} = (76.3)(280) = 21364 \text{ W}$$

Supply

4.92

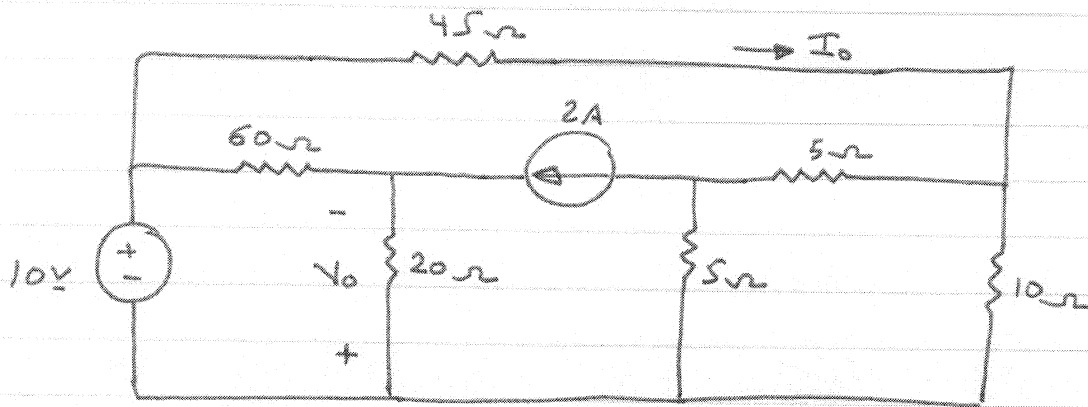

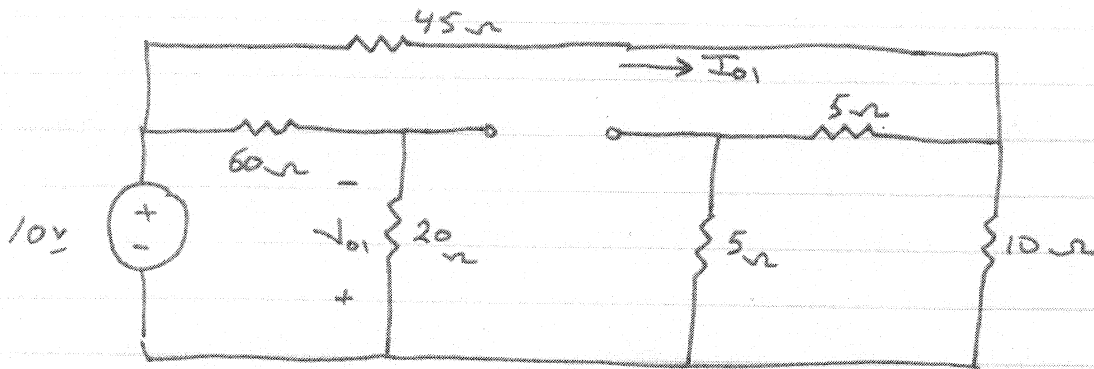1) let  $V_s$  on,  $I_s$  off (open circuit)




$$I_{01} = \frac{10}{45 + 10 \parallel (5+5)} = 0.2 \text{ A}$$

$$V_{01} = \frac{20}{20+60} (-10) = -2.5 \text{ V}$$



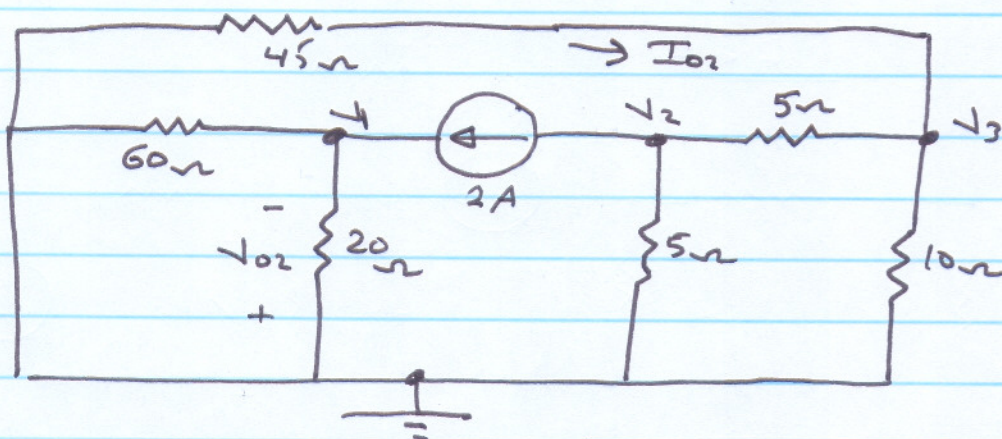2) let  $I_s$  on,  $V_s$  OFF (short circuit)



$$2 = \left(\frac{1}{20} + \frac{1}{60}\right) V_1 -$$

$$-2 = \left(\frac{1}{5} + \frac{1}{5}\right) V_2 - \frac{1}{5} V_3$$

$$0 = -\frac{1}{5} V_2 + \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{45}\right) V_3$$

Solving :

$$V_2 = -7.25, \quad V_3 = -4.5 \text{ V}, \quad \text{and } V_1 = 30 \text{ V}$$

$$V_{02} = -V_1 = -30 \text{ V}$$

$$I_{02} = -\frac{V_3}{45} = 0.1 \text{ A}$$

$$\therefore I_0 = I_{01} + I_{02} = 0.3 \text{ A}$$

$$V_0 = V_{01} + V_{02} = -32.5$$