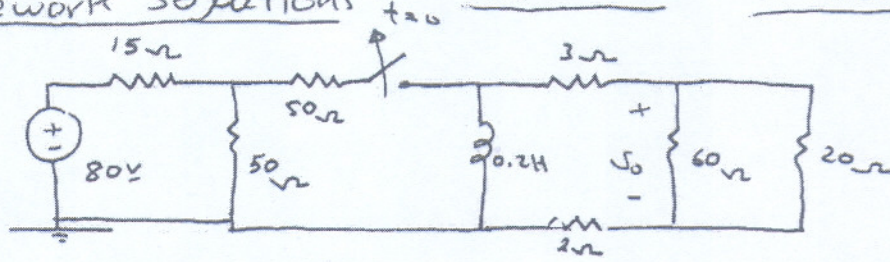


Homework Solutions


Ch. 7

ENEE 231

7.6



For $t < 0$

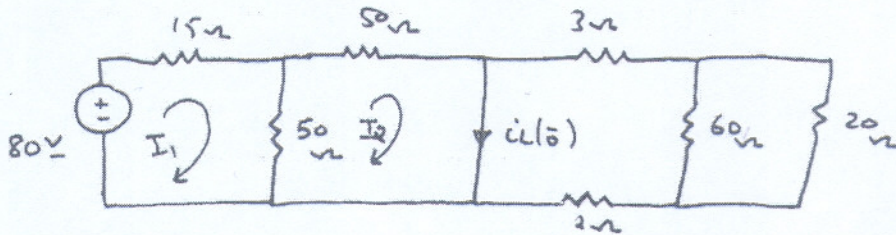


$$80 = 65 I_1 - 50 I_2$$

$$0 = -50 I_1 + 100 I_2$$


$$I_2 = 1 \text{ A} \rightarrow i_L(t) = 1 \text{ A}$$

For $t > 0$

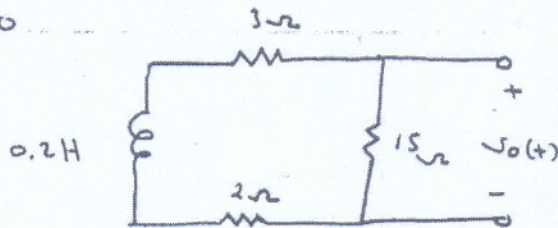

$$60\Omega \parallel 20\Omega = 15\Omega$$

at $t = 0^+$

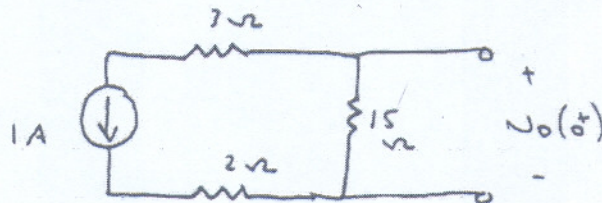

$$v_o(0^+) = -15 \text{ V}$$

at $t = \infty$

L is short

$$v_o(\infty) = 0$$


$$v_o(t) = v_o(\infty) + [v_o(0^+) - v_o(\infty)] e^{-t/\tau}$$

$$\tau = \frac{L}{R_{eq}} = \frac{0.2 \text{ H}}{3+2+15} = 0.01 \text{ s}$$


$$\therefore v_o(t) = -15 e^{-100t} \text{ V for } t > 0$$

Homework Solutions ch. 7 EE 231

7.11

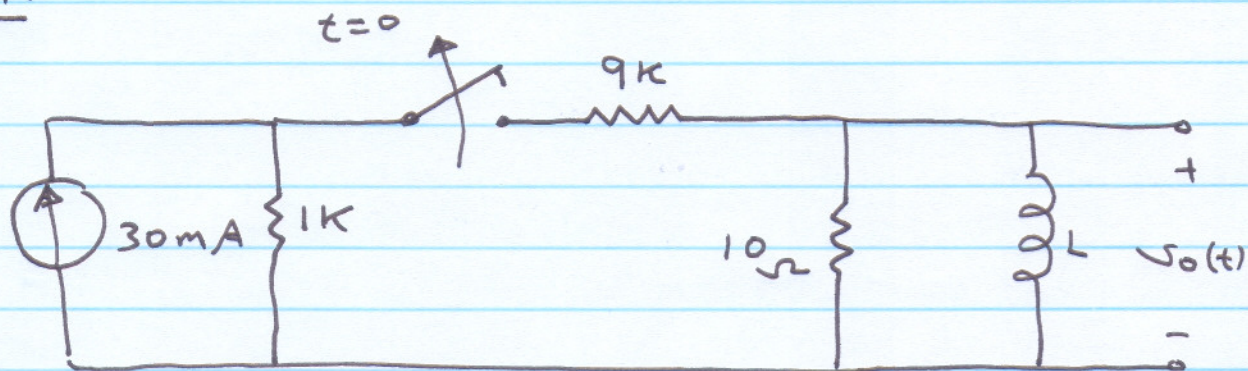


for $t < 0$

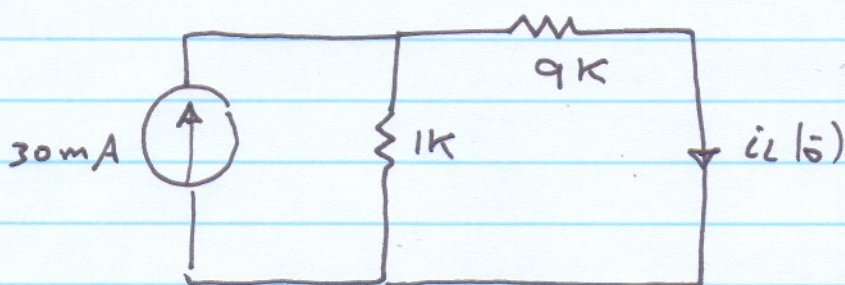

$$i_L(0^-) = \frac{1k}{1k+9k} (30mA) = 3mA$$

for $t > 0$

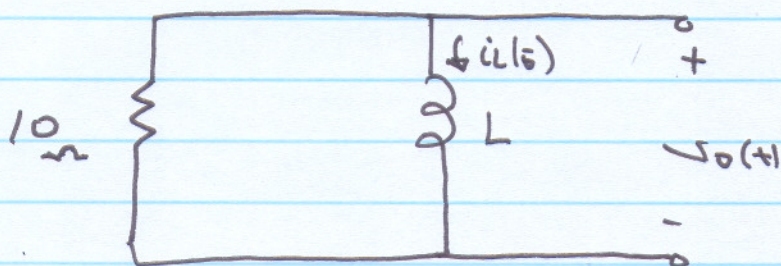

$$v_o(t) = v_o(0^+) e^{-t/\tau} \quad t > 0$$

$$v_o(1ms) = v_o(0^+) e^{\frac{-1 \times 10^{-3}}{\tau}} = 0.5 v_o(0^+)$$

$$\therefore 0.5 = e^{\frac{-1 \times 10^{-3}}{\tau}}$$

$$\therefore \tau = \frac{1 \times 10^{-3}}{\ln 2} = 1.443ms$$

$$\tau = \frac{L}{R} = \frac{L}{10}$$

$$\therefore L = 14.43 \text{ mH}$$

$$b) v_o(0^+) = -10 i_L(0^+) = -10 i_L(0) = -30 \text{ mV}$$

$$\therefore v_o(t) = -0.03 e^{-t/\tau} \text{ V for } t > 0$$

$$p_{10\Omega} = \frac{v_o^2(t)}{10} = 9 \times 10^{-5} e^{-2t/\tau}$$

$$W_{10\Omega}(1\text{ms}) = \int_0^{10^{-3}} 9 \times 10^{-5} e^{-\frac{2t}{\tau}} dt$$

$$W_{10\Omega}(1\text{ms}) = (4.5 \tau)(10^{-5}) \left(1 - e^{-2\left(\frac{0.001}{\tau}\right)} \right)$$


$$W_{10\Omega}(1\text{ms}) = 48.69 \text{ nJ}$$

$$W_L(0) = \frac{1}{2} L i_L^2(0)$$

$$W_L(0) = 64.92 \text{ nJ}$$

$$\begin{aligned} \% \text{ dissipated in } 1\text{ms} &= \frac{48.69}{64.92} \times 100\% \\ &= 75\% \end{aligned}$$


7.23

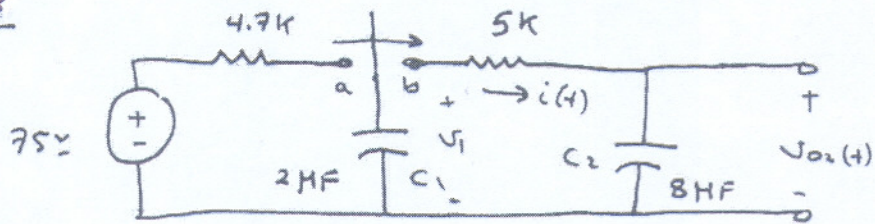


For $t < 0$

$$V_{C1}(0^-) = 75 \text{ V}, \quad V_{C2}(0^-) = 0$$

For $t > 0$

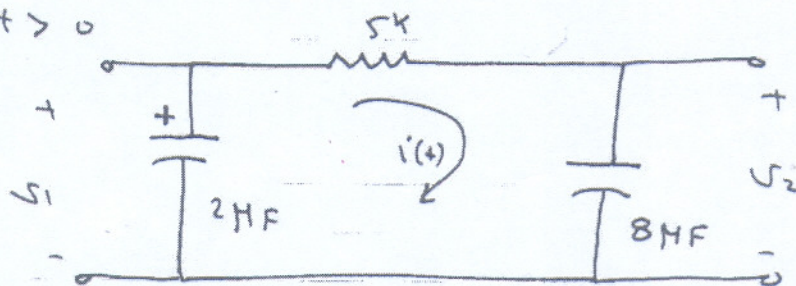

at $t = 0^+$

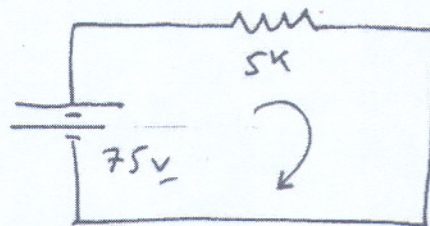

$$i(0^+) = \frac{75 \text{ V}}{5 \text{ k}} = 15 \text{ mA}$$

$$V_{C1}(0^+) = 75 \text{ V}, \quad V_{C2}(0^+) = 0$$

at $t = \infty$

$$i(\infty) = 0$$

$$\therefore i(t) = 15 e^{-t/\tau} \quad t > 0$$

$$\tau = R C_{eq} = (5k) \left(\frac{(2M)(8M)}{2M+8M} \right) = 8ms$$

$$v_2(t) = \frac{1}{C_2} \int_0^t i(t) dt = \frac{1}{8M} \int_0^t 15 e^{-t/\tau} dt$$

$$v_2(t) = 15 - 15 e^{-t/\tau} \quad t \geq 0$$

$$v_1(t) = v_1(0) - \frac{1}{C_1} \int_0^t i(t) dt$$

$$v_1(t) = 15 + 60 e^{-t/\tau} \quad t \geq 0$$

b) $W_i = \frac{1}{2} C_1 v_{c1}(0)^2 = \left(\frac{1}{2}\right)(2 \times 10^6)(75)^2$

$$W_i = 5625 \mu J$$

c) The total energy dissipated in the 5k resistor

$$W_R = \int_0^{\infty} P(t) dt = \int_0^{\infty} i^2(t) R dt$$

$$= \int_0^{\infty} R (15 \times 10^3)^2 e^{-2t/\tau} dt$$

$$W_R = (15 \times 10^3)^2 \left. \frac{e^{-2t/\tau} \cdot R}{-2/\tau} \right|_0^{\infty} = 4500 \mu J$$

∴ The energy trapped in the circuit = W_t

$$W_t = W_1 - W_2$$
$$= 5625 - 4500$$

$$W_t = 1125 \text{ MJ}$$

or second method

$$V_{c1}(\infty) = 15 \text{ V}$$

$$V_{c2}(\infty) = 15 \text{ V}$$


$$W_{c1}(\infty) = \left(\frac{1}{2}\right)(2)(10^6)(15)^2 = 225 \text{ MJ}$$

$$W_{c2}(\infty) = \left(\frac{1}{2}\right)(8)(10^6)(15)^2 = 900 \text{ MJ}$$


∴

$$W_t = W_{c1}(\infty) + W_{c2}(\infty)$$
$$= 1125 \text{ MJ.}$$

7.42

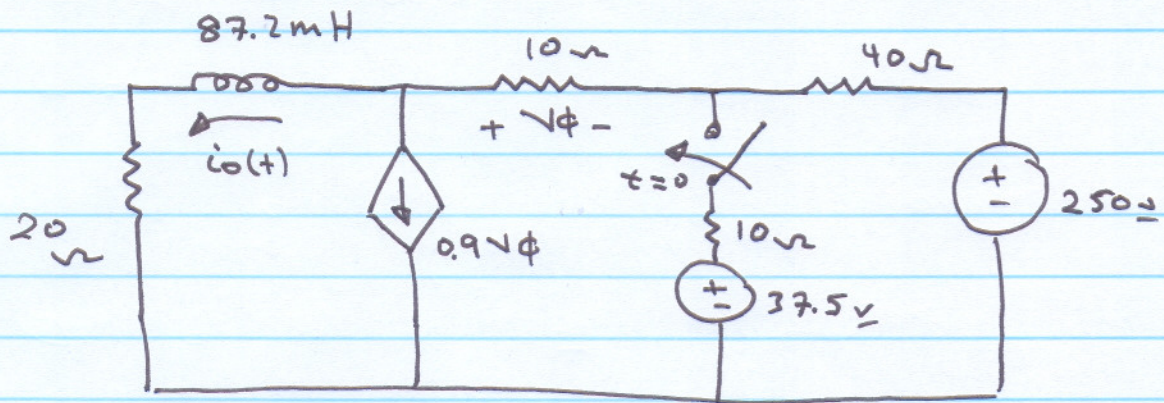

for $t < 0$

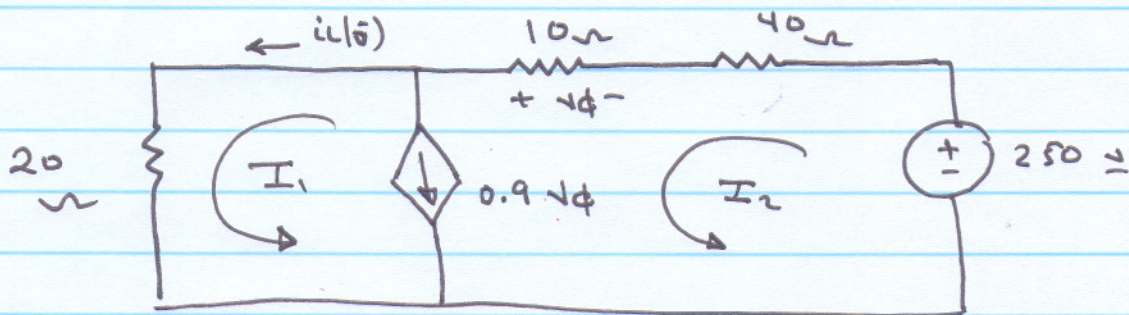

$$I_2 - I_1 = 0.9 \sqrt{\phi}$$

Constraint equation

$$\sqrt{\phi} = -10 I_2$$

$$\therefore 10 I_2 - I_1 = 0$$


$$250 = 20 I_1 + 50 I_2$$

Supermesh

$$\therefore I_1 = 10 \text{ A}$$


$$\therefore i(t) = I_1 = 10 \text{ A}$$

for $t > 0$

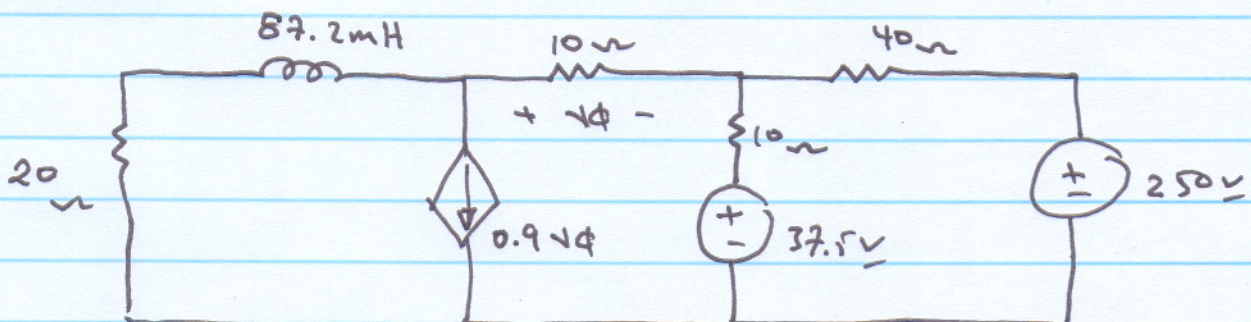

$$i_0(t) = i_0(\infty) + [i_0(0^+) - i_0(\infty)] e^{-t/\tau}$$

at $t = \infty$

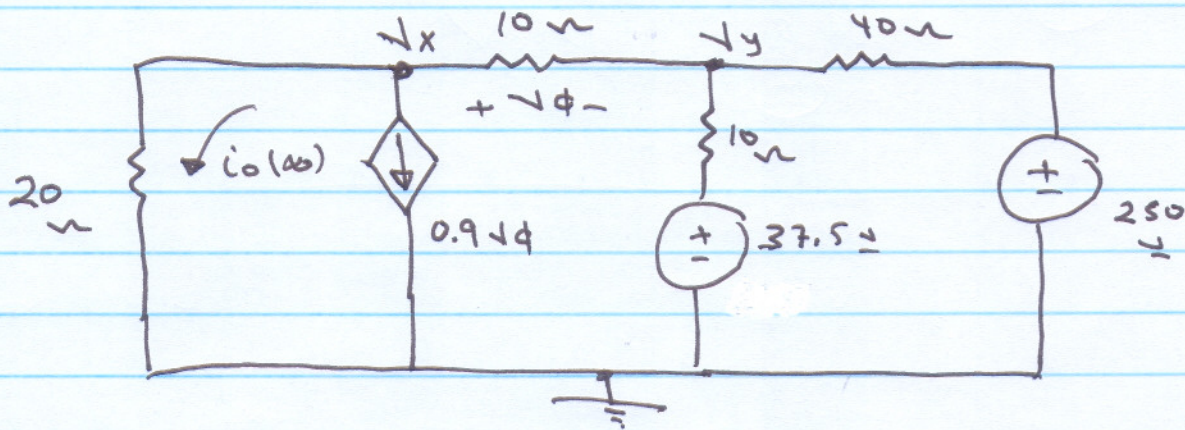

$$-0.9V_\phi = \left(\frac{1}{20} + \frac{1}{10}\right)V_x - \frac{1}{10}V_y$$

$$V_\phi = V_x - V_y$$

$$\frac{V_y - V_x}{10} + \frac{V_y - 37.5}{10} + \frac{V_y - 250}{40} = 0$$


$$\therefore V_x = 73.39 \text{ V}$$

$$i_0(\infty) = \frac{V_x}{20} = 3.67 \text{ A}$$

$$i_0(0^+) = i_0(0^-) = 10 \text{ A}$$

To find R_{TH}

$$R_{TH} = \frac{V_{TH}}{I_N}$$

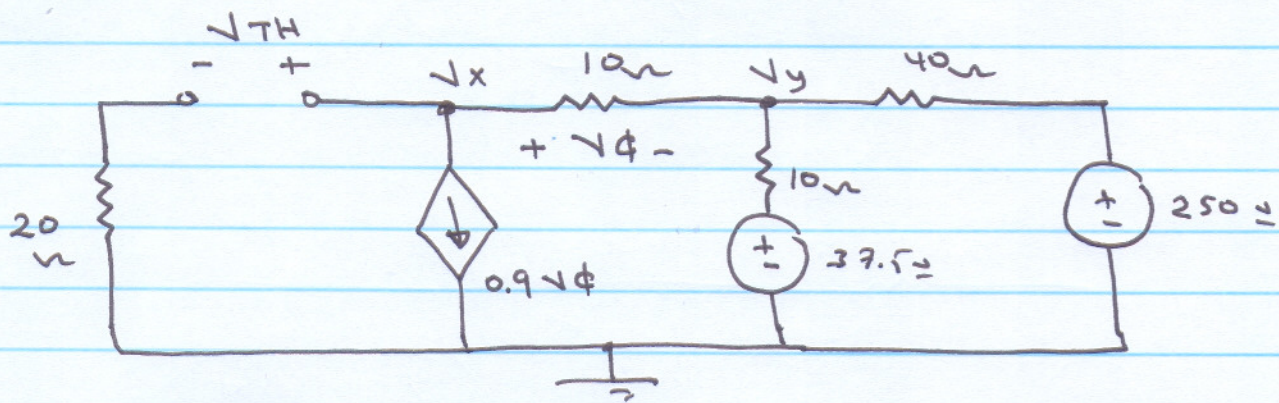

$$V_{TH} = V_x$$

$$-0.9 V_\phi = \frac{1}{10} V_x - \frac{1}{10} V_y$$

$$V_\phi = V_x - V_y$$

$$\frac{V_y - V_x}{10} + \frac{V_y - 37.5}{10} + \frac{V_y - 250}{40} = 0$$

$$\therefore V_{TH} = V_x = 80 \text{ V}$$

$$I_N = 3.67 \text{ A}$$


$$R_{TH} = \frac{V_{TH}}{I_N} = 21.8 \text{ } \Omega$$

$$\tau = \frac{L}{R_{TH}} = 4 \text{ ms}$$


$$i_o(t) = \left[3.67 + (10 - 3.67) e^{-2500t} \right] \text{ A for } t > 0$$

$$i_o(t) = 3.67 + 6.33 e^{-2500t} \text{ A for } t > 0$$

7.54

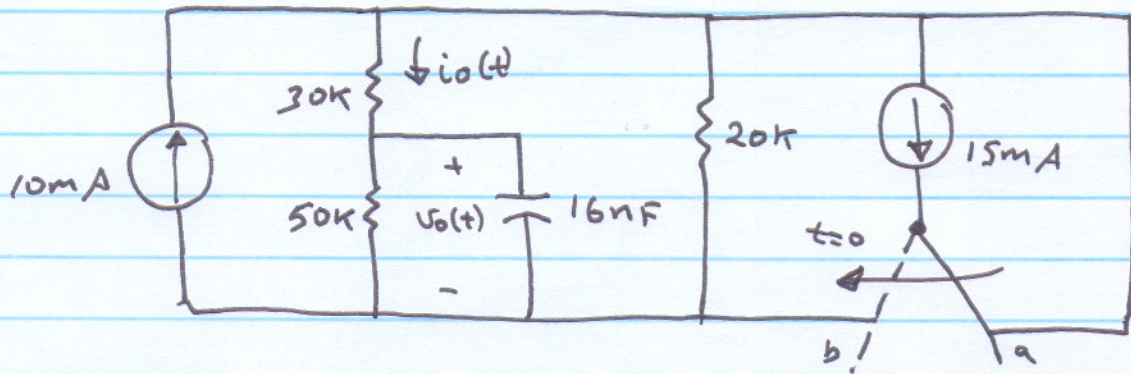


for $t < 0$

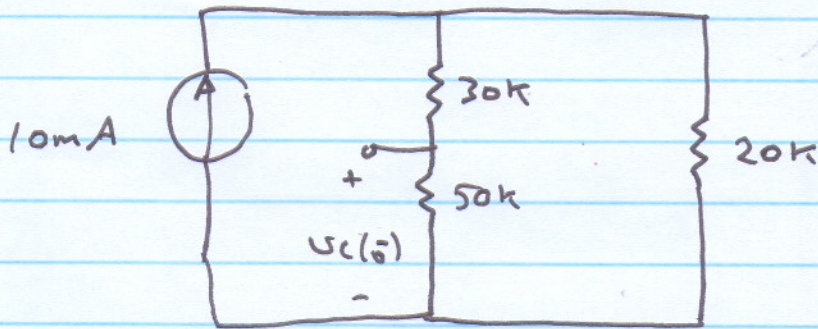

$$v_c(t) = (50k) \left(\frac{20k}{20k + 80k} \right) (10mA) = 100 \text{ mV}$$


at $t = \infty$

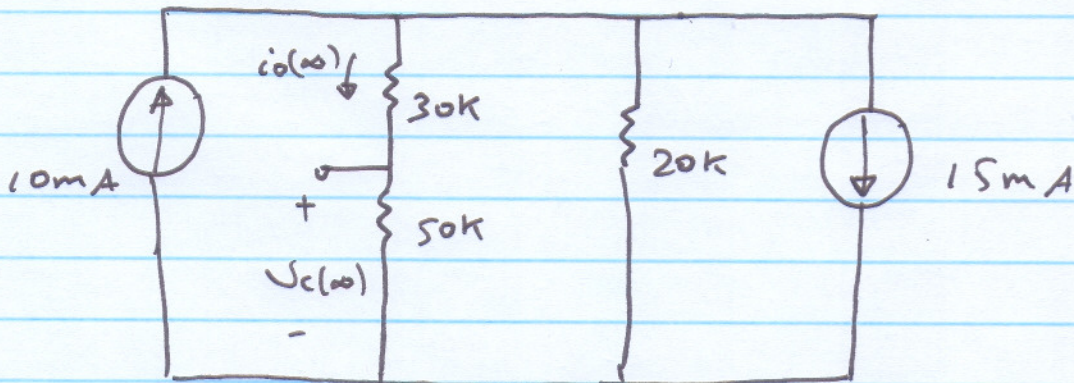

$$v_c(\infty) = (10mA - 15mA) \left(\frac{20k}{20k + 80k} \right) (50k) = -50 \text{ mV}$$

$$i_o(\infty) = (10\text{mA} - 15\text{mA}) \left(\frac{20\text{k}}{20\text{k} + 80\text{k}} \right) = -1\text{mA}$$

at $t = 0^+$

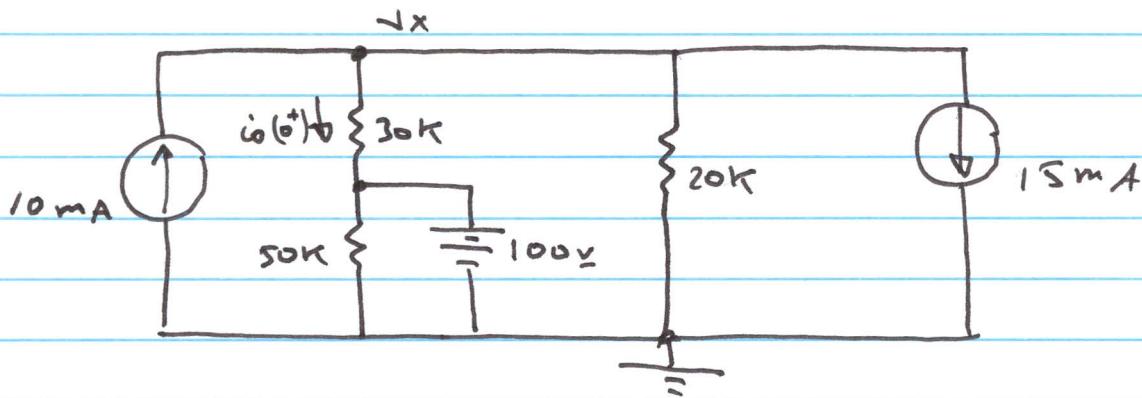

$$v_o(0^+) = 100 \text{ V}$$

$$10\text{mA} = \frac{v_x - 100}{30\text{k}} + 15\text{mA} + \frac{v_x}{20\text{k}}$$

$$v_x = -20 \text{ V}$$

$$i_o(0^+) = \frac{v_x - v_o(0^+)}{30\text{k}} = -4\text{mA}$$

$$\tau = R_{TH} C$$

$$R_{TH} = (30\text{k} + 20\text{k}) \parallel 50\text{k} = 25\text{k}$$

$$\tau = 0.4\text{ms}$$

$$i_o(t) = i_o(\infty) + (i_o(0^+) - i_o(\infty)) e^{-t/\tau} \quad t > 0$$

$$i_o(t) = - \left(1 + 3 e^{-2500t} \right) \text{ mA} \quad \text{for } t > 0$$

$$v_o(t) = v_o(\infty) + (v_o(0^+) - v_o(\infty)) e^{-t/\tau} \quad \text{for } t > 0$$

$$v_o(t) = \left(-50 + 150 e^{-2500t} \right) \text{ V} \quad \text{for } t > 0$$