

# Phasors

Given the sinusoids  $i(t) = I_m \cos(\omega t + \Phi_i)$

and  $v(t) = V_m \cos(\omega t + \Phi_v)$

We can obtain the phasor forms as:

$i(t) = I_m \cos(\omega t + \Phi_i)$ , then  $\vec{I} = I_m \angle \Phi_i$

$v(t) = V_m \cos(\omega t + \Phi_v)$ , then  $\vec{V} = V_m \angle \Phi_v$

$$i(t) = 6 \cos(50t - 40^\circ) \text{ A}$$

$$\therefore \vec{I} = 6 \angle -40^\circ \text{ A}$$


$$v(t) = -4 \sin(30t + 50^\circ) \text{ V}$$

$$v(t) = 4 \cos(30t + 140^\circ) \text{ V}$$

$$\therefore \vec{V} = 4 \angle 140^\circ \text{ V}$$

# Phasor Relationships for Circuit Elements

Resistor :

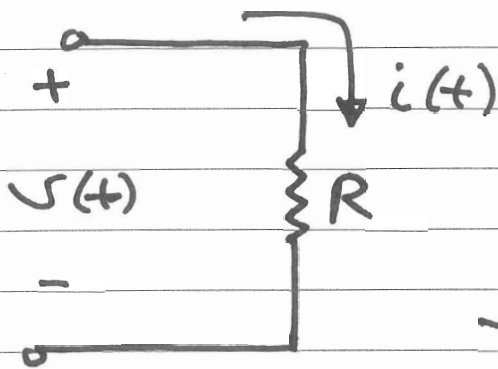

$$v(t) = R i(t)$$

$$V_m e^{j(\omega t + \theta_v)} = R I_m e^{j(\omega t + \phi)}$$

$$V_m e^{j\theta_v} = R I_m e^{j\phi}$$

$$V_m \angle \theta_v = R I_m \angle \phi$$


$$\vec{V} = R \vec{I}$$

$$V_m = R I_m$$

$$\theta_v = \phi$$

\* Voltage and Current of a resistor are in phase.

Inductor :

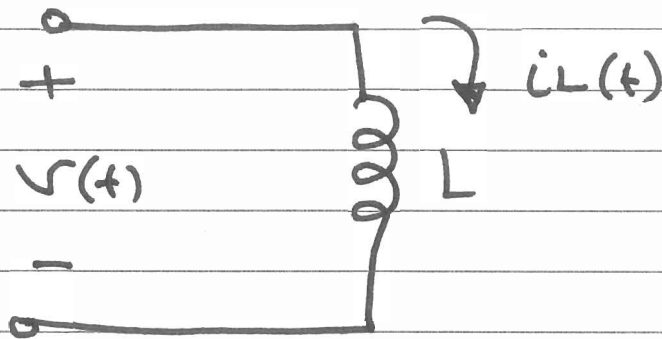

$$v(t) = L \frac{di(t)}{dt}$$

$$\sqrt{m} e^{j(\omega t + \theta_v)} = L \frac{d}{dt} \left( I_m e^{j(\omega t + \phi_i)} \right)$$

$$\sqrt{m} e^{j(\omega t + \theta_v)} = j\omega L I_m e^{j(\omega t + \phi_i)}$$

$$\sqrt{m} e^{j\theta_v} = j\omega L I_m e^{j\phi_i}$$

$$\sqrt{m} \angle \theta_v = j\omega L I_m \angle \phi_i$$

$$\vec{V} = j\omega L \vec{I}$$

\*  $\sqrt{m} = \omega L I$

$$\sqrt{m} \angle \theta_v = \omega L \angle 90^\circ \cdot I_m \angle \phi_i$$

$$\sqrt{m} \angle \theta_v = \omega L I_m \angle \phi_i + 90^\circ$$


$$V_m \angle \phi_v = \omega L I_m \angle \phi_i + 90^\circ$$

$$\therefore V_m = \omega L I_m$$

$$\phi_v = \phi_i + 90^\circ$$

The voltage leads the current  
by  $90^\circ$

Capacitor :

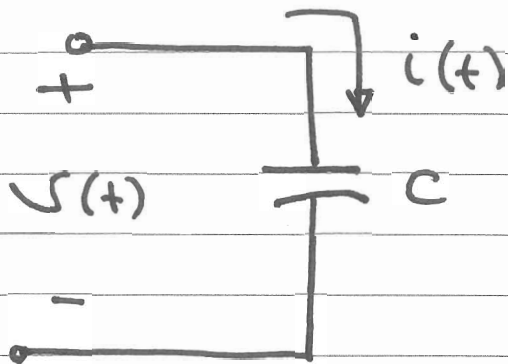

$$i(t) = C \frac{dv(t)}{dt}$$

$$\operatorname{Im} e^{j(\omega t + \phi_i)} = C \frac{d}{dt} \left( \sqrt{v_m} e^{j(\omega t + \theta_v)} \right)$$

$$\operatorname{Im} e^{j(\omega t + \phi_i)} = j\omega C \sqrt{v_m} e^{j(\omega t + \theta_v)}$$

$$\operatorname{Im} e^{j\phi_i} = j\omega C \sqrt{v_m} e^{j\theta_v}$$

$$\operatorname{Im} \angle \phi_i = j\omega C \sqrt{v_m} \angle \theta_v$$

$$\boxed{\vec{I} = j\omega C \vec{V}}$$

$$\operatorname{Im} \angle \phi_i = \omega C \angle 90^\circ \sqrt{v_m} \angle \theta_v$$


$$\operatorname{Im} \angle \phi_i = \omega C \sqrt{v_m} \angle \theta_v + 90^\circ$$

$$\therefore I_m = \omega C V_m$$


$$\phi_i = \phi_v + 90^\circ$$

The Current Leads the Voltage  
by  $90^\circ$ .

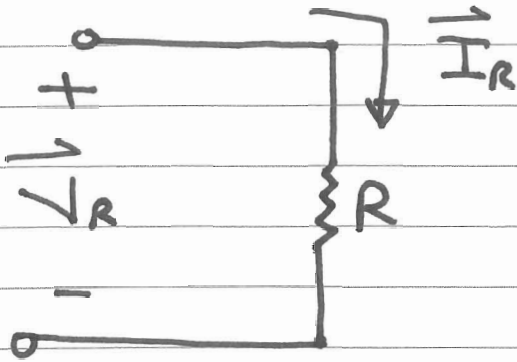
# Phasor Relationships For Circuit Elements



$$\vec{V}_R = R \vec{I}_R$$

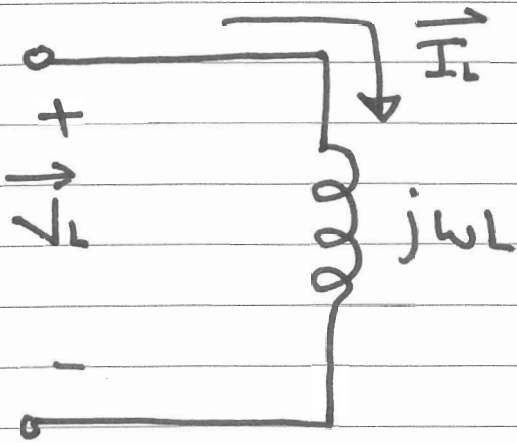

$$\vec{V}_L = j\omega L \vec{I}_L$$

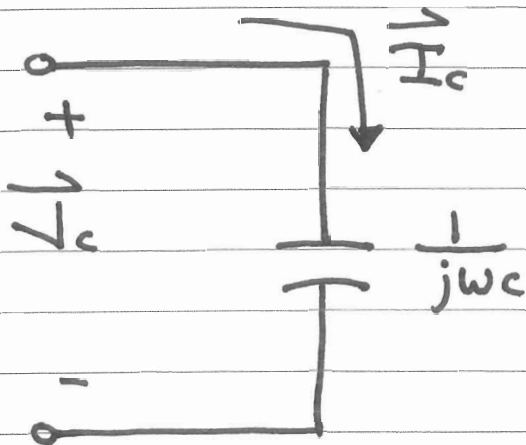

$$\vec{V}_C = \frac{1}{j\omega C} \vec{I}_C$$

$$\vec{V} = Z(j\omega) \vec{I}$$

# Impedance and Admittance

$$Z(j\omega) = \frac{\vec{V}}{\vec{I}} \quad \text{Impedance, } \Omega$$

$$\text{or } \vec{V} = Z(j\omega) \vec{I}$$

$$Y(j\omega) = \frac{\vec{I}}{\vec{V}} \quad \text{Admittance, } \Omega^{-1}$$

$$\text{or } \vec{I} = Y(j\omega) \vec{V}$$

$$\therefore Z(j\omega) = \frac{1}{Y(j\omega)}$$

Element	Impedance	Admittance
---------	-----------	------------


R	$Z(j\omega) = R$	$Y(j\omega) = \frac{1}{R}$
---	------------------	----------------------------

C	$Z(j\omega) = \frac{1}{j\omega C}$	$Y(j\omega) = j\omega C$
---	------------------------------------	--------------------------

L	$Z(j\omega) = j\omega L$	$Y(j\omega) = \frac{1}{j\omega L}$
---	--------------------------	------------------------------------



Impedance :  $Z(j\omega)$

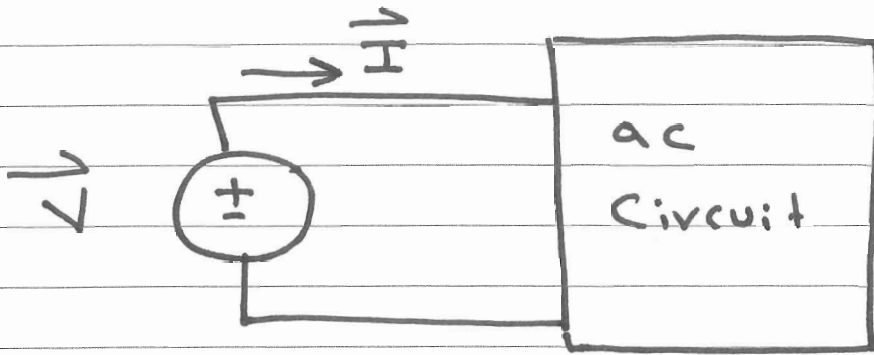

$$Z(j\omega) = \frac{\vec{V}}{\vec{I}} = \frac{V_m \angle \theta_v}{I_m \angle \theta_i}$$

$$Z(j\omega) = \frac{V_m}{I_m} \angle \theta_v - \theta_i$$

$$Z(j\omega) = |Z| \angle \theta_z$$

The unit of impedance is Ohm

Impedance is not a phasor but

a complex number that can be

written in polar or Cartesian forms

$$\vec{Z} = R + jX$$

$R \equiv$  Resistive part

$X \equiv$  Reactive part

$$\underline{Z} = |Z| \angle \theta_z$$

$$\underline{Z} = R + jX$$


$$|Z| = \sqrt{R^2 + X^2}$$

$$\theta_z = \tan^{-1} \frac{X}{R}$$

$$X = |Z| \sin \theta_z$$

$$R = |Z| \cos \theta_z$$

# A pplication of KVL for phasors

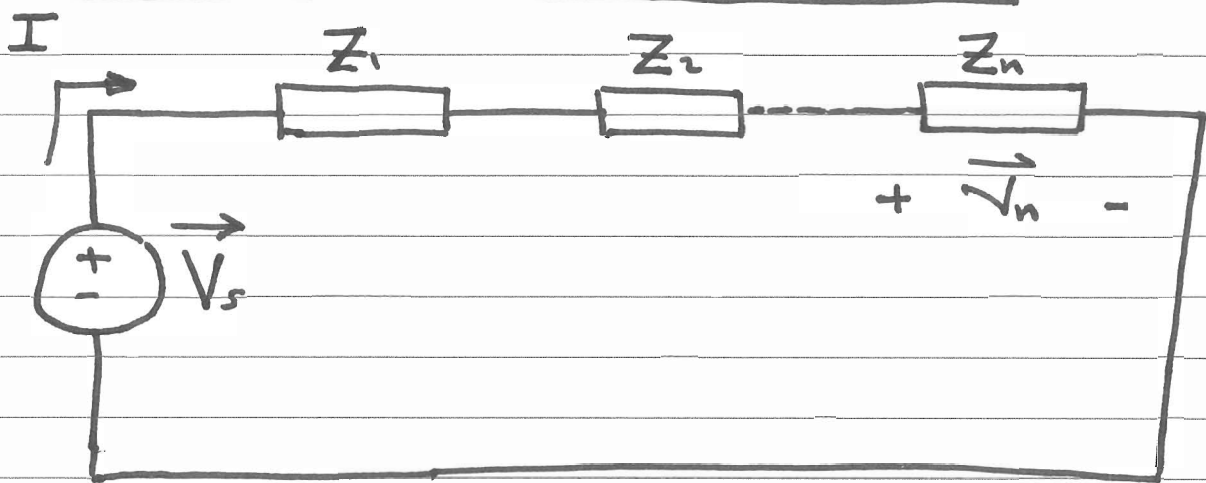


$$\text{KVL : } V_s(t) = V_1(t) + V_2(t) + \dots + V_n(t)$$

$$\vec{V}_s = \vec{V}_1 + \vec{V}_2 + \dots + \vec{V}_n$$


$$Z_{eq} = Z_1 + Z_2 + Z_3 + \dots + Z_n$$

$$\vec{V}_n = \frac{Z_n}{Z_1 + Z_2 + \dots + Z_n} \cdot \vec{V}_s$$

# Application of KCL for phasors

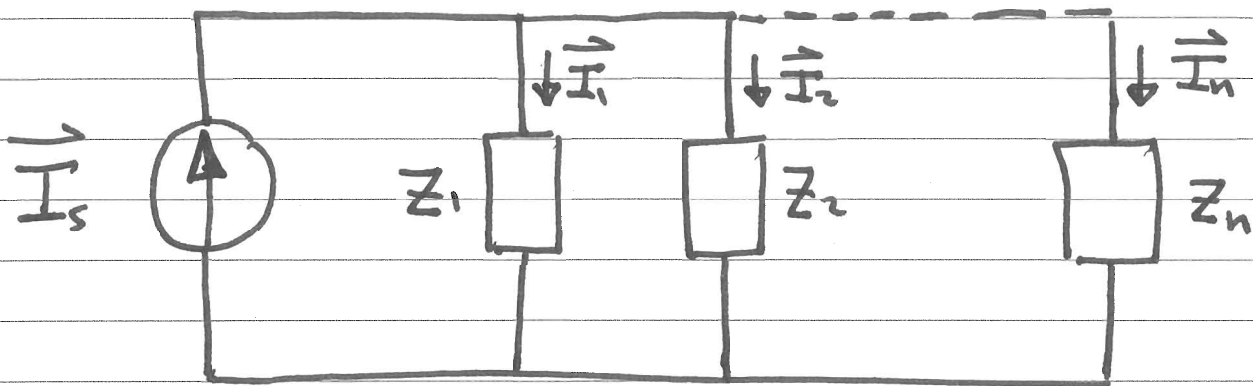

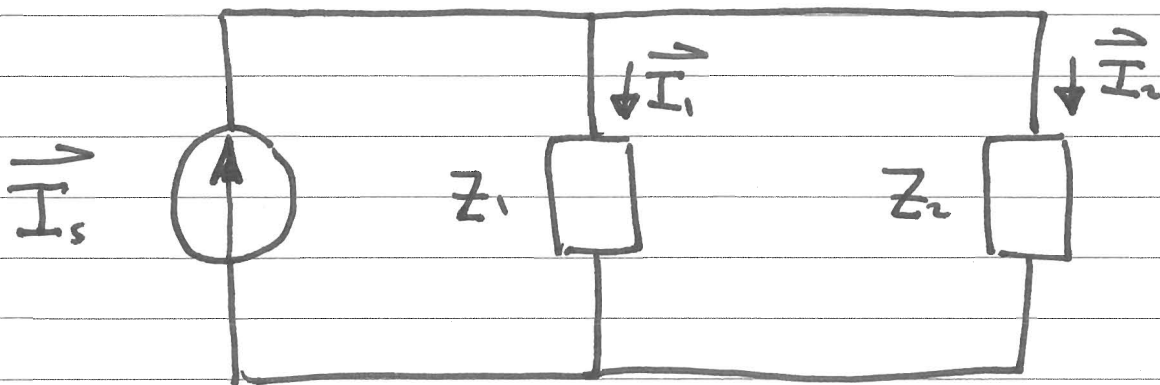
KCL: 
$$\vec{I}_s = \vec{I}_1 + \vec{I}_2 + \dots + \vec{I}_n$$



$$\vec{I}_1 = \frac{Z_2}{Z_1 + Z_2} \vec{I}_s$$

$$\vec{I}_2 = \frac{Z_1}{Z_1 + Z_2} \vec{I}_s$$

Find  $Z_{eq}$

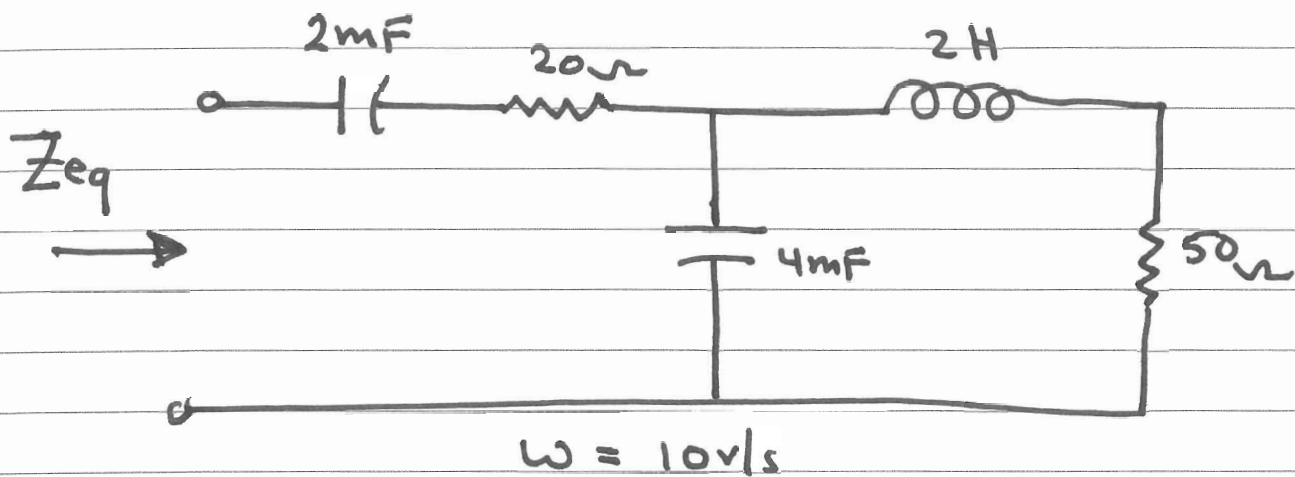

$$Z_1 = 20 + \frac{1}{j(10)(2)(10^{-3})} = 20 - j50$$

$$Z_2 = 50 + j(10)(2) = 50 + j20$$


$$Z_3 = (50 + j20) \parallel \frac{1}{j(10)(4)(10^{-3})}$$

$$Z_3 = (50 + j20) \parallel -j25$$

$$Z_3 = \frac{(50 + j20)(-j25)}{50 + j20 - j25} = 12.38 - j23.76$$

$$Z_{eq} = Z_1 + Z_3 = 32.38 - j73.76 \Omega$$


Calculate  $v_o(t)$

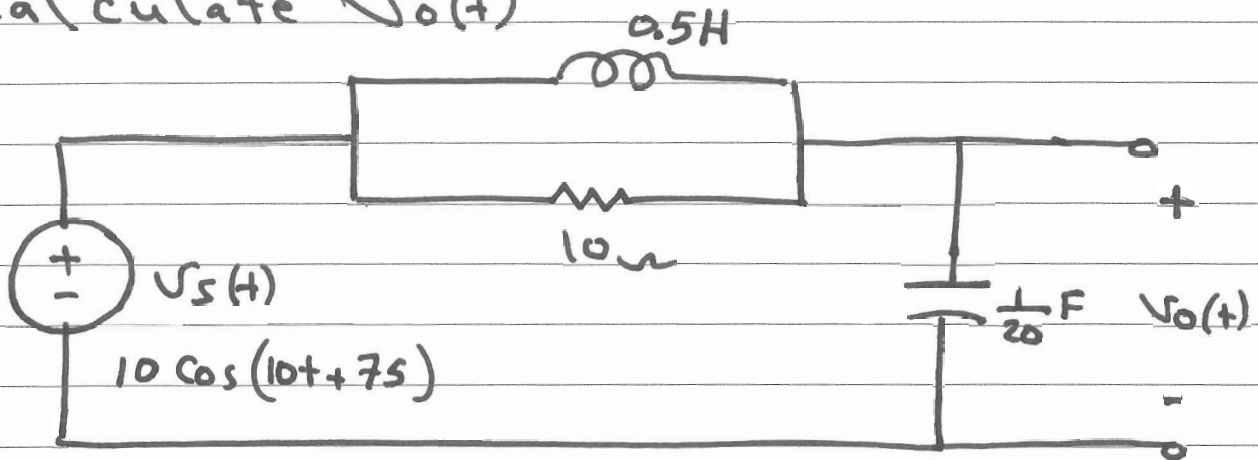

$$Z_L(j\omega) = j\omega L = j5 \Omega$$

$$Z_C(j\omega) = -j \frac{1}{\omega C} = -j2 \Omega$$
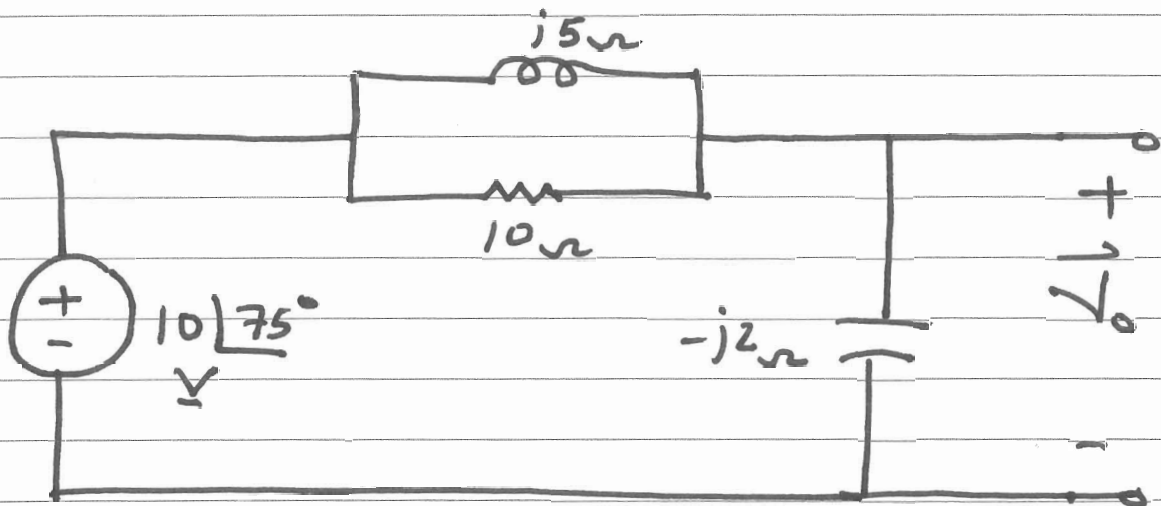
$$\vec{v}_s = 10 \angle 75^\circ \text{ V}$$




$$\vec{v}_o = \frac{-j2}{-j2 + 10 \parallel j5} \cdot 10 \angle 75^\circ$$

$$\vec{v}_o = 7.071 \angle -60^\circ \text{ V}$$

$$\therefore v_o(t) = 7.071 \cos(10t - 60^\circ) \text{ V}$$

Calculate  $i_o(t)$

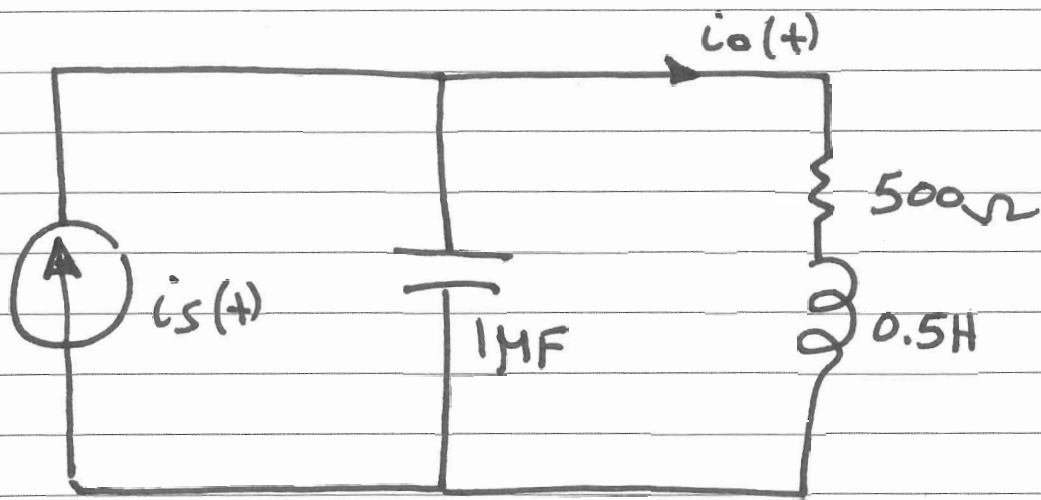


$$i_s(t) = 0.05 \cos 2000t \text{ A}$$

$$Z_C(j\omega) = -j \frac{1}{\omega C} = -j 500 \Omega$$

$$Z_L(j\omega) = j\omega L = j1000 \Omega$$
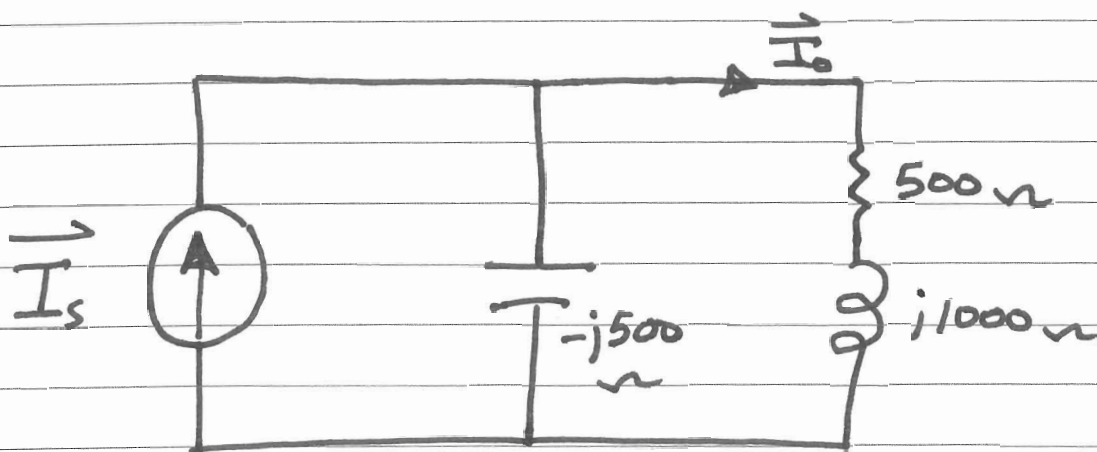
$$\vec{I}_s = 0.05 \angle 0^\circ \text{ A}$$





$$\vec{I}_o = \frac{-j 500}{-j 500 + 500 + j 1000} (0.05 \angle 0^\circ)$$

$$\vec{I}_0 = 0.03535 \angle -45^\circ \text{ A}$$

$$\therefore \vec{I}_0(t) = 0.03535 \cos(2000t - 45^\circ) \text{ A}$$



# Y- $\Delta$ Transformation

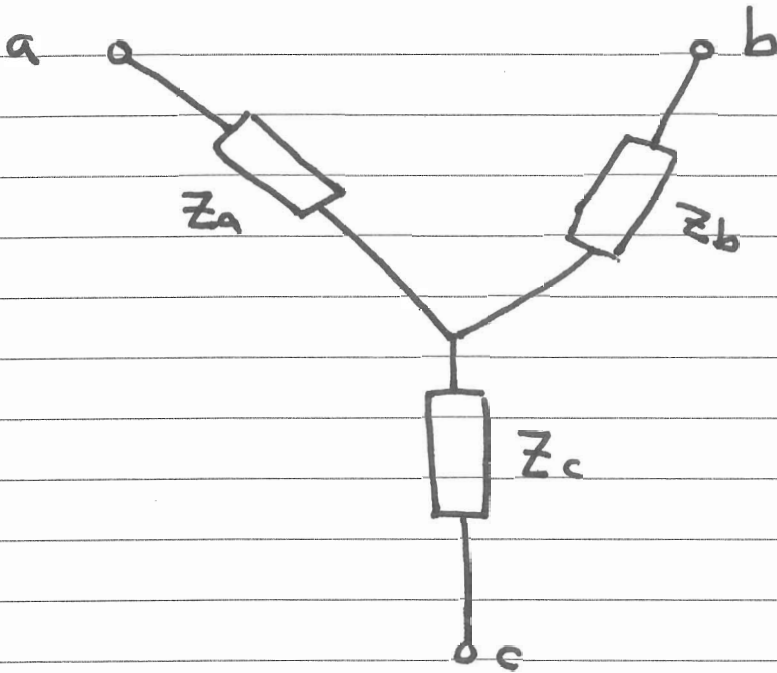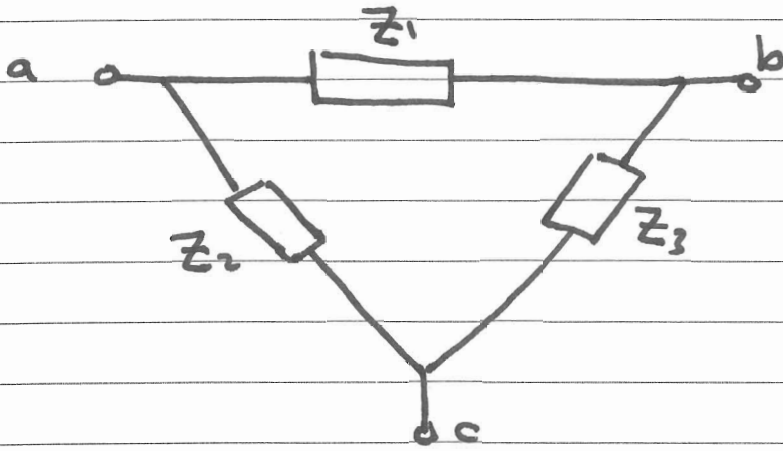

$$Z_a = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$


$$Z_b = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_c = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$


$$Z_1 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_c}$$

$$Z_2 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_b}$$
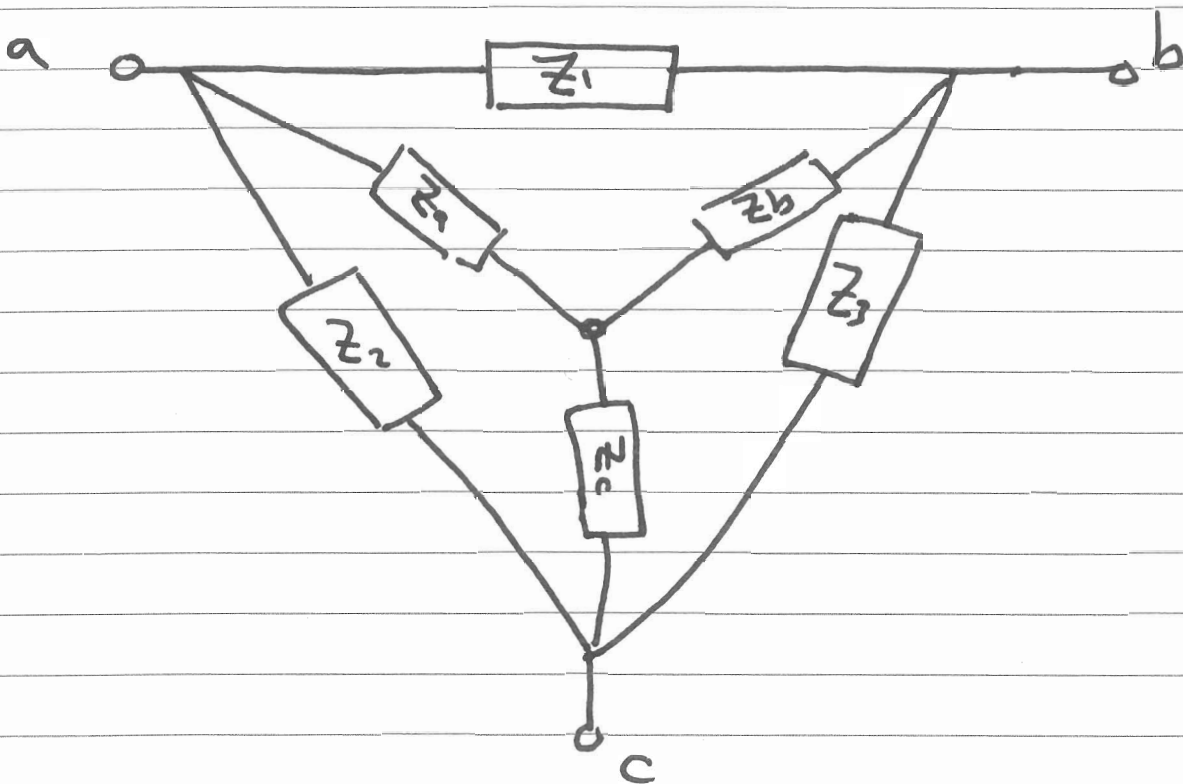
$$Z_3 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_a}$$



## Series RL circuit

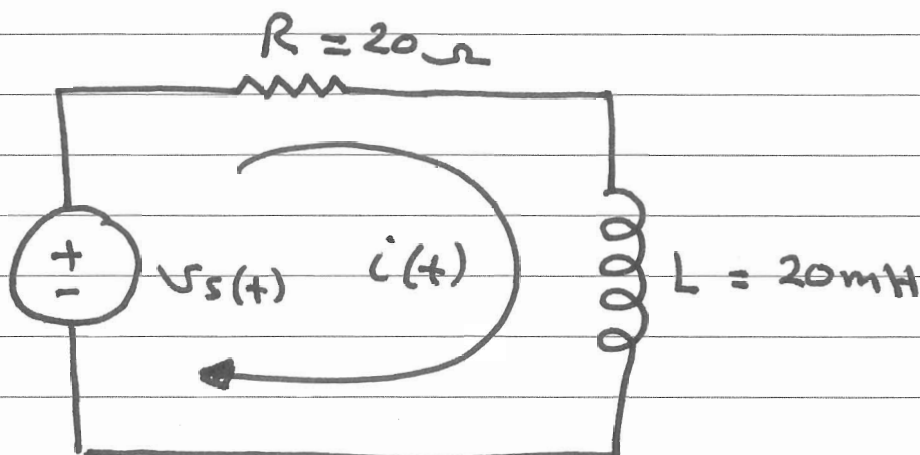


$$v_s(t) = 60 \cos(200\pi t) \text{ V}$$

Find  $i(t)$

$$Z_R(j\omega) = 20 \Omega$$

$$Z_L(j\omega) = j12.57 \Omega$$
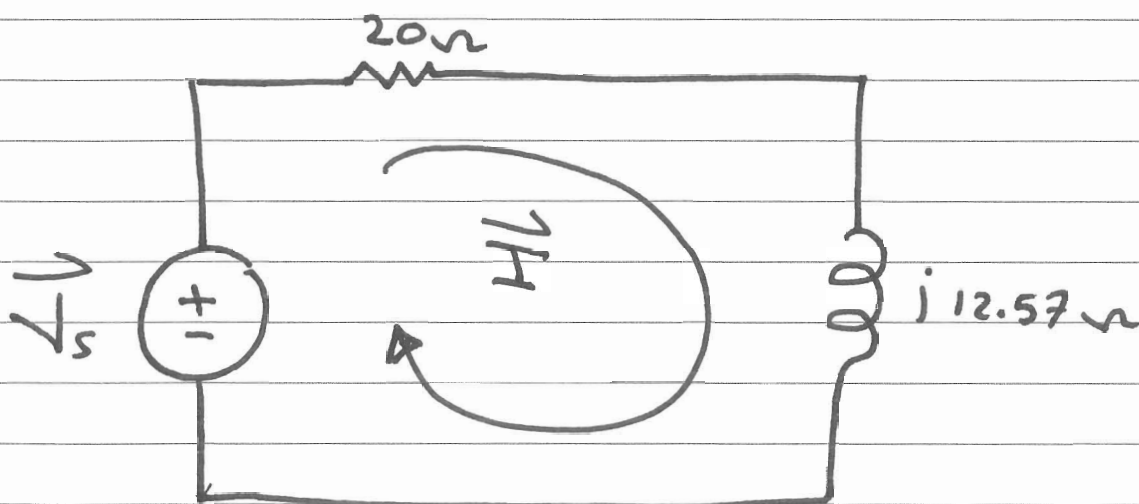
$$\vec{v}_s = 60 \angle 0^\circ \text{ V}$$



$$\text{KVL: } \vec{v}_s = \vec{v}_R + \vec{v}_L$$

$$60 \angle 0^\circ = 20 \vec{I} + j12.57 \vec{I}$$

$$\vec{I} = \frac{60 \angle 0^\circ}{20 + j12.57} = \frac{60 \angle 0^\circ}{23.6 \angle 32.1^\circ}$$

$$\therefore \vec{I} = 2.54 \angle -32.1^\circ \text{ A}$$

$$\vec{V}_R = 20 \vec{I} = 50.8 \angle -32.1^\circ \text{ V}$$


$$\vec{V}_L = j12.57 \vec{I} = 31.9 \angle +57.9^\circ \text{ V}$$

$\vec{V}_L$  Leads  $\vec{V}_R$  by  $90^\circ$

$\vec{I}_L$  Lags  $\vec{V}_L$  by  $32.1^\circ$


$$Z_{eq} = 20 + j12.57 \ \Omega \text{ inductive}$$
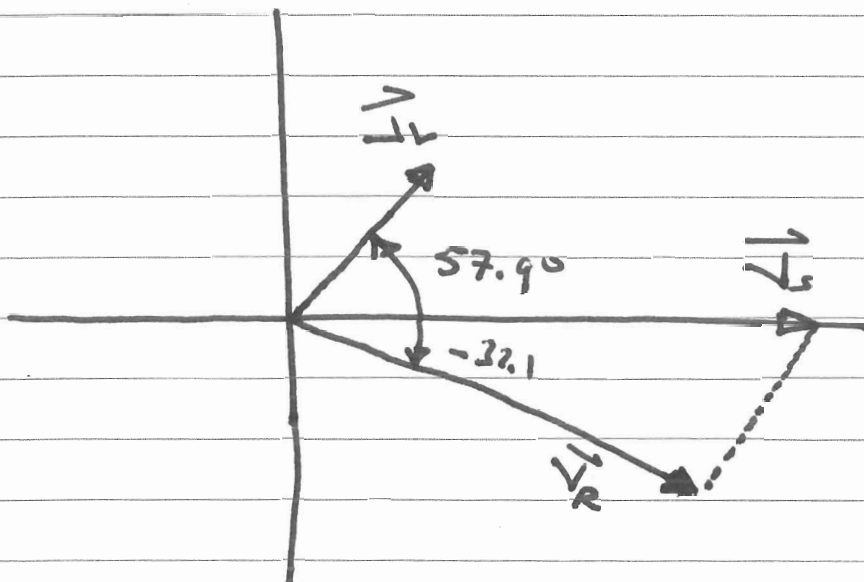
$$= 23.6 \angle 32.1^\circ \ \Omega \text{ inductive}$$



phasor diagram

## Series RC Circuit

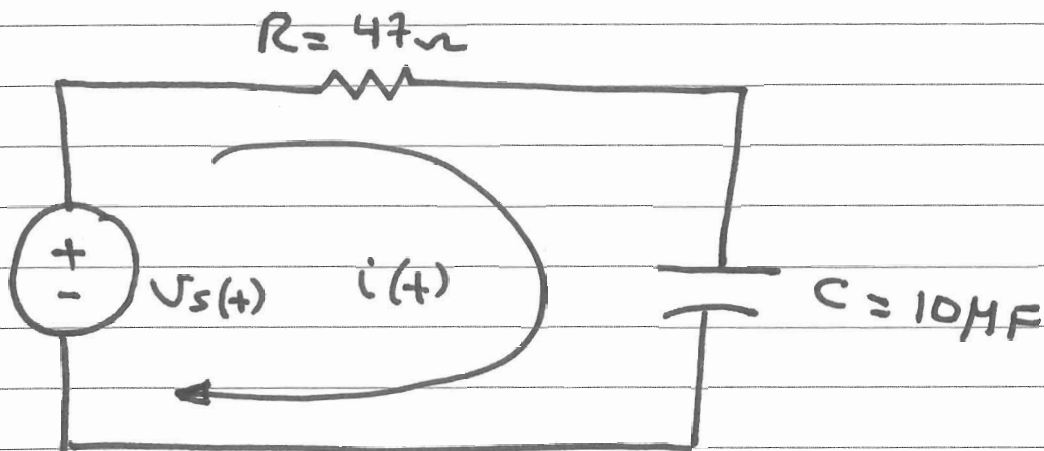


$$v_s(t) = 100 \cos 600\pi t \text{ V}$$

$$Z_R(j\omega) = 47 \text{ } \Omega$$

$$Z_C(j\omega) = -j \frac{1}{\omega C} = -j 53.1 \text{ } \Omega$$
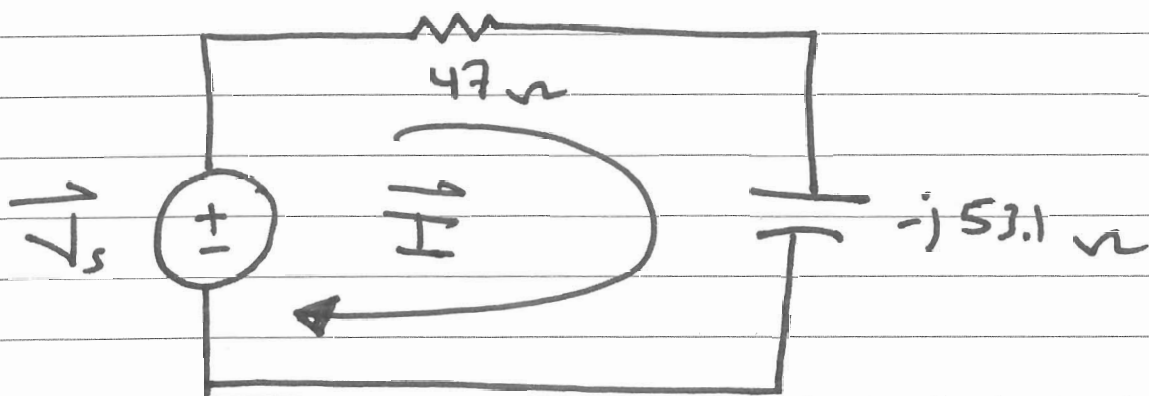
$$\vec{V}_s = 100 \angle 0^\circ \text{ V}$$



KVL:

$$\vec{V}_s = 47 \vec{I} - j 53.1 \vec{I}$$

$$\vec{I} = \frac{\vec{V}_s}{47 - j 53.1} = \frac{100 \angle 0^\circ}{47 - j 53.1}$$

$$\vec{I} = \frac{100 \angle 0^\circ}{70.9 \angle -48.5^\circ}$$

$$\vec{I} = 1.41 \angle 48.5^\circ \text{ A}$$

$\vec{I}$  Leads  $\vec{V}_s$  by  $48.5^\circ$

→ Capacitive Circuit


$$Z(j\omega) = 47 - j53.1^\circ \quad \text{Capacitive}$$

$$Z(j\omega) = 70.9 \angle -48.5^\circ \quad \text{Capacitive}$$


$$\vec{V}_R = 47 \vec{I} = 66.3 \angle 48.5^\circ \text{ V}$$

$$\vec{V}_C = -j53.1 \vec{I} = 74.9 \angle -41.5^\circ \text{ V}$$

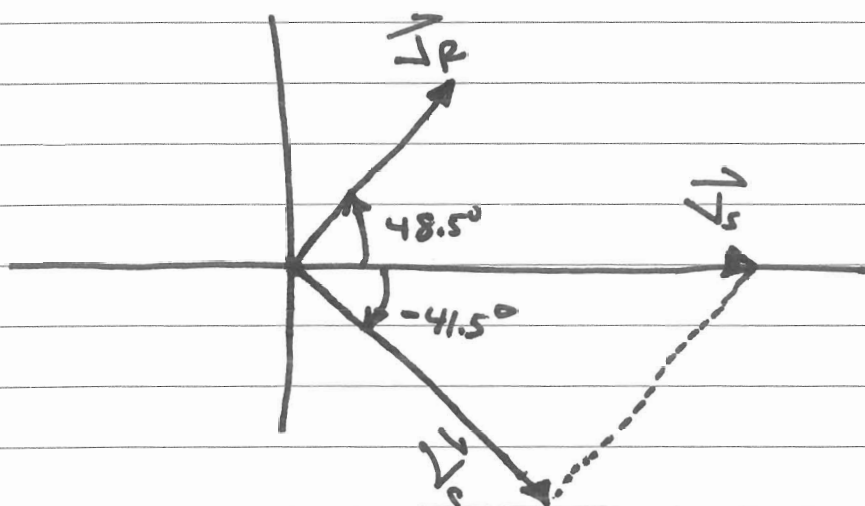$\vec{V}_C$  Lags  $\vec{I}$  by  $90^\circ$



# Series RLC

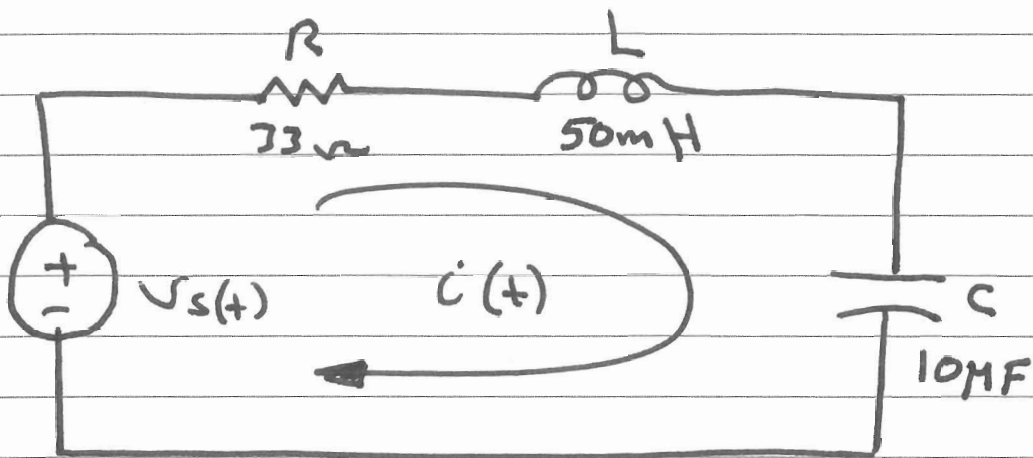


$$v_s(t) = 75 \cos 400\pi t \text{ V}$$

$$Z_R(j\omega) = 33 \Omega$$

$$Z_L(j\omega) = j\omega L = j62.8 \Omega$$
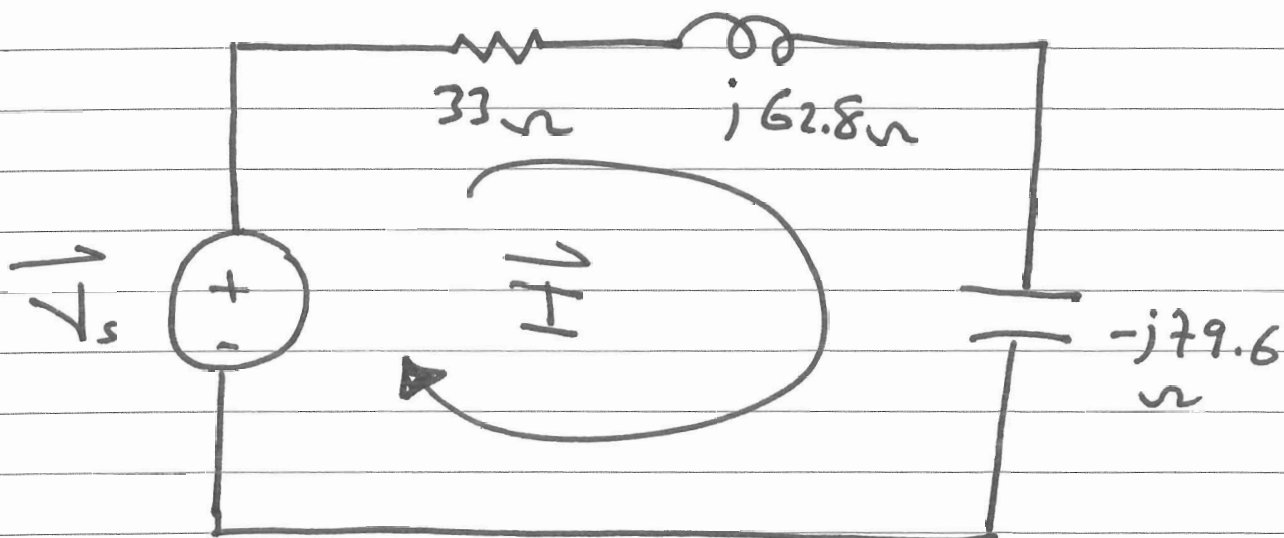
$$Z_C(j\omega) = -j \frac{1}{\omega C} = -j79.6 \Omega$$



$$\text{KVL: } \vec{v}_s = \vec{v}_R + \vec{v}_L + \vec{v}_C$$

$$\vec{V}_s = 33 \vec{I} + j62.8 \vec{I} - j79.6 \vec{I}$$

$$\vec{I} = \frac{\vec{V}_s}{33 - j16.8} = \frac{75 \angle 0^\circ}{37 \angle -27^\circ}$$

$$\vec{I} = 2.03 \angle 27^\circ \text{ A}$$

$\vec{I}$  Leads  $\vec{V}_s$  by  $27^\circ$

$\therefore$  Capacitive Circuit

$$Z_{eq} = R + j\omega L - j \frac{1}{\omega C}$$

$$Z_{eq} = 33 + j62.8 - 79.6$$

$$Z_{eq} = 33 - j16.8 \quad \Omega \quad \text{Capacitive}$$


$$Z_{eq} = 37 \angle -27^\circ \quad \Omega \quad \text{Capacitive}$$

$$\vec{V}_R = R \vec{I} = 67 \angle 27^\circ \text{ V}$$

$$\vec{V}_L = j\omega L \vec{I} = 127 \angle 117^\circ \text{ V}$$
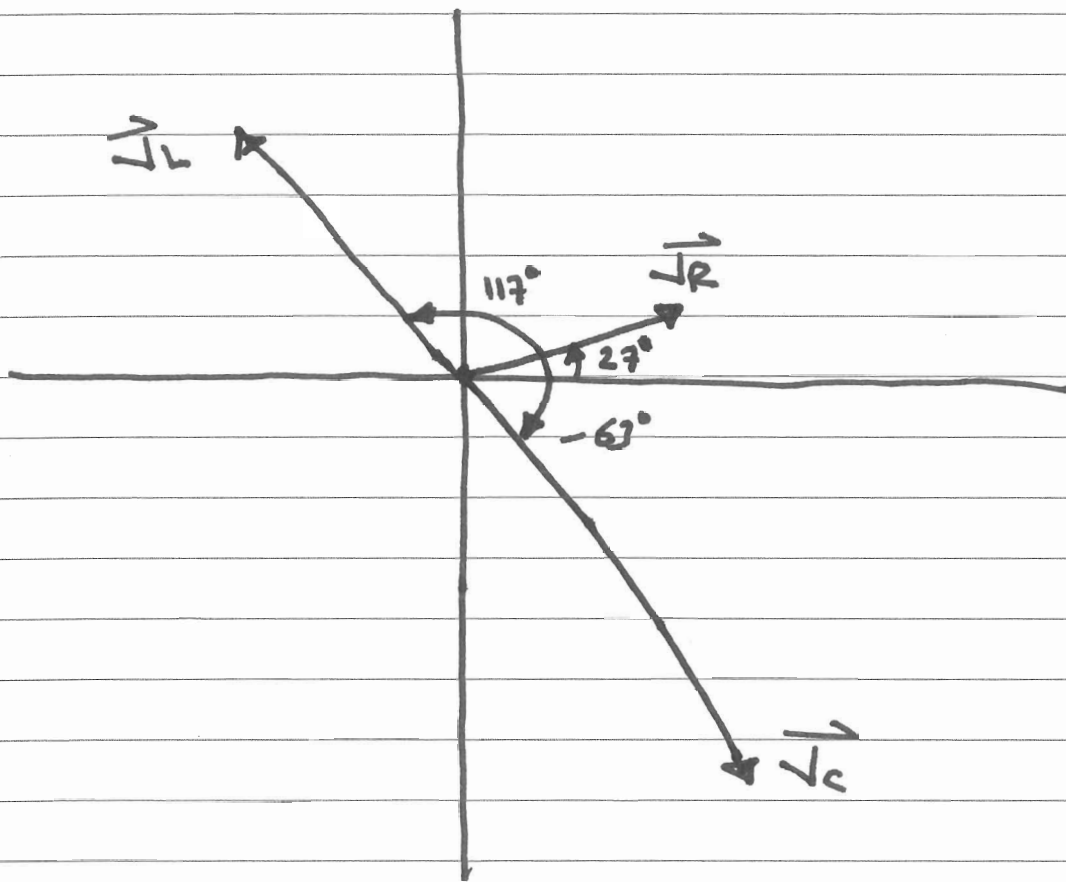
$$\vec{V}_C = -j \frac{1}{\omega C} \vec{I} = 162 \angle -63^\circ \text{ V}$$






$$\text{If } j\omega L - j\frac{1}{\omega C} = 0$$

$$\omega = \frac{1}{\sqrt{LC}}$$

resonant frequency


$$Z_{eq} = R \quad \text{resistive}$$

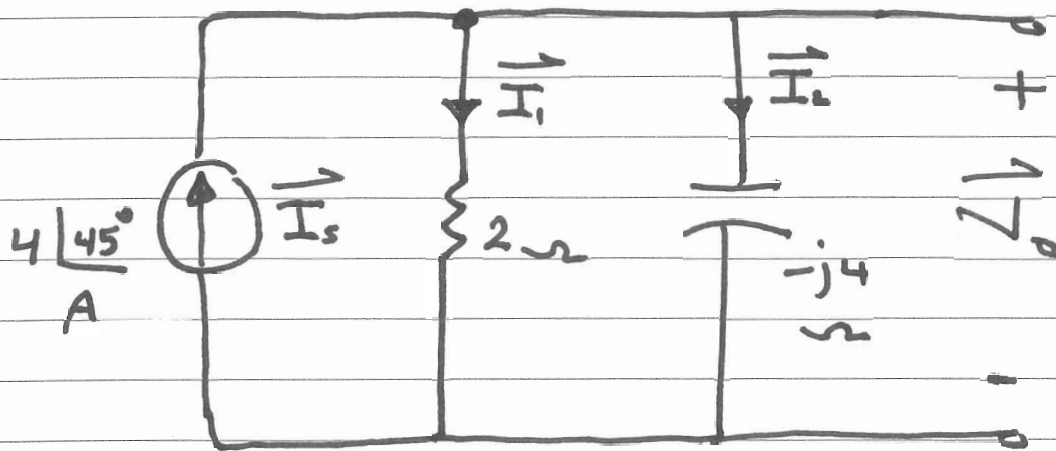


$$\vec{I}_1 = \frac{-j4}{-j4+2} \vec{I}_s = 3.578 \angle 18.435^\circ \text{ A}$$

$$\vec{I}_2 = \frac{2}{2-j4} \vec{I}_s = 1.789 \angle 108.435^\circ \text{ A}$$
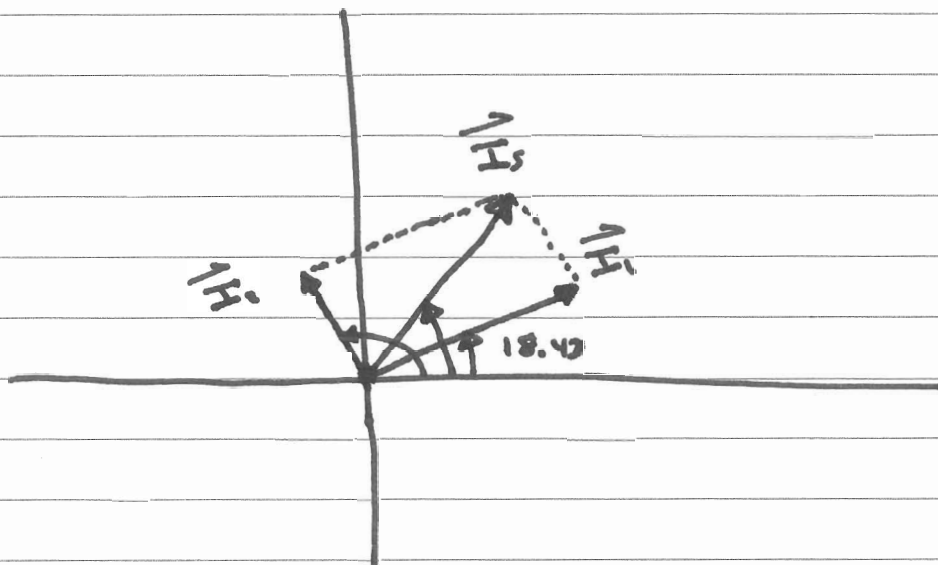
$$\vec{V}_o = 2 \vec{I}_1 = 7.156 \angle 18.435^\circ \text{ V}$$



phasor diagram

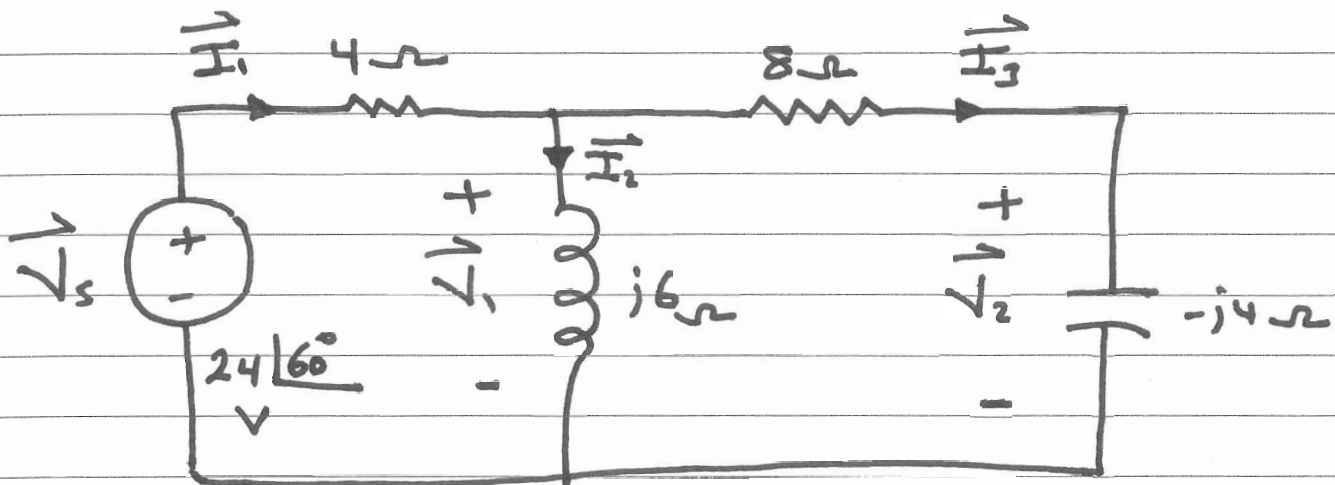

Calculate all the voltages and currents

$$Z_{eq} = 4 + j6 \parallel (8 - j4)$$

$$Z_{eq} = 9.604 \angle 30.964^\circ \Omega$$

$$\vec{I}_1 = \frac{\vec{V}_s}{Z_{eq}} = \frac{24 \angle 60^\circ}{9.604 \angle 30.964^\circ} = 2.498 \angle 29.036^\circ \text{ A}$$


$$\vec{I}_2 = \frac{j6}{j6 + 8 - j4} \vec{I}_1 = 1.82 \angle 105^\circ \text{ A}$$

$$\vec{I}_2 = \frac{8 - j4}{8 - j4 + j6} \vec{I}_1 = 2.71 \angle -11.58^\circ \text{ A}$$

$$\vec{V}_1 = j6 \vec{I}_2 = 16.26 \angle 78.42^\circ \text{ V}$$

$$\vec{V}_2 = -j4 \vec{I}_2 = 7.28 \angle 15^\circ \text{ V}$$

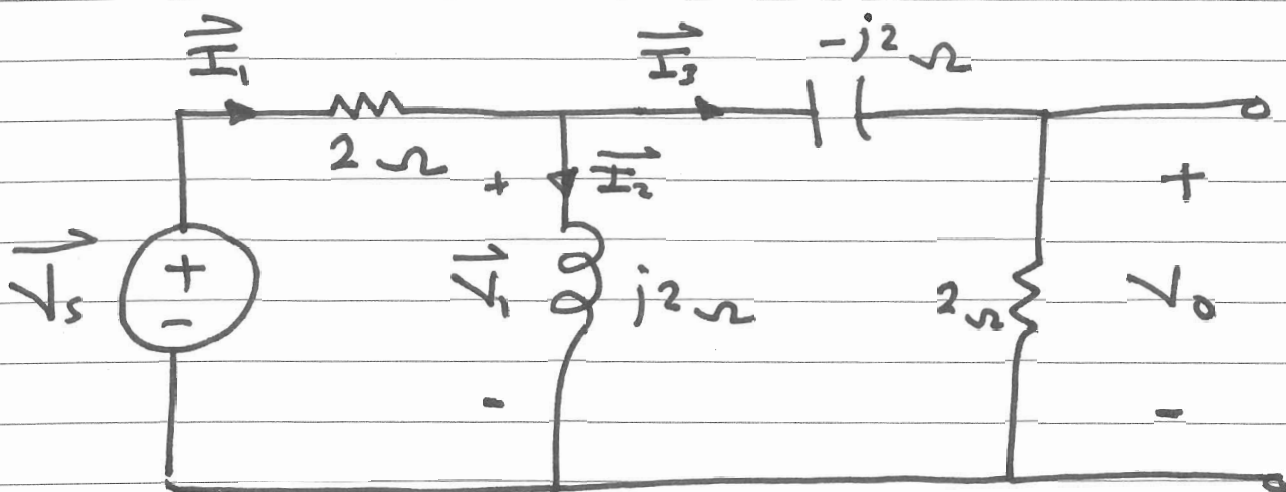If  $\vec{V}_0 = 8 \angle 45^\circ$  V, find  $\vec{V}_s$



$$\vec{I}_3 = \frac{\vec{V}_0}{2} = 4 \angle 45^\circ \text{ A}$$

$$\vec{V}_1 = (2 - j2) \vec{I}_3 = 11.314 \angle 0^\circ$$

$$\vec{I}_2 = \frac{\vec{V}_1}{j2} = 5.657 \angle -90^\circ \text{ A}$$

$$\vec{I}_1 = \vec{I}_2 + \vec{I}_3 = (2.828 - j2.828) \text{ A}$$

$$\vec{V}_s = 2 \vec{I}_1 + \vec{V}_1$$

$$\vec{V}_s = 17.888 \angle -18.439^\circ \text{ V}$$