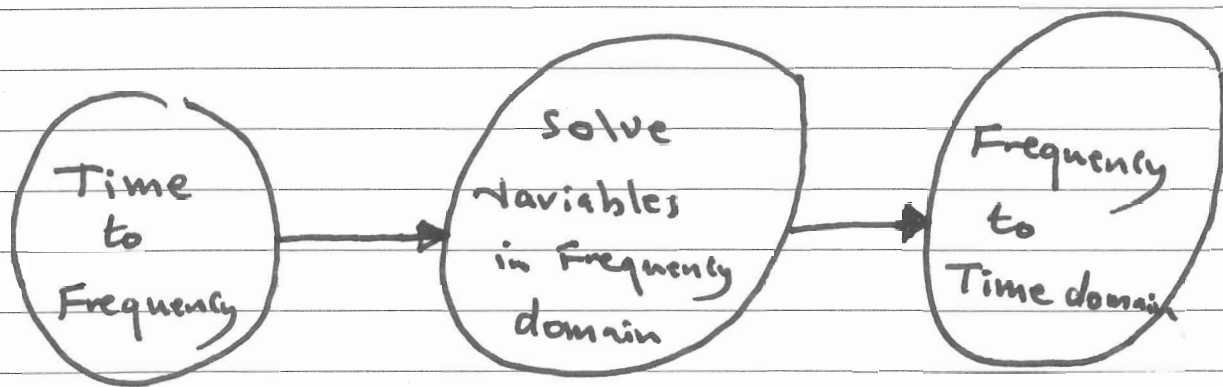


## Steps to Analyze Ac Circuits


\* Transform the circuit to the phasor or frequency domain.

\* Solve the problem using circuit techniques (nodal analysis, mesh analysis, superposition, etc.....)

\* Transform the resulting phasor to the time domain.



# Nodal Analysis

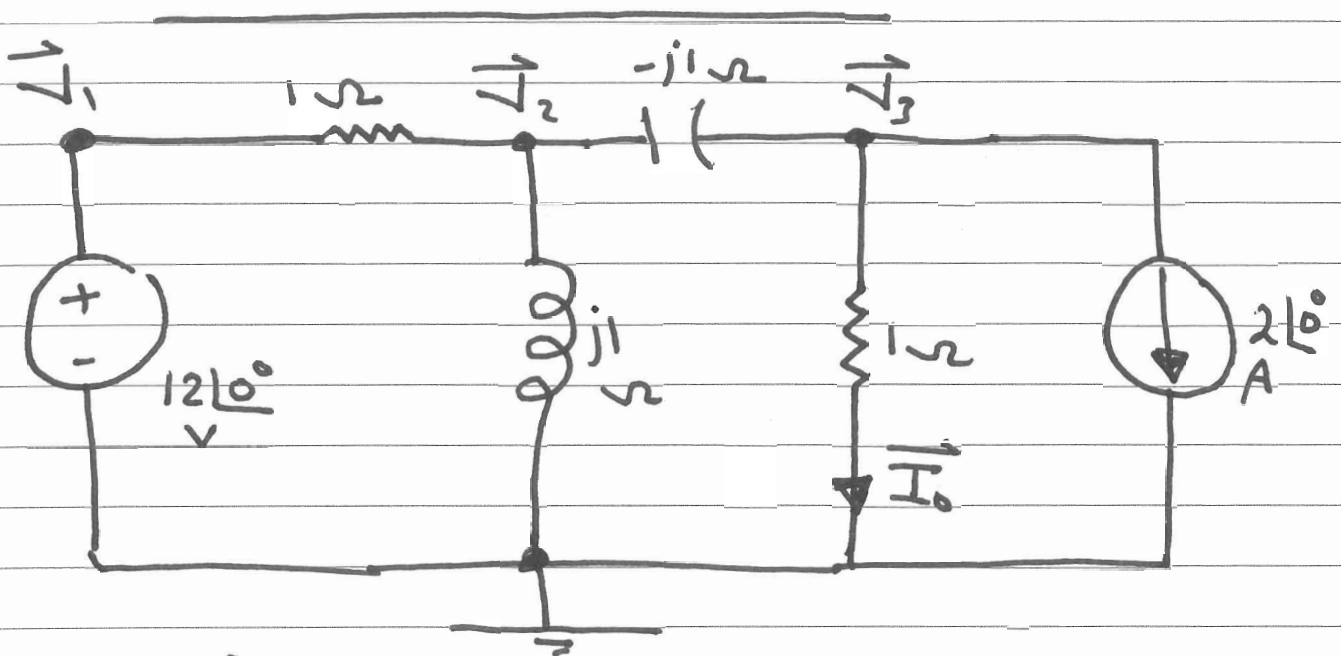

Find  $\vec{I}_0$  using Nodal Analysis

$$\vec{I}_0 = \frac{\vec{V}_3}{1}$$

$$\vec{V}_1 = 12\angle 0^\circ \quad \text{Constraint equation}$$

KCL at node 2:

$$\frac{\vec{V}_2 - \vec{V}_1}{1} + \frac{\vec{V}_2}{j1} + \frac{\vec{V}_2 - \vec{V}_3}{-j1} = 0$$

$$-\vec{V}_1 + \vec{V}_2 - j\vec{V}_2 = 0$$

KCL at node 3:

$$-2\angle 0^\circ = -\frac{1}{-j1} \vec{V}_2 + \left( \frac{1}{-j1} + 1 \right) \vec{V}_3$$


$$-2\angle 0^\circ = -j \vec{V}_2 + (1+j) \vec{V}_3$$

Solving for  $\vec{V}_3$ ;

$$\vec{V}_3 = \left( \frac{8}{5} + j \frac{26}{5} \right) \angle$$

$$\therefore \vec{I}_0 = \frac{\vec{V}_3}{1} = \left( \frac{8}{5} + j \frac{26}{5} \right) \text{ A}$$

## Mesh Analysis

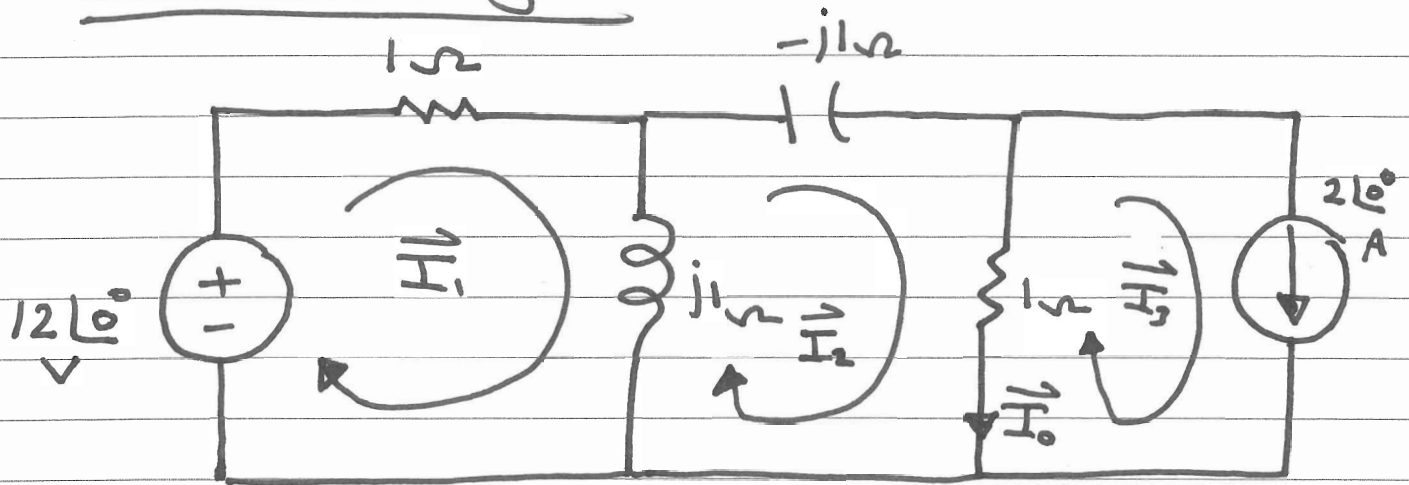

Find  $\vec{I}_0$  using Mesh Analysis

$$\vec{I}_0 = \vec{I}_2 - \vec{I}_3$$

KVL for mesh 1 :

$$12\angle 0^\circ = (1+j1)\vec{I}_1 - j1\vec{I}_2$$

KVL for mesh 2 :

$$0 = -j1\vec{I}_1 + (1+j1-j1)\vec{I}_2 - \vec{I}_3$$

$$0 = -j1\vec{I}_1 + \vec{I}_2 - \vec{I}_3$$

$$\vec{I}_2 = 2\angle 0^\circ \text{ A} \quad \text{Constrain equation}$$


Solving for  $\vec{I}_2$  and  $\vec{I}_3$

$$\vec{I}_2 = \left( \frac{18}{5} + j \frac{26}{5} \right) \text{ A}$$


$$\vec{I}_2 = 2 \angle 0^\circ \text{ A}$$

$$\therefore \vec{I}_0 = \left( \frac{8}{5} + j \frac{26}{5} \right) \text{ A}$$


# Source Transformation

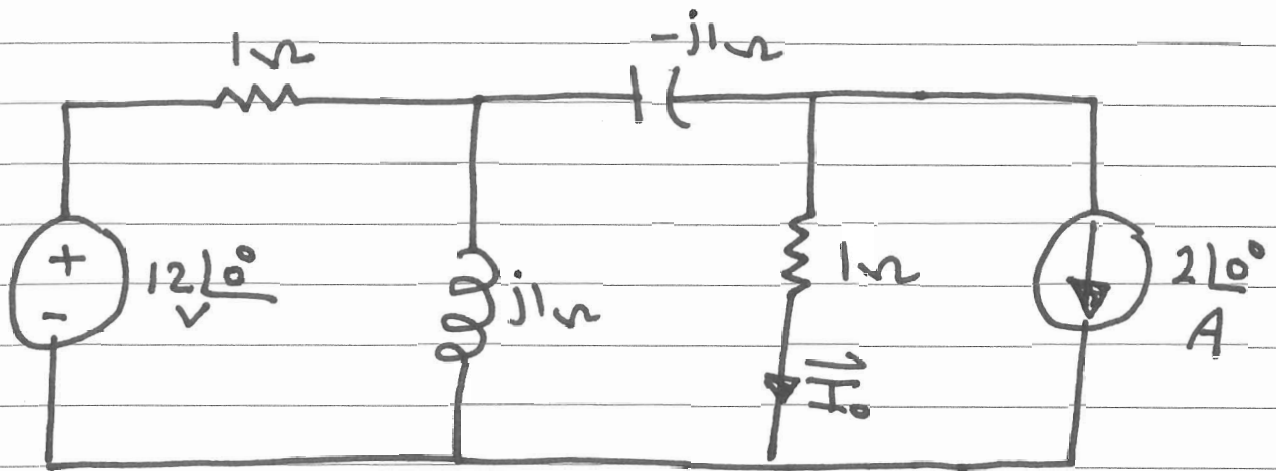

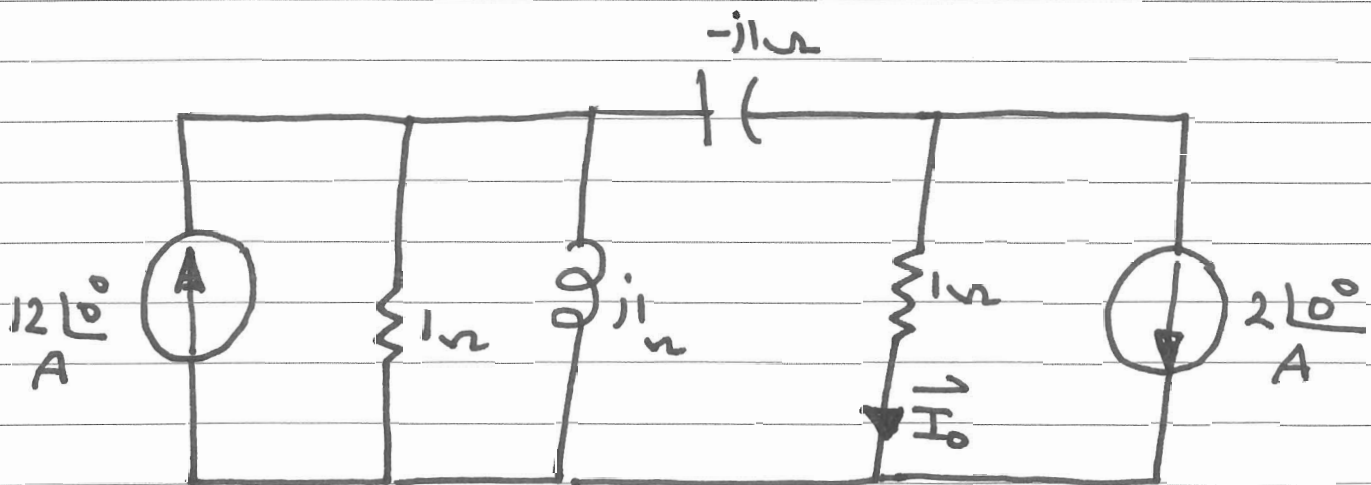
Find  $\vec{I}_0$  using Source Transformation


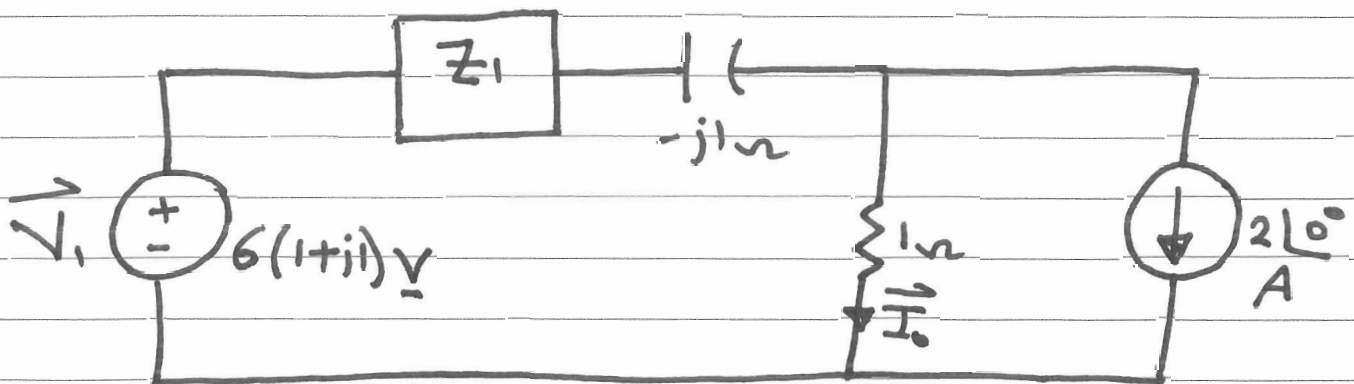
$$Z_1 = 1\Omega \parallel j1\Omega = \left(\frac{1}{2} + j\frac{1}{2}\right)\Omega$$



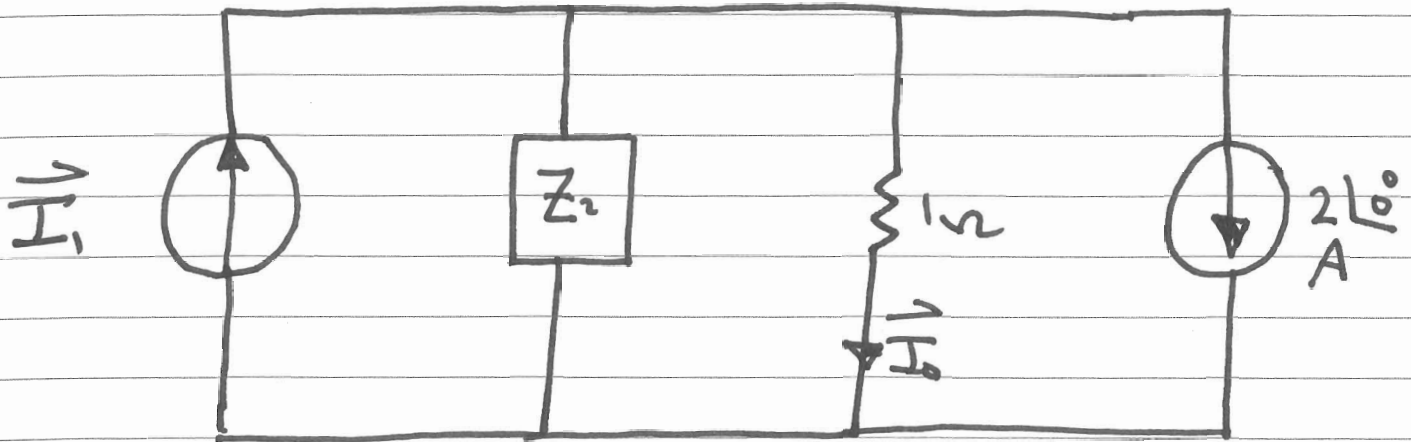
$$V_1 = 12\angle 0^\circ \cdot Z_1 = 6(1+j1) \text{ V}$$



$$\vec{I}_1 = \frac{\vec{V}_1}{Z_2} = \frac{12(1+j)}{1-j}$$
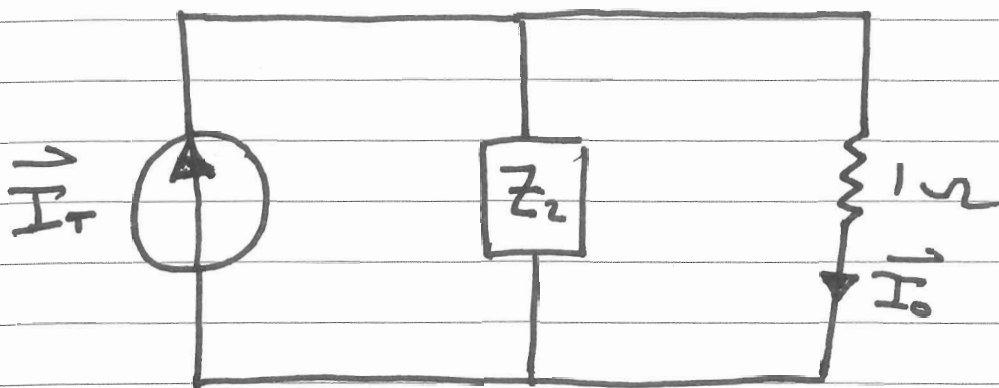
$$Z_2 = -j1 + Z_1 = \left(\frac{1}{2} - j\frac{1}{2}\right) \Omega$$




$$\vec{I}_T = \vec{I}_1 - 2\angle 10^\circ$$

$$\vec{I}_T = \left(\frac{10+j14}{1-j}\right) \text{A}$$

$$\vec{I}_0 = \frac{Z_2}{Z_2+1} \vec{I}_T = \left(\frac{8}{5} + j\frac{26}{5}\right) \text{A}$$


# Superposition

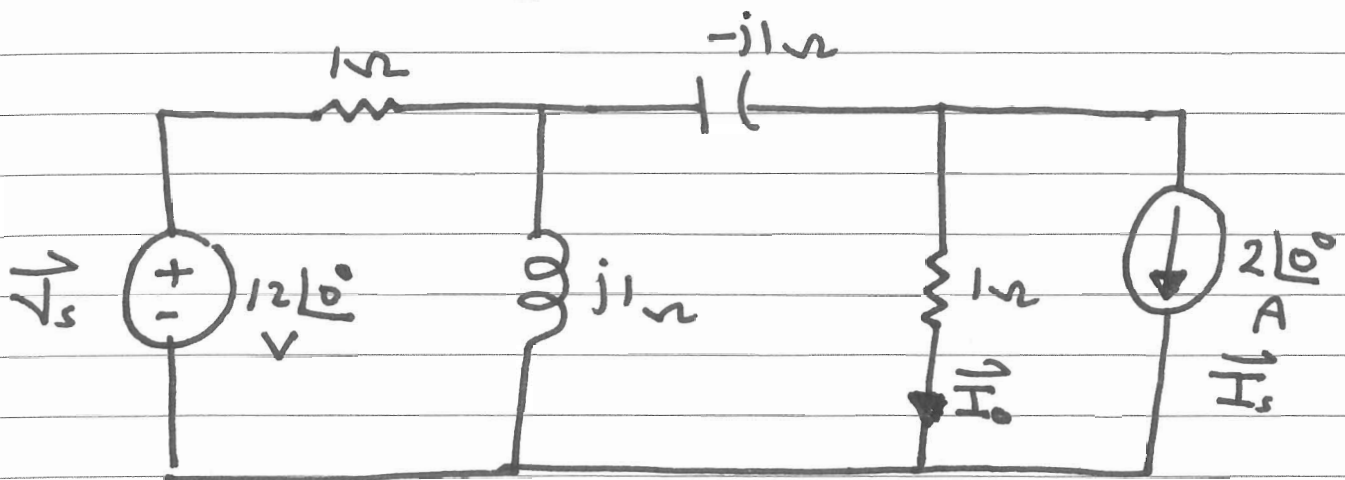

Find  $\vec{I}_o$  using Superposition

$$\vec{I}_o = \vec{I}_{o1} + \vec{I}_{o2}$$

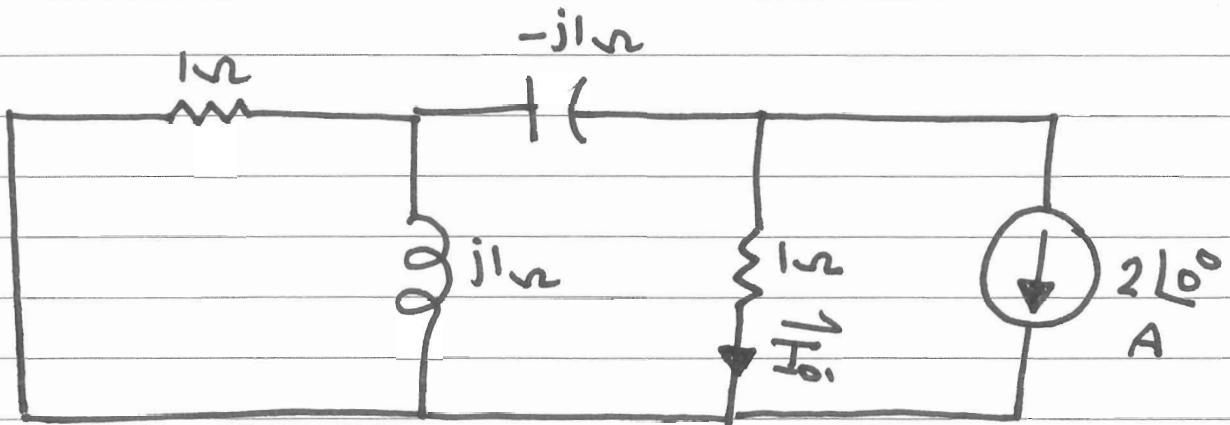1) let  $\vec{V}_s$  OFF, and  $\vec{I}_s$  on




$$\vec{I}_{o1} = -2 \angle 0^\circ \frac{Z_1}{Z_1 + 1}$$

$$Z_1 = -j1 + 1 \parallel j1 = -j1 + \frac{j1}{1+j1}$$

$$\vec{I}_{o1} = \frac{-2}{2+j1} \text{ A}$$



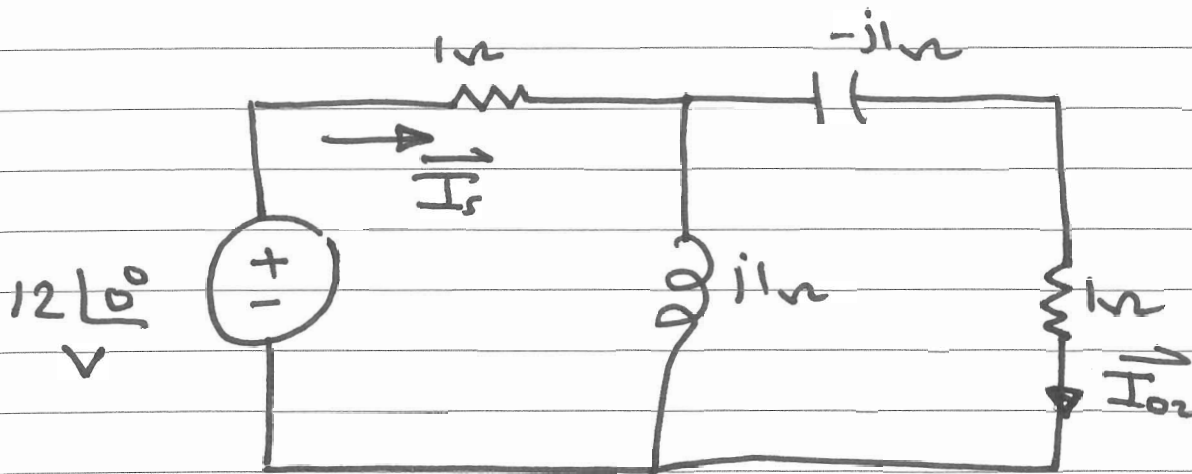2) let  $\vec{I}_s$  off, and  $\vec{V}_r$  on



$$\vec{I}_s = \frac{12\angle 0^\circ}{Z_{eq}}$$

$$Z_{eq} = 1 + j1 \parallel (1 - j1) = (2 + j1) \Omega$$

$$\therefore \vec{I}_s = \frac{12\angle 0^\circ}{2 + j1} \text{ A}$$


$$\vec{I}_{o2} = \vec{I}_s \frac{j1}{j1 + 1 - j1}$$

$$\vec{I}_{o2} = \vec{I}_s \cdot j1 = \frac{12}{1 - j2} \text{ A}$$

$$\therefore \vec{I}_o = \vec{I}_{o1} + \vec{I}_{o2}$$

$$\vec{I}_o = \left( \frac{8}{5} + j \frac{26}{5} \right) \text{ A}$$

# The Power of Superposition

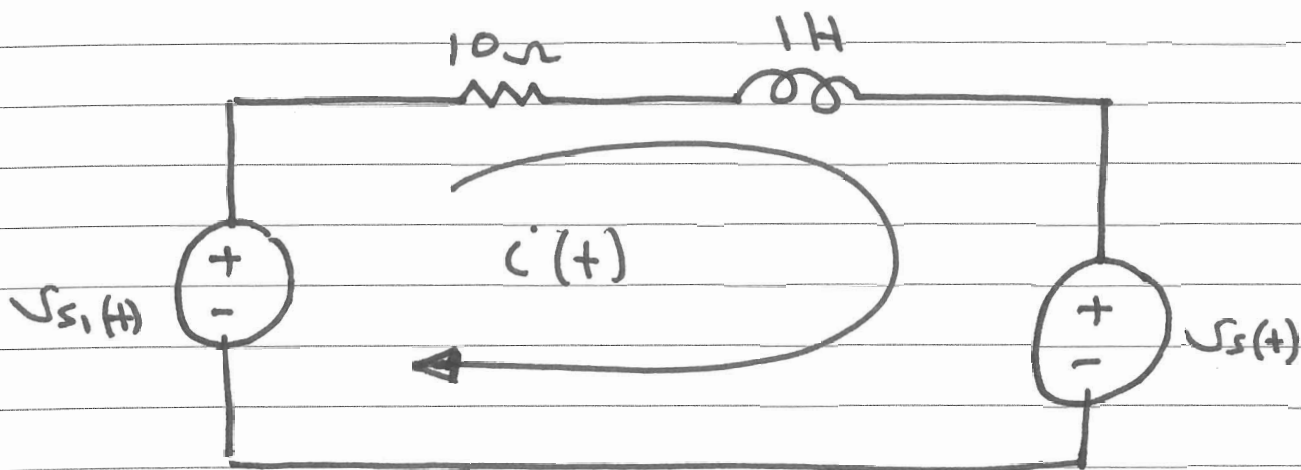

$$v_{s1}(t) = 100 \cos 10t \text{ V}$$

$$v_{s2}(t) = 50 \cos (20t - 10^\circ) \text{ V}$$


note that  $\omega_1 = 10 \text{ rad/s}$  and

$$\omega_2 = 20 \text{ rad/s}$$


$\therefore$  Superposition is the Only method of analysis.

$$i(t) = i_1(t) + i_2(t)$$

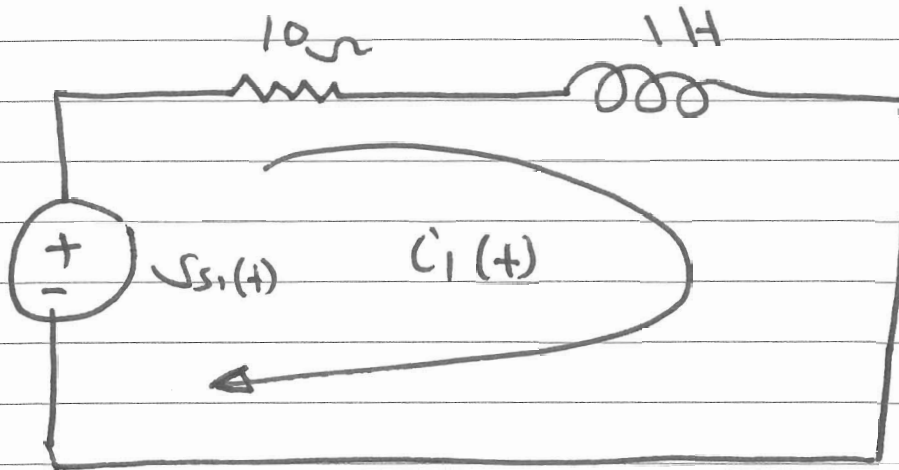1) Let  $v_{s2}(t)$  OFF, and  $v_{s1}(t)$  ON




$$v_{s1}(t) = 100 \cos 10t \text{ V}$$

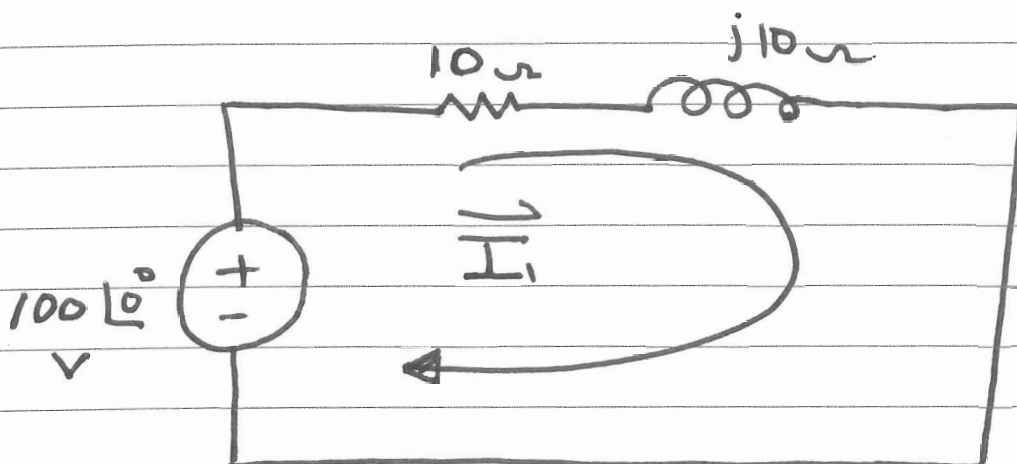


$$\vec{I}_1 = \frac{100 \angle 0^\circ}{10 + j10} = 7.07 \angle -45^\circ \text{ A}$$

$$\therefore i_1(t) = 7.07 \cos(10t - 45^\circ) \text{ A}$$

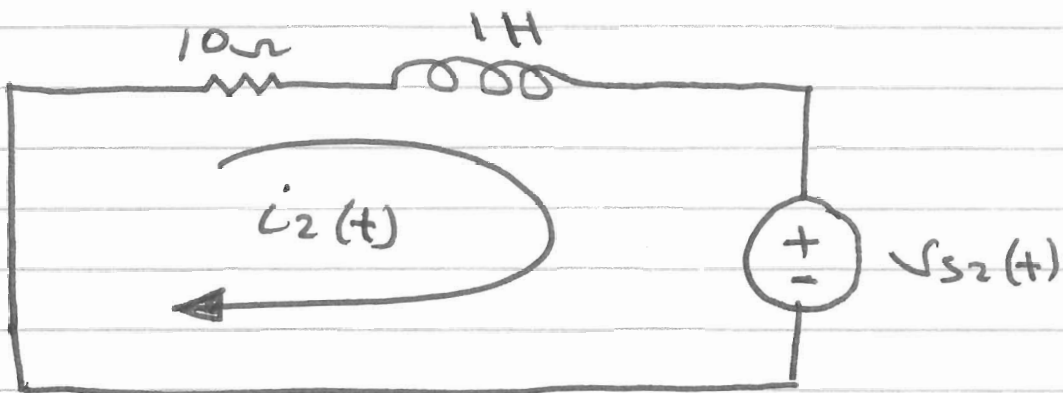2) let  $v_{s1}(t)$  OFF, and  $v_{s2}(t)$  ON


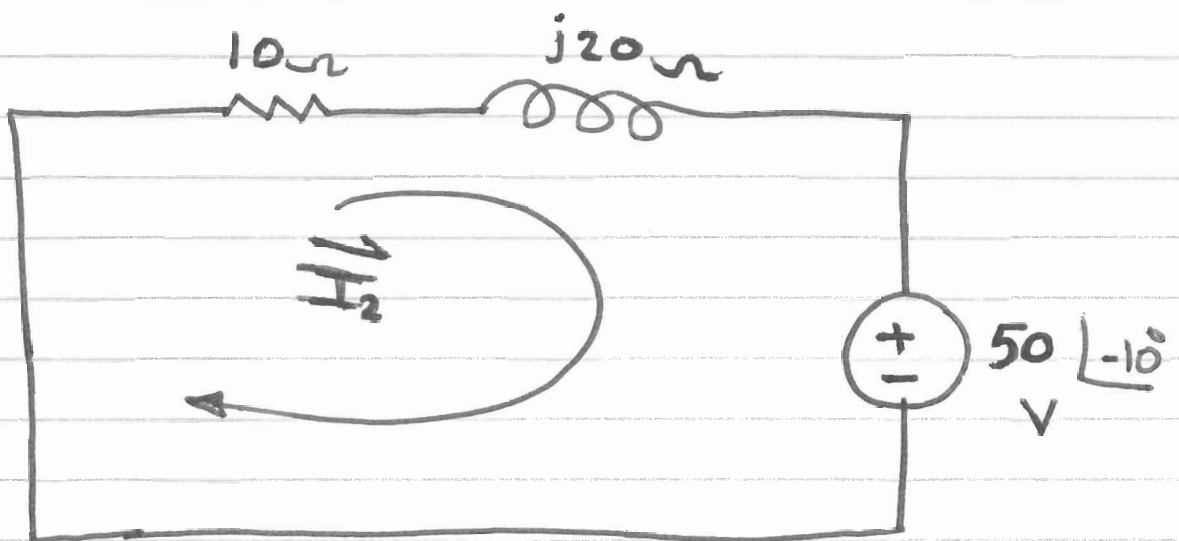
$$v_{s2}(t) = 50 \cos(20t - 10^\circ) \text{ V}$$



$$\vec{I}_2 = \frac{-50 \angle -10^\circ}{10 + j20} = \frac{50 \angle 170^\circ}{10 + j20}$$

$$\vec{I}_2 = 2.24 \angle 106.57^\circ \text{ A}$$


$$\therefore i_2(t) = 2.24 \cos(20t + 106.57^\circ) \text{ A}$$

$$\therefore i(t) = i_1(t) + i_2(t)$$


$$i(t) = 7.07 \cos(10t - 45^\circ) \text{ A}$$

$$+ 2.24 \cos(20t + 106.57^\circ) \text{ A}$$

# Thevenin's and Norton's Theorems

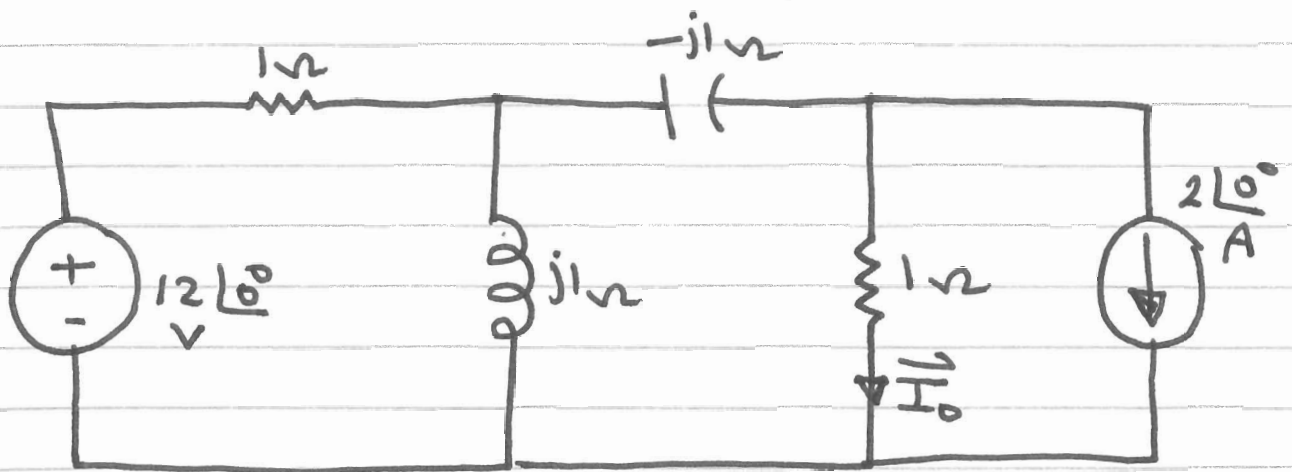


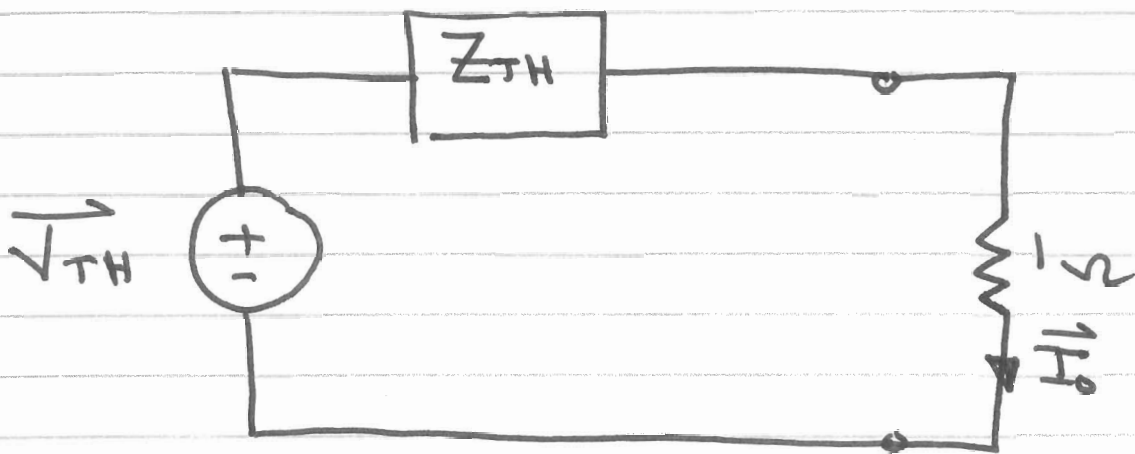Find  $\vec{I}_0$  using Thevenin's theorem



$$\vec{I}_0 = \frac{\vec{V}_{TH}}{Z_{TH} + 1\Omega}$$

1) To find  $\vec{V}_{TH}$

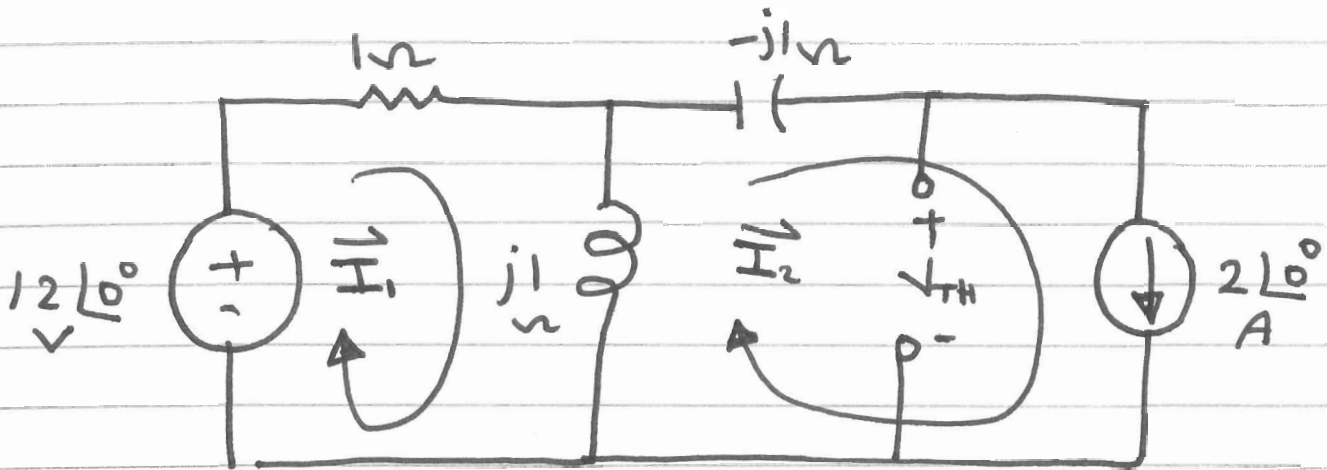

$$\vec{V}_{TH} = -(-j1\Omega) \vec{I}_2 + j1\Omega (\vec{I}_1 - \vec{I}_2)$$

$$\vec{I}_2 = 2\angle 0^\circ \quad \text{constraint equation}$$


KVL for mesh 1 :

$$12\angle 0^\circ = (1+j1) \vec{I}_1 - j1 \vec{I}_2$$

$$\therefore \vec{I}_1 = \left( \frac{12+j2}{1+j1} \right) \text{ A}$$


$$\therefore \vec{V}_{TH} = \left( \frac{-2+j12}{1+j1} \right) \text{ V}$$

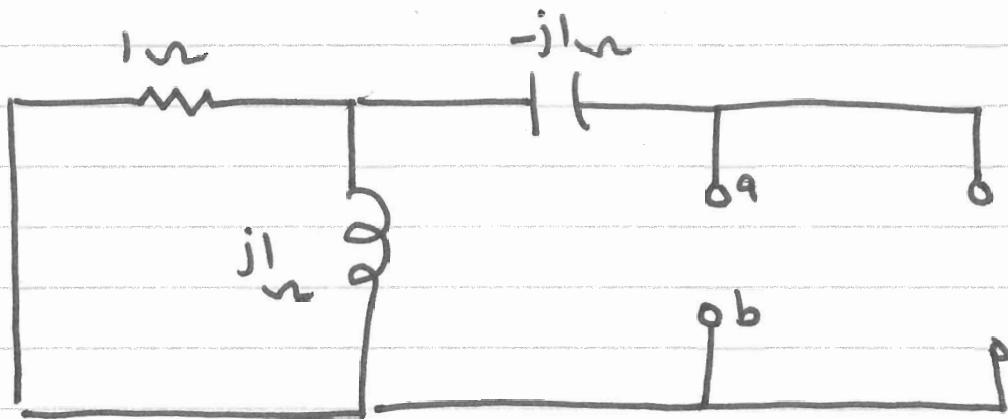2) To find  $Z_{TH}$ , set all the independent sources to zero



$$Z_{TH} = -j1 + (1 \parallel j1)$$
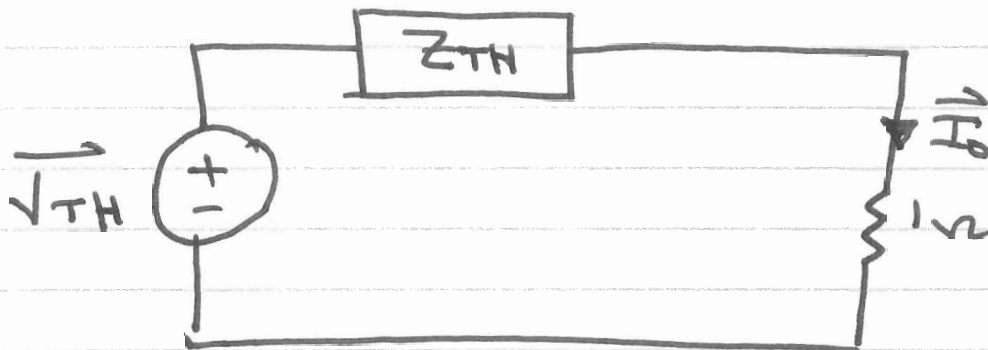
$$Z_{TH} = \left(\frac{1}{2} - j\frac{1}{2}\right)\ \Omega$$




$$\vec{I}_0 = \frac{\vec{V}_{TH}}{Z_{TH} + 1\ \Omega}$$


$$I_0 = \left(\frac{8}{5} + j\frac{26}{5}\right)\ A$$



# Norton's Theorem

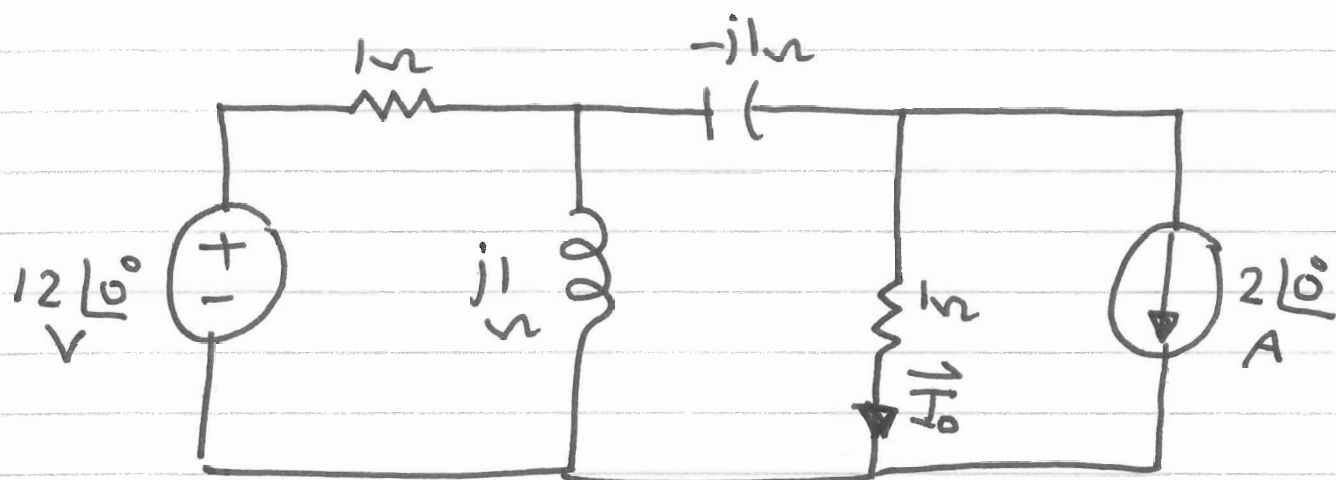


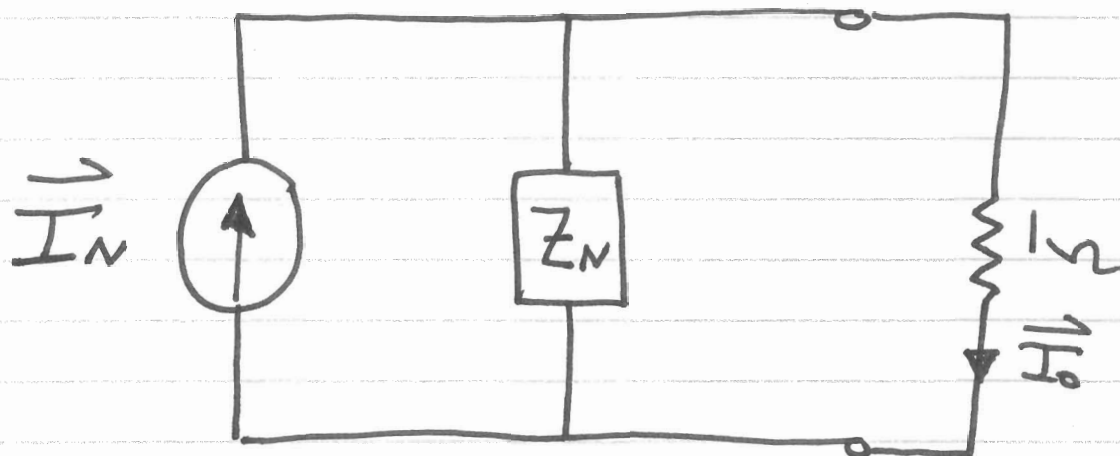Find  $\vec{I}_0$  using Norton's theorem



$$\vec{I}_0 = \vec{I}_N \frac{Z_N}{Z_N + 1\Omega}$$

1) To find  $I_N$

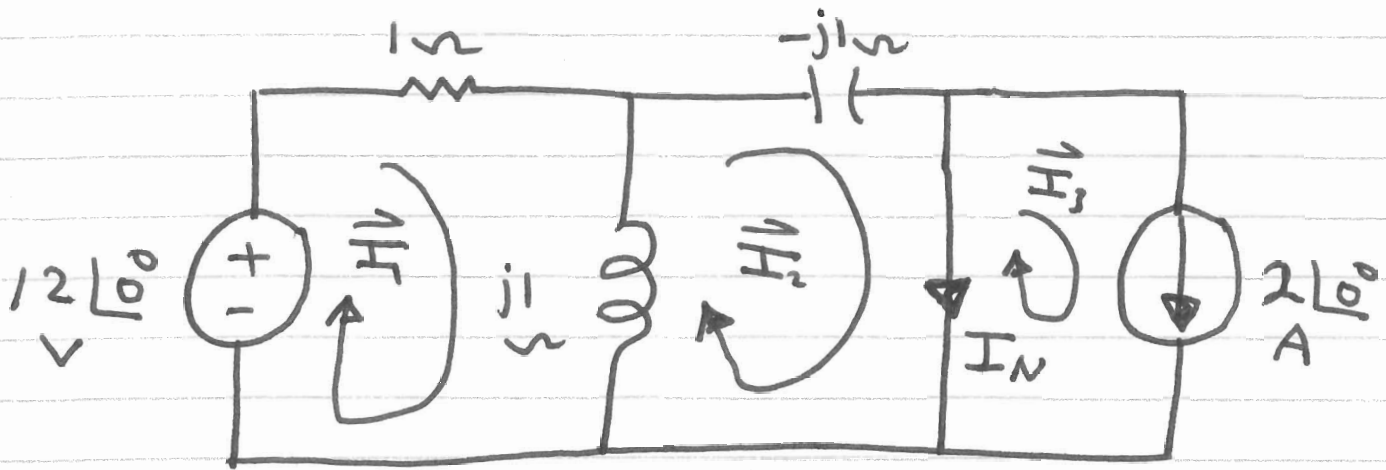

$$\vec{I}_N = \vec{I}_2 - \vec{I}_3$$

$$\vec{I}_3 = 2\angle 0^\circ \text{ A} \quad \text{Constraint equation}$$

KVL for mesh 1:

$$12\angle 0^\circ = (1+j1)\vec{I}_1 - j1\vec{I}_2$$

KVL for mesh 2:

$$0 = -j1\vec{I}_1 + (j1-j1)\vec{I}_2$$


$$0 = -j1\vec{I}_1$$

$$\therefore \vec{I}_1 = 0$$

$$\therefore \vec{I}_2 = 12\angle 90^\circ \text{ A}$$

$$\therefore \vec{I}_N = \vec{I}_2 - \vec{I}_3 = -2 + j12$$

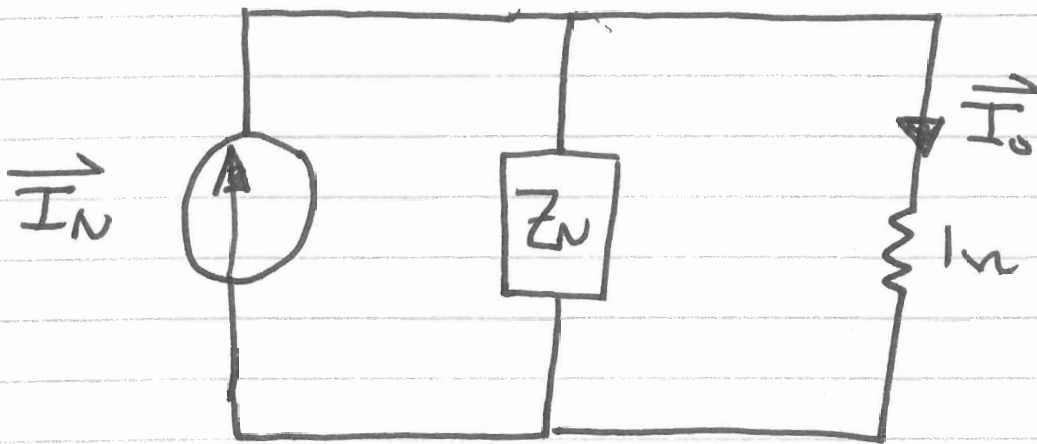
$$Z_N = Z_{TH} = \left(\frac{1}{2} - j\frac{1}{2}\right) \Omega$$




$$\vec{I}_0 = \vec{I}_N \frac{Z_N}{Z_N + 1 \Omega}$$

$$\vec{I}_0 = \left(\frac{8}{5} + j\frac{26}{5}\right) A$$

# Thevenin's Theorem

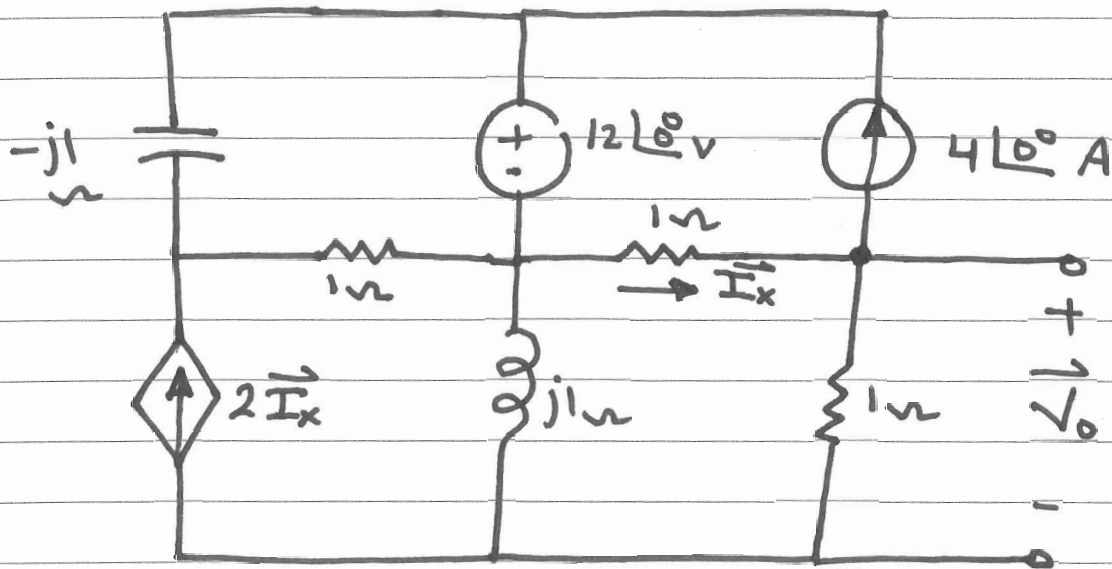


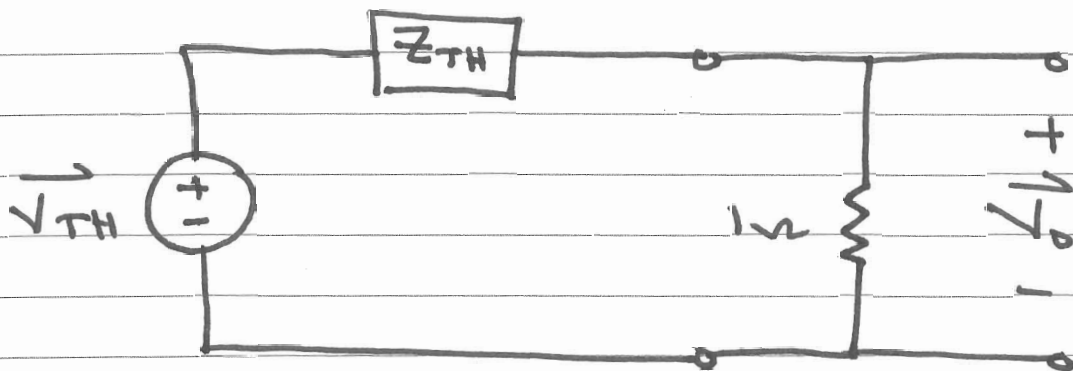Find  $\vec{V}_o$  using Thevenin's theorem



$$\vec{V}_o = \frac{1\Omega}{1\Omega + Z_{TH}} \vec{V}_{TH}$$

1) To find  $\vec{V}_{TH}$

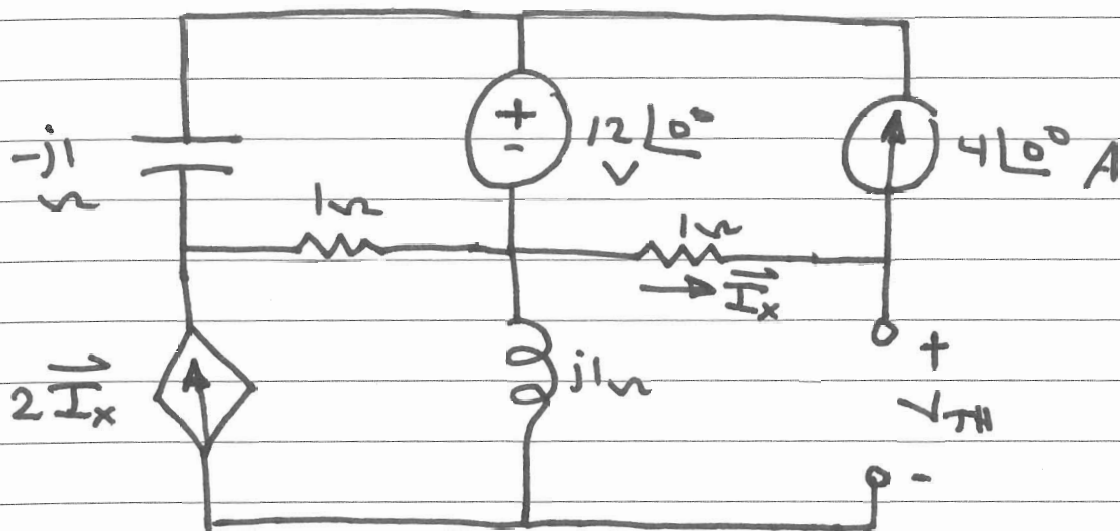

$$\vec{V}_{TH} = -1 \vec{I}_x + j1 (2\vec{I}_x)$$

$$\vec{I}_x = 4 \angle 0^\circ \text{ A}$$

$$\therefore \vec{V}_{TH} = (-4 + j8) \text{ V}$$

2) To find  $Z_{TH}$


$$a) Z_{TH} = \frac{\vec{V}_{TH}}{\vec{I}_x}$$

$$b) Z_{TH} = \frac{\vec{V}_x}{\vec{I}_x}$$

all independent sources are set to zero

$$a) Z_{TH} = \frac{\vec{V}_{TH}}{\vec{I}_N}$$

To find  $\vec{I}_N$

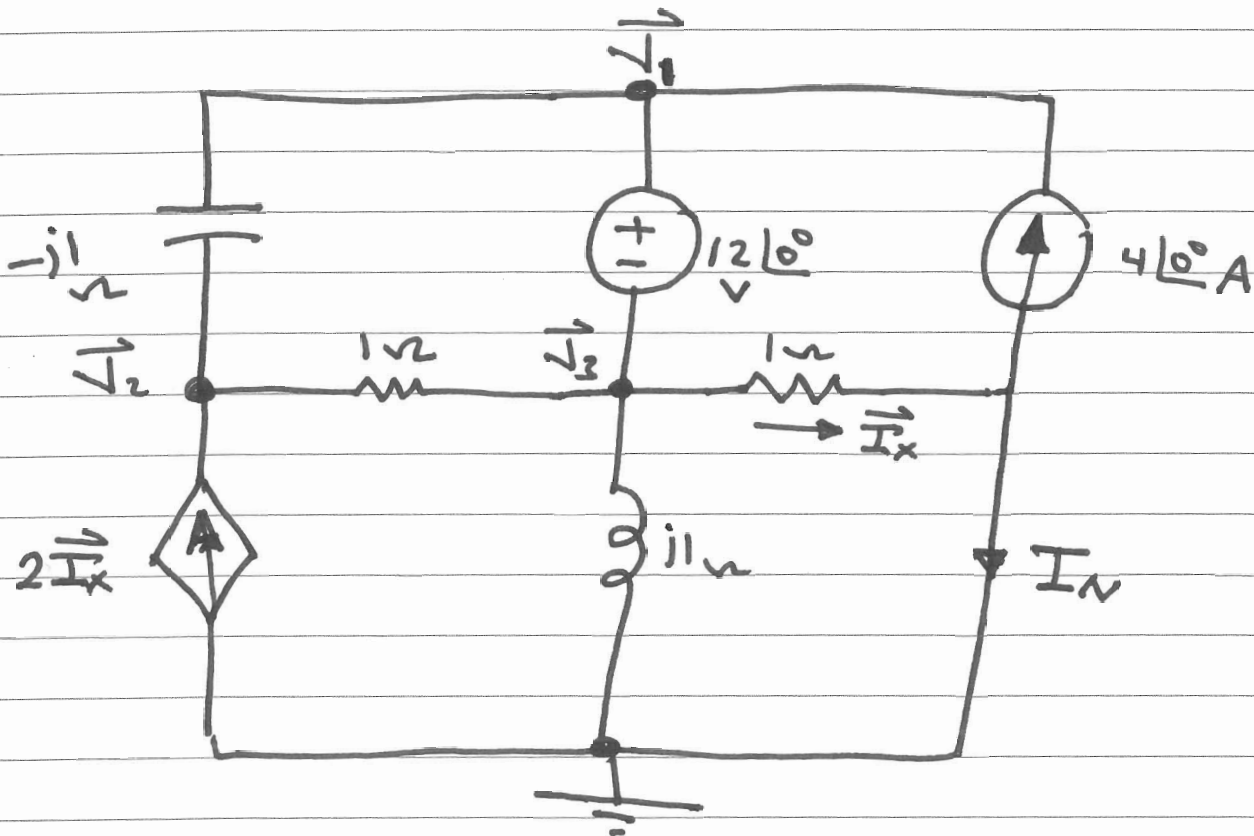

$$\vec{I}_N = \vec{I}_x - 4\angle 0^\circ$$

$$\vec{I}_x = \frac{\vec{V}_2}{1\Omega} = \vec{V}_2$$

Nodal Analysis

$$\vec{V}_2 - \vec{V}_3 = 12\angle 0^\circ \quad \text{Constraint equation}$$

KCL at node 2 :

$$2\vec{I}_x = \left(1 + \frac{1}{-j1}\right)\vec{V}_2 + jV_1 - 1V_3$$

KCL for the Supernode (1,3)

$$4 \angle 0^\circ = \left( \frac{1}{-j1} \right) V_1 + \left( 1+1 + \frac{1}{j1} \right) V_3 - \left( 1 + \frac{1}{-j1} \right) V_2$$

Solving for  $\vec{V}_3$

$$\vec{V}_3 = \frac{4j}{1-j1}$$


$$\therefore \vec{I}_N = - \left( \frac{8+j4}{1+j1} \right)$$

$$\therefore Z_{TH} = \frac{\vec{V}_{TH}}{\vec{I}_N}$$

$$Z_{TH} = (1-j1) \Omega$$

$$\therefore \vec{V}_o = \frac{-4+j8}{1+1-j} = 4 \angle 143.13^\circ \text{ V}$$

$$b) Z_{TH} = \frac{\vec{V}_T}{\vec{I}_T} \quad \left| \quad \text{independent sources are } \text{3oo} \right.$$

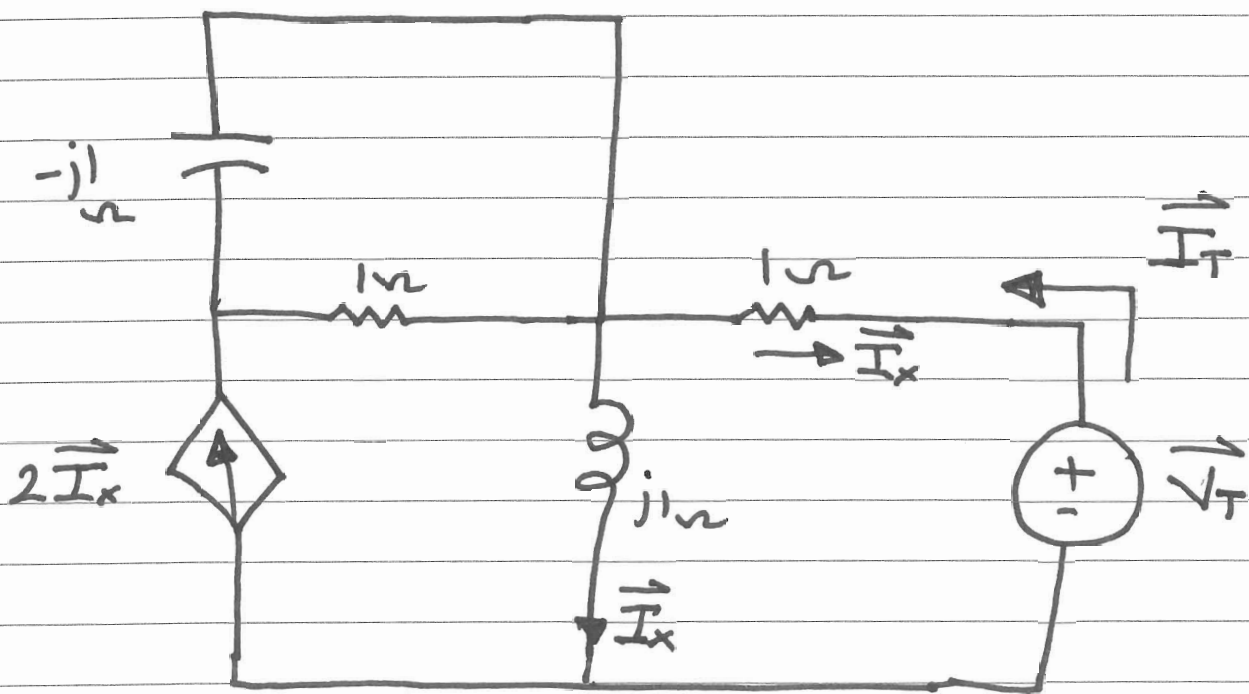

$$\vec{V}_T = -1(\vec{I}_x) + j1(\vec{I}_x)$$

$$\vec{V}_T = (-1 + j1)\vec{I}_x$$

$$\vec{I}_x = -\vec{I}_T$$

$$\vec{V}_T = (-1 + j1)\vec{I}_T$$

$$\therefore Z_{TH} = \frac{\vec{V}_T}{\vec{I}_T} = (1 - j1)\Omega$$