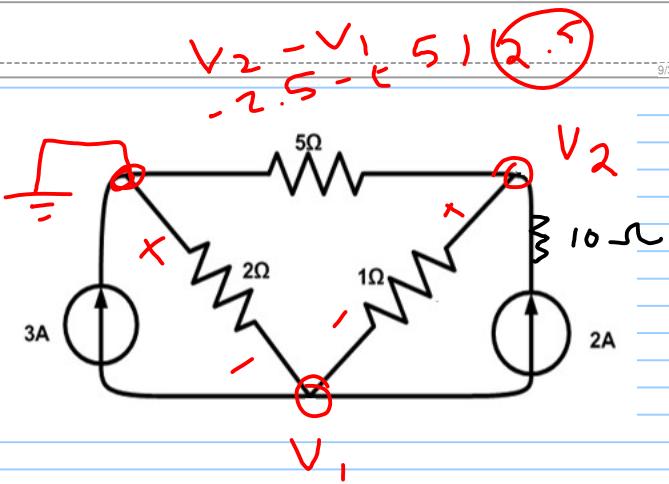


$$C_L = 4$$

Nodal method

@ node V_1

All currents are out
OR $\sum I_{out} = \sum I_{in}$



$$I_{out} = 3 + \frac{V_1}{2} + \frac{V_1 - V_2}{1} + 2 = 0$$

$$\sum I_{out} = 0 \quad \text{OR}$$

$$\sum I_{in} = 0$$

@ Node V_2

$$I_{out} = -2 + \frac{V_2 - V_1}{1} + \frac{V_2}{5} = 0$$

$$-V_1 + 1.2V_2 = 2 \quad \text{--- (2)}$$

$$V_1 = -5 \text{ V}$$


$$V_2 = -2.5 \text{ V}$$

@ node V_1

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_1 - \left(\frac{1}{R_1}\right)V_2 = I_{S1}$$

@ node V_2

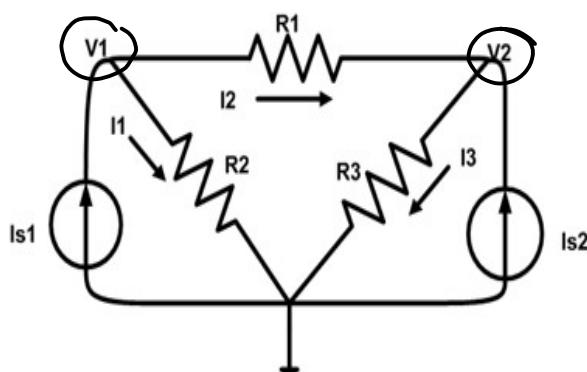
$$-\left(\frac{1}{R_1}\right)V_1 + \left(\frac{1}{R_1} + \frac{1}{R_3}\right)V_2 = I_{S2}$$



@ node 1

$$\sum I_{out} = \sum I_{in}$$

$$7V_1 - 3V_2 - 4V_3 = -11 \quad (1)$$

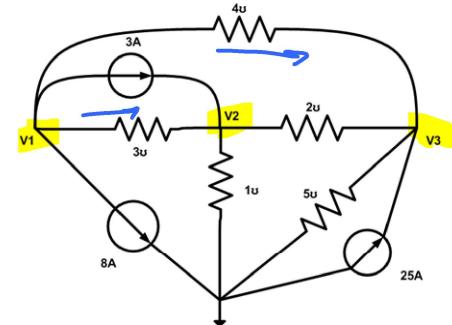

@ node V_2

$$3(V_1 - V_2) + 4(V_1 - V_3) + 3 + 8 = 0$$


$$-(3)V_1 + (3+2+1)V_2 - (2)V_3 = 3 \quad (2)$$

@ node V_3

$$-4V_1 - 2V_2 + (5+2+4)V_3 = 25 \quad (3)$$

$\left[\begin{matrix} E \\ X \end{matrix} \right]$

$$\sum I_{out} = 2 \text{ cmv}$$

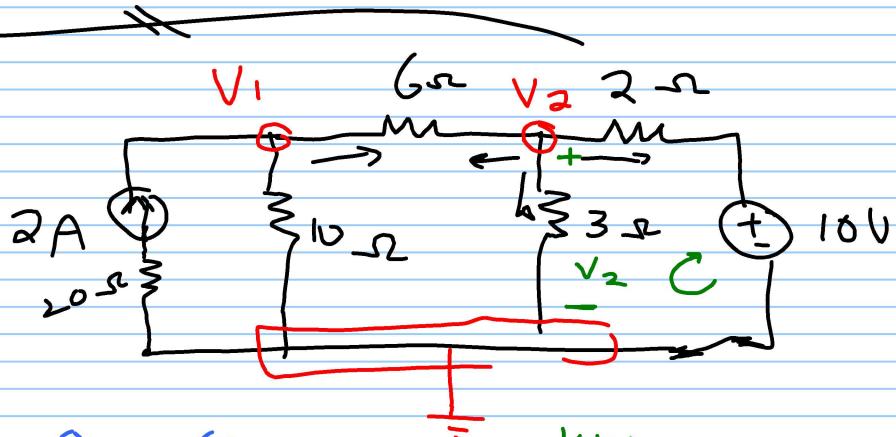

~~node 1~~

$$-2 + \frac{V_1}{10} + \frac{V_1 - V_2}{6} = 0 \quad (1)$$

KVL

~~node 2~~

$$\sum I_{out} = 0$$

$$-V_2 + 2I_X + 10 = 0$$


$$\frac{V_2 - V_1}{6} + \frac{V_2}{3} + \frac{V_2 - 10}{2} = 0 \quad (2)$$

$$I_X = \frac{V_2 - 10}{2}$$

$$V_1 = \underline{\hspace{2cm}}$$

$$V_2 = \underline{\hspace{2cm}} \quad \checkmark$$

EX

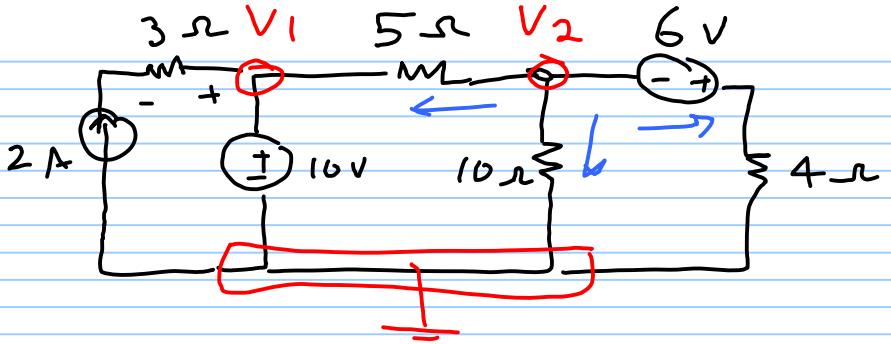

$$\text{A} \quad V \\ (-2) + (V_1 - 10) \times \cancel{\text{X}}$$

$$V_1 = 10 \text{ V} \quad \text{U10}$$


@ node V_2

$$\frac{V_2 - 10}{5} + \frac{V_2}{10} + \frac{V_2 + 6}{4} = 0$$

$$0.55V_2 = 2 - 1.5$$

$$V_2 = \frac{0.5}{0.55} = 0.909 \text{ Volt}$$

EX

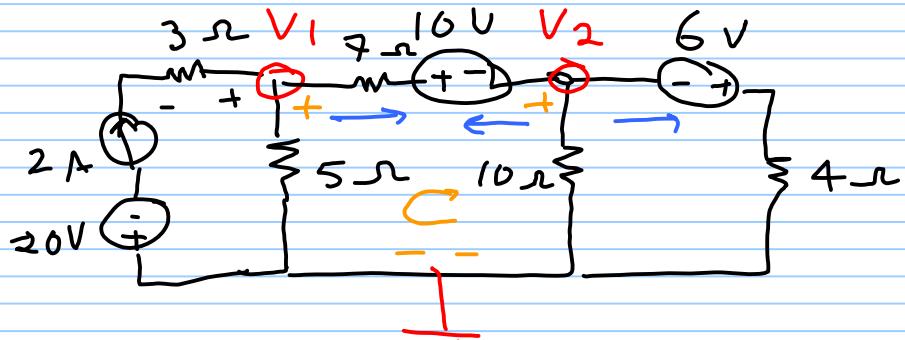

$$\sum I_{\text{out}} = 2 \text{ A}$$

@ node V_1

$$-2 + \frac{V_1}{5} + \frac{V_1 - 10 - V_2}{7} = 0 \quad \text{--- (1)}$$

$$-V_1 + 7I_x + 10 + V_2 = 0$$

@ node V_2

$$\frac{V_2 - V_1 + 10}{7} + \frac{V_2}{10} + \frac{V_2 + 6}{4} = 0 \quad \text{--- (2)}$$

Special Case


E-X

@ node V_1

$$-2 + \frac{V_1}{5} + I_x = 0$$

$$-2 + \frac{V_1}{5} + \frac{V_2 + 6}{10} + \frac{V_2 + 6}{4} = 0 \quad \text{--- (1) KVL}$$

$$V_1 - V_2 = 10$$

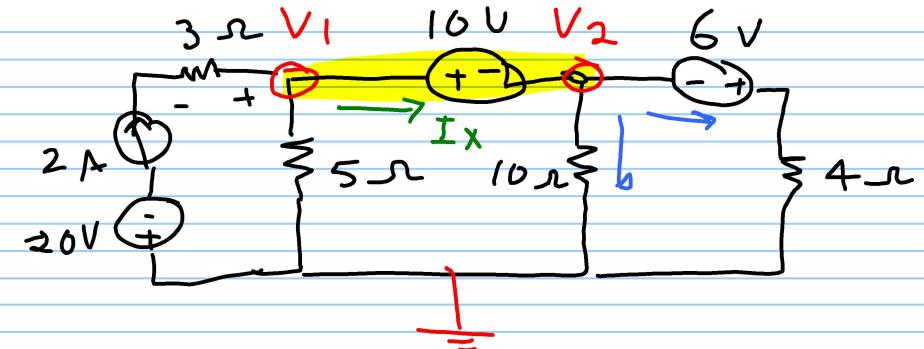

E-X

$$I_o = \frac{V_2}{3k} \quad \text{--- (1)}$$


@ node V_1

$$2I_o + \frac{V_1}{12k} + \frac{V_1 - V_2}{6k} = 0$$

$$2\left(\frac{V_2}{3k}\right) + \frac{V_1}{12k} + \frac{V_1 - V_2}{6k} = 0 \quad \text{--- (1)} \quad \text{↓↓↓}$$

@ node V_2
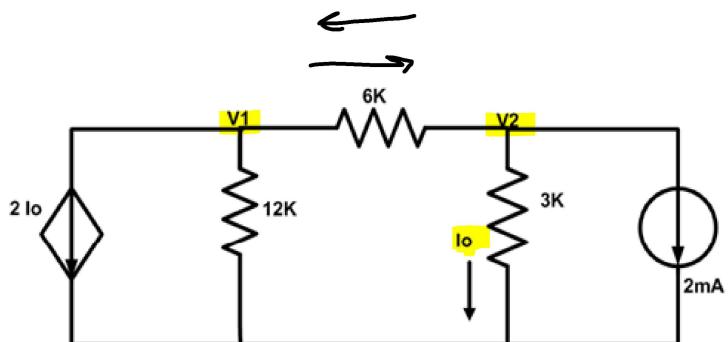
$$\frac{V_2 - V_1}{6k} + \frac{V_2}{3k} + 2mA = 0 \quad \text{--- (2)} \quad \text{↓↓↓}$$



$$V_1 = -\frac{24}{5} V \quad , \quad V_2 = \frac{12}{5} V$$


Mesh method

$$I_{R_2} = I_A$$

$$I_{R_2} = I_A - I_C$$


$$I_{R_{13}} = -I_D$$

$$I_{R_{10}} = I_B - I_A$$

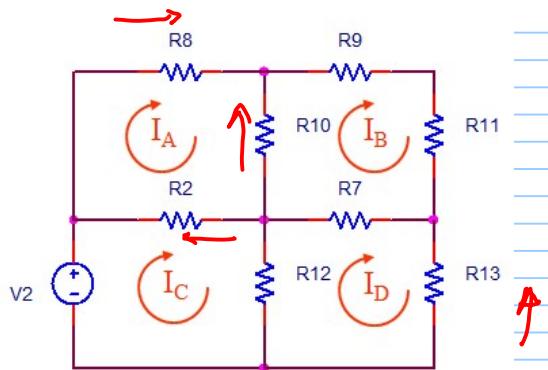

4 equations

4 unknowns I_A, I_B, I_C
X I_D

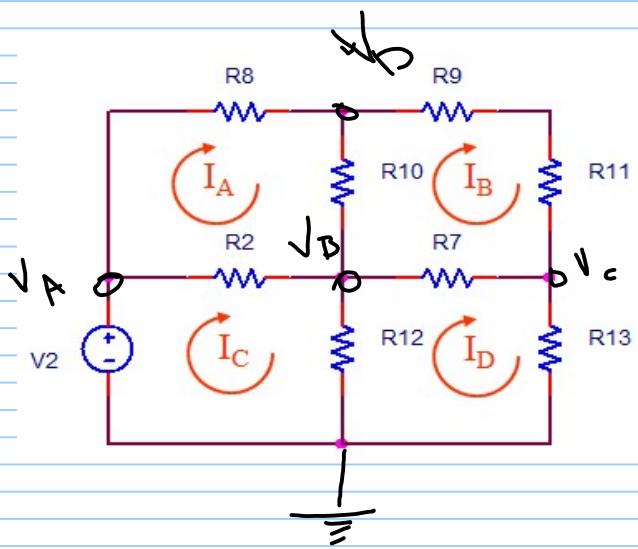


$V_A = V_2$

Nodal method

3 eqs

3 unknowns

$V_{B, C \& D}$

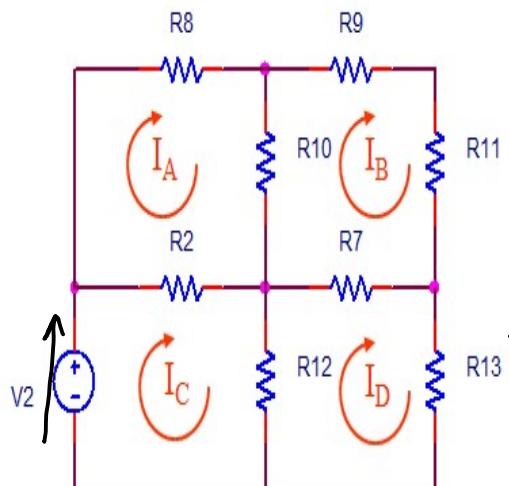

Mesh KV L

$$R_8 I_A + R_{10} (I_A - I_B) + R_2 (I_A - I_C) = 0$$

$$(R_8 + R_{10} + R_2) I_A - R_{10} I_B - R_2 I_C = 0 \quad (1)$$

$$- (R_{10}) I_A + (R_{10} + R_9 + R_{11} + R_7) I_B$$

$$- R_7 I_D = 0 \quad (2)$$

$$-V_2 + R_2 (I_C - I_A) + R_{12} (I_C - I_D) = 0$$

$$(R_2 + R_{12}) I_C - R_2 I_A - R_{12} I_D = V_2 \quad (3)$$

$$(R_{12} + R_7 + R_{13})I_D - 0I_A - R_7I_B - R_{12}I_C = 0 \quad \text{--- (4)}$$

Ex

$$-42 + 6I_1 + 3(I_1 - I_2) = 0$$

$$9I_1 - 3I_2 = 42 \quad \text{--- (1)}$$

$$-3I_1 + 7I_2 = 10 \quad \text{--- (2)}$$

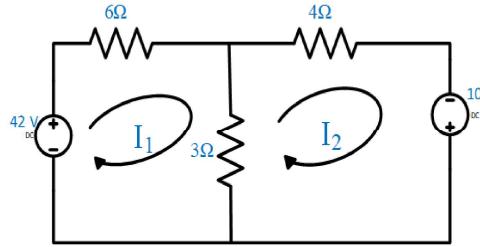


Figure 3: example 1 of mesh analysis

6A, 4A

special case 1 current source exists
only in one mesh

Ex

$$I_2 = -5A \quad \checkmark$$

$$-10 + 4I_1 + 6(I_1 - 5) = 0$$

$$I_1 = -2A \quad \checkmark$$

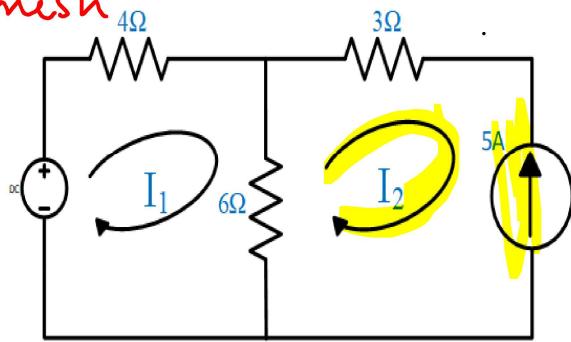


Figure 6: mesh with current source.

Case 2:

Current source exists between two meshes, a **Super mesh** is obtained

→ KVL for mesh (2)

$$(1+2+3)I_2 - (1)I_1 - (3)I_3 = 0 \quad \text{--- (1)}$$


→ constraint equation

$$I_1 - I_3 = 7 \quad \text{--- (2)}$$

→ Super mesh equation

$$-7 + (1)(I_1 - I_2) + (3)(I_3 - I_2) + (1)I_3 = 0$$
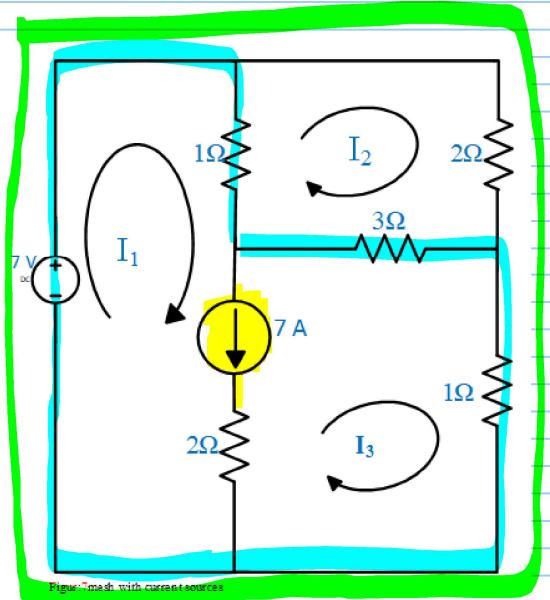
$$I_1 - 4I_2 + 4I_3 = 7 \quad \text{--- (3)}$$



$$I_3 = -7 \text{ A} \times$$

OR

$$-7 + 2I_2 + I_3 = 0 \quad \text{--- (3)*}$$

EX] Mesh Analysis with dependent sources

$$\rightarrow V_x = (3)(I_3 - I_2)$$

$$I_1 = 15 \text{ A} \quad \checkmark$$

→ constraint equation

$$\frac{V_x}{9} = I_3 - I_2$$

$$\frac{3}{9}(I_3 - I_2) = I_3 - 15$$

$$\frac{3}{9}I_2 + \frac{2}{3}I_3 = 15$$


$$I_2 + 2I_3 = 45 \quad \text{--- (1)}$$

$$(1)(I_2 - 15) + (2)I_2 + (3)(I_2 - I_3) = 0$$

$$6I_2 - 3I_3 = 15 \quad \text{--- (2)}$$

$$I_2 = 11 \text{ A} \quad \checkmark$$

$$I_3 = 17 \text{ A} \quad \checkmark$$

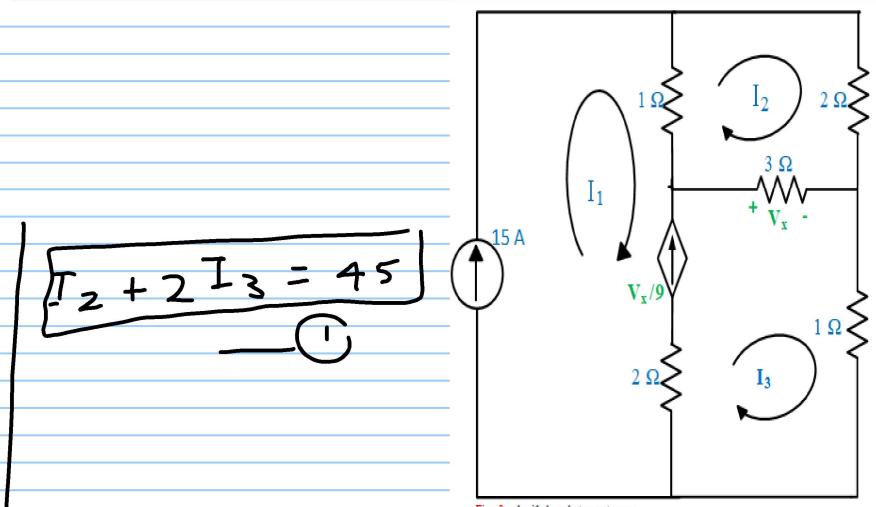


Node or mesh: How to choose?

- Use the one with fewer equations.
- Use the method you like best.


Slides

Source Transformation

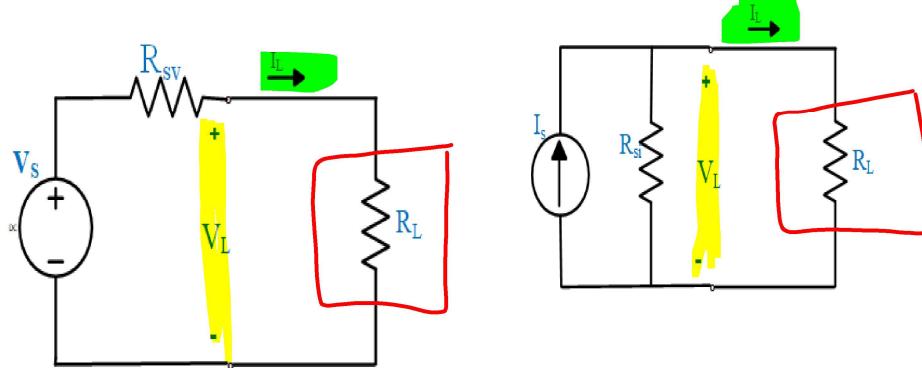

Two sources are equivalent, if each produces identical current and identical voltage in any load which is placed across its terminal.

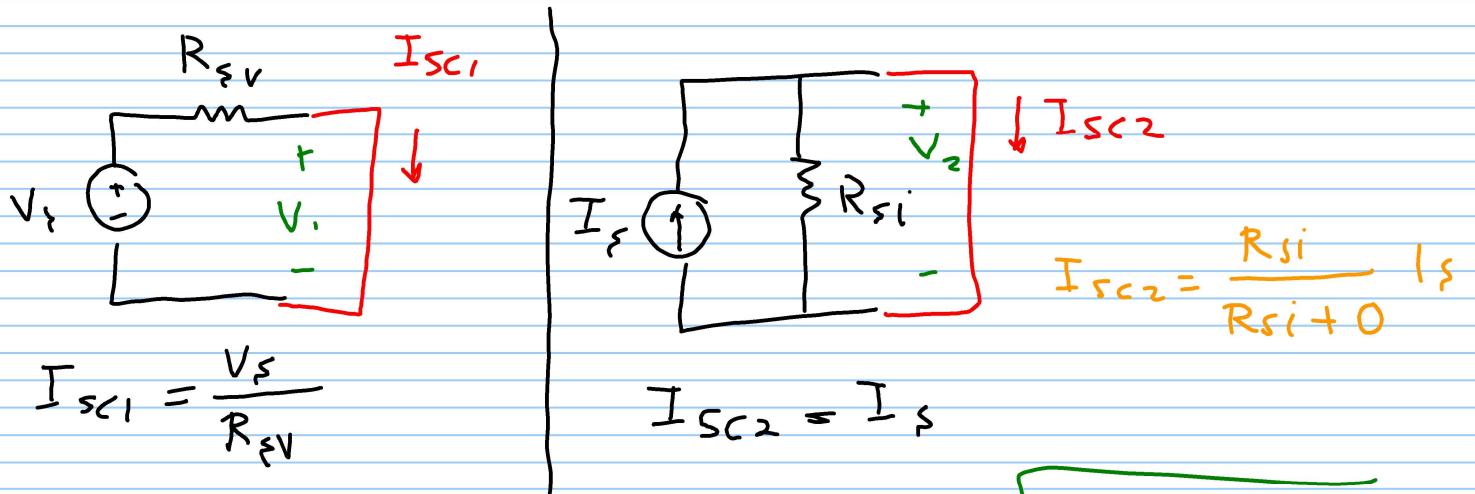→ let $R_L = \text{zero}$ (short circuit sc.)





for $I_{sc1} = I_{sc2}$

$$I_s = \frac{V_s}{R_{sv}}$$

$$V_1 = V_2 = 2 \text{ v}$$

→ let $R_L = \infty$ (open circuit)

$$I_1 = I_2 = \text{zero}$$

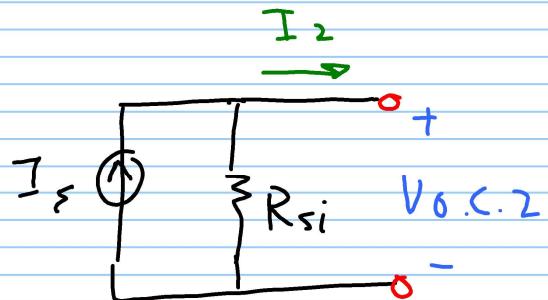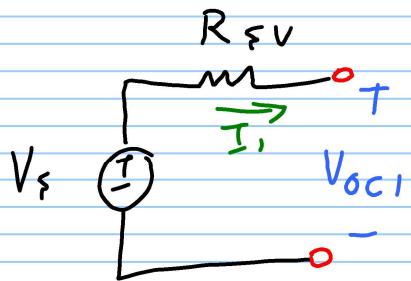

$$V_{oc1} = V_s$$

$$V_{oc2} = I_s R_{si}$$

$$\text{For } V_{oc1} = V_{oc2}$$




$$V_s = I_s R_{si}$$

$$\text{GR} \quad I_s = \frac{V_s}{R_{si}}$$

$$I_s = \frac{V_s}{R_{fv}}$$


$$\text{or } R_{si} = R_{fv}$$

E-X find V_o

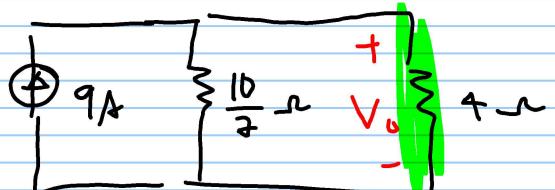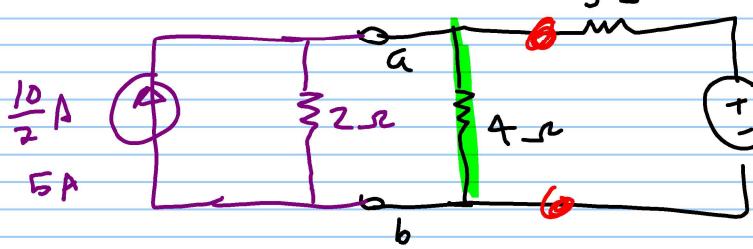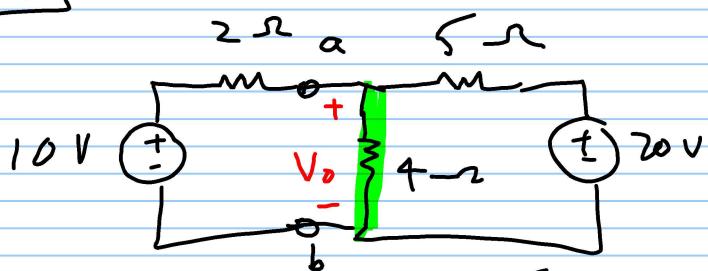

$$\left(\frac{10/7}{10/7 + 4} \cdot 9 \right) (4) = V_o$$

$$V_o = 9.47 \text{ Volt. } \checkmark$$

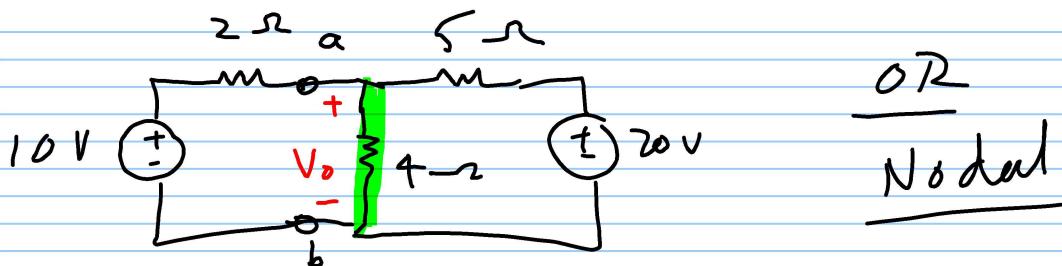

$$\frac{V_o - 10}{2} + \frac{V_o}{4} + \frac{V_o - 20}{5} = 0$$

$$V_o \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{5} \right) = \frac{10}{2} + \frac{20}{5}$$

$$V_o (0.95) = 9$$

$$V_o = 9.473 \text{ Volt.}$$


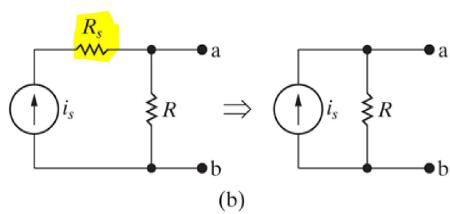


Figure: 04-39a,b
Copyright © 2008 Pearson Prentice Hall, Inc.

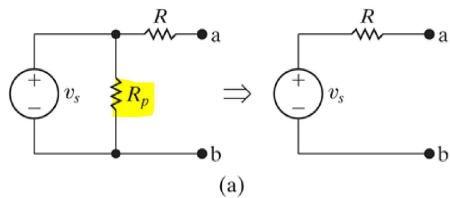- The two circuits depicted in Fig. 4.39(a) are equivalent with respect to terminals a,b because they produce the same voltage and current in any resistor R_L inserted between nodes a,b.
- The same can be said for the circuits in Fig. 4.39(b).



Thevenin

Norton eq. circuit

Example: Find V_o using source transformation



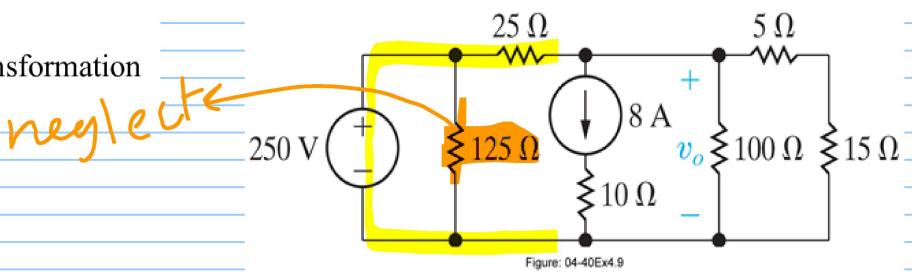
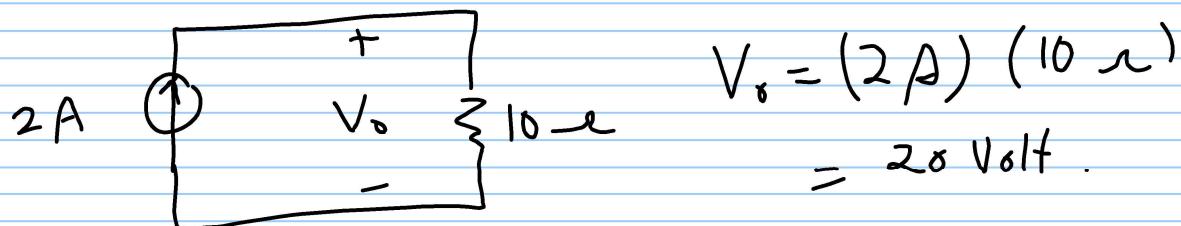
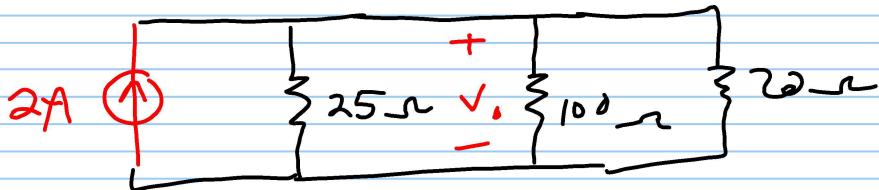





Figure: 04-40Ex4.9
Copyright © 2008 Pearson Prentice Hall, Inc.

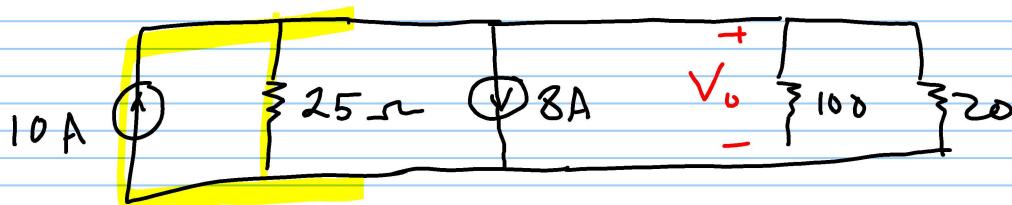


Dependent sources

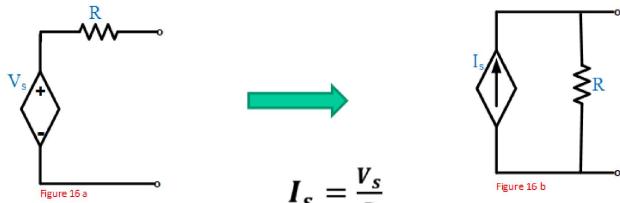

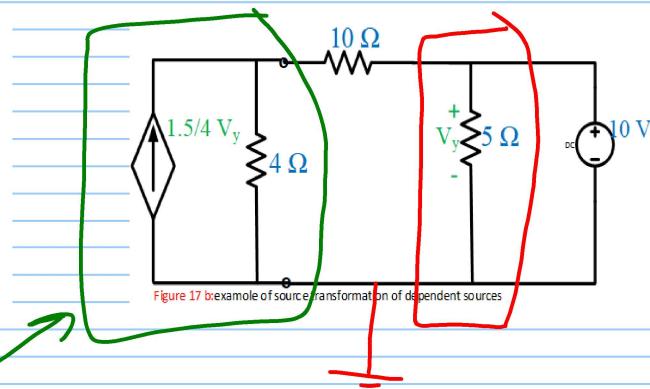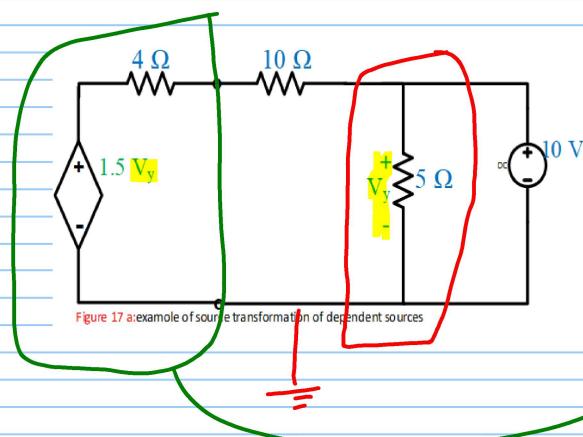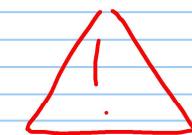The control variable must be outside the transformation.



OR

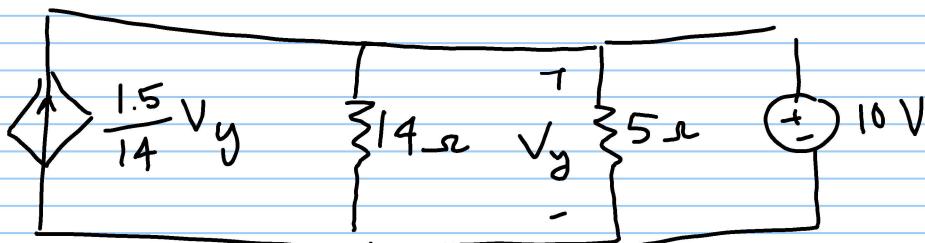

The Superposition Theorem

In a linear network, the voltage across or the current through any element may be calculated by adding algebraically all the individual voltages or currents caused by the separate independent sources acting alone, i.e. with:

- ① All other independent voltage sources replaced by short circuits.
- ② All other independent current sources replaced by open circuits.
- ③ Dependent sources are left intact because they are controlled by circuit variables.




Steps to apply superposition principle


- Turn off all independent sources except one source. Find the output (voltage or current) due to that source using nodal, mesh.... .
- Repeat step 1 for each of the other independent sources.
- Find the total contribution by adding algebraically all contributions due to each independent sources.

E X)

find (I) using
superposition

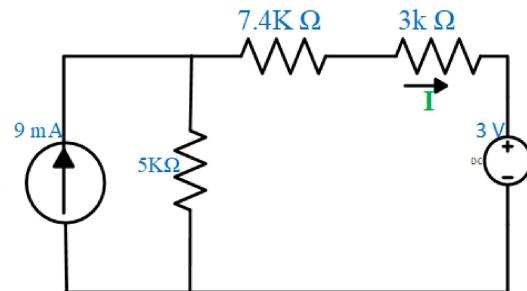


① I_1 due to (9 mA)

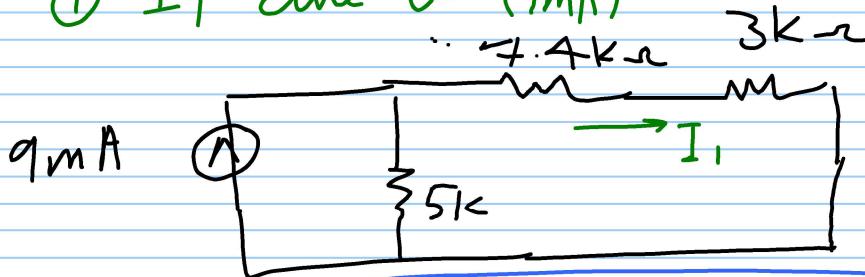

$$I_1 = \frac{5k}{5k + 7.4k + 3k} \times 9m = 2.922 \text{ mA}$$

② I_2 due to (3 V)

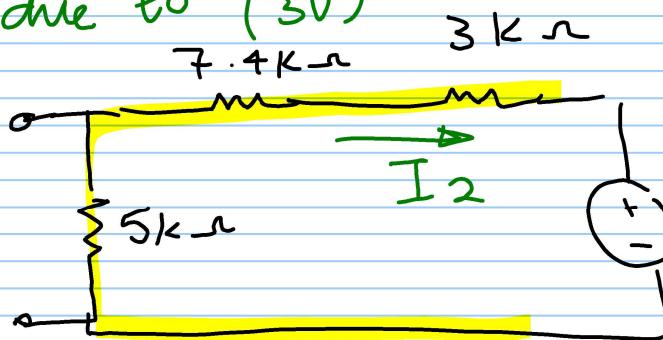


$$I_2 = \frac{-3}{15.4k} = -0.194 \text{ mA}$$

$$\therefore I = I_1 + I_2$$

$$= 2.992 - 0.194$$

$$= 2.728 \text{ mA}$$

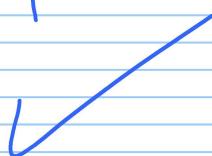

Use superposition to solve for i_x

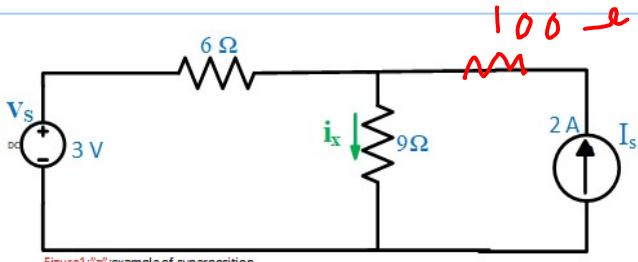


Figure 1: "a" example of superposition


① i_{x_1} due to (3V)

$$i_{x_1} = \frac{3}{9+6} = 0.2 \text{ A}$$


② i_{x_2} due to 2A

$$i_{x_2} = \frac{6}{6+9} 2\text{A} = 0.8 \text{ A}$$
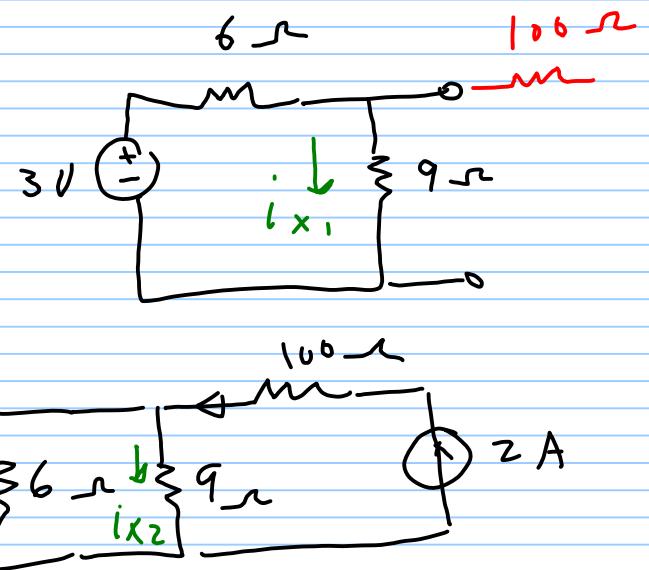
$$\therefore i_x = i_{x_1} + i_{x_2} = 0.2 + 0.8 = 1 \text{ A}$$




EX

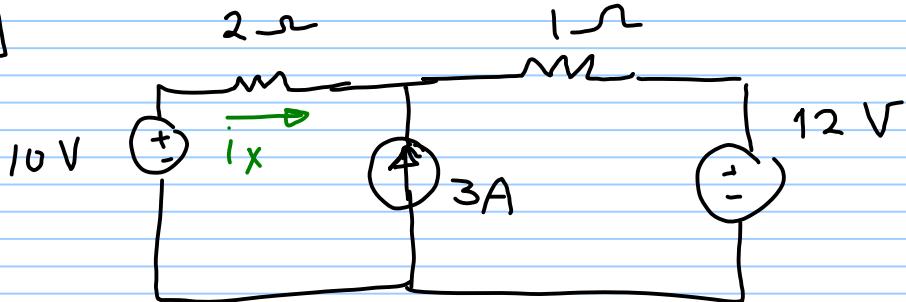


find I_x using superposition.

① i_{x_1} due to (10V)

$$i_{x_1} = \frac{10}{3} \text{ A}$$

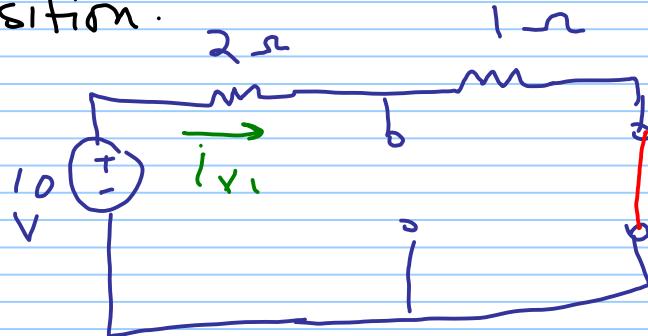


② i_{x_2} due to (3A)

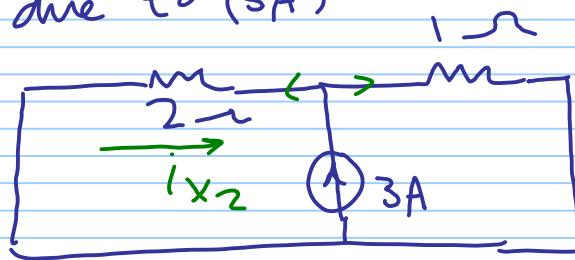

$$i_{x_2} = -\frac{1}{3} \cdot 3 = -1 \text{ A}$$


③ i_{x_3} due to 12V
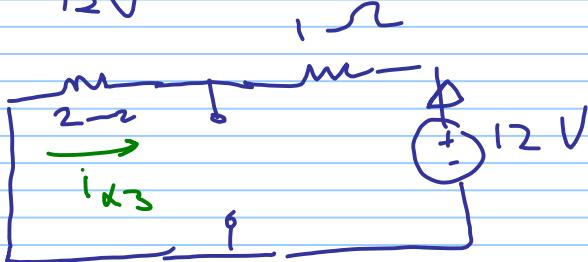
$$i_{x_3} = -\frac{12}{3} = -4 \text{ A}$$



$$\begin{aligned} I_x &= i_{x_1} + i_{x_2} + i_{x_3} \\ &= 3.33 - 1 - 4 \\ &= -1.666 \text{ A} \end{aligned}$$


EX]

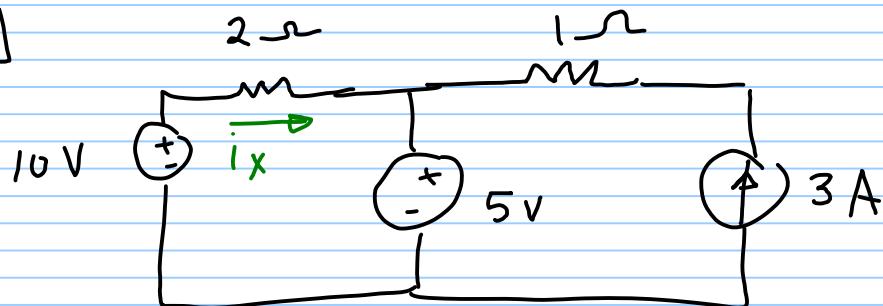

find I_x using superposition.


① i_{x_1} due to (10V)

$$i_{x_1} = \frac{10}{2} = 5 \text{ A}$$

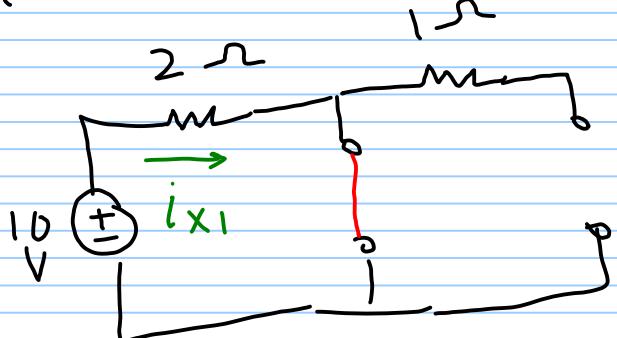


② i_{x_2} due to (5V)
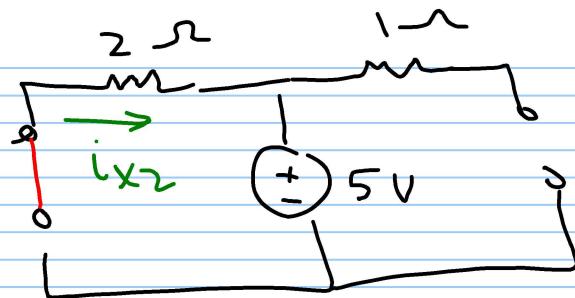
$$i_{x_2} = -\frac{5}{2} = -2.5 \text{ A}$$



③ i_{x_3} due to (3A)

$$i_{x_3} = \text{Zero}$$

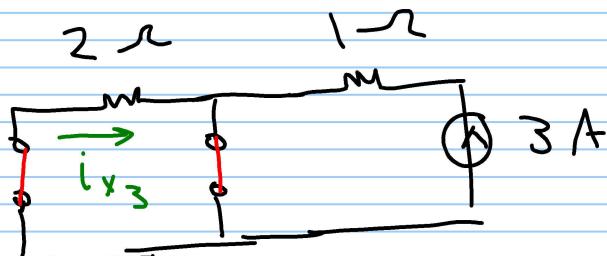


$$\text{or } i_x = i_{x_1} + i_{x_2} + i_{x_3}$$

$$= 5 - 2.5 + 0$$

$$= 2.5 \text{ A}$$

Find I_x using superposition

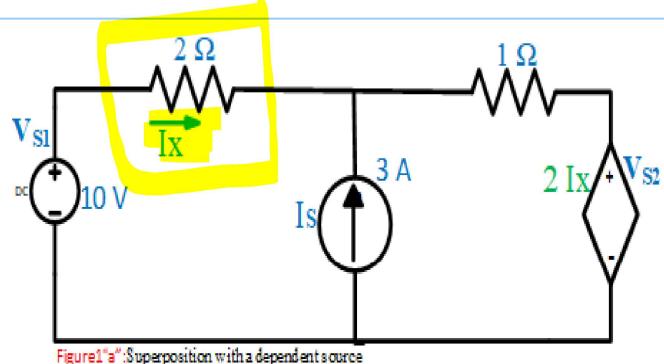


① i_{x_1} due to 10V


KVL

$$-10 + 3i_{x_1} + 2i_{x_1} = 0$$

$$i_{x_1} = 2 \text{ A}$$

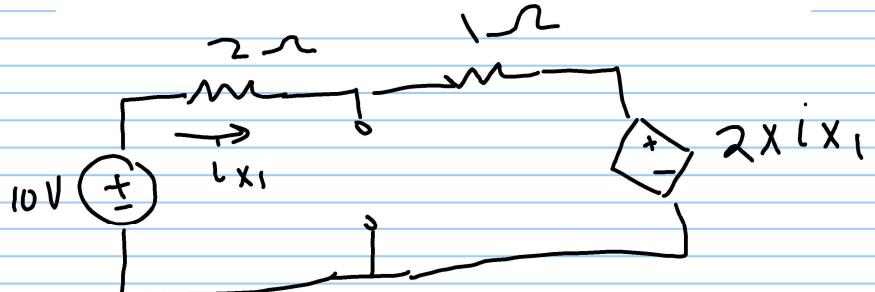

② i_{x_2} due to (3A)

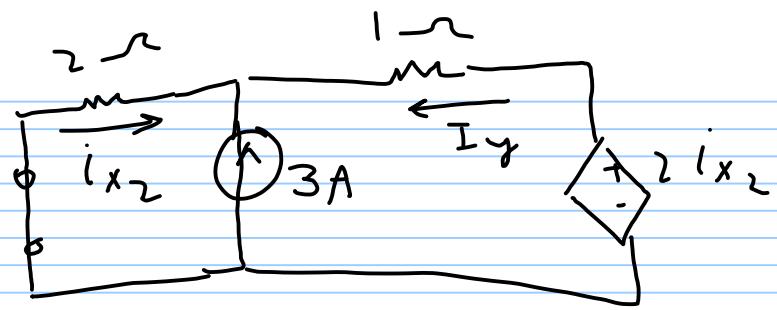

KVL

$$2i_{x_2} - I_y + 2i_{x_2} = 0$$

$$4i_{x_2} - I_y = 0$$

KCL $i_{x_2} + I_y = 3$


$$5i_{x_2} = 3$$

$$i_{x_2} = \frac{3}{5} = -0.6 \text{ A}$$

∴ $I_x = i_{x_1} + i_{x_2} = 2 - 0.6$
 $= 1.4 \text{ A}$


[Ex] Find i_x

$i_x = 10 \text{ A}$

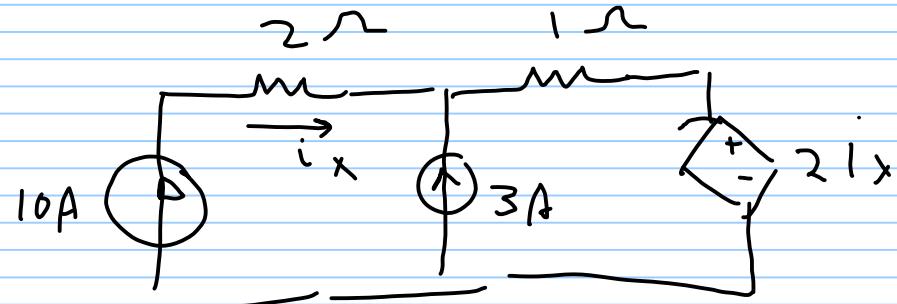


① i_{x_1} due to (10A)

$$i_{x_1} = 10 \text{ A}$$

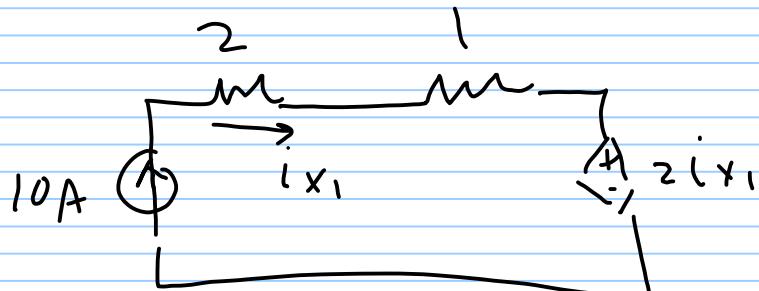



(2) i_{x_2} due to (3A)

$$i_{x_2} = 0$$

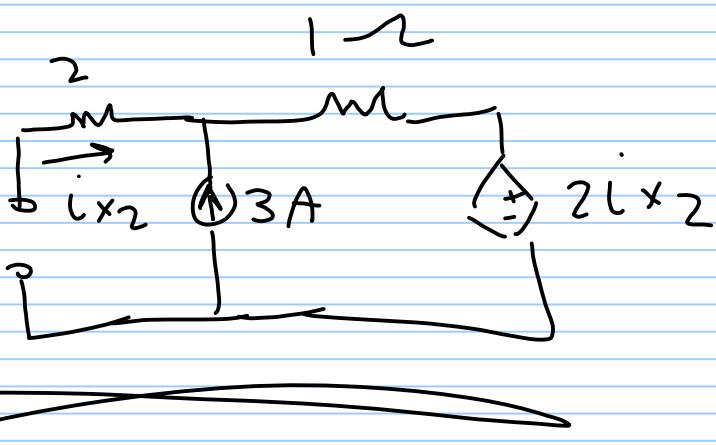

Thevenin & Norton eq. Circuits

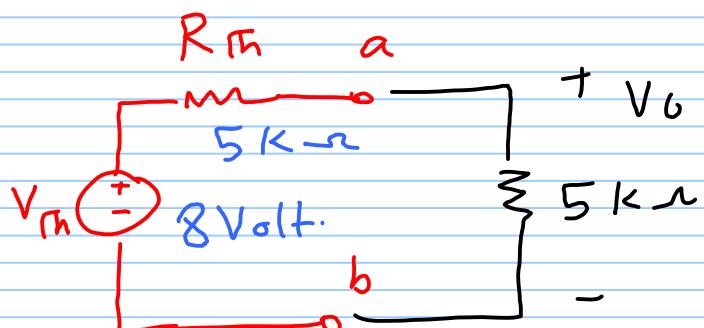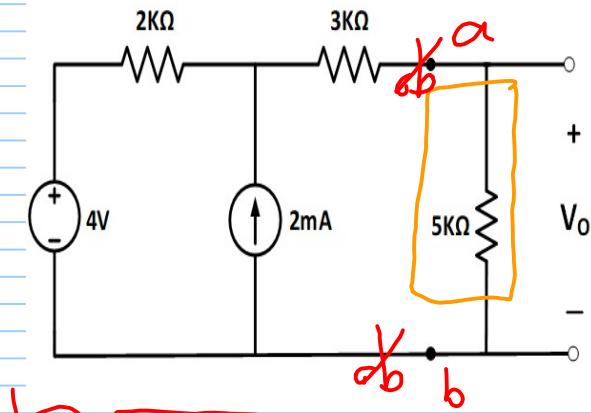Example: Find V_o using thevenin's equivalent circuit




V_{Th}, R_{Th}

→ to find V_{Th}

$$V_{Th} = V_{O.C.}$$
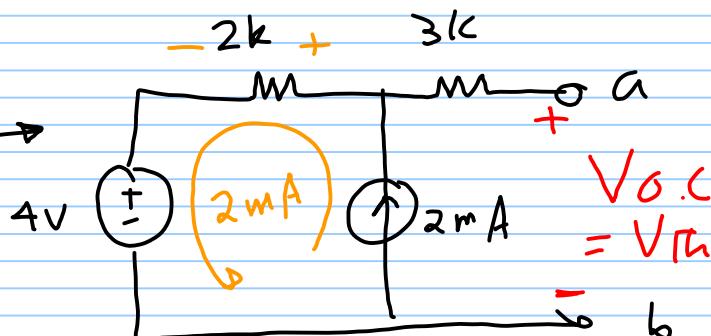
$$\therefore V_{Th} = (2k)(2m) + 4 \\ = 8 \text{ Volt.}$$



→ How to find R_{Th} .


(No dependent sources)

{Best method}

→ Kill all independent sources → set to zero

all indep. V sources $0V \rightarrow S.C.$ (short circuit)

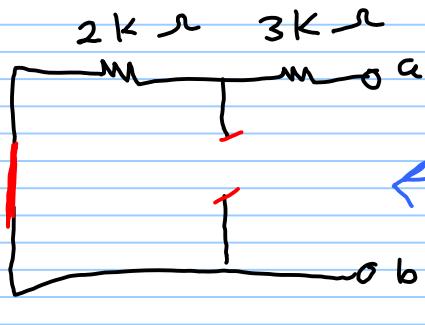
all indep. I sources $0A \rightarrow O.C.$ (open circuit)



$$R_{Th} = 3k + 2k \\ = 5 \Omega$$

J_w^+
 J_w^-

$$V_o = \frac{5}{5+5} * 8 \\ = 4V$$

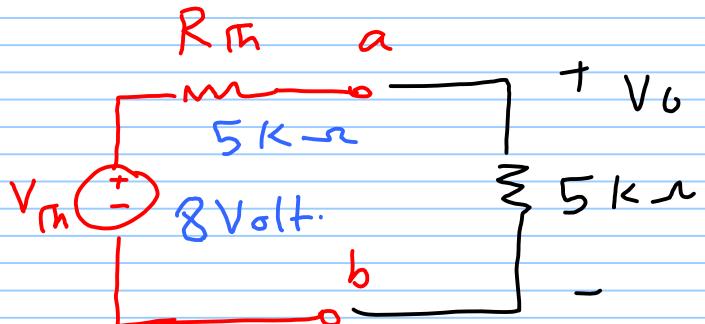

→ to find R_{Th} using $V_{o.c.} \& I_{s.c.}$ ↗ dep. sources ✓ ↗ indep. sources ✓

(Note: you can use this method when there


is NO dep. sources, But → time consuming !!)

method (2)

$V_{o.c.} = 8V$ (the same as before)

$$R_{Th} = \frac{V_{o.c.}}{I_{s.c.}}$$

Find $I_{S.C.}$

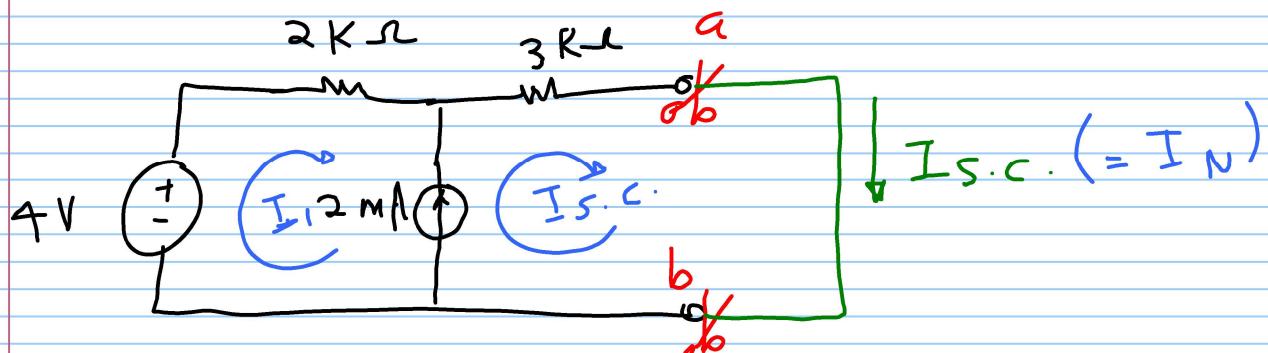

$$2k \times (I_{S.C.} - I_1 = 2 \text{ mA}) \quad (1)$$

$$+ \quad -4 + 2k I_1 + 3k I_{S.C.} = 0$$

$$(3k I_{S.C.} + 2k I_1 = 4) \quad (2)$$

$$5k I_{S.C.} = 8$$

$$I_{S.C.} = \frac{8}{5} \text{ mA}$$

$$= I_N.$$

$$g_o R_{Th} = \frac{V_{o.c.}}{I_{S.C.}} = \frac{8}{\frac{8}{5} \text{ mA}} = 5 \text{ k}\Omega$$


method ③ R_{Th} using test sources

$$R_{Th} = \frac{V_T}{I_T} \quad | \quad \begin{array}{l} \text{dep & indep} \\ \text{sources are set to zero} \end{array}$$

$$\text{let } V_T = 5 \text{ V}$$

$$\text{then } I_T = \frac{V_T}{R_{eq}} = \frac{5}{5 \text{ k}\Omega} = 1 \text{ mA}$$
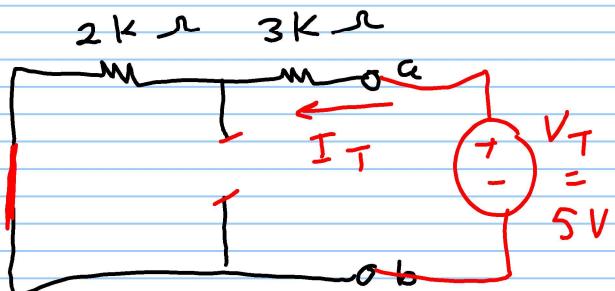
$$\therefore R_{Th} = \frac{5}{1 \text{ mA}} = 5 \text{ k}\Omega \quad \checkmark$$



* methods to Find R_{Th} :-

method 1] if there is no dep. source (best method) (easy one)



→ kill all indep. sources, then find R_{Th} (series/parallel combination)

method 2] $R_{Th} = \frac{V_{o.c.}}{I_{s.c.}}$ General method

can be applied if the circuit has dep. source (also it can be applied if the circuit does not have dep. sources)

method 3] $R_{Th} = \frac{V_T}{I_T}$ / all indep. sources = 0 (dep. sources are left intact.)

Find V_o using Thevenin's theorem

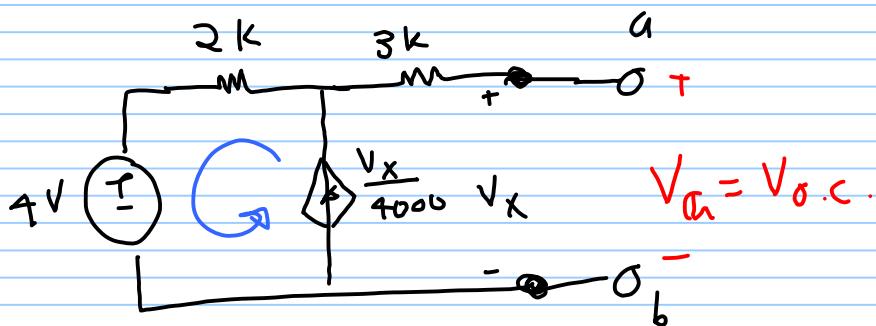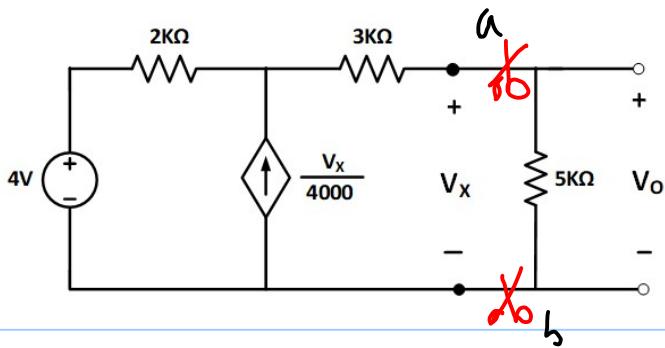

for this
circuit

$$V_{Th} = V_{o.c.} = V_x !$$

$$V_{o.c.} = \left(\frac{V_x}{4000} \right) 2k + 4V = \left(\frac{V_{o.c.}}{4000} \right) 2k + 4$$

$$V_{o.c.} = \frac{1}{2} V_{o.c.} + 4$$

$$V_{o.c.} = 8 \text{ Volt.}$$

to find R_{Th} - method 1 X

method 2 OR method 3 ✓ (dep. source)

method 2 | $V_{O.C.} = 8V$.

find I_{SC} .



$V_X = \text{zero}!!$

$$\frac{V_X}{4000} = 0 \text{ A (o.c.)}$$

$$I_{SC} = \frac{4}{5k} = 0.8 \text{ mA}$$

$$R_{Th} = \frac{V_{O.C.}}{I_{SC}} = \frac{8}{0.8m} = 10k\Omega$$

$$= 10k\Omega \quad \checkmark$$

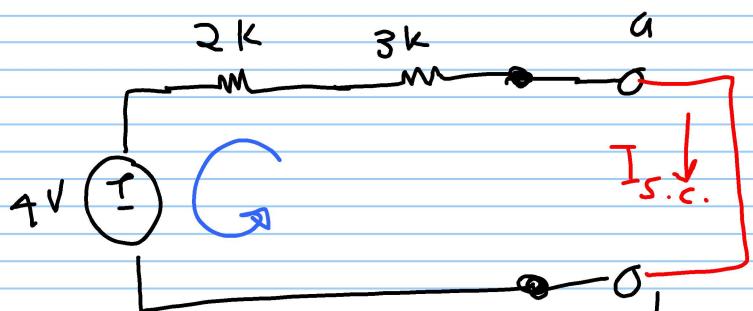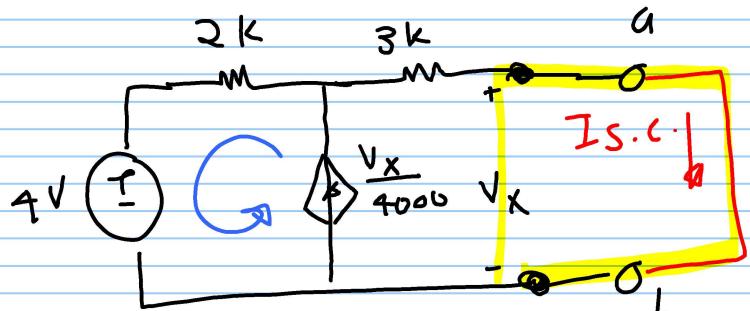

method 3




$$R_{Th} = \frac{V_T}{I_T}$$

all indep. sources killed




let $V_T = 4000 \text{ V}$

$$I_T = \frac{4000 - 2000}{5000} = 0.4 \text{ A}$$
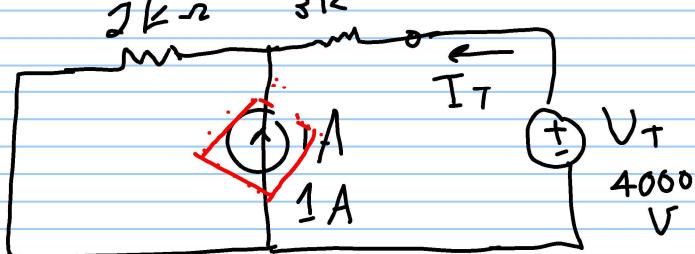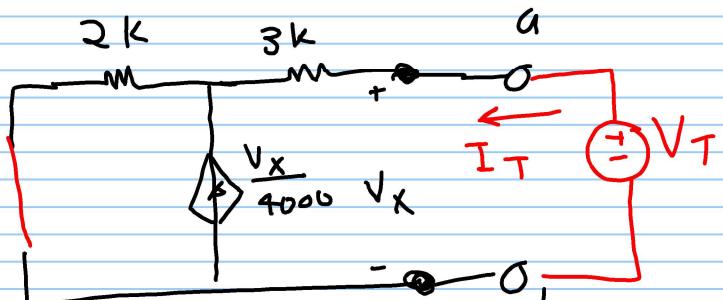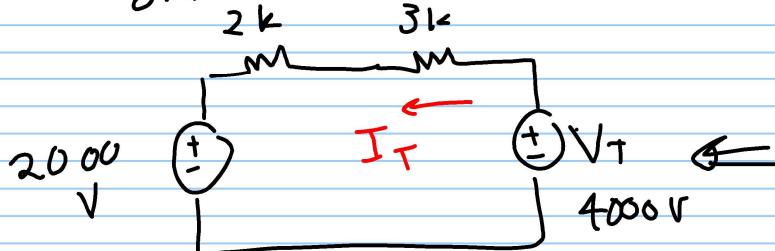
$$R_{Th} = \frac{2000}{0.4} = 10k\Omega$$



Find I_x using Thevenin's theorem

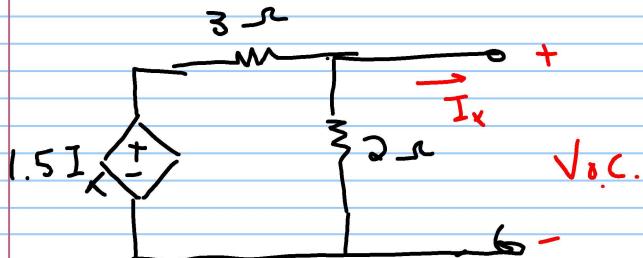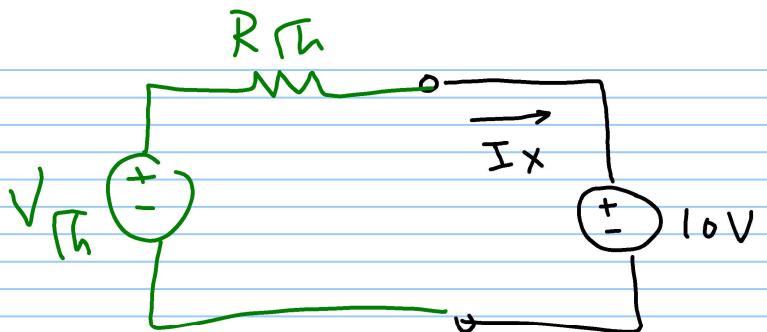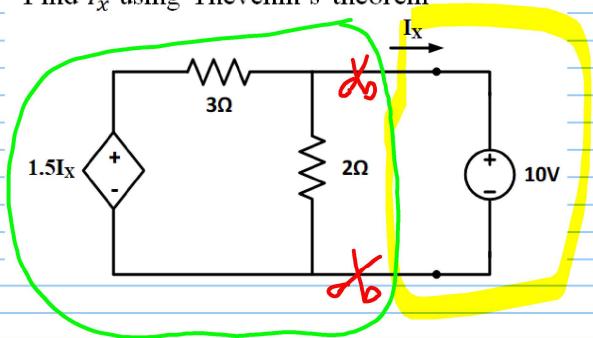

Since there is only dep. sources



$$\therefore V_{o.c.} = V_{Th} = 0 \text{ V}$$

✓ to find R_{Th}


$$R_{Th} = \frac{V_T}{I_T} \mid \text{all indep. sources}$$

are set to zero

method (2) X

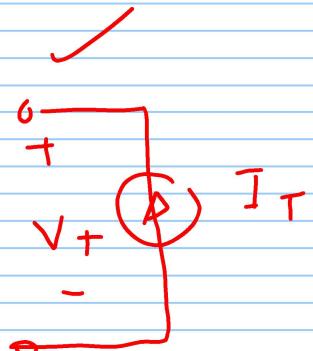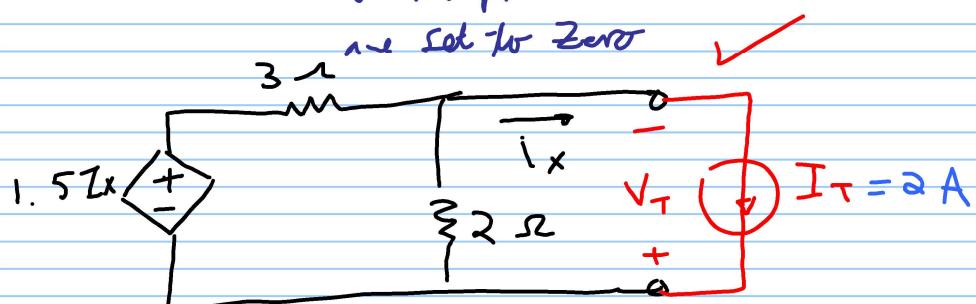
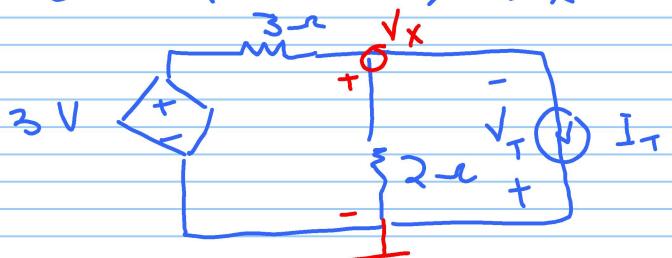
$$\text{let } I_T = 2 \text{ A}, \quad I_x = I_T$$



Nodal

$$\frac{V_x - 3}{3} + \frac{V_x}{2} + 2 = 0$$

$$V_x \left(\frac{1}{3} + \frac{1}{2} \right) = -2 + 1$$

I_T


$$V_x = -\frac{6}{5} \text{ V}$$

$$\therefore V_T = -V_x = \frac{6}{5} \text{ V}$$

$$\therefore R_{Th} = \frac{V_T}{I_T} = \frac{\frac{6}{5}}{2} = 0.6 \Omega \quad \checkmark$$

$$I_x = -\frac{10}{0.6}$$




$$= -16.67 \text{ A}$$

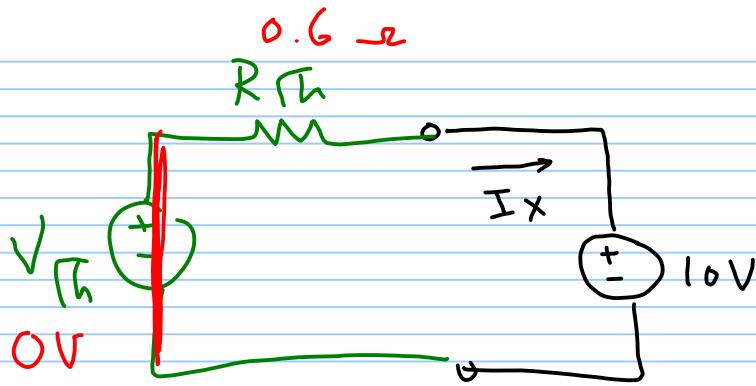

$$R_{Th} = R_N$$

$V_{Th} \rightarrow V_{o.c.}$

$I_N \rightarrow I_{S.C.}$

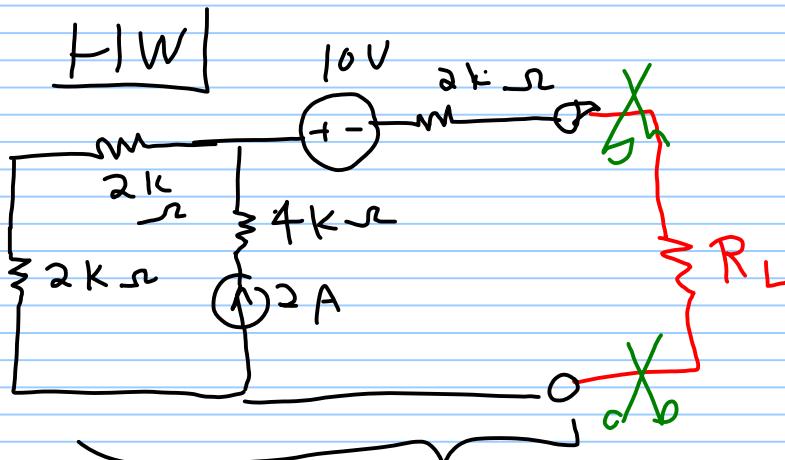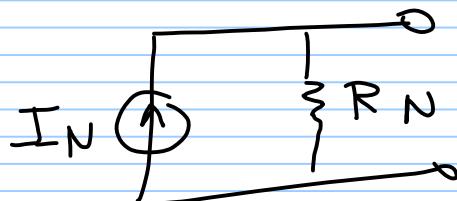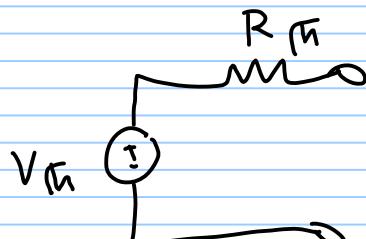

Find the Thévenin eq. circuit.