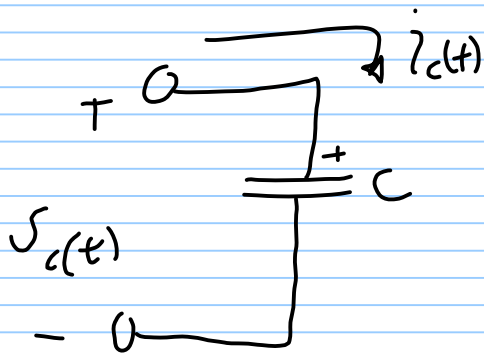


Response of first-order RL & RC circuits



$$i_c(t) = C \frac{d}{dt} v_c(t)$$

$$v_c(t) = \frac{1}{C} \int_0^t i_c(t) dt + \underline{v_c(0)}, \text{ for } t > 0$$


initial voltage
of the capacitor

at $t = 0^+$

$$v_c(0^+) = \frac{1}{C} \int_{0^-}^{0^+} i_c(t) dt + v_c(0^-)$$

$$v_c(0^+) = v_c(0^-)$$

at $t = 0$

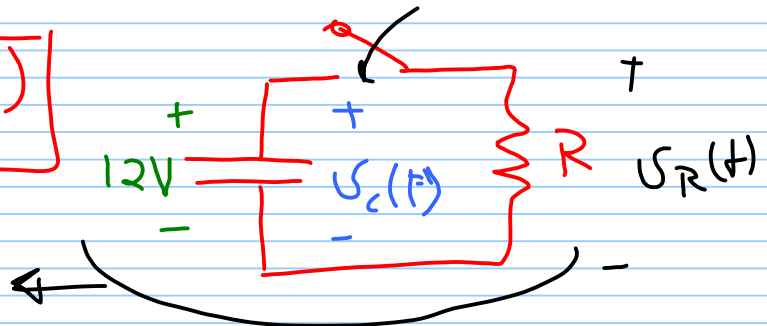

$$v_c(0^-) = 12V$$

$$v_c(0^+) = 12V$$

$$v_c(\infty) = \text{zero}$$

$$v_R(0^-) = \text{zero}$$

$$v_R(0^+) = 12V$$


0.0000001

1. The current through a capacitor is zero if the voltage across it is not changing with time.


$$i_c(t) = C \frac{dV_c(t)}{dt} \quad \rightarrow \text{steady state}$$

∴ at steady state
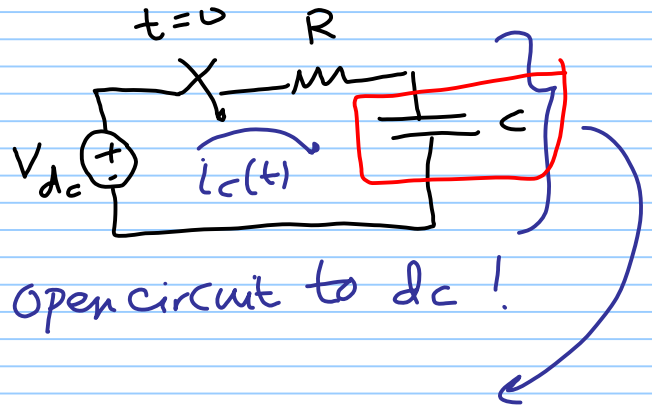
$$\boxed{i_c(\infty)} \text{ OR } \boxed{i_c(\text{steady state})} = \text{zero}$$



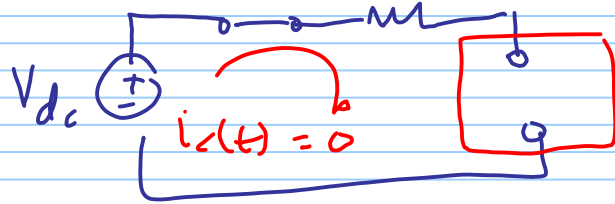A capacitor is therefore an open circuit to dc!




2. A finite amount of energy can be stored in a capacitor even if the current through the capacitor is zero.
3. The capacitor never dissipate energy, but only store it.

$$V_c(0^-) = V_c(0^+)$$


4. it is impossible to change the voltage across a capacitor by a finite amount in zero time,

5. At $t = 0^+$

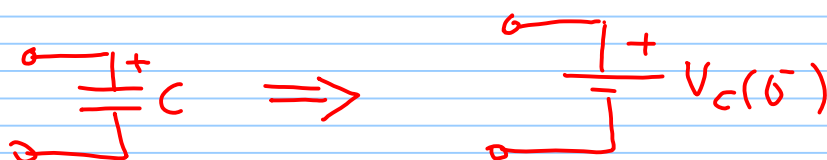




@ $t = 0^+$

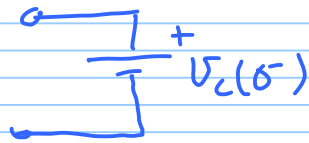


@ $t = \infty$

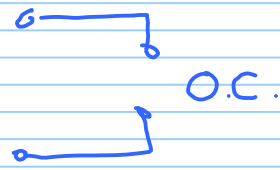


charging


discharging

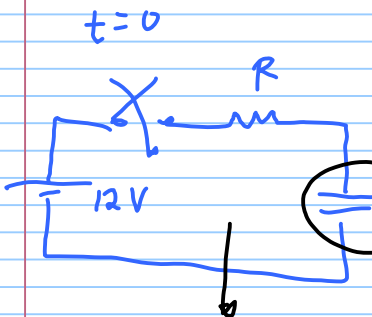

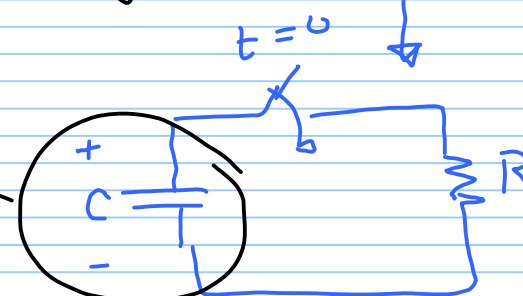@ $t = \infty$
 $V_C(\infty) = 12V$
 $i_C(\infty) = \text{zero}$



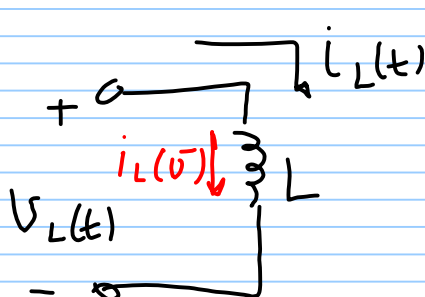@ $t = 0^-$
 $V_C(0^-) = 12V$
 $V_C(0^+) = 12V$
 @ $t = \infty$
 $V_C(\infty) = \text{zero}$
 $i_C(\infty) = \text{zero}$



$$V_L(t) = L \frac{d}{dt} i(t)$$

$$i_L(t) = i_L(0^-) + \frac{1}{L} \int_0^t V_L(t) dt, \text{ for } t \geq 0$$

1. There is no voltage across an inductor if the current through it is not changing with time.
 An inductor is therefore a short circuit to dc.

@ $t = \infty$

$$V_L(\infty) = L \frac{d}{dt} \underbrace{i_L(\infty)}_{\text{const.}} \\ = \text{zero}$$

2. A finite amount of energy can be stored in an inductor even if the voltage across the inductor is zero.
3. The inductor never dissipate energy, but only store it.

4.
$$i_L(t) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} V_L(t) dt, t \geq 0$$




@ $t = 0^+$

$$i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} \cancel{V_L(t) dt}^{\text{zero}}$$

$$\boxed{i_L(0^+) = i_L(0^-)}$$

it is impossible to change the current through an inductor by a finite amount in zero time, for this requires an infinite voltage across the inductor.


@ $t = 0^+$

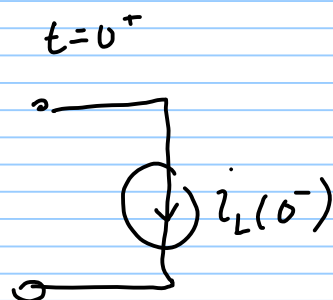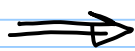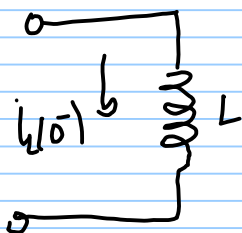

$t = \infty$

$$V_L(t) = L \frac{d}{dt} i_L(t)$$

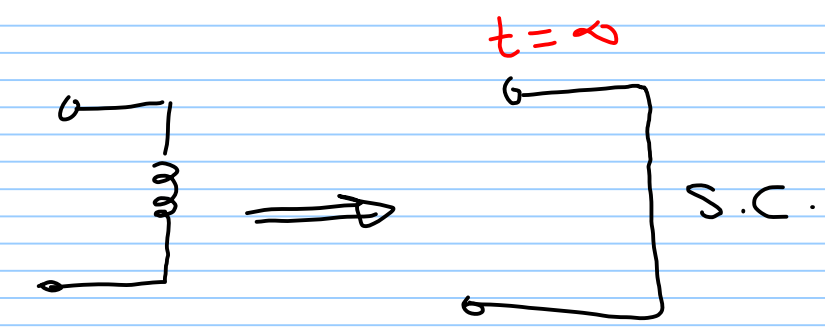An inductor is therefore a short circuit to dc.




First Order Circuit

$R + L$ } RL, RC circuits.
 OR $R + C$ }

Natural Response of 1st order circuit


↳ discharging.

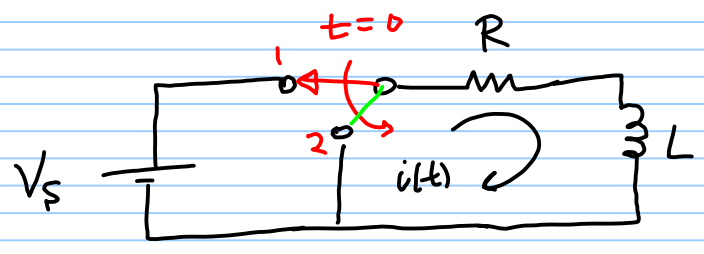

find $i(t)$ for $t > 0$


$$V_L = L \frac{di}{dt}$$

1) for $t < 0$; $t = 0^-$

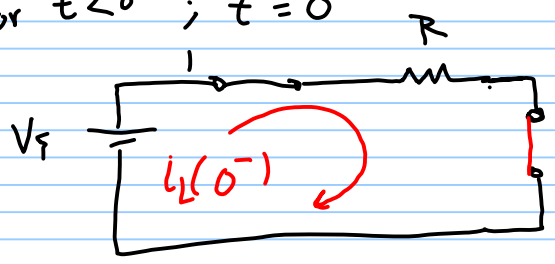

$$\text{so } i_L(0^-) = \frac{V_S}{R}$$

2) for $t > 0$

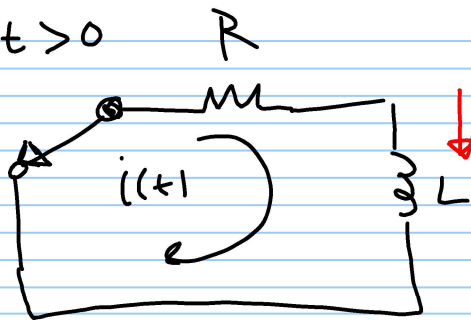

$$i_L(0^-) = i_L(0^+)$$

→ KVL

$$R i(t) + L \frac{d}{dt} i(t) = 0$$

$$i(t) = A e^{st} \text{ for } t > 0$$

$$R A e^{st} + L A s e^{st} = 0$$

$$A e^{st} (R + L s) = 0$$

$$s = -\frac{R}{L}$$

How to find A

From initial conditions

$$i(t) = A e^{st} \quad t > 0$$


$$i(0^+) = A$$

$$i(0^+) = i_L(0^+) = i_L(0^-) = \frac{V_F}{R}$$


$$i(t) = \frac{V_F}{R} e^{-\frac{R}{L} t} \quad t > 0$$

$\tau = \frac{L}{R}$, Time constant


$$i(t) = \frac{V_F}{R} e^{-t/\tau}$$

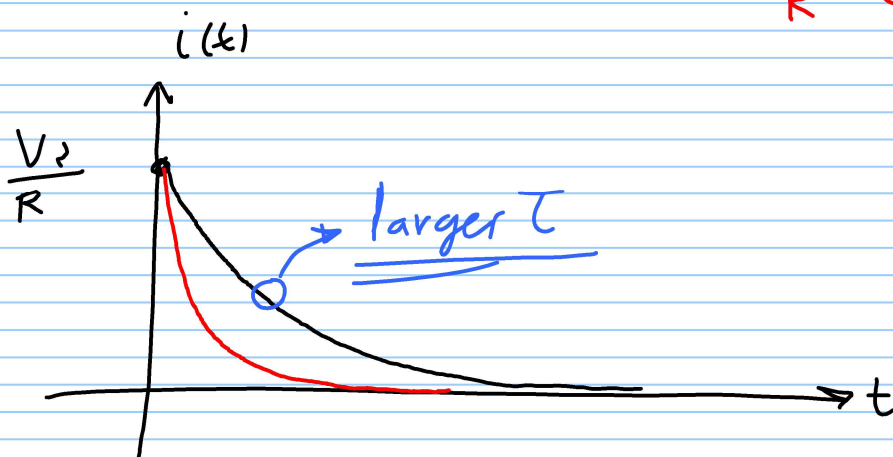

Ex] find $i_L(t)$ for $t > 0$

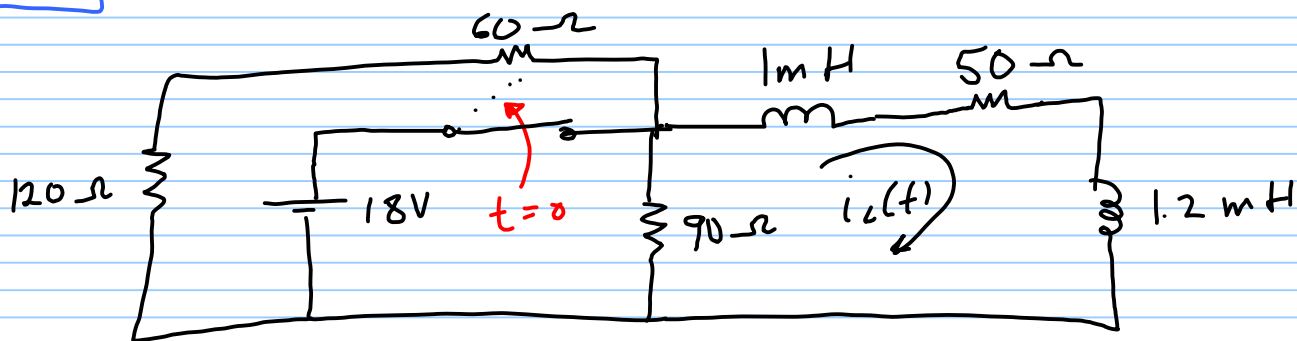


1) for $t < 0$, $t = 0^-$

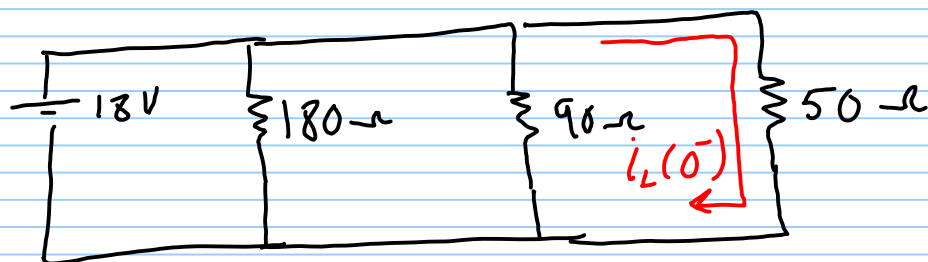

$$i_L(0^-) = \frac{18}{50} = 0.36 \text{ A}$$

$i_L(0^-) = i_L(0^+) \checkmark$
 $V(0^-) \neq V(0^+)$

2) for $t > 0$

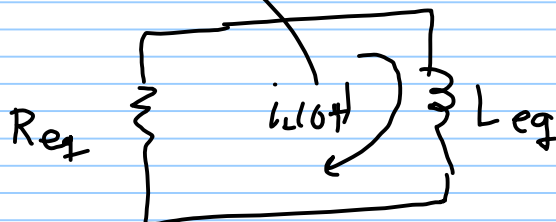

$$R_{eq} = (180 // 90) + 50 = 110 \text{ } \Omega$$


$$L_{eq} = 1 \text{ mH} + 1.2 \text{ mH} = 2.2 \text{ mH}$$

$$\tau = \frac{L_{eq}}{R_{eq}} = 20 \text{ } \mu \text{ sec}$$


$$i_L(t) = A e^{-t/\tau} \quad \text{for } t > 0$$

$$i_L(t) = 0.36 e^{-50000t}, \quad t > 0$$

RC circuit

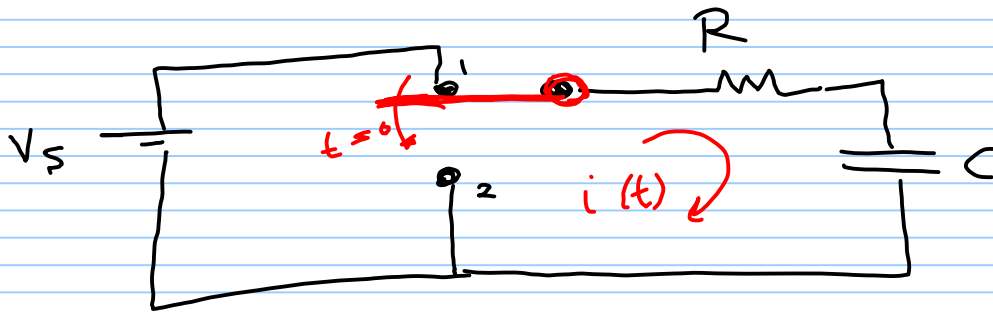


1) for $t < 0$; $t = 0^-$

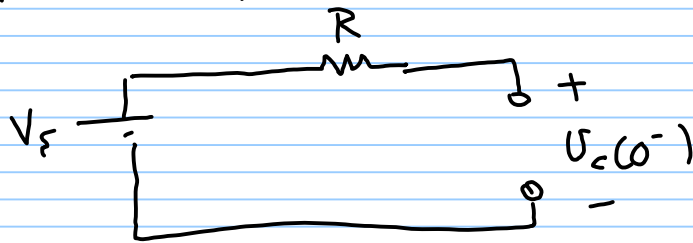

$$V_c(0^-) = V_s$$

2) for $t > 0$

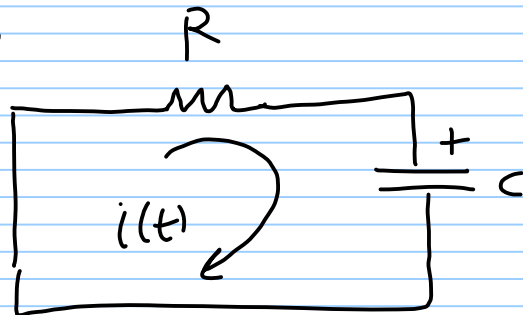

KVL

$$R i(t) + V_c(0^-) + \frac{1}{C} \int_{0^-}^t i(t) dt = 0, \quad t > 0$$

$$R \frac{d}{dt} i(t) + \frac{1}{C} i(t) = 0$$

$$i(t) = A e^{-\frac{t}{RC}}, \quad t > 0$$

$$R A \left(-\frac{1}{RC}\right) e^{-\frac{t}{RC}} + \frac{1}{C} A e^{-\frac{t}{RC}} = 0$$

$$A e^{st} \left(RS + \frac{1}{C} \right) = 0$$

$$\therefore \boxed{S = -\frac{1}{RC}}$$

✓

$$\therefore i(t) = A e^{-\frac{1}{RC} t} \quad t > 0$$

$$\therefore \tau = RC \quad (\text{time constant})$$

$$i(t) = A e^{-t/\tau} \quad t > 0$$

→ to find A

$$i(t) = A e^{-t/\tau}$$


$$\boxed{i(0^+) = A}$$

$$\frac{1}{\tau} \rightarrow i(0^-) \times$$

$$i(0^-) \neq i(0^+) \quad !!$$

$$V_c(0^-) = V_c(0^+) \quad \checkmark$$


to find $i(0^+)$

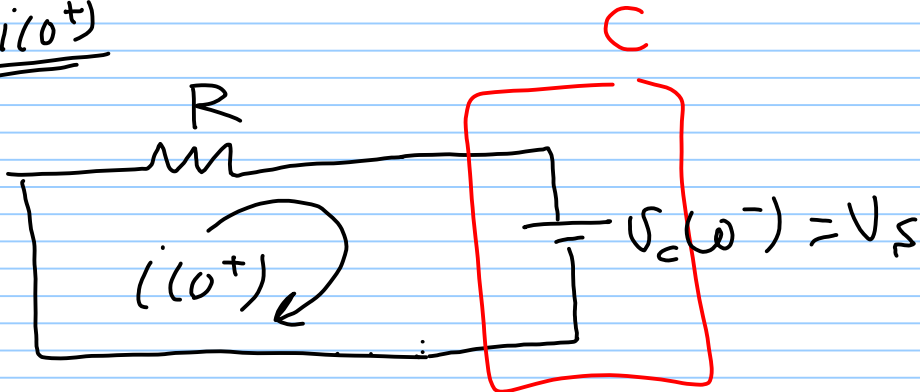


$$i(0^+) = -\frac{V_c(0^-)}{R} = -\frac{V_S}{R} = \underline{\underline{A}} \quad \checkmark$$

$$\therefore \boxed{i(t) = -\frac{V_S}{R} e^{-t/\tau}, \quad t > 0}$$


$$\tau = RC$$

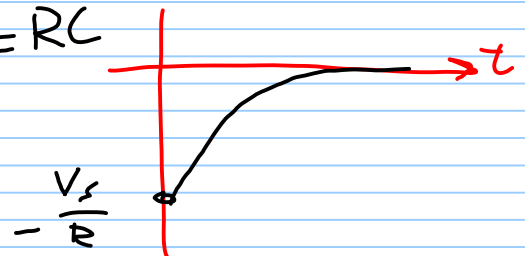

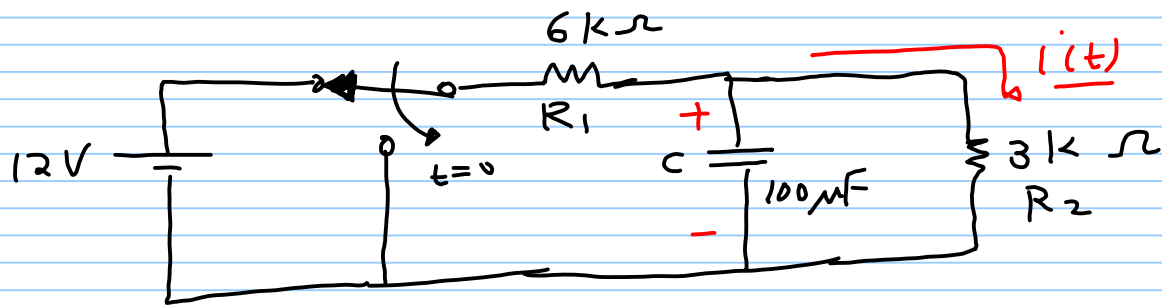EX] calculate $v_c(t)$ & $i(t)$ for $t > 0$




1) for $t < 0$; $t = 0^-$

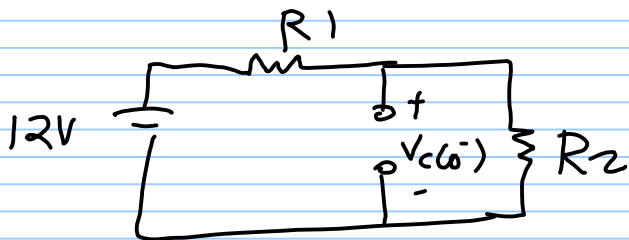

$$v_c(0^-) = \frac{R_2}{R_2 + R_1} \cdot 12 = \frac{3}{3 + 6} \times 12 = 4V$$

$$v_c(0^-) = 4V$$

2) for $t > 0$

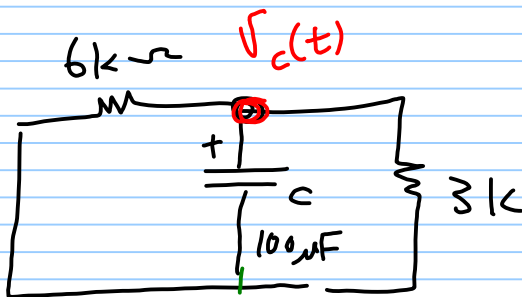


$$\frac{v_c(t)}{6k} + \frac{v_c(t)}{3k} + C \frac{d}{dt} v_c(t) = 0$$

$$\frac{d}{dt} v_c(t) + 5 v_c(t) = 0$$

$$v_c(t) = A e^{-t/\tau} \quad t > 0, \quad \tau = \underline{\underline{R_{eq} C}}$$

seen by C ←

$$R_{eq} = 6k // 3k \\ = 2k \Omega$$

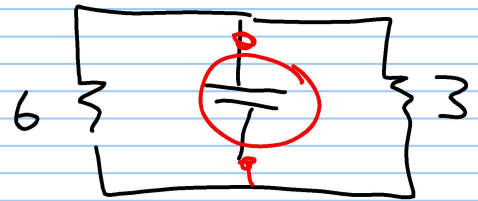

$$T = R_{eq}C = 0.2 \text{ Sec.}$$

$$V_c(t) = A e^{-5t} \quad t > 0$$

to find A

$$V_c(0^+) = A = V_c(0^-) = 4 \text{ Volt.}$$

$$\therefore V_c(t) = 4 e^{-5t} \quad V, \quad t > 0$$

$$\therefore i_c(t) = \frac{V_c(t)}{3k} = \frac{4}{3} e^{-5t} \text{ mA} \quad t > 0.$$


→ find $i_c(t)$

$$i_c(t) = C \frac{d}{dt} V_c(t)$$

The step response of RC & RL circuits

↳ The response of a circuit to the sudden application of a const. voltage or current source.


* The step response of RL circuits

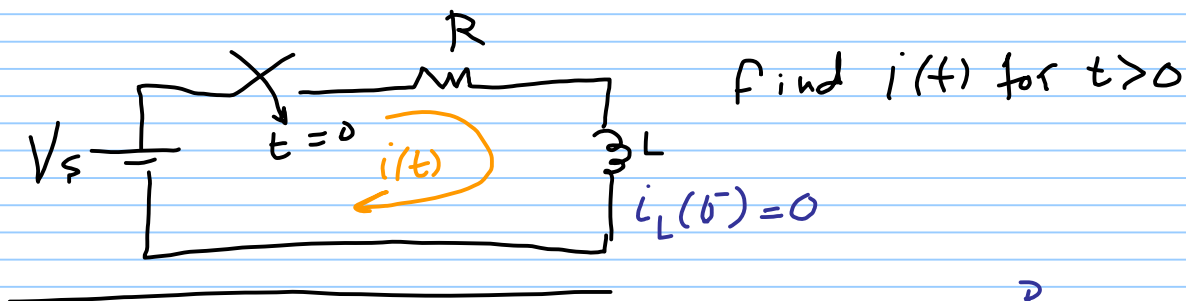

for $t > 0$

KVL
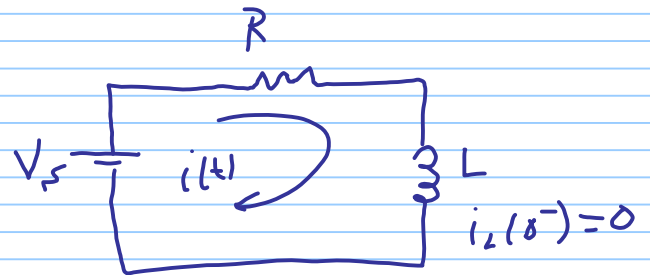
$$V_s = R i(t) + L \frac{d}{dt} i(t) \quad t > 0$$



non homogenous differential equation

$$i(t) = i_n(t) + i_f(t) \quad *$$



$i_n(t)$ = Natural response (e^{\wedge})

$i_f(t)$ = forced response. [final value]

↳ to find $i_f(t)$

$$\left. \begin{array}{l} \text{let } i_f(t) = K \\ V_s = R i(t) + L \frac{d}{dt} i(t) \\ V_s = R K + L [0] \end{array} \right\} \Rightarrow K = \frac{V_s}{R} = i_f(t)$$

OR to find $i_f(t)$

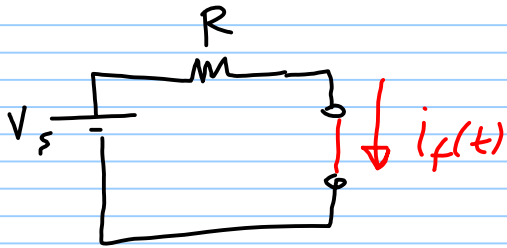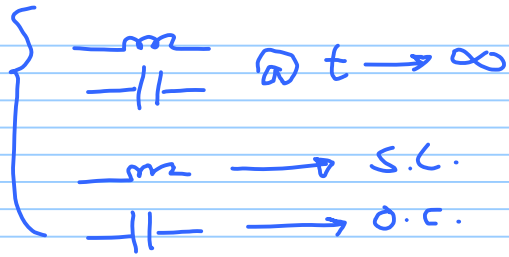

∴ $i_f(t) = V_s/R$ ✓

∴ Now

$$i(t) = i_n(t) + \frac{V_s}{R}$$

$$= A e^{-t/\tau} + \frac{V_s}{R}$$

$$\tau = \frac{L}{R_{eq}} = \frac{L}{R} \quad t > 0$$



→ to find A

$$i(t) = \frac{V_s}{R} + A e^{-t/\tau}$$

$$i(0^+) = \frac{V_s}{R} + A \quad \text{But} \quad i(0^+) = i_L(0^+) = i_L(0^-) = 0$$

$$\therefore A = -\frac{V_s}{R}$$

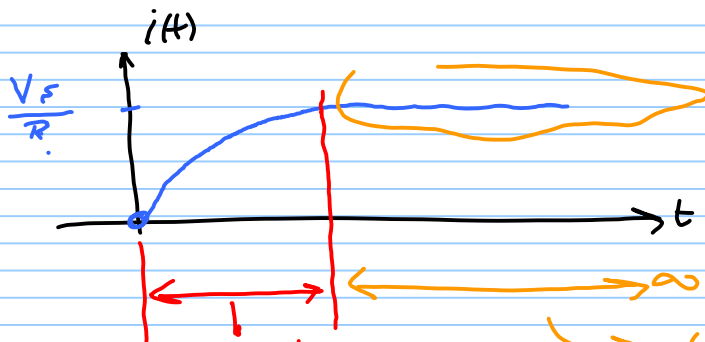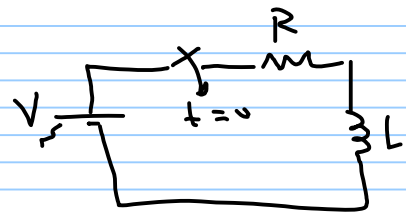
$$i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-t/\tau} \quad t \geq 0$$



transient Natural response


forced Response

The step response of RC circuits

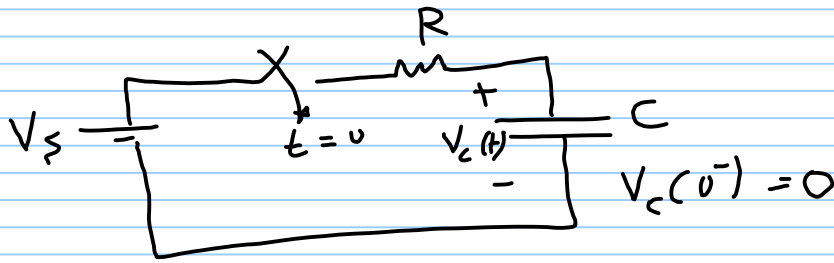

find $V_c(t)$ for $t > 0$

for $t > 0$


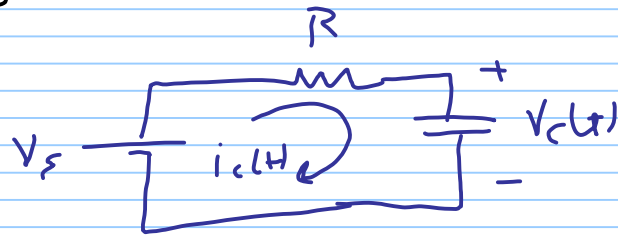


$$-V_s + V_R + V_c(t) = 0$$

$$V_s = R i_c(t) + V_c(t)$$

$$V_s = RC \frac{d}{dt} V_c(t) + V_c(t)$$
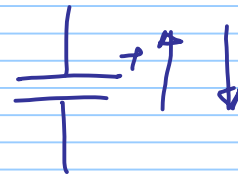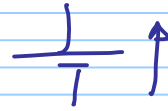
$$\frac{V_s}{R} = C \frac{d}{dt} V_c(t) + \frac{V_c(t)}{R}$$




$$V_c(t) = V_{c,n}(t) + V_{c,f}(t) \quad t > 0$$

$$= A e^{-t/\tau} + K$$

to find K

$t \rightarrow \infty \rightarrow C$ is O.C.

$$K = V_s$$

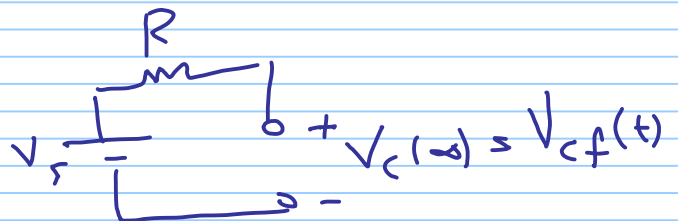

$$\therefore V_c(t) = A e^{-t/\tau} + V_s \quad t > 0$$

$$\tau = R_{eq}C = RC$$


to find A

$$V_c(0^+) = V_c(0^-) = 0$$

$$V_c(0^+) = \underline{A [1] + V_f = 0}$$

$$A = -V_f$$
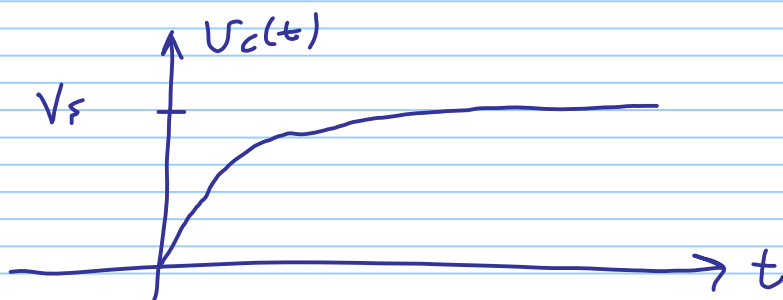
$$V_c(t) = V_f - V_f e^{-t/\tau} \quad t \geq 0$$
$$= V_f (1 - e^{-t/\tau}) \quad t \geq 0$$



7.4 A General Solution for Step and Natural Responses

General solution for natural and step responses of *RL* and *RC* circuits ▶

$$x(t) = x_f + [x(t_0) - x_f]e^{-(t-t_0)/\tau} \quad (7.59)$$

The importance of Eq. 7.59 becomes apparent if we write it out in words:

$$\begin{array}{l} \text{the unknown} \\ \text{variable as a} \\ \text{function of time} \end{array} = \begin{array}{l} \text{the final} \\ \text{value of the} \\ \text{variable} \end{array} + \left[\begin{array}{l} \text{the initial} \\ \text{value of the} \\ \text{variable} \end{array} - \begin{array}{l} \text{the final} \\ \text{value of the} \\ \text{variable} \end{array} \right] \times e^{\frac{-(t - (\text{time of switching}))}{(\text{time constant})}} \quad (7.60)$$


In many cases, the time of switching—that is, t_0 —is zero.

When computing the step and natural responses of circuits, it may help to follow these steps:

1. Identify the variable of interest for the circuit. For *RC* circuits, it is most convenient to choose the capacitive voltage; for *RL* circuits, it is best to choose the inductive current.
2. Determine the initial value of the variable, which is its value at t_0 . Note that if you choose capacitive voltage or inductive current as your variable of interest, it is not necessary to distinguish between $t = t_0^-$ and $t = t_0^+$.² This is because they both are continuous variables. If you choose another variable, you need to remember that its initial value is defined at $t = t_0^+$.
3. Calculate the final value of the variable, which is its value as $t \rightarrow \infty$.
4. Calculate the time constant for the circuit.

Calculating the natural or step response of *RL* or *RC* circuits ▶


EX find $i(t)$ for $t > 0$

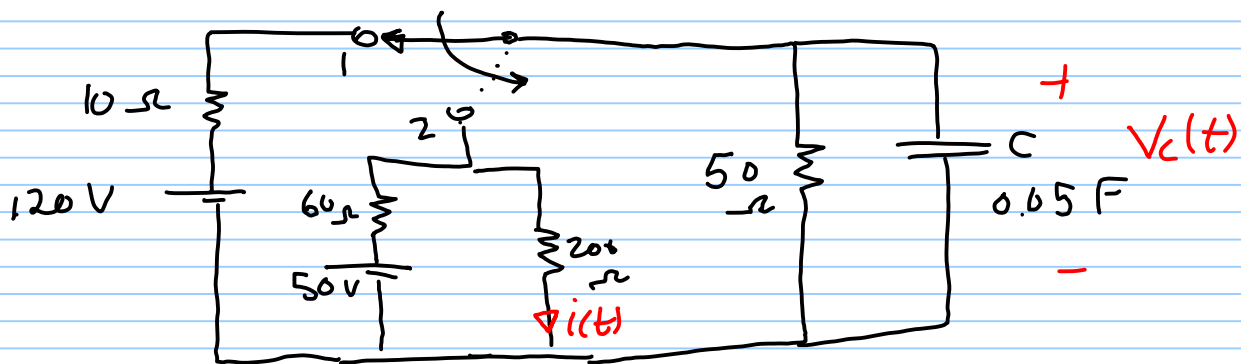

1st we will find $V_c(t)$, then $i(t)$

$$V_c(t) = V_{cf} + [V_{ci} - V_{cf}] e^{-t/\tau}$$


V_{ci} $t < 0$

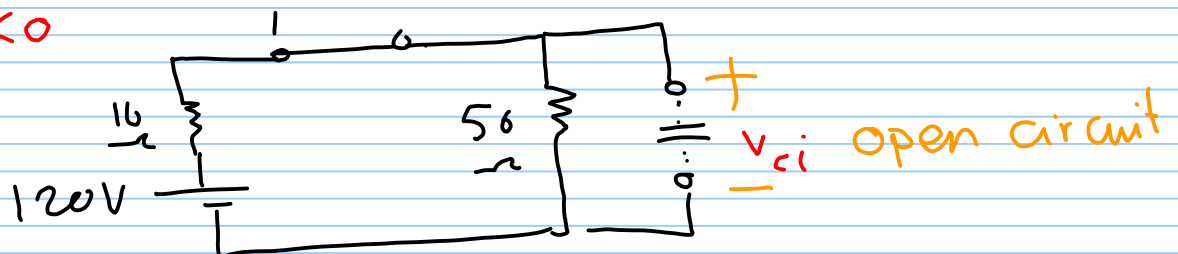

$$V_{ci} = \frac{50}{50+10} * 120$$


$$= 100 \text{ V}$$

$$V_{cf} \quad t \rightarrow \infty$$

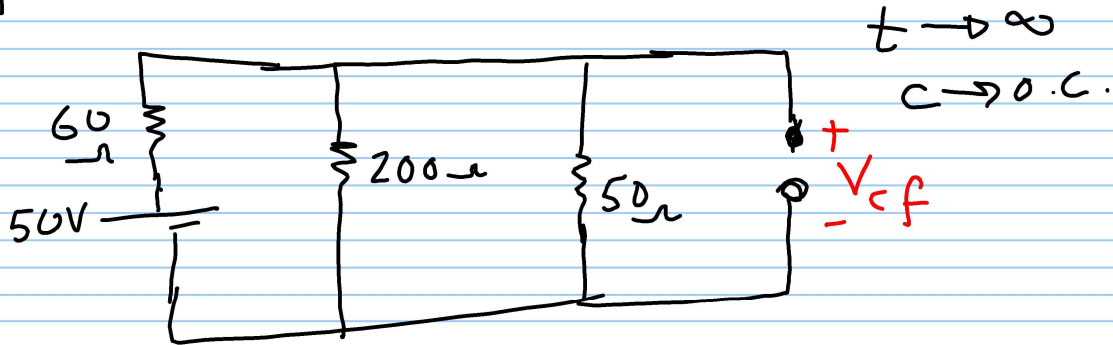

$$V_{cf} = \frac{[50//200]}{[50//200] + 60} \times 50 = 20 \text{ V}$$

to find T

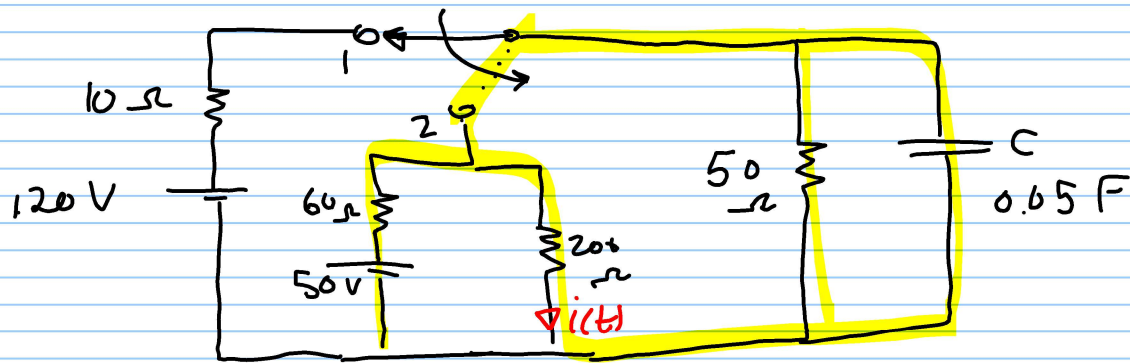


$$T = R_{eq} C$$

$$R_{eq} = 60 // 200 // 50$$

$$= 24 \Omega$$

$$T = 24 \times 0.05$$

$$= 1.2 \text{ Sec.}$$

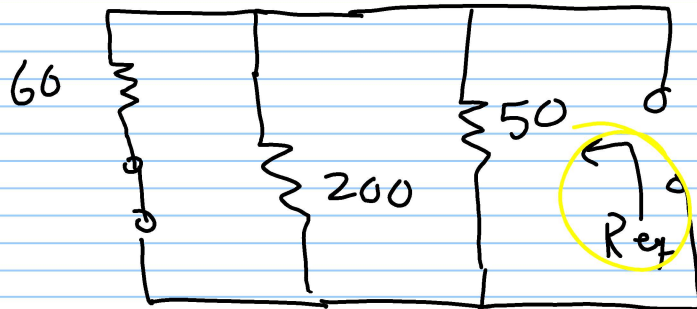

$$V_c(t) = 20 + [100 - 20] e^{-t/1.2}$$


$$= 20 + 80 e^{-t/1.2} \text{ V, } t \geq 0$$

Now, $V_c(t) = V_{200\Omega}$



$$i(t) = \frac{V_{200}}{200} = \frac{V_c(t)}{200}$$

$$= 0.1 + 0.4 e^{-t/1.2} \text{ A}, t > 0$$

$V_c(0^-) = V_c(0^+)$

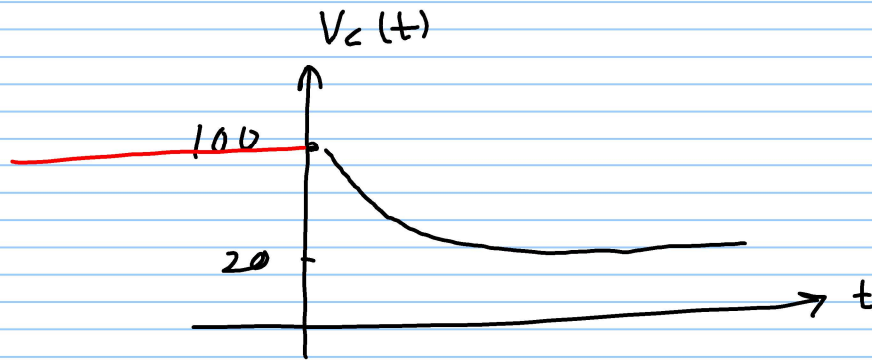

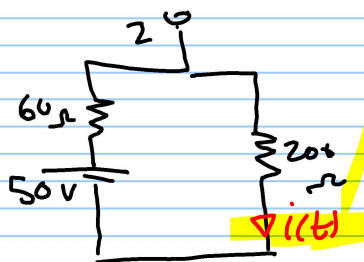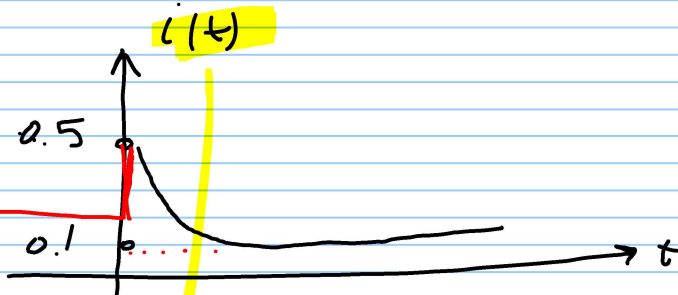
sudden change
of $i(t)$ for $R=200\Omega$



$$i(0^-) = \frac{50}{260}$$

$$= 0.1923 \text{ A}$$

HW

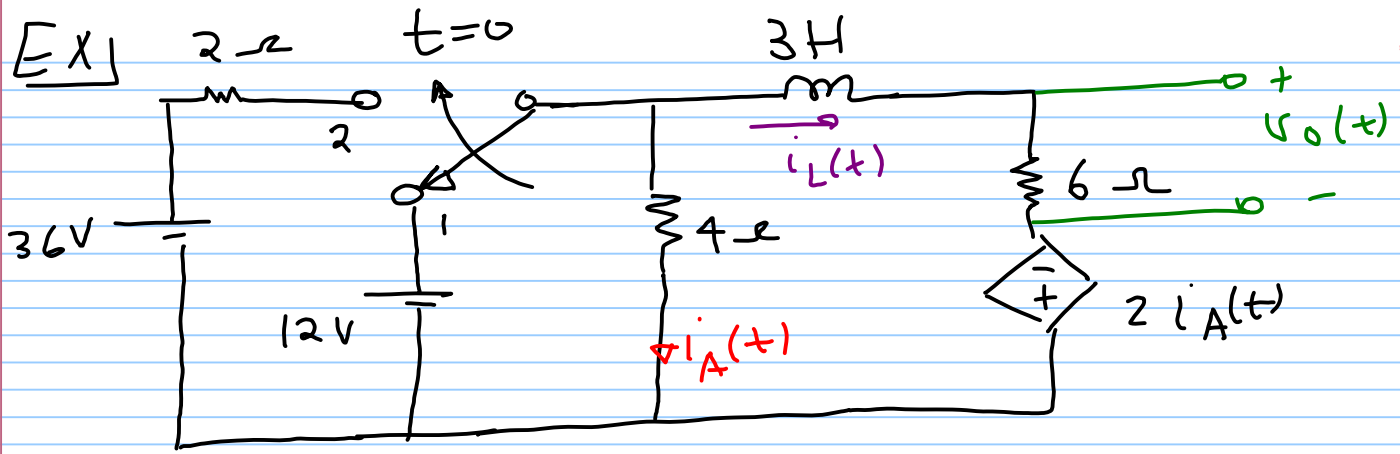

find $v_o(t)$ for $t > 0$

$$i_L(t) = i_f + [i_i - i_f] e^{-t/\tau}$$