
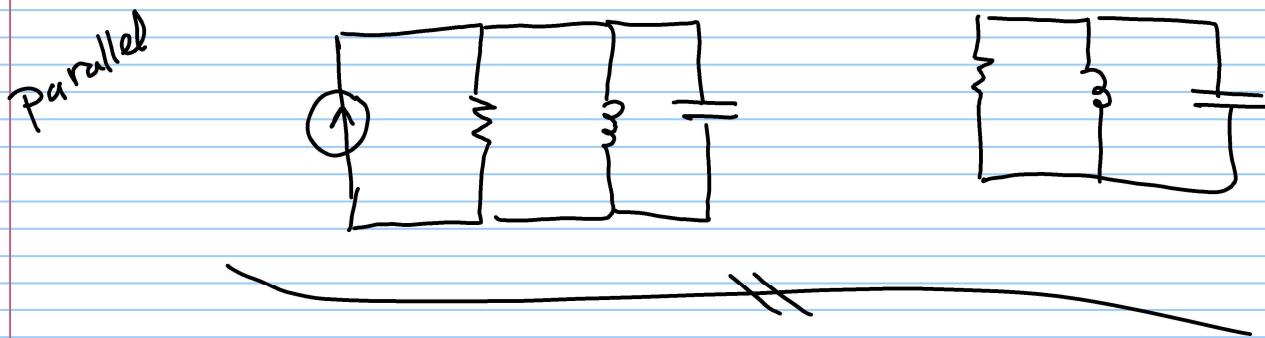
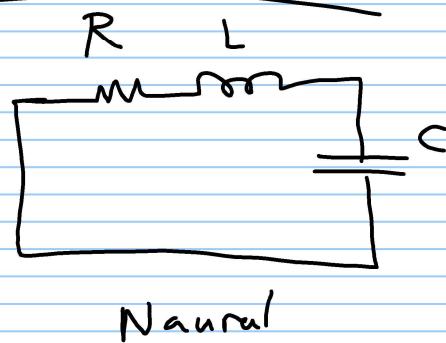


## chapter 8


11/25/2020

### Natural & step Response of RLC circuits

2<sup>nd</sup>-order

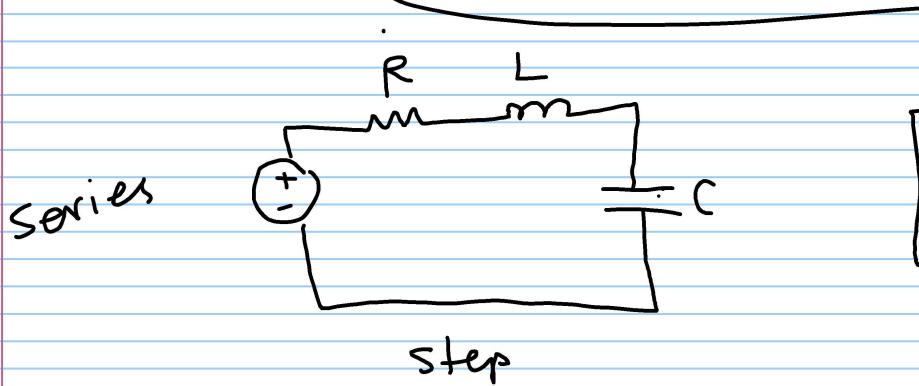
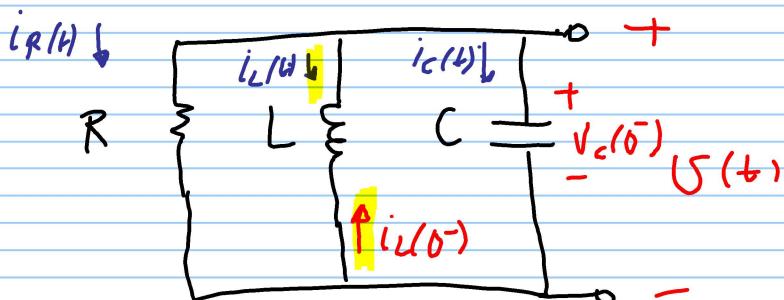
### \* Natural Response of parallel RLC circuits



$$V_L = L \frac{di_L}{dt}$$

$$\frac{1}{L} V_L = \frac{d}{dt} i_L$$

$$\frac{1}{L} \int v + i_C = i_L$$

let  $\mathcal{V}_c(0^-) = 0$  ;  $i_L(0^-) = 10 \text{ A}$

KCL

$$\frac{d}{dt} \left( \frac{\mathcal{V}(t)}{R} + \frac{1}{L} \int_0^t \mathcal{V}(t) dt - i_L(0^-) + C \frac{d}{dt} \mathcal{V}(t) \right) = 0$$

$$\frac{1}{R} \frac{d}{dt} V(t) + \frac{1}{L} I(t) + C \frac{d^2}{dt^2} V(t) = 0$$

$$\boxed{\frac{d^2}{dt^2} V(t) + \frac{1}{RC} \frac{d}{dt} V(t) + \frac{1}{LC} V(t) = 0}$$

2<sup>nd</sup>-order homogeneous differential equation

$$\therefore V(t) \propto A e^{\zeta t} \quad \text{for } t > 0$$

$$A e^{\zeta_1 t} + A e^{\zeta_2 t}$$

$$A \zeta^2 e^{\zeta t} + \frac{1}{RC} A \zeta e^{\zeta t} + \frac{1}{LC} A e^{\zeta t} = 0$$

$$A e^{\zeta t} \left[ \zeta^2 + \frac{1}{RC} \zeta + \frac{1}{LC} \right] = 0$$

$$\zeta^2 + \frac{1}{RC} \zeta + \frac{1}{LC} = 0$$

characteristic equation

$$\zeta_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$\zeta \pm \omega_n \sqrt{1 - \frac{\zeta^2}{\omega_0^2}}$$

$$\zeta_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\approx \omega_0 \quad \omega_0^2$$


$$\zeta_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\text{let } \omega_0 = \frac{1}{\sqrt{LC}} \quad \text{resonant frequency}$$

$$K \alpha = \frac{1}{2RC} \quad \text{damping coefficient}$$

$$\zeta_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$
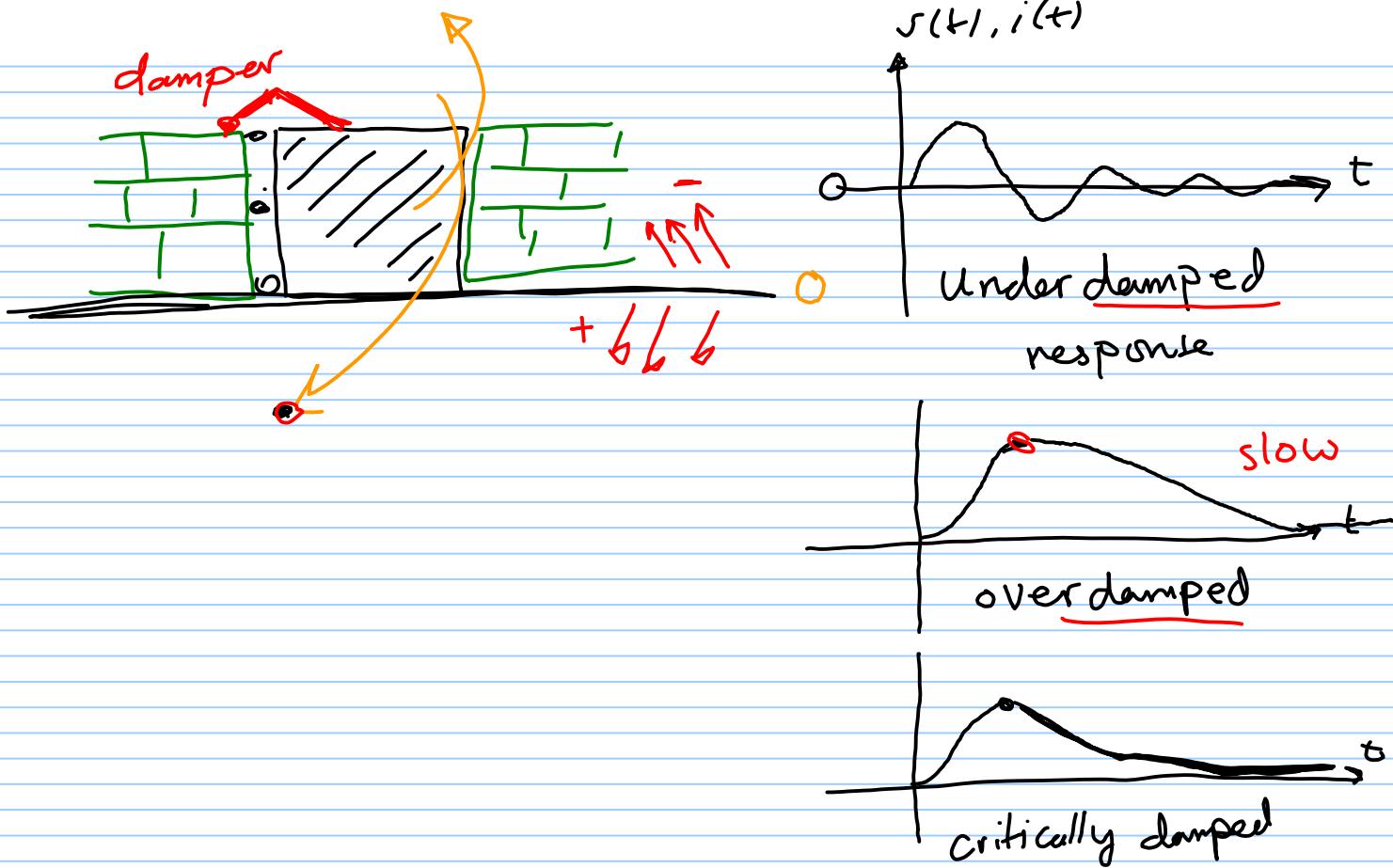
$$\zeta_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$



$$\xi_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$\xi_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

1) if  $\alpha > \omega_0$ , the solutions are real, unequal & the response is **overdamped**

2) if  $\alpha < \omega_0$ , the solutions are complex conjugates & the response is termed **underdamped**

3) if  $\alpha = \omega_0$ , the solutions are real and equal, & the response is termed **critically damped**.

## 1 Overdamped Case

$$\alpha > \omega_0 \quad \alpha = \frac{1}{2RC}$$

$$\zeta_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad -ve$$


$$\zeta_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad -ve$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

real & unequal (real & distinct)

$$f, \boxed{V(t) = A_1 e^{\zeta_1 t} + A_2 e^{\zeta_2 t}} \quad t > 0$$

## EX] overdamped parallel RLC

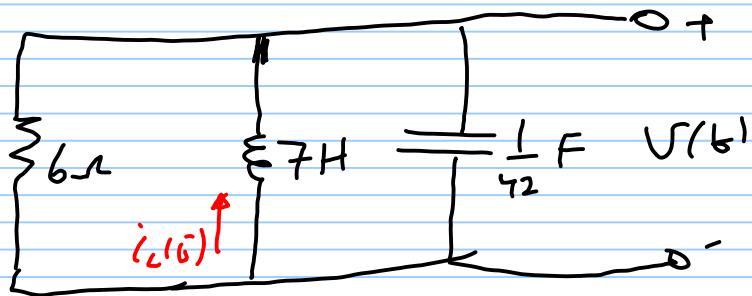

if  $i_L(0^-) = 10A$  &  $V_C(0^-) = 0$ . find  $V(t)$  for  $t > 0$

$$(1) \quad \alpha = \frac{1}{2RC} = 3.5, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2.45$$

$\alpha > \omega_0 \rightarrow$  overdamped

$$(2) \quad \zeta_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1$$

$$\zeta_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -6$$

$$\therefore V(t) = A_1 e^{-t} + A_2 e^{-6t}, \quad t > 0$$

(3) to find  $A_1, A_2 \rightarrow$  from the initial conditions

$$V(0^+) \& \frac{d}{dt} V(0^+)$$

$$\star \quad v(t) = A_1 e^{-t} + A_2 e^{-6t}$$

$$\rightarrow v(0^+) = A_1 + A_2 \quad \left. \begin{array}{l} \\ \end{array} \right\}$$

$$\rightarrow \frac{d}{dt} v(0^+) = -A_1 - 6A_2 \quad \left. \begin{array}{l} \\ \end{array} \right\}$$

$$A_1 + 6A_2$$

circuit

$v(0^+)$  → The initial voltage on the capacitor

$\frac{d}{dt} v(0^+)$  → ??

$$\text{KCL} \quad i_c(t) + i_R(t) + i_L(t) = 0$$

$$i_c(0^+) \quad C \frac{d}{dt} v(t) + \frac{v(t)}{R} + \frac{1}{L} \int_0^t v(t) dt \stackrel{+}{=} I_o = 0$$

$t \rightarrow 0^+$

$$i_c(0^+) \quad C \frac{d}{dt} v(0^+) + \frac{v(0^+)}{R} \stackrel{+}{=} I_o = 0 \quad v(0^+) = V_0$$

$$\therefore \frac{d}{dt} v(0^+) = \left( \stackrel{+}{=} I_o - \frac{V_0}{R} \right) \frac{1}{C}$$

$$\boxed{\frac{d}{dt} v(0^+) = \frac{i_c(0^+)}{C} = \stackrel{+}{=} I_o - \frac{V_0}{R}}$$

 Summary

---

---