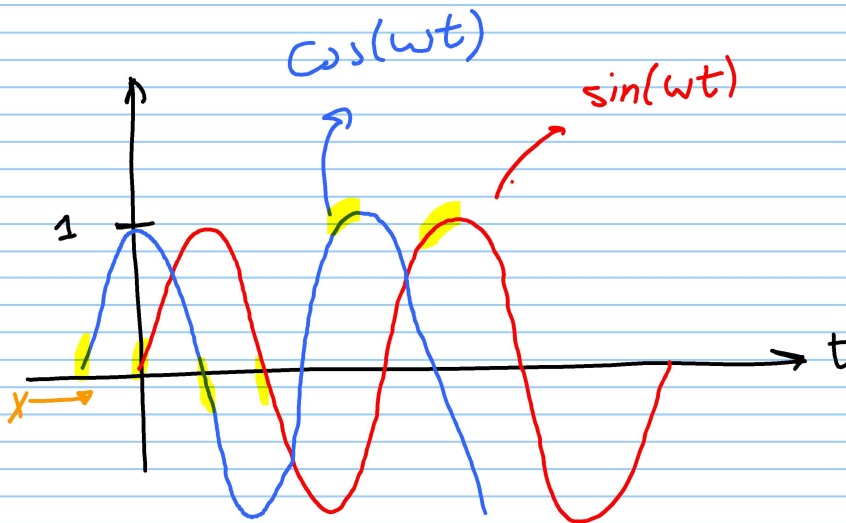


chapter 9:



$$\sin(\omega t) = \cos(\omega t - 90^\circ)$$

$$\cos(\omega t) = \sin(\omega t + 90^\circ)$$

* $Z = 10 + j10$ (Rectangular)

= $\boxed{14.14} \angle \boxed{45^\circ}$ (Polar)


$\boxed{\text{Pol}}$ 10 $\boxed{}$ 10 $\boxed{=}$

14.14 → magnitude (stored in E)


45° → angle (stored in F)

* $Z = 25 \angle -30^\circ$

= $21.6 - j12.5$

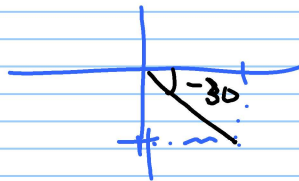

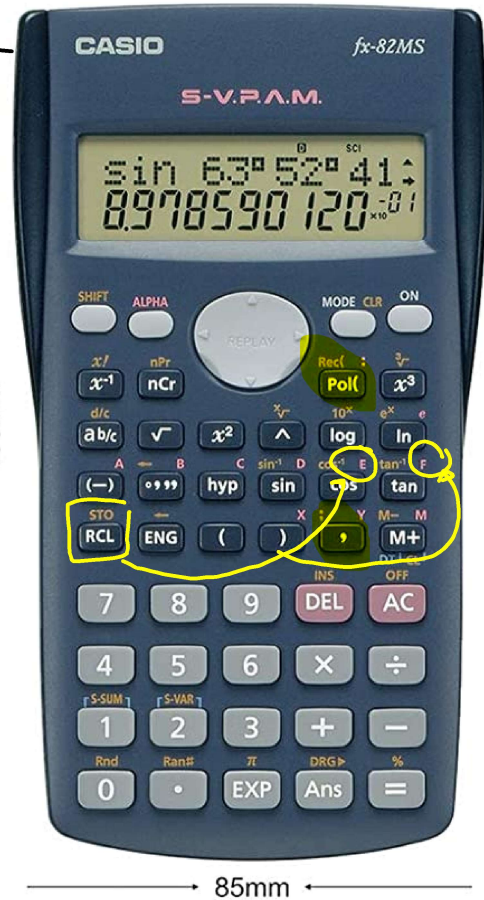$\boxed{\text{Rec}}$ 25 $\boxed{}$ $\boxed{30}$ $\boxed{=}$







$$(10 \angle 20^\circ) + (15 \angle -35^\circ) = X$$

Rec. ↓

$$\underline{x_1 + jy_1} + \underline{x_2 + jy_2}$$


$$(x_1 + x_2) + j(y_1 + y_2)$$

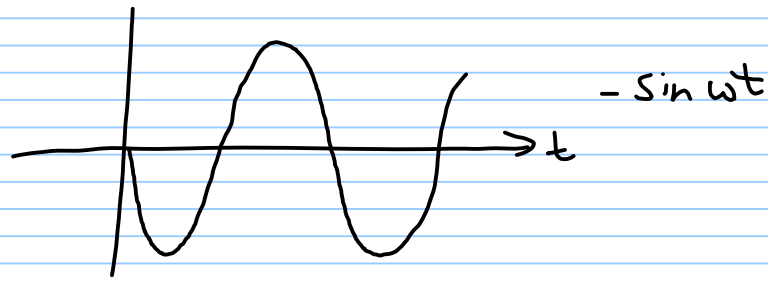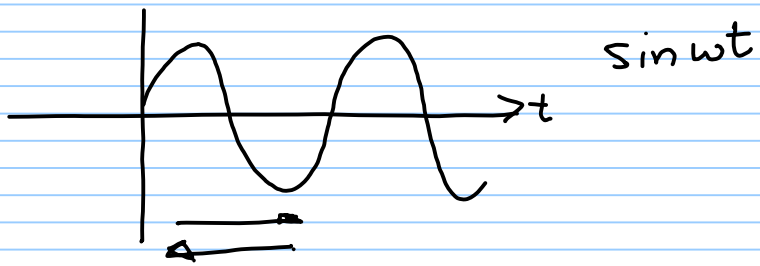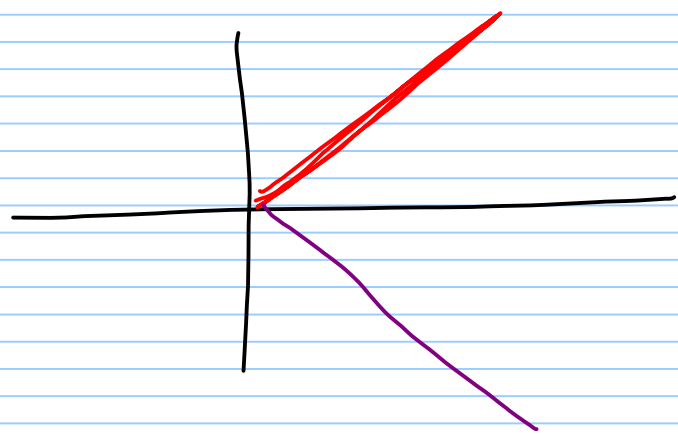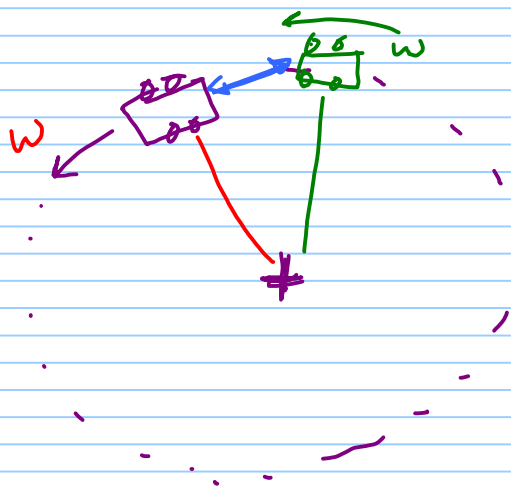



Phasor Relationships for circuit elements

Resistors

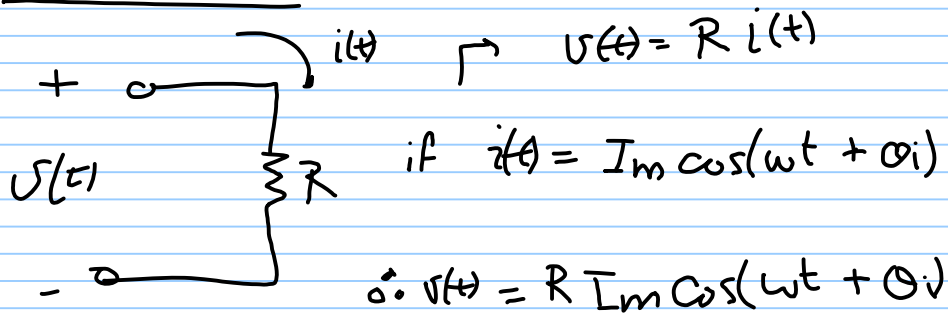



→ Phasor transformation:-

$$\vec{I} = I_m \angle \phi_i \quad \rightarrow \quad \vec{V} = R I_m \angle \phi_i$$


$$\vec{V} = R \vec{I}$$

Note for (R), there is no phase shift between the current and voltage.
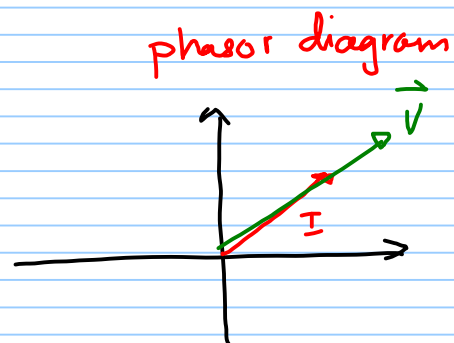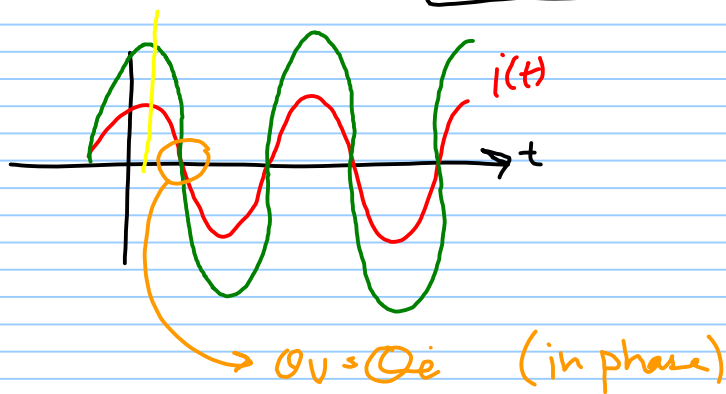
$$\vec{V} \ \& \ \vec{I} \text{ are in phase}$$



Inductors

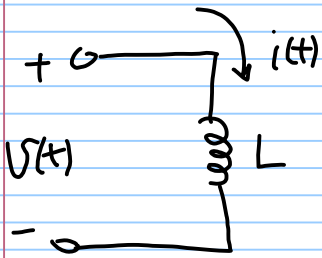

$$V(t) = L \frac{d}{dt} i(t)$$

$$\text{let } i(t) = I_m \cos(\omega t + \phi_i)$$

$$V(t) = L \frac{d}{dt} i(t) = -I_m \omega L \sin(\omega t + \phi_i)$$

↪ cosine (reference)

$$V(t) = -\omega L I_m \cos(\omega t + \phi_i - 90^\circ)$$


↪ In phasor representation $j(\phi_i - 90^\circ)$

$$\begin{aligned} \vec{V} &= -\omega L I_m e^{j(\phi_i - 90^\circ)} \\ &= -\omega L I_m e^{j\phi_i} e^{-j90^\circ} \end{aligned}$$


$$\begin{aligned} e^{-j90^\circ} &= \cos(-90^\circ) + j\sin(-90^\circ) \\ &= -j \end{aligned}$$

$$= j\omega L I_m e^{j\phi_i}$$

$$\boxed{\vec{V} = j\omega L \vec{I}}$$

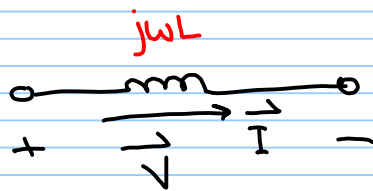

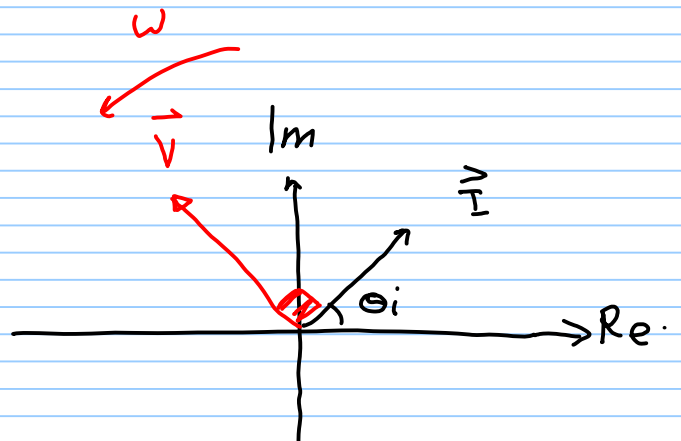
$$\begin{aligned} \vec{V} &= j\omega L \vec{I} \\ &= (\omega L \angle 90^\circ) (I_m \angle \phi_i) \\ &= \omega L I_m \angle \phi_i + 90^\circ \end{aligned}$$




NOTE The voltage & current are out of phase

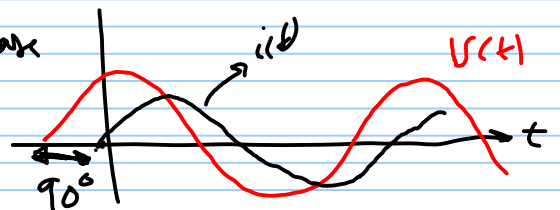\$V\$ leads \$i\$ by \$90^\circ\$
\$i\$ lags \$V\$ by \$90^\circ\$



Capacitors

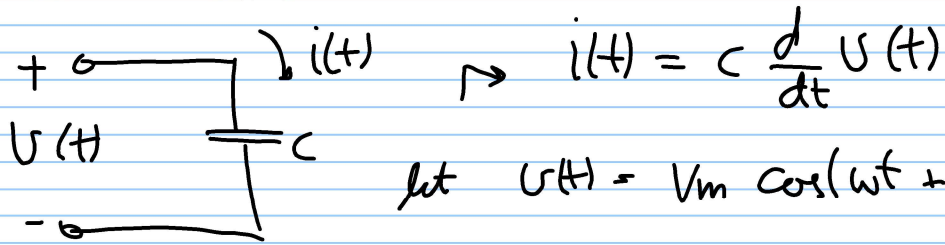

let $U(t) = V_m \cos(\omega t + \phi_v)$

so $i(t) = -C V_m \omega \sin(\omega t + \phi_v)$


$= -\omega C V_m \cos(\omega t + \phi_v - 90^\circ)$

$\vec{I} = -\omega C V_m e^{j(\omega t + \phi_v - 90^\circ)}$


$= -\omega C V_m e^{j\omega t - j90^\circ}$

$\vec{I} = j\omega C \underbrace{V_m e^{j\phi_v}}_{\vec{V}}$

$\vec{I} = j\omega C \vec{V}$

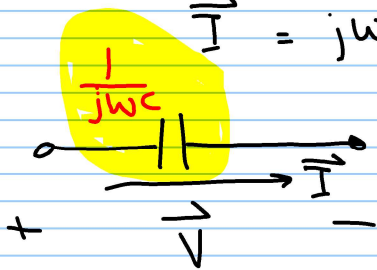
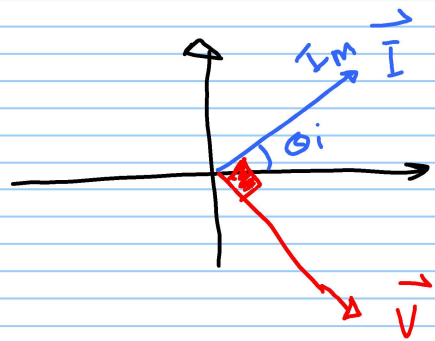
$$\begin{aligned} \vec{V} &= \frac{1}{j\omega C} \vec{I} \\ &= -j \frac{1}{\omega C} \vec{I} \\ &= \left(\frac{1}{\omega C} \angle -90^\circ \right) (I_m \angle \phi_i) \\ &= \frac{I_m}{\omega C} \angle \phi_i - 90^\circ \end{aligned}$$



i leads v by 90°

v lags i by 90°

Impedance & Reactance

$$\begin{array}{l}
 \text{---} \quad \vec{V} = R \vec{I} \\
 \text{---} \quad \vec{V} = j\omega L \vec{I} \\
 \text{---} \quad \vec{V} = \frac{1}{j\omega C} \vec{I} \\
 \vec{V} = \underline{Z} \vec{I}
 \end{array}$$

is The Impedance Z is the ratio of a circuit element's voltage phasors to it's current phasor.

Z is NOT a phasor

complex number ✓

- 1 $Z \rightarrow$ Impedance (Ω)
- 2 $Y = \frac{1}{Z} \rightarrow$ admittance (S)
- 3 Reactance ?


	<u>Impedance</u> Ω	<u>Reactance</u> Ω
---	R	---
---	$Z_L = j\omega L$	$X_L = \omega L$
---	$Z_C = \frac{1}{j\omega C}$ $= -j \frac{1}{\omega C}$	$X_C = -\frac{1}{\omega C}$

\rightarrow Reactance is the imaginary part of the impedance

$\left. \begin{array}{l} +ve \rightarrow \text{Inductor} \\ -ve \rightarrow \text{Capacitor} \end{array} \right\} \text{$

In General, if Z is a combination of R, L, C in frequency domain, then it will be in a form of

$$Z = R + jX$$

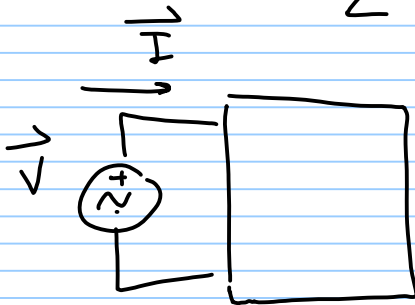

$$Z = \frac{\vec{V}}{\vec{I}} = \frac{V_m \angle \theta_v}{I_m \angle \theta_i}$$

$$= \frac{V_m}{I_m} \angle \theta_v - \theta_i$$

$$Z = |Z| \angle \theta_z$$


$$= R + jX$$

$$\left\{ \begin{array}{l} |Z| = \sqrt{R^2 + X^2} \\ \theta_z = \tan^{-1} \frac{X}{R} \end{array} \right.$$


$R \equiv$ Resistive part
 $X \equiv$ Reactive part

$$R = |Z| \cos \theta_z$$

$$X = |Z| \sin \theta_z$$

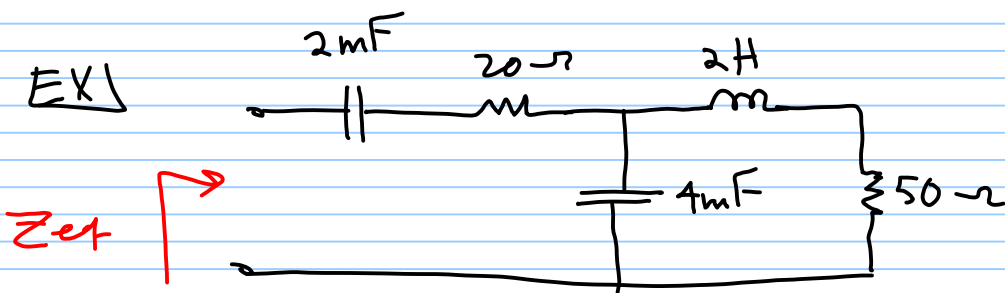

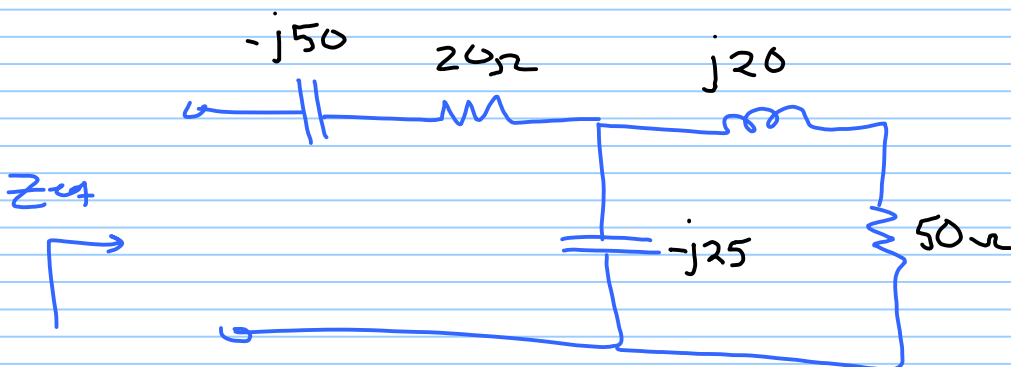find Z_{eq} if $\omega = 10 \text{ rad/sec}$.



$$Z_{eq} = \left\{ [50 + j20] // [-j25] \right\} + [20 - j50]$$

$$= 32.38 - j73.76 \ \Omega$$



$$\frac{j}{\omega c} = 73.76$$

$$\frac{1}{1000 c} = 73.76$$

$$C = \frac{1}{737.6} = 1.35 \text{ mF}$$