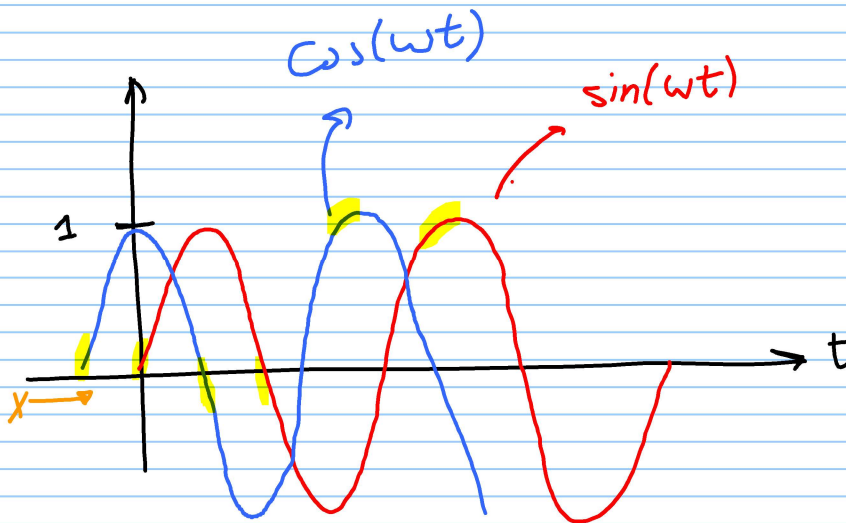


# chapter 9:



$$\sin(\omega t) = \cos(\omega t - 90^\circ)$$

$$\cos(\omega t) = \sin(\omega t + 90^\circ)$$

\*  $Z = 10 + j10$  (Rectangular)

=  $\boxed{14.14} \angle \boxed{45^\circ}$  (Polar)


$\boxed{\text{PolC}} \ 10 \ \boxed{9} \ 10 \ \boxed{=}$

14.14 → magnitude (stored in E)


45° → angle (stored in F)

\*  $Z = 25 \angle -30^\circ$

=  $21.6 - j12.5$

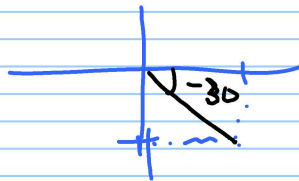

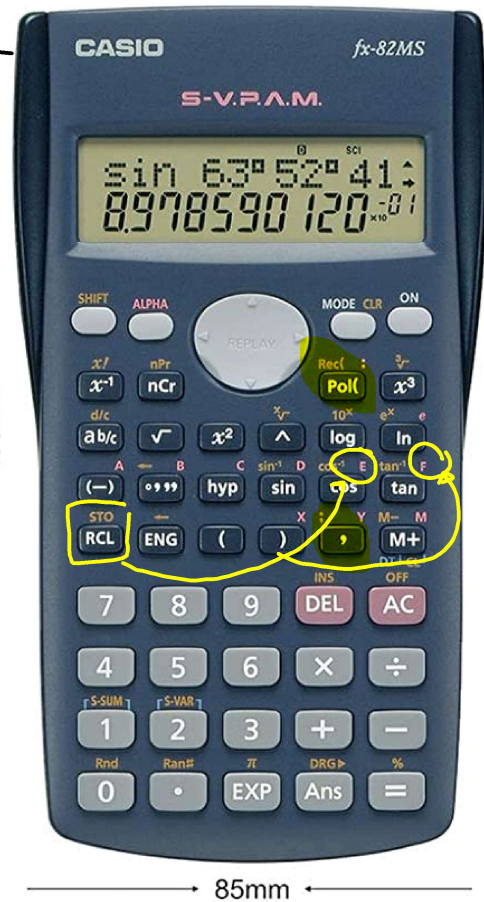$\boxed{\text{RecL}} \ 25 \ \boxed{9} \ \boxed{30} \ \boxed{=}$







$$(10 \angle 20^\circ) + (15 \angle -35^\circ) = X$$

Rec. ↓

$$\underline{x_1 + jy_1} + \underline{x_2 + jy_2}$$


$$(x_1 + x_2) + j(y_1 + y_2)$$

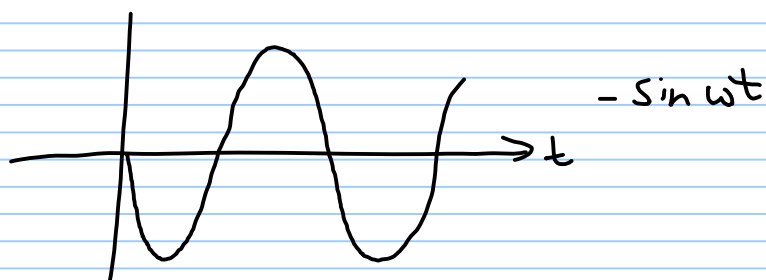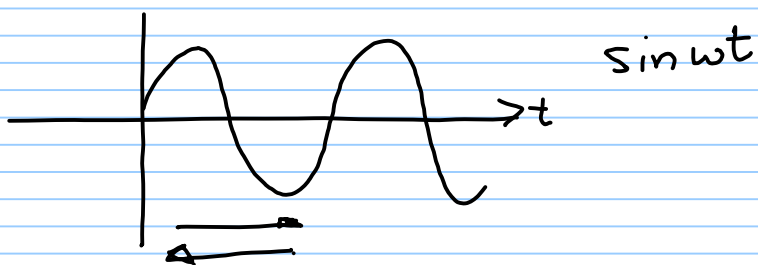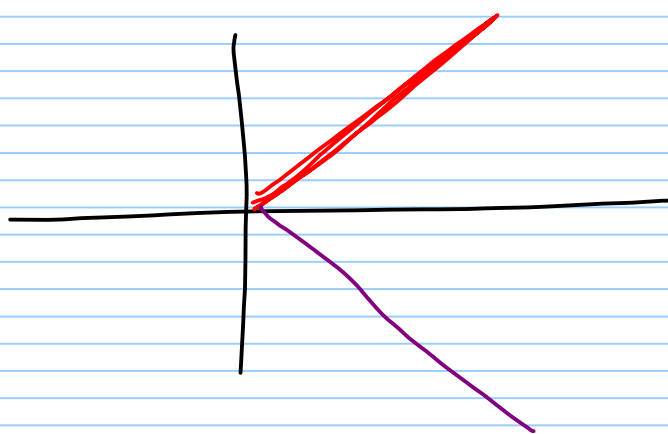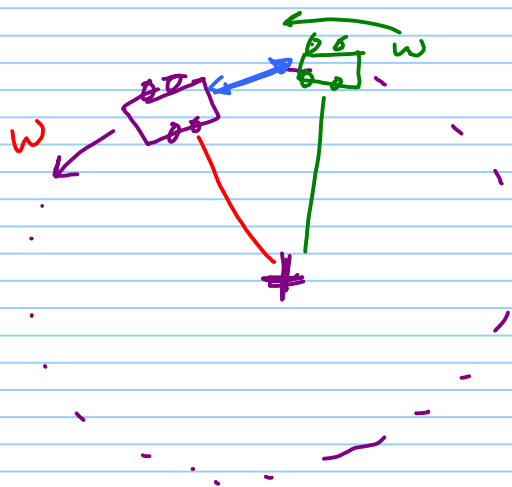



## Phasor Relationships for circuit elements

### Resistors

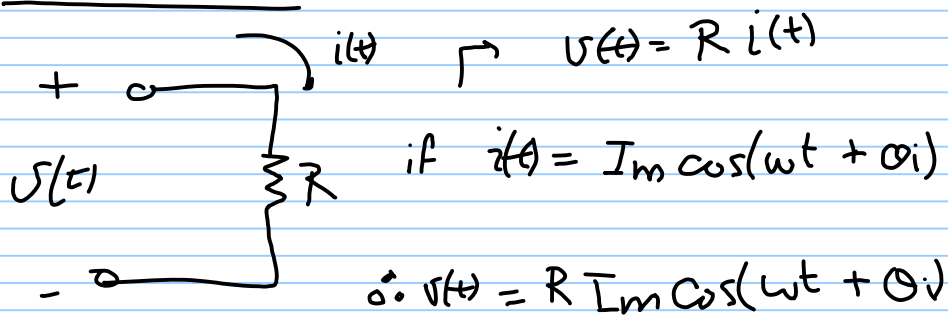



→ Phasor transformation:-

$$\vec{I} = I_m \angle \phi_i \quad \rightarrow \quad \vec{V} = R I_m \angle \phi_i$$


$$\vec{V} = R \vec{I}$$

Note for (R), there is no phase shift between the current and voltage.
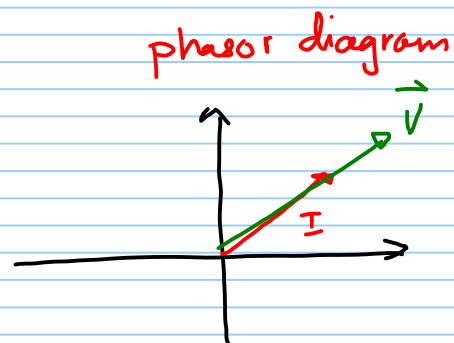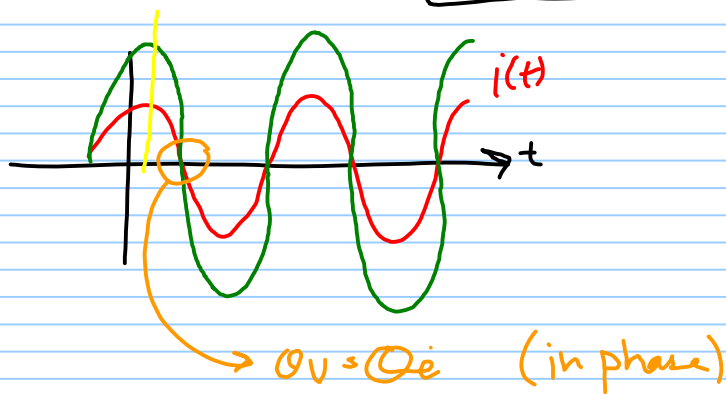
$$\vec{V} \ \& \ \vec{I} \text{ are in phase}$$



# Inductors

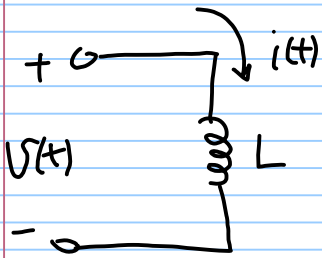

$$V(t) = L \frac{d}{dt} i(t)$$

$$\text{let } i(t) = I_m \cos(\omega t + \phi_i)$$

$$V(t) = L \frac{d}{dt} i(t) = -I_m \omega L \sin(\omega t + \phi_i)$$

↪ cosine (reference)

$$V(t) = -\omega L I_m \cos(\omega t + \phi_i - 90^\circ)$$


↪ In phasor representation  $j(\phi_i - 90^\circ)$

$$\begin{aligned} \vec{V} &= -\omega L I_m e^{j(\phi_i - 90^\circ)} \\ &= -\omega L I_m e^{j\phi_i} e^{-j90^\circ} \end{aligned}$$


$$\begin{aligned} e^{-j90^\circ} &= \cos(-90^\circ) + j\sin(-90^\circ) \\ &= -j \end{aligned}$$

$$= j\omega L I_m e^{j\phi_i}$$

$$\boxed{\vec{V} = j\omega L \vec{I}}$$

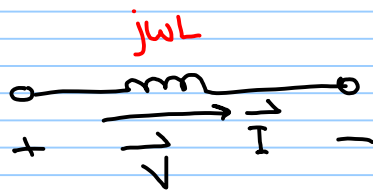

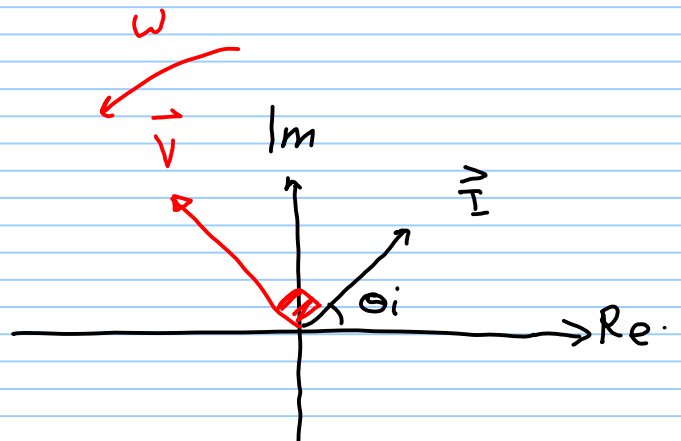
$$\begin{aligned} \vec{V} &= j\omega L \vec{I} \\ &= (\omega L \angle 90^\circ) (I_m \angle \phi_i) \\ &= \omega L I_m \angle \phi_i + 90^\circ \end{aligned}$$




**NOTE** The voltage & current are out of phase

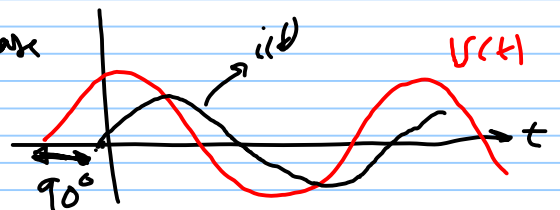$V$  leads  $i$  by  $90^\circ$   
 $i$  lags  $V$  by  $90^\circ$



# Capacitors

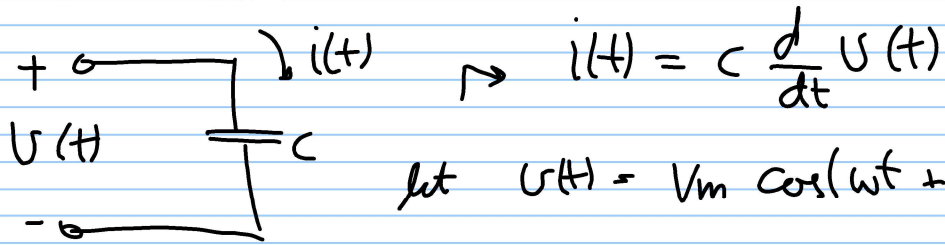

let  $U(t) = V_m \cos(\omega t + \phi_v)$


$\therefore i(t) = -C V_m \omega \sin(\omega t + \phi_v)$

$= -\omega C V_m \cos(\omega t + \phi_v - 90^\circ)$


$\rightarrow \vec{I} = -\omega C V_m e^{j(\omega t + \phi_v - 90^\circ)}$

$= -\omega C V_m e^{j\omega t - j90^\circ}$

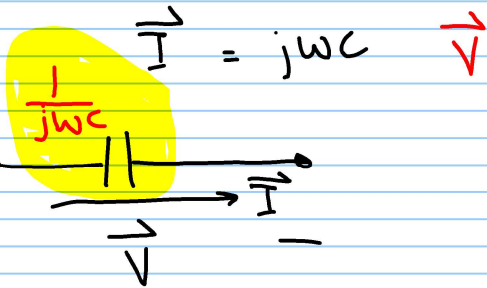$\vec{I} = j\omega C \underbrace{V_m e^{j\phi_v}}_{\vec{V}}$


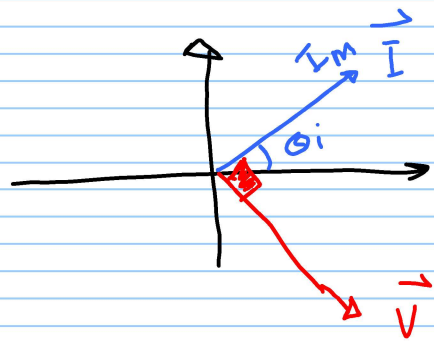
$$\begin{aligned} \vec{V} &= \frac{1}{j\omega C} \vec{I} \\ &= -j \frac{1}{\omega C} \vec{I} \\ &= \left( \frac{1}{\omega C} \angle -90^\circ \right) (I_m \angle \phi_i) \\ &= \frac{I_m}{\omega C} \angle \phi_i - 90^\circ \end{aligned}$$



$i$  leads  $v$  by  $90^\circ$

$v$  lags  $i$  by  $90^\circ$

# Impedance & Reactance

$$\begin{array}{l}
 \text{---} \quad \vec{V} = R \vec{I} \\
 \text{---} \quad \vec{V} = j\omega L \vec{I} \\
 \text{---} \quad \vec{V} = \frac{1}{j\omega C} \vec{I} \\
 \vec{V} = \underline{Z} \vec{I}
 \end{array}$$

is The Impedance  $Z$  is the ratio of a circuit element's voltage phasors to it's current phasor.

$Z$  is NOT a phasor

complex number ✓

- 1  $Z \rightarrow$  Impedance ( $\Omega$ )
- 2  $Y = \frac{1}{Z} \rightarrow$  admittance ( $S$ )
- 3 Reactance ?


	<u>Impedance</u> $\Omega$	<u>Reactance</u> $\Omega$
---	$R$	---
---	$Z_L = j\omega L$	$X_L = \omega L$
---	$Z_C = \frac{1}{j\omega C}$ $= -j \frac{1}{\omega C}$	$X_C = -\frac{1}{\omega C}$

$\rightarrow$  Reactance is the imaginary part of the impedance

$+ve \rightarrow$  Inductor } 
  
 $-ve \rightarrow$  capacitor }

In General, if  $Z$  is a combination of  $R, L, C$  in frequency domain, then it will be in a form of

$$Z = R + jX$$

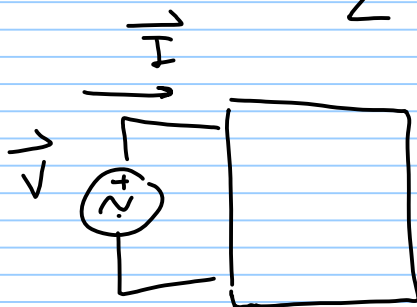

$$Z = \frac{\vec{V}}{\vec{I}} = \frac{V_m \angle \theta_v}{I_m \angle \theta_i}$$

$$= \frac{V_m}{I_m} \angle \theta_v - \theta_i$$

$$Z = |Z| \angle \theta_z$$

$$= R + jX$$


$$\left\{ \begin{array}{l} |Z| = \sqrt{R^2 + X^2} \\ \theta_z = \tan^{-1} \frac{X}{R} \end{array} \right.$$

$$R = |Z| \cos \theta_z$$


$$X = |Z| \sin \theta_z$$

$R \equiv$  Resistive part

$X \equiv$  Reactive part

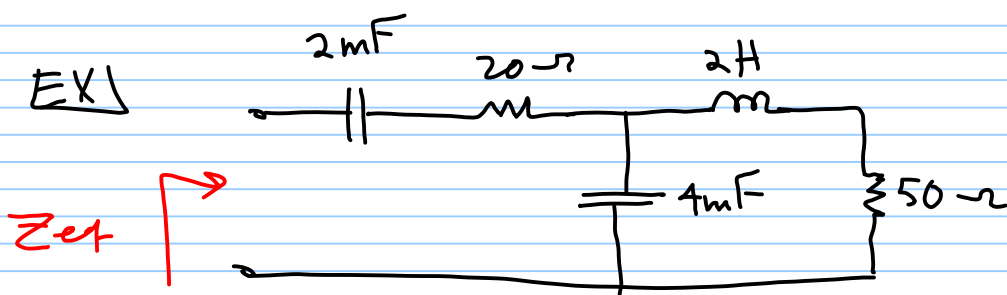

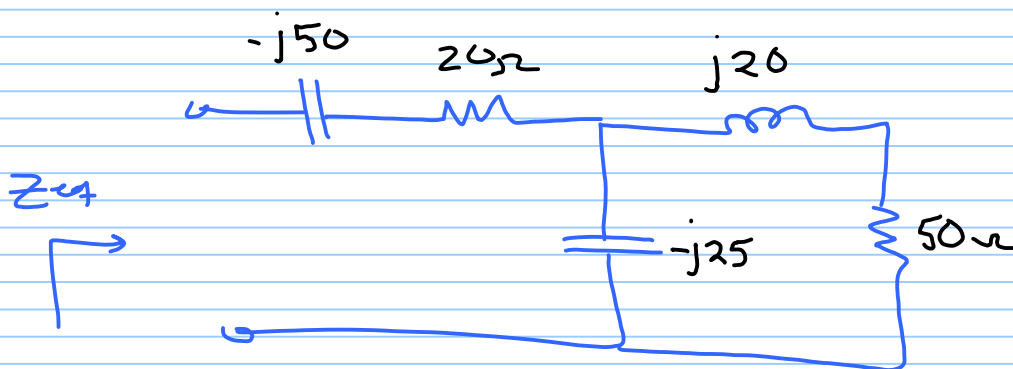find  $Z_{eq}$  if  $\omega = 10$  rad/sec.



$$Z_{eq} = \left\{ [50 + j20] // [-j25] \right\} + [20 - j50]$$

$$= 32.38 - j73.76 \ \Omega$$



$$\frac{j}{\omega C} = 73.76$$



$$\frac{1}{10^3 C} = 73.76$$

$$C = \frac{1}{737.6} = 1.35 \text{ mF}$$


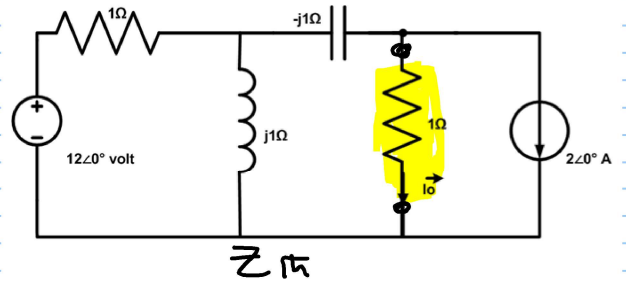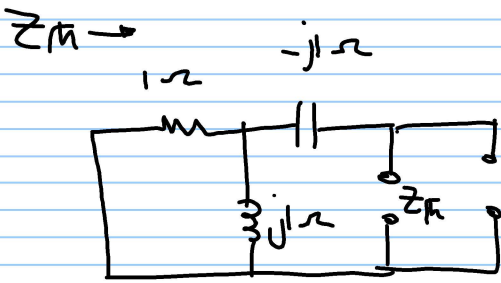
# Thevenin's and Norton's theorems

find  $\vec{I}_0$  using thevenin's theorem




$$\vec{Z}_{Th} = (1 // j1) + (-j1)$$


$$= \frac{j}{1+j} - j = \frac{1 \angle 90}{\sqrt{2} \angle 45} - j$$

$$= \frac{1}{\sqrt{2}} \angle 45 - j$$
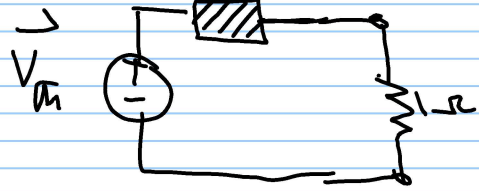
$$= \frac{1}{2} + \frac{1}{2}j - j = \frac{1}{2} - \frac{1}{2}j = \frac{\sqrt{2}}{2} \angle -45 \Omega$$



$\vec{V}_{Th} = V_{o.c.}$

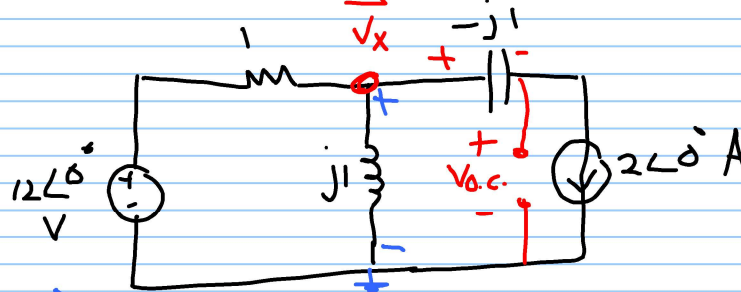

$$\frac{\vec{V}_x - 12 \angle 0^\circ}{1} + \frac{\vec{V}_x}{j1} + 2 \angle 0^\circ = 0$$

$$\vec{V}_x \left(1 + \frac{1}{j1}\right) - 12 + 2 = 0$$

$$\vec{V}_x = \frac{10}{1 + \frac{1}{j}} = \frac{10}{1 - j} = \frac{10(1+j)}{(1-j)(1+j)} = \frac{10(1+j)}{2} = 5 + j5 \text{ V}$$

$$= 5\sqrt{2} \angle 45^\circ \text{ V}$$


o.o. KVL

$$-V_{o.c.} + V_c + V_x = 0$$

$$V_{o.c.} = V_c + V_x = -(-j)(2) + 5 + j5$$

$$= j2 + 5 + j5 = 5 + j7 \text{ V}$$

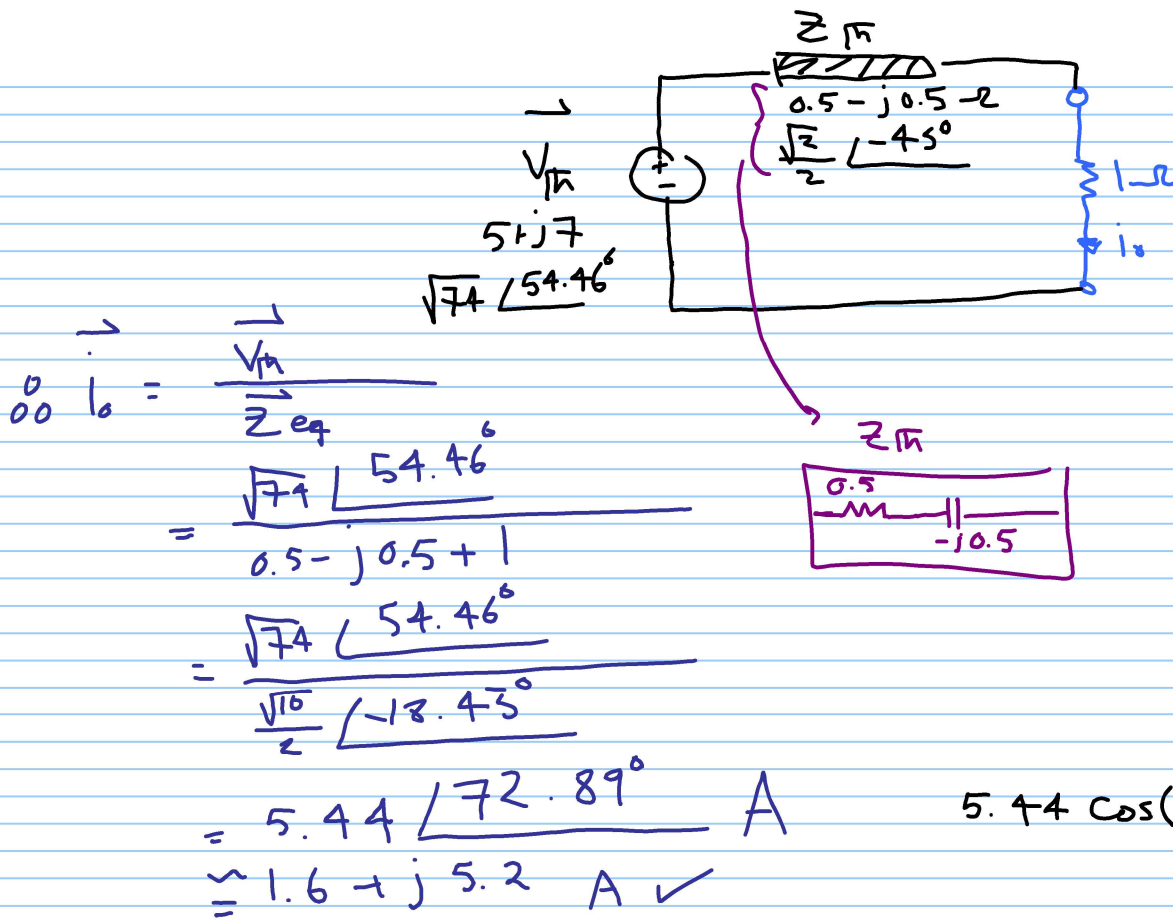
$$= \sqrt{74} \angle 54.46^\circ \text{ V}$$



series, parallel, KVL, KCL, VDR, CDR  
 source transformation, thevenin, Norton  
 nodal, mesh, **superposition**

### Superposition

find  $\vec{I}_o$  using super position

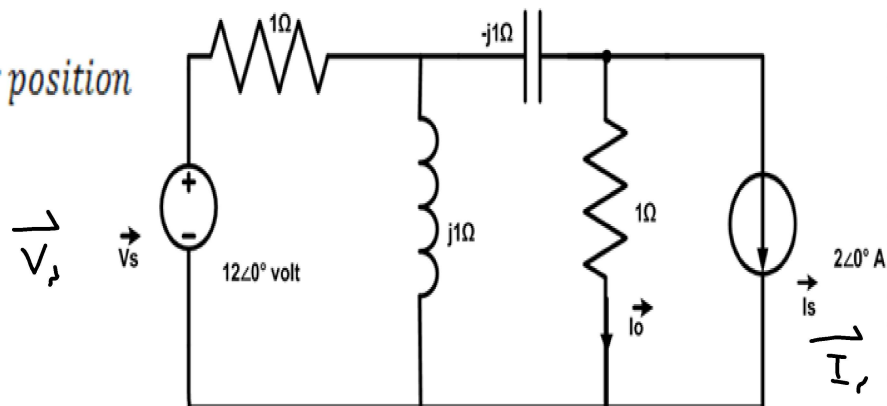

$$\vec{I}_o = \vec{I}_{o1} + \vec{I}_{o2}$$

due to  $\vec{V}_s$       due to  $\vec{I}_s$

①  $\vec{I}_{o1}$  due to  $\vec{V}_F$

$$\vec{I}_{o1} = \frac{(1 \parallel j)}{(1 \parallel j) + (1 - j)} * (12 \angle 0^\circ)$$




$$= \frac{j / (1+j)}{j / (1+j) + (1-j)} * 12 \angle 0^\circ$$

$$= \frac{j}{j + (1-j)(1+j)} * 12 \angle 0^\circ$$

$$= (0.2 + 0.4j)(12 \angle 0^\circ)$$

$$= 2.4 + j4.8 \text{ A}$$

$$= 5.366 \angle 63.43^\circ \text{ A}$$

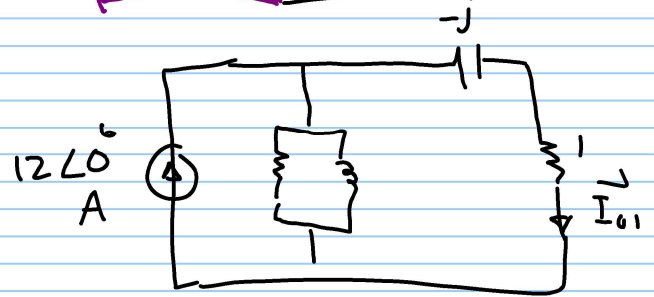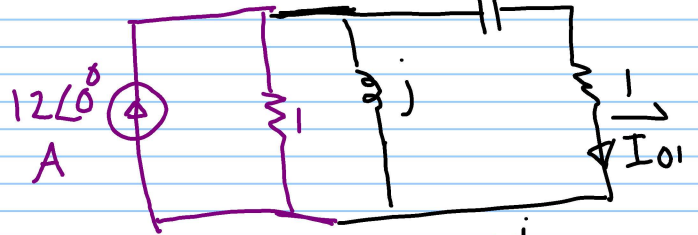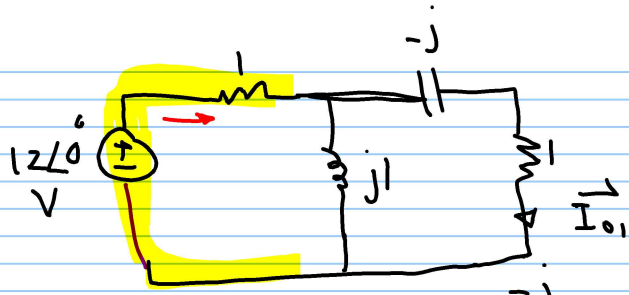


$\vec{I}_{o2}$  due to  $\vec{I}_F$

$$\vec{I}_{o2} = - \frac{[(1 \parallel j) - j]}{[(1 \parallel j) - j] + 1} * 2 \angle 0^\circ$$

$$= - \frac{j / (1+j) - j}{j / (1+j) - j + 1} * 2 \angle 0^\circ$$
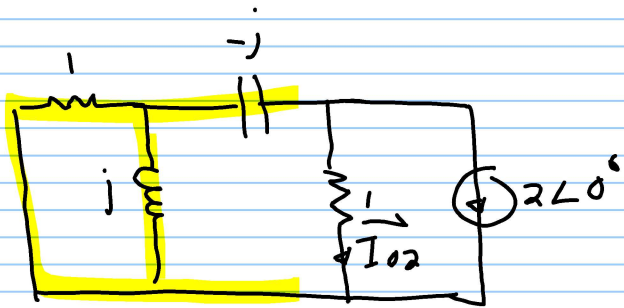
$$= - \frac{0.5 - 0.5j}{1.5 - 0.5j} * 2 \angle 0^\circ = \frac{-0.5 + 0.5j}{1.5 - 0.5j} * 2 \angle 0^\circ = -0.8 + 0.4j \text{ A}$$



$$\vec{I}_0 = \vec{I}_{01} + \vec{I}_{02}$$

$$= (2.4 + 4.8j) + (-0.8 + 0.4j)$$

$$= 1.6 + 5.2j \text{ A}$$


Power of super position :

$$V_{s1}(t) = 100 \cos 10t \text{ volt}$$

$$V_{s2}(t) = 50 \cos(20t - 10^\circ) \text{ volt.}$$

note that  $\omega_1 = 10 \text{ rad/sec}$

and  $\omega_2 = 20 \text{ rad/sec}$

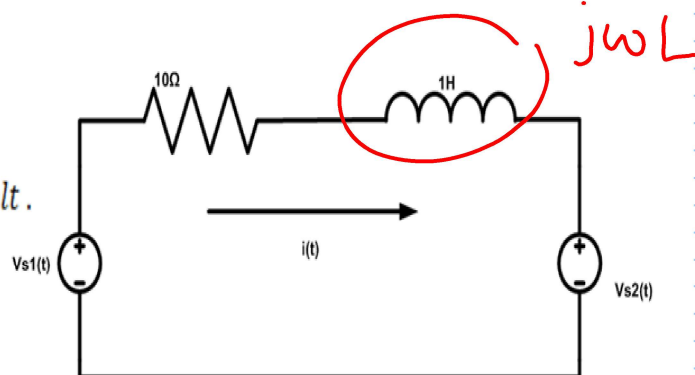


∴ super position is the only method of analysis.

$$i(t) = i_1(t) + i_2(t).$$

$$\vec{I}_1 = \frac{100 \angle 0^\circ}{10 + j10}$$

$$= 5 - j5 \text{ A}$$


$$= 7.07 \angle -45^\circ \text{ A}$$

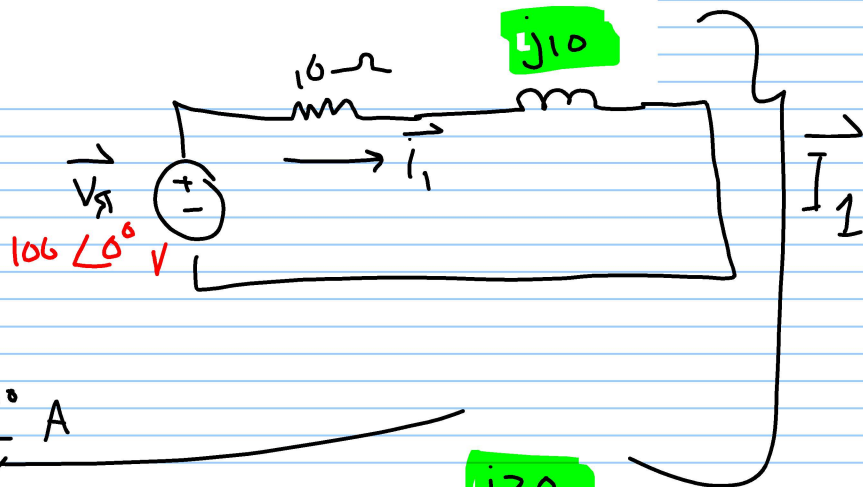

$$\vec{I}_2 = \frac{50 \angle -10^\circ}{10 + j20}$$

$$= -0.637 + j2.143 \text{ A}$$

$$= 2.235 \angle 106.5^\circ \text{ A}$$

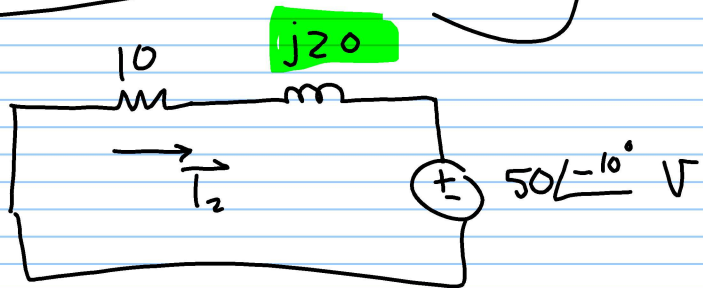


$$\vec{I} = \vec{I}_1 + \vec{I}_2$$

= You can't add them !!

$$i(t) = i_1(t) + i_2(t)$$

$$= 7.07 \cos(16t - 45^\circ) + 2.235 \cos(20t + 106.5^\circ)$$

## Superposition (dc+ac) sources

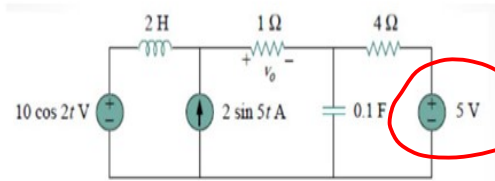

DC !!



Find  $v_o(t)$  using the superposition theorem