

**CHAPTER
12**

Introduction to the Laplace Transform

TABLE 12.1 An Abbreviated List of Laplace Transform Pairs

Type	$f(t)$ ($t > 0^-$)	$F(s)$
(impulse)	$\delta(t)$	1
(step)	$u(t)$	$\frac{1}{s}$
(ramp)	t	$\frac{1}{s^2}$
(exponential)	e^{-at}	$\frac{1}{s + a}$
(sine)	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
(cosine)	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
(damped ramp)	te^{-at}	$\frac{1}{(s + a)^2}$
(damped sine)	$e^{-at} \sin \omega t$	$\frac{\omega}{(s + a)^2 + \omega^2}$
(damped cosine)	$e^{-at} \cos \omega t$	$\frac{s + a}{(s + a)^2 + \omega^2}$

TABLE 12.2 An Abbreviated List of Operational Transforms

Operation	$f(t)$	$F(s)$
Multiplication by a constant	$Kf(t)$	$KF(s)$
Addition/subtraction	$f_1(t) + f_2(t) - f_3(t) + \dots$	$F_1(s) + F_2(s) - F_3(s) + \dots$
First derivative (time)	$\frac{df(t)}{dt}$	$sF(s) - f(0^-)$
Second derivative (time)	$\frac{d^2f(t)}{dt^2}$	$s^2F(s) - sf(0^-) - \frac{df(0^-)}{dt}$
n th derivative (time)	$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1}f(0^-) - s^{n-2}\frac{df(0^-)}{dt} - \dots - \frac{d^{n-1}f(0^-)}{dt^{n-1}}$
Time integral	$\int_0^t f(x)dx$	$\frac{F(s)}{s}$
Translation in time	$f(t-a)u(t-a), a > 0$	$e^{-as}F(s)$
Translation in frequency	$e^{-at}f(t)$	$F(s+a)$
Scale changing	$f(at), a > 0$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
First derivative (s)	$tf(t)$	$\frac{dF(s)}{ds}$
n th derivative (s)	$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$
s integral	$\frac{f(t)}{t}$	$\int_s^\infty F(u)du$


12.7 Inverse Transforms

Partial Fraction Expansion:


CHAPTER 13

The Laplace Transform in Circuit Analysis

13.1 Circuit Elements in the s Domain

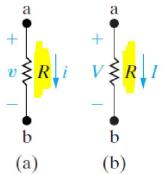

(a)

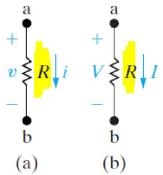

(b)

Figure 13.1 ▲ The resistance element. (a) Time domain.
(b) Frequency domain.

$$V = R i$$

$$\mathcal{L}$$

Time Domain

$$V = R I$$

s-Domain

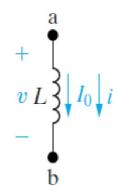




Figure 13.2 ▲ An inductor of L henrys carrying an initial current of I_0 amperes.

$$\mathcal{L}(V = L \frac{di}{dt})$$

$$s = j\omega$$

$$V = L [sI - i(0^-)]$$

$$(V = L s I - L I_0)$$

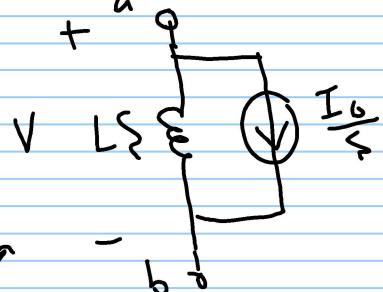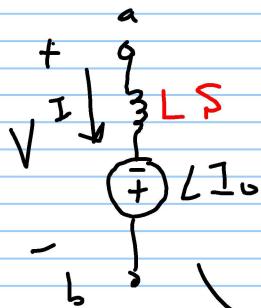

Source Transformation


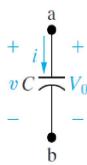


Figure 13.6 ▲ A capacitor of C farads initially charged to V_0 volts.


$$\mathcal{L}(i = C \frac{dv}{dt})$$

$$I = C [sV - V(0^-)]$$

$$I = C s V - C V_0$$

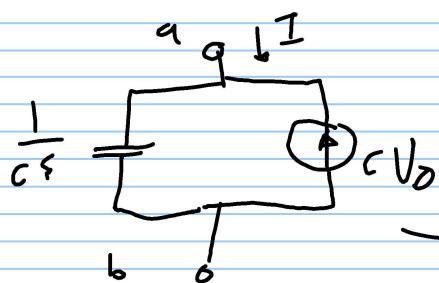

Source Transf →

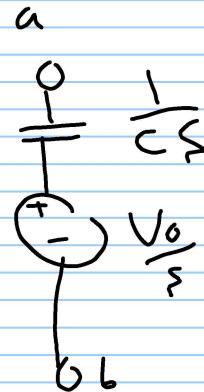


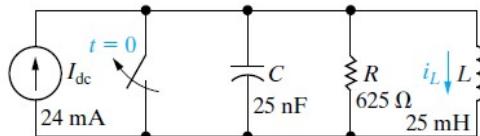


Figure 13.13 ▲ The step response of a parallel RLC circuit.

find $i_L(t)$, V , & $I_0 = 24 \text{ mA}$

ζ -domain

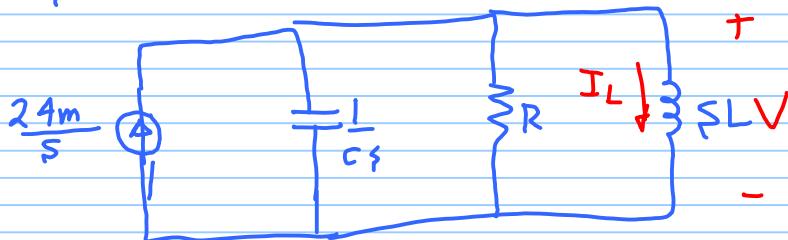

$$\frac{24 \text{ mA}}{\zeta} = C \zeta V + \frac{V}{R} + \frac{V}{sL}$$

$$V = \frac{24 \text{ mA}/\zeta}{\zeta^2 + \frac{1}{RC}\zeta + \frac{1}{LC}}, \quad I_L = \frac{V}{sL}$$

$$I_L = \frac{24 \text{ mA}/\zeta}{s(\zeta^2 + \frac{1}{RC}\zeta + \frac{1}{LC})}$$

$$= \frac{384 \times 10^5}{\zeta(\zeta^2 + 64000\zeta + 16 \times 10^8)} + \left(\frac{64000}{2} \right)^2 - \left(\frac{64000}{2} \right)^2$$

$$= \frac{384 \times 10^5}{\zeta \left[(\zeta^2 + 64000\zeta + 1.024 \times 10^9) + 576 \times 10^6 \right]}$$

$$= \frac{384 \times 10^5}{\zeta \left[(\zeta + 32000)^2 + 576 \times 10^6 \right]}$$

$$= \frac{k_1}{\zeta} + \frac{k_2 \zeta + k_3}{(\zeta + 32000)^2 + 576 \times 10^6}$$

TIME DOMAIN	FREQUENCY DOMAIN

$$K_1 = 24 \times 10^{-3}, K_2 = -24 \times 10^{-3}, K_3 = -1536$$

$$\begin{aligned} \text{oo } I_L &= \frac{24 \times 10^{-3}}{\omega} - 24 \times 10^{-3} \frac{\omega + 64000}{(\omega + 32000)^2 + 576 \times 10^6} \omega \sin \omega t \leftarrow \frac{\omega}{\omega^2 + \omega^2} \\ &= \frac{24 \times 10^{-3}}{\omega} - 24 \times 10^{-3} \frac{(\omega + 32000) + 32000}{(\omega + 32000)^2 + 576 \times 10^6} \sin \omega t \leftarrow \frac{\omega}{\omega^2 + \omega^2} \\ &= \frac{24 \times 10^{-3}}{\omega} - 24 \times 10^{-3} \left[\frac{(\omega + 32000)}{(\omega + 32000)^2 + 576 \times 10^6} + \frac{32000}{(\omega + 32000)^2 + 576 \times 10^6} \right] \\ &= \frac{24 \times 10^{-3}}{\omega} - 24 \times 10^{-3} \left[\frac{\omega + 32000}{(\omega + 32000)^2 + (24000)^2} + \frac{1}{3} \frac{24000}{(\omega + 32000)^2 + (24000)^2} \right] \end{aligned}$$

$$i_L(t) = 24m - 24m \left(e^{\frac{-32000t}{\omega}} \cos 24000t + \frac{1}{3} \sin 24000t e^{\frac{-32000t}{\omega}} \right)$$

$$= 24m - 24m e^{\frac{-32000t}{\omega}} \left(\cos 24000t + \frac{1}{3} \sin 24000t \right)$$

$$+ 90^\circ$$

$$1L0 + \frac{4}{3} \angle -70^\circ$$

$$1 - j \frac{4}{3}$$

$$5 \angle -53.13^\circ$$

$$\text{oo } i_L(t) = 24m - 40m e^{\frac{-32000t}{\omega}} \cos(24000t - 53.13^\circ) A \quad \checkmark$$

$$\text{OR } i_L(t) = 24m + 40m e^{\frac{-32000t}{\omega}} \cos(24000t + 126.87^\circ) A \quad \checkmark$$

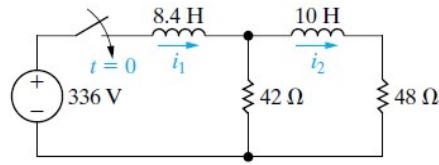


Figure 13.15 ▲ A multiple-mesh RL circuit.

Figure P13.86

