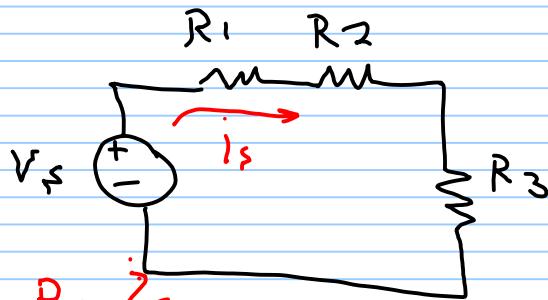


→ Resistors in series :-

KVL

$$-V_s + R_1 i_s + R_2 i_s + R_3 i_s = 0$$

$$V_s = (R_1 + R_2 + R_3) i_s \quad V_s = R_{eq} i_s$$




$$\hookrightarrow R_{eq} = R_1 + R_2 + R_3$$

↳ series elements have the same current.

→ Resistors in Parallel :-

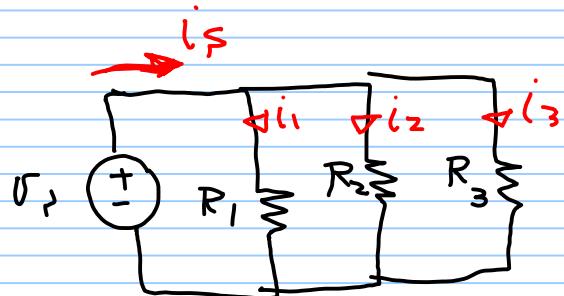↳ parallel elements have the same voltage




$$i_1 = \frac{V_s}{R_1}, \quad i_2 = \frac{V_s}{R_2}, \quad i_3 = \frac{V_s}{R_3}$$

$$\hookrightarrow i_s = i_1 + i_2 + i_3$$

$$i_s = V_s \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\therefore \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
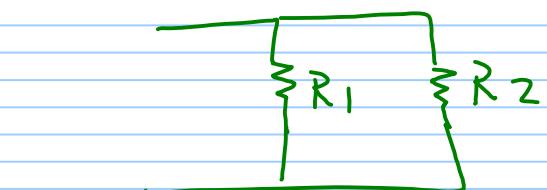
$$\frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i}$$



$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


Ex)

find  $i_1$ ,  $i_1$ ,  $i_2$

$$R_{\text{eq}} = \left[ \frac{(3+6)}{18} \parallel 18 \right] + 4$$

$$= 10 \Omega$$
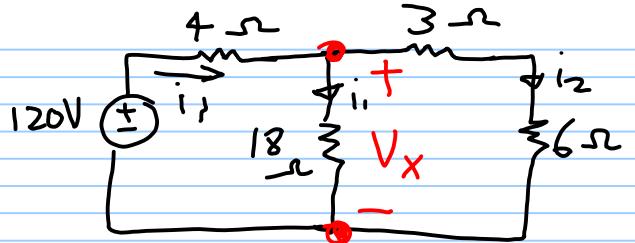
$$\text{or } i_1 = \frac{V_F}{R_{\text{eq}}} = \frac{120}{10} = 12 \text{ A}$$



$$\begin{cases} i_1 = \frac{9}{9+18} * 12 \\ i_2 = \frac{18}{18+9} * 12 \end{cases}$$

CDR




$$\rightarrow -120 + 4 \times 12 + V_x = 0 \quad (\text{KVL})$$


$$V_x = 72 \text{ V}$$

$$\therefore i_1 = \frac{V_x}{18} = \frac{72}{18} = 4 \text{ A}$$

$$\text{or } i_2 = i_1 - i_1 = 12 - 4 = 8 \text{ A}$$

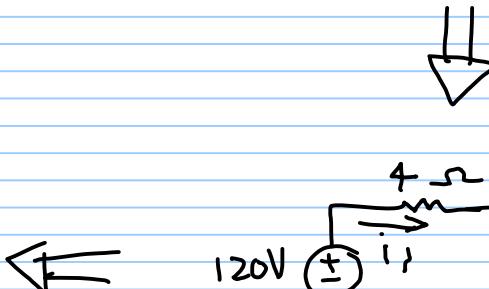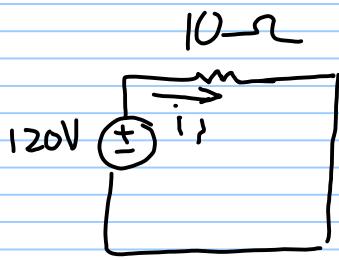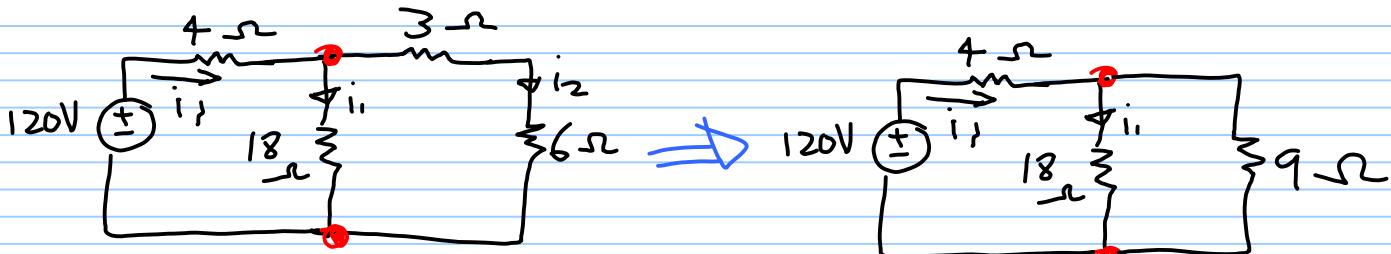
$$\text{OR } i_2 = \frac{V_x}{3+6} = \frac{72}{9} = 8 \text{ A}$$



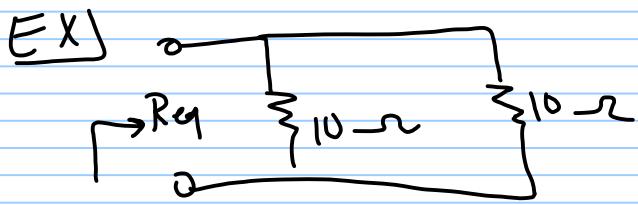

$$R_{eq} = \frac{10 \times 10}{10 + 10} = 5$$


$$= 10/2$$

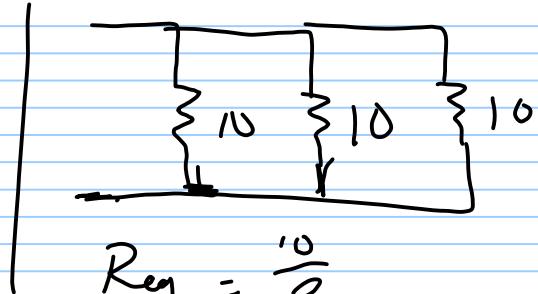

$$R_{eq} = \frac{10}{3}$$
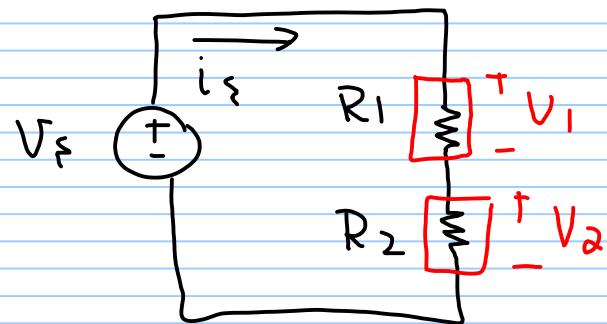
## The Voltage Divider Rule VDR

→ applied when the voltage is divided between series elements.



$$\rightarrow i_s = \frac{V_s}{R_1 + R_2}$$

$$\therefore V_1 = i_s R_1$$

$$V_1 = \frac{R_1}{R_1 + R_2} V_s$$


$$V_1 = \frac{R_1}{R_{eq}} V_s$$

$$\therefore V_2 = i_s R_2$$

$$V_2 = \frac{R_2}{R_1 + R_2} V_s$$

$$V_2 = \frac{R_2}{R_{eq}} V_s$$

Ex]

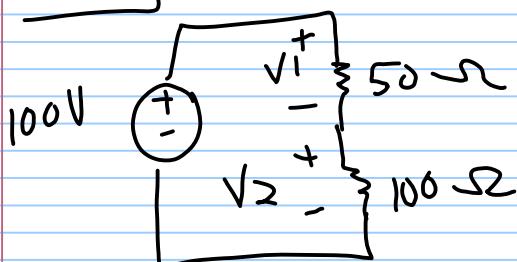


$$V_1 = \frac{50}{50 + 100} \times 100 = 33.33 V$$

$$V_2 = \frac{100}{100 + 50} \times 100 = 66.66 V$$

$$= 2 \times V_1$$


Ex

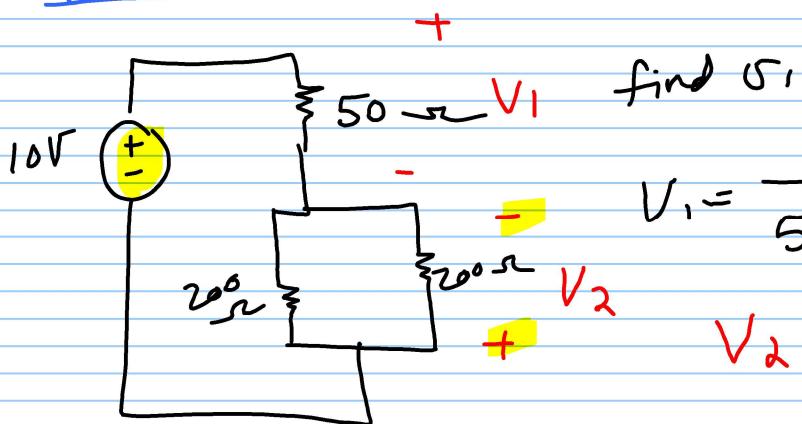

find  $V_1$

$$V_1 = \frac{50}{50 + \frac{200}{2}} * 10$$
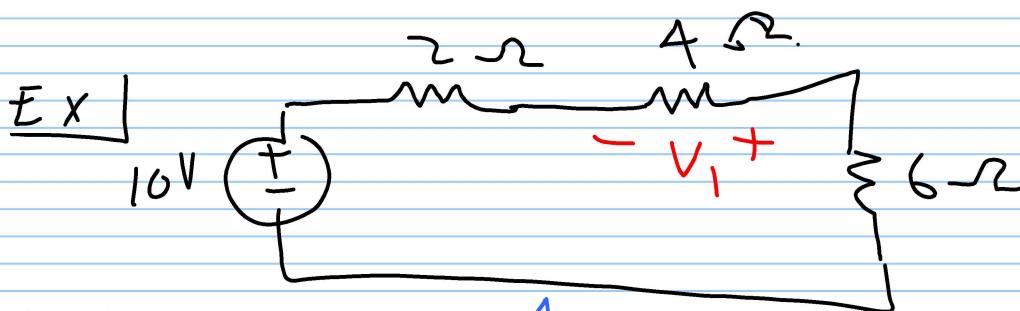
$$V_2 = \frac{-200/2}{(200/2) + 50} * 10$$




find  $V_1$

$$V_1 = \frac{4}{4 + (2+6)} * 10$$



$R_y$

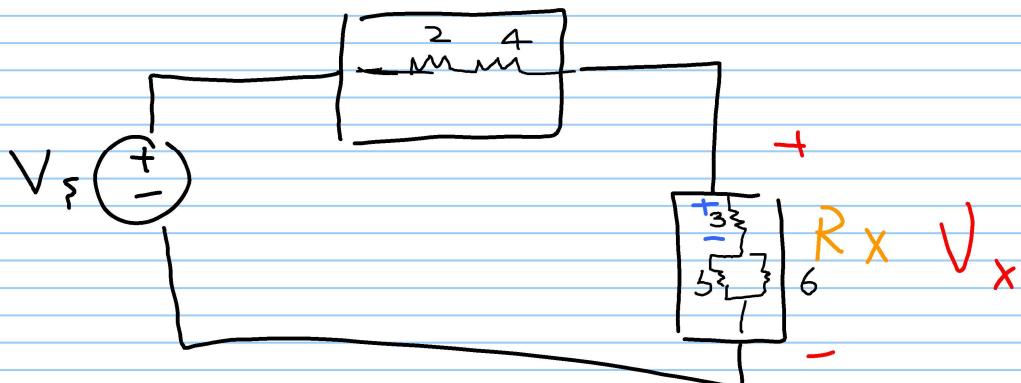

$$\textcircled{1} \quad V_x = \frac{R_x}{R_x + R_y} V_s$$


$$R_x = [3 + (6//5)]$$

$$R_y = (2+4)$$

$$\textcircled{2} \quad \text{find } V_{3\Omega} \quad V_{3\Omega} = \frac{3}{3 + [2+4+\frac{30}{11}]} V_s$$

OR

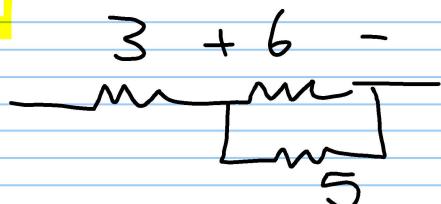
$$V_{3\text{-}\Omega} = \frac{3}{3 + [6/5]} \quad V_X$$



& find  $V_{6\text{-}\Omega}$

$$V_{6\text{-}\Omega} = \frac{[6/5]}{[6/5] + 3} * V_X$$

-----#-----

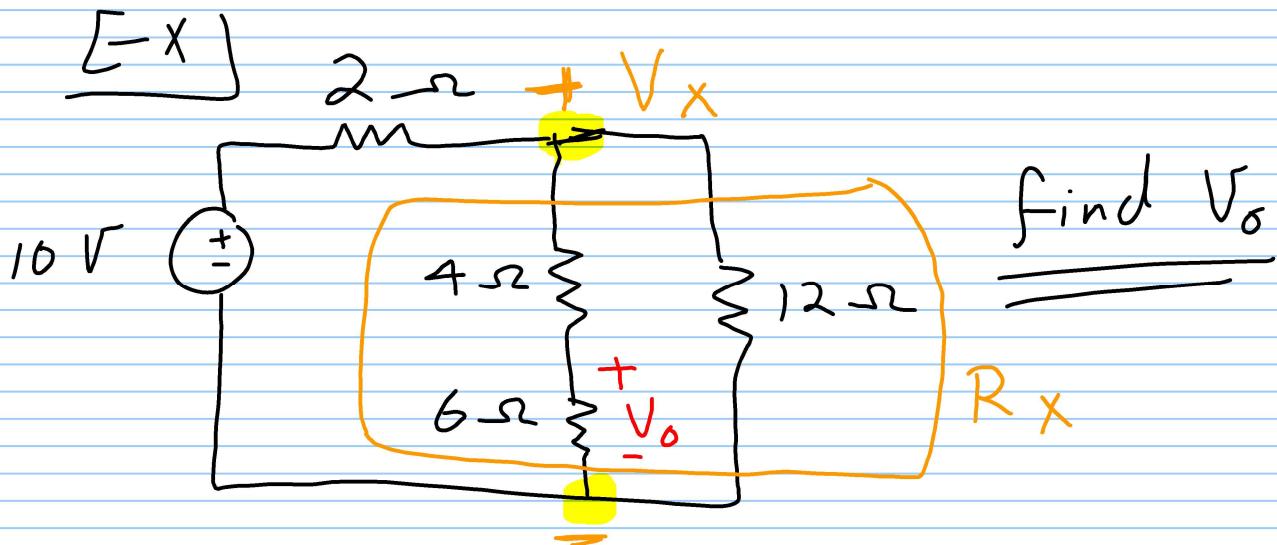

$$V_X = \frac{R_X}{R_X + 2} \times 10 \quad , \text{ then}$$

$$R_X = 10/12 \\ = 5.45 \Omega$$

$$V_o = \frac{6}{6+4} * V_X$$

$$\Rightarrow V_o = \frac{6}{6+4} \left( \frac{R_X}{R_X + 2} \right) \times 10$$


$$= \left( \frac{6}{10} \right) \left( \frac{5.45}{7.45} \right) * 10 \checkmark = 4.389 V$$

# The current Divider Rule
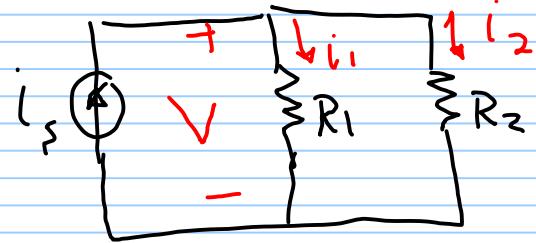
## CDR

$$V = i_1 R_1 = i_2 R_2$$

$$= i_s \times \frac{R_1 R_2}{R_1 + R_2}$$



$$\therefore i_1 = \frac{R_{eq}}{R_1} i_s \quad \text{OR}$$

$$= \frac{R_2}{R_2 + R_1} i_s$$


$$i_2 = \frac{R_{eq}}{R_2} i_s \quad \text{OR}$$

$$= \frac{R_1}{R_1 + R_2} i_s$$

Ex find  $i_1$

$$i_1 = -\frac{6}{6+4} \times 2$$

$$= -1.2 \text{ A}$$

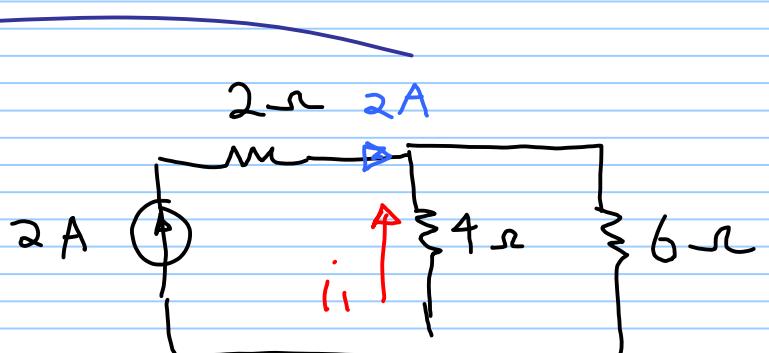

E = X

find  $V_o$

① find  $i_f$

$$\begin{aligned} R_{eq} &= 2 + [10//12] \\ &= 2 + 5 \cdot 45 \\ &= 7 \cdot 45 \Omega \end{aligned}$$

$$\therefore i_f = \frac{10}{R_{eq}} = \frac{10}{7 \cdot 45} = \underline{1.34 A}$$

② find  $i_x$


$$i_x = \frac{12}{12 + (4+6)} * (1.34) = 0.73 A$$

$$o\ o V_o = (6 \Omega)(0.73 A)$$


$$= 4.38 \text{ Volt.}$$

E X

find  $i_x$

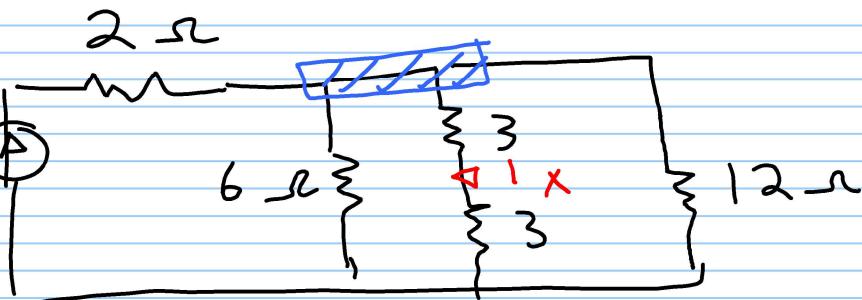
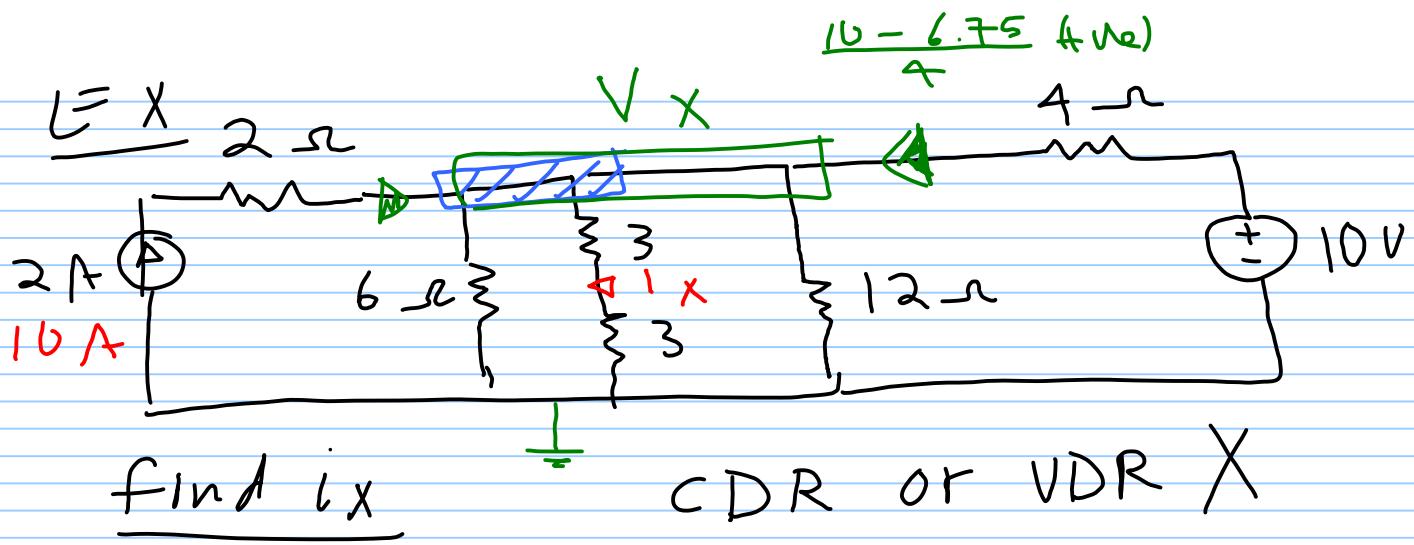
$$i_x = \frac{[6//12]}{[6//12] + [3+3]} * 2 \text{ A}$$



use KVL & KCL

ch 4

$$-2 + \frac{V_x}{6} + \frac{V_x}{3+3} + \frac{V_x}{12} + \frac{V_x - 10}{4} = 0$$

$$V_x = \text{Volt}$$


$$\text{or } i_x = \frac{V_x}{3+3} \text{ A}$$

$$V_x \left( \frac{1}{6} + \frac{1}{6} + \frac{1}{12} + \frac{1}{4} \right) = 2 + \frac{10}{4}$$



$$V_x \left( \frac{2}{3} \right) = 4.5$$

$$V_x = 6.75 \text{ Volt}$$

when using  
(10A)  
 $V_x = 18.75$

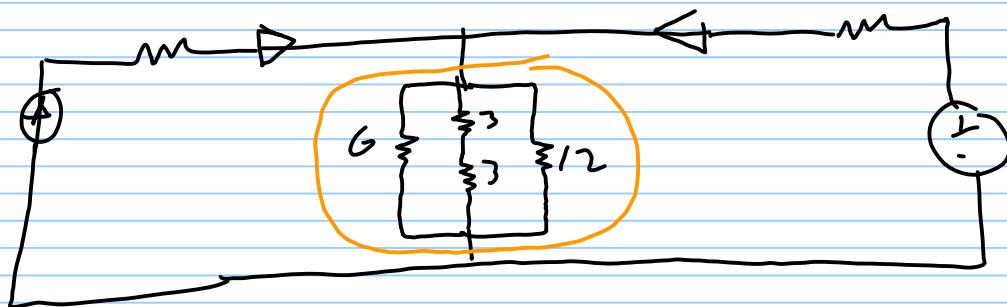

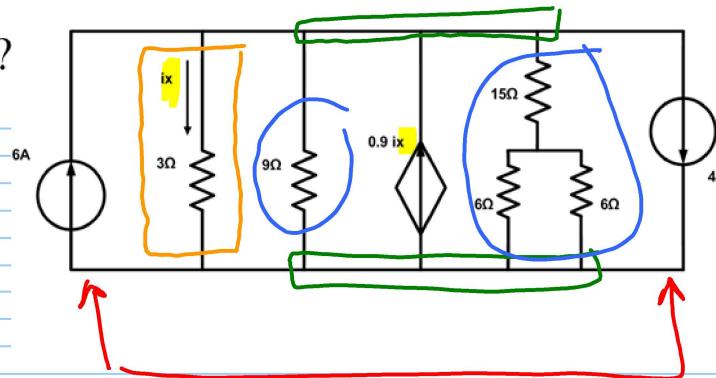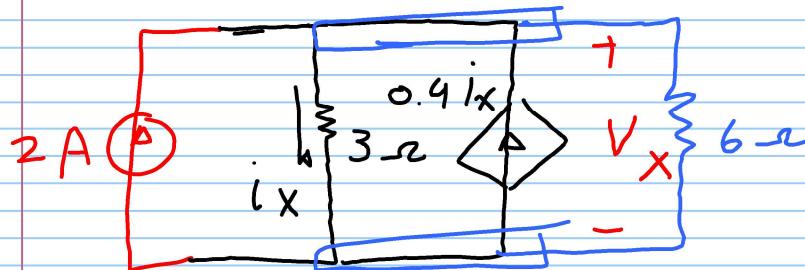Find the power supplied by the  $0.9 i_x$  source?



$$R_{eq}^* = 9 // [15 + 3]$$

$$= 9 // 18$$

$$= 6\Omega$$

CDR

$$i_x = \frac{6}{6+3} [2 + 0.9 i_x]$$

$$i_x = \frac{12 + 5.4 i_x}{9}$$

$$\{ 9 i_x = 12 + 5.4 i_x \}$$

$$\therefore i_x = \frac{12}{9 - 5.4} = 3.33 A$$

$$V_x = (3\Omega)(3.33)$$

$$\approx 10 V_{olt}$$

$$P_{0.9 i_x} = -(0.9 i_x)(V_x)$$

$$= -30 W$$

### Bridge Circuits

One type of resistive circuit that cannot be simplified through series and/or parallel combinations is the “bridge circuit.” A bridge circuit is shown below (drawn twice). Study the circuit to verify that there are no series resistors and no parallel resistors.

