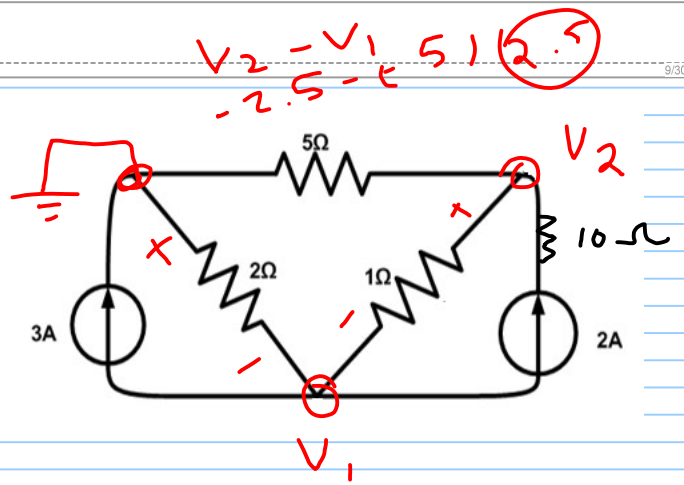


$$\underline{\underline{CN = 4}}$$

Nodal  
method

@ node  $V_1$

All currents are out }  
OR " ~ " IN }



$$\underline{I_{out}} \quad 3 + \frac{V_1}{2} + \frac{V_1 - V_2}{1} + 2 = 0$$

$$\sum I_{out} = 0 \quad \text{OR}$$

$$\sum I_{IN} = 0$$

$$(1.5) \quad V_1 - V_2 = -5 \quad \text{--- (1)}$$

@ Node  $V_2$

$$\underline{I_{out}} \quad -2 + \frac{V_2 - V_1}{1} + \frac{V_2}{5} = 0$$

$$-V_1 + 1.2V_2 = 2 \quad \text{--- (2)}$$

$$V_1 = -5V$$


$$V_2 = -2.5V$$

@ node  $V_1$

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_1 - \left(\frac{1}{R_1}\right)V_2 = I_{S1}$$

@ node  $V_2$

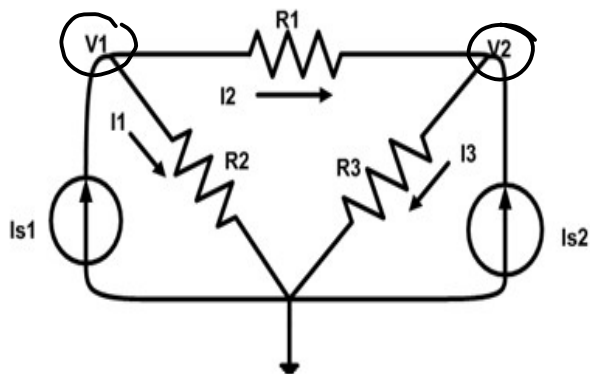
$$-\left(\frac{1}{R_1}\right)V_1 + \left(\frac{1}{R_1} + \frac{1}{R_3}\right)V_2 = I_{S2}$$



@ node 1

$$\sum I_{out} = \sum I_{in}$$
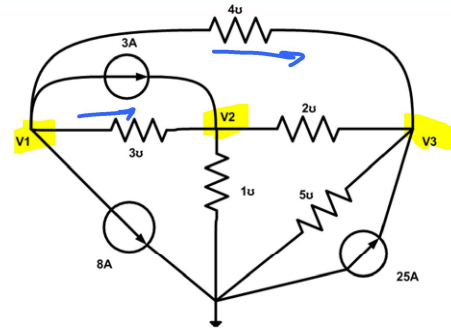
$$7V_1 - 3V_2 - 4V_3 = -11 \quad \text{--- (1)}$$



@ node  $V_2$


$$3(V_1 - V_2) + 4(V_1 - V_3) + 3 + 8 = 0$$

$$-(3)V_1 + (3+2+1)V_2 - (2)V_3 = 3 \quad \text{--- (2)}$$

@ node  $V_3$

$$-4V_1 - 2V_2 + (5+2+4)V_3 = 25 \quad \text{--- (3)}$$

EX

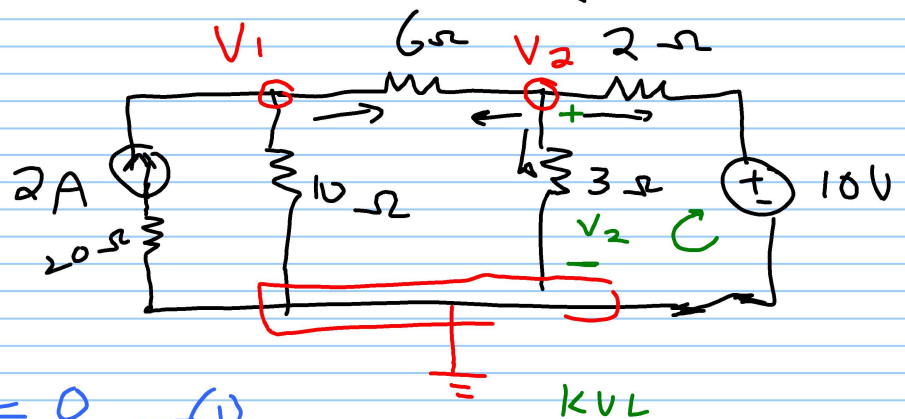

$$\sum I_{out} = \sum I_{in}$$

node 1

$$-2 + \frac{V_1}{10} + \frac{V_1 - V_2}{6} = 0 \quad \text{--- (1)}$$

node 2

$$\sum I_{out} = 0$$

$$\frac{V_2 - V_1}{6} + \frac{V_2}{3} + \frac{V_2 - 10}{2} = 0 \quad \text{--- (2)}$$


$$-V_2 + 2I_x + 10 = 0$$

$$I_x = \frac{V_2 - 10}{2}$$

$$V_1 = \text{---}$$

$$V_2 = \text{---} \quad \checkmark$$

EX1

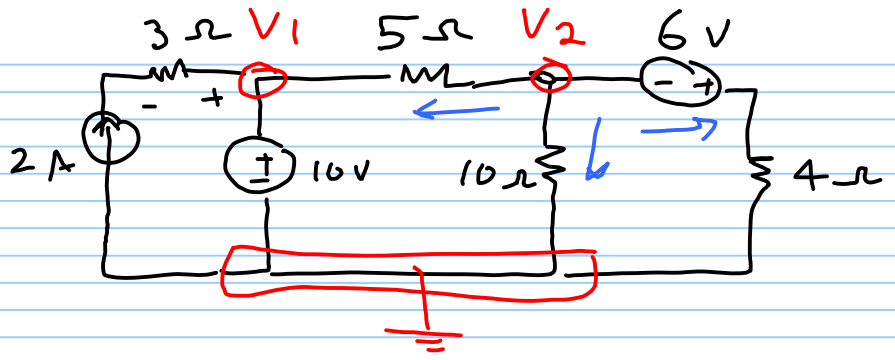

$$(-2) + (V_1 - 10) \quad \times$$

$$V_1 = 10 \text{ V} \quad (\text{smiley face})$$


@ node V2

$$\frac{V_2 - 10}{5} + \frac{V_2}{10} + \frac{V_2 + 6}{4} = 0$$

$$0.55 V_2 = 2 - 1.5$$

$$V_2 = \frac{0.5}{0.55} = 0.909 \text{ Volt}$$

EX2

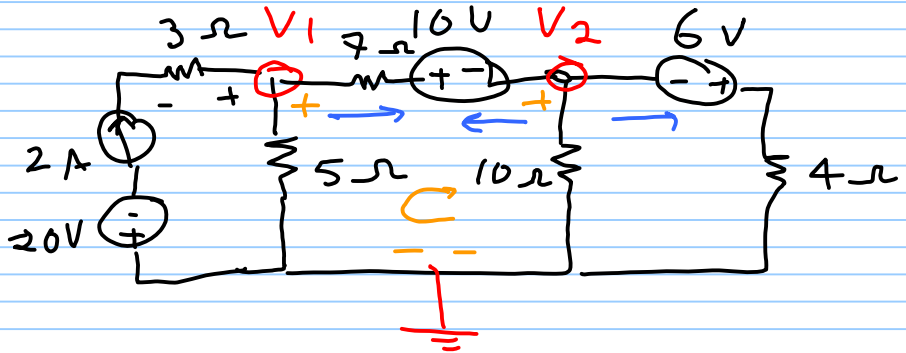

$$\sum I_{out} = 2 \text{ amp}$$

@ node V1

$$-2 + \frac{V_1}{5} + \frac{V_1 - 10 - V_2}{7} = 0 \quad \text{--- (1)}$$

@ node V2

$$\frac{V_2 - V_1 + 10}{7} + \frac{V_2}{10} + \frac{V_2 + 6}{4} = 0 \quad \text{--- (2)}$$

Special case

$I_x$

@ node  $V_1$

$$-2 + \frac{V_1}{5} + \underline{I_x} = 0$$

$$-2 + \frac{V_1}{5} + \frac{V_2}{10} + \frac{V_2 + 6}{4} = 0 \quad \text{--- (1) KVL}$$

$$\underline{V_1 - V_2 = 10} \quad \text{--- (2) KVL @ supernode}$$

