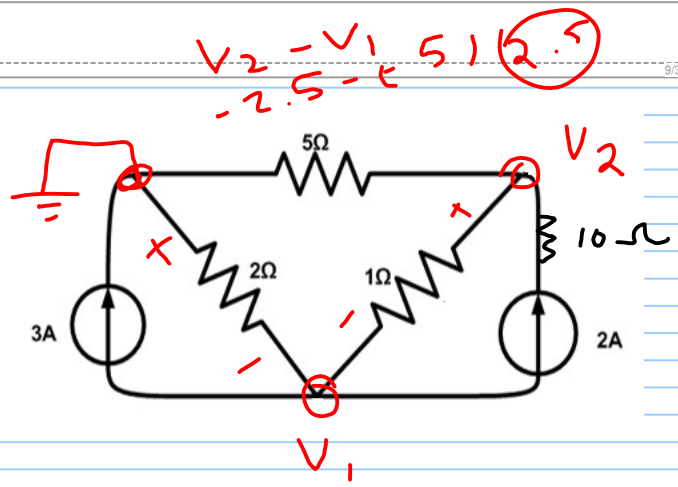


CK = 4

Nodal method

@ node V_1

All currents are out }
OR " ~ " IN }



I_{out} $3 + \frac{V_1}{2} + \frac{V_1 - V_2}{1} + 2 = 0$

$\sum I_{out} = 0$ OR $\sum I_{IN} = 0$

(1.5) $V_1 - V_2 = -5$ — (1)

@ Node V_2

I_{out} $-2 + \frac{V_2 - V_1}{1} + \frac{V_2}{5} = 0$

$-V_1 + 1.2V_2 = 2$ — (2)


$V_1 = -5V$
 $V_2 = -2.5V$

@ node V_1

$(\frac{1}{R_1} + \frac{1}{R_2})V_1 - (\frac{1}{R_1})V_2 = I_{S1}$

@ node V_2

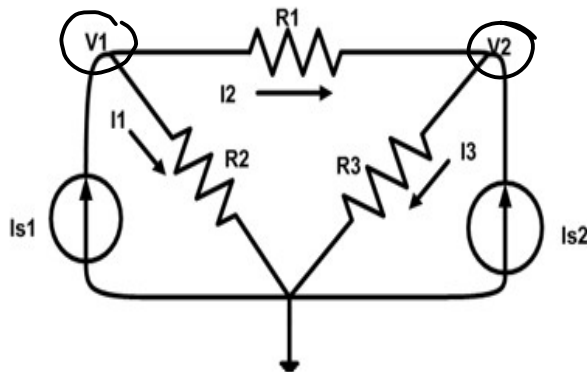
$-(\frac{1}{R_1})V_1 + (\frac{1}{R_1} + \frac{1}{R_3})V_2 = I_{S2}$



@ node 1

$$\sum I_{out} = \sum I_{in}$$
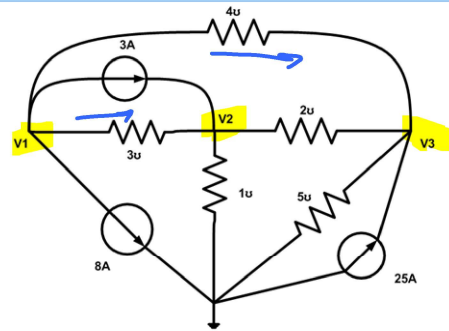
$$7V_1 - 3V_2 - 4V_3 = -11 \quad \text{--- (1)}$$



@ node V_2

$$3(V_1 - V_2) + 4(V_1 - V_3) + 3 + 8 = 0$$

$$-(3)V_1 + (3+2+1)V_2 - (2)V_3 = 3 \quad \text{--- (2)}$$

@ node V_3


$$-4V_1 - 2V_2 + (5+2+4)V_3 = 25 \quad \text{--- (3)}$$

EX

$$\sum I_{out} = 2 \text{ cr}$$

node 1

$$-2 + \frac{V_1}{10} + \frac{V_1 - V_2}{6} = 0 \quad \text{--- (1)}$$

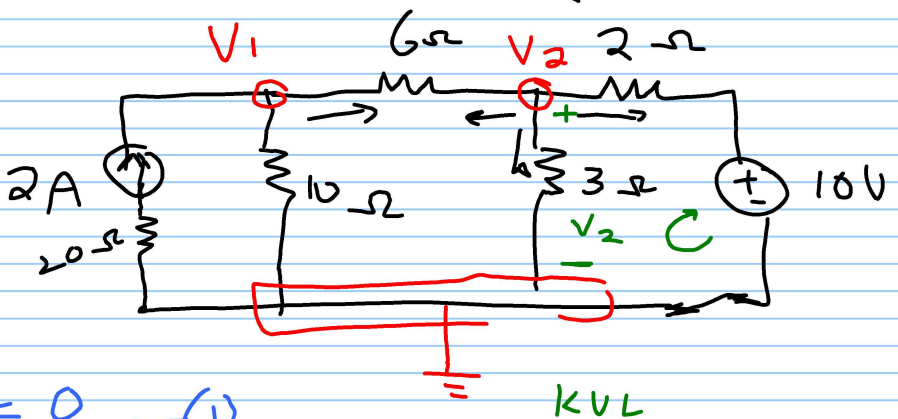

node 2

$$\sum I_{out} = 0$$

$$\frac{V_2 - V_1}{6} + \frac{V_2}{3} + \frac{V_2 - 10}{2} = 0 \quad \text{--- (2)}$$


$$-V_2 + 2I_x + 10 = 0$$

$$I_x = \frac{V_2 - 10}{2}$$

$$V_1 = \text{---}$$

$$V_2 = \text{---} \quad \checkmark$$

EX1

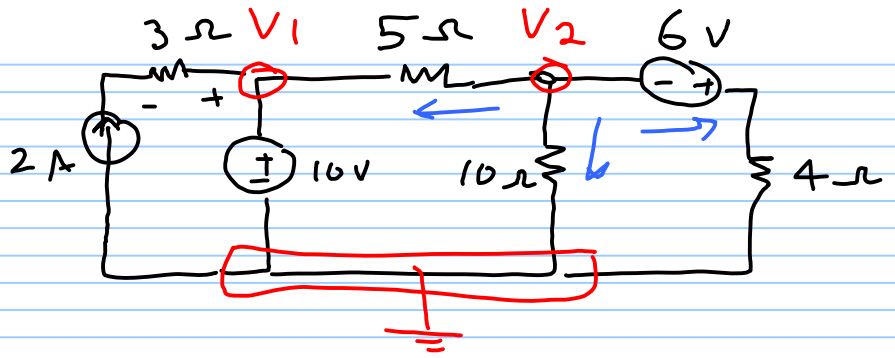

$$(-2) + (V_1 - 10) = 0$$

$$V_1 = 10 \text{ V} \quad (\text{yep})$$


@ node V2

$$\frac{V_2 - 10}{5} + \frac{V_2}{10} + \frac{V_2 + 6}{4} = 0$$

$$0.55 V_2 = 2 - 1.5$$

$$V_2 = \frac{0.5}{0.55} = 0.909 \text{ Volt}$$

EX2

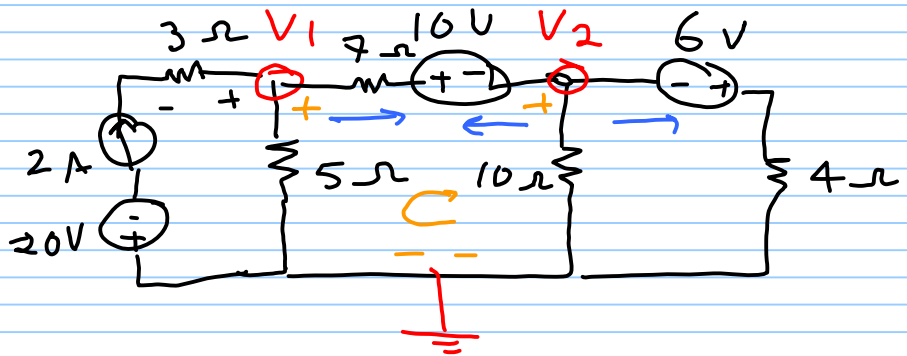

$$\sum I_{out} = 2 \text{ A}$$

@ node V1

$$-2 + \frac{V_1}{5} + \frac{V_1 - 10 - V_2}{7} = 0 \quad \text{--- (1)}$$

@ node V2

$$\frac{V_2 - V_1 + 10}{7} + \frac{V_2}{10} + \frac{V_2 + 6}{4} = 0 \quad \text{--- (2)}$$

Special case


EX

@ node V_1

$$-2 + \frac{V_1}{5} + \underline{I_x} = 0$$

$$-2 + \frac{V_1}{5} + \frac{V_2}{10} + \frac{V_2 + 6}{4} = 0 \quad \text{--- (1) KVL}$$
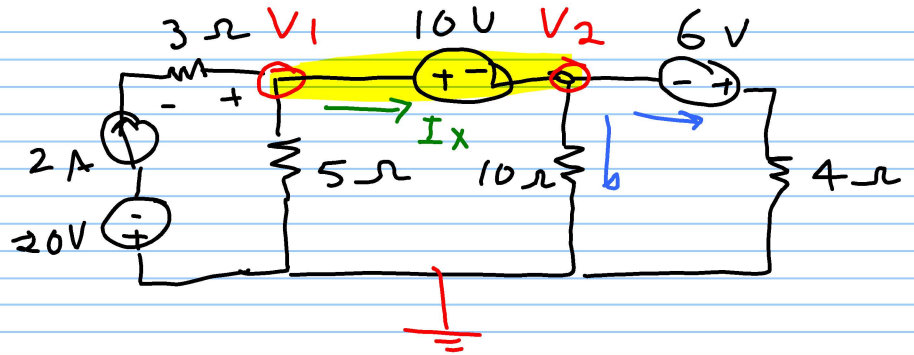
$$\underline{V_1 - V_2 = 10} \quad \text{--- (2) KVL @ supernode}$$



EX

$$I_o = \frac{V_2}{3k} \quad \text{--- (1)}$$

@ node V_1


$$2I_o + \frac{V_1}{12k} + \frac{V_1 - V_2}{6k} = 0$$

$$2\left(\frac{V_2}{3k}\right) + \frac{V_1}{12k} + \frac{V_1 - V_2}{6k} = 0 \quad \text{--- (1) } \checkmark$$

@ node V_2

$$\frac{V_2 - V_1}{6k} + \frac{V_2}{3k} + 2mA = 0 \quad \text{--- (2) } \checkmark$$
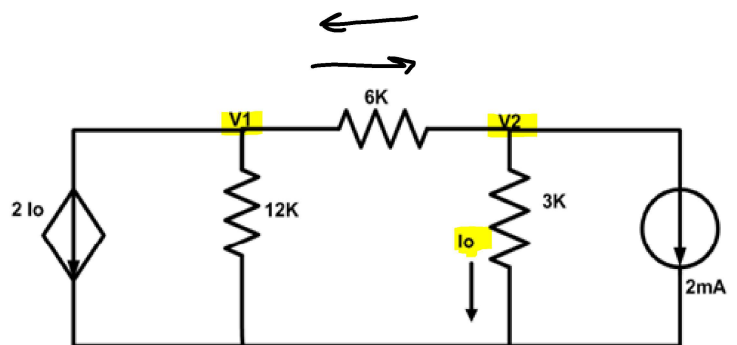
$$V_1 = -\frac{24}{5} V, \quad V_2 = \frac{12}{5} V$$




Mesh method

$$I_{R_3} = I_A$$

$$I_{R_2} = I_A - I_C$$


$$I_{R_{13}} = -I_D$$

$$I_{R_{10}} = I_B - I_A$$

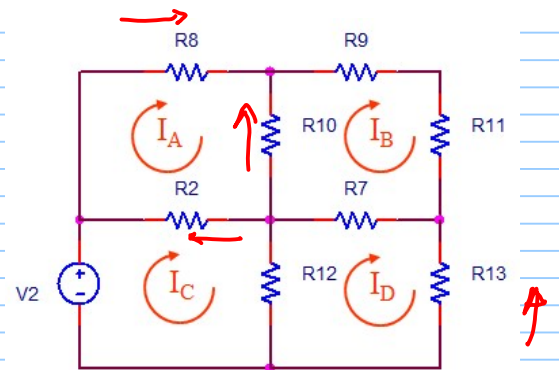

4 equations

4 unknowns I_A, I_B, I_C
 ~~I_D~~

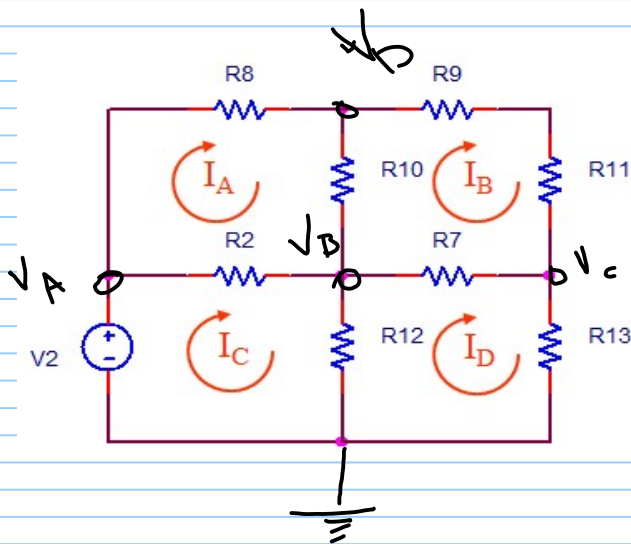


$$V_A = V_2$$

Nodal method

3 eqs

3 unknowns

$$V_B, V_C, V_D$$

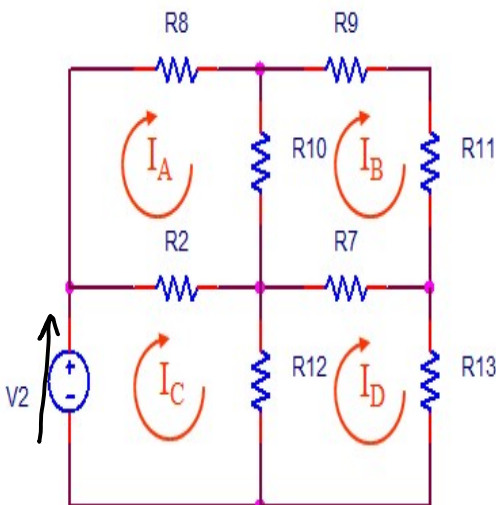

Mesh KVL

$$R_8 I_A + R_{10} (I_A - I_B) + R_2 (I_A - I_C) = 0$$

$$(R_8 + R_{10} + R_2) I_A - R_{10} I_B - R_2 I_C = 0 \quad (1)$$

$$-R_{10} I_A + (R_{10} + R_9 + R_{11} + R_7) I_B$$

$$- 0 I_C - R_7 I_D = 0 \quad (2)$$

$$-V_2 + R_2 (I_C - I_A) + R_{12} (I_C - I_D) = 0$$

$$(R_2 + R_{12}) I_C - R_2 I_A - R_{12} I_D = V_2 \quad (3)$$

$$(R_{12} + R_7 + R_{13})I_D - 0I_A - R_7I_B - R_{12}I_C = 0 \quad \text{--- (4)}$$

EX]

$$-42 + 6I_1 + 3(I_1 - I_2) = 0$$

$$9I_1 - 3I_2 = 42 \quad \text{--- (1)}$$

$$-3I_1 + 7I_2 = 10 \quad \text{--- (2)}$$

$$6A, 4A$$

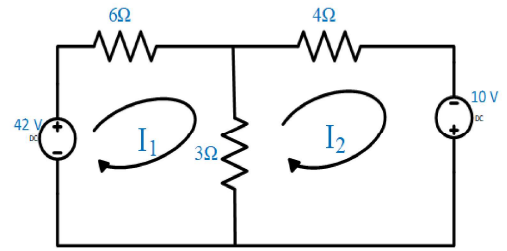


Figure 3: example 1 of mesh analysis

EX]

$$I_2 = -5A \quad \checkmark$$

$$-10 + 4I_1 + 6(I_1 - 5) = 0$$

$$I_1 = -2A \quad \checkmark$$

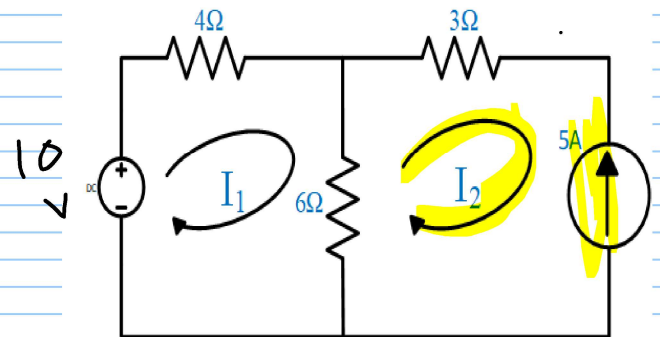


Figure 6: mesh with current source.