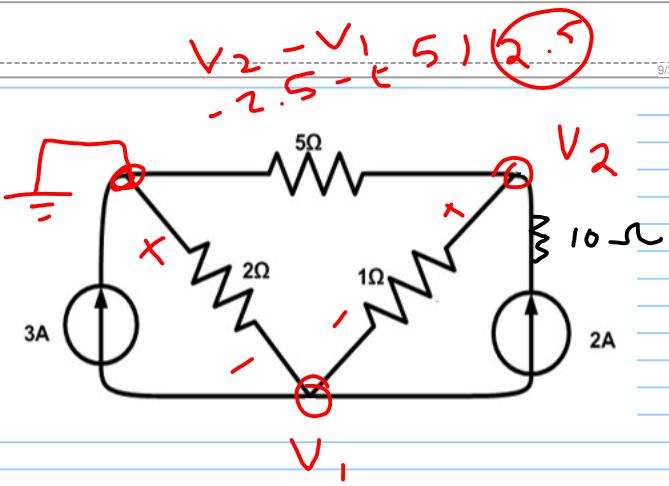


$$C_L = 4$$

Nodal method

@ node V_1

All currents are out
OR $\sum I_{out} = \sum I_{in}$



$$I_{out} = 3 + \frac{V_1}{2} + \frac{V_1 - V_2}{1} + 2 = 0$$

$$\sum I_{out} = 0 \quad \text{OR}$$

$$\sum I_{in} = 0$$

@ Node V_2

$$I_{out} = -2 + \frac{V_2 - V_1}{1} + \frac{V_2}{5} = 0$$

$$-V_1 + 1.2V_2 = 2 \quad \text{--- (2)}$$

$$V_1 = -5 \text{ V}$$


$$V_2 = -2.5 \text{ V}$$

@ node V_1

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_1 - \left(\frac{1}{R_1}\right)V_2 = I_{S1}$$

@ node V_2

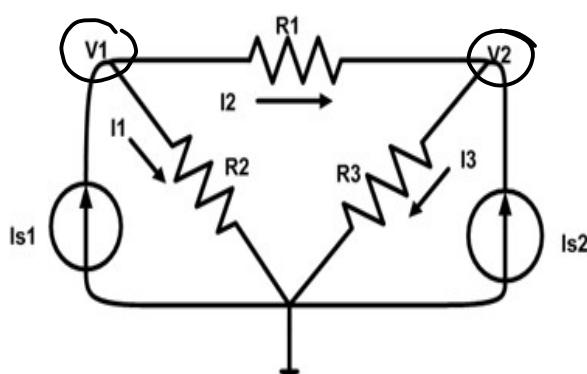
$$-\left(\frac{1}{R_1}\right)V_1 + \left(\frac{1}{R_1} + \frac{1}{R_3}\right)V_2 = I_{S2}$$



@ node 1

$$\sum I_{out} = \sum I_{in}$$

$$7V_1 - 3V_2 - 4V_3 = -11 \quad (1)$$

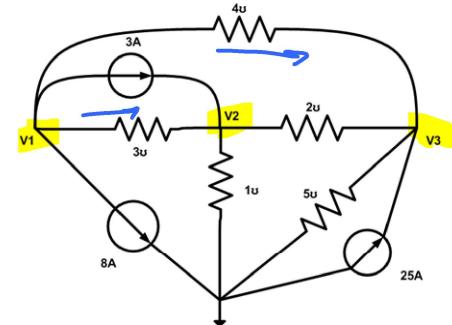

@ node V_2

$$3(V_1 - V_2) + 4(V_1 - V_3) + 3 + 8 = 0$$


$$-(3)V_1 + (3+2+1)V_2 - (2)V_3 = 3 \quad (2)$$

@ node V_3

$$-4V_1 - 2V_2 + (5+2+4)V_3 = 25 \quad (3)$$

$\left[\begin{matrix} E \\ X \end{matrix} \right]$

$$\sum I_{out} = 2 \text{ cmv}$$

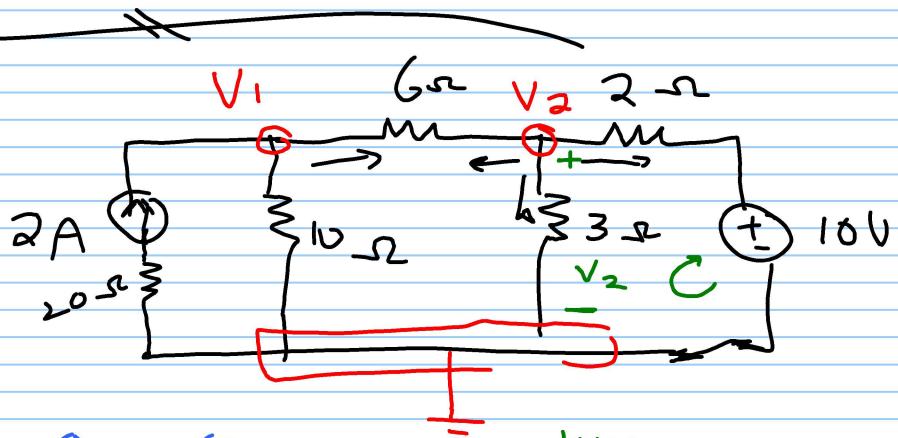

~~node 1~~

$$-2 + \frac{V_1}{10} + \frac{V_1 - V_2}{6} = 0 \quad (1)$$

KVL

~~node 2~~

$$\sum I_{out} = 0$$

$$-V_2 + 2I_X + 10 = 0$$


$$\frac{V_2 - V_1}{6} + \frac{V_2}{3} + \frac{V_2 - 10}{2} = 0 \quad (2)$$

$$I_X = \frac{V_2 - 10}{2}$$

$$V_1 = \underline{\hspace{2cm}}$$

$$V_2 = \underline{\hspace{2cm}} \quad \checkmark$$

EX

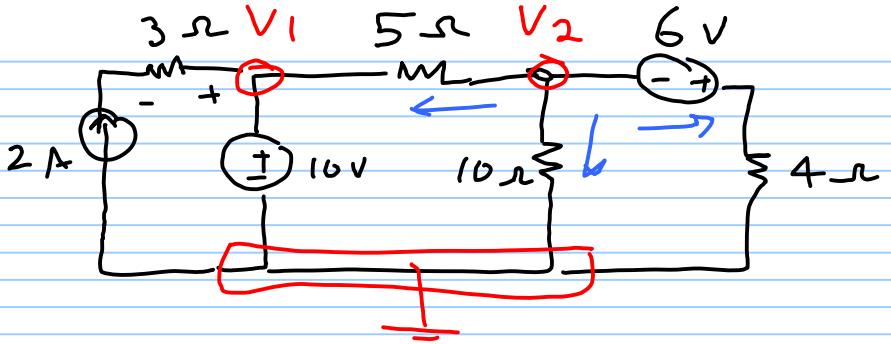

$$\text{A} \quad V \\ (-2) + (V_1 - 10) \times \cancel{\text{X}}$$

$$V_1 = 10 \text{ V} \quad \text{U10}$$


@ node V_2

$$\frac{V_2 - 10}{5} + \frac{V_2}{10} + \frac{V_2 + 6}{4} = 0$$

$$0.55V_2 = 2 - 1.5$$

$$V_2 = \frac{0.5}{0.55} = 0.909 \text{ Volt}$$

EX

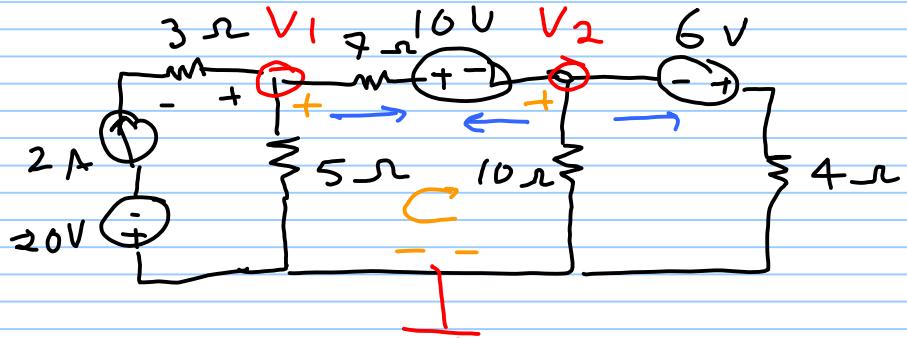

$$\sum I_{\text{out}} = 2 \text{ A}$$

@ node V_1

$$-2 + \frac{V_1}{5} + \frac{V_1 - 10 - V_2}{7} = 0 \quad \text{--- (1)}$$

$$-V_1 + 7I_x + 10 + V_2 = 0$$

@ node V_2

$$\frac{V_2 - V_1 + 10}{7} + \frac{V_2}{10} + \frac{V_2 + 6}{4} = 0 \quad \text{--- (2)}$$

Special Case


E-X

@ node V_1

$$-2 + \frac{V_1}{5} + I_x = 0$$

$$-2 + \frac{V_1}{5} + \frac{V_2 + 6}{10} + \frac{V_2 + 6}{4} = 0 \quad \text{--- (1) KVL}$$

$$V_1 - V_2 = 10$$

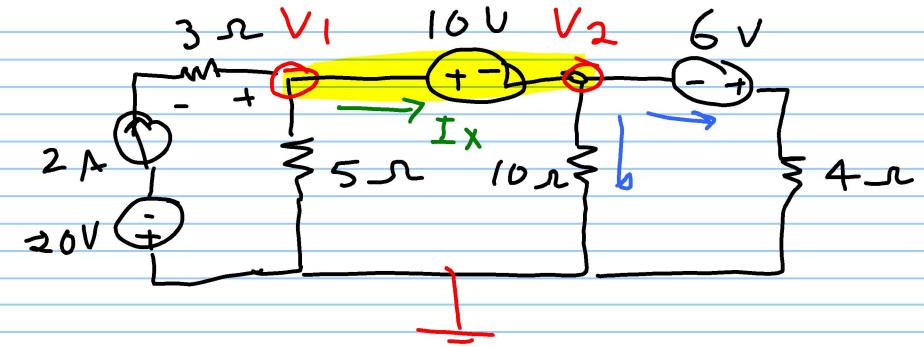

KVL @ super node

E-X

$$I_o = \frac{V_2}{3k} \quad \text{--- (1)}$$


@ node V_1

$$2I_o + \frac{V_1}{12k} + \frac{V_1 - V_2}{6k} = 0$$

$$2\left(\frac{V_2}{3k}\right) + \frac{V_1}{12k} + \frac{V_1 - V_2}{6k} = 0 \quad \text{--- (1)} \quad \text{↓↓↓}$$

@ node V_2
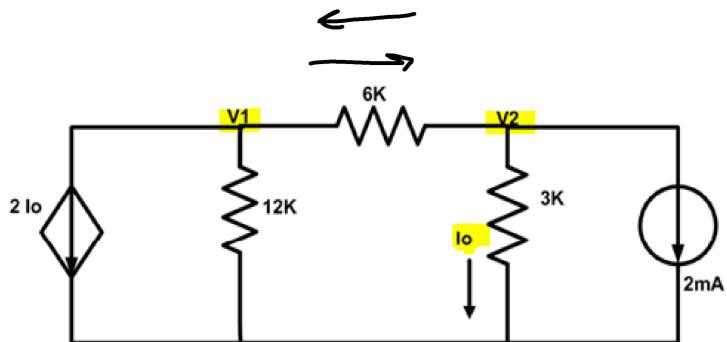
$$\frac{V_2 - V_1}{6k} + \frac{V_2}{3k} + 2mA = 0 \quad \text{--- (2)} \quad \text{↓↓↓}$$



$$V_1 = -\frac{24}{5} V \quad , \quad V_2 = \frac{12}{5} V$$


Mesh method

$$I_{R_2} = I_A$$

$$I_{R_2} = I_A - I_C$$


$$I_{R_{13}} = -I_D$$

$$I_{R_{10}} = I_B - I_A$$

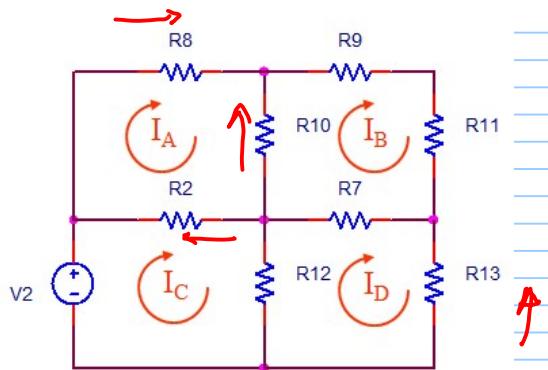

4 equations

4 unknowns I_A, I_B, I_C
X I_D

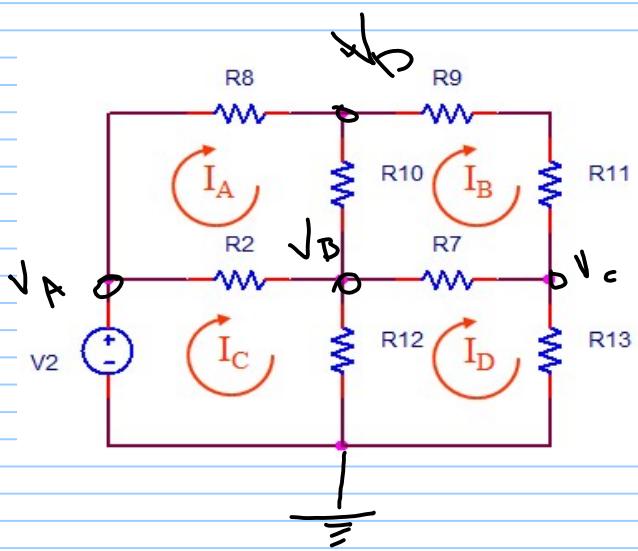


$V_A = V_2$

Nodal method

3 eqs

3 unknowns

$V_{B, C \& D}$

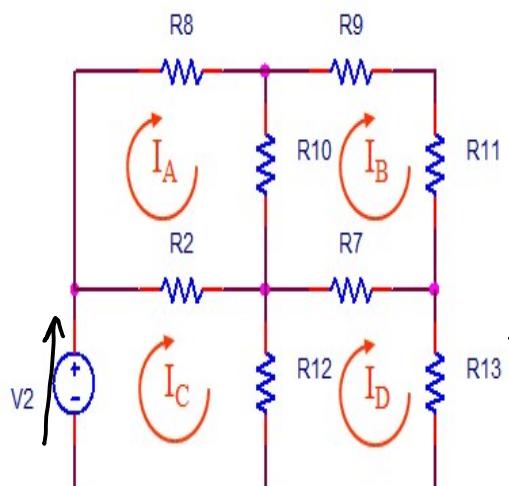

Mesh KV L

$$R_8 I_A + R_{10} (I_A - I_B) + R_2 (I_A - I_C) = 0$$

$$(R_8 + R_{10} + R_2) I_A - R_{10} I_B - R_2 I_C = 0 \quad (1)$$

$$- (R_{10}) I_A + (R_{10} + R_9 + R_{11} + R_7) I_B$$

$$- R_7 I_D = 0 \quad (2)$$

$$-V_2 + R_2 (I_C - I_A) + R_{12} (I_C - I_D) = 0$$

$$(R_2 + R_{12}) I_C - R_2 I_A - R_{12} I_D = V_2 \quad (3)$$

$$(R_{12} + R_7 + R_{13})I_D - 0I_A - R_7I_B - R_{12}I_C = 0 \quad \text{--- (4)}$$

Ex

$$-42 + 6I_1 + 3(I_1 - I_2) = 0$$

$$9I_1 - 3I_2 = 42 \quad \text{--- (1)}$$

$$-3I_1 + 7I_2 = 10 \quad \text{--- (2)}$$

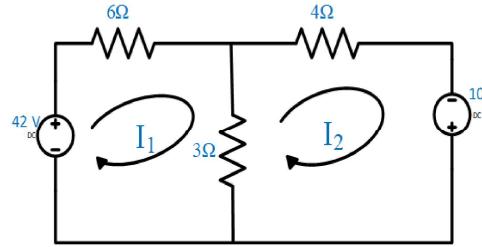


Figure 3: example 1 of mesh analysis

6A, 4A

special case 1 current source exists
only in one mesh

Ex

$$I_2 = -5A \quad \checkmark$$

$$-10 + 4I_1 + 6(I_1 - 5) = 0$$

$$I_1 = -2A \quad \checkmark$$

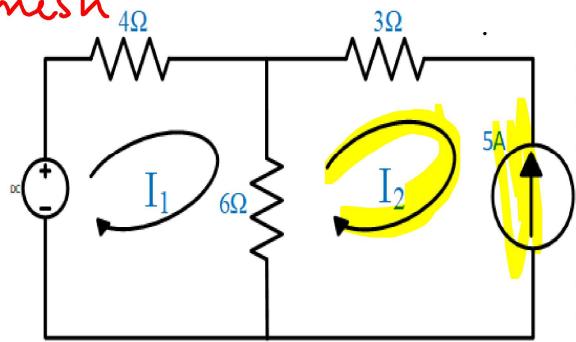


Figure 6: mesh with current source.

Case 2:

Current source exists between two meshes, a **Super mesh** is obtained

→ KVL for mesh (2)

$$(1+2+3)I_2 - (1)I_1 - (3)I_3 = 0 \quad \text{--- (1)}$$


→ constraint equation

$$I_1 - I_3 = 7 \quad \text{--- (2)}$$

→ Super mesh equation

$$-7 + (1)(I_1 - I_2) + (3)(I_3 - I_2) + (1)I_3 = 0$$
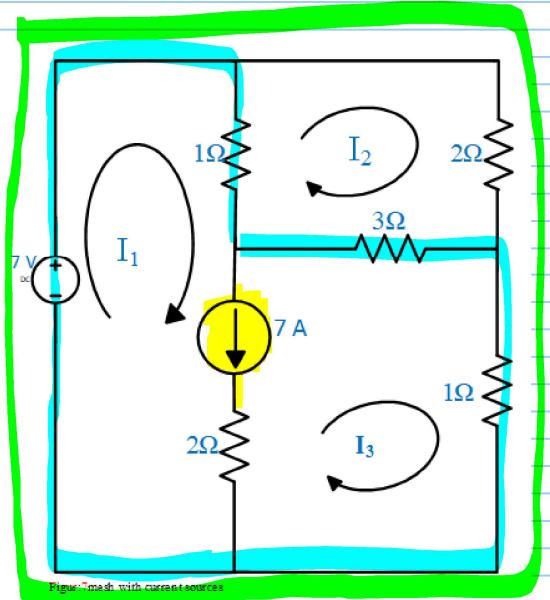
$$I_1 - 4I_2 + 4I_3 = 7 \quad \text{--- (3)}$$



$$I_3 = -7 \text{ A} \times$$

OR

$$-7 + 2I_2 + I_3 = 0 \quad \text{--- (3)*}$$

EX] Mesh Analysis with dependent sources

$$\rightarrow V_x = (3)(I_3 - I_2)$$

$$I_1 = 15 \text{ A} \quad \checkmark$$

→ constraint equation

$$\frac{V_x}{9} = I_3 - I_2$$

$$\frac{3}{9}(I_3 - I_2) = I_3 - 15$$

$$\frac{3}{9}I_2 + \frac{2}{3}I_3 = 15$$


$$I_2 + 2I_3 = 45 \quad \text{--- (1)}$$

$$(1)(I_2 - 15) + (2)I_2 + (3)(I_2 - I_3) = 0$$

$$6I_2 - 3I_3 = 15 \quad \text{--- (2)}$$

$$I_2 = 11 \text{ A} \quad \checkmark$$

$$I_3 = 17 \text{ A} \quad \checkmark$$

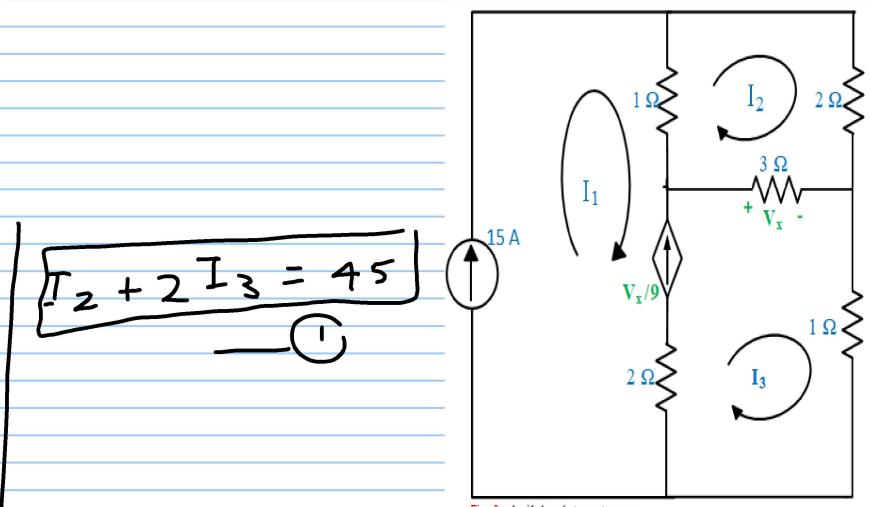


Node or mesh: How to choose?

- Use the one with fewer equations.
- Use the method you like best.


Slides

Source Transformation

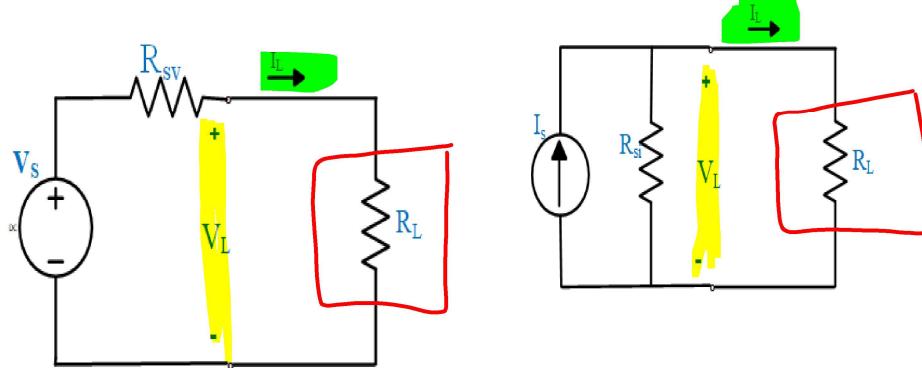

Two sources are equivalent, if each produces identical current and identical voltage in any load which is placed across its terminal.

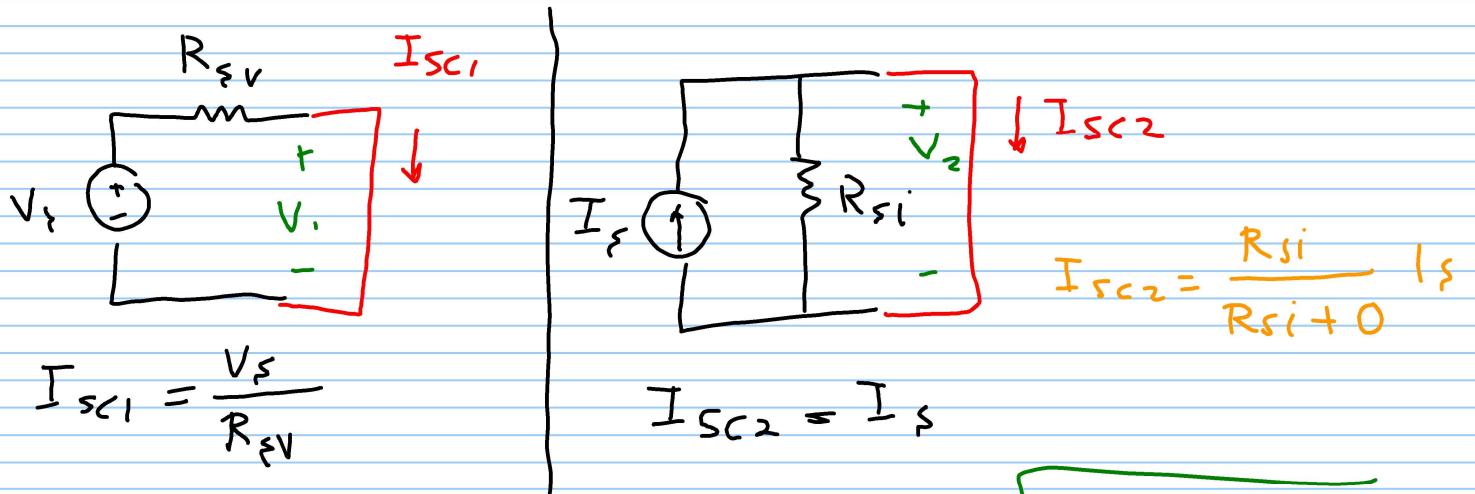→ let $R_L = \text{zero}$ (short circuit sc.)





for $I_{sc1} = I_{sc2}$

$$I_s = \frac{V_s}{R_{sv}}$$

$$V_1 = V_2 = 2 \text{ v}$$

→ let $R_L = \infty$ (open circuit)

$$I_1 = I_2 = \text{zero}$$

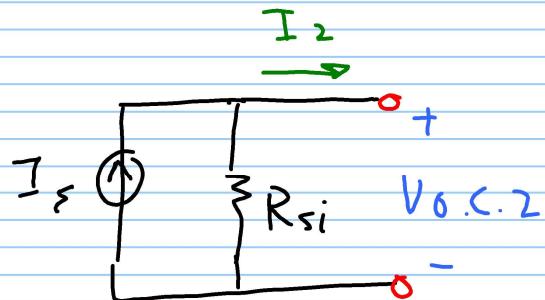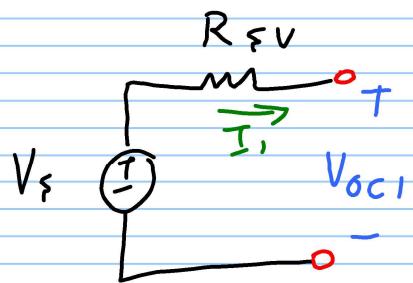

$$V_{oc1} = V_s$$

$$V_{oc2} = I_s R_{si}$$

$$\text{For } V_{oc1} = V_{oc2}$$




$$V_s = I_s R_{si}$$

$$\text{GR} \quad I_s = \frac{V_s}{R_{si}}$$

$$I_s = \frac{V_s}{R_{fv}}$$


$$\text{or } R_{si} = R_{fv}$$

E-X find V_o

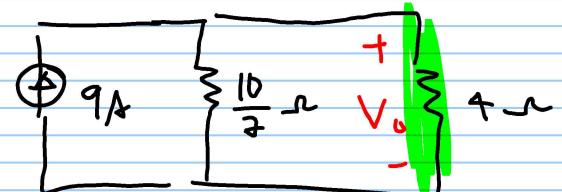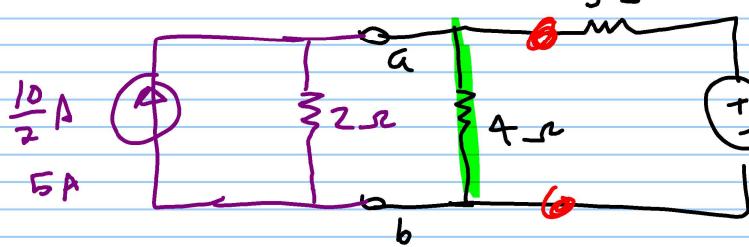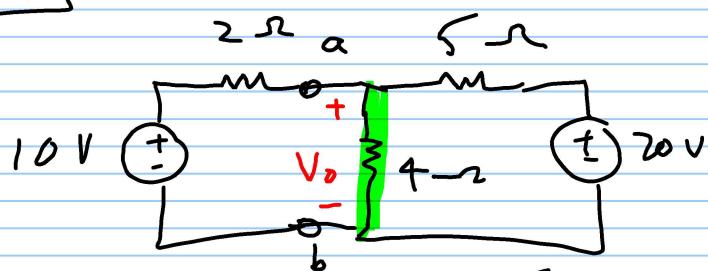

$$\left(\frac{10/7}{10/7 + 4} \cdot 9 \right) (4) = V_o$$

$$V_o = 9.47 \text{ Volt. } \checkmark$$

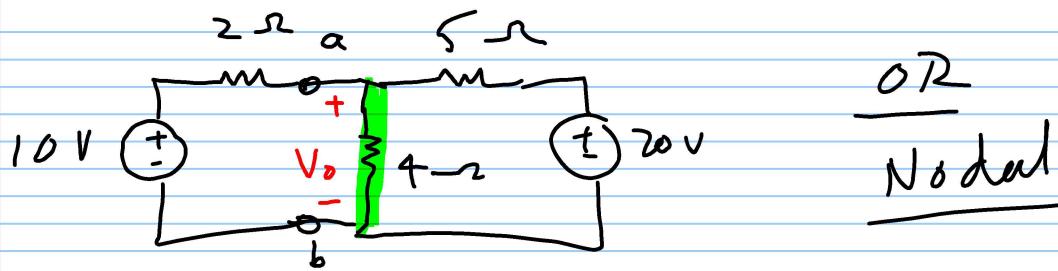

$$\frac{V_o - 10}{2} + \frac{V_o}{4} + \frac{V_o - 20}{5} = 0$$

$$V_o \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{5} \right) = \frac{10}{2} + \frac{20}{5}$$

$$V_o (0.95) = 9$$

$$V_o = 9.473 \text{ Volt.}$$